

Lecture 17

◆ Logistics

- HW5 due on Wednesday
- HW6 will be out on Wednesday, due in one week
- Lab6 this week

◆ Last lecture

- Memory storage elements
- State diagrams

◆ Today

- Registers
- Counters
- Start of Finite State Machine (FSM)

The “WHY” slide

◆ Registers and Counters

- Registers and counters are very simple yet powerful examples of how you can use the basic memory elements to conduct productive behavior. They are used everywhere in a computer.

◆ Finite State Machine


- This is what we have been waiting for in this class. Using combinational and sequential logics, now you can design a lot of clever digital logic circuits for functional products. We will learn different steps you take to go from word problems to logic circuits in the next few lectures.

Registers

- ◆ Group of storage elements read/written as a unit.
 - Store related values (e.g. a binary word)
- ◆ Collection of flip-flops with common control
 - Share clock, reset, set lines
- ◆ Example:
 - Storage registers
 - Shift registers
 - Counters


Storage registers

 - ◆ Basic storage registers uses flip flops
- ◆ Example: 4 bit storage register




Shift registers

 - ◆ Hold successively sampled input values
 - Delays values in time
 - Example: 4-bit shift register
 - ✦ Stores 4 input values in sequence




Shift-register applications

 - ◆ Parallel-to-serial conversion for signal transmission




 - ◆ Pattern recognition (circuit recognizes 1001)




Counters

 - ◆ Ring counter: Sequence is 1000, 0100, 0010, 0001
 - Assuming one of these patterns is the starting state




 - ◆ Johnson counter: Sequence is 1000, 1100, 1110, 1111, 0111, 0011, 0001, 0000




A binary counter

- ◆ Has logic between flip-flops

 


"States" for finite state machines are kept in the storage elements

 - ◆ Combinational logic and storage elements
 - Localized feedback loops
 - Choice of storage elements alters the logic





Finite-state machines (FSMs)

 - ◆ States: Possible storage-element values
- ◆ Transitions: Changes in state
 - Clock synchronizes the state changes
- ◆ Sequential logic
 - Sequences through a series of states
 - Based on inputs and present state



Drawing state diagrams

  - ◆ Show input values on transition arcs
- ◆ Show output values in state nodes



Counters revisited

- ◆ Great simple examples of state machines
 - Output is the counter's state
- ◆ Next state is well defined
 - Does not depend on input (no inputs)




FSM design procedure (using counters)

1. Draw a state diagram
2. Draw a state-transition table
3. Encode the next-state functions
 - Minimize the logic using k-maps
4. Implement the design

We will use a '3-bit up counter' as an example

1. Draw a state diagram

 

2. Draw a state-transition table

- ◆ Like a truth-table
 - State encoding is easy for counters → Use count value

	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

3. Encode the next state functions

- ◆ Assume D flip-flops as state elements

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

	C3			
N1	1	1	1	1
C1	0	0	0	0
	C2			

$$N1 := C1'$$

$$N2 := C1C2' + C1'C2$$

$$:= C1 \text{ xor } C2$$

$$N3 := C1C2C3' + C1'C3 + C2'C3$$

$$:= C1C2C3' + (C1' + C2')C3$$

$$:= (C1C2) \text{ xor } C3$$

	C3			
N2	0	1	1	0
C1	1	0	0	1
	C2			

	C3			
N3	0	0	1	1
C1	0	1	0	1
	C2			

4. Implement the design

- ◆ 3 flip-flops hold state
 - Counter is synchronously clocked
- ◆ Minimized logic computes next state

