
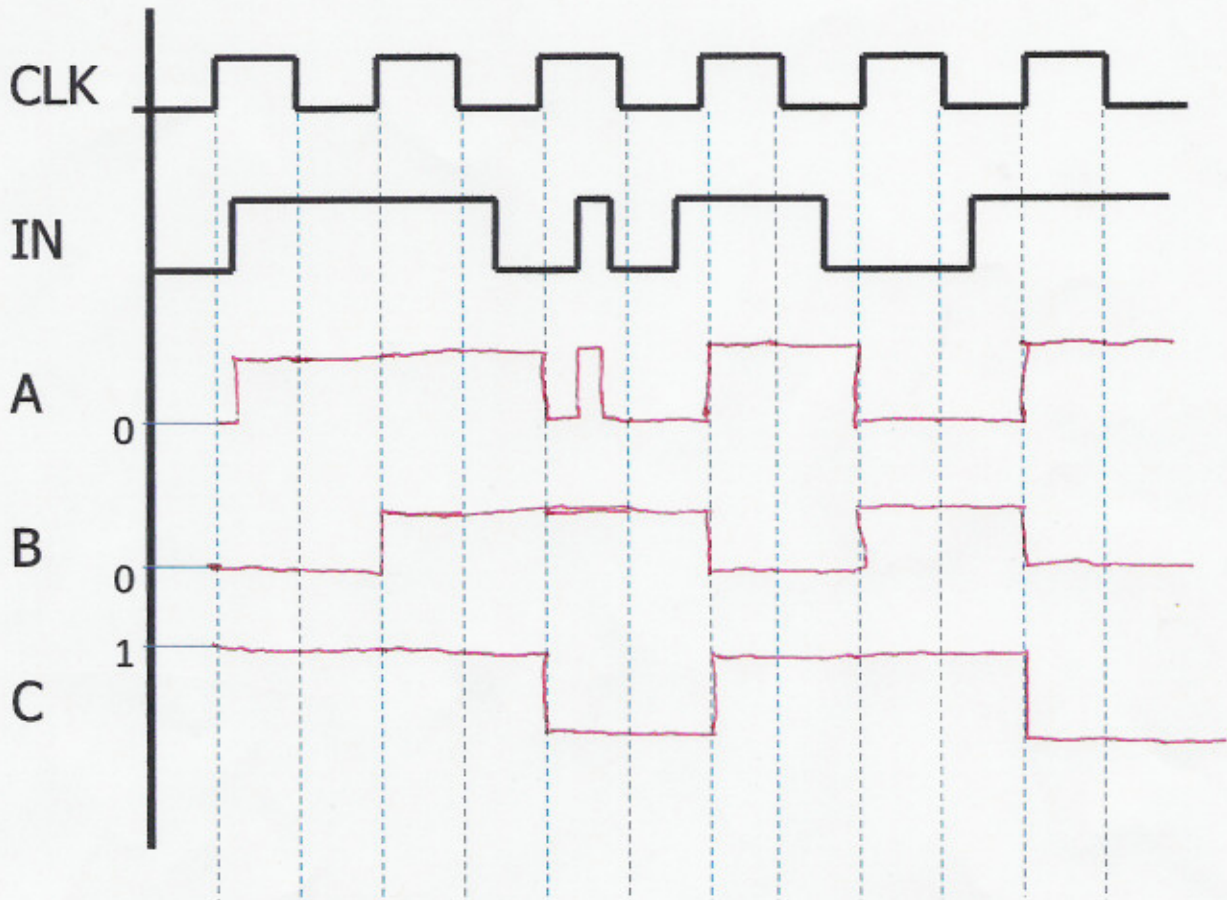


(20pts) Problem 1: Fill in the three empty lines of the timing diagram below.

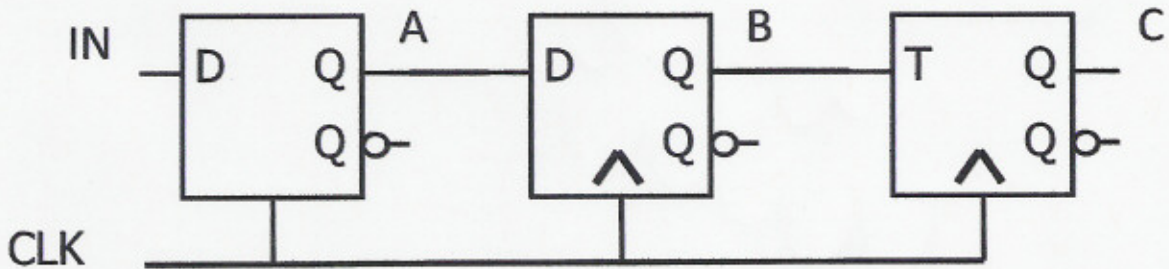A starts with 0, B starts with 0, C starts with 1. Assume each setup time, hold time, etc. is respected (so none of the inputs is changing too close to the clock edge).



-4 Didn't perceive propagation time


didn't treat latch, flipflop, toggle correctly.

-4 each

(40pts) Problem 2:



We have the following 4-state counter. 000 → 100 → 010 → 001 → 000 → ...

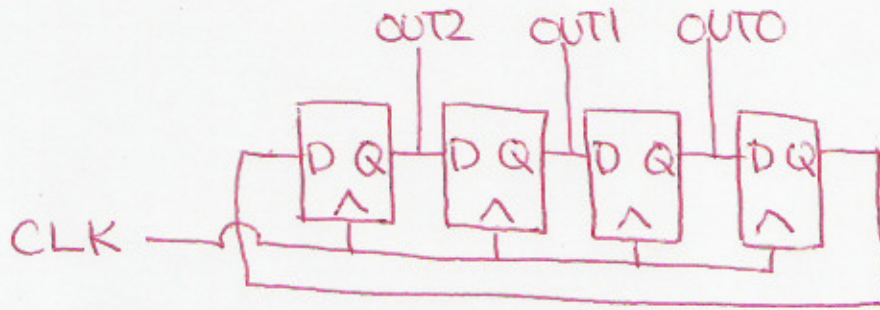- (a) (8 pts) Build this counter as a ring counter (like shift registers) with D flip flops. (hint: no need to take the four steps in this part of the question.) Label output bits as Out2, Out1, and Out0.



8

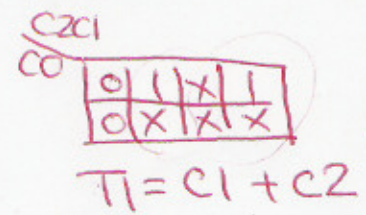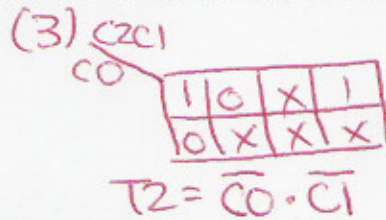
- (b) (32pts) Now, you want to build this counter using T flip flops. Don't worry about self-starting issues. Take the following four steps: (1) draw a state diagram, (2) fill in the state transition table (hint: don't forget to also fill in the inputs to T flip flops), (3) minimize the logic using k-maps, and (4) implement the design into a circuit.



8

(2)

c2	c1	c0	N2	N1	N0	T2	T1	T0
0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	1	0	1	1
0	1	1	X	X	X	X	X	X
1	0	0	0	1	0	1	1	0
1	0	1	X	X	X	X	X	X
1	1	0	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X

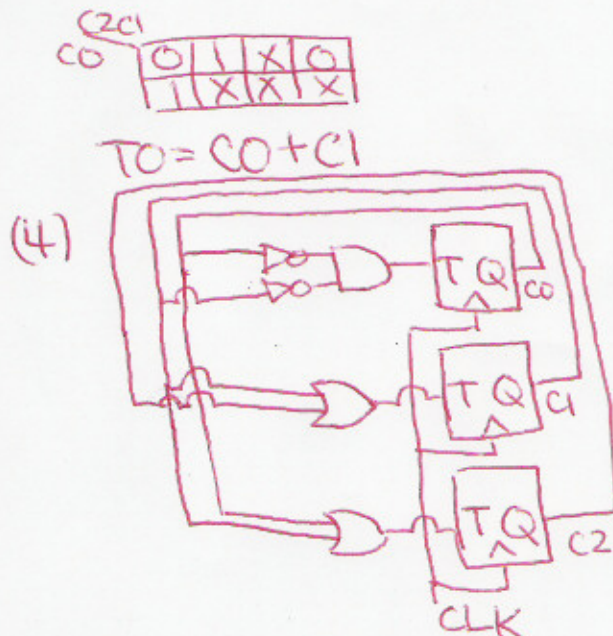


18

10 + 2 = 12

(40pts) Problem 3:

You are building a "MEALY" vending machine that sells flip-flops (the shoes!) using flip-flops. They cost 75 cents. The machine only takes quarters (Q). You can put in other coins (A), but they will all result in resetting the machine to 0 cents. The machine only has a single slot (can't put in more than one coin at a time), and after you get your flip-flops, putting in any coins (including quarters) results in resetting the machine to 0 cents.

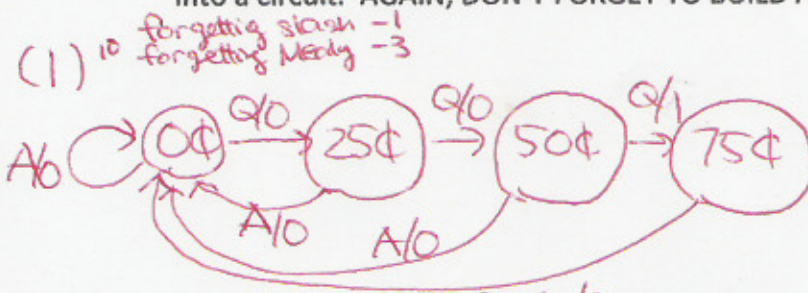Take the following 4 steps (steps 1 and 2 combine a couple of steps so you are basically going through all 6 steps). (1) Draw a state diagram (minimize), (2) fill in a state transition table (encode the states), (3) minimize the logic using k-maps, and (4) implement the design into a circuit. **AGAIN, DON'T FORGET TO BUILD A MEALY MACHINE!**



(2) ¹⁰ combining is not correct.

	C1 C0	A Q	N1	N0	OUT
0¢	0 0	0 0	0	0	0
	0 0	0 1	0	1	0
	0 0	1 0	X	X	X
	0 0	1 1	X	X	X
25¢	0 1	0 0	0	0	0
	0 1	0 1	0	0	0
	0 1	1 0	X	X	X
	0 1	1 1	X	X	X
50¢	1 0	0 0	0	0	0
	1 0	0 1	0	0	0
	1 0	1 0	X	X	X
	1 0	1 1	X	X	X
75¢	1 1	0 0	0	0	0
	1 1	0 1	0	0	0
	1 1	1 0	X	X	X
	1 1	1 1	X	X	X

(3) ¹⁰ C1 C0 A Q

	C1	
A Q	0	1
	0	1
A	X	X
	0	0

C1 C0 A Q

	C1	
A Q	0	1
	1	0
A	X	X
	0	0

$$N1 = Q \cdot \bar{C1} \cdot \bar{C0} + \bar{A} \cdot Q \cdot C1 + \bar{A} \cdot C1 \cdot \bar{C0}$$


$$N0 = Q \cdot C0 + A \cdot Q \cdot C0$$

C1 C0 A Q

	0	0	0	0
	0	0	0	1
A	X	X	X	X
	0	0	0	0

$$OUT = C1 \cdot \bar{C0} \cdot Q$$

(4) ¹⁰

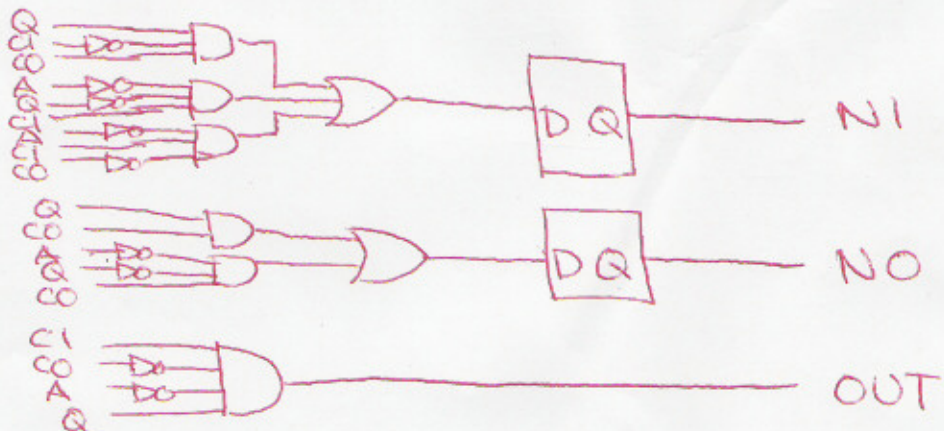

Problem - 2 grading

Part (a)

- (i) 4 FF version : Full credit
- 3 FF + NOR : Full credit

- 1 for unlabeled diagrams (FFs)
- 2 for unlabeled outputs
- 5 for non-functional designs



Part (b)

1. 4 points (~~1~~ partial credit)

2. ~~12~~ 12 points (-10 if no T-FF)

3. 8 points

4. ~~8~~ 8 points

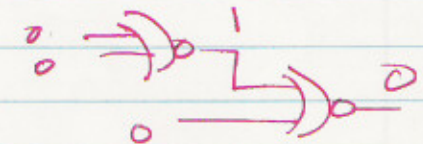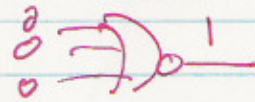

-8 if
D-FF

