 


Realizing Boolean logic

- Algebraic expressions to gates
- Mapping between different gates
- Discrete logic gate components (used in lab 1)

A simple example: 1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

$$Cout = A' B Cin + A B' Cin + A B Cin' + A B Cin$$

Apply the theorems to simplify expressions


- The theorems of Boolean algebra can simplify expressions
 - e.g., full adder's carry-out function

$$\begin{aligned}
 \text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \boxed{A B \text{Cin} + A B \text{Cin}} \\
 &= A' B \text{Cin} + A B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= (A' + A) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= (1) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \boxed{A B \text{Cin} + A B \text{Cin}} \\
 &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= B \text{Cin} + A (B' + B) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= B \text{Cin} + A (1) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\
 &= B \text{Cin} + A \text{Cin} + A B (\text{Cin}' + \text{Cin}) \\
 &= B \text{Cin} + A \text{Cin} + A B (1) \\
 &= B \text{Cin} + A \text{Cin} + A B
 \end{aligned}$$

adding extra terms
creates new factoring
opportunities

A simple example: 1-bit binary adder

 - Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out




A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1





$$\text{Cout} = B \text{Cin} + A \text{Cin} + A B$$

$$\begin{aligned}
 S &= A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin} \\
 &= A' (B' \text{Cin} + B \text{Cin}') + A (B' \text{Cin}' + B \text{Cin}) \\
 &= A' Z + A Z' \\
 &= A \text{ xor } Z = A \text{ xor } (B \text{ xor } \text{Cin})
 \end{aligned}$$

From Boolean expressions to logic gates

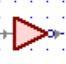
- NOT** X' \bar{X} $\sim X$ $X/$

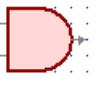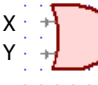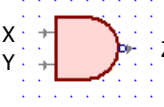
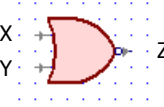
X	Y
0	1
1	0
- AND** $X \cdot Y$ XY $X \wedge Y$


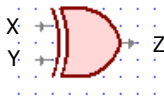
X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1
- OR** $X + Y$ $X \vee Y$


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1


From Boolean expressions to logic gates (cont'd)

- NAND**


X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0
- NOR**


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0
- XOR** $X \oplus Y$


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

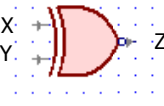$X \text{ xor } Y = X Y' + X' Y$
 X or Y but not both
 ("inequality", "difference")
- XNOR** $X = Y$


 
X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$X \text{ xnor } Y = X Y + X' Y'$
 X and Y are the same
 ("equality", "coincidence")

Full adder: Carry-out


Before Boolean minimization

$$\text{Cout} = A'BCin + AB' Cin + ABCin' + ABCin$$



After Boolean minimization


$$\text{Cout} = BCin + ACin + AB$$

 

Full adder: Sum


Before Boolean minimization
 
$$\text{Sum} = A'B'Cin + A'BCin' + AB'Cin' + ABCin$$




After Boolean minimization

$$\text{Sum} = (A \oplus B) \oplus Cin$$

 

Preview: A 2-bit ripple-carry adder

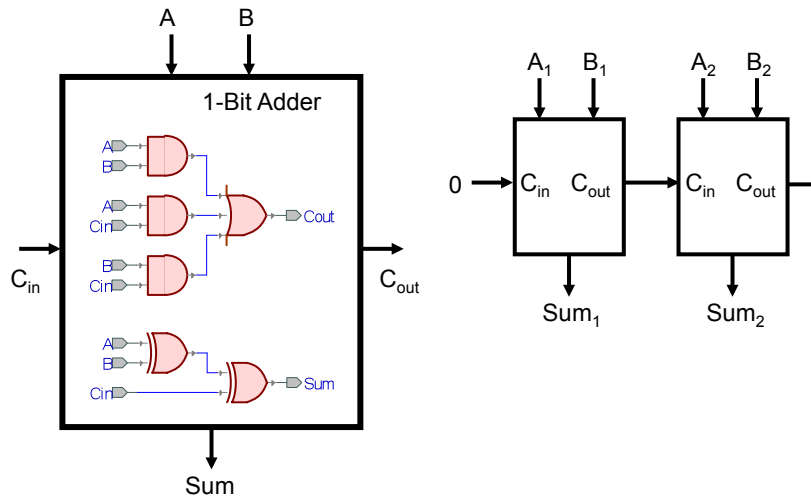

Spring 2010

CSE370 - III - Realizing Boolean Logic

9


Mapping truth tables to logic gates

- Given a truth table:
 1. Write the Boolean expression
 2. Minimize the Boolean expression
 3. Draw as gates
 4. Map to available gates

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

②

$$\begin{aligned}
 F &= A'BC' + A'BC + AB'C + ABC \\
 &= A'B(C'+C) + AC(B'+B) \\
 &= A'B + AC
 \end{aligned}$$

 


Spring 2010

CSE370 - III - Realizing Boolean Logic

10

Conversion between gate types

- Example: map AND/OR network to NOR-only network

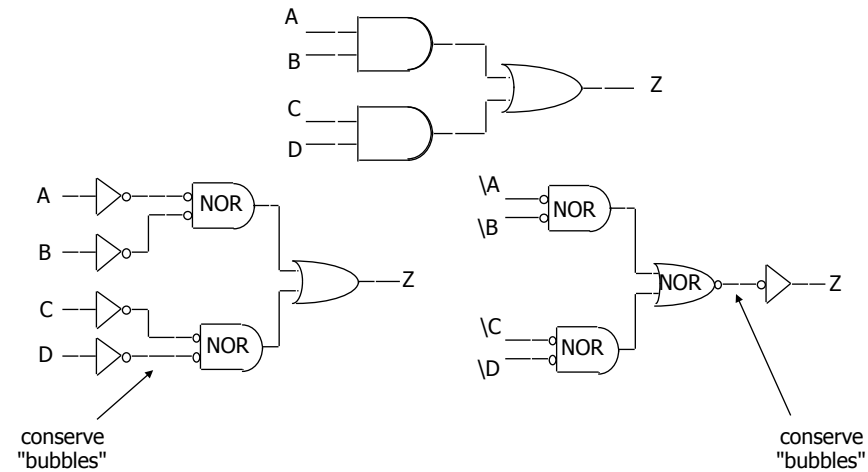


Spring 2010

CSE370 - III - Realizing Boolean Logic

11

Conversion between gate types (cont'd)

 - Example: verify equivalence of two forms




$$\begin{aligned}
 Z &= \{ [(A' + B') + (C' + D)']' \}' \\
 &= \{ (A' + B') \cdot (C' + D)' \}' \\
 &= (A' + B)' + (C' + D)' \\
 &= (A \cdot B) + (C \cdot D)
 \end{aligned}$$

Spring 2010

CSE370 - III - Realizing Boolean Logic

12

Activity: convert to NAND gates

 

Example: tally circuit (outputs # of 1s in inputs)

X1	X2	X3	T2	T1
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$\begin{aligned}
 T1 &= X1' X2' X3 + X1' X2 X3' \\
 &\quad + X1 X2' X3' + X1 X2 X3 \\
 &= (X1' X2' + X1 X2) X3 \\
 &\quad + (X1' X2 + X1 X2') X3' \\
 &= (X1 \text{ xor } X2)' X3 \\
 &\quad + (X1 \text{ xor } X2) X3' \\
 &= (X1 \text{ xor } X2) \text{ xor } X3
 \end{aligned}$$

$$\begin{aligned}
 T2 &= X1' X2 X3 + X1 X2' X3 \\
 &\quad + X1 X2 X3' + X1 X2 X3 \\
 &= X1' (X2 X3) + X1 (X2 + X3)
 \end{aligned}$$

From Boolean expressions to logic gates


- More than one way to map expressions to gates

 e.g., $Z = A' \cdot B' \cdot (C + D) = (A' \cdot (B' \cdot (C + D)))$




Waveform view of logic functions

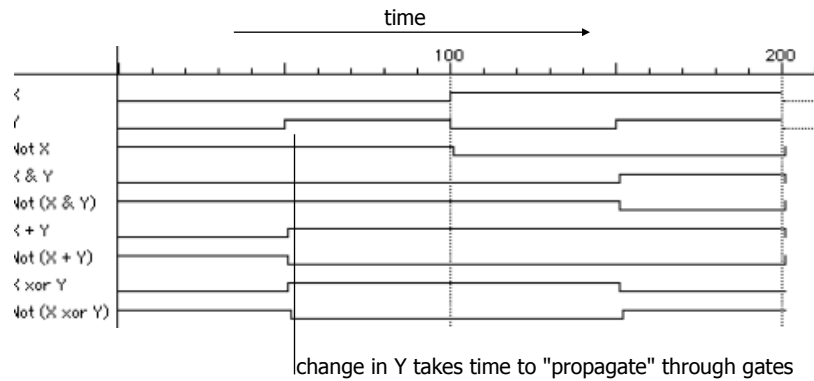- Just a sideways truth table
 - but note how edges don't line up exactly
 - it takes time for a gate to switch its output!



Choosing different realizations of a function

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

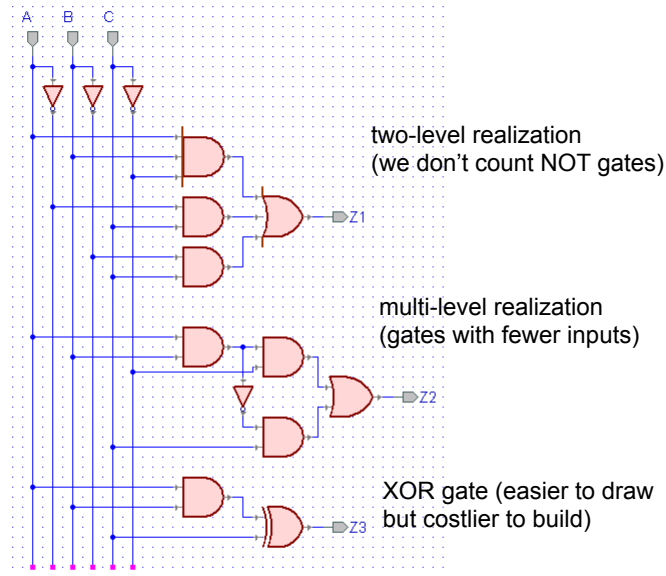


Spring 2010

CSE370 - III - Realizing Boolean Logic

17

Are all realizations equivalent?

- Under the same input stimuli, the three alternative implementations have almost the same waveform behavior
 - delays are different
 - glitches (hazards) may arise – these could be bad, it depends
 - variations due to differences in number of gate levels and structure
- The three implementations are functionally equivalent

 

Spring 2010

CSE370 - III - Realizing Boolean Logic

18

Which realization is best?

- Reduce number of inputs
 - literal: input variable (complemented or not)
 - can approximate cost of logic gate as 2 transistors per literal
 - why not count inverters?
 - fewer literals means less transistors
 - smaller circuits
 - fewer inputs implies faster gates
 - gates are smaller and thus also faster
 - fan-ins (# of gate inputs) are limited in some technologies
 - the programmable logic we'll be using later in the quarter
- Reduce number of gates
 - fewer gates (and the packages they come in) means smaller circuits
 - directly influences manufacturing costs

Which realization is best? (cont'd)

- Reduce number of levels of gates
 - fewer level of gates implies reduced signal propagation delays
 - minimum delay configuration typically requires more gates
 - wider, less deep circuits
- Hazards/glitches
 - one without hazards may be preferable/necessary
- How do we explore tradeoffs between increased circuit delay and size?
 - automated tools to generate different solutions
 - logic minimization: reduce number of gates and complexity
 - logic optimization: reduction while trading off against delay

Random logic gates


- Transistors quickly integrated into logic gates (1960s)
- Catalog of common gates (1970s)
 - Texas Instruments Logic Data Book – the yellow “bible”
 - all common packages listed and characterized (delays, power)
 - typical packages:
 - in 14-pin IC: 6-inverters, 4 NAND gates, 4 XOR gates
- Today, very few of these parts are still in use
- However, parts libraries exist for chip design
 - designers reuse already characterized logic gates on chips
 - same reasons as before
 - difference is that the parts don't exist in physical inventory – created as needed

Spring 2010


CSE370 - III - Realizing Boolean Logic

21


Some logic gate components

 


Quad 2-input NANDs – '00

 

Quad 2-input NORs – '02

 

6 inverters (NOTs) – '04

 

3 3-input NANDs – '10

Spring 2010

CSE370 - III - Realizing Boolean Logic

22