



CSE 370

Sample Final Exam Questions

1) Logic Minimization

CD \ AB	00	01	11	10
00				
01				
11				
10				

$$F = \sum m(0,6,7,8,9,11,15) + d(1,13)$$

1) Logic Minimization

	AB			
CD	00	01	11	10
00	1			1
01	d		d	1
11		1	1	1
10		1		

$$F = \sum m(0,6,7,8,9,11,15) + d(1,13)$$

1) Prime Implicants

	AB			
CD	00	01	11	10
00	1			1
01	d		d	1
11		1	1	1
10		1		

Note: Prime Implicant = largest box covering a 1

1) Essential PI's

	AB			
CD \	00	01	11	10
00	1			1
01	d		d	1
11		1	1	1
10		1		

Note: Essential PI = PI's that cover a 1 not covered by any other PI's

1) Logic Minimization


	AB			
CD \	00	01	11	10
00	1			1
01	d		d	1
11		1	1	1
10		1		

Prime Implicants: $B'C'$, AD , $A'BC$, BCD


Essential Prime Implicants: $B'C'$, AD , $A'BC$

Minimal Cover: $F = B'C' + AD + A'BC$

2a) Gates to Functions back into Gates

 


2a) Gates to Functions back into Gates

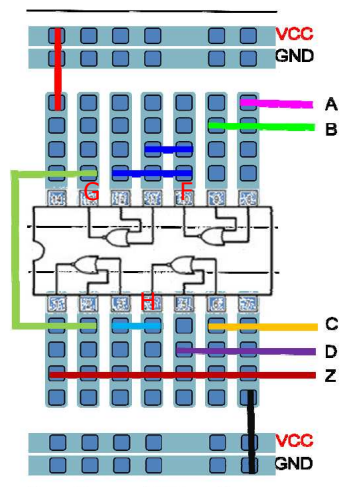

- $Z = \sim(H + G)$
- $Z = \sim H \& \sim G$
- $Z = \sim(\sim(C+D)) \& \sim(\sim(F+F))$
- $Z = (C+D) \& F$
- $Z = (C+D) \& \sim(A+B)$
- $Z = (C+D) \& \sim A \& \sim B$
- $Z = A'B'C + A'B'D$

2b) Gates to Functions back into Gates

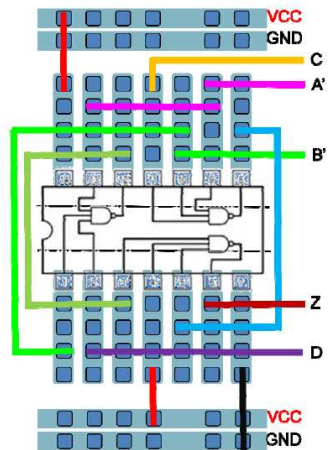

$$Z = A'B'C + A'B'D$$

Using deMorgan's Law...

$$Z = \sim(\sim(A'B'C) \& \sim(A'B'D))$$

2c) Gates to Functions back into Gates

- NOR Circuit
 - 3 gate delays @ 7ns
 - 21ns total
- NAND Circuit
 - 2 gate delays @ 9ns
 - 18ns total



3a) Multiplexer Logic

A	B	C	D	Z
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

$$Z = B'C + A'BD + AB'$$



3a) Multiplexer Logic

A	B	C	D	Z
0	0	0	0	
0	0	0	1	
0	0	1	0	1
0	0	1	1	1
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	1
1	0	1	1	1
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

$$Z = B'C + A'BD + AB'$$



3a) Multiplexer Logic

A	B	C	D	Z
0	0	0	0	
0	0	0	1	
0	0	1	0	1
0	0	1	1	1
0	1	0	0	
0	1	0	1	1
0	1	1	0	
0	1	1	1	1
1	0	0	0	
1	0	0	1	
1	0	1	0	1
1	0	1	1	1
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

$$Z = B'C + A'BD + AB'$$



3a) Multiplexer Logic

A	B	C	D	Z
0	0	0	0	
0	0	0	1	
0	0	1	0	1
0	0	1	1	1
0	1	0	0	
0	1	0	1	1
0	1	1	0	
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	


$$Z = B'C + A'BD + AB'$$

3a) Multiplexer Logic


A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$Z = B'C + A'BD + AB'$$

3b) Multiplexer Logic

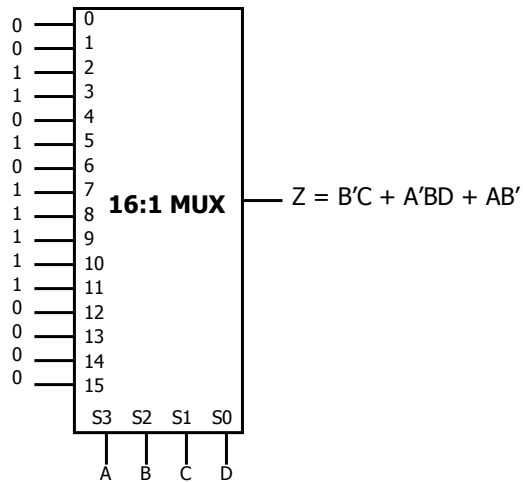

3c) Multiplexer Logic

 


Note: Requires no extra logic

4) Decoder Logic


A	B	C	W
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$W = (A \text{ xor } C) + B$$

4) Decoder Implementation

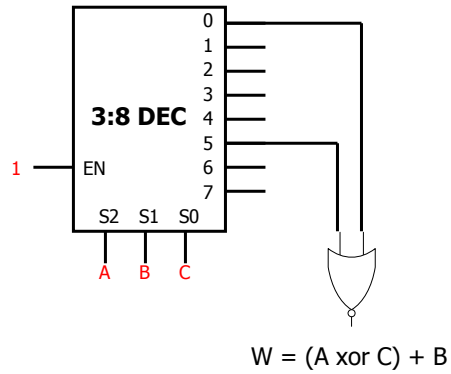

5) Programmable Logic

 


$Z = A'BCD' + ABC'D'$
 Note: 2 Common Prime Implicants can be used by X and Y
 $X = Z + A'B'CD + AB'C'D$
 $Y = Z + A'B'C + AB'C'$

5) Programmable Logic


$$Z = A'BCD' + ABC'D'$$

$$X = Z + A'B'CD + AB'C'D$$


$$Y = Z + A'B'C + AB'C'$$

 

6) Verilog to Circuit

 

7) Circuit to Verilog

 


7) Circuit to Verilog

```
module maxValue (DataOut, strobe, Data);  
    // Port Definitions  
    output reg [7:0] DataOut;  
    input strobe;  
    input [7:0] Data;  
  
    // Behavioral Statements for DataOut  
  
    // other required internal signals  
  
endmodule
```

7) Circuit to Verilog

```
// Behavioral Statements for DataOut
always @ (posedge clk) begin
    if (regEnable) DataOut <= Data;
    else DataOut <= DataOut;
end
```

7) Circuit to Verilog

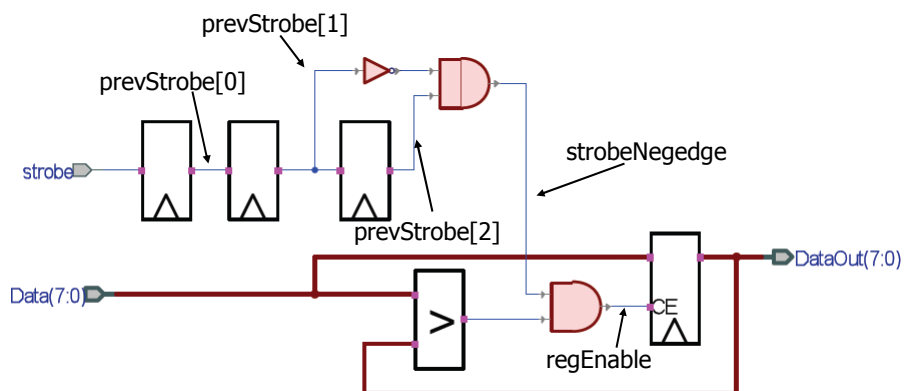



7) Circuit to Verilog

```
// other required internal signals
wire regEnable, strobeNegedge;
reg prevStrobe[2:0];

assign regEnable = (Data > DataOut) && strobeNegedge
assign strobeNegedge = prevStrobe[2] & ~prevStrobe[1];

always @ (posedge clk)
    prevStrobe = {prevStrobe[1:0],strobe};
```



8) Carry Look-ahead Adder

Recall:

$$\text{Sum} = A \text{ xor } B \text{ xor } C$$

$$\text{Cout} = AB + BC + AC$$

Rewrite Cout:

$$\text{Cout} = AB + C (A + B)$$

8) Carry Look-ahead Adder

A	B	P_{XOR}	P_{OR}
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	1

2 functions are only different if A and B are 1

8) Carry Look-ahead Adder

- Need carry out if A and B are 1
 - carry is generated in this case
 - don't need propagate to cover this case
 - these are then functionally equivalent
- Recall: $\text{Sum} = A \text{ xor } B \text{ xor } C$
 - $P = A + B$: have to calculate A xor B
 - $P = A \text{ xor } B$: reuse this to compute Sum
 - $P = A \text{ xor } B$ uses less logic

9) Verilog State Machine

S[1]	S[0]	A	B	NS[1]	NS[0]	out
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	1	0	0
0	1	1	0	0	1	0
0	1	1	1	1	0	0
1	0	0	0	1	1	0
1	0	0	1	1	1	0
1	0	1	0	1	0	1
1	0	1	1	1	0	0
1	1	0	0	0	0	0
1	1	0	1	1	1	0
1	1	1	0	0	0	0
1	1	1	1	0	0	0
1	1	1	1	1	1	1

9) Verilog State Machine

out S[1:0]

AB	00	01	11	10
00		1		
01	1			
11			1	
10				1

out = S[1]'S[0]'A'B +
S[1]'S[0]A'B' + S[1]S[0]'AB' +
S[1]S[0]AB

NS[1] S[1:0]

AB	00	01	11	10
00				1
01		1	1	1
11		1	1	1
10				1


NS[1]=S[0]B +
S[1]S[0]'

NS[0] S[1:0]

AB	00	01	11	10
00		1		1
01			1	1
11	1		1	
10	1	1		

NS[0] = S[1]'S[0]B' +
S[1]S[0]'A' + S[1]S[0]B
+ S[1]'S[0]A


9) Verilog State Machine

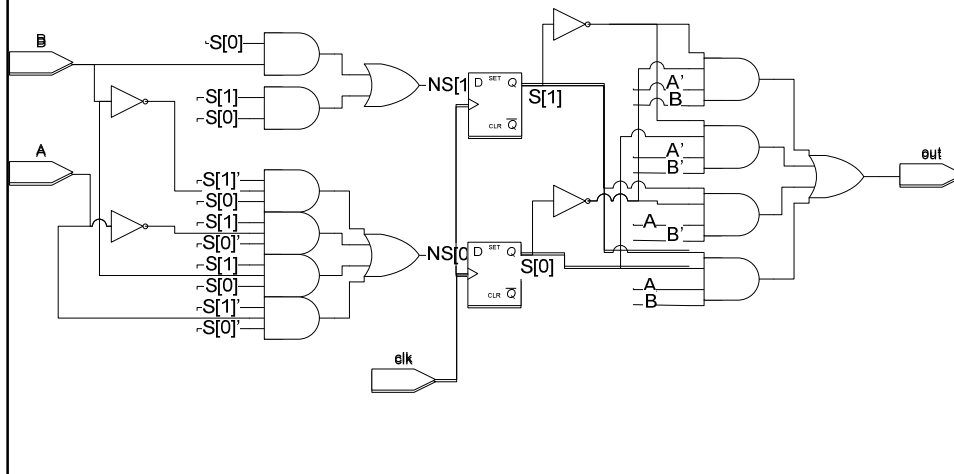


10) Design: Parallel to Serial

- Shift Register
 - Load parallel data
 - Shift out serial data
- Counter
 - How many bits have shifted out
- Controller
 - Shift Enable
 - Done Shifting


10a) Design: Parallel to Serial

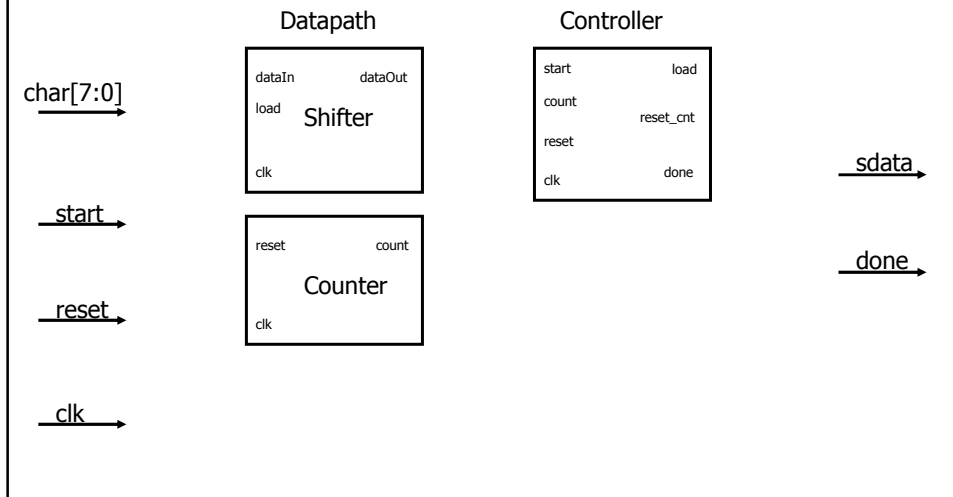


10b) Design: Parallel to Serial

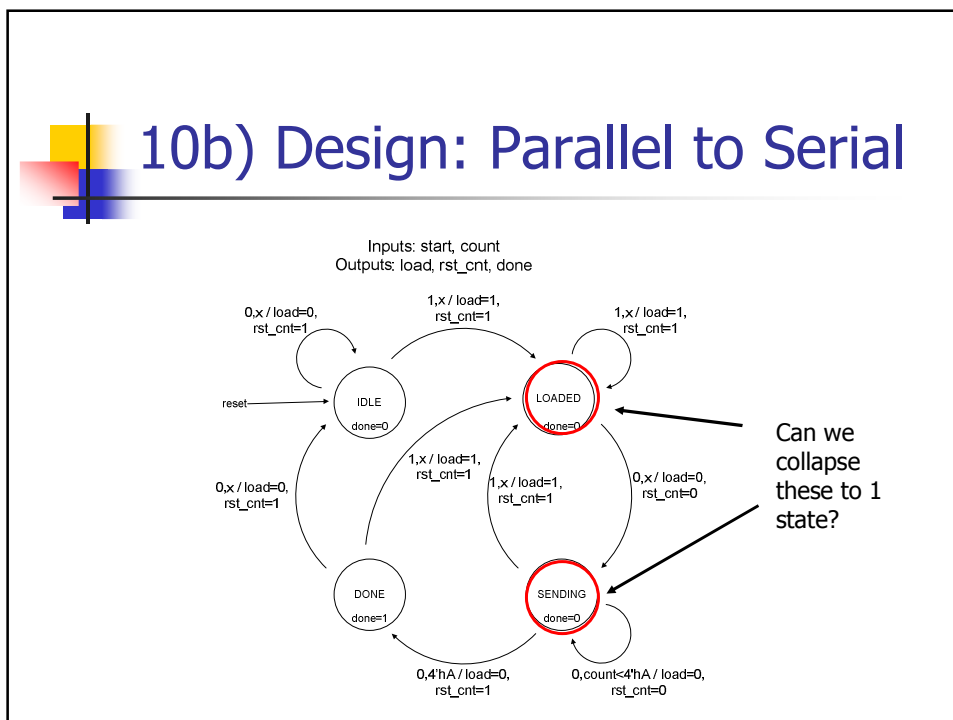

10b) Design: Parallel to Serial

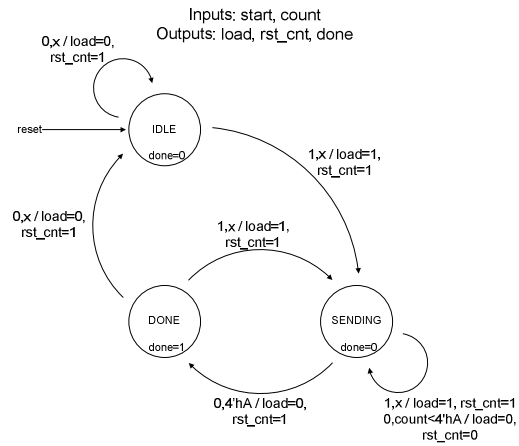

10c) Design: Parallel to Serial

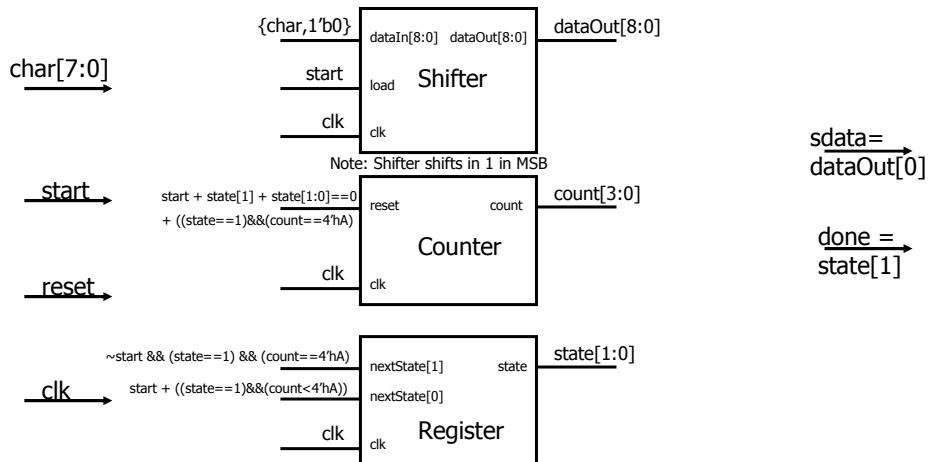



11) x370 CALL Instruction

- CALL Requirements
 - Load address into PC from instruction
 - Store PC+1 into RD



11) Implementation

- Load address into PC
 - inst[5:0] muxed to input of PC
 - Load PC asserted
- Store PC+1 into RD
 - PC muxed to A input of ALU
 - ALU inst set to INC
 - ALU output muxed to reg write data
 - Reg write address set to R_D



Final Notes

- Homework 9
 - Due today 5:30 pm
 - Can accept until Sunday 5:30 if dropbox doesn't close
- Final Exam
 - Wednesday June 9, 8:30-10:20
 - EEB 045
 - Don't be late!!!



Final Questions?
