

Specifying digital circuits

- Schematics (what we've done so far)
 - Structural description
 - Describe circuit as interconnected elements
 - Build complex circuits using hierarchy
 - Large circuits are unreadable
- Hardware description languages (HDLs)
 - Structural and behavioral descriptions
 - Not programming languages
 - They are **parallel languages tailored to digital design**
 - Synthesize code to produce a circuit from descriptions
 - Easier to modify designs
 - Details of realization take care of by compiler

Hardware description languages

- Describe hardware at varying levels of abstraction
- Structural description
 - textual replacement for schematic
 - hierarchical composition of modules from primitives
- Behavioral/functional description
 - describe what module does, not how
 - synthesis generates circuit for module
- Simulation semantics

Hardware description languages (HDLs)


- Abel (~1983)
 - Developed by Data-I/O
 - Targeted to two-level logic (most popular at the time)
 - Limited capabilities
- Verilog (~1985) – IEEE standard
 - Developed by Gateway (now part of Cadence)
 - **Syntax** similar to C
 - Supports both two-level and multi-level logic
 - Moved to public domain in 1990
- VHDL (~1987) – IEEE standard
 - DoD-sponsored
 - Supports both two-level and multi-level logic
 - **Syntax** similar to Ada
- SystemC (late 90s) – developing into IEEE standard
 - Support mixed hardware/software systems
 - Not as widely accepted yet

Verilog

- Supports structural and behavioral descriptions
- Structural
 - explicit structure of the circuit
 - e.g., each logic gate instantiated and connected to others
- Behavioral
 - program describes input/output behavior of circuit
 - many structural implementations could have same behavior
 - e.g., different implementation of one Boolean function
- We'll mostly be using behavioral Verilog in Aldec ActiveHDL
 - rely on schematic when we want structural descriptions

Simulation and synthesis

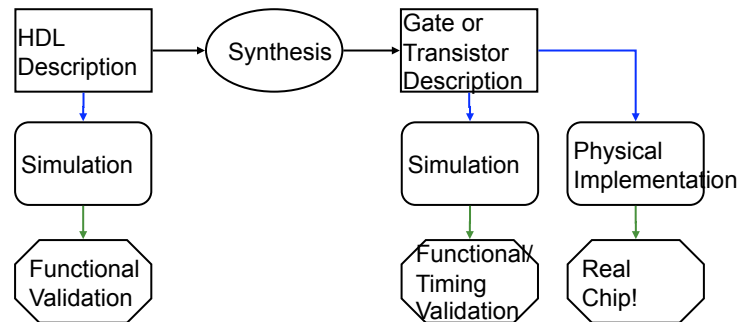- Simulation
 - “Execute” a design to verify correctness
- Synthesis
 - Generate a physical implementation from HDL code




Simulation and synthesis (con't)

- Simulation
 - Models what a circuit does
 - Ignore implementation options
 - Can include static timing
 - Allows you to test design options at an abstract level
- Synthesis
 - Converts your code to a netlist (circuit)
 - Can simulate synthesized design
 - Tools map your netlist to the hardware you'll be using
- Simulation and synthesis in the CSE curriculum
 - CSE370: Learn simulation
 - CSE467: Learn synthesis

Simulation

 - You provide an environment in which to test your circuit
 - Using non-circuit constructs
 - Active-HDL waveforms, read files, print
 - Using Verilog simulation code
 - A “test fixture”



Structural model

```
module xor_gate (out, a, b);
  input  a, b;
  output out;
  wire  abar, bbar, t1, t2;

  inverter invA (abar, a);
  inverter invB (bbar, b);
  and_gate and1 (t1, a, bbar);
  and_gate and2 (t2, b, abar);
  or_gate or1 (out, t1, t2);

endmodule
```

Simple behavioral model

- Continuous assignment

```
module xor_gate (out, a, b);  
  input      a, b;  
  output    out;  
  reg       out;  
  
  assign #6 out = a ^ b;  
  
endmodule
```

simulation register - keeps track of value of signal

NOTE: anything on the left side of an assignment must have a "reg" declaration

delay from input change to output change

Simple behavioral model

- always block

```
module xor_gate (out, a, b);  
  input      a, b;  
  output    out;  
  reg       out;  
  
  always @(a or b) begin  
    #6 out = a ^ b;  
  end  
  
endmodule
```

specifies when block is executed ie. triggered by which signals

NOTE: this "or" is not a Boolean OR, it just says: re-evaluate this expression whenever a or b change

Driving a simulation through a “testbench”

```
module testbench (x, y);  
  output      x, y;  
  reg [1:0]   cnt;  
  
  initial begin  
    cnt = 0;  
    repeat (4) begin  
      #10 cnt = cnt + 1;  
      $display ("@ time=%d, x=%b, y=%b, cnt=%b",  
        $time, x, y, cnt); end  
      #10 $finish;  
    end  
  
  assign x = cnt[1];  
  assign y = cnt[0];  
endmodule
```

2-bit vector


initial block executed only once at start of simulation

print to a console

directive to stop simulation


Complete simulation

 - Instantiate stimulus component and device to test in a schematic



Specifying circuits in Verilog

 - There are three major styles
 - Instances 'n wires
 - Continuous assignments
 - "always" blocks



"Structural"

```

wire E;
and g1(E,A,B);
not g2(Y,C);
or g3(X,E,Y);
    
```

"Behavioral"

```

wire E;
assign E = A & B;
assign Y = ~C;
assign X = E | Y;
    
```

```

reg E, X, Y;
always @ (A or B or C)
begin
    E = A & B;
    Y = ~C;
    X = E | Y;
end
    
```

Data types

- Values on a wire
 - 0, 1, x (unknown or conflict), z (tri-state or unconnected)
- Vectors
 - A[3:0] vector of 4 bits: A[3], A[2], A[1], A[0]
 - Unsigned integer value
 - Indices **must** be constants
 - Concatenating bits/vectors (curly brackets on left or right side)
 - e.g. sign-extend
 - B[7:0] = {A[3], A[3], A[3], A[3], A[3:0]};
 - {4{A[3]}, A[3:0]} = B[7:0];
 - Style: Use `a[7:0] = b[7:0] + c;`
 Not `a = b + c;`
 - Bad style but legal syntax: `C = &A[6:7];` // and of bits 6 and 7 of A

Data types that do not exist

- Structures
- Pointers
- Objects
- Recursive types
- (Remember, Verilog is not C or Java or Lisp or ...!)

Numbers

- Format: <sign><size><base format><number>
- 14
 - Decimal number
- $-4'b11$
 - 4-bit 2's complement binary of 0011 (is 1101)
- $12'b0000_0100_0110$
 - 12-bit binary number (_ is ignored, just used for readability)
- $3'h046$
 - 3-digit (12-bit) hexadecimal number
- Verilog values are unsigned
 - $C[4:0] = A[3:0] + B[3:0];$
 - if $A = 0110$ (6) and $B = 1010$ (-6), then $C = 10000$ (*not* 00000)
 - B is zero-padded, *not* sign-extended

Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
! ~ & ~& ~ ^ ~^ or ^~	logical negation negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{}	concatenation	Concatenation
{() }	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

>	greater than	Relational
>=	greater than or equal to	Relational
<	less than	Relational
<=	less than or equal to	Relational
==	logical equality	Equality
!=	logical inequality	Equality
===	case equality	Equality
!==	case inequality	Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional


Similar to C operators

Two abstraction mechanisms

- Modules
 - More structural
 - Heavily used in 370 and “real” Verilog code
- Functions
 - More behavioral
 - Used often in “real” Verilog
 - Just used in test fixtures in 370

Basic building blocks: Modules


- ❑ Instantiated into a design
 - Not called like a procedure/method
- ❑ Illegal to nest module definitions
- ❑ Modules execute in parallel
- ❑ Names are case sensitive
- ❑ // for comments
- ❑ Name can't begin with a number
- ❑ Use wires for connections
- ❑ *and*, *or*, *not* are keywords
- ❑ All keywords are lower case
- ❑ Gate declarations (and, or, etc.)
 - List outputs first (convention), then inputs

 

```
// first simple example
module smpl (X,Y,A,B,C);
  input A,B,C;
  output X,Y;
  wire E
  and g1 (E,A,B);
  not g2 (Y,C);
  or g3 (X,E,Y);
endmodule
```

Modules are circuit components

- ❑ Module has ports
 - External connections
 - A, B, C, X, Y in this example
- ❑ Port types
 - input (A, B, C)
 - output (X, Y)
 - inout (tri-state) – more later
- ❑ Use assign statements for Boolean expressions
 - and \Leftrightarrow &
 - or \Leftrightarrow |
 - not \Leftrightarrow ~

 


```
// previous example as a
// Boolean expression
module smpl2 (X,Y,A,B,C);
  input A,B,C;
  output X,Y;
  assign X = (A&B) | ~C;
  assign Y = ~C;
endmodule
```

Structural Verilog

```
module xor_gate (out,a,b);
  input  a,b;
  output out;
  wire  abar, bbar, t1, t2;
  not   inva (abar,a);
  not   invb (bbar,b);
  and   and1 (t1,abar,b);
  and   and2 (t2,bbar,a);
  or    or1 (out,t1,t2);
endmodule
```


8 basic gates (keywords):

and, or, nand, nor
buf, not, xor, xnor

 

Behavioral Verilog

 - Describe circuit behavior
 - Not implementation



```
module full_addr (Sum,Cout,A,B,Cin);
  input  A, B, Cin;
  output Sum, Cout;
  assign {Cout, Sum} = A + B + Cin;
endmodule
```

{Cout, Sum} is a concatenation of 2 1-bit signals

Behavioral 4-bit adder

```
module add4 (SUM, OVER, A, B);  
  input [3:0] A;  
  input [3:0] B;  
  output [3:0] SUM;  
  output OVER;  
  assign {OVER, SUM[3:0]} = A[3:0] + B[3:0];  
endmodule
```

“[3:0] A” is a 4-wire bus labeled “A”
Bit 3 is the MSB
Bit 0 is the LSB

Can also write “[0:3] A”
Bit 0 is the MSB
Bit 3 is the LSB

Buses are implicitly connected
If you write BUS[3:2], BUS[1:0]
They become part of BUS[3:0]

Continuous assignment

- Assignment is continuously evaluated
 - Corresponds to a logic gate
 - Assignments execute in parallel

```
assign A = X | (Y & ~Z);
```

Boolean operators
(~ for bit-wise negation)

```
assign B[3:0] = 4'b01XX;
```

bits can assume four values
(0, 1, X, Z)

```
assign C[15:0] = 4'h00ff;
```

variables can be n-bits wide
(MSB:LSB)

```
assign #3 {Cout, Sum[3:0]} = A[3:0] + B[3:0] + Cin;
```

Gate delay (used by simulator)

multiple assignment (concatenation)

arithmetic operator

Example: A comparator

```
module Compare1 (Equal, Alarger, Blarger, A, B);
  input      A, B;
  output     Equal, Alarger, Blarger;

  assign #5 Equal  = (A & B) |
                    (~A & ~B);
  assign #3 Alarger = (A & ~B);
  assign #3 Blarger = (~A & B);
endmodule
```

assign statement ordering doesn't matter because they execute in parallel

Comparator example (con't)

```
// Make a 4-bit comparator from 4 1-bit comparators

module Compare4 (Equal, Alarger, Blarger, A4, B4);
  input [3:0] A4, B4;
  output Equal, Alarger, Blarger;
  wire E0, E1, E2, E3, AL0, AL1, AL2, AL3, BL0, BL1, BL2, BL3;

  Compare1 cp0 (E0, AL0, BL0, A4[0], B4[0]);
  Compare1 cp1 (E1, AL1, BL1, A4[1], B4[1]);
  Compare1 cp2 (E2, AL2, BL2, A4[2], B4[2]);
  Compare1 cp3 (E3, AL3, BL3, A4[3], B4[3]);

  assign #5 Equal  = (E0 & E1 & E2 & E3);
  assign #10 Alarger = (AL3 | (AL2 & E3) |
                      (AL1 & E3 & E2) |
                      (AL0 & E3 & E2 & E1));
  assign #3 Blarger = (~Alarger & ~Equal);
endmodule
```

Sequential `assign` don't make any sense

```
assign A = X | (Y & ~Z);
```

```
assign B = W | A;
```

```
assign A = Y & Z;
```

“Reusing” a variable on the LHS in multiple assign statements is not allowed – they execute in parallel – indeterminate result

Always Blocks

```
reg A, B, C;
```

Variables that appear on the left hand side in an always block must be declared as “reg”s

```
always @ (W or X or Y or Z)
```

Sensitivity list

```
begin
  A = X | (Y & ~Z);
  B = W | A;
  A = Y & Z;
  if (A & B) begin
    B = Z;
    C = W | Y;
  end
end
```

Statements in an always block are executed in sequence

All variables must be assigned on every possible path through the code!!!
- otherwise, the simulator gets confused and decides it needs memory (the dreaded “inferred latch”) so it can remember the old value it had

Functions

- Use functions for complex combinational logic

```
module and_gate (out, in1, in2);
    input        in1, in2;
    output       out;

    assign out = myfunction(in1, in2);

    function myfunction;
        input in1, in2;
        begin
            myfunction = in1 & in2;
        end
    endfunction
endmodule
```

Benefit:

Compiler will fail if function does not generate a result

Verilog tips

- **Do not** write C-code
 - Think hardware, not algorithms
 - Verilog is **inherently parallel**
 - Compilers don't map algorithms to circuits well
- **Do** describe hardware circuits
 - First draw a dataflow diagram
 - Then start coding
- References
 - Tutorial and reference manual are found in ActiveHDL help
 - Wikipedia – search for “Verilog” – tutorials and external resources
 - Sutherland quick reference guide
 - “Starter’s Guide to Verilog 2001” by Michael Ciletti – copies for borrowing in hardware lab

Hardware description languages vs. programming languages

- Program structure
 - instantiation of multiple components of the same type
 - specify interconnections between modules via schematic
 - hierarchy of modules (only leaves can be HDL)
- Assignment
 - continuous assignment (logic always computes)
 - propagation delay (computation takes time)
 - timing of signals is important (when does computation have its effect)
- Data structures
 - size explicitly spelled out - no dynamic structures
 - no pointers
- Parallelism
 - hardware is naturally parallel (must support multiple threads)
 - assignments can occur in parallel (not just sequentially)

Hardware description languages and combinational logic

- Modules - specification of inputs, outputs, bidirectional, and internal signals
- Continuous assignment - a gate's output is a function of its inputs at all times (doesn't need to wait to be "called")
- Propagation delay- concept of time and delay in input affecting gate output
- Composition - connecting modules together with wires
- Hierarchy - modules encapsulate functional blocks