

## Hardware Description Languages and Sequential Logic

- Flip-flops
  - representation of clocks - timing of state changes
  - asynchronous vs. synchronous
- Shift registers
- Simple counters

## Flip-flop in Verilog

- Use always block's sensitivity list to wait for clock edge

```
module dff (clk, d, q);  
  
    input  clk, d;  
    output q;  
    reg   q;  
  
    always @(posedge clk)  
        q = d;  
  
endmodule
```

## More Flip-flops

- Synchronous/asynchronous reset/set
  - single thread that waits for the clock
  - three parallel threads – only one of which waits for the clock

### Synchronous

```
module dff (clk, s, r, d, q);
  input  clk, s, r, d;
  output q;
  reg    q;

  always @(posedge clk)
    if (r)      q = 1'b0;
    else if (s) q = 1'b1;
    else       q = d;
endmodule
```

### Asynchronous

```
module dff (clk, s, r, d, q);
  input  clk, s, r, d;
  output q;
  reg    q;

  always @(posedge r)
    q = 1'b0;
  always @(posedge s)
    q = 1'b1;
  always @(posedge clk)
    q = d;
endmodule
```

## Incorrect Flip-flop in Verilog

- Use always block's sensitivity list to wait for clock to change

```
module dff (clk, d, q);

  input  clk, d;
  output q;
  reg    q;

  always @(clk)
    q = d;

endmodule
```

Not correct! Q will change whenever the clock changes (both edges), not just on one edge.

## Blocking and Non-Blocking Assignments

- Blocking assignments ( $X=A$ )
  - completes the assignment before continuing on to next statement
- Non-blocking assignments ( $X<=A$ )
  - completes in zero time and doesn't change the value of the target until a blocking point (delay/wait) is encountered
- Example: swap

```
always @(posedge CLK)
begin
    temp = B;
    B = A;
    A = temp;
end
```

```
always @(posedge CLK)
begin
    A <= B;
    B <= A;
end
```

```
always @(posedge CLK)
begin
    A = A ^ B;
    B = A ^ B;
    A = A ^ B;
end
```

## Swap

- The following code executes incorrectly
  - One block executes first
  - Loses previous value of variable

```
always @(posedge CLK)
begin
    A = B;
end
```

```
always @(posedge CLK)
begin
    B = A;
end
```

- Non-blocking assignment fixes this
  - Both blocks are scheduled to execute by posedge CLK


```
always @(posedge CLK)
begin
    A <= B;
end
```

```
always @(posedge CLK)
begin
    B <= A;
end
```

 
## Register-transfer-level (RTL) Assignment

- Non-blocking assignment is also known as an RTL assignment
  - if used in an always block triggered by a clock edge
  - all flip-flops change together

```
// B,C,D all get the value of A
always @(posedge clk)
begin
    B = A;
    C = B;
    D = C;
end
```


 
```
// implements a shift register
always @(posedge clk)
begin
    B <= A;
    C <= B;
    D <= C;
end
```



## Shift register in Verilog

```
module shift_register (clk, in, out);

    input  clk;
    input  in;
    output [0:3] out;


    reg [0:3] out;

    initial begin
        out = 0; // out[0:3] = {0, 0, 0, 0};
    end

    always @(posedge clk) begin
        out = {in, out [0:2]};
    end

endmodule
```

## Activity

 

```
initial
begin
    A = 1'b0; B = 1'b0; C = 1'b0; D = 1'b0;
end

always @(posedge clk)
begin

end
```

## Binary Counter in Verilog

```
module binary_counter (clk, c8, c4, c2, c1);
```

```
    input    clk;
    output   c8, c4, c2, c1;

    reg [3:0] count;

    initial begin
        count = 0;
    end

    always @(posedge clk) begin
        count = count + 4'b0001;
    end

    assign c8 = count[3];
    assign c4 = count[2];
    assign c2 = count[1];
    assign c1 = count[0];
endmodule
```

add RCO

```
module binary_counter (clk, c8, c4, c2, c1, rco);
```

```
    input    clk;
    output   c8, c4, c2, c1, rco;

    reg [3:0] count;
    reg      rco;

    initial begin . . . end

    always @(posedge clk) begin . . . end

    assign c8 = count[3];
    assign c4 = count[2];
    assign c2 = count[1];
    assign c1 = count[0];
    assign rco = (count == 4b'1111);
endmodule
```

## 8-bit register of Lab 5


```
module register_8_bit (  
    input [7:0] D,  
    input clear,  
    input store,  
    output reg [7:0] Q );  
  
    // buttons are active low so look for  
    // negedges and test for !clear  
  
    always @(negedge clear, negedge store)  
        if (!clear) Q <= 8'b0000_0000;  
        else      Q <= D;  
  
endmodule
```

## Parallel versus serial execution

- **assign** statements are implicitly parallel
  - “=” means continuous assignment
  - Example

```
    assign E = A & D;  
    assign A = B & C;
```

     - **A** and **E** change if **B** changes
- **always** blocks execute in parallel
  - **always** @(posedge clock)
- Always block internals not necessarily parallel
  - “=” is a blocking assignment (sequential)
  - “<=” is a non-blocking assignment (parallel)



## Sequential logic summary

- Fundamental building blocks of circuits with state
  - latch and flip-flop
  - R-S latch, R-S master/slave, D master/slave, edge-triggered D flip-flop
- Timing methodologies
  - use of clocks
  - cascaded FFs work because  $T_{prop} > T_{hold}$
  - beware of clock skew
  - $period > T_{propFF} + T_{propCL} + T_{setup}$
- Basic registers
  - shift registers
  - counters
- Hardware description languages and sequential logic
  - always (@ posedge clk)
  - blocking and non-blocking assignments

## Verilog review/style

## Variables in Verilog

- wire
  - Connects components together
- reg
  - Saves a value
    - Part of a behavioral description
  - Does **NOT** necessarily become a register when you synthesize
    - May become a wire
- Important rule
  - Declare a variable as reg if it is a target of an assignment statement inside an always block
    - Continuous assign doesn't count

## Always block

- A construct that describes a circuit's behavior
  - begin/end groups multiple statements within an always block
  - Can contain if, for, while, case
  - Triggers at the specified conditions in sensitivity list: @(...)

```
module register(Q, D, clock);
  input  D, clock;
  output Q;
  reg    Q;

  always @(posedge clock) begin
    Q <= D;
  end
endmodule
```

## Sequential Verilog

- Sequential circuits: Registers & combinational logic
  - Use positive edge-triggered registers
  - Avoid latches and negative edge-triggered registers
- Register is triggered by “posedge clk”

```
module register(Q, D, clock);  
  input  D, clock;  
  output Q;  
  reg    Q;  
  
  always @(posedge clock) begin  
    Q <= D;  
  end  
endmodule
```

Example: a D flip-flop

Register: in this case, holds value of *Q* between clock edges - We want this register to be SYNTHESIZED

## Always example

```
module and_gate(out, in1, in2);  
  input  in1, in2;  
  output out;  
  reg    out;  
  
  always @(in1 or in2) begin  
    out = in1 & in2;  
  end  
endmodule
```

Holds assignment in always block – but we do NOT want a SYNTHESIZED register

The compiler will not synthesize this code to a register, because *out* changes whenever *in1* or *in2* change. Could simply write  

```
wire out, in1, in2;  
and (out, in1, in2);
```

specifies when block is executed i.e. triggered by changes in *in1* or *in2*

## Incomplete sensitivity list or incomplete assignment

- What if you omit an input trigger (e.g. *in2*)
  - Compiler will insert a latch to hold the state
  - Becomes a sequential circuit — **NOT** what you want

```
module and_gate (out, in1, in2);
  input          in1, in2;
  output         out;
  reg            out;

  always @(in1) begin
    out = in1 & in2;
  end
endmodule
```

Real state!! Holds *out* because *in2* isn't specified in *always* sensitivity list – a register is synthesized that we DO NOT want

### 2 rules:

- 1) Include all inputs in the trigger list
- 2) Use complete assignments
  - ⇒ Every path must lead to an assignment for *out*
  - ⇒ Otherwise *out* needs a state element

## Assignments

- Be careful with **always** assignments
  - Which of these statements generate state?

```
always @(c or x) begin
  if (c) begin
    value = x;
  end
  y = value;
end
```

```
always @(c or x) begin
  value = x;
  if (c) begin
    value = 0;
  end
  y = value;
end
```

```
always @(c or x) begin
  if (c)
    value = 0;
  else if (x)
    value = 1;
end
```

```
always @(a or b)
  f = a & b & c;
end
```

### 2 rules:

- 1) Include all inputs in the sensitivity list
- 2) Use complete assignments
  - ⇒ Every path must lead to an assignment for *out*
  - ⇒ Otherwise *out* gets a state element

## if

- Same as Java/C if statement

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel;    // 2-bit control signal
input A, B, C, D;
output Y;
reg Y;             // target of assignment

always @(sel or A or B or C or D)
    if (sel == 2'b00) Y = A;
    else if (sel == 2'b01) Y = B;
    else if (sel == 2'b10) Y = C;
    else if (sel == 2'b11) Y = D;
endmodule
```

⇒ Single *if* statements synthesize to multiplexers  
⇒ Nested *if/else* statements usually synthesize to logic

## if (another way)

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel;    // 2-bit control signal
input A, B, C, D;
output Y;
reg Y;             // target of assignment

always @(sel or A or B or C or D)
    if (sel[0] == 0)
        if (sel[1] == 0) Y = A;
        else Y = B;
    else
        if (sel[1] == 0) Y = C;
        else Y = D;
endmodule
```

## case

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel; // 2-bit control signal
input A, B, C, D;
output Y;
reg Y; // target of assignment

always @(sel or A or B or C or D)
  case (sel)
    2'b00: Y = A;
    2'b01: Y = B;
    2'b10: Y = C;
    2'b11: Y = D;
  endcase
endmodule
```

case executes sequentially  
⇒ First match executes  
⇒ Don't need to break out of case  
case statements synthesize to muxes

## default case

```
// Simple binary encoder (input is 1-hot) - comb. logic
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment

always @(A)
  case (A)
    8'b00000001: Y = 0;
    8'b00000010: Y = 1;
    8'b00000100: Y = 2;
    8'b00001000: Y = 3;
    8'b00010000: Y = 4;
    8'b00100000: Y = 5;
    8'b01000000: Y = 6;
    8'b10000000: Y = 7;
    default: Y = 3'bx; // Don't care about other cases
  endcase
endmodule
```

If you omit the *default*,  
the compiler will create  
a latch for Y – not good

## case executes sequentially

```
// Priority encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg    [2:0] Y;           // target of assignment

always @(A)
  case (1'b1)
    A[0]: Y = 0;
    A[1]: Y = 1;
    A[2]: Y = 2;
    A[3]: Y = 3;
    A[4]: Y = 4;
    A[5]: Y = 5;
    A[6]: Y = 6;
    A[7]: Y = 7;
    default: Y = 3'bx; // Don't care when input is all 0's
  endcase
endmodule
```

Case statements execute sequentially  
⇒ Take the first alternative that matches

## for

```
// simple encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg    [2:0] Y;           // target of assignment
integer i;                // Temporary variables for program
reg    [7:0] test;

always @(A) begin
  test = 8b'00000001;
  Y = 3'bx;
  for (i = 0; i < 8; i = i + 1) begin
    if (A == test) Y = i;
    test = test << 1; // Shift left, pad with 0s
  end
end
endmodule
```

for statements synthesize as  
cascaded combinational logic  
⇒ Verilog unrolls the loop

## Verilog while/repeat/forever

- while (expression) statement
  - execute statement while expression is true
- repeat (expression) statement
  - execute statement a fixed number of times
- forever statement
  - execute statement forever

## Some simple synthesis examples

