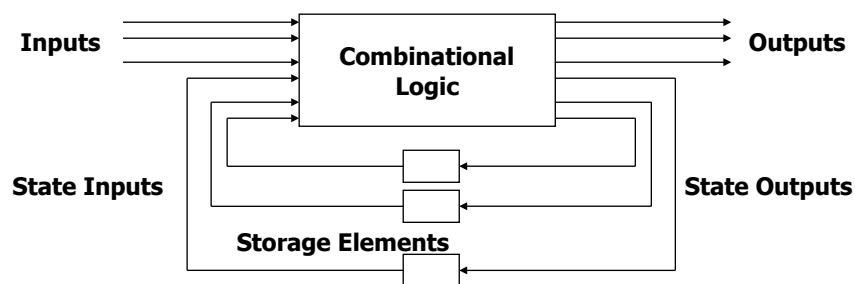


## Finite State Machines

- Finite State Machines (FSMs)
  - general models for representing sequential circuits
  - two principal types based on output behavior (Moore and Mealy)
- Basic sequential circuits revisited and cast as FSMs
  - shift registers
  - counters
- Design procedure for FSMs
  - state diagrams
  - state transition table
  - next state functions
  - potential optimizations
- Hardware description languages


## Abstraction of state elements

- Divide circuit into combinational logic and state
- Localize the feedback loops and make it easy to break cycles
- Implementation of storage elements leads to various forms of sequential logic



 
## Forms of sequential logic

- Asynchronous sequential logic – state changes occur whenever state inputs change (seq. elements may be simple wires or delay elements)
- Synchronous sequential logic – state changes occur in lock step across all storage elements (using a periodic waveform to trigger FFs)



 
## Finite state machine representations

- States: determined by possible values in sequential storage elements
- Transitions: change of state
- Clock: controls when state can change by controlling storage elements
- Sequential logic
  - transitions through a series of states
  - which transitions are taken depends on values of input signals
  - clock period defines elements of input sequence



 
## Example finite state machine diagram

- 5 states
- 8 other transitions between states
  - 6 conditioned by input
  - 1 self-transition (on 0 from 001 to 001)
  - 2 independent of input (to/from 111)
- 1 reset transition (from all states) to state 100
  - represents 5 transitions (from each state to 100), one a self-arc
  - simplifies condition on other transitions –all would include **AND reset'** )
  - short-hand – rather than drawing a transition arc from each state


 
## Counters are simple finite state machines



- Counters
  - proceed through well-defined sequence of states (if enabled)
- Many types of counters: binary, BCD, Gray-code, etc....
  - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
  - 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...



## Can any sequential system be represented with a state diagram?
  
### ■ Shift register


- input value shown on transition arcs
- output values shown within state node



## How do we turn a state diagram into logic?
 
### ■ Counter

- 3 flip-flops to hold state
- logic to compute next state
  - wait long enough for combinational logic to compute new value
  - though waiting too long is a waste of time




## FSM design procedure

- We started with counters
  - simple because the output is just its state
  - simple because there is no input used to choose next state
- State diagram to state transition table
  - tabular form of state diagram
  - like a truth-table
- State encoding
  - decide on representation of states
  - for counters it is simple: just its value
- Implementation
  - flip-flop for each state bit
  - combinational logic based on encoding
 
## FSM design procedure: state diagram to encoded state transition table

- Tabular form of state diagram
- Like a truth-table (specify output for all input combinations)
- Encoding of states: easy for counters – just use value



	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

## Implementation




- D flip-flop for each state bit
- Combinational logic based on state encoding

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Verilog notation to show function represents an input to D-FF

```

   
N1 <= C1'
    <= C1 xor 1
N2 <= C1C2' + C1'C2
    <= C1 xor C2
N3 <= C1C2C3' + C1'C3 + C2'C3
    <= (C1C2)C3' + (C1' + C2')C3
    <= (C1C2)C3' + (C1C2)'C3
    <= (C1C2) xor C3
    
```



## Back to the shift register


- Input determines next state

In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 


```

N1 <= In
N2 <= C1
N3 <= C2
    
```

 
 
## More complex counter example

- Complex counter
  - repeats 5 states in sequence
  - not a binary number representation
- Step 1: derive the state transition diagram
  - count sequence: 000, 010, 011, 101, 110
- Step 2: derive the state transition table from the state transition diagram



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	-	-	-
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	-	-	-

note the don't care conditions that arise from the unused state codes

## More complex counter example (cont'd)

- Step 3: K-maps for next state functions

	C			
C+	0	0	0	X
A	X	1	X	1
	B			

	C			
B+	1	1	0	X
A	X	0	X	1
	B			

	C			
A+	0	1	0	X
A	X	1	X	0
	B			


$$C+ \leq A$$

$$B+ \leq B' + AC'$$

$$A+ \leq BC'$$

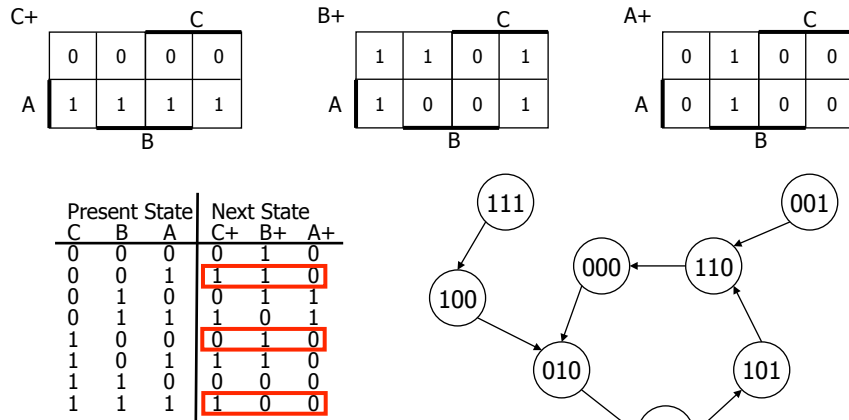
## Self-starting counters (cont'd)

- Re-deriving state transition table from don't care assignment


 
## Self-starting counters

- Start-up states
  - at power-up, counter may be in an unused or invalid state
  - designer must guarantee that it (eventually) enters a valid state
- Self-starting solution
  - design counter so that invalid states eventually transition to a valid state
    - this may or may not be acceptable
  - may limit exploitation of don't cares









## Activity (cont'd)

S1	S0	C	D	N1	N0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	1	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	1	0

 


$$\begin{aligned}
 N1 &\leq C'S1 \\
 &\quad + CDS0'S1' + CDS0S1 \\
 &\quad + CD'S0S1' + CD'S0'S1 \\
 &\leq C'S1 \\
 &\quad + C(D'(S1 \oplus S0) + D(S1 == S0)) \\
 &\leq C'S1 + C(D \oplus (S1 \oplus S0))
 \end{aligned}$$

$$N0 \leq CS0' + C'S0$$

 

 
## Counter/shift-register model

- Values stored in registers represent the state of the circuit
- Combinational logic computes:
  - next state
    - function of current state and inputs
  - outputs
    - values of flip-flops




 
## General state machine model

- Values stored in registers represent the state of the circuit
- Combinational logic computes:
  - next state
    - function of current state and inputs
  - outputs
    - function of current state and inputs (Mealy machine)
    - function of current state only (Moore machine)



  
## State machine model (cont'd)

- States:  $S_1, S_2, \dots, S_k$
- Inputs:  $I_1, I_2, \dots, I_m$
- Outputs:  $O_1, O_2, \dots, O_n$
- Transition function:  $F_s(S_i, I_j)$
- Output function:  $F_o(S_i)$  or  $F_o(S_i, I_j)$




## Comparison of Mealy and Moore machines (cont'd)


### ■ Moore

 

### ■ Mealy

 

### ■ Synchronous Mealy

 

Autumn 2010

CSE370 - XVI - Finite State Machines

23

## Comparison of Mealy and Moore machines

- Mealy machines tend to have less states
  - outputs depend on arc taken from a state to another state ( $n^2$ ) rather than just the state of the FSM ( $n$ )
- Moore machines are safer to use
  - outputs change at next clock edge
  - in Mealy machines, input change can cause async output change (after prop delay of logic) – a BIG problem when two machines are interconnected – asynchronous feedback may occur if one isn't careful (input to fsm1, changes output of fsm1, which is an input to fsm2, whose output changes, and turns out to be input to fsm1)
- Mealy machines advantage? – they react faster to inputs
  - react in same cycle – don't need to wait for clock
  - in Moore machines, more logic may be necessary to decode state into outputs that are needed – more gate delays after clock edge


Autumn 2010

CSE370 - XVI - Finite State Machines

24

## Specifying outputs for a Moore machine

- Output is only function of state
  - specify in state bubble in state diagram
  - example: sequence detector for 01 or 10

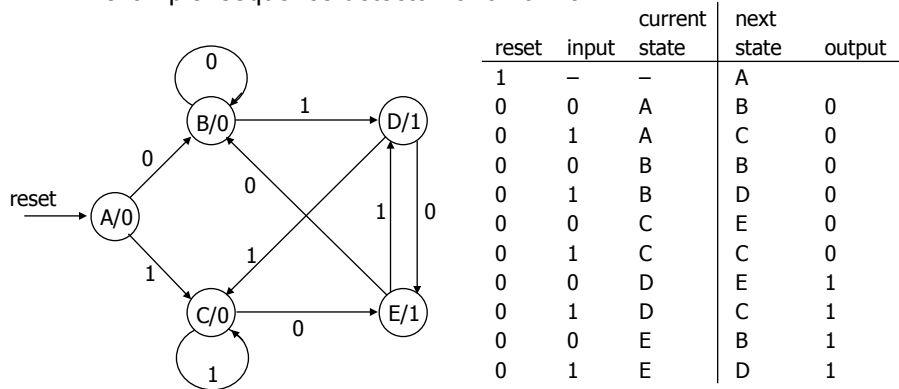


Autumn 2010

CSE370 - XVI - Finite State Machines

25

## Specifying outputs for a Mealy machine

- Output is function of state and inputs
  - specify output on transition arc between states
  - example: sequence detector for 01 or 10

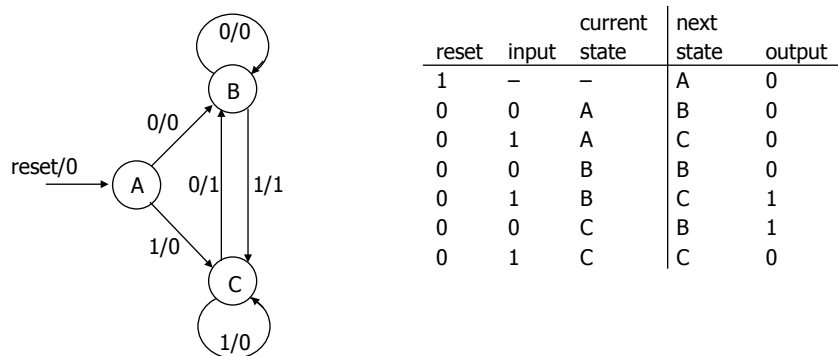


Autumn 2010

CSE370 - XVI - Finite State Machines

26

 
## Synchronous Mealy machine (really Moore)

- Synchronous (or registered) Mealy machine
  - state AND output FFs
  - avoids 'glitchy' outputs (no hazards)
  - easy to implement in programmable logic (function blocks + FF)
- Same as a Moore machine with no output decoding
  - outputs computed on transition to next state rather than after entering state
  - view outputs as expanded state vector – “output-encoded state”


 
## Tug-of-War Game FSM

- Tug of War game
  - 7 LEDs, 2 push buttons (LPB, RPB)



## Light Game FSM Verilog

```
module Light_Game (LEDS, LPB, RPB, CLK, RESET);
```

```
    input LPB ;
    input RPB ;
    input CLK ;
    input RESET;
    output [6:0] LEDS ;

    reg [6:0] position;
    reg left;
    reg right;
```

combinational logic and wires

```
    wire L, R;
    assign L = ~left && LPB;
    assign R = ~right && RPB;
    assign LEDS = position;
```

sequential logic


```
    always @(posedge CLK)
    begin
        left <= LPB;
        right <= RPB;
        if (RESET) position <= 7'b0001000;
        else if ((position == 7'b0000001) || (position == 7'b1000000)) ;
        else if (L) position <= position << 1;
        else if (R) position <= position >> 1;
    end
```

```
endmodule
```

Autumn 2010

CSE370 - XVI - Finite State Machines

29

 

positive edge detector

Do you see a problem with this game?

## Activity

- Where is the problem? What is the fix?

```
always @(posedge CLK) begin
    left <= LPB;
    right <= RPB;
    if (RESET) position <= 7'b0001000;
    else if ( (position == 7'b0000001) || (position == 7'b1000000) )
        position <= position;
    else if (L) position <= position << 1;
    else if (R) position <= position >> 1;
end
```

```
always @(posedge CLK) begin // no longer biased in favor of L player
    left <= LPB;
    right <= RPB;
    if (RESET) position <= 7'b0001000;
    else if ( (position == 7'b0000001) || (position == 7'b1000000) )
        position <= position;
    else if (L & ~R) position <= position << 1; // correct error in state diag.
    else if (R & ~L) position <= position >> 1; // favoring L player
    else
        position <= position; // otherwise, just hold
```


Autumn 2010

CSE370 - XVI - Finite State Machines

30

 
## Example: vending machine

- Release item after 15 cents are deposited
- Single coin slot for dimes, nickels
- No change


 
## Example: vending machine (cont'd)


- Suitable abstract representation
  - tabulate typical input sequences:
    - 3 nickels
    - nickel, dime
    - dime, nickel
    - two dimes
  - draw state diagram:
    - inputs: N, D, reset
    - output: open chute
  - assumptions:
    - assume N and D asserted for one cycle
    - each state has a self loop for  $N = D = 0$  (no coin)





 
## Example: vending machine (cont'd)

- Suitable abstract representation
  - tabulate typical input sequences:
    - 3 nickels
    - nickel, dime
    - dime, nickel
    - two dimes
  - draw state diagram:
    - inputs: N, D, reset
    - output: open chute
  - assumptions:
    - assume N and D asserted for one cycle
    - each state has a self loop for  $N = D = 0$  (no coin)



 
## Activity: reuse states

- Redraw the state diagram using as few states as possible


 
## Example: vending machine (cont'd)

- Minimize number of states - reuse states whenever possible



present state	inputs		next state	output open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	-	-
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	-	-
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	-	-
15¢	-	-	15¢	1

symbolic state table

## Example: vending machine (cont'd)

- Uniquely encode states

present state	inputs	next state		output open
		D1	D0	
0 0	0 0	0 0	0	
	0 1	0 1	0	
	1 0	1 0	0	
	1 1	- -	-	
0 1	0 0	0 1	0	
	0 1	1 0	0	
	1 0	1 1	0	
	1 1	- -	-	
1 0	0 0	1 0	0	
	0 1	1 1	0	
	1 0	1 1	0	
	1 1	- -	-	
1 1	- -	1 1	1	


## Example: Moore implementation

- Mapping to logic

D1	Q1		
	0	1	
	0	1	1
	1	1	1
D	X	X	X
	1	1	1
	Q0		N

D0	Q1		
	0	1	0
	1	0	1
	1	1	1
D	X	X	X
	0	1	1
	Q0		N

Open	Q1		
	0	1	0
	0	0	1
	0	1	0
D	X	X	X
	0	0	1
	Q0		N

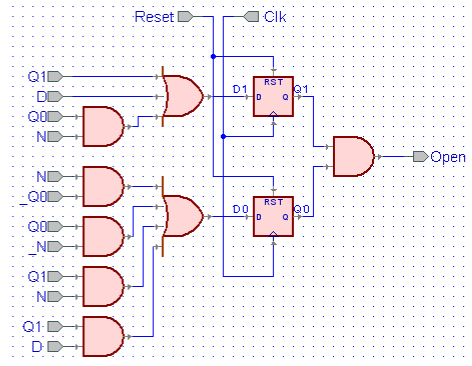

$$D1 = Q1 + D + Q0 N$$


$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$

## Equivalent Mealy and Moore state diagrams


- Moore machine

- outputs associated with state

 


- Mealy machine

- outputs associated with transitions

 

## Example: Mealy implementation

 

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	-	-	-
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	1
		1	1	-	-	-
1	0	0	0	1	0	0
		0	1	1	1	1
		1	0	1	1	1
		1	1	-	-	-
1	1	-	-	1	1	1

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$


Open		Q1	
D	N	0	1
0	0	1	0
0	0	1	1
X	X	1	X
0	1	1	1

## Example: Mealy implementation

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$


$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$

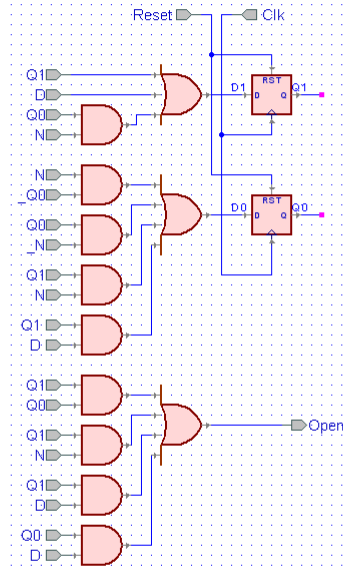
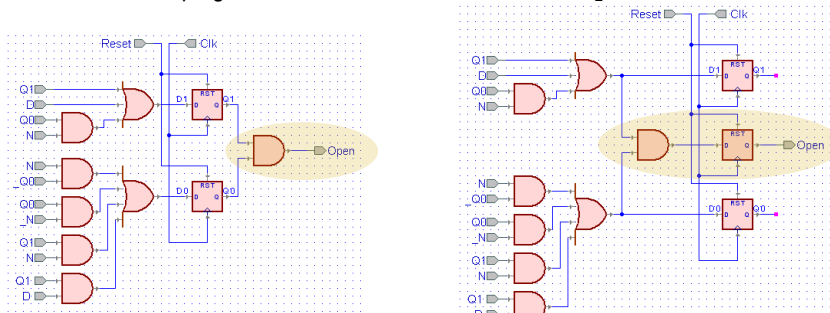
## Vending machine: Moore to synch. Mealy

- OPEN = Q1Q0 creates a combinational delay after Q1 and Q0 change in Moore implementation
- This can be corrected by retiming, i.e., move flip-flops and logic through each other to improve delay – pre-compute OPEN then store it in FF
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$   
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$
- Implementation now looks like a synchronous Mealy machine
  - another reason programmable devices have FF at end of logic




## Vending machine: Mealy to synch. Mealy

- $OPEN.d = Q1Q0 + Q1N + Q1D + Q0D$
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$   
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$


D	Q1	
	0	1
0	0	1
1	0	1
X	X	X
0	1	1

D	Q1	
	0	1
0	0	1
0	0	1
1	0	1
0	1	1

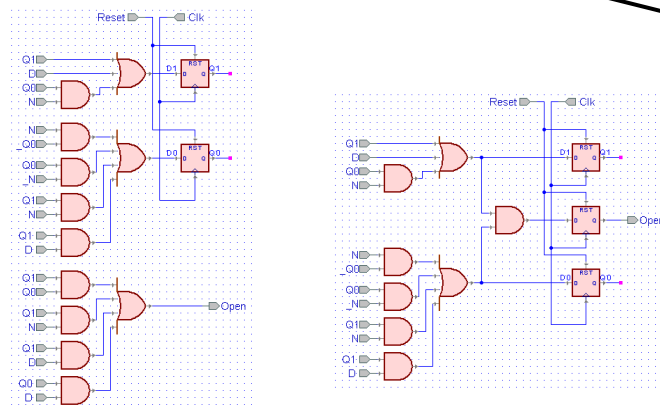

## Vending machine example (Moore PLD mapping)

$D0 = \text{reset}'(Q0'N + Q0N' + Q1N + Q1D)$   
 $D1 = \text{reset}'(Q1 + D + Q0N)$   
 $\text{OPEN} = Q1Q0$

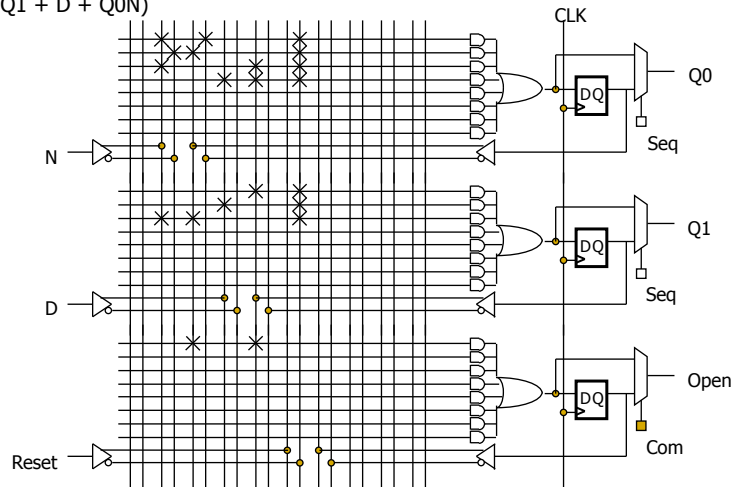


Autumn 2010

CSE370 - XVI - Finite State Machines

43

## Vending machine (synch. Mealy PLD mapping)

$\text{OPEN} = \text{reset}'(Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D)$

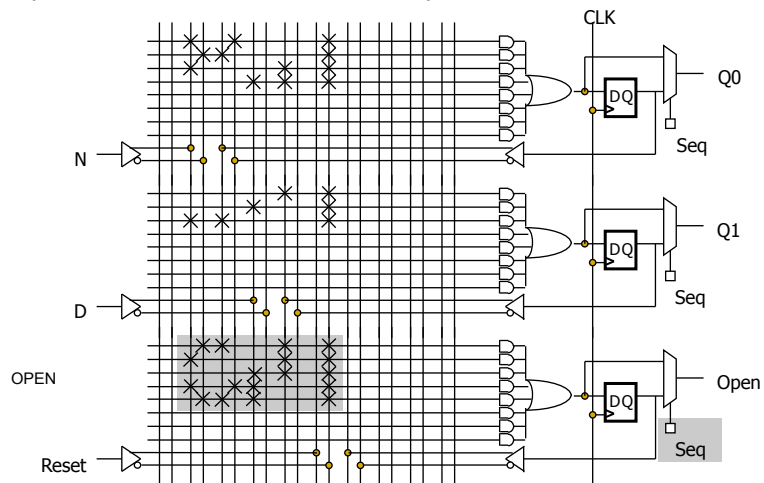

Autumn 2010

CSE370 - XVI - Finite State Machines

44

## One-hot encoded transition table

present state inputs						next state				output
Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	D	N	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	open
0	0	0	1	0	0	0	0	0	1	0
				0	1	0	0	1	0	0
				1	0	0	1	0	0	0
				1	1	-	-	-	-	-
0	0	1	0	0	0	0	0	1	0	0
				0	1	0	1	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
0	1	0	0	0	0	0	1	0	0	0
				0	1	1	0	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
1	0	0	0	-	-	1	0	0	0	1

$$D_0 = Q_0 D' N'$$


$$D_1 = Q_0 N + Q_1 D' N'$$

$$D_2 = Q_0 D + Q_1 N + Q_2 D' N'$$

$$D_3 = Q_1 D + Q_2 D + Q_2 N + Q_3$$

$$\text{OPEN} = Q_3$$

## Designing from the state diagram

 


$$D_0 = Q_0 D' N'$$

$$D_1 = Q_0 N + Q_1 D' N'$$

$$D_2 = Q_0 D + Q_1 N + Q_2 D' N'$$

$$D_3 = Q_1 D + Q_2 D + Q_2 N + Q_3$$

$$\text{OPEN} = Q_3$$


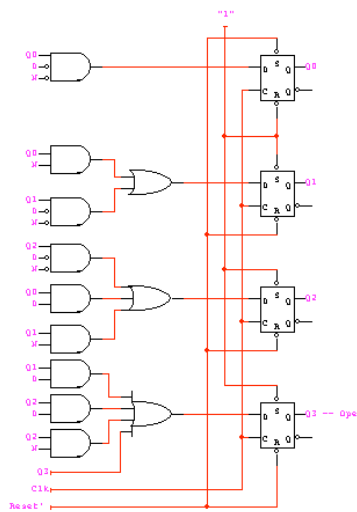


## Output encoding

- Reuse outputs as state bits
  - Why create new functions when you can use outputs?
  - Bits from state assignments are the outputs for that state
    - Take outputs directly from the flip-flops
- ad hoc - no tools
  - Yields small circuits for most FSMs
  - Fits nicely with synchronous Mealy machines
  
## Mealy and Moore examples


- Recognize  $A, B = 0, 1$ 
  - Mealy or Moore?




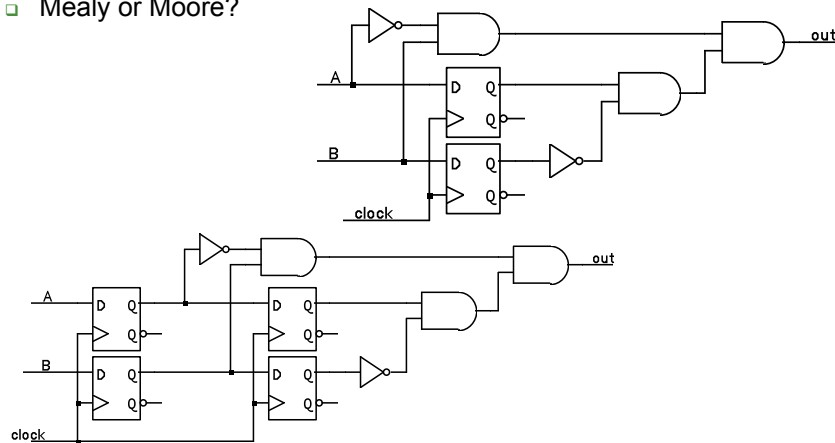
## Mealy and Moore examples (cont'd)

- Recognize A,B = 1,0 then 0,1
  - Mealy or Moore?





## Hardware Description Languages and Sequential Logic

- Flip-flops
  - representation of clocks - timing of state changes
  - asynchronous vs. synchronous
- FSMs
  - structural view (FFs separate from combinational logic)
  - behavioral view (synthesis of sequencers – not in this course)
- Data-paths = data computation (e.g., ALUs, comparators) + registers
  - use of arithmetic/logical operators
  - control of storage elements
  
## Example: reduce-1-string-by-1

- Remove one 1 from every string of 1s on the input (a *filter*)
  - E.g., 00011100 -> 00001100; 00100110 -> 00000010



## Verilog FSM - Reduce 1s example

- Moore machine

```


module reduce (clk, reset, in, out);
    input clk, reset, in;
    output out;

    parameter zero = 2'b00;
    parameter one1 = 2'b01;
    parameter two1s = 2'b10;

    reg out;
    reg [2:1] state; // state variables
    reg [2:1] next_state;

    always @(posedge clk)
        if (reset) state = zero;
        else state = next_state;
    
```

 state assignment  
(easy to change,  
if in one place)



## Moore Verilog FSM (cont'd)

```
always @(in or state)
case (state)
zero:
// last input was a zero
begin
if (in) next_state = one1;
else next_state = zero;
end
one1:
// we've seen one 1
begin
if (in) next_state = twos;
else next_state = zero;
end
twos:
// we've seen at least 2 ones
begin
if (in) next_state = twos;
else next_state = zero;
end
endcase
```

crucial to include  
all signals that are  
input to state determination

note that output  
depends only on state

```
always @(state)
case (state)
zero: out = 0;
one1: out = 0;
twos: out = 1;
endcase
```


endmodule

## Mealy Verilog FSM

```
module reduce (clk, reset, in, out);
input clk, reset, in;
output out;
reg out;
reg state; // state variables
reg next_state;

always @(posedge clk)
if (reset) state = zero;
else state = next_state;

 always @(in or state)
case (state)
zero: // last input was a zero
begin
out = 0;
if (in) next_state = one;
else next_state = zero;
end
one: // we've seen one 1
if (in) begin
next_state = one; out = 1;
end else begin
next_state = zero; out = 0;
end
endcase
endmodule
```



## Synchronous Mealy Machine

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables

  always @(posedge clk)
    if (reset) state = zero;
    else
      case (state)
        zero: // last input was a zero
          begin
            out = 0;
            if (in) state = one;
            else state = zero;
          end
        one: // we've seen one 1
          if (in) begin
            state = one; out = 1;
          end else begin
            state = zero; out = 0;
          end
        end
      endcase
endmodule
```

## Finite state machines summary

- Models for representing sequential circuits
  - abstraction of sequential elements
  - finite state machines and their state diagrams
  - inputs/outputs
  - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
  - deriving state diagram
  - deriving state transition table
  - determining next state and output functions
  - implementing combinational logic
- Hardware description languages