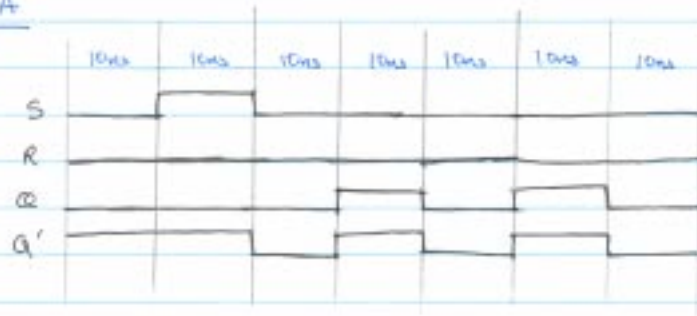


CSE 370 Fall '99
solution 7.

PART A



So as seen above the latch keeps on toggling. The reason for this behaviour is that the effect of setting the latch takes TWO gate delay to propagate from $S \rightarrow Q$. So Q' must remain Low for that time.

\Rightarrow

Minimum Pulse required is 20ns.

PART B




$$\begin{aligned} Q^+ &= (R + Q')' \\ Q'^+ &= (S + Q)' \\ S^+ &= (Q' \cdot \text{DATA}) \\ R^+ &= (Q \cdot \text{DATA}) \end{aligned}$$

As seen above there is a potential for a glitch in R and S, which can also propagate. Note that there is still exactly one state transition per input pulse so the circuit IS CORRECT.

Adding a further 20ns delay between P and Q (and b/w P' and Q') gets rid of this glitch

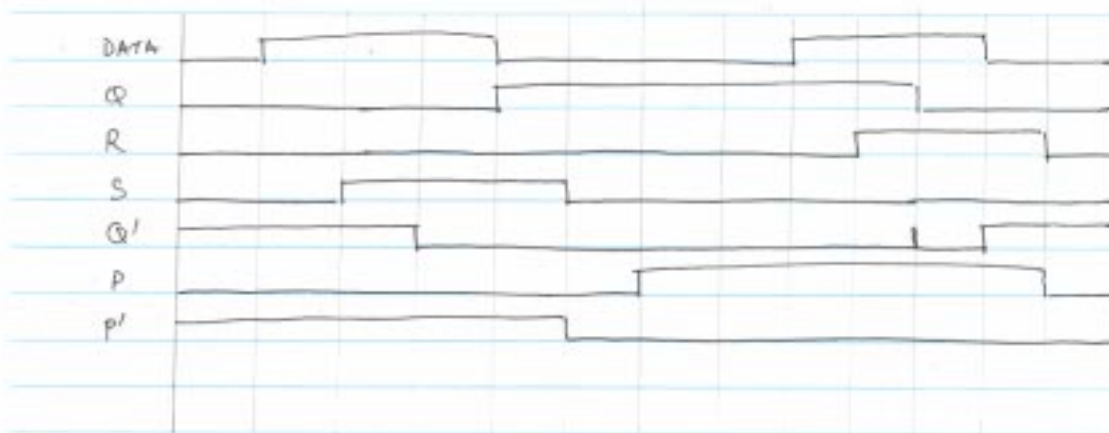There are various ways of adding this delay like.






$$\begin{aligned}
 Q^+ &= (R + Q')' \\
 Q'^+ &= (S + Q)' \\
 S^+ &= (P' \cdot \text{DATA}) \\
 R^+ &= (P \cdot \text{DATA}) \\
 P^{++} &= Q \\
 P'^{++} &= Q'
 \end{aligned}$$

As seen above there is no glitch (or possibility of it) as no two inputs to the same gate change at the same time.

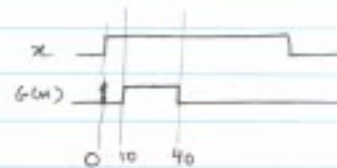PART C

Width of the pulse = 0.136 seconds.

To generate a glitch of 30ns, following circuits would do it
(Assuming each gate as 10ns delay)



PART D

Sensor 1	Sensor 2	$Q(t^-) = PK$	$Q(t^+)$	R	S
0	0	0	0	X	0
0	0	1	1	0	X
0	1	0	1	0	1
0	1	1	0	1	0
1	0	0	1	0	1
1	0	1	0	1	0
1	1	0	X	X	X
1	1	1	X	X	X

Minimizing this one gets.

$$R(P, S_1, S_2) = P(S_1 + S_2)$$

$$S(P, S_1, S_2) = P'(S_1 + S_2)$$

So combining everything, the whole circuit looks like.

