

Simplify the following equations:

$$f(x, y, z) = \overline{xy} + \overline{xz}$$

$$f(x, y, z) = \overline{\overline{xy} + z} + x\overline{y}z + x\overline{y}\overline{z}$$

Implement with only NAND gates:

$$f(a, b, c) = \overline{ab} + c$$

Draw a schematic for the following (in DesignWorks):

$$f(x, y, z) = \overline{\overline{x}y} + xy + x\overline{y}$$