

Design of Digital Circuits and Systems

Finite State Machine Review

Instructor: Justin Hsia

Teaching Assistants:

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder

Lancelot Wathieu

Matthew Hung

Relevant Course Information

- ❖ hw1 due on Monday (4/1)
 - Homework can be completed in groups of up to 4
- ❖ Lab 1 report due Friday (4/5)
 - Labs can be completed in groups of up to 2
- ❖ Lab demos:
 - Lab demo sign up sheet sent out soon (check with partner)
 - 15 minutes for demos, early labs will be quicker
 - Make sure LabsLand is set up and synthesized *beforehand*
- ❖ Quiz 1 is Thursday, April 4 in last 25 min of lecture
 - Draw FSM state diagram & make design decisions

Lecture 1 Review

- ❖ Useful operators:
 - Ternary operator: <cond> ? <then> : <else>
 - Concatenation: {sig, ..., sig}
 - Replication: {n{m}}
- ❖ A **parameter** is a named constant

```
parameter N = 8;           // bus width
parameter period = 100;    // timing constant
```

- ❖ A parameterized module:
 - `module <name> #(<parameter list>) (<port list>);`
 - Parameters can be given default values
 - e.g., `#(parameter N = 8)`

Review Question

Ob 0100 Ob 0000 0100
zero sign Ob 0000 0100
Ob 1100 Ob 0000 1100
zero sign Ob 1111 1100

- ❖ There are two forms of bit extensions: zero-extension (add 0s) and sign-extension (copy MSB)
- ❖ Write out SystemVerilog pseudocode for a parameterized *extender* module
 - Inputs sign (1 bit), in (M bits); output out (N bits $> M$)
 - out should either be the sign-extended version of in (sign = 1) or the zero-extended version of in (sign = 0)

Review Question (Possible) Solution


```
module extender #(parameter M = 4, N = 8)
    (output [N-1:0] out,
     input  [M-1:0] in,
     input      sign);
    assign out = sign ? {{(N-M){in[M-1]}},in} : {{(N-M){1'b0}},in};
endmodule
```

conditional/ternary

replication

concatenation

- ❖ Hardware if $M = 4$ and $N = 8$:

 

Lecture Outline

- ❖ SystemVerilog Review & Tips (Cont.)
- ❖ FSMs
- ❖ Test Benches

Structural vs. Behavioral Revisited

- ❖ Not a strict definition of these terms, so exact classification is not that important
- ❖ Structural:
 - Instantiating modules (library and user-defined) and defining port connections
 - **assign**: continuous assignment
 - Used with nets


Verilog Procedural Blocks

- ❖ A *procedural block* is made up of behavioral code in the form of procedural statements whose effects are interpreted sequentially
 - The block itself is awakened/triggered in a non-sequential manner
- ❖ **initial**: block triggered once at time zero
 - Non-synthesizable (*i.e.*, for simulation/testbenches only)
- ❖ **always**: block triggered by a *sensitivity list*
 - Any object that is assigned a value in an **always** statement must be declared as a variable (*e.g.*, **logic** or **reg**).

SystemVerilog Procedural Blocks

- ❖ SystemVerilog introduced variants on always that are generally more robust and more specialized
~~@(posedge clk)~~
- ❖ **always_comb**: intended for combinational logic
 - Sensitivity list is automatically built
- ❖ **always_latch**: intended for latch-based logic
 - Sensitivity list is automatically built
 ~~@(posedge clk)~~
- ❖ **always_ff**: intended for sequential logic (*i.e.*, synchronous/clocked)
 - Sensitivity list must be specified

Latch vs. Flip-Flop


 


- ❖ Both are bistable multivibrators (2 stable states) that can store information
- ❖ A latch is *asynchronous*; a flip-flop is *edge-triggered*

```
module my_latch(input logic clk,
                  input logic [3:0] d,
                  output logic [3:0] q);
    always_latch
        if (clk) q <= d;
    endmodule
```

q will update to d as long as clk=1

"latched" when clk=0

  


```
module my_ff(input logic clk,
              input logic [3:0] d,
              output logic [3:0] q);
    always_ff @(posedge clk)
        q <= d;
    endmodule
```

only updates at rising edge of clock

Inferred Latches

 - ❖ **Warning:** easy to write code with inadvertent latches
 - Check your synthesis output for “Inferred latch”
 - Usually from incomplete assignments – unspecified branch infers latch behavior
- ❖ **Question:** which of the following will synthesize and, if so, what will the hardware look like?



- **Demo:** Tools → “Netlist Viewers” → “RTL Viewer”

case Statement

- ❖ Create combinational logic and is easier to read than lots of `if/else` statements
 - Must always be inside an `always` block
 - Each case has an implied C-style break

```
module seven_seg(bcd, segs);  
  input  logic [3:0] bcd;  
  output logic [6:0] segs;  
  
  always_comb  
    case (bcd)  
      // abc_defg  
      0: segs = 7'b011_1111;  
      1: segs = 7'b000_0110;  
      2: segs = 7'b101_1011;  
      3: segs = 7'b100_1111;  
      4: segs = 7'b110_0110;  
      5: segs = 7'b110_1101;  
      6: segs = 7'b111_1101;  
      7: segs = 7'b000_0111;  
      8: segs = 7'b111_1111;  
      9: segs = 7'b110_1111;  
  
    endcase  
  
endmodule
```

case Statement

- ❖ Create combinational logic and is easier to read than lots of `if/else` statements
 - Must always be inside an `always` block
 - Each case has an implied C-style break
 - Remember to use `default` to avoid incomplete assignments!

```
module seven_seg(bcd, segs);  
  input  logic [3:0] bcd;  
  output logic [6:0] segs;  
  
  always_comb  
    case (bcd)  
      // abc_defg  
      0: segs = 7'b011_1111;  
      1: segs = 7'b000_0110;  
      2: segs = 7'b101_1011;  
      3: segs = 7'b100_1111;  
      4: segs = 7'b110_0110;  
      5: segs = 7'b110_1101;  
      6: segs = 7'b111_1101;  
      7: segs = 7'b000_0111;  
      8: segs = 7'b111_1111;  
      9: segs = 7'b110_1111;  
    → default: segs = 7'bX;  
    endcase  
  
endmodule
```

Other SystemVerilog Resources

- ❖ SystemVerilog Language Reference Manual
 - On website, Verilog → Reference Manual
 - 586 pages...
- ❖ SystemVerilog articles
 - <https://www.systemverilog.io/>
 - <http://www.verilogpro.com/>
 - <https://www.chipverify.com/systemverilog/systemverilog-tutorial>
- ❖ One style guide for SystemVerilog
 - <https://www.systemverilog.io/styleguide>
 - We won't enforce, but good guidelines


Technology Break

Lecture Outline

- ❖ SystemVerilog Review & Tips (Cont.)
- ❖ **Finite State Machine Design**
- ❖ Test Benches

Finite State Machines (FSMs)

 - ❖ A convenient way to conceptualize computation over time using a *state transition diagram*
 - Consists of a *set of states*, an *initial state*, and a *transition function*
- ❖ FSM implementations come in 3 blocks:
 - State register (SL)
 - Next state logic (CL)
 - Output logic (CL)



FSM Implementation Notes

- ❖ States must be assigned a binary encoding
 - More readable by using parameters or an enum
 - Encoding choices can affect logic simplification
- ❖ Reset signal can be synchronous (responds to clk) or asynchronous (responds to reset)
 - Determined by whether or not reset is in sensitivity list
- ❖ State logic (next state logic + state update) can be written as 1 combined block or 2 separate blocks
- ❖ If input is asynchronous, may want to add a two-flip-flop *synchronizer* to deal with metastability



FSM SystemVerilog Design Pattern


- ❖ Which, if any, construct(s) would you expect to use for each of the following basic sections of a module that implements an FSM?

				enum logic [N-1:0] { A, B, C } ps, ns;
<i>not logic!</i>	▪ // define states and state variables	initial assign always_comb	always_ff	None
<i>combinational logic</i>	▪ // next state logic (ns)	initial <u>assign</u> <u>always_comb</u>	always_ff	None
<i>combinational logic</i>	▪ // output logic	initial <u>assign</u> <u>always_comb</u>	always_ff	None
<i>sequential logic</i>	▪ // state update logic (ps)	initial assign always_comb	<u>always_ff</u>	None

alternatives exist!

FSM Example: String Manipulator

 - ❖ Takes in a stream of inputs and removes the *second 1* from every consecutive string of 1's.



- Example inputs: 0 1 0 1 1 0 1 1 1 0 1 1 1 ...
outputs: 0 1 0 1 0 0 1 0 1 0 1 0 1 1 1 ...

String Manipulator FSM

```
module fsm (input logic clk, reset, in,  
           output logic out);
```

(1) // present and next state

```
enum logic [1:0] {S0, S1, S3} ps, ns;
```

(2) // next state logic

```
always_comb
```

```
case (ps)  
    S0: if (in) ns = S1;  
         else ns = S0;
```

```
    S1: if (in) ns = S3;  
         else ns = S0;
```

```
    S3: if (in) ns = S3;  
         else ns = S0;
```

```
endcase
```

(3) // output logic

```
assign out = in & (ps[1] | ~ps[0]);
```

...

? S1: S0

...

// sequential logic (DFFs)

(4) // synchronous reset

```
always_ff @(posedge clk)  
    if (reset)  
        ps <= S0; // reset state  
    else  
        ps <= ns;
```

```
endmodule // fsm
```



Moore vs. Mealy

- ❖ **Moore** machines define their outputs based on states ($(00/1)$) and **Mealy** machines define outputs based on transitions ($\underline{0/1}$)
 - Mealy machines are more *flexible*
 - Moore outputs are function of state; Mealy outputs are function of state *and inputs*
 - All FSMs can be expressed in either form, but some systems are more naturally expressed one way versus the other
 - Feel free to use either in this class if not specified
- ★ However, there *are* implementation differences!

Mealy \leftrightarrow Moore Conversions

Not testable material

 
 
- ❖ **Moore \rightarrow Mealy:** copy the state output to every transition *entering* the state
- ❖ Example: FSM for a *turnstile*, which is locked until someone swipes their Husky ID (input H) and then locks once you push through (input P) the unlocked gate. Outputs a light that glows red (0) or green (1).



Mealy \leftrightarrow Moore Conversions

Not testable material

  
- ❖ **Mealy \rightarrow Moore:** more complicated process; if incoming transitions differ in output, may need to “split” the state
- ❖ Example: the threeOnes FSM from Lecture 1




Moore vs. Mealy Outputs

- ❖ Compare a Moore and Mealy FSM for the turnstile. Complete the statements and waveform below, assuming no delays:


Moore:

 

Mealy:

 


```
assign out_moore = (ps == U);
assign out_mealy = ((ps == U & ~P) | ((ps == L) & H & ~P));
```

 


Moore vs. Mealy Outputs

❖ Moore:

 

- Outputs change synchronously with state changes

❖ Mealy:

 

can add register to synchronize output changes
DQ

- Input changes can cause *immediate* output changes

(often change sooner than Moore outputs)

Lecture Outline

- ❖ SystemVerilog Review & Tips (Cont.)
- ❖ Finite State Machine Design
- ❖ **Test Benches**

Test Benches

- ❖ Special modules *needed for simulation only!*
 - Software constraint to mimic hardware
- ❖ ModelSim runs entirely on your computer
 - Tries to simulate your FPGA environment without actually using hardware – no physical signals available
 - Must create fake inputs for FPGA's physical connections
 - *e.g.*, LEDR, HEX, KEY, SW, CLOCK_50
 - Unnecessary when code is loaded onto FPGA
- ❖ Need to define both input signal combinations as well as their timing

Test Bench Timing Controls

- ❖ Delay: #<time> #10 #(period/2)
 - Delays by a specific amount of simulation time
- ❖ Edge-sensitive: @(<pos/neg>edge <signal>)
 - Delays next statement until specified transition on signal
- ❖ Level-sensitive Event: wait(<expression>)
 - Waits until <expression> evaluates to TRUE
- ❖ Stop simulation: \$stop;
- ❖ Timescale: `timescale <time unit> / <precision>
 - e.g., `timescale 1 ns / 1 ps

each arbitrary simulation time unit (#1)

↑ rounding

Extender Test Bench

```
`timescale 1 ns / 1 ns
module extender_tb();

parameter M = 4, N = 8;
logic [M-1:0] in;
logic [N-1:0] out;
logic sign;


extender #(M, N) dut (.*);

int i;
initial begin
    for (i = 0; i < 2**2; i++) begin
        sign = i[0]; in = {i[1], {(M-1){1'b0}}}; #10;
    end // for
    $stop;
end // initial
endmodule // extend
```

i = 0 b0...0 0 0
0 b0...0 0 1
0 b0...0 1 0
0 b0...0 1 1

MSB of in
sign

exponentiation (2^2)

 

FSM Test Bench Notes

- ❖ Your main goal is to test every transition that we care about – may take extra clock cycles
- ❖ For simulation, you need to generate a clock signal
 - Assume we have parameter `clock_period`;

Explicit Edges:

```
initial
    clk = 0;

always_comb begin
    #(clock_period/2) clk <= 1;
    #(clock_period/2) clk <= 0;
end
```

Toggle:

```
initial begin
    clk <= 0;
    forever #(clock_period/2) clk <= ~clk;
end
```

String Manipulator Test Bench

```
module fsm_tb();  
  
logic clk, reset, in, out;  
  
fsm dut (.*);  
  
// simulated clock  
parameter period = 100;  
initial begin  
    clk <= 0;  
    forever  
        #(period/2)  
        clk <= ~clk;  
end // initial clock  
  
...
```



...

```
initial begin  
    reset <= 1; in <= 0; @(posedge clk);  
    reset <= 0; in <= 0; @(posedge clk);  
    in <= 0; @(posedge clk);  
    in <= 1; @(posedge clk);  
    in <= 0; @(posedge clk);  
    in <= 1; @(posedge clk);  
    in <= 0; @(posedge clk);  
    in <= 1; @(posedge clk);  
    in <= 0; @(posedge clk);  
    in <= 1; @(posedge clk);  
    in <= 1; @(posedge clk);  
    in <= 0; @(posedge clk);  
    in <= 1; @(posedge clk);  
    in <= 1; @(posedge clk);  
    $stop; // end simulation  
end // initial signals  
  
endmodule // fsm_tb
```

① signal changes


② the clock edge that reads the new signal values

String Manipulator Waveforms

  

Checking Responses

- ❖ Visually checking simulated waveforms quickly becomes impractical for large designs simulated over thousands of clock cycles
 - Displaying and explaining your waveforms for labs can be tedious
- ❖ There are simulator-independent system tasks to write messages to the user/tester!
 - Look similar to `printf()` in C
 - `$<system_task>(<format_string>, <sig_1>, <sig_2>, ...)`
 - Will look at `$display` today and others later on

 


`$<system_task>(<format_string>, <sig_1>, <sig_2>, ...)`

Checking Responses: \$display

- ❖ Triggers once when encountered, prints the given format string and adds a new line:
 
```
// define test inputs
int i;
initial begin
    for (i = 0; i < 2**2; i++) begin
        sign = i[0]; in = {i[1], {(M-1){1'b0}}}; #10;
        $display("t = %0t, %b %s %b",
(current simulation time) $time, in, sign ? "->" : "-0->", out);
    end // for
    $stop;
end // initial
```



Format Specifiers

Table 5.7: Format Specifiers.

Specifier	Meaning
%h	Hexadecimal format
%d	Decimal format <i>(signed)</i>
%o	Octal format
%b	Binary format
%c	ASCII character format
%v	Net signalstrength
%m	Hierarchical name of current scope
%s	String
%t	Time
%e	Real in exponential format
%f	Real in decimal format
%g	Real in exponential or decimal format

\

escape character

Table 5.8: Special characters.

Symbol	Meaning
\n	New line
\t	Tab
\\"	\character
\\"	” character
\xyz	Where xyz is are octal digits - the character given by that octal code
%%	% character

- **Warning:** these differ from the specifiers for `printf`
- The *minimum* field width is specified by numbers between the '%' and specifier letter
 - e.g., `%3d` will pad out to 3 digits if necessary,
`%0d` will show just the minimum number of digits needed