

Design of Digital Circuits and Systems

Memory II

Instructor: Justin Hsia

Teaching Assistants:

Colton Harris

Gayathri Vadhyan

Lancelot Wathieu

Deepti Anoop

Jared Yoder

Matthew Hung

Relevant Course Information

- ❖ Lab 1 report due tomorrow (4/5)
- ❖ Lab 1 demo due by end of 4/12
 - See Lab Demo Slot assignment on Canvas
- ❖ Lab 2 report due next Friday (4/12)
- ❖ Homework 2 due next Wednesday (4/10)
- ❖ Use Ed Discussion to ask course questions
 - If sensitive, can email *from a UW-associated email account*
 - Do NOT use Canvas messages

Lab 2 Notes

- ❖ Implementing a few **RAM variants** on the DE1-SoC
 - Using both a library catalog and user-specified RAM modules
- ❖ Learn how to create and use a **memory initialization file (.mif)** to initialize memory on your board
- ❖ Feel free to reuse other modules (*e.g.*, input, clock divider, 7-seg, counter) from 271/369
 - Simple modules don't need diagrams or simulations, but they should be shown in the block diagram and mentioned in your report

Synchronous Single-Port RAM (Review)

❖ Synchronous Inputs:


- wren (1 = write, 0 = read)
- addr (A -bit address)
- din (D -bit data)

❖ Synchronous Output:

- dout (D -bit data)

❖ Implementation hints:

 - Will need an internal RAM array of what size? $2^A \times D$
- To synchronize, should update on clock triggers *always-ff @ (posedge clk)*
- What should dout do when wren = 1? *also set to din*



Synchronous Single-Port RAM (Review)

```
module RAM_single #(parameter A, D)
    (clk, wren, addr, din, dout);

    input  logic clk, wren;
    input  logic [A-1:0] addr;
    input  logic [D-1:0] din;
    output logic [D-1:0] dout;

    logic [D-1:0] RAM [0:2**A-1];

    always_ff @(posedge clk) begin
        if (wren) begin // write
            RAM[addr] <= din;
            dout <= din;
        end
        else // read
            dout <= RAM[addr];
        end // always_ff
    endmodule
```

could be either ordering since we aren't loading from a file

↑ can't be RAM[addr] because non-blocking assignment

Simplified Synchronous Dual-Port RAM


- ❖ 2 ports with 1 dedicated to writing and the other dedicated to reading

- ❖ Synchronous Inputs:

- `wren` (1 = write, 0 = read)
- `addr_w` (A -bit address)
- `addr_r` (A -bit address)
- `din_w` (D -bit data)

- ❖ Synchronous Output:

- `dout_r` (D -bit data)

 

- ❖ Differences in SystemVerilog?

read from `addr_r`, write to `addr_w`
edge case only if `addr_r == addr_w`

Simplified Synchronous Dual-Port RAM (SV)

```
module RAM_dual_simple #(parameter A, D)
    (clk, wren, addr_w, addr_r, din_w, dout_r);

    input  logic clk, wren;
    input  logic [A-1:0] addr_w, addr_r;
    input  logic [D-1:0] din_w;
    output logic [D-1:0] dout_r;

    logic [D-1:0] RAM [0:2**A-1];

    always_ff @(posedge clk) begin
        if (wren) begin
            RAM[addr_w] <= din_w;           // write to addr_w
            dout_r <= (addr_r == addr_w) ? din_w : RAM[addr_r];
            // only a conflict if addr_r == addr_w
        end
        else
            dout_r <= RAM[addr_r];         // read from addr_r
        end // always_ff
    endmodule
```

Synchronous Dual-Port RAM


- ❖ The most general configuration – each port can either read or write

- ❖ Synchronous Inputs:

- wren_a and wren_b
- addr_a and addr_b
- din_a and din_b

- ❖ Synchronous Output:

- dout_a and dout_b

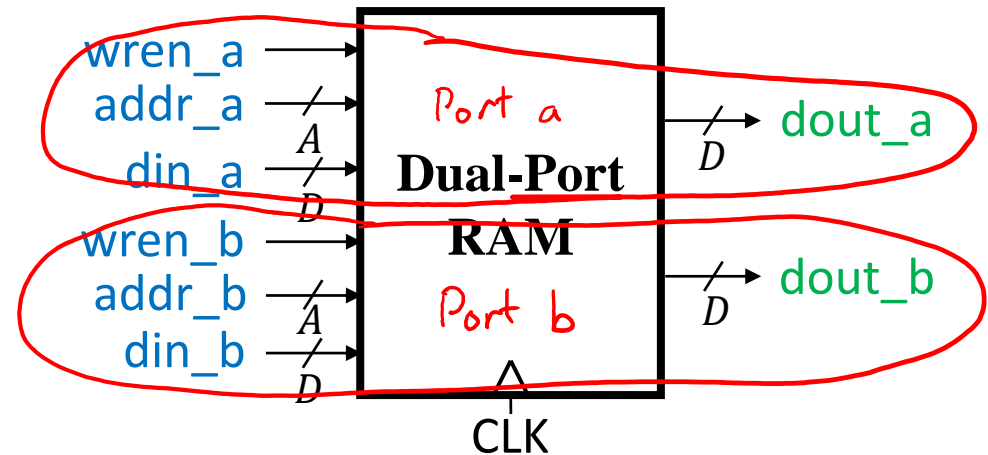

- ❖ Differences in SystemVerilog?

two sets of reading & writing connections
 what if writing to both
 addr_a == addr_b ?


Memory

- ❖ Several forms of memory are available, which include:
 - ~~Secondary memory (e.g., hard disk, flash drive)~~
 - Read-only memory (ROM)
 - Random-access memory (RAM)
 - Register files
 - Small, fast, fixed-sized memory that hold CPU data state
 - First in, first out (FIFO) buffers



Memory Type #3: Register File

- ❖ Register File – a collection of registers
 - 1 input data port – can only write to 1 register at a time
 - 1+ output data ports – can read from 1+ register at a time
 - Address inputs to specify read/write targets
 - Write enable
- ❖ Frequently used in CPUs or as fast buffers

- ❖ Example:

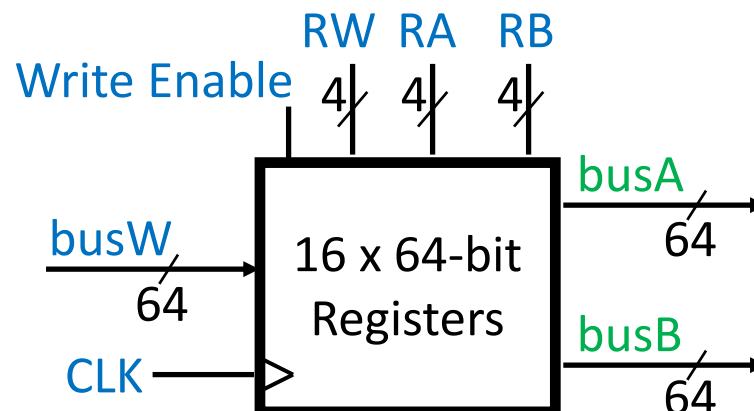


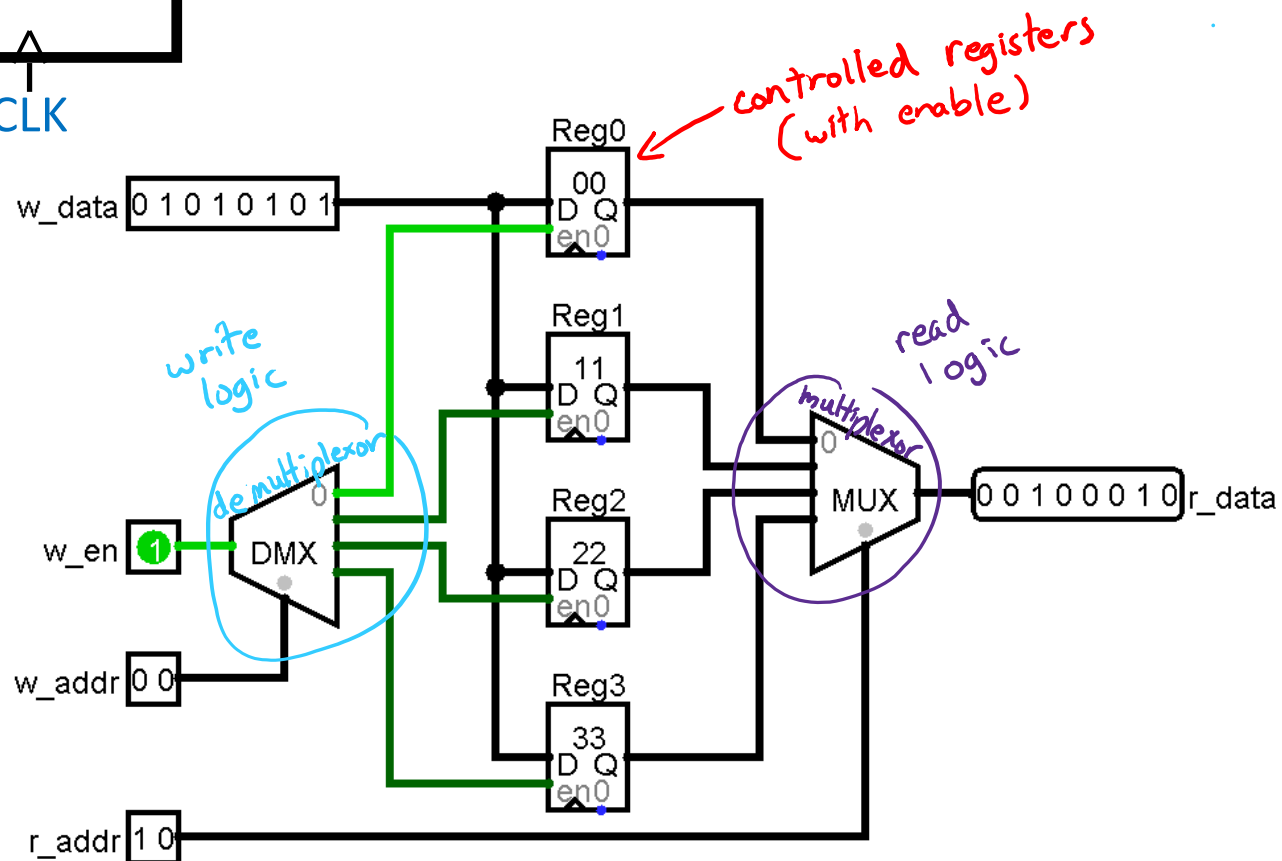 Simple Register File (4 reg, 1 read port)



Memory Review

 - ❖ Can think of reg file as a 2-D array of D flip-flops:



- ❖ The simple reg file was labeled 4×8

- SystemVerilog array declaration: `logic [7:0] reg_array [0:3];`

- ❖ For a generic reg file with parameters D_WIDTH and A_WIDTH:

- Depth: 2^{A_WIDTH}

- Width: D_WIDTH

- SystemVerilog array declaration:

`logic [D_WIDTH-1:0] reg_array [0:2**A_WIDTH-1];`

Register File with 1 Read Port (SV)

```
module reg_file #(parameter D_WIDTH=8, A_WIDTH=2)
    (clk, w_data, w_en, w_addr, r_addr, r_data);

    input  logic clk, w_en;
    input  logic [A_WIDTH-1:0] w_addr, r_addr;
    input  logic [D_WIDTH-1:0] w_data;
    output logic [D_WIDTH-1:0] r_data;

    // array declaration (registers)
    logic [D_WIDTH-1:0] array_reg [0:2**A_WIDTH-1];

    // write operation (synchronous)
    always_ff @(posedge clk)
        if (w_en)
            array_reg[w_addr] <= w_data;

    // read operation (asynchronous)
    assign r_data = array_reg[r_addr];

endmodule
```

← registers

} write logic

} read logic

Where's the Hardware?

```

module reg_file #(parameter D_WIDTH=8, A_WIDTH=2)
    (clk, w_data, w_en, w_addr, r_addr, r_data);

    input  logic clk, w_en;
    input  logic [A_WIDTH-1:0] w_addr, r_addr;
    input  logic [D_WIDTH-1:0] w_data;
    output logic [D_WIDTH-1:0] r_data;

    // array declaration (registers)
    logic [D_WIDTH-1:0] array_reg [0:2**A_WIDTH-1];

    // write operation (synchronous)
    always_ff @(posedge clk)
        if (w_en)
            array_reg[w_addr] <= w_data;


    // read operation (asynchronous)
    assign r_data = array_reg[r_addr];

endmodule


```

← registers

 
DEMUX of w.en
with w-addr as
selector to
enable inputs



MUX with r-addr
as selector

 


Register File with 2 Read Ports

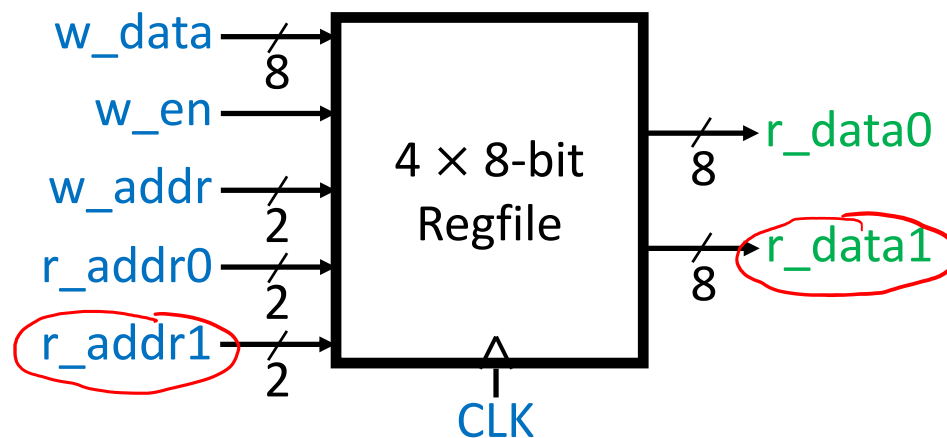

❖ What would change in hardware?

add an extra MUX

 

❖ What would change in SystemVerilog?

add second assign statement:

```
assign r_data1 = array_reg[r_addr1];
```

Register File with Synchronous Read


- ❖ Back to the 1 read port version, but now we want to make reading *synchronous*:

- What would change in SystemVerilog?

move the `r_data = array_reg[r_addr];`
into the `always_ff` block,
but outside the `if (w-en)`

- What would change in hardware?

add a register after the MUX:

 


Short Tech Break

Memory Type #4: FIFO Buffer

❖ First-In First-Out (FIFO) Buffer

 
- Data storage such that elements that arrived earlier are accessed before elements that arrived later



- Has a limited capacity, so there is a notion of fullness (full, empty)
- Useful for synchronization, especially in communication (e.g., UART, disk, network)

FIFO Buffer Functionality

- ❖ Implementation we will work towards:

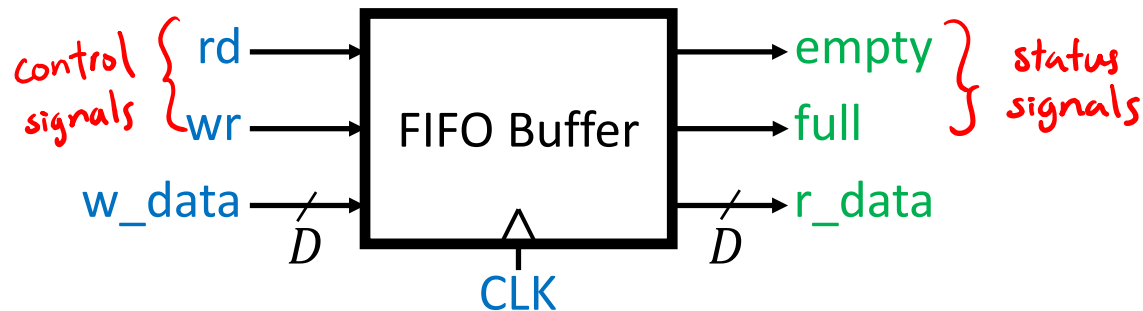

- **rd** signals to read the next element on **r_data**,
wr signals to write **w_data** into the buffer
- Outgoing data is read from the *front/head* of the buffer and incoming data is written to the *back/tail* of the buffer
- Can be implemented by wrapping a regular memory component with a special *controller*
 - However, the FIFO buffer has no visible notion of address!


FIFO Read Configurations

- ❖ First Word Fall Through (FWFT)
 - *Asynchronous* read: front element of buffer always “falls through” and is immediately available on the output bus
 - Including when an element is written to an empty buffer!
 - rd therefore acts more like a “remove” signal

- ❖ Standard
 - *Synchronous* read: front element of buffer becomes available on next clock cycle after rd is asserted
 - rd therefore acts more like a “request” signal

FIFO Read Configurations

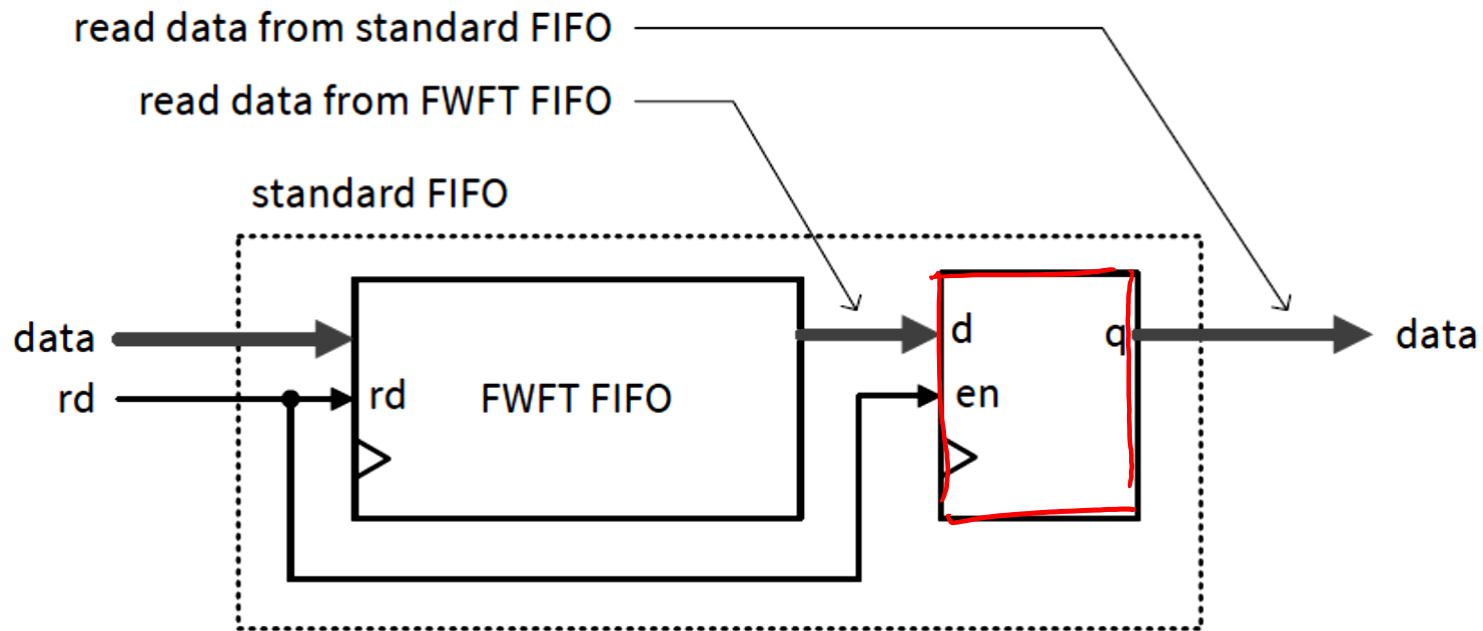
- ❖ Read configuration comparison
 - FWFT can be converted to standard by registering the output:




FIFO Implementation

❖ A FIFO buffer is often implemented as a *circular queue* with two pointers:

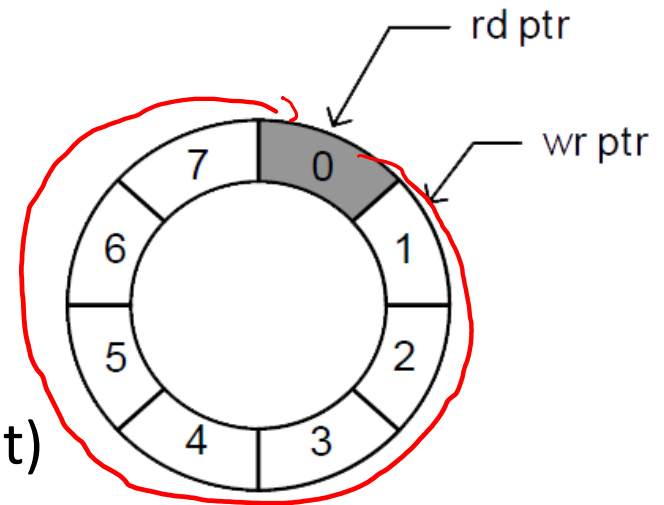- **rd_ptr** indicates the location of the front/head (*i.e.*, the first valid data) and advances when rd is asserted
- **wr_ptr** indicates the location of the back/tail (*i.e.*, the first empty element) and advances when wr is asserted
- empty and full as buffer fullness status indicators
 - These are tricky because both situations have rd_ptr == wr_ptr




Circular Queue Example Operation

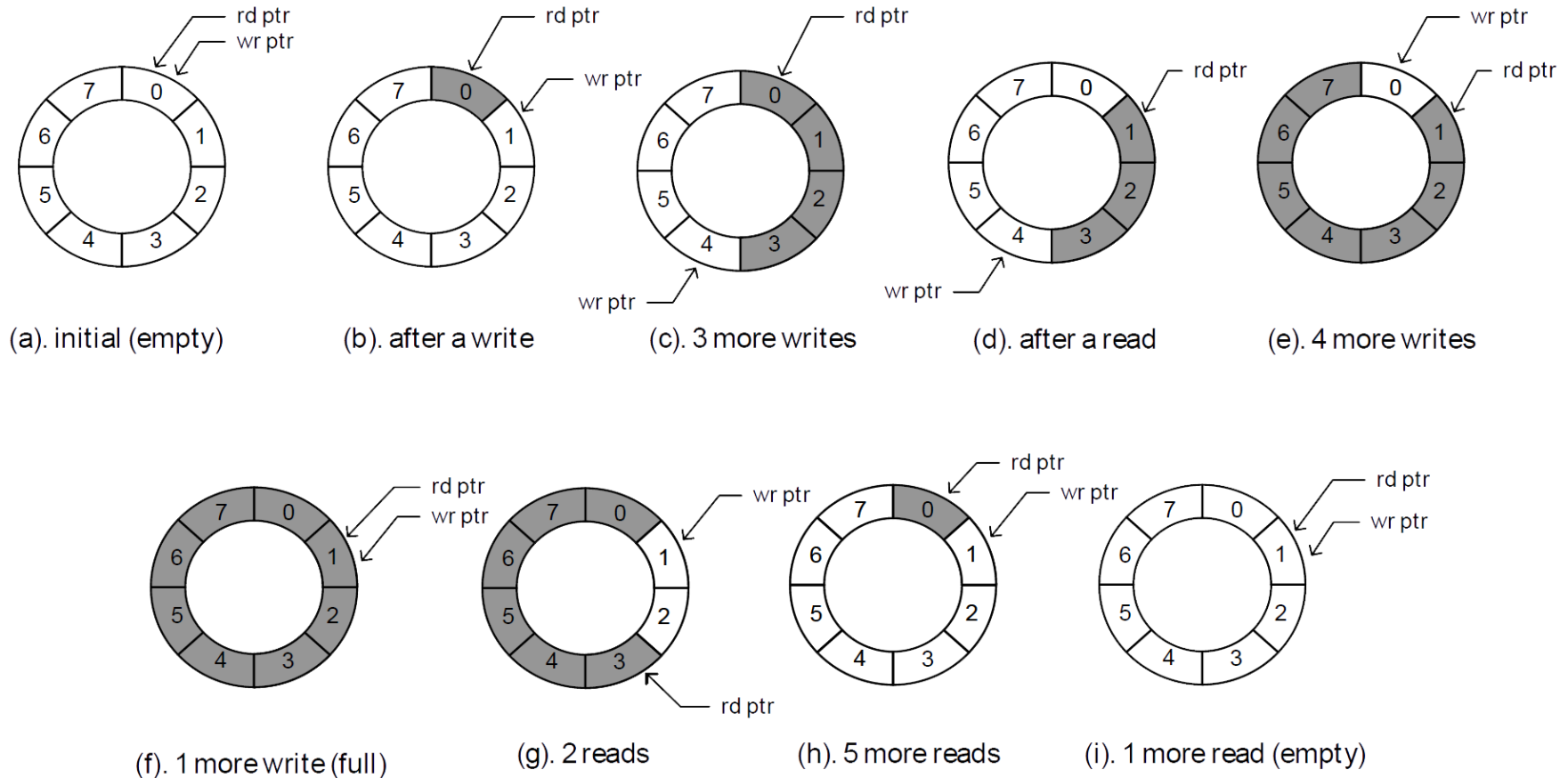

Circular Queue Implementation

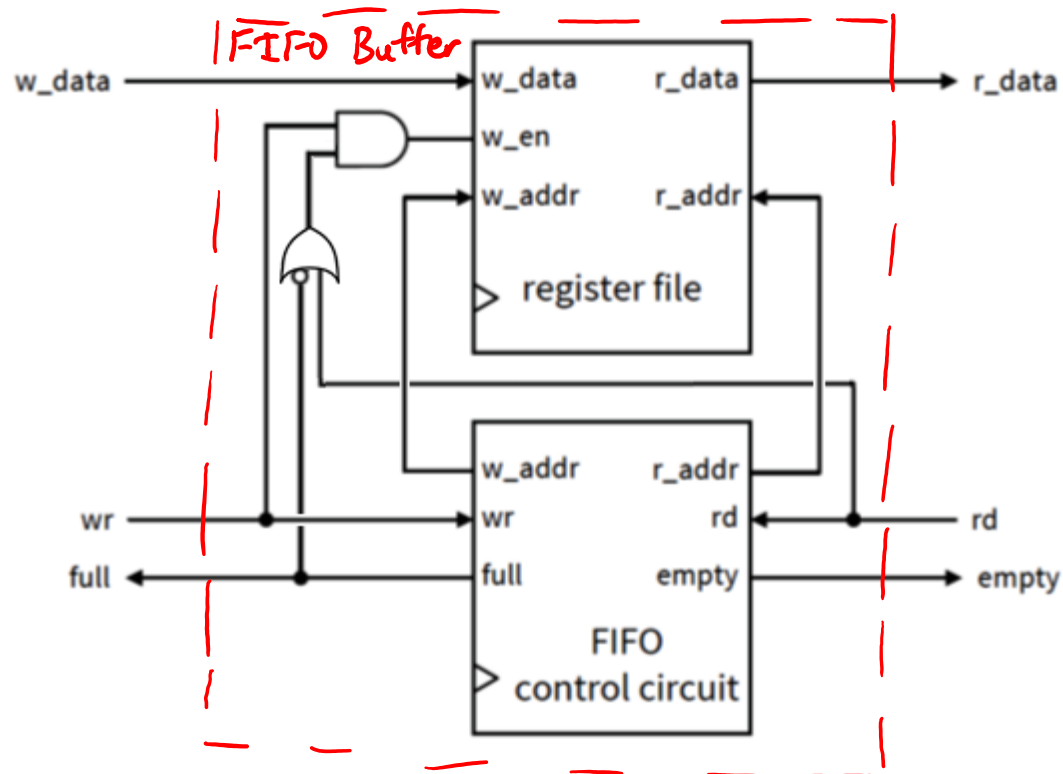- ❖ A circular queue can be implemented using a RAM module and a *FIFO controller*
 - The controller handles the “arrangement” of the linear memory space into a circular queue



FIFO Controller

- ❖ FIFO controller internals:
 - rd_ptr and wr_ptr are *counters*
 - empty and full are *flip-flops*
 - Next state logic based on inputs rd and wr:

rd	wr	rd_ptr	wr_ptr	empty	full
0	0	—	—	—	—
0	1	—	+ 1	0	1 if new wr_ptr == rd_ptr
1	0	+ 1	—	1 if new rd_ptr == wr_ptr	0
1	1	+ 1	+ 1	—	—

only if ~full
only if ~empty

FIFO Controller

- ❖ FIFO controller internals:
 - rd_ptr and wr_ptr are *counters*
 - empty and full are *flip-flops*
 - Next state logic based on inputs rd and wr:
 - rw
 - 00 → no change
 - 11 → advance both rd_ptr and wr_ptr
full and empty don't change
 - 10 → if not empty: advance rd_ptr,
set full = 0,
set empty = 1 if rd_ptr == wr_ptr
 - 01 → if not full: advance wr_ptr,
set empty = 0,
set full = 1 if rd_ptr == wr_ptr

FIFO Controller (SV, 1/3)

```
module fifo_ctrl #(parameter A_WIDTH=4)
    (clk, reset, rd, wr, empty, full, w_addr, r_addr);

    input  logic clk, reset, rd, wr;
    output logic empty, full;
    output logic [A_WIDTH-1:0] w_addr, r_addr;

    // next state signal declarations
    logic [A_WIDTH-1:0] rd_ptr, rd_ptr_next;
    logic [A_WIDTH-1:0] wr_ptr, wr_ptr_next;
    logic empty_next, full_next;

    // output assignments
    assign w_addr = wr_ptr;
    assign r_addr = rd_ptr;

    // [continued on next slide...]
```

} port declarations

} equivalent to
declaring ps, ns

FIFO Controller (SV, 2/3)

```
// fifo controller logic
always_ff @(posedge clk) begin
  if (reset)
    begin
      wr_ptr <= 0;
      rd_ptr <= 0;
      full   <= 0;
      empty  <= 1;
    end
  else
    begin
      wr_ptr <= wr_ptr_next;
      rd_ptr <= rd_ptr_next;
      full   <= full_next;
      empty  <= empty_next;
    end
end
```

} reset state

} equivalent to $ps \leq ns;$

```
// [continued on next slide...]
```

FIFO Controller (SV, 3/3)

```
// next state logic
always_comb begin
    // default: keep current values
    rd_ptr_next = rd_ptr;
    wr_ptr_next = wr_ptr;
    empty_next = empty;
    full_next = full;

    // [continued in next box...]
```

implements the next state logic from 3 slides ago

```
case ({rd, wr})
    2'b11: // read and write
        begin
            rd_ptr_next = rd_ptr + 1'b1;
            wr_ptr_next = wr_ptr + 1'b1;
        end
    2'b10: // read
        if (~empty) begin
            rd_ptr_next = rd_ptr + 1'b1;
            if (rd_ptr_next == wr_ptr)
                empty_next = 1;
            full_next = 0;
        end
    2'b01: // write
        if (~full) begin
            wr_ptr_next = wr_ptr + 1'b1;
            empty_next = 0;
            if (wr_ptr_next == rd_ptr)
                full_next = 1;
        end
    2'b00: ; // no change
endcase
end // always_comb

endmodule
```

FIFO Buffer (SV)

```
module fifo #(parameter D_WIDTH=8, A_WIDTH=4)
    (clk, reset, rd, wr, empty, full, w_data, r_data);
```

```
    input logic clk, reset, rd, wr;
    output logic empty, full;
    input logic [D_WIDTH-1:0] w_data;
    output logic [D_WIDTH-1:0] r_data;
```

// signal declarations

```
    logic [A_WIDTH-1:0] w_addr, r_addr;
    logic w_en;
```


// enable write only when FIFO is not full

```
    assign w_en = wr & (~full | rd);
```

// instantiate FIFO controller and register file

```
    fifo_ctrl #(A_WIDTH) control (.*);
    reg_file #(D_WIDTH, A_WIDTH) mem (.*);
```

```
endmodule
```

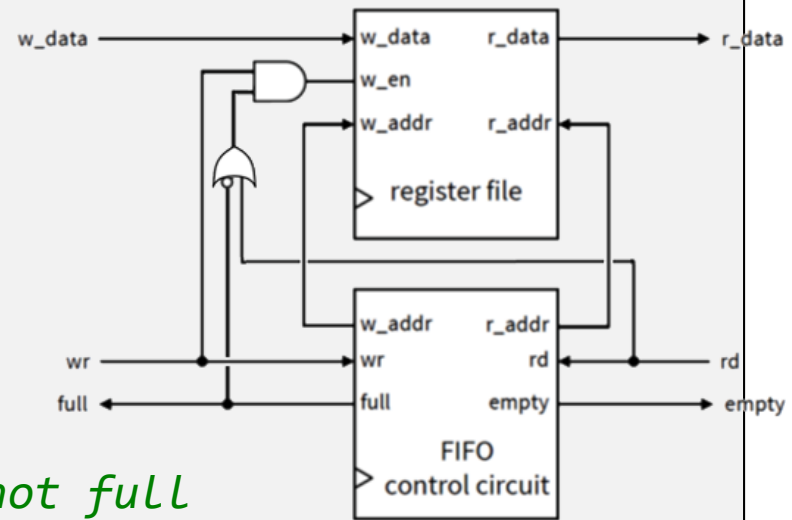

writes when $wr == 1$ and $rd == 1$

Memory Controllers

- ❖ A *memory controller* is an interface circuit between user logic and the physical memory device
 - Abstracts away details of physical memory device while providing a consistent interface to the user
 - The FIFO controller we just discussed allows a user to interface with the register file we implemented on the FPGA's internal memory module
- ❖ Memory controllers are found with all kinds of memory
 - Your DE1-SoC contains memory controllers for SDRAM and DDR3 (and controllers for a bunch of other things like USB, VGA, PS/2, I2C)

DE1-SoC Memory Revisited


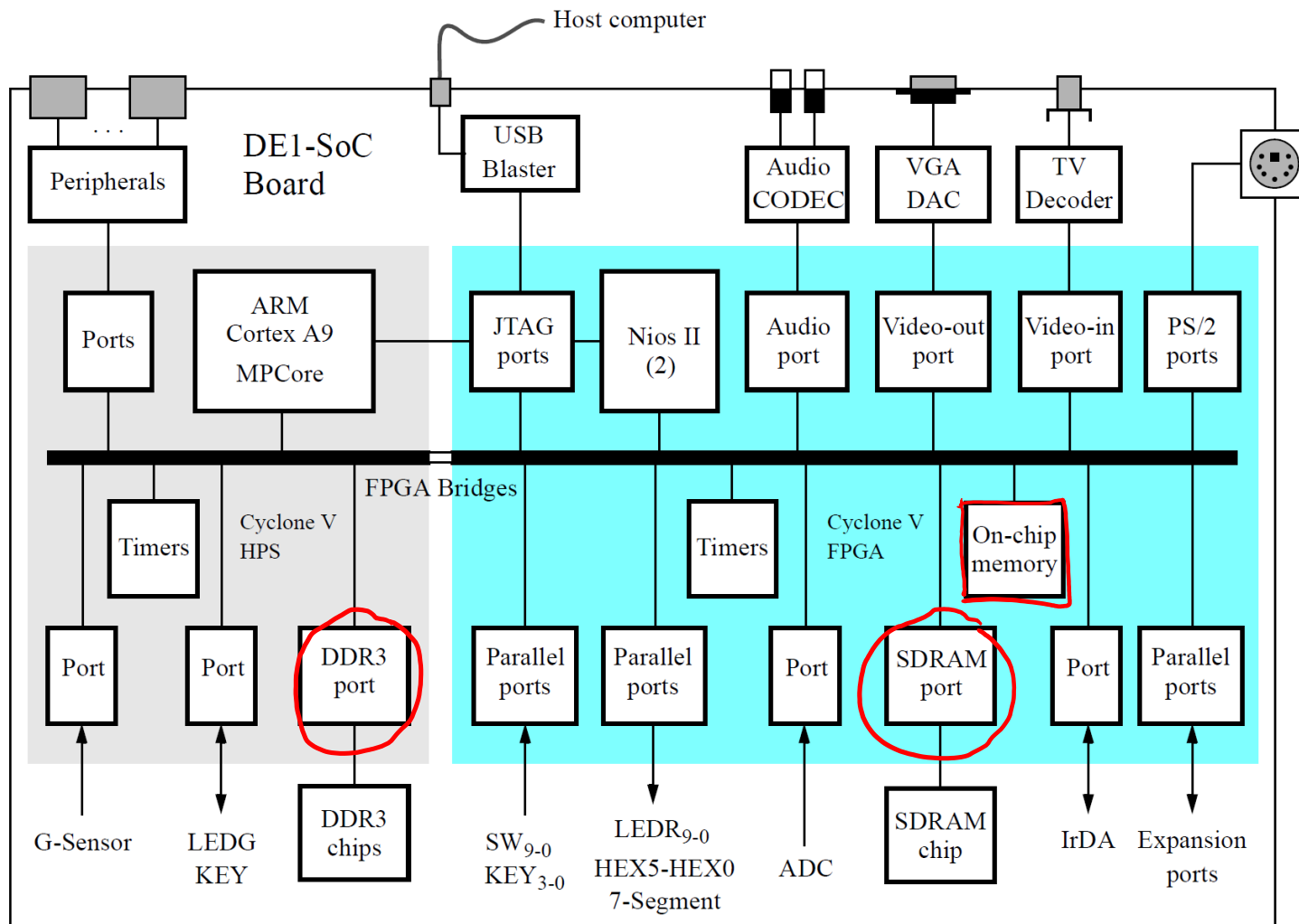


Figure 1. Block diagram of the DE1-SoC Computer.

SDRAM Controller

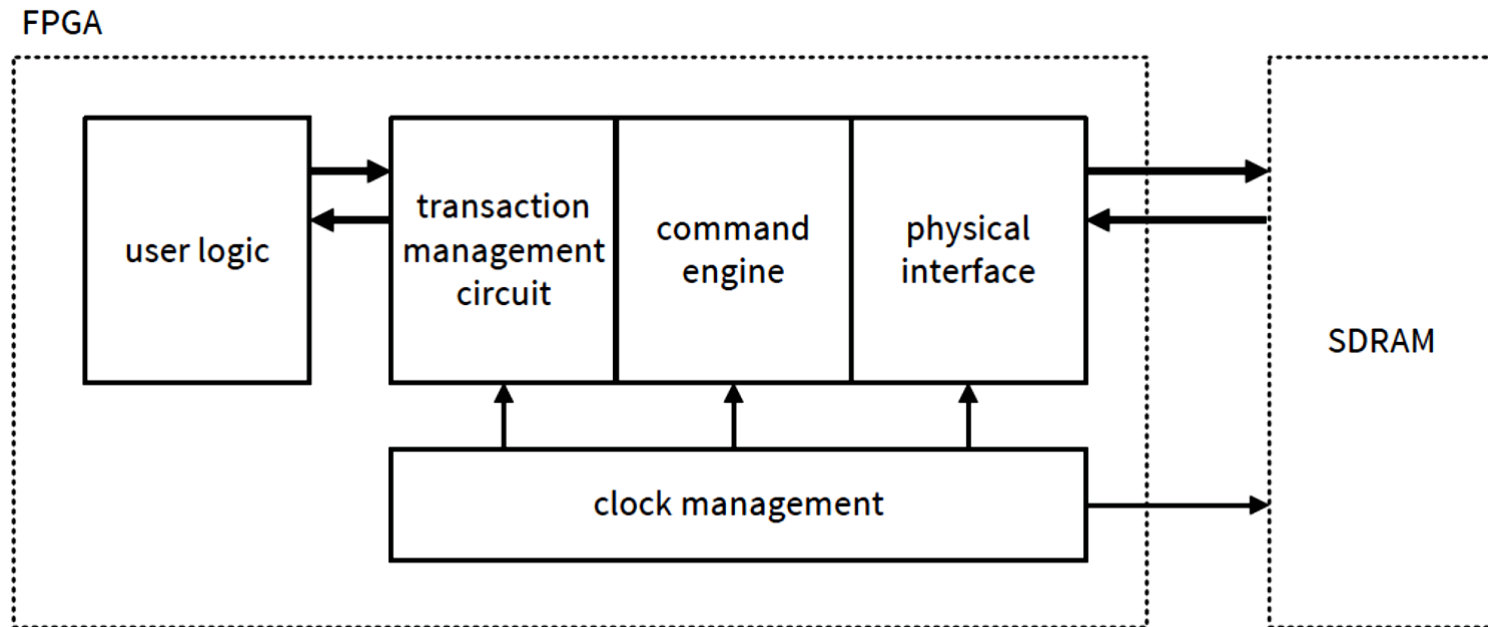

- ❖ High-performance controllers are very complex!
 - Design depends on individual FPGA and SDRAM devices
 - Usually constructed with vendor-supplied IP core