

Design of Digital Circuits and Systems

Algorithmic State Machines

Instructor: Justin Hsia

Teaching Assistants:

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder

Lancelot Wathieu


Matthew Hung

Relevant Course Information

- ❖ Homework 2 due Wednesday (4/10)
- ❖ Homework 3 released today, due next Friday (4/19)
- ❖ Lab 2 reports due 4/12, demos 4/15-19
- ❖ Lab 3 released today, due in two weeks (4/26)
 - Lab 3 + 4 are really ~1.5 weeks long, so don't wait!
- ❖ Quiz 2 not until *next* Thursday (4/18)
 - Spacing between material and quiz will get longer and longer; make sure to give time to review

Lab 3 Notes

 - ❖ More practical **applications of memory** on the DE1-SoC using **audio generation and filtering**
 - Task 2: ROM with MIF file to generate audio
 - Task 3: Use a FIFO buffer to implement a noise filter
- ❖ See *Audio_Guide.pdf* in the spec for how to use the LabsLand Audio Interface to send audio input and record audio output:




Lab 3 Notes

- ❖ Example of *communication* as you interface with an audio CODEC (coder/decoder)

- Inputs: read,
write,
writedata_left,
writedata_right

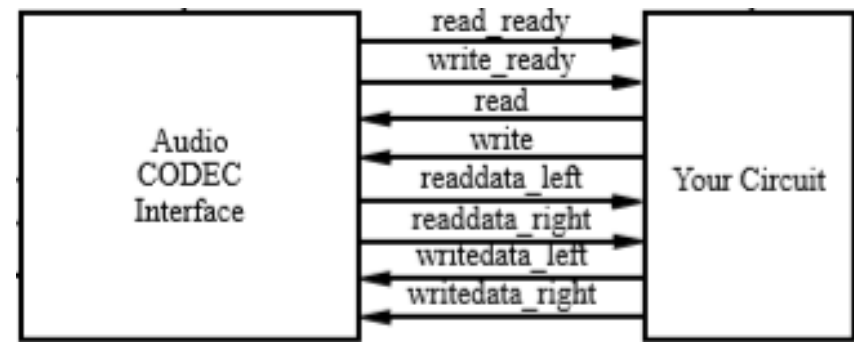
- Outputs: read_ready,
write_ready,
readdata_left,
readdata_right




- **Must wait for both sides (CODEC + your circuit) to be ready for data transmission in either direction!**
 - Data is ready/generated and receiver is ready to accept

Review Question: Decoder

 - ❖ 2:4 binary decoder has 2 select bits that specify which of 4 output bits is high (the others are low) – implement one below using only NOT, AND, and OR gates:




Review Question: DEMUX


 


❖ Implement a 2-bit, 2-to-4 DEMUX:

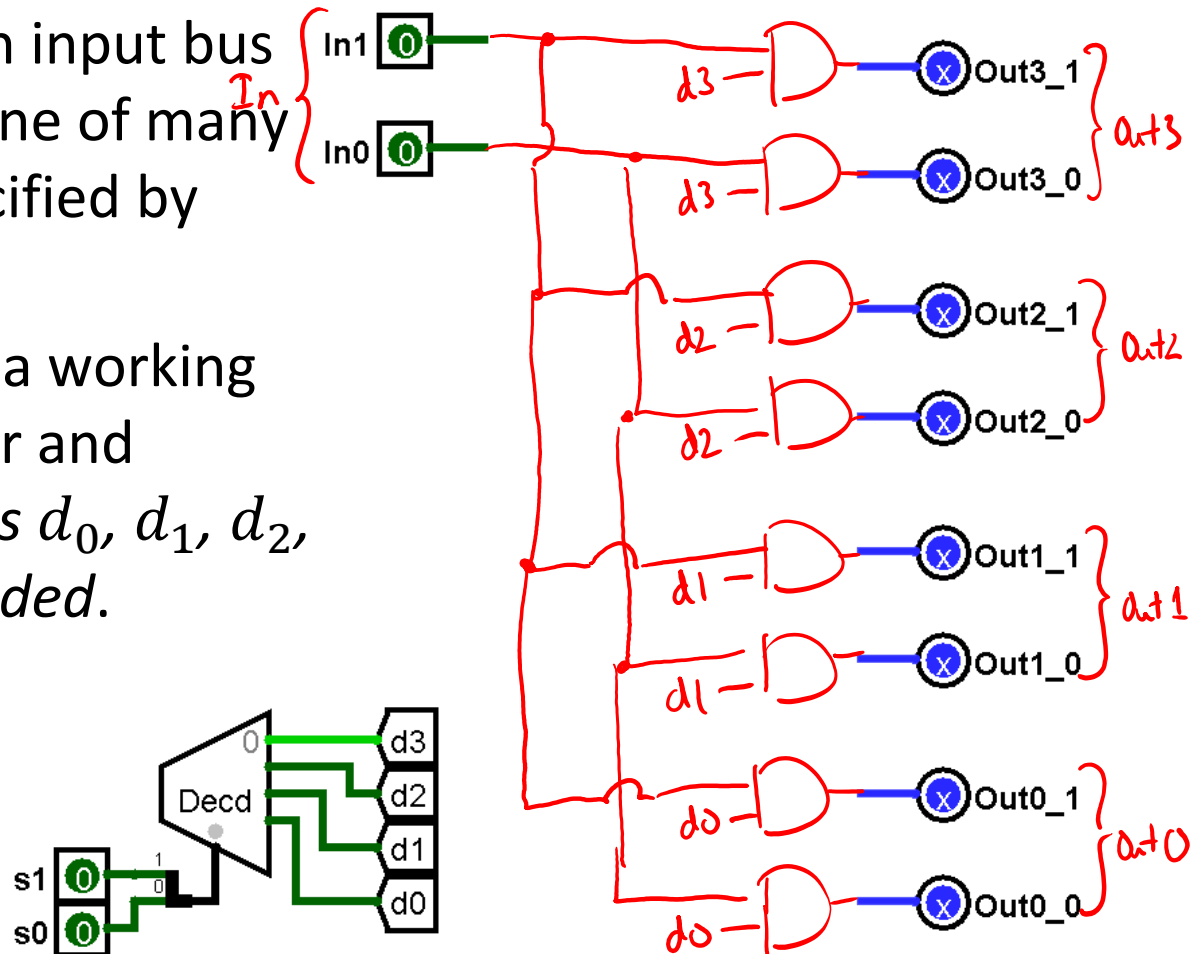- A DEMUX takes an input bus In and connects to one of many output buses specified by selector bits
- Assume you have a working 2:4 binary decoder and write in the signals $d_0, d_1, d_2,$ and d_3 where needed.



Simple Reg File uses DEMUX

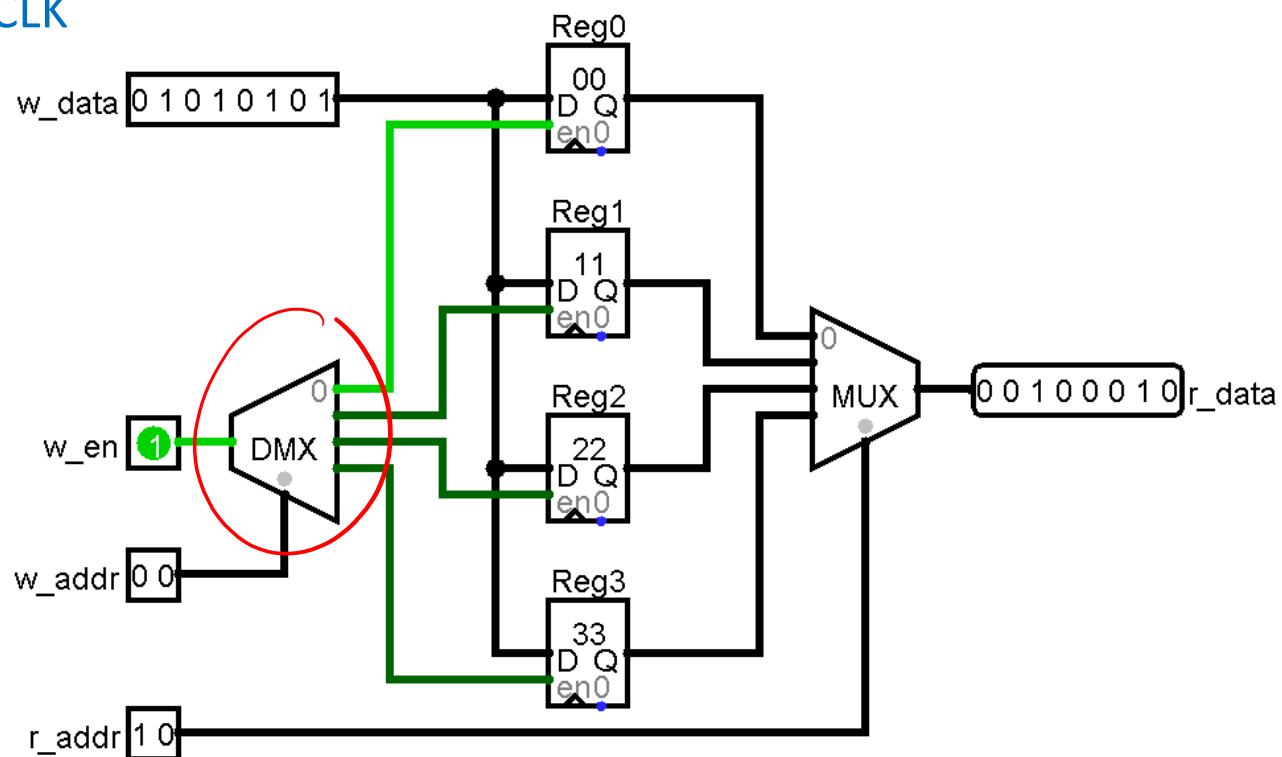 

or a decoder with w-en connected to enable.

Specifying Synchronous Digital Systems

❖ So far:


- SystemVerilog
- Block diagrams
- Finite State Machines
- Circuit/gate diagrams

❖ Issues:

- SV is a specified language (rigid syntax) and can be very abstract (behavioral)
- Block diagrams can be vague or unspecified
- FSMs don't scale well (# of states + transitions)
- Gate-level is too detailed and specific

Algorithmic State Machine (ASM)

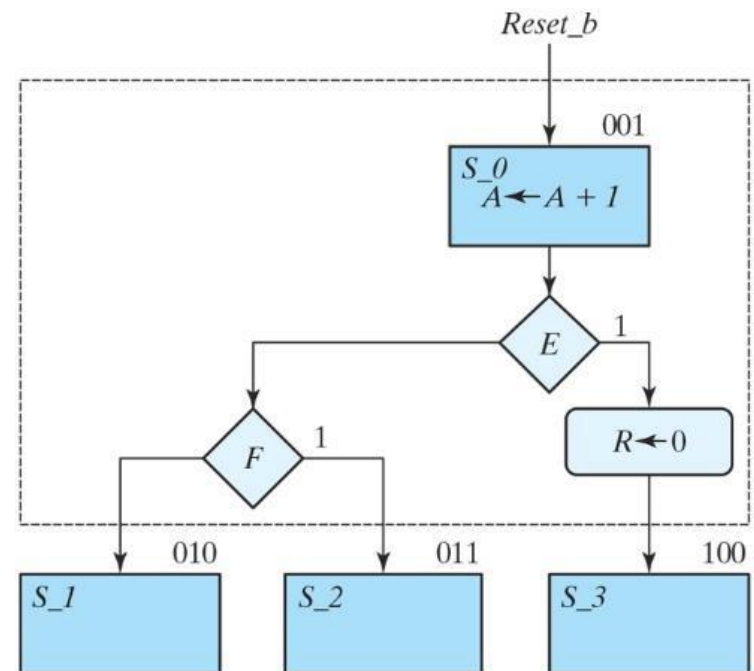- ❖ ASM charts are a method for designing and depicting synchronous digital systems
 - Use more generic syntax (RTL) than SystemVerilog
 - Contain more structured information than FSM state diagrams
- ★ Can more easily design your system from a *hardware algorithm*




Control and Datapath

- ❖ Signal classification in a SDS:
 - *Data*: information manipulated/processed by the system
 - *Control*: signals that coordinate and execute the system operations


- ❖ We can logically separate a SDS into two distinct parts/circuits:

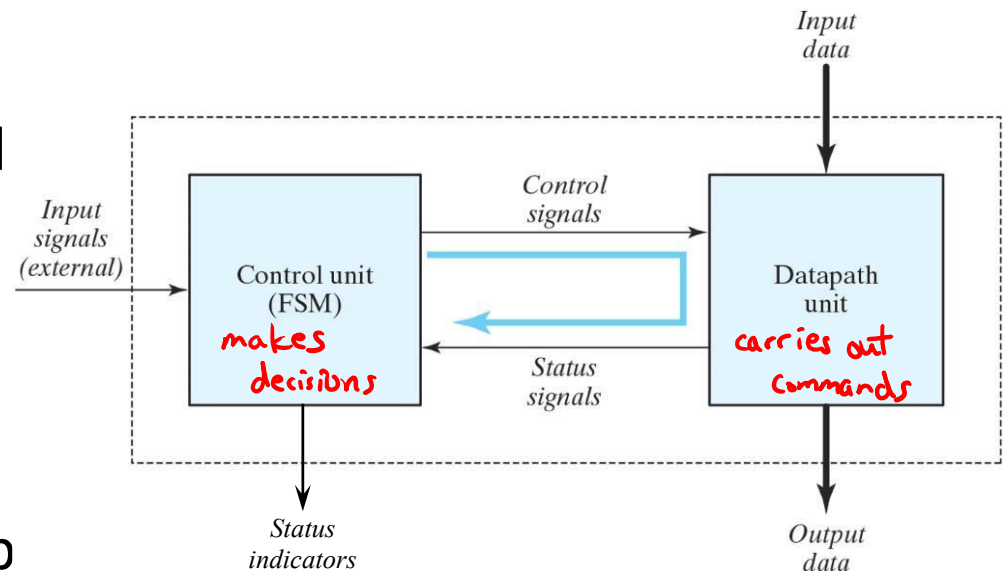- **Datapath**: parts needed for data manipulation (“the brawn”)
- **Control**: logic that tells the datapath what needs to be done (“the b



Control and Datapath: FIFO Buffer

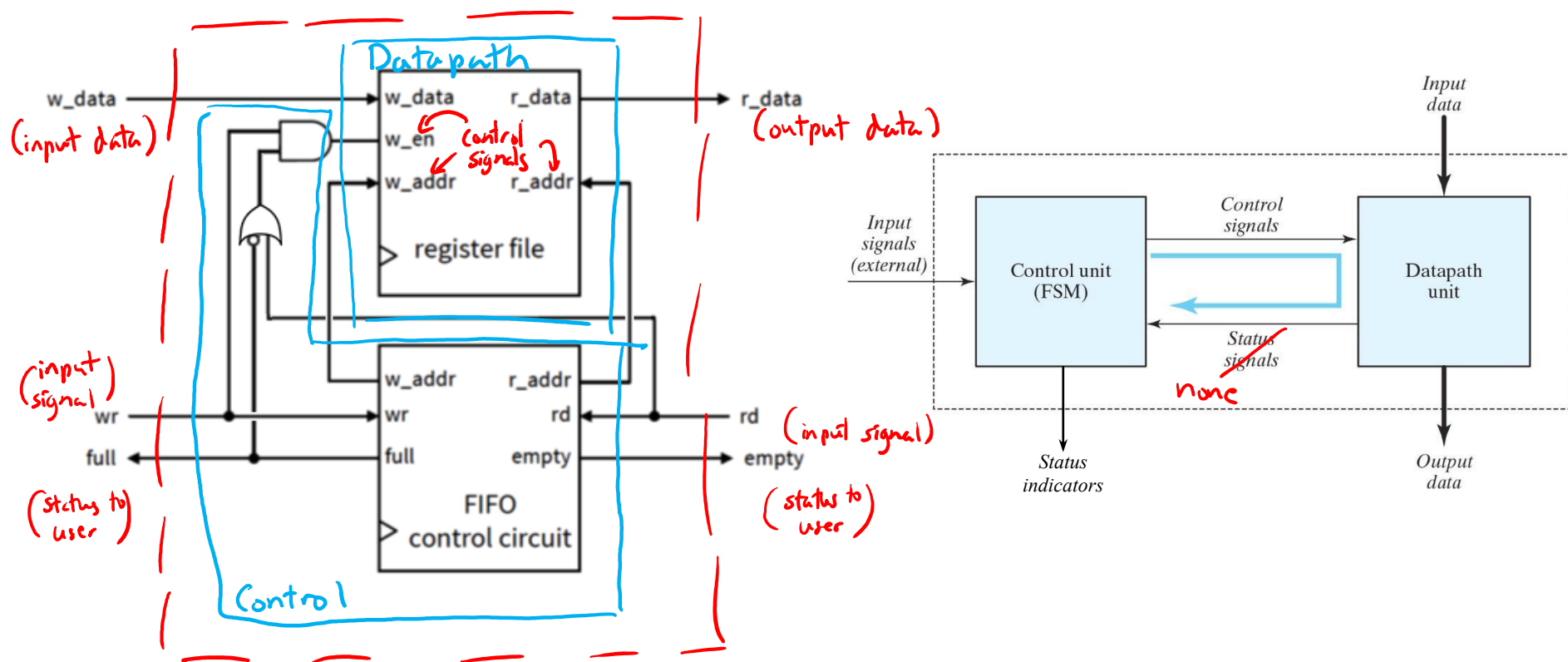- ❖ Circular queue implementation from last lecture:
 - Datapath and control split?




Algorithms for Hardware

- ❖ *Sequential* algorithms:
 - Variables used as symbolic memory locations
 - Sequential execution dictates the ordering of operations
- ❖ Hardware implementation:
 - Registers store intermediate data (variables)
 - Datapath implements all necessary register operations (computations attached to register inputs)
 - A control path FSM specifies the ordering of register operations
- ❖ This design scheme sometimes referred to as **register-transfer level (RTL)** design

Algorithms for Hardware

CL = combinational logic
SL = sequential logic

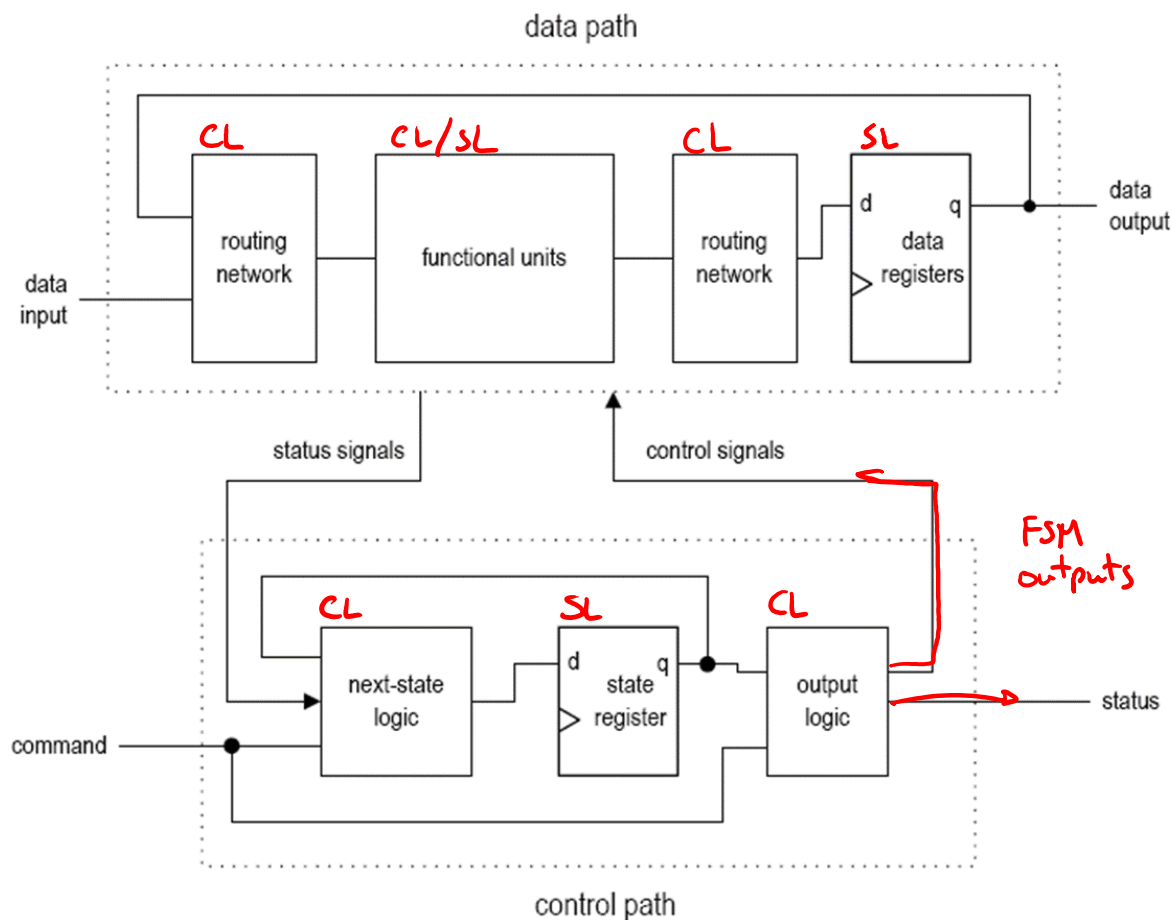- ❖ The resulting system is called an algorithmic state machine (ASM) or FSM with a datapath (FSMD):



RTL Operations

❖ Basic form:

$$r_{\text{dest}} \leftarrow f(r_{\text{src1}}, r_{\text{src2}}, \dots, r_{\text{srcn}})$$

replacement operator

- r_i represent registers and $f()$ represents some combinational function

❖ Examples:


- $r_1 \leftarrow 0$

"clear r_1 "

- $r_2 \leftarrow r_1$

"replace r_2 with the value in r_1 "


- $r_2 \leftarrow r_2 \gg 3$

 

- $i \leftarrow i + 1$

- $d \leftarrow s_1 + s_2 + s_3$

- $y \leftarrow a * a$

 

RTL Operations


❖ Basic form:

$$r_{\text{dest}} \leftarrow f(r_{\text{src1}}, r_{\text{src2}}, \dots, r_{\text{srcn}})$$

- r_i represent registers and $f()$ represents some combinational function

❖ Timing Interpretation:

 - After the start of a clock cycle, the outputs of all registers update and become available
- During the rest of the clock cycle, these outputs propagate through the combinational circuit that performs $f()$
- At the *next* clock trigger/cycle, the result is stored into r_{dest}





RTL Operations

❖ Basic form:

$$r_{\text{dest}} \leftarrow f(r_{\text{src1}}, r_{\text{src2}}, \dots, r_{\text{srcn}})$$


- r_i represent registers and $f()$ represents some combinational function

  ❖ Implementation Example: $a \leftarrow a - b + 1$






Technology Break

ASM Chart

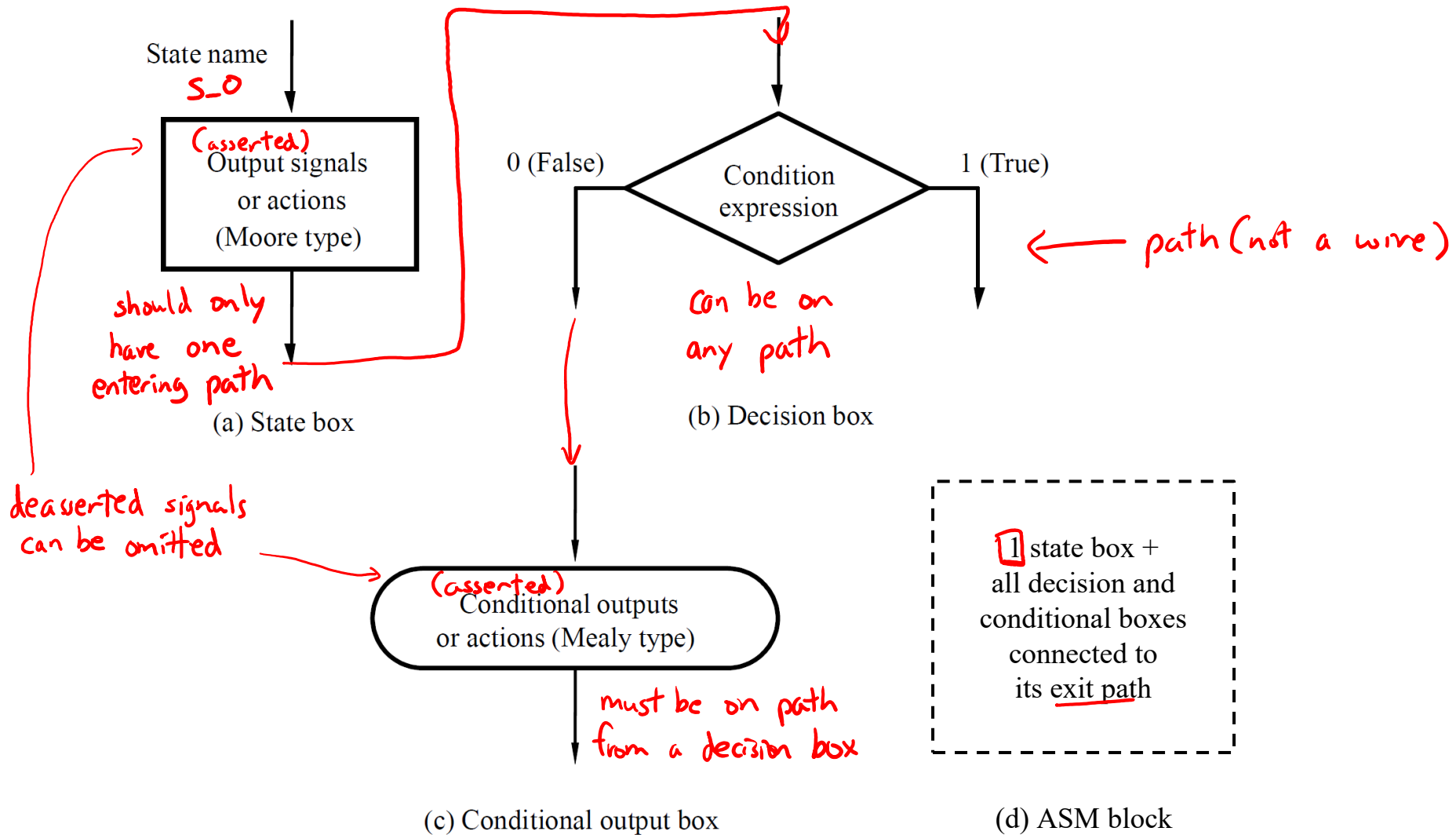


ASM Blocks

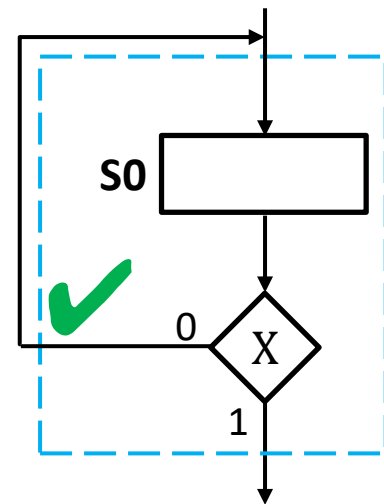  - ❖ Each block describes the state machine operation in a given state
 - For every valid combination of inputs, there must be **exactly one** exit path
 - There should be **no internal feedback**




Worked Example #1

 ❖ Convert this state machine to an ASM chart:




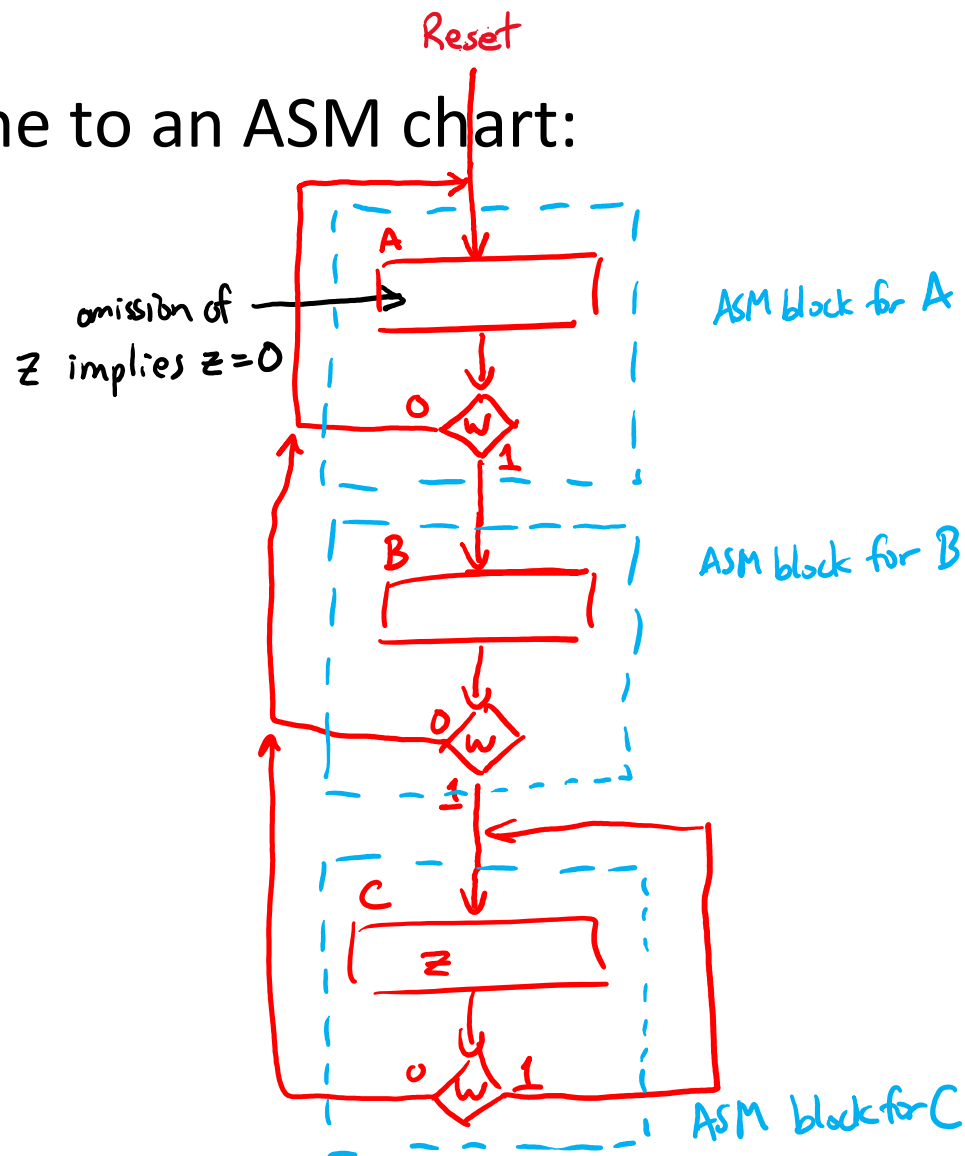Moore Machine
 ↳ no conditional output boxes




Worked Example #2

 - ❖ Convert this state machine to an ASM chart:



Mealy Machine
 ↳ no output signals in state boxes

 omission of conditional output box implies $z=0$




ASM block includes conditional output boxes

Example #3



- ❖ Draw an ASM chart for threeOnes: asserts out iff last 3 values of in were all 1's.

Moore machine
Mealy machine

 

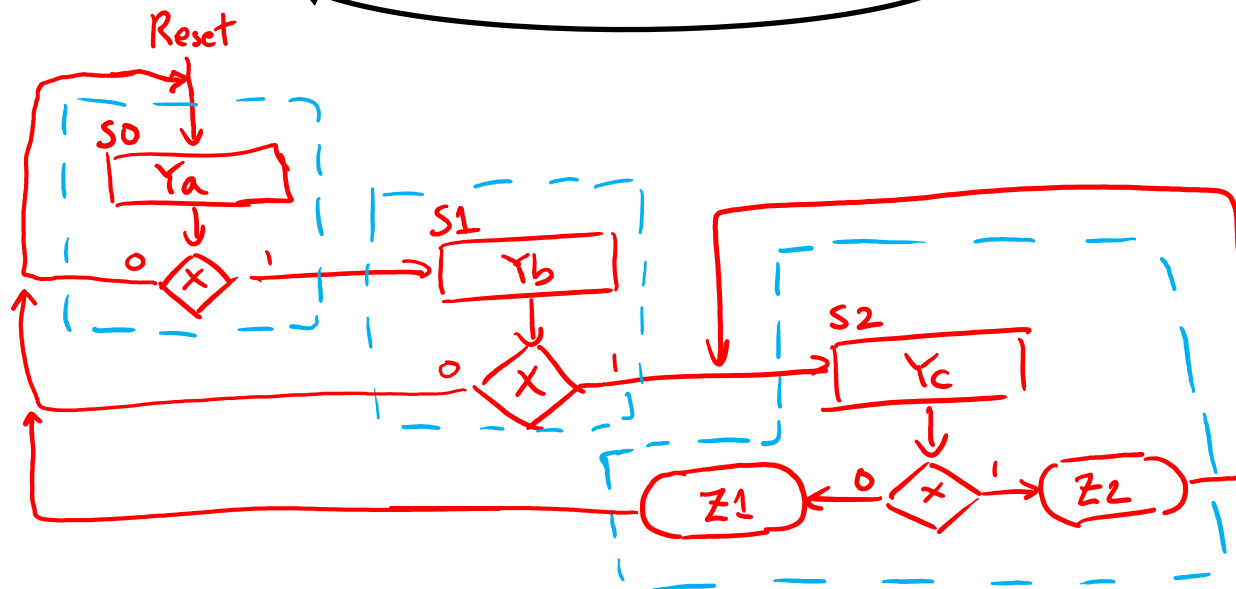 Example #4

- ❖ Convert this state machine to an ASM chart:
 - 1 input: X , 5 outputs: Y_a, Y_b, Y_c (Moore), Z_1, Z_2 (Mealy)



Worked Example #5 (Preview)

- ❖ Convert the ASM chart for a control circuit shown in figure (b) to a state diagram:

