

Design of Digital Circuits and Systems

ASM with Datapath I

Instructor: Justin Hsia

Teaching Assistants:

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder


Lancelot Wathieu

Matthew Hung

Relevant Course Information


- ❖ Homework 2 late deadline tonight (4/11)
- ❖ Homework 3 due next Friday (4/19)
 - FIFO buffers & ASM charts
- ❖ Lab 2 reports due Friday (4/12), demos 4/15-19
 - Same lab demo slots for whole quarter
- ❖ Lab 3 due 4/26
 - Lab 3 + 4 are really ~1.5 weeks long, so don't wait!
- ❖ Quiz 2 next Thursday (4/18)
 - Memory (ROM, RAM, reg files)

Review: ASM Chart

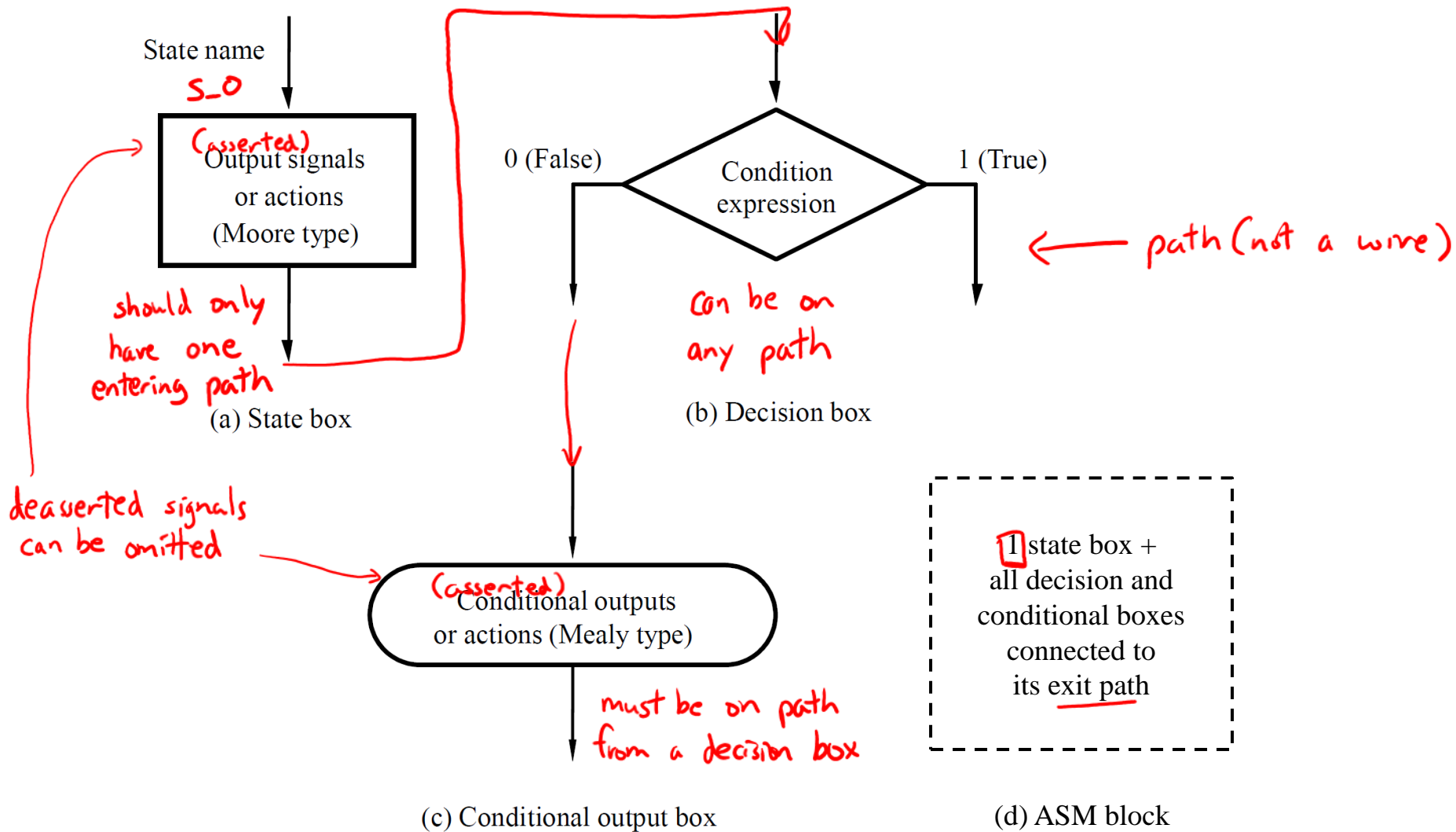


Review Question: 3-way Switch

 - ❖ Create an ASM chart for a 3-way switch system using *Mealy*-type output
 - LTog and RTog pulse 1 when switch is flipped/toggled, output called light



ASMD Charts

 - ❖ An **A**lgorithmic **S**tate **M**achine with a **D**atapath chart is created by adding RTL operations to an ASM chart
 - Timing of operations can be confusing – *NOT* a flowchart
- ❖ School of Thought #1:
 - RTL operations are triggered by control signals, so they can appear anywhere an output signal can:




ASMD Charts

- ❖ An **Algorithmic State Machine** with a **Datapath** chart is created by adding RTL operations to an ASM chart
 - Timing of operations can be confusing – *NOT* a flowchart


- ❖ School of Thought #2:
 - It's clearer to separate control signals (Control) from RTL operations (Datapath)

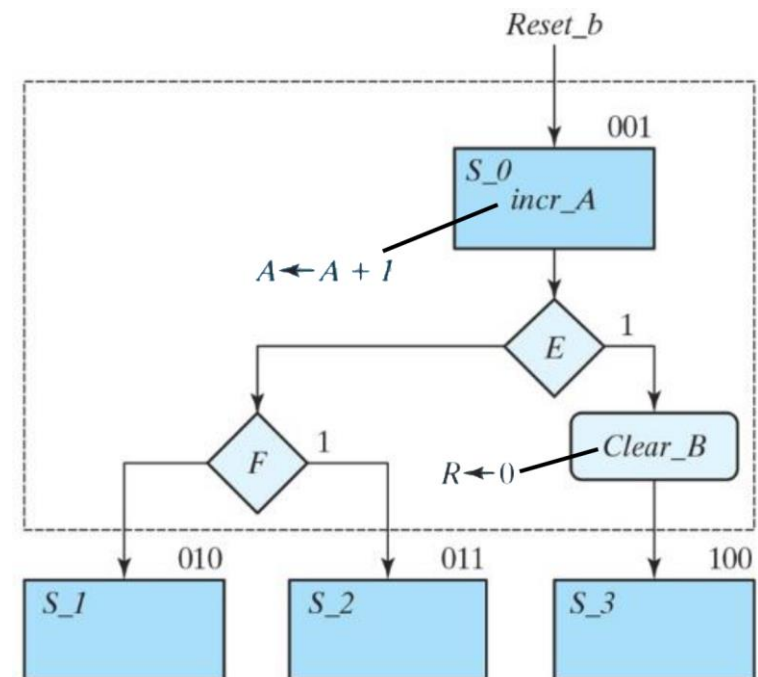- ❖ There isn't a set standard
 - You may see both or variants
 - ***We use School of Thought #2***



ASMD Hardware

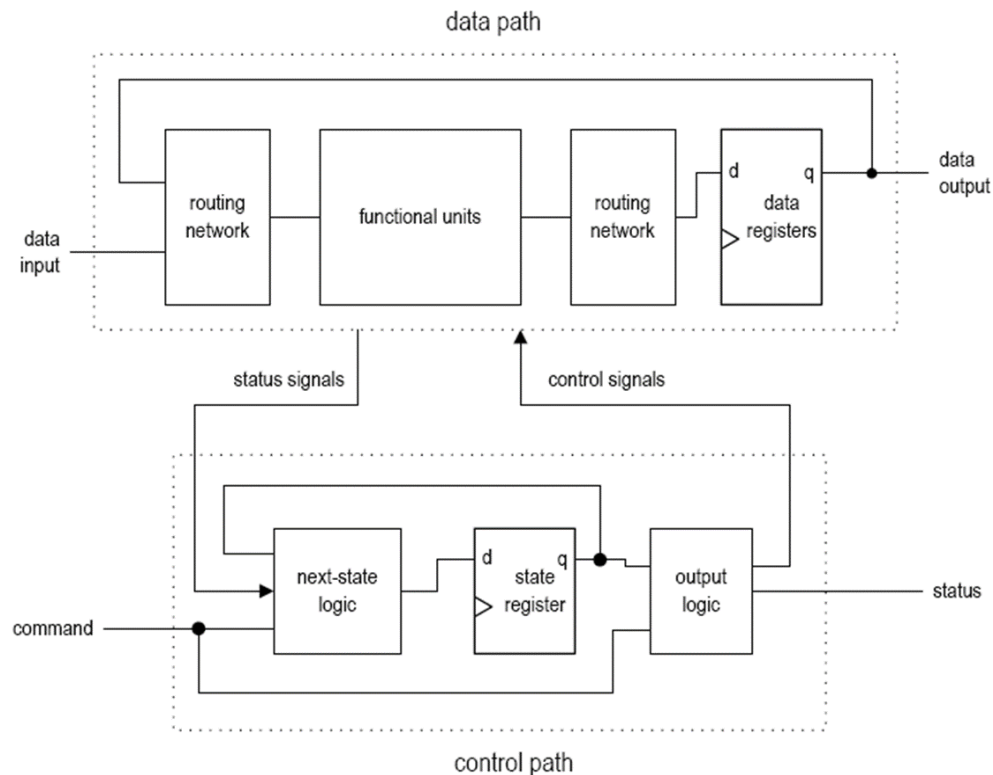- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!




ASMD Hardware

- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!
- ❖ The behavior of both state and data registers depend on the current control state
 - Can conceptually think of as a MUX to the registers' inputs that uses the current state as its selector bits



Hardware Example #1

 - ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





Hardware Example #2

 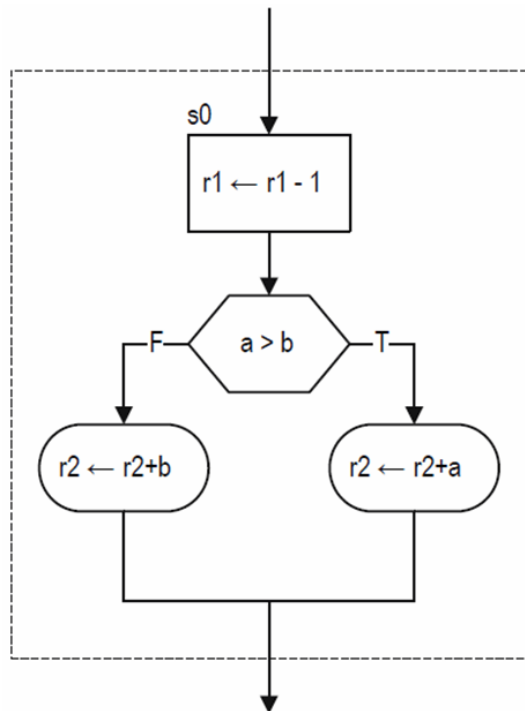- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





ASMD Timing

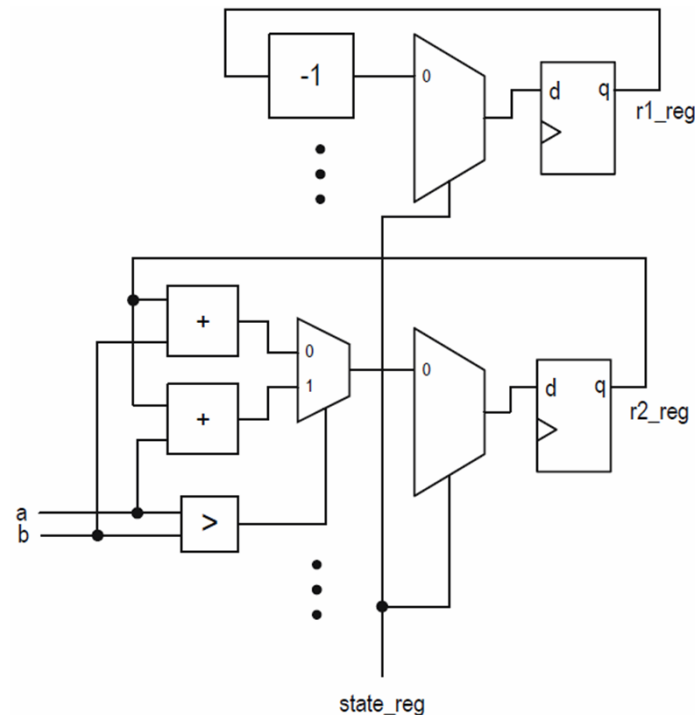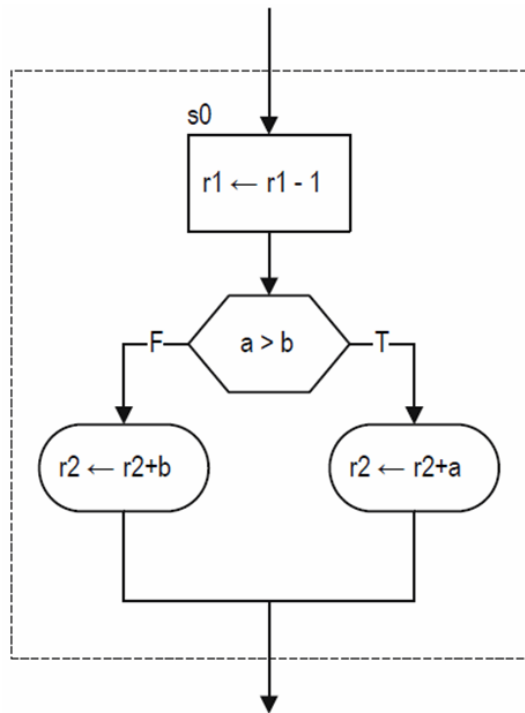- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than *entrance*




ASMD Timing

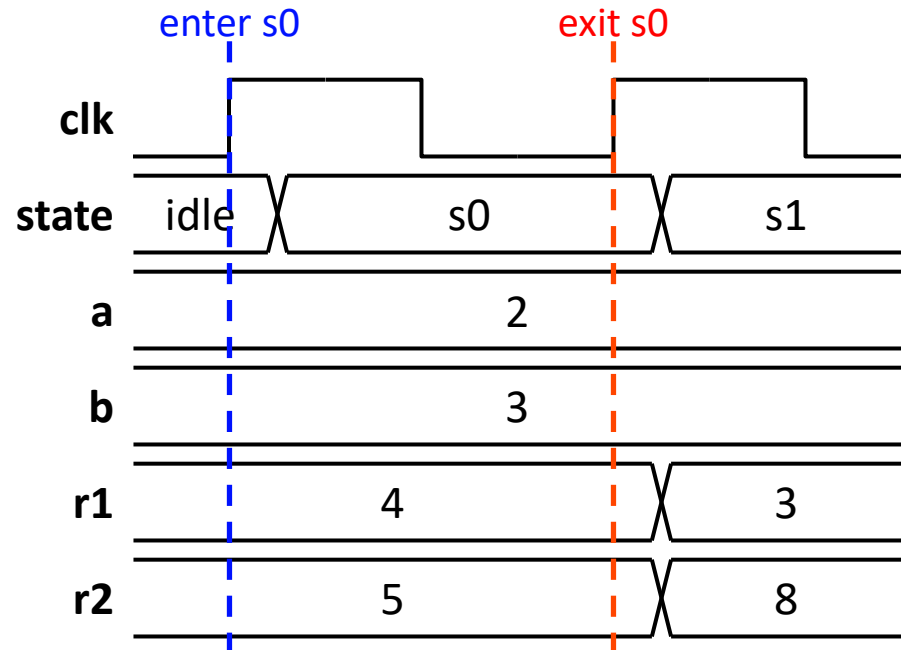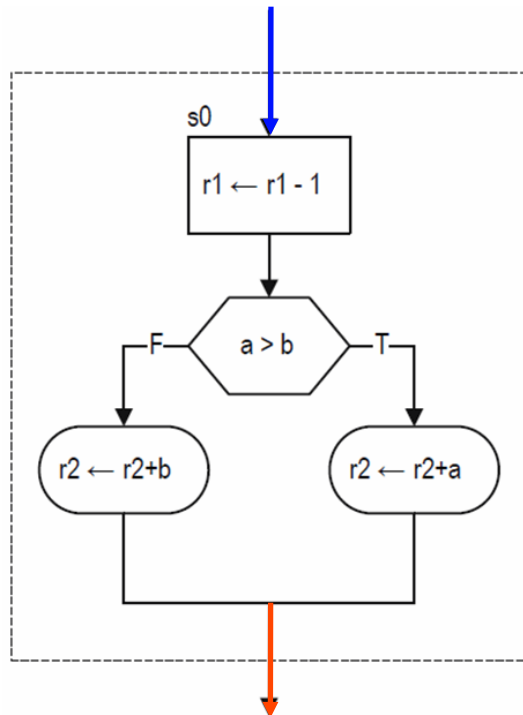- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than *entrance*



ASMD Timing Question

 - ❖ What value will be stored in r when we transition from state $s1$ to the next state? -1, 0, 1



Short Tech Break


ASMD Design Procedure

- ❖ From problem description or algorithm pseudocode:
 - 1) Identify necessary datapath components and operations**
 - 2) Identify states and signals that cause state transitions** (external inputs and status signals), based on the necessary sequencing of operations
 - 3) Name the control signals** that are generated by the controller that cause the indicated operations in the datapath unit
 - 4) Form an ASM chart for your controller**, using states, decision boxes, and signals determined above
 - 5) Add the datapath RTL operations** associated with each control signal

Design Example #1


❖ System specification:

- Flip-flops E and F
- 4-bit binary up-counter $A = 0bA_3A_2A_1A_0$
- Active-low reset signal $reset_b$ puts us in state S_idle , where we remain while signal $Start = 0$
- $Start = 1$ initiates the system's operation by clearing A and F . At each subsequent clock pulse, the counter is incremented by 1 until the operations stop.
- Bits A_2 and A_3 determine the sequence of operations:
 - If $A_2 = 0$, set E to 0 and the count continues
 - If $A_2 = 1$, set E to 1; additionally, if $A_3 = 0$, the count continues, otherwise, wait one clock pulse to set F to 1 and stop counting (*i.e.*, back to S_idle)

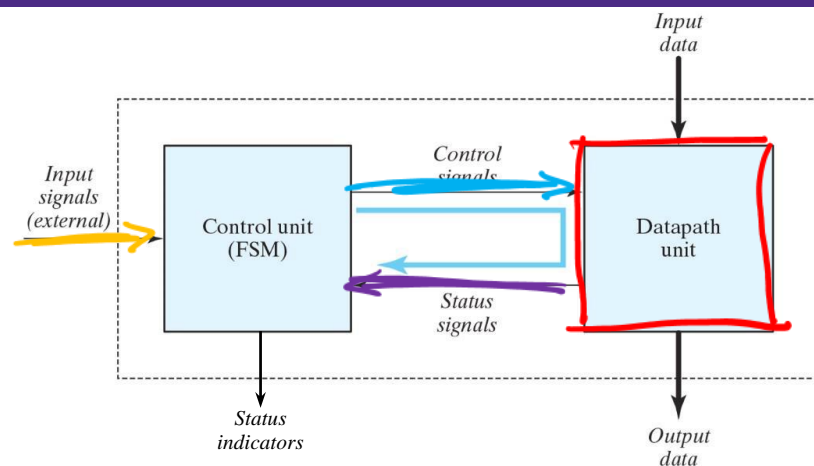

Design Example #1

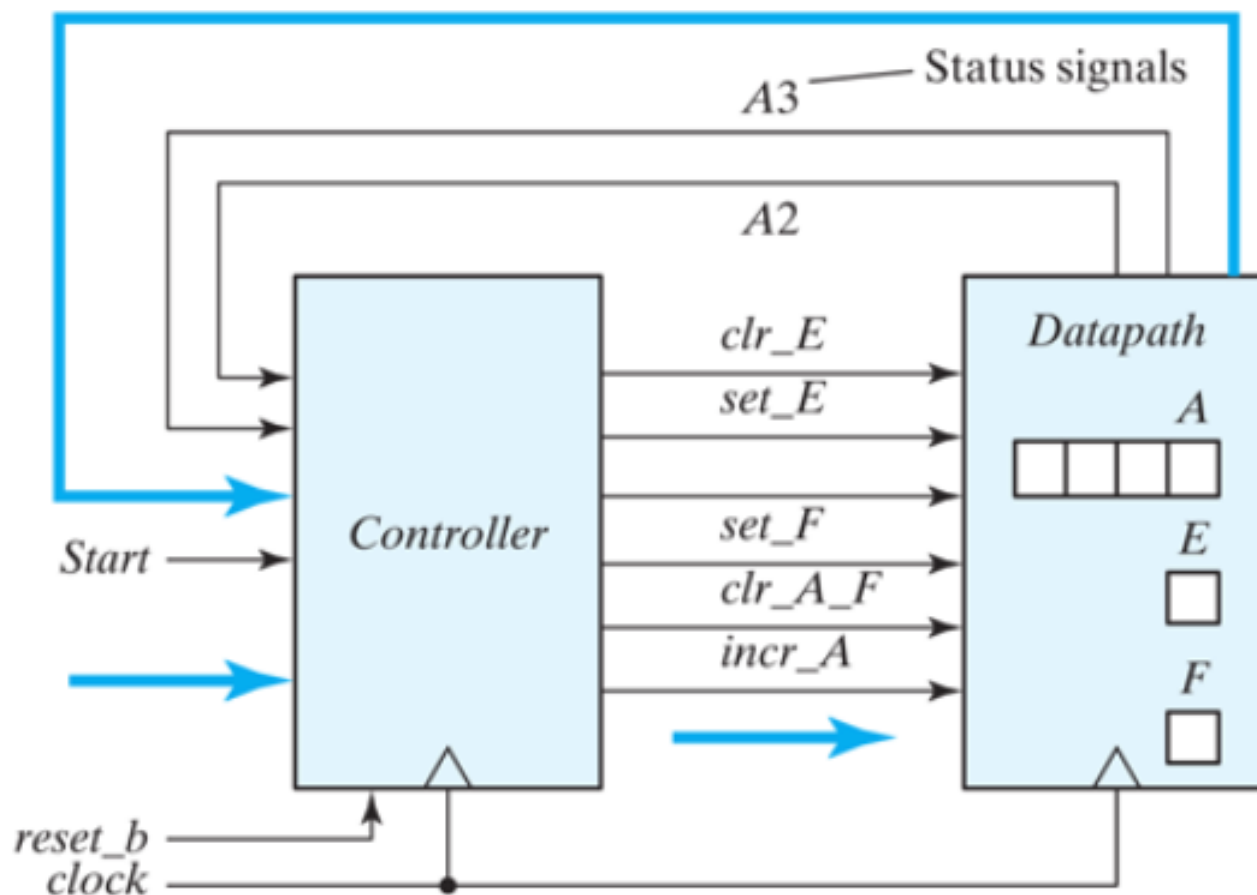- ❖ The system can be represented by the following block diagram:



Design Example #1 (ASM \rightarrow ASMD Chart)

- ❖ Synchronous or asynchronous reset?

Design Example #1 (Timing)

❖ Sequence of operations:

Counter				Flip-Flops		Conditions	State
A_3	A_2	A_1	A_0	E	F		
X	X	X	X	1	X	<i>Start</i>	<i>S_idle</i>
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	<i>S_count</i>
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	
1	1	0	1	1	0		
1	1	0	1	1	1		
1	1	0	1	1	1		

Design Example #1 (Logic)

❖ Controller:

■ State Table:

Present-State Symbol	Present State		Inputs			Next State		Outputs				
	P_1	P_0	Start	A_2	A_3	N_1	N_0	set_E	clr_E	set_F	clr_A_F	incr_A
S_idle	0	0	0	X	X	0	0	0	0	0	0	0
S_idle	0	0	1	X	X	0	1	0	0	0	1	0
S_count	0	1	X	0	X	0	1	0	1	0	0	1
S_count	0	1	X	1	0	0	1	1	0	0	0	1
S_count	0	1	X	1	1	1	1	1	0	0	0	1
S_F	1	1	X	X	X	0	0	0	0	1	0	0

■ Logic:

$$\begin{aligned}
 N_1 &= & set_F &= \\
 N_0 &= & clr_A_F &= \\
 set_E &= & incr_A &= \\
 clr_E &= & &=
 \end{aligned}$$

Short Tech Break

Design Example #1 (SV, Controller)

```
module controller (set_E, clr_E, set_F, clr_A_F,  
                 incr_A, A2, A3, Start, clk,  
                 reset_b);  
  
    // port definitions  
    input  logic Start, clk, reset_b, A2, A3;  
    output logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // define state names and variables  
  
    // controller logic w/synchronous reset
```

Design Example #1 (SV, Controller)

```
// next state logic
```

```
// output assignments
```

```
endmodule // controller
```

Design Example #1 (SV, Datapath)

```
module datapath (A, E, F, clk, set_E, clr_E, set_F, clr_A_F,
                incr_A);

    // port definitions
    output logic [3:0] A;
    output logic E, F;
    input  logic clk, set_E, clr_E, set_F, clr_A_F, incr_A;

    // datapath logic

endmodule // datapath
```


Design Example #1 (SV, Top-Level Design)

```
module top_level (A, E, F, clk, Start, reset_b);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input  logic clk, Start, reset_b;  
  
    // internal signals  
    logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // instantiate controller and datapath  
    controller c_unit (.set_E, .clr_E, .set_F,  
                     .clr_A_F, .incr_A, .A2(A[2]),  
                     .A3(A[3]), .Start, .clk,  
                     .reset_b);  
  
    datapath d_unit (.*);  
  
endmodule // top_level
```