

# Design of Digital Circuits and Systems

## Algorithms to Hardware II, Timing Review

**Instructor:** Justin Hsia

**Teaching Assistants:**

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder

Lancelot Wathieu

Matthew Hung



# Relevant Course Information

- ❖ Anonymous mid-quarter survey on Canvas (due 4/29)
- ❖ Homework 4 due on Monday (4/29)
- ❖ Lab 3 due Friday (4/26)
- ❖ Lab 4 due next Friday (5/3)
- ❖ Lab 5 will be released next week, due 5/17
- ❖ Quiz 3 (ASM, ASMD) next Thursday (5/2)


# Outline

- ❖ **Algorithm → Hardware Wrap-up**
- ❖ Timing Constraints Review

# Sorting Algorithm (ASMD Chart)

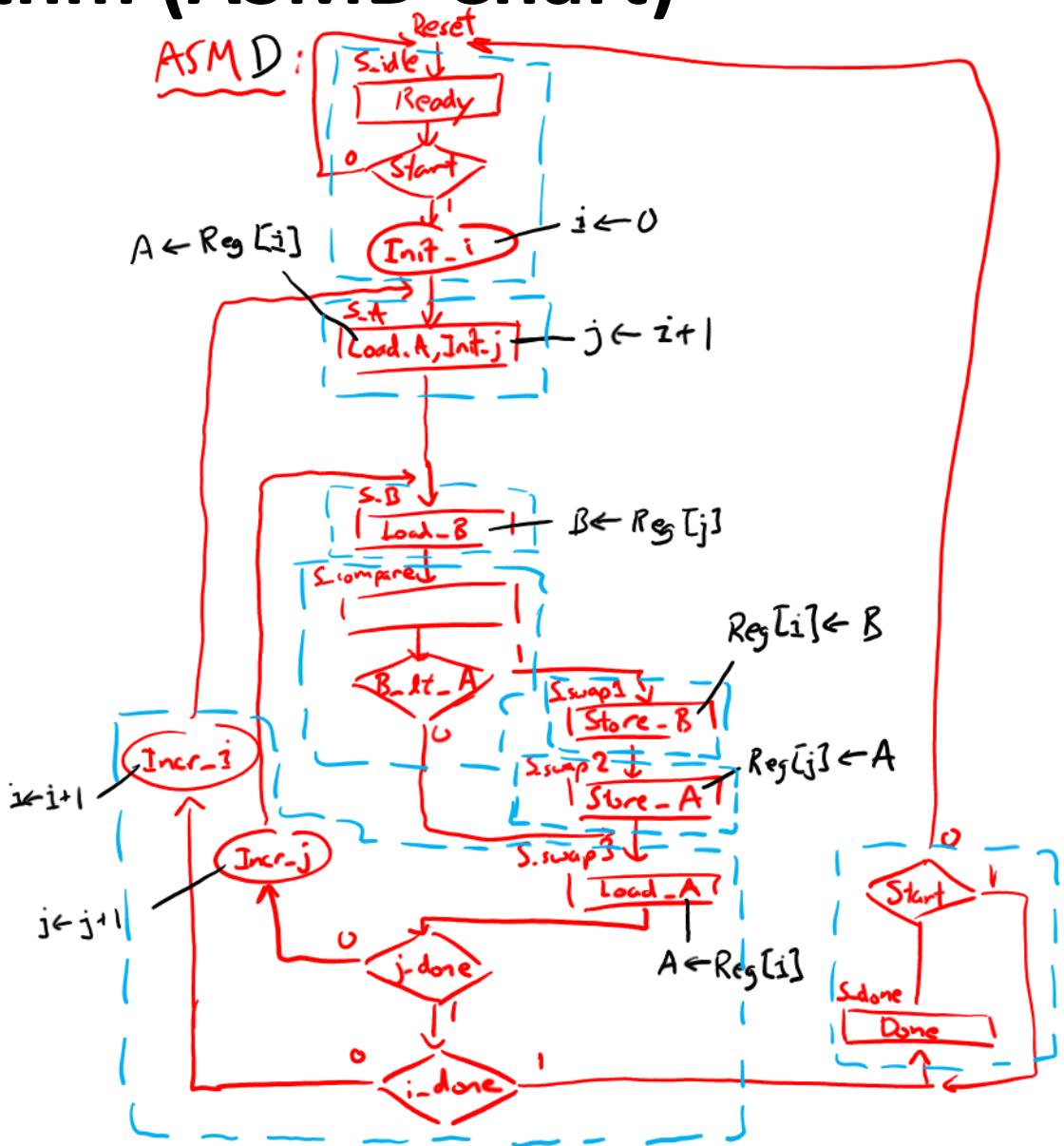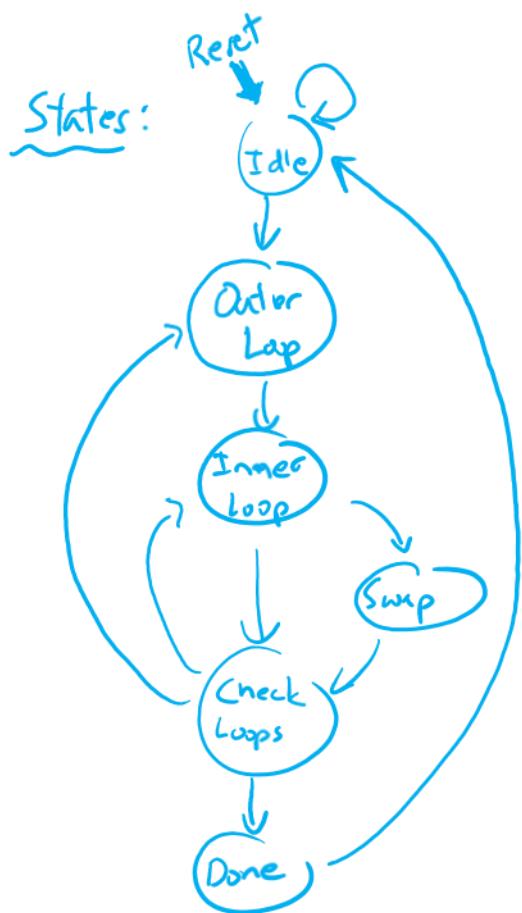

# Sorting Algorithm Datapath

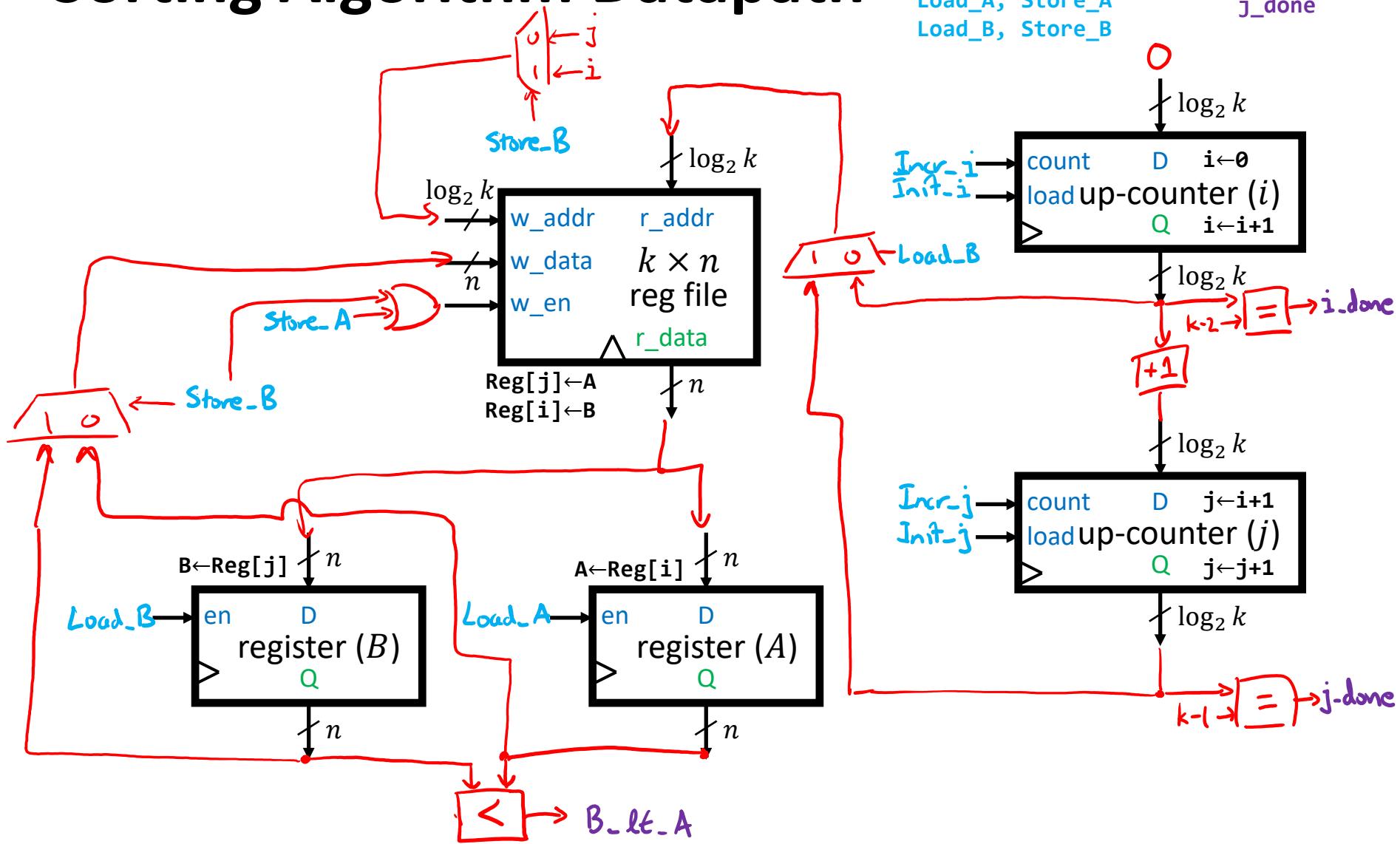


# isPrime Algorithm

- ❖ Design a sequential circuit that determines if an input **Num** is a prime number (e.g., 2, 3, 5, 7) or not
  - **Num** has width  $w$ , output **P** is 1 (prime) or 0 (not prime)
  - Assume the usual **Ready**, **Done**, **Start**, **Reset**
- ❖ Algorithm:

```
N = Num
copy of
input Num
so we can't
change it during
the algorithm
if N < 3 do          // handle special cases
    return (N == 2)
for F = 2 to N/2 do  // factor to check
    if (N % F == 0) do
        return 0         // factor found, not a prime
    endif
endfor
return 1              // no factors found, is prime
```


# isPrime (ASMD Chart)

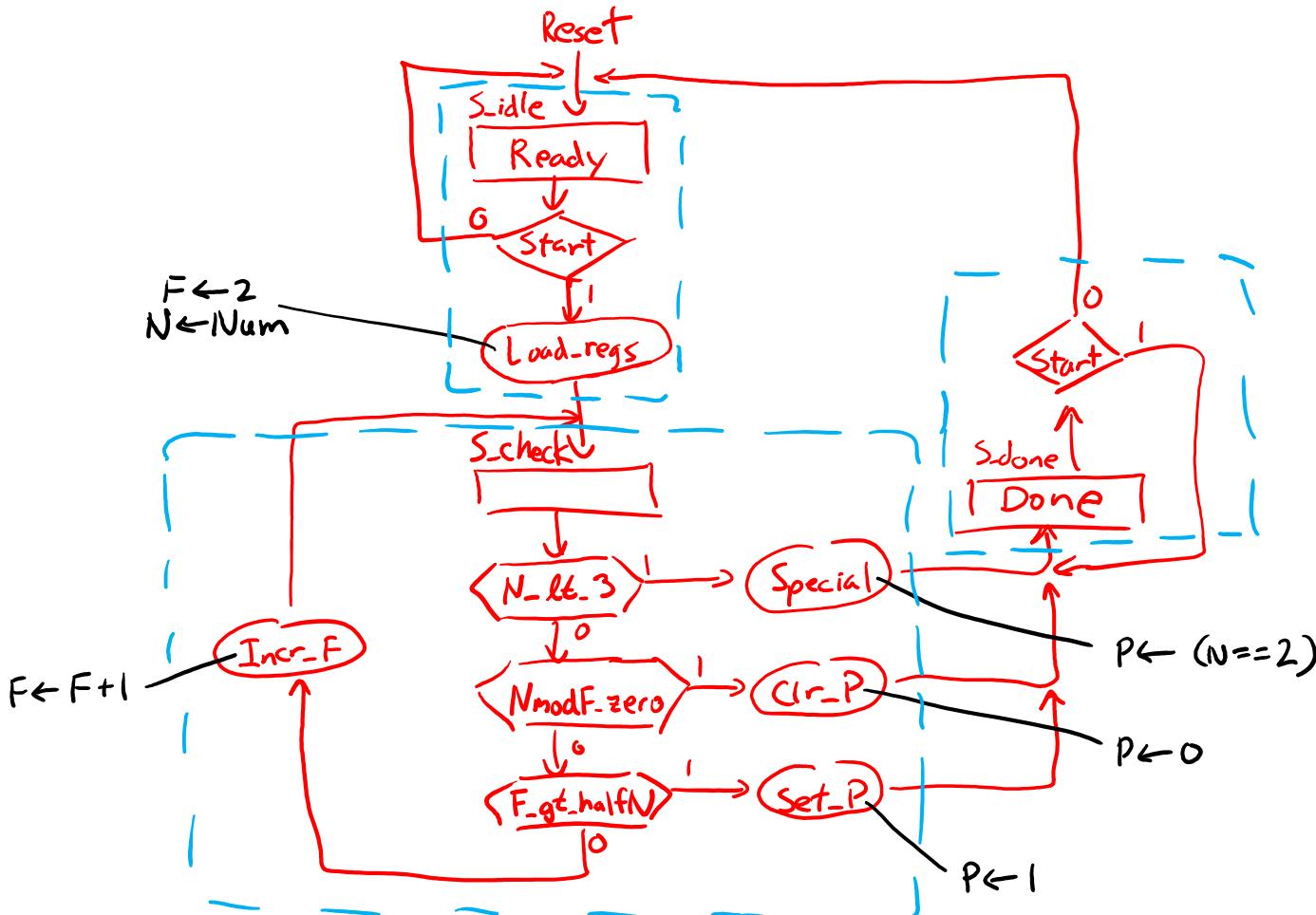

## Alternatives:

- **Incr\_F** could be Moore output on **S\_check**
- **Special** could be extra decision box on **N=2** that uses **Clr\_P** & **Set\_P** on its outbound paths
- **N\_lt\_3** check could be done in **S\_idle**

# isPrime (Block Diagram)

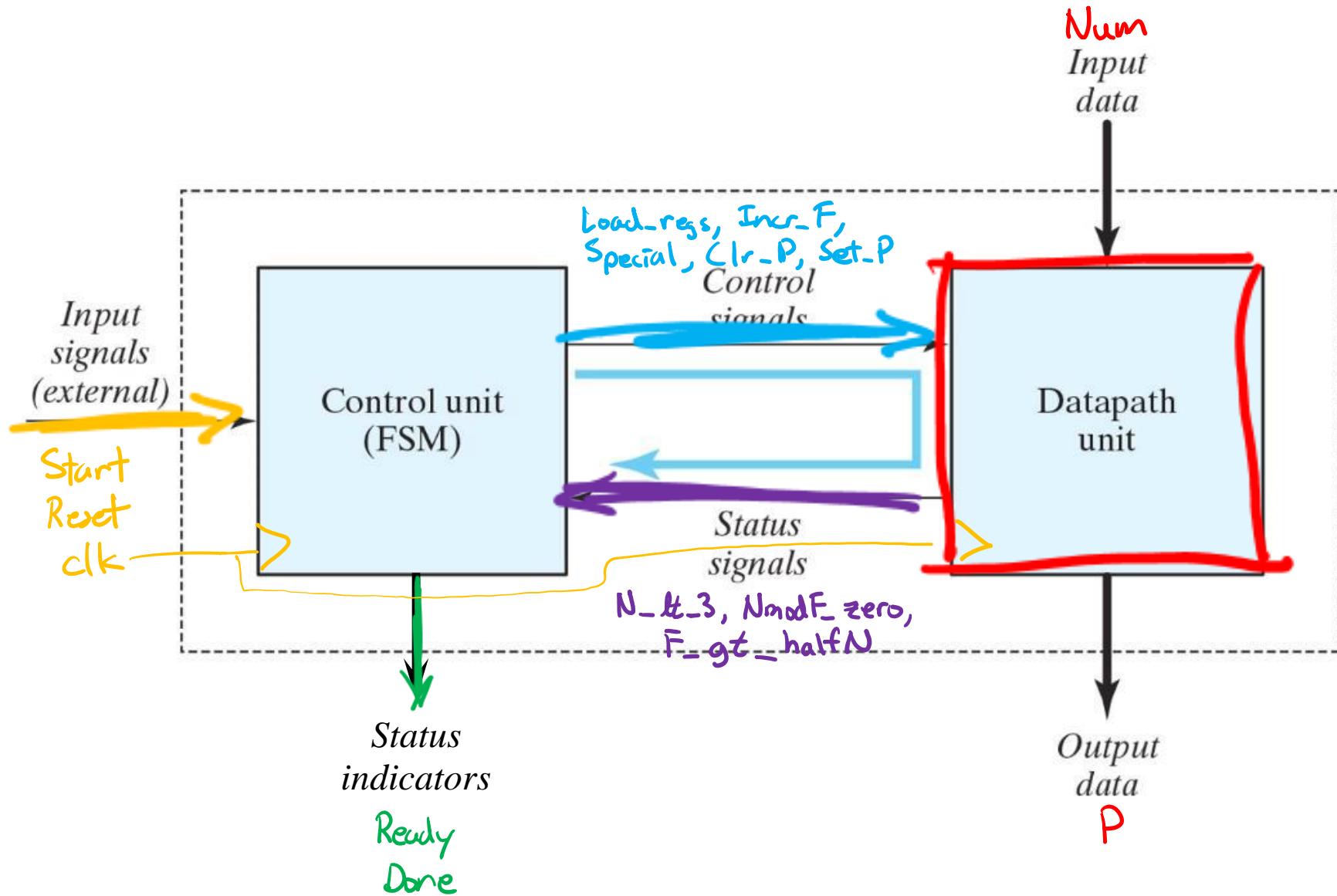

# Short Tech Break

# isPrime Live Coding Demo

```
isPrime_control:
```

```
    // port definitions  
    // define state names and variables  
    // controller logic w/synchronous reset  
    // next state logic  
    // output assignments
```

```
isPrime_datapath:
```

```
    // port definitions  
    // internal datapath signals and registers  
    // datapath logic  
    // output assignments
```

```
isPrime:
```

```
    // port definitions  
    // define status and control signals  
    // instantiate control and datapath
```

# Basic Testbench Review

- ❖ How to start a testbench:
  - 1) Create a <name>\_tb module with no ports
  - 2) Create variables that match the module's ports
  - 3) Instantiate an instance of the module can call it dut or uut
  - 4) If needed, create a simulated clock
  - 5) Create an **initial** block to define your test inputs
  
- ❖ Tools we know about:
  - Timing controls: #<time>;, @(posedge <signal>);
  - Loops: **integer i;** **for (i = 0; i < 2\*\*3; i++)**  
**repeat (2\*\*4)**

# Testing Your Algorithm

- ❖ Create a testbench for our `isPrime` module:

```
module isPrime_tb ();  
    // define parameters  
  
    // define module port connections  
  
    // instantiate module  
  
    // create simulated clock  
  
    //define test inputs  
  
endmodule
```

# Testing Your Algorithm

- ❖ Create a testbench for our `isPrime` module:
  - Single Num value (arbitrary wait):

```
// define test inputs

initial begin
    Num = 3;      // test value
    Reset = 1;    // reset system
    Start = 0;    // idle
    Start = 1;    // start computation
    Start = 0;

    repeat (2**4) // make sure we don't get stuck in S-done
        @(posedge clk); // wait 16 clock cycles

    @(posedge clk); // extra cycle of output
    $stop();
end
```

Annotations:

- Num value (arbitrary wait): A red bracket underlines "Num" and "wait".
- test value: A red annotation above "Num = 3;".
- reset system: A red annotation above "Reset = 1;".
- idle: A red annotation above "Start = 0;".
- start computation: A red annotation above "Start = 1;".
- make sure we don't get stuck in S-done: A red annotation above the "repeat" loop.
- wait 16 clock cycles: A red annotation above the first "@(posedge clk);".
- extra cycle of output: A red annotation above the second "@(posedge clk);".

# Testing Your Algorithm

- ❖ Create a testbench for our `isPrime` module:

- Single `Num` value (check `Ready`):

*Done also works, but detects  
1 cycle earlier*

```
// define test inputs

initial begin
    Num = 3;
    Reset = 1; Start = 0; @(posedge clk);
    Reset = 0; @(posedge clk);
    Start = 1; @(posedge clk);
    Start = 0;

    // wait until module says it's ready
    @(posedge Ready); // wait until module says it's ready

    @(posedge clk); // extra cycle of output
    $stop();
end
```

# Testing Your Algorithm

- ❖ Create a testbench for our `isPrime` module:
  - All `Num` values:

```
// define test inputs
integer i;
initial begin
    Reset = 1; Start = 0; @(posedge clk);           // reset system
    Reset = 0;                                     @(posedge clk);           // idle
    for (i = 0; i < 2**W; i++) begin
        Start = 1; Num = i; @(posedge clk);          // loop through all Num's
        Start = 0;                                     @(posedge Ready);      // set Num & start computation
    end                                              // wait until Ready again
                                                    // extra cycle of output
                                                    $stop();
end
```

The code is annotated with red comments explaining its purpose:

- `// reset system`
- `// idle`
- `// loop through all Num's`
- `// set Num & start computation`
- `// wait until Ready again`

# Testing Your Algorithm: \$display

- ❖ Triggers once when encountered, prints the given format string and adds a new line:

```
// define test inputs
integer i;
initial begin
    Reset = 1; Start = 0; @(posedge clk);
    Reset = 0; @(posedge clk);
    for (i = 0; i < 2**W; i++) begin
        Start = 1; Num = i; @(posedge clk);
        Start = 0; @(posedge Ready);
    {
        $display("T = %4t, isPrime(%2d) = %s",
                $time, Num, P ? "Yes" : "No ");
        current simulation time
    end
    @(posedge clk); // extra cycle of output
    $stop();
end
```

```
VSIM 4> run -all
# T = 90, isPrime( 0) = No
# T = 150, isPrime( 1) = No
# T = 210, isPrime( 2) = Yes
# T = 270, isPrime( 3) = Yes
# T = 330, isPrime( 4) = No
# T = 410, isPrime( 5) = Yes
# T = 470, isPrime( 6) = No
# T = 570, isPrime( 7) = Yes
# T = 630, isPrime( 8) = No
# T = 710, isPrime( 9) = No
# T = 770, isPrime(10) = No
# T = 910, isPrime(11) = Yes
# T = 970, isPrime(12) = No
# T = 1130, isPrime(13) = Yes
# T = 1190, isPrime(14) = No
# T = 1270, isPrime(15) = No
```


# Short Tech Break

# Outline

- ❖ Algorithm → Hardware Wrap-up
- ❖ **Timing Constraints Review**
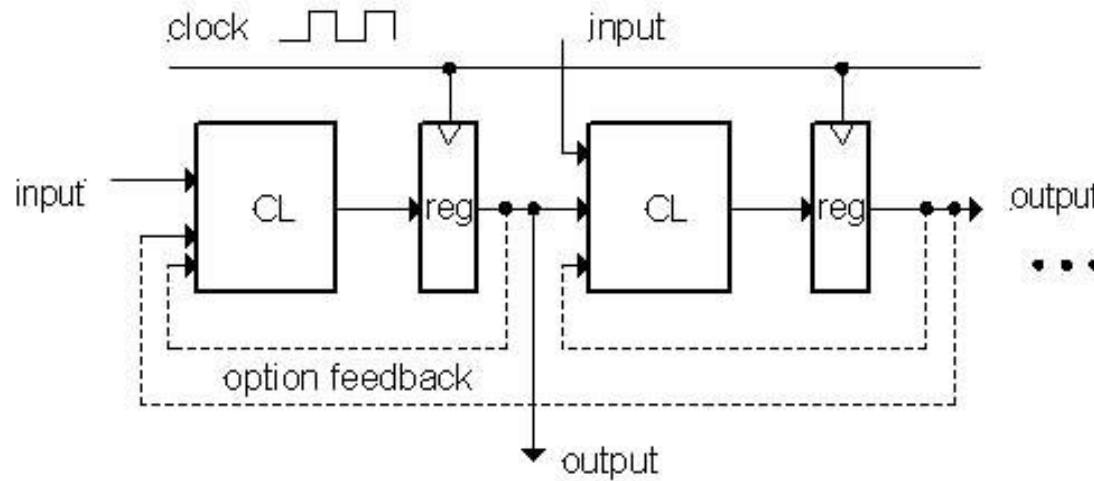
# Why Are Timing Constraints Important?

- ❖ Our model of synchronous digital systems relies on timing behavior of the clock and logic stages
  - Combinational logic blocks separated by registers




- Violations can cause incorrect behavior or can cause produced semiconductor circuits to fail!
- Timing considerations can limit how fast our system/clock can run

# Review: Timing Issues

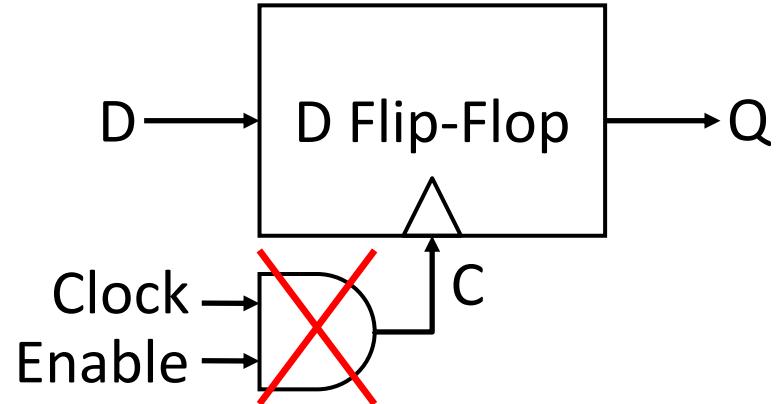
## ❖ NEVER GATE THE CLOCK!!!

- Delays can cause part of circuit to get out of sync with rest
  - Adds to *clock skew*
- Hard to track non-uniform triggers



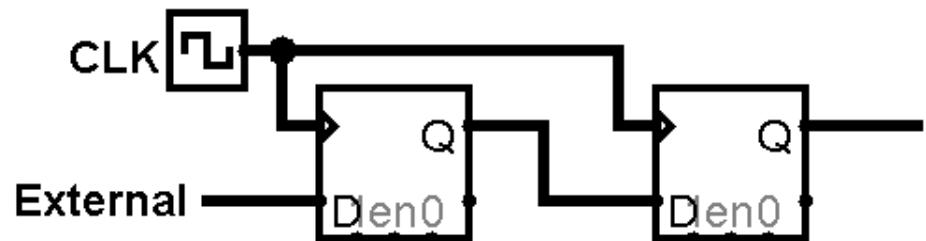
## ❖ Metastability is the ability of a digital system to persist for an unbounded time in an unstable equilibrium or metastable state

- Add chains of registers to allow to settle:



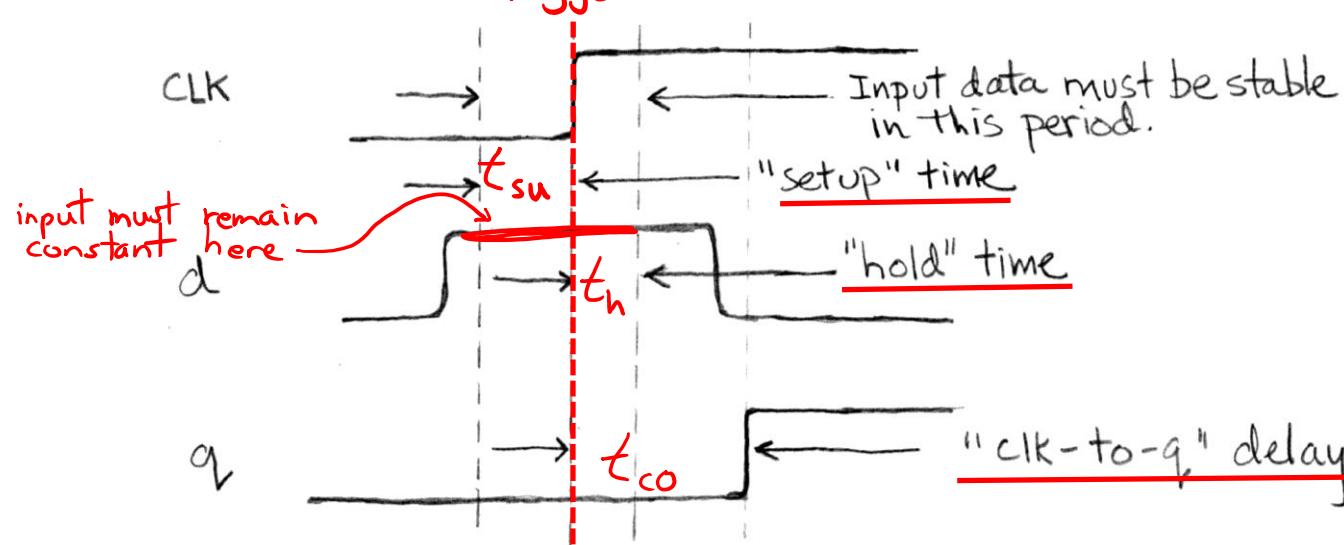
# Review: Sequential Timing Constraints

- ❖ *Setup Time ( $t_s$  or  $t_{su}$ ):* how long the input must be stable *before* the CLK trigger for proper input read
- ❖ *Hold Time ( $t_h$ ):* how long the input must be stable *after* the CLK trigger for proper input read
- ❖ *"CLK-to-Q" Delay ( $t_{C2Q}$  or  $t_{CO}$ ):* how long it takes the output to change, measured from the CLK trigger



# Where Do Timing Terms Come From?

Edge-triggered  
D flip-flop:

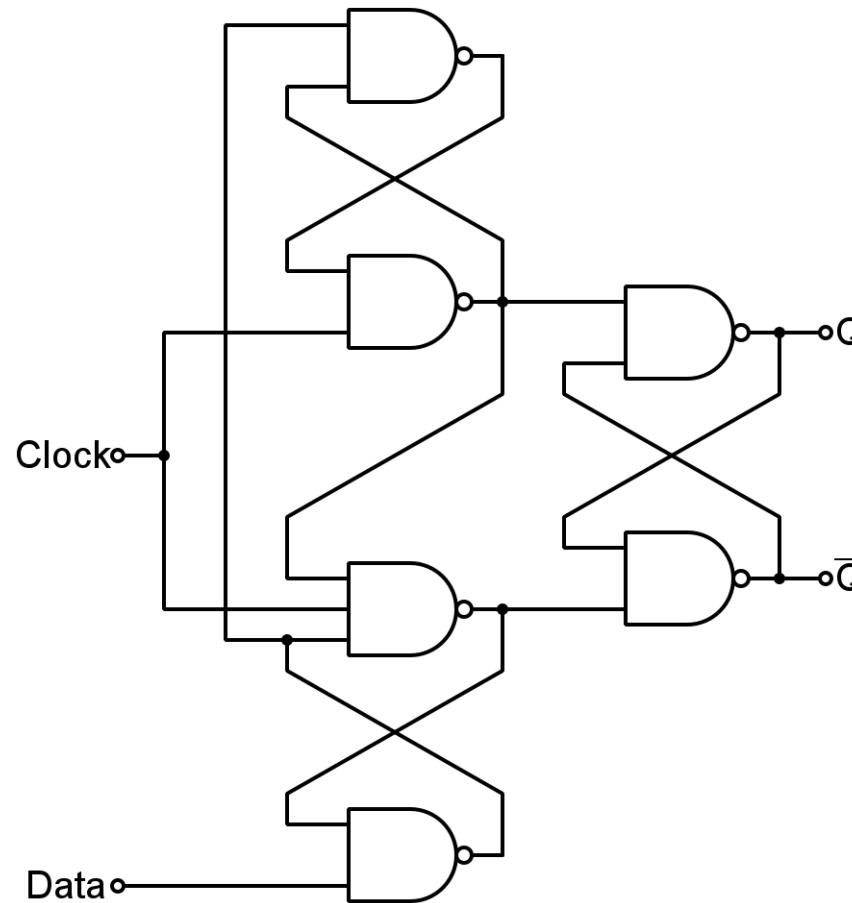


By Nolanjshettle at English Wikipedia, CC BY-SA 3.0,  
<https://commons.wikimedia.org/w/index.php?curid=40852354>

# When Can the Input Change?

- ❖ When a register input changes shouldn't violate hold time ( $t_h$ ) or setup time ( $t_{su}$ ) constraints within a clock period ( $T$ )
- ❖ Let  $t_{input,i}$  be the time it takes for the input of a register to change for the  $i$ -th time in a single clock cycle, measured from the CLK trigger:
  - Then we need  $t_h \stackrel{(1)}{\leq} t_{input,i} \stackrel{(2)}{\leq} T - t_{su}$  for all  $i$
  - Two separate constraints!

$$\textcircled{1} \quad t_{input,1} \geq t_h$$
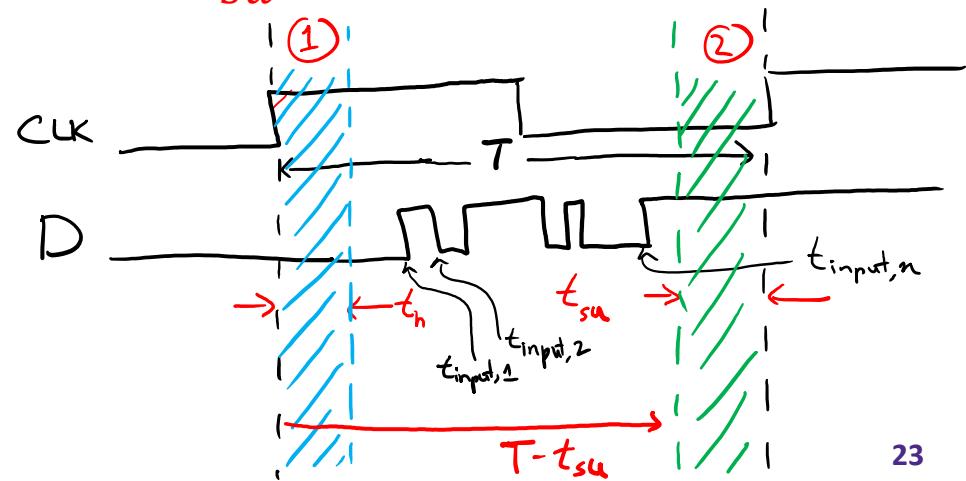
$$\textcircled{2} \quad t_{input,n} \leq T - t_{su}$$




# Timing Constraint Considerations

- ❖ Use *worst-case analysis*
  - Asynchronous inputs are *really* problematic
  - Use the **critical path** – the longest delay between *any* two registers in a circuit – for setup time constraint
  - Use the shortest path for the hold time constraint
- ❖ A timing violation could be caused by a signal change from the previous clock cycle
  - A really late input change could violate the hold time constraint in the next clock cycle
- ❖ Setup time constraint helps determine feasibility of clock frequency:  $\text{max freq} = 1/(\text{min period})$
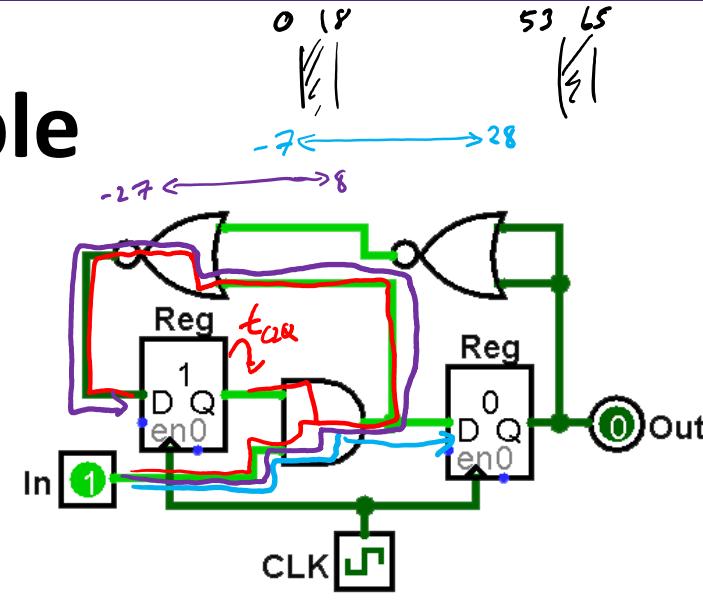
# Timing Constraint Example

- $t_{su} = 12 \text{ ns}$ ,  $t_h = 18 \text{ ns}$ ,  
 $t_{CO} = 8 \text{ ns}$ ,  $t_{AND} = 25 \text{ ns}$ ,  
and  $t_{NOR} = 20 \text{ ns}$



- If In changes  $t_{CO}$  after each clock trigger, what is the **minimum clock period** we can use? *critical path(s) shown in red.*

$$t_{CO} + t_{AND} + t_{NOR} \leq T - t_{su}$$

$$8 + 25 + 20 \leq T - 12$$

$$\boxed{T \geq 65 \text{ ns}}$$

- If we use the minimum clock period, when within a clock period can In change without causing a timing violation?

In changes propagate to register inputs along 2 paths (- and -).

$$t_h \leq t_{In} + t_{AND} \leq T - t_{su}$$

$$t_h \leq t_{In} + t_{AND} + t_{NOR} \leq T - t_{su}$$

$$\Rightarrow -7 \text{ ns} \leq t_{In} \leq 28 \text{ ns} \quad \text{intersect}$$

$$\Rightarrow -27 \text{ ns} \leq t_{In} \leq 8 \text{ ns}$$

$$\Rightarrow -7 \text{ ns} \leq t_{In} \leq 8 \text{ ns}$$

$$\boxed{\begin{array}{l} [0, 8] \text{ ns} \\ \text{or} \\ [58, 65] \text{ ns} \end{array}}$$