

Design of Digital Circuits and Systems

Static Timing Analysis

Instructor: Justin Hsia

Teaching Assistants:

Colton Harris

Deepti Anoop

Gayathri Vadhyan

Jared Yoder

Lancelot Wathieu


Matthew Hung

Relevant Course Information

- ❖ Lab 4 due Friday (5/3)
- ❖ Quiz 3 is this Thursday at 11:50 am (30 min)
 - ASM and ASMD charts
- ❖ Homework 5 (5/10) and Lab 5 (5/17) will be released on Thursday
 - Lab 5 is the longest “regular” lab, mostly because of debugging – careful with number representation
- ❖ Rest of course material will NOT show up in labs

Review: Sequential Timing Constraints

 - ❖ *Setup Time (t_s or t_{su}):* how long the input must be stable *before* the CLK trigger for proper input read
- ❖ *Hold Time (t_h):* how long the input must be stable *after* the CLK trigger for proper input read
- ❖ *"CLK-to-Q" Delay (t_{C2Q} or t_{CO}):* how long it takes the output to change, measured from the CLK trigger




When Can the Input Change?

- ❖ When a register input changes shouldn't violate hold time (t_h) or setup time (t_{su}) constraints within a clock period (T)
- ❖ Let $t_{input,i}$ be the time it takes for the input of a register to change for the i -th time in a single clock cycle, measured from the CLK trigger:
 - Then we need $t_h \stackrel{(1)}{\leq} t_{input,i} \stackrel{(2)}{\leq} T - t_{su}$ for all i
 - Two separate constraints!

$$\textcircled{1} \quad t_{input,1} \geq t_h$$
 
$$\textcircled{2} \quad t_{input,n} \leq T - t_{su}$$




Timing Constraint Questions

 - 1) What are you solving for? Which constraint/inequality is relevant?
 - $t_h \rightarrow$ hold time constraint
 - t_{su} or $T \rightarrow$ setup time constraint
 - Combinational logic delay \rightarrow “max” means setup time constraint, “min” means hold time constraint
- 2) Find the most relevant pathway to a register input
 - Hold time constraint \rightarrow shortest pathway
 - Setup time constraint \rightarrow longest pathway
- 3) Solve the inequality for chosen path using the given constants

Practice Question

- ❖ Let $T = 300$ ps,
 $t_{su} = 80$ ps, $t_h = 50$ ps,
 $t_{CO} = 100$ ps.



- 1) If In changes exactly on clock triggers, what are the limits on the XOR gate delay that ensure proper behavior?


$$t_{XOR} \in (\underline{\quad}, \underline{\quad}) \text{ ps}$$

- 2) Now let $t_{XOR} = 100$ ps and In change a fixed t_{in} after each clock trigger, what ranges of t_{in} will result in proper behavior? Answer within a single clock cycle:


$$t_{in} \in [0, \underline{\quad}) \cup (\underline{\quad}, 300] \text{ ps}$$

What Affects Circuit Timing?

 - ❖ A more realistic picture:
 - **Logic depth of circuit pathways**
 - Length, resistance, and capacitance of wire
 - Size of the transistors
 - Operating conditions: Voltage & Temperature




Review: FPGA-Based Design Flow

 


Source: Figure 2.3 from "FPGA Prototyping" by P. Chu

Static Timing Analysis Flow

 


Circuit Path Categorization

 - ❖ **Data paths** are between inputs, sequential elements, and outputs
- ❖ **Clock paths** are from device ports or internally-generated clocks to the clock pins of sequential elements
- ❖ **Asynchronous paths** are between inputs and asynchronous set and clear pins of sequential elements




Data Paths

 - ❖ Three data path types:
 - 1) Input to sequential element
 - 2) Sequential element to sequential element
 - 3) Sequential element to output




Data Path Validity

 - ❖ A data signal is considered **valid** when it has finished computing and is stable
 - Note that this remains true until the next round of computation begins, which can cross clock cycle boundaries
- ❖ For proper behavior (*i.e.*, correct reads), the input to a register must remain valid throughout the setup and hold time constraints



Clock Edges

 - ❖ Looking at a single clock cycle
 - **Launch Edge:** the clock edge that activates or *launches* the source register
 - **Latch Edge:** the clock edge that *lashes* the data into the destination register




Timing Delays and Points of Interest

- ❖ **Clock Network Delay (t_{clk})**
 - How long it takes for changes in the clock signal to arrive at the register – the cause of *clock skew*
- ❖ **Clock-to-Q or Clock-to-out Delay (t_{C2Q} , t_{CQ} , or t_{CO})**
 - How long it takes the output to change, measured from the register's *received* clock edge – a property of the FF/register
- ❖ **Data Arrival Time (DAT)**
 - The time at which the destination register's input is settled
- ❖ **Clock Arrival Time (CAT)**
 - The time at which a clock edge arrives at the destination register

Timing Delays and Points of Interest

DAT = data arrival time


CAT = clock arrival time

 

- $DAT_{su} = \text{launch edge} + t_{clk1,\max} + t_{co,\max} + t_{data,\max}$
- $DAT_h = \text{launch edge} + t_{clk1,\min} + t_{co,\min} + t_{data,\min}$
- $CAT_{\text{latch/launch}} = \text{edge} + t_{clk2}$


Data Required Time (DRT)

 - ❖ Data Required Time for Setup (DRT_{su})
 - The minimum time required *before* the *latch edge* for data to get latched into the destination register
 - Clock Arrival Time_{latch} – Setup Time




Data Required Time (DRT)

 - ❖ Data Required Time for Hold (DRT_h)
 - The minimum time required *after* the *launch edge* for the data to remain valid for successful latching
 - Clock Arrival Time_{launch} + Hold Time




Setup Slack

 - ❖ Wiggle room for setup time violations
 - Setup slack = $DRT_{su} - DAT_{su}$
 - Depends on clock frequency




Hold Slack

 - ❖ Wiggle room for hold time violations
 - Hold slack = $DAT_h - DRT_h$
 - Does not depend on clock frequency




Technology Break

Setup Slack Example

 


- ❖ Assume 100 MHz clock; clock period $T = 10 \text{ ns}$
- ❖ Setup slack = $DRT_{su} - DAT_{su}$
= *min clock path* – *max data path*

Hold Slack Example

 


- ❖ Assume 100 MHz clock; clock period $T = 10$ ns
- ❖ Hold slack = $DAT_h - DRT_h$
= *min* data path – *max* clock path

Slack Example

 

- ❖ Calculate the setup and hold slacks:
 - Assume 50 MHz clock; clock period $T = 20 \text{ ns}$
 - setup slack = *min clock path* – *max data path*
 - hold slack = *min data path* – *max clock path*

Slack Example

 


- ❖ What is the fastest clock we can use with this circuit?

Synopsys Design Constraints (SDC)

- ❖ Synopsys Design Constraints describe timing constraints and exceptions
 - Quartus uses *.sdc* files to define clocks, I/O constraints, and other information that the fitter needs to make the best decisions
 - You can make and edit these using the TimeQuestGUI or by editing the *.sdc* file in a text editor (see hw5)

I/O Constraints

 
- ❖ Let's examine the design constraints for the following example FPGA setup:
 - FPGA circuit between two external chips
 - T_w are wire/board delays, T_{clk} are clock delays *



* every delay has a min and max range

Input Delays

 
- ❖ **set_input_delay**
 - Command to specify external delays feeding into the FPGA's input ports
 - https://www.intel.com/content/www/us/en/programmable/quartushelp/13.0/mergedProjects/tafs/tafs/tcl_pkg_sdc_ver_1.5_cmd_set_input_delay.htm



- ❖ Applied to this setup:
 - $\text{input delay}_{\min} = (T_{\text{clk2,min}} - T_{\text{clk1,max}}) + T_{\text{CO,min}} + T_{\text{W1,min}}$
 - $\text{input delay}_{\max} = (T_{\text{clk2,max}} - T_{\text{clk1,min}}) + T_{\text{CO,max}} + T_{\text{W1,max}}$

Output Delays

 - ❖ `set_output_delay`
 - Command to specify external delays leaving the FPGA's output ports
 - https://www.intel.com/content/www/us/en/programmable/quartushelp/13.0/mergedProjects/tafs/tafs/tcl_pkg_sdc_ver_1.5_cmd_set_output_delay.htm



- ❖ Applied to this setup:
 - $\text{output delay}_{\min} = (T_{\text{clk1,min}} - T_{\text{clk3,max}}) + T_{W2,\min} - T_{h,\max}$
 - $\text{output delay}_{\max} = (T_{\text{clk1,max}} - T_{\text{clk3,min}}) + T_{W2,\max} + T_{su,\max}$

I/O Constraints


- ❖ Check the datasheet!

READ/WRITE CYCLE SWITCHING CHARACTERISTICS (Over Operating Range)

Symbol	Parameter	-166		-133		Unit
		Min.	Max.	Min.	Max.	
fMAX ⁽³⁾	Clock Frequency	—	166	—	133	MHz
t _{CK} ⁽³⁾	Cycle Time	6	—	7.5	—	ns
t _{KH}	Clock High Time	2.4	—	2.8	—	ns
t _{KL} ⁽³⁾	Clock Low Time	2.4	—	2.8	—	ns
t _{QA} ⁽³⁾	Clock Access Time	—	3.5	—	4	ns
t _{QX} ⁽¹⁾	Clock High to Output Invalid	3	—	3	—	ns
t _{QLZ} ^(1,2)	Clock High to Output Low-Z	0	—	0	—	ns
t _{QHZ} ^(1,2)	Clock High to Output High-Z	1.5	3.5	1.5	3.5	ns
t _{OEQ} ⁽³⁾	Output Enable to Output Valid	—	3.5	—	3.8	ns
t _{OEQX} ⁽¹⁾	Output Disable to Output Invalid	0	—	0	—	ns
t _{ELZ} ^(1,2)	Output Enable to Output Low-Z	0	—	0	—	ns
t _{EHZ} ^(1,2)	Output Disable to Output High-Z	2	4.5	2	5	ns
t _{AS} ⁽³⁾	Address Setup Time	2.1	—	2.1	—	ns
t _{SS} ⁽³⁾	Address Status Setup Time	1.5	—	1.5	—	ns
t _{WS} ⁽³⁾	Write Setup Time	1.5	—	1.5	—	ns
t _{CES} ⁽³⁾	Chip Enable Setup Time	1.5	—	1.5	—	ns
t _{AVS} ⁽³⁾	Address Advance Setup Time	1.5	—	1.5	—	ns
t _{AH} ⁽³⁾	Address Hold Time	1.0	—	1.0	—	ns
t _{SH} ⁽³⁾	Address Status Hold Time	0.5	—	0.5	—	ns
t _{WH} ⁽³⁾	Write Hold Time	0.5	—	0.5	—	ns
t _{CEH} ⁽³⁾	Chip Enable Hold Time	0.5	—	0.5	—	ns
t _{AVH} ⁽³⁾	Address Advance Hold Time	0.5	—	0.5	—	ns


Clock Effects

 - ❖ **Clock Latency:** delay for clock signal to reach components
 - Source latency: the delay between the clock definition and its source
 - Network latency: the delay between the clock definition and register clock pins
 - [extra] Often dealt with using an onboard phase-locked loop (PLL) – see `derive_pll_clocks` command



Clock Effects

 - ❖ **Clock Uncertainty:** clock signal does not arrive at every clock pin simultaneously
 - Skew: differences in arrival time of a clock signal to different components
 - Jitter: deviations from defined period
 - Synchronous clock domain crossings (future lecture)



Timing Closure

- ❖ Timing constraints need to be met *simultaneously*
 - Sometimes fixing one violation will introduce another
- ❖ Fixing **hold violations**: caused by fast data path and destination register's clock latency
 - Add delay in the data path with buffers or pairs of inverters (done automatically by Quartus)
- ❖ Fixing **setup violations**: data arrives too late compared to the destination register's clock speed
 - Slow down the clock (undesirable)
 - Tell fitter to try harder or confine logic to a smaller area
 - Rewrite code to simplify logic
 - Add *pipelining* (next lecture)