

# Design of Digital Circuits and Systems

## Pipelining

**Instructor:** Justin Hsia

**Teaching Assistants:**

Colton Harris

Gayathri Vadhyan

Lancelot Wathieu

Deepti Anoop

Jared Yoder


Matthew Hung

# Relevant Course Information

- ❖ Quiz 3 starts at 11:50 am
- ❖ Lab 4 due Friday (5/3), demos next week
- ❖ Homework 5 released today, due next Friday (5/10)
  - Static Timing Analysis and Pipelining
- ❖ Lab 5 released today, due in two weeks (5/17)
  - Hardest lab for many students
  - You will need to use the VGA interface on LabsLand
  - There's a creative component and opportunity for extra credit

# Review: Timing Closure


(setup and hold slack)

 

- ❖ Fixing hold violations: caused by fast data path and destination register's clock latency
  - Add delay in the data path with buffers or pairs of inverters (done automatically by Quartus)
- ❖ Fixing setup violations: data arrives too late compared to the destination register's clock speed
  - Slow down the clock (undesirable)
  - Tell fitter to try harder or confine logic to a smaller area
  - Rewrite code to simplify logic
  - ↳ ■ Add *pipelining* (today!)
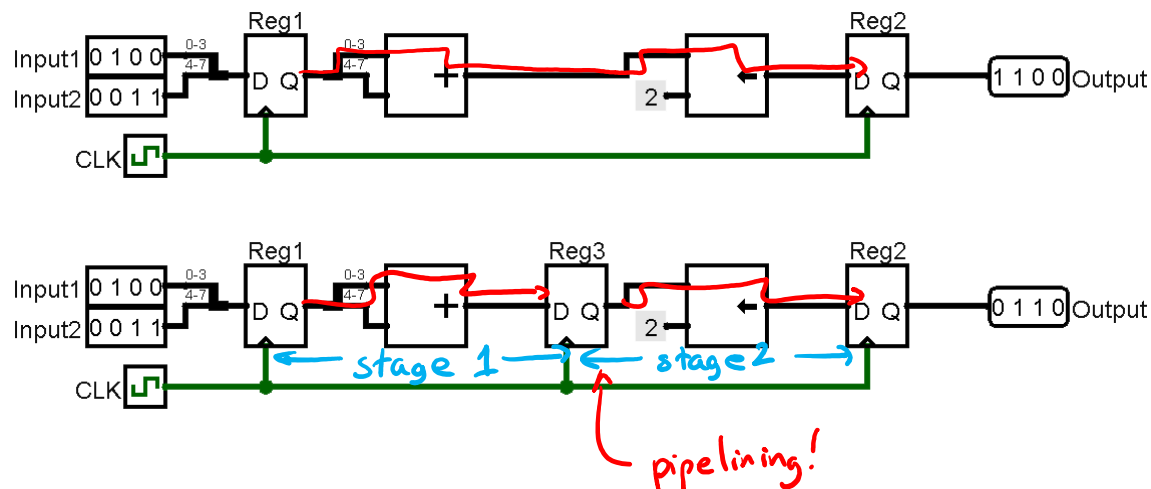
# Pipelining

- ❖ **Pipelining** is a set of data processing elements connected in series with buffer storage inserted between
  - In digital systems, the buffer storage are FFs & registers and data processing elements are "stages" of combinational logic
  - In its simplest form, can be thought of as adding registers in the middle of a computation to reduce our clock period



# Performance

- ❖ What does it mean to say X performs better than Y?
- ❖ Silly example: a Tesla vs. a school bus
  - 2015 Tesla Model S P90D
    - 5 passengers, 2.8 secs in quarter mile
  - 2011 Type D school bus
    - Up to 90 passengers, quarter mile time?



# Performance

- ❖ What does it mean to say X performs better than Y?
- ❖ Silly example: a Tesla vs. a school bus
  - 2015 Tesla Model S P90D
    - 5 passengers, 2.8 secs in quarter mile
  - 2011 Type D school bus
    - Up to 90 passengers, quarter mile time?



# Measurements of Performance



- ❖ *Latency* (or *response time* or *execution time*)
  - Time to complete one task
- ❖ *Throughput* (or *bandwidth*)
  - Tasks completed per unit time
  
# Analogy: Doing Laundry

- ❖ **D**eep*t*i, **G**ayathri, **J**ared, and **L**ancelot each have one load of clothes to wash, dry, fold, and put away




- Washer takes 30 minutes
- Dryer takes 30 minutes
- “Folder” takes 30 minutes
- “Stasher” takes 30 minutes to put clothes into drawers






# Sequential Laundry

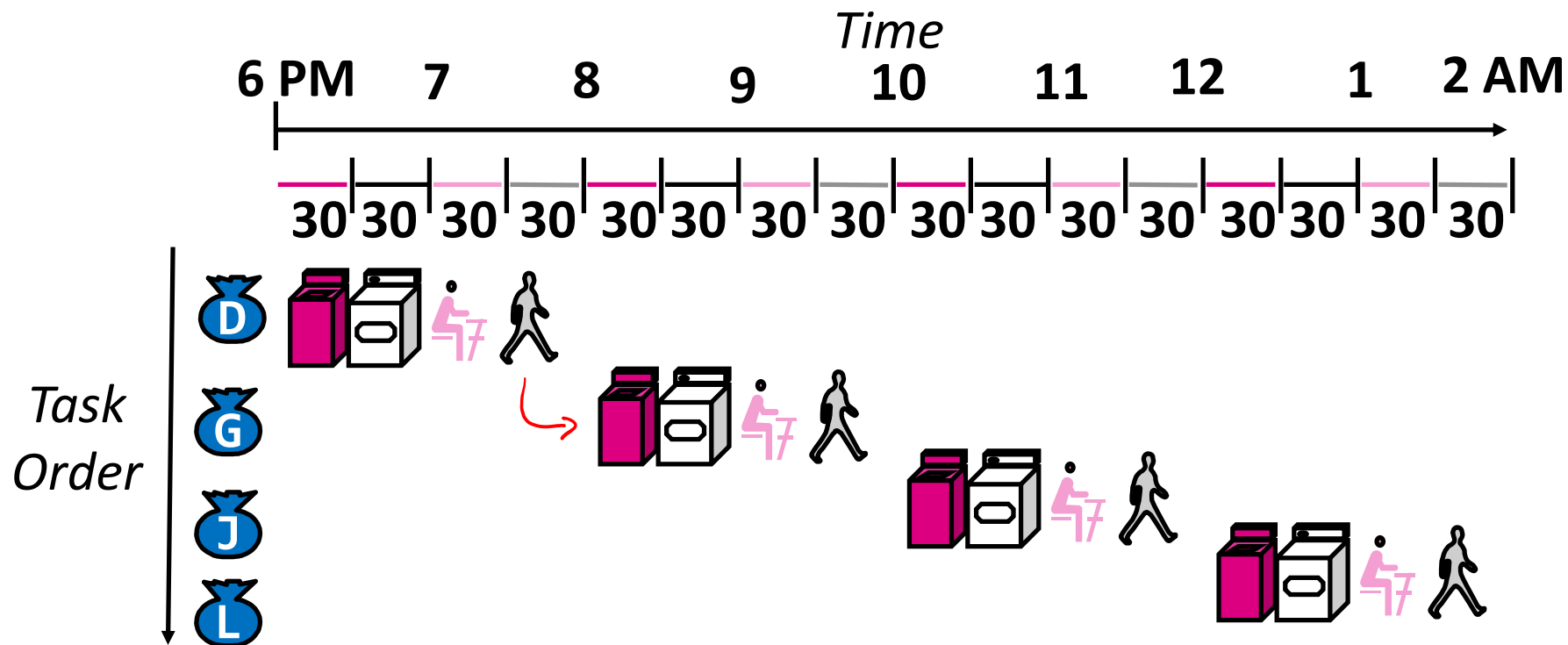

- Sequential laundry takes 8 hours for 4 loads  
*only 1 person in laundry room at a time!*

# Pipelined Laundry

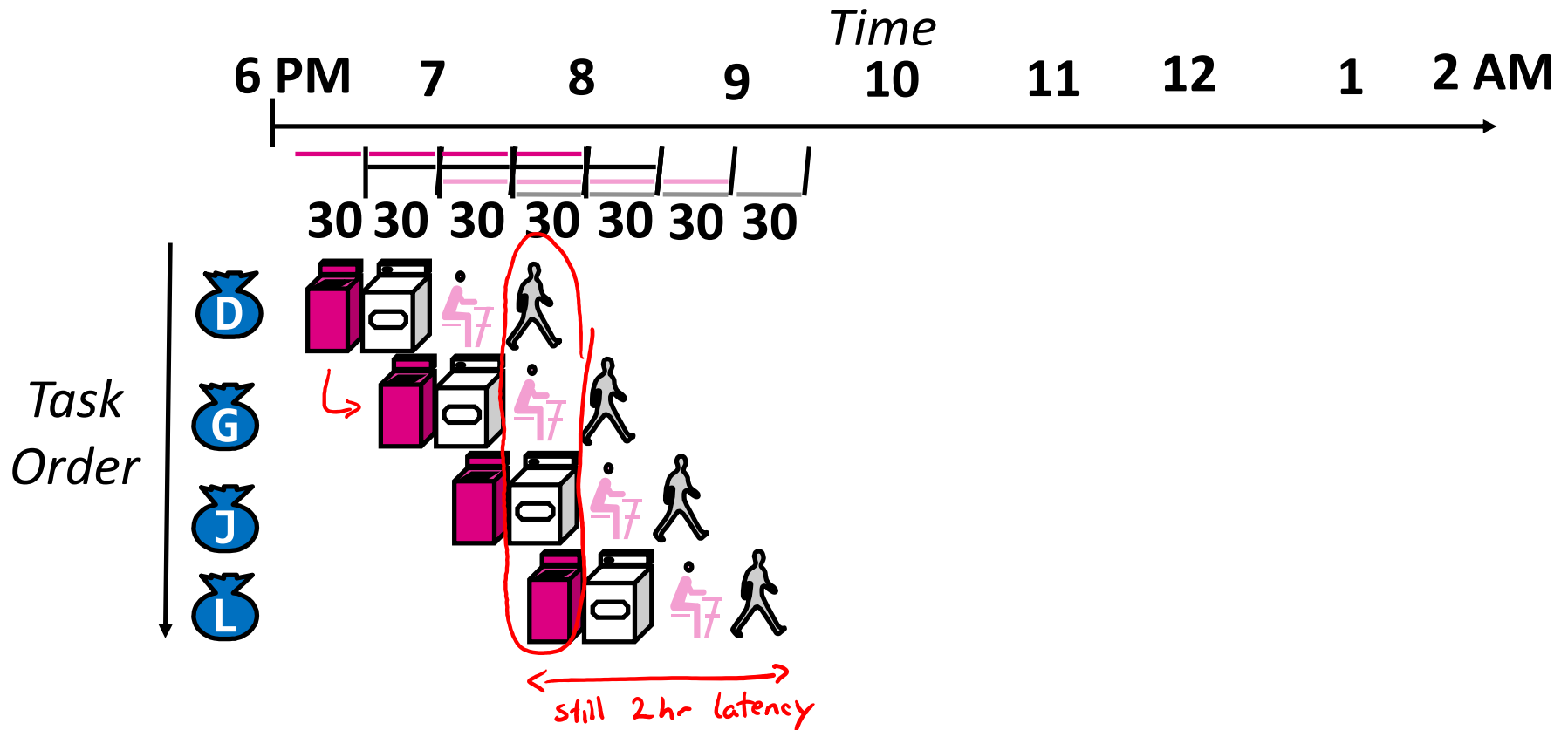

- Pipelined laundry takes 3.5 hours for 4 loads!

*up to 4 people in the laundry room at a time!*

*at most 1 person using any station at a time*


# Pipelining Notes

- ❖ Pipelining helps throughput of overall workload, but not latency of single task

- Reduction in critical pathway allows for shorter clock period

- ❖ *Multiple* tasks operating simultaneously using different resources

 
- Executing different parts of multiple computations at the same time using the same hardware – like an assembly line
- Greater utilization of logic resources



# Pipelined Performance Example

- ❖ Assume  $t_{CO} = 10\text{ ns}$ ,  $t_{add} = 90\text{ ns}$ ,  $t_{shl} = 50\text{ ns}$ 
  - For simplicity, assume  $t_{clk} = t_{wire} = t_h = t_{su} = 0$
- ❖ Solve for the minimum clock period for each circuit
  - Given this minimum clock period, solve for the latency and throughput of each circuit


## Circuit 1:

 

$T_{min} = 150\text{ ns}$   
 throughput =  $1/T = 1/(150\text{ ns})$   
 latency =  $T + t_{CO} = 160\text{ ns}$

critical path =  $t_{CO} + t_{add} + t_{shl} \leq T - t_{su}$

## Circuit 2:

 


$T_{min} = 100\text{ ns}$   
 throughput =  $1/T = 1/(100\text{ ns})$   
 latency =  $2T + t_{CO} = 210\text{ ns}$

critical path =  $\max(t_{CO} + t_{add}, t_{CO} + t_{shl}) \leq T - t_{su}$
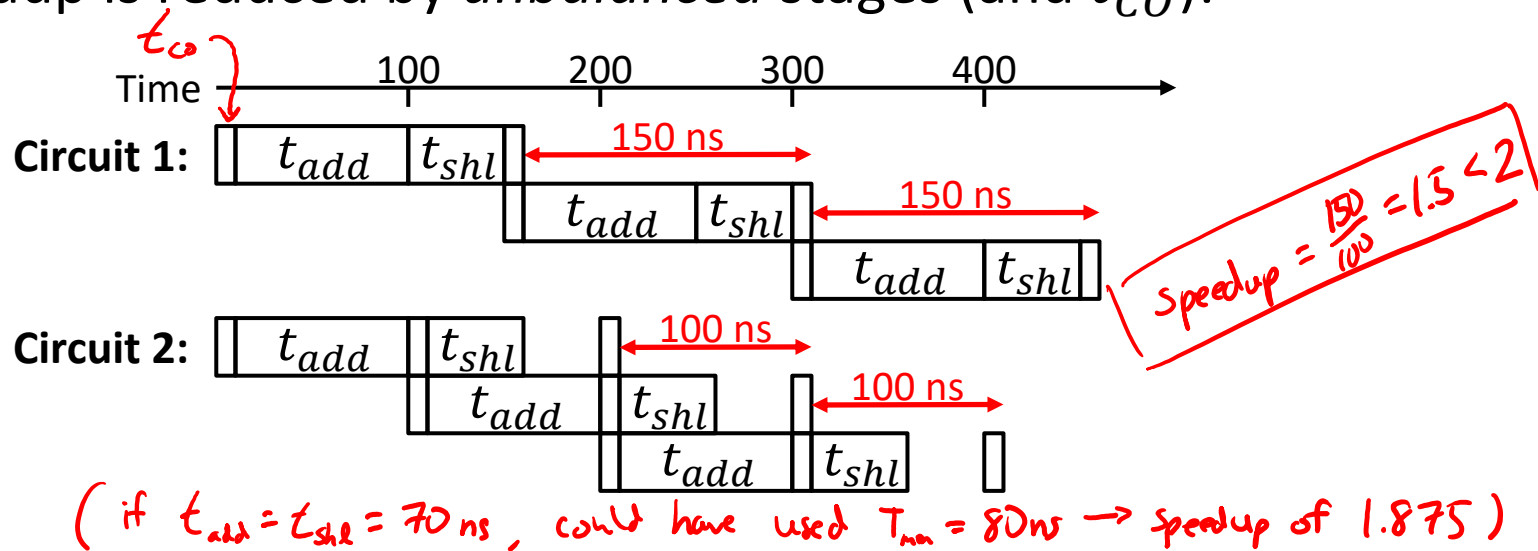
# Pipeline Performance

❖ In theory, can measure “speedup” as the ratio in time per completion (TC) of computations


- $speedup = \frac{TC_{original}}{TC_{pipelined}}$
- $speedup_{max} = \# \text{ of pipeline stages}$
- Speedup is reduced by *unbalanced* stages (and  $t_{CO}$ ):



# Technology Break
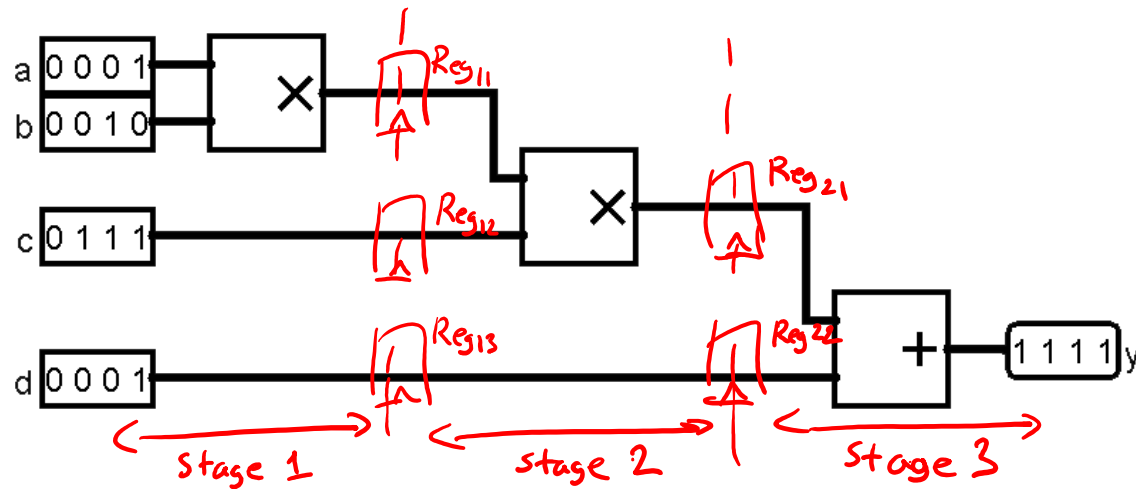
# Pipeline Registers

- ❖ Where to add pipeline registers?
  - For a given computation, all paths from any input to output must pass through the *same number* of pipeline registers
- ❖ Example:  $y_i = (a_i \times b_i) \times c_i + d_i$




# Pipeline Registers

- ❖ Where to add pipeline registers?
  - For a given computation, all paths from any input to output must pass through the *same number* of pipeline registers

❖ Example:  $y_i = (a_i \times b_i) \times c_i + d_i$

- Signal flow:

 


Cycle	1	2	3	4
Reg11	X	$a_1 b_1$	$a_2 b_2$	$a_3 b_3$
Reg12	X	$c_1$	$c_2$	$c_3$
Reg13	X	$d_1$	$d_2$	$d_3$
Reg21	X	X	$a_1 b_1 c_1$	$a_2 b_2 c_2$
Reg22	X	X	$d_1$	$d_2$



 
# Data Flow Graph

- ❖ A **data flow graph** (DFG) is a visualization tool that can be used to simplify circuits into *directed graphs*
  - Nodes are computations (and their delays)
  - Edges represent data dependencies



 
# Pipeline Cutset

- ❖ A **cutset** is a set of edges that form two disjoint graphs when removed/cut
  - *Feedforward* cutset: data travels only forward in the cutset
  - *Feedback* cutset: data travels in both directions in the cutset
- ❖ Pipelining is done by placing a register along every edge in a **pipeline (feedforward) cutset**:


 
# Pipeline Cutset Example

- ❖ The following data flow graph shows the propagation delay in each node
  - For simplicity, assume  $t_{CO} = 0$
  - Original (non-pipelined) performance:




critical path has delay of  $12+7+15+6+9+4 = 53$

$$\boxed{T_{mm} = 53} \xrightarrow{\times 1} \text{latency} > 53$$

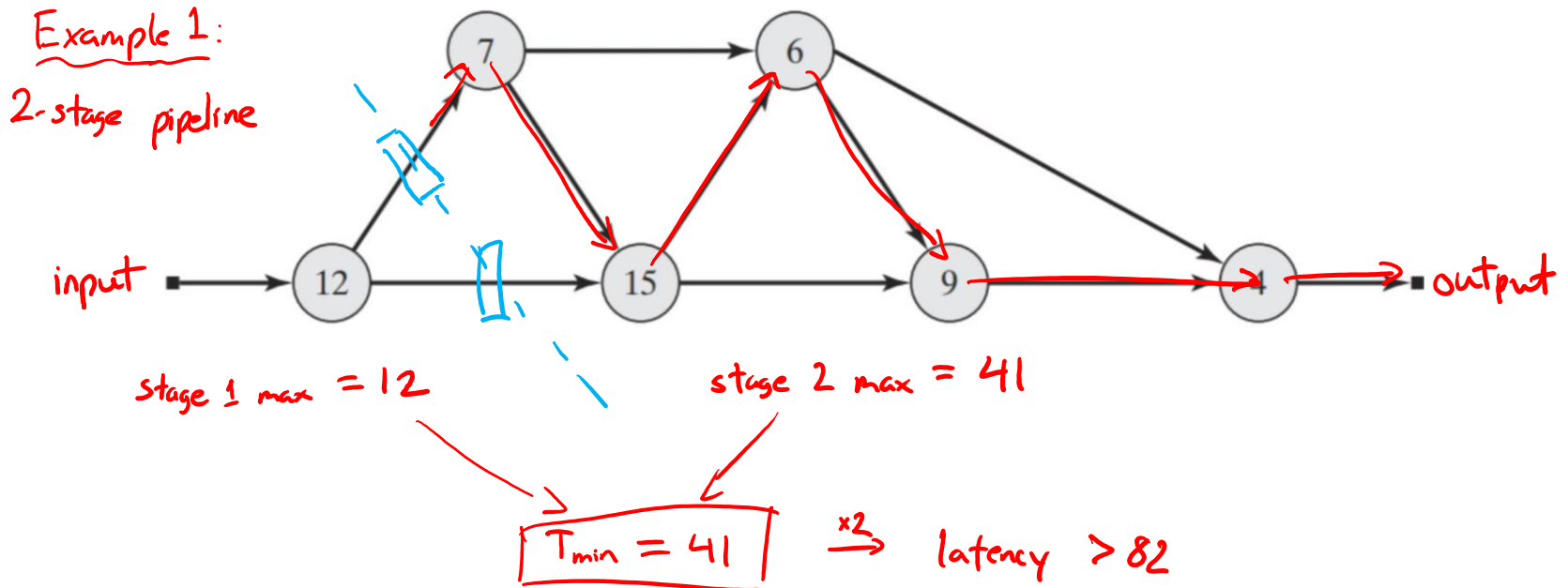
# Pipeline Cutset Example

- ❖ The following data flow graph shows the propagation delay in each node
  - Create 2-3 different pipelined versions of this DFG and compute the maximum delay of each stage and minimum clock period for the pipelined computation
    - For simplicity, assume  $t_{CO} = 0$


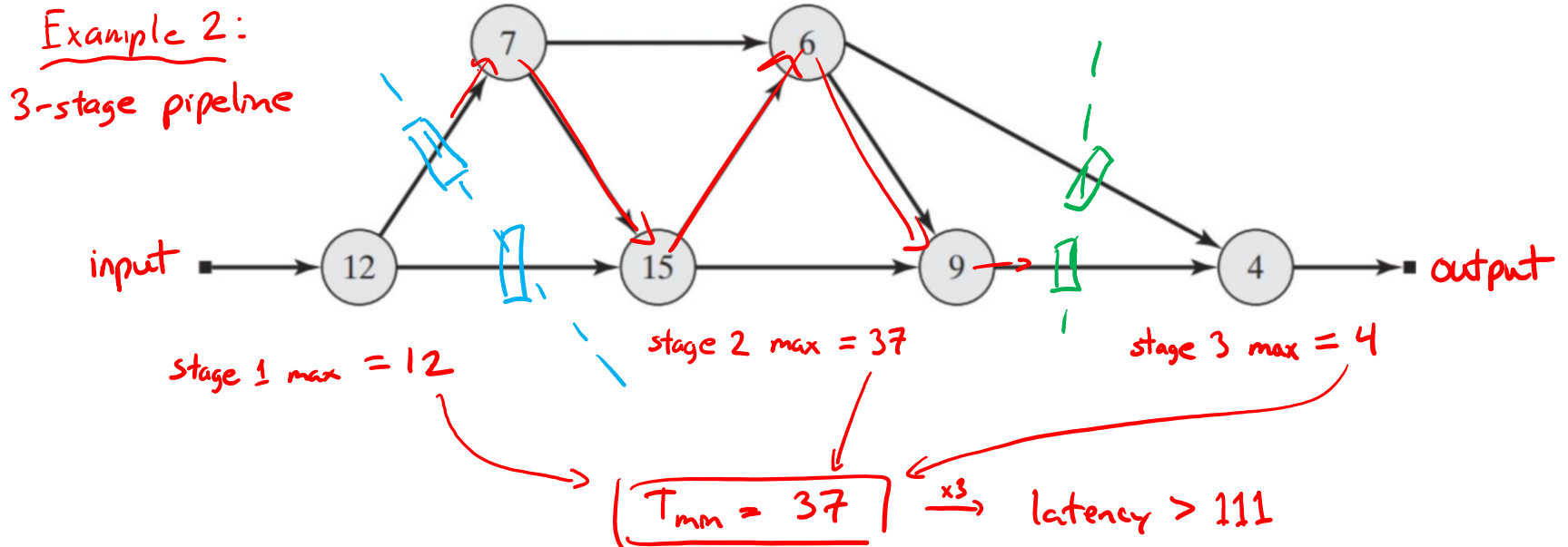
# Pipeline Cutset Example


- ❖ The following data flow graph shows the propagation delay in each node
  - Create 2-3 different pipelined versions of this DFG and compute the maximum delay of each stage and minimum clock period for the pipelined computation
    - For simplicity, assume  $t_{CO} = 0$



# Pipeline Cutset Example

- ❖ The following data flow graph shows the propagation delay in each node
  - Create 2-3 different pipelined versions of this DFG and compute the maximum delay of each stage and minimum clock period for the pipelined computation
    - For simplicity, assume  $t_{CO} = 0$

Example 3:  
"best" pipeline

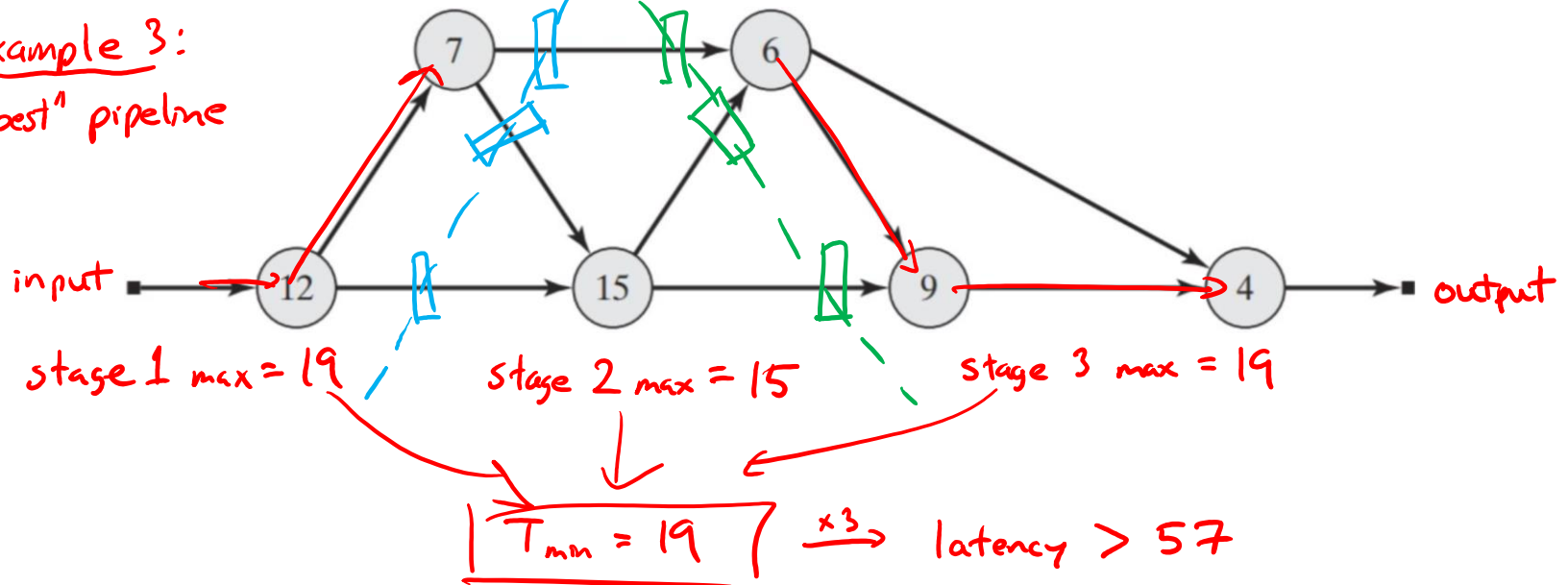


# Pipeline Design Questions


- ❖ When should I add pipelining?
  - Check if it is possible first (*i.e.*, a pipeline cutset must exist)
  - Want to reduce the **critical path** in your computation/system
  - Your system can afford the increase in latency and hardware
- ❖ Where do the pipeline registers go?
  - Must be placed at proper pipeline cutsets
  - Want to make pipeline stages as balanced as possible to maximize speedup
 
# Design Example: 16-bit Ripple-Carry Adder

- ❖ Problem:  $C_n$  takes a long time to compute!




 - ❖ 2-stage pipeline: which cutset to use? *cut evenly in half*







# Design Example: 16-bit Pipelined Adder

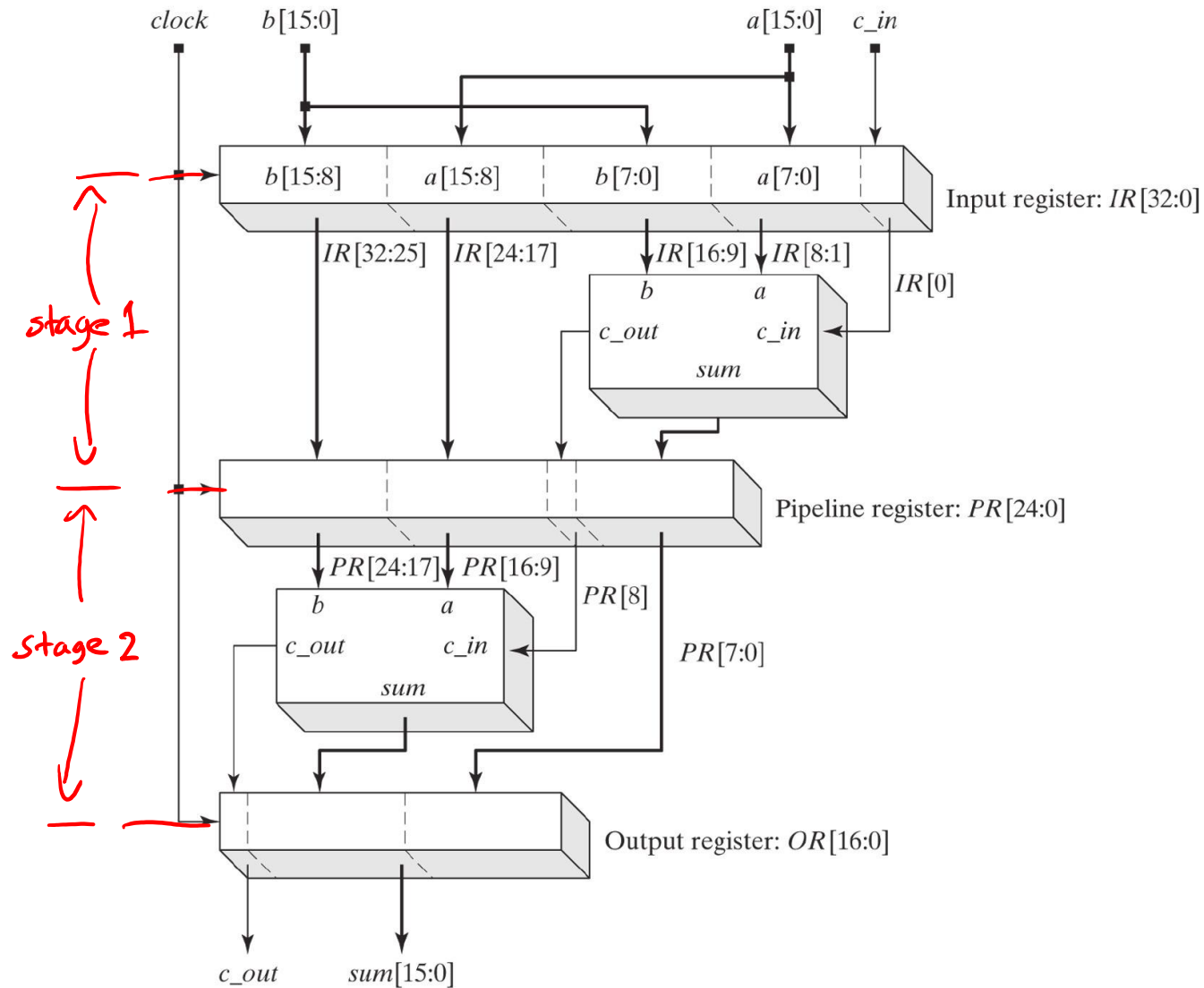

# Design Example: 16-bit Pipelined Adder

 

# Design Example: FIR Filter

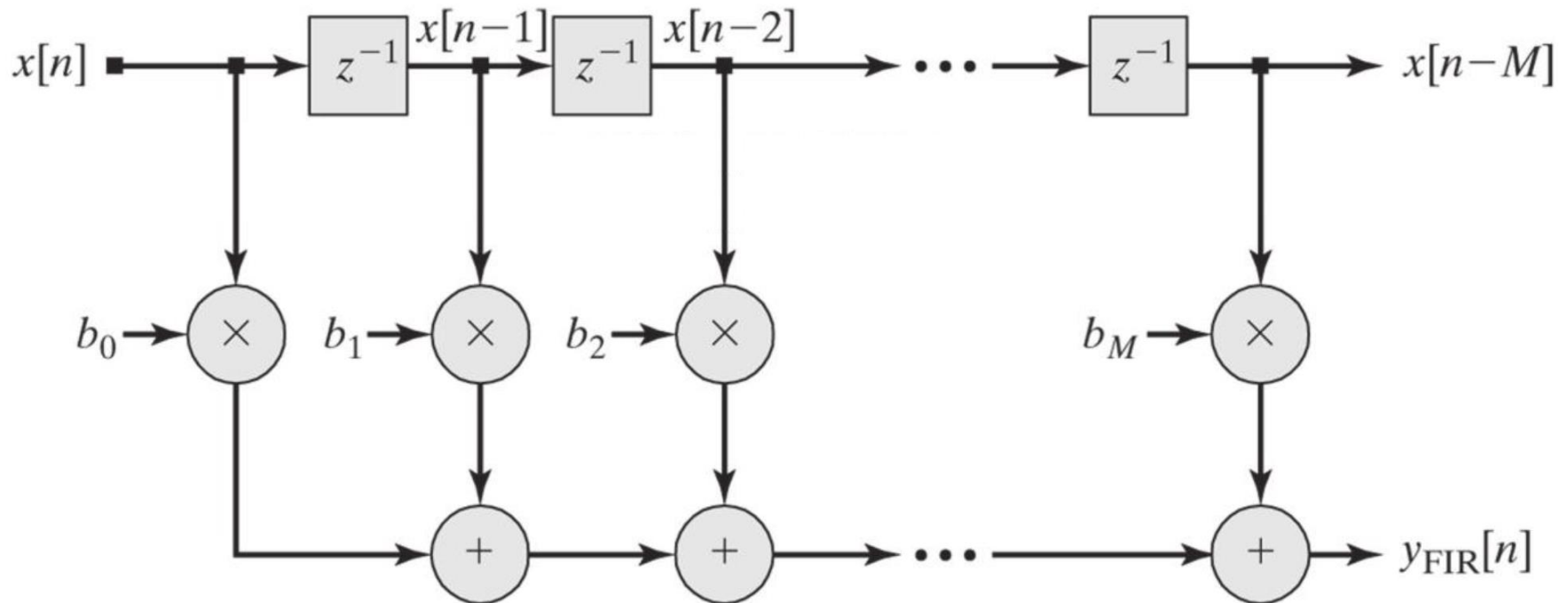

# Design Example: Pipelined FIR Filter

