

Design of Digital Circuits and Systems

SystemVerilog Review & Tips

Instructor: Vikram Iyer

Teaching Assistants:

Ariel Kao

Josh Wentzien

Selim Saridede

Jared Yoder

Derek Thorp

Adapted from material by Justin Hisa

Relevant Course Information

- ❖ hw1 due on Monday (4/7)
 - Homework can be completed in groups of up to 4
- ❖ Lab 1 report due Friday (4/11)
 - Labs can be completed in groups of up to 2
- ❖ Lab demos:
 - Lab demo sign up sheet sent out soon (check with partner)
 - 15 minutes for demos, early labs will be quicker
 - Make sure LabsLand is set up and synthesized *beforehand*
- ❖ Quiz 1 is Thursday, April 4 in last 25 min of lecture
 - Draw FSM state diagram & make design decisions

Lecture Outline

- ❖ **SystemVerilog Review & Tips (Cont.)**
- ❖ FSMs
- ❖ Test Benches

Review: Integers in Computing

- ❖ **Unsigned integers** follow the standard base 2 system

- $b_7b_6b_5b_4b_3b_2b_1b_0 = b_72^7 + b_62^6 + \dots + b_12^1 + b_02^0$
- In n bits, represent integers 0 to $2^n - 1$

- ❖ **Signed integers** use *Two's Complement representation*

- b_{w-1} has weight -2^{w-1} , other bits have usual weights $+2^i$



- In n bits, represent integers -2^{n-1} to $2^{n-1} - 1$
- Most significant bit acts as a *sign bit* (0 = pos, 1 = neg)
- Handy negation procedure: take the bitwise complement and then add one ($\sim x + 1 == -x$)

- ❖ **⚠ The choice affects the behavior of operations such as bit extension, shifting, and comparisons**

271/369 SystemVerilog Refresher

- ❖ Multi-bit constants: `<n> ' <s> #...#`
 - `<n>` is width (*unsized* by default)
 - `<s>` is signed designation (omit or 's')
 - `` is radix/base specifier (decimal by default)
 - All letters are case-*insensitive*, `_` can be used to add spaces

Literal	Width	Base	Bits
3'd6	3	10	110
6'o42			
8'hAB			

Literal	Width	Base	Bits
42			
'b101			
-3'd5			

- ❖ Compiler will usually warn you if there is a size mismatch
 - Can “cast” using `#' (<sig>)` syntax

Basic Operators

❖ Possibly new:

■ $371 \% 271 \rightarrow 100$

■ $2 ** 3 \rightarrow 8$

Type	Symbol	Description
Arithmetic	+	addition
	-	subtraction
	*	multiplication
	/	division
	%	modulus
	**	exponentiation
Shift	>>	logical right shift
	<<	logical left shift
	>>>	arithmetic right shift
	<<<	logical left shift
Relational	>	greater than
	<	less than
	>=	greater than or equal to
	<=	less than or equal to
Equality	==	equality
	!=	inequality
	===	case equality
	!==	case inequality
Bitwise	~	bitwise negation
	&	bitwise and
		bitwise or
	^	bitwise xor
Logical	!	logical negation
	&&	logical and
		logical or

Ternary Operator

❖ Conditional assignment

- `select ? <then_expr> : <else_expr>`
 - If `select` is true, then evaluates to `<then_expr>`, otherwise evaluates to `<else_expr>`
- What does this look like in hardware?

❖ **Example:** tristate buffer

- `enable ? in : 'bZ`
 - When enabled, pass the input to the output, otherwise be high impedance

Bit Manipulation

- ❖ Concatenation: $\{sig, \dots, sig\}$
 - Ordering matters; result will have combined widths of all signals
- ❖ Replication operator: $\{n\{m\}\}$
 - repeats value m , n times
- ❖ Exercise: arithmetic right shift preserves the sign bit

```
logic [7:0] x = <some 8-bit constant>;  
// replicate the behavior of y = x >>> 3  
assign y =
```


“Looping”

- ❖ Code is compiled to hardware, so no execution
 - “Loops” must be *statically unrolled* into multiple statements
 - Loops are just for convenience in code writing
- ❖ `repeat (#) <statement(s)>`
 - Makes # copies of statement(s)
- ❖ `for (i=0; i<#; i++) <statement(s)>`
 - Makes # copies of statement(s) that vary based on i
- ❖ `generate` (see reference docs)
 - More “powerful” for-loop typically used for:
 - 1) Module instantiation
 - 2) Changing the structure of parameterized modules
 - 3) Functional and formal verification using assertions

Modules

- ❖ “Black boxes” that we define and instantiate that form the basic building blocks of our design hierarchy
 - **Ports** form the connections between a module and its environment
 - Ports have directionality (**input**, **output**, **inout**), which can be declared within the module or within the port list

```
module tristate(out, in, enable);  
    input logic in, enable;  
    output tri out;  
  
    assign out = enable ? in : 'Z;  
endmodule
```

```
module tristate(output tri out,  
                input logic in,  
                input logic enable);  
    assign out = enable ? in : 'Z;  
endmodule
```

Module Instantiation

- ❖ Name an instance and define its port connections

- `<type> <name> (<port connections>);`

- ❖ Assume we have: `logic in, enable; tri out;`

1) Positional connections:

```
// must follow defined port ordering  
// signal names can be anything  
tristate my_tri(out, in, enable);
```

2) Named/explicit connections:

```
// any ordering & names allowed  
tristate my_tri(.out(out), .in(in), .enable(enable));
```

3) *.name* implicit connection:

```
// signal and port names must match exactly  
tristate my_tri(.out, .in, .enable);
```

Parameters

❖ A **parameter** is a named constant

- Typically used for widths and timing

```
parameter N = 8;           // bus width
parameter period = 100;    // timing constant
```

❖ A parameterized module:


- `module <name> #(<parameter list>) (<port list>);`
- Parameters should be given default values
 - e.g., `#(parameter N = 8)`

❖ Extra exercises:

- Define a parameterized tristate (tristate buffer)
- Define a parameterized multibitAND

Lab 1 Notes

 - ❖ Read the spec carefully!
 - For scenarios that are not described, it's up for you to define; describe and defend your decisions in your report
 - Also read *371_Assignments.pdf*
- ❖ Plan and design *before* you start coding!
- ❖ Test your code in small pieces *as you go*
 - Lab report due before your demo
 - Short sessions (3 min) on LabsLand



Lecture 1 Review

❖ Useful operators:

- Ternary operator: `<cond> ? <then> : <else>`
- Concatenation: `{sig, ..., sig}`
- Replication: `{n{m}}`

❖ A **parameter** is a named constant

```
parameter N = 8;           // bus width  
parameter period = 100;    // timing constant
```

❖ A parameterized module:

- `module <name> #(<parameter list>) (<port list>);`
- Parameters can be given default values
 - e.g., `#(parameter N = 8)`


Review Question

- ❖ There are two forms of bit extensions: zero-extension (add 0s) and sign-extension (copy MSB)
- ❖ Write out SystemVerilog pseudocode for a parameterized *extender* module
 - Inputs `sign` (1 bit), `in` (M bits); output `out` (N bits $> M$)
 - `out` should either be the sign-extended version of `in` (`sign` = 1) or the zero-extended version of `in` (`sign` = 0)

Review Question (Possible) Solution

```
module extender #(parameter M = 4, N = 8)
    (output [N-1:0] out,
     input  [M-1:0] in,
     input          sign);
    assign out = sign ? {{(N-M){in[M-1]}},in} : {{(N-M){1'b0}},in};
endmodule
```

❖ Hardware if $M = 4$ and $N = 8$:

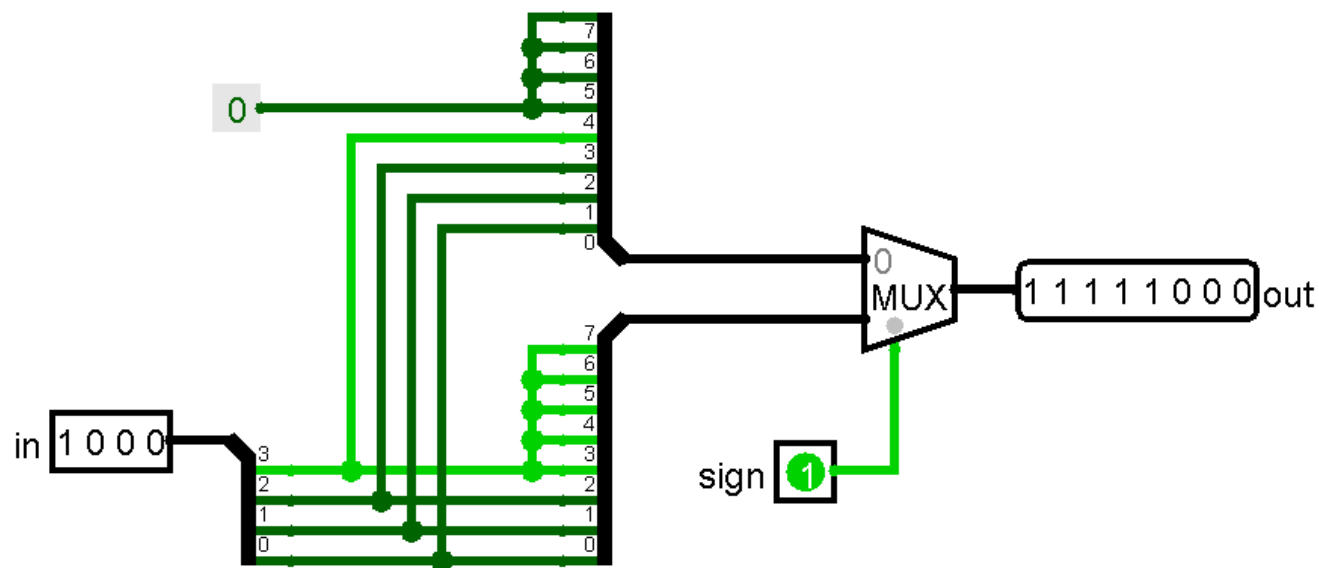

Structural vs. Behavioral Revisited

- ❖ Not a strict definition of these terms, so exact classification is not that important
- ❖ Structural:
 - Instantiating modules (library and user-defined) and defining port connections
 - `assign`: continuous assignment
 - Used with nets

Verilog Procedural Blocks

- ❖ A *procedural block* is made up of behavioral code in the form of procedural statements whose effects are interpreted sequentially
 - The block itself is awakened/triggered in a non-sequential manner
- ❖ **initial**: block triggered once at time zero
 - Non-synthesizable (*i.e.*, for simulation/testbenches only)
- ❖ **always**: block triggered by a *sensitivity list*
 - Any object that is assigned a value in an **always** statement must be declared as a variable (*e.g.*, **logic** or **reg**).

SystemVerilog Procedural Blocks

- ❖ SystemVerilog introduced variants on always that are generally more robust and more specialized
- ❖ `always_comb`: intended for combinational logic
 - Sensitivity list is automatically built
- ❖ `always_latch`: intended for latch-based logic
 - Sensitivity list is automatically built
- ❖ `always_ff`: intended for sequential logic (*i.e.*, synchronous/clocked)
 - Sensitivity list must be specified

Latch vs. Flip-Flop



- ❖ Both are bistable multivibrators (2 stable states) that can store information
- ❖ A latch is *asynchronous*; a flip-flop is *edge-triggered*

```

module my_latch(input logic      clk,
               input logic [3:0] d,
               output logic [3:0] q);

    always_latch
        if (clk) q <= d;

endmodule
    
```

  

```

module my_ff(input logic      clk,
             input logic [3:0] d,
             output logic [3:0] q);

    always_ff @(posedge clk)
        q <= d;

endmodule
    
```

Inferred Latches

- ❖ **Warning:** easy to write code with inadvertent latches
 - Check your synthesis output for “Inferred latch”
 - Usually from *incomplete assignments* – unspecified branch infers latch behavior
- ❖ **Question:** which of the following will synthesize and, if so, what will the hardware look like?

```
always_latch  
  if (clk) q <= d;
```

```
always_comb  
  if (clk) q = d;
```

```
always_latch  
  if (clk) q <= d;  
  else    q <= ~d;
```

```
always_comb  
  if (clk) q = d;  
  else    q = ~d;
```

- Demo: Tools → “Netlist Viewers” → “RTL Viewer”

case Statement

- ❖ Create combinational logic and is easier to read than lots of `if/else` statements
 - Must always be inside an `always` block
 - Each case has an implied C-style break

```
module seven_seg(bcd, segs);  
  
    input  logic [3:0] bcd;  
    output logic [6:0] segs;  
  
    always_comb  
        case (bcd)  
            //                abc_defg  
            0: segs = 7'b011_1111;  
            1: segs = 7'b000_0110;  
            2: segs = 7'b101_1011;  
            3: segs = 7'b100_1111;  
            4: segs = 7'b110_0110;  
            5: segs = 7'b110_1101;  
            6: segs = 7'b111_1101;  
            7: segs = 7'b000_0111;  
            8: segs = 7'b111_1111;  
            9: segs = 7'b110_1111;  
  
        endcase  
  
    endmodule
```

case Statement

- ❖ Create combinational logic and is easier to read than lots of `if/else` statements
 - Must always be inside an `always` block
 - Each case has an implied C-style break
 - Remember to use `default` to avoid incomplete assignments!

```
module seven_seg(bcd, segs);  
  
    input  logic [3:0] bcd;  
    output logic [6:0] segs;  
  
    always_comb  
        case (bcd)  
            //                                abc_defg  
            0: segs = 7'b011_1111;  
            1: segs = 7'b000_0110;  
            2: segs = 7'b101_1011;  
            3: segs = 7'b100_1111;  
            4: segs = 7'b110_0110;  
            5: segs = 7'b110_1101;  
            6: segs = 7'b111_1101;  
            7: segs = 7'b000_0111;  
            8: segs = 7'b111_1111;  
            9: segs = 7'b110_1111;  
            → default: segs = 7'bX;  
        endcase  
  
endmodule
```

Other SystemVerilog Resources

- ❖ SystemVerilog Language Reference Manual
 - On website, Verilog → Reference Manual
 - 586 pages...
- ❖ SystemVerilog articles
 - <https://www.systemverilog.io/>
 - <http://www.verilogpro.com/>
 - <https://www.chipverify.com/systemverilog/systemverilog-tutorial>
- ❖ One style guide for SystemVerilog
 - <https://www.systemverilog.io/styleguide>
 - We won't enforce, but good guidelines


Technology Break

Lecture Outline

- ❖ SystemVerilog Review & Tips (Cont.)
- ❖ **Finite State Machine Design**
- ❖ Test Benches

Finite State Machines (FSMs)

 - ❖ A convenient way to conceptualize computation over time using a *state transition diagram*
 - Consists of a *set of states*, an *initial state*, and a *transition function*
- ❖ FSM implementations come in 3 blocks:
 - State register (SL)
 - Next state logic (CL)
 - Output logic (CL)



FSM Implementation Notes

- ❖ States must be assigned a binary encoding
 - More readable by using parameters or an `enum`
 - Encoding choices can affect logic simplification
- ❖ Reset signal can be synchronous (responds to `clk`) or asynchronous (responds to `reset`)
 - Determined by whether or not `reset` is in sensitivity list
- ❖ State logic (next state logic + state update) can be written as 1 combined block or 2 separate blocks
- ❖ If input is asynchronous, may want to add a two-flip-flop *synchronizer* to deal with metastability

FSM SystemVerilog Design Pattern

❖ Which, if any, construct(s) would you expect to use for each of the following basic sections of a module that implements an FSM?

■ *// define states and state variables*

initial assign always_comb always_ff None

■ *// next state logic (ns)*

initial assign always_comb always_ff None

■ *// output logic*


initial assign always_comb always_ff None

■ *// state update logic (ps)*

initial assign always_comb always_ff None

FSM Example: String Manipulator

 - ❖ Takes in a stream of inputs and removes the *second* 1 from every consecutive string of 1's.



- Example inputs: 0 1 0 1 1 0 1 1 1 0 1 1 1 1 ...
outputs:

String Manipulator FSM

```
module fsm (input logic clk, reset, in,
            output logic out);

    // present and next state
    enum logic [1:0] {S0, S1, S3} ps, ns;

    // next state logic
    always_comb
        case (ps)
            S0: if (in) ns = S1;
                else ns = S0;
            S1: if (in) ns = S3;
                else ns = S0;
            S3: if (in) ns = S3;
                else ns = S0;
        endcase

    // output logic
    assign out = in & (ps[1] | ~ps[0]);

    ...
```

```
...

    // sequential logic (DFFs)
    // synchronous reset
    always_ff @(posedge clk)
        if (reset)
            ps <= S0; // reset state
        else
            ps <= ns;

endmodule // fsm
```


Moore vs. Mealy

- ❖ **Moore** machines define their outputs based on states ($\textcircled{00/1}$) and **Mealy** machines define outputs based on transitions ($\xrightarrow{0/1}$)
 - Mealy machines are more *flexible*
 - Moore outputs are function of state; Mealy outputs are function of state *and inputs*
 - All FSMs can be expressed in either form, but some systems are more naturally expressed one way versus the other
 - Feel free to use either in this class if not specified
 - However, there *are* implementation differences!

Mealy \leftrightarrow Moore Conversions

Not testable
material

 
- ❖ **Moore \rightarrow Mealy:** copy the state output to every transition *entering* the state
- ❖ Example: FSM for a *turnstile*, which is locked until someone swipes their Husky ID (input H) and then locks once you push through (input P) the unlocked gate. Outputs a light that glows red (0) or green (1).



Mealy \leftrightarrow Moore Conversions

Not testable
material

 
- ❖ **Mealy \rightarrow Moore:** more complicated process; if incoming transitions differ in output, may need to “split” the state
- ❖ Example: the threeOnes FSM from Lecture 1



Moore vs. Mealy Outputs

- ❖ Compare a Moore and Mealy FSM for the turnstile. Complete the statements and waveform below, assuming no delays:



Moore:

 

```


assign out_moore =
assign out_mealy =
  
```

Mealy:

  


Moore vs. Mealy Outputs

❖ Moore:

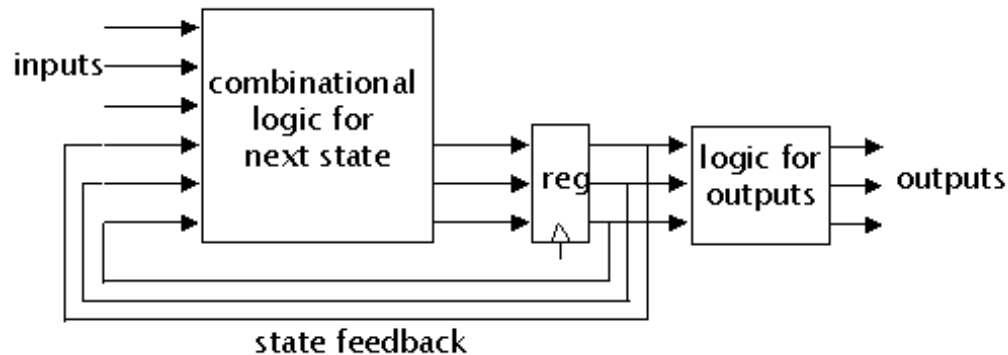

- Outputs change synchronously with state changes

❖ Mealy:

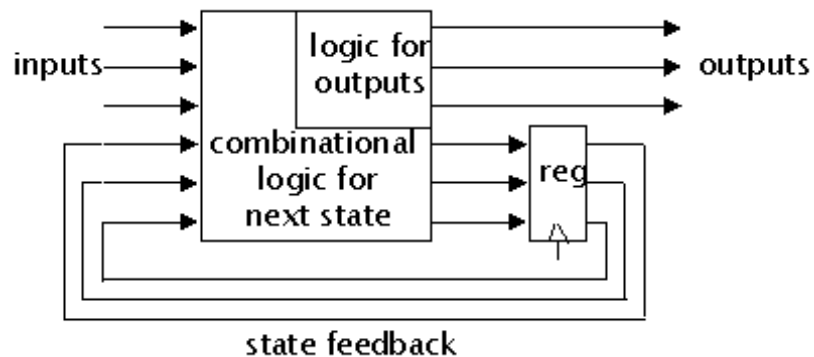

- Input changes can cause *immediate* output changes

Lecture Outline

- ❖ SystemVerilog Review & Tips (Cont.)
- ❖ Finite State Machine Design
- ❖ **Test Benches**

Test Benches

- ❖ Special modules *needed for simulation only!*
 - Software constraint to mimic hardware
- ❖ ModelSim runs entirely on your computer
 - Tries to simulate your FPGA environment without actually using hardware – no physical signals available
 - Must create fake inputs for FPGA's physical connections
 - *e.g.*, LEDR, HEX, KEY, SW, CLOCK_50
 - Unnecessary when code is loaded onto FPGA
- ❖ Need to define both input signal combinations as well as their *timing*

Test Bench Timing Controls

- ❖ Delay: `#<time>`
 - Delays by a specific amount of simulation time
- ❖ Edge-sensitive: `@(<pos/neg>edge <signal>)`
 - Delays next statement until specified transition on signal
- ❖ Level-sensitive Event: `wait(<expression>)`
 - Waits until `<expression>` evaluates to TRUE
- ❖ Stop simulation: `$stop;`
- ❖ Timescale: ``timescale <time unit> / <precision>`
 - *e.g.*, ``timescale 1 ns / 1 ps`

Extender Test Bench

```


`timescale 1 ns / 1 ns
module extender_tb();

    parameter M = 4, N = 8;
    logic [M-1:0] in;
    logic [N-1:0] out;
    logic sign;

    extender #(M, N) dut (.*);

    int i;
    initial begin
        for (i = 0; i < 2**2; i++) begin
            sign = i[0]; in = {i[1], {(M-1){1'b0}}}; #10;
        end // for
        $stop;
    end // initial
endmodule // extender_tb

```

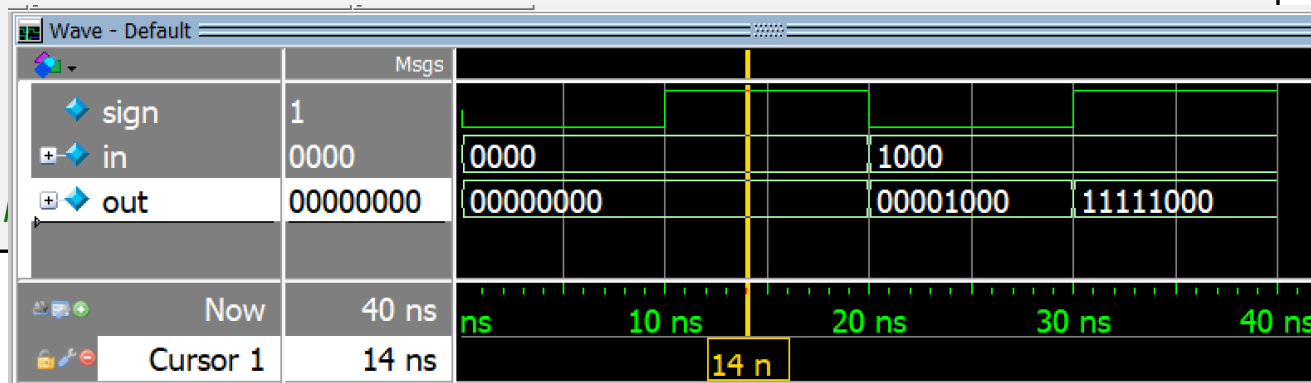

FSM Test Bench Notes

- ❖ Your main goal is to test *every transition* that we care about – may take extra clock cycles
- ❖ For simulation, you need to generate a clock signal
 - Assume we have `parameter clock_period;`

Explicit
Edges:

```
initial
    clk = 0;

always_comb begin
    #(clock_period/2) clk <= 1;
    #(clock_period/2) clk <= 0;
end
```

Toggle:



```
initial begin
    clk <= 0;
    forever #(clock_period/2) clk <= ~clk;
end
```

String Manipulator Test Bench

```
module fsm_tb();  
    logic clk, reset, in, out;  
    fsm dut (.*);  
  
    // simulated clock  
    parameter period = 100;  
    initial begin  
        clk <= 0;  
        forever  
            #(period/2)  
            clk <= ~clk;  
    end // initial clock  
    ...
```

```
    ...  
    initial begin  
        reset <= 1; in <= 0; @(posedge clk);  
        reset <= 0; in <= 0; @(posedge clk);  
        in <= 0; @(posedge clk);  
        in <= 1; @(posedge clk);  
        in <= 0; @(posedge clk);  
        in <= 1; @(posedge clk);  
        in <= 1; @(posedge clk);  
        in <= 0; @(posedge clk);  
        in <= 1; @(posedge clk);  
        in <= 1; @(posedge clk);  
        in <= 1; @(posedge clk);  
        @(posedge clk);  
        $stop; // end simulation  
    end // initial signals  
endmodule // fsm_tb
```

String Manipulator Waveforms

  


Checking Responses

- ❖ Visually checking simulated waveforms quickly becomes impractical for large designs simulated over thousands of clock cycles
 - Displaying and explaining your waveforms for labs can be tedious
- ❖ There are simulator-independent system tasks to write messages to the user/tester!
 - Look similar to `printf()` in C
 - `$<system_task>(<format_string>, <sig_1>, <sig_2>, ...)`
 - Will look at `$display` today and others later on

Checking Responses: \$display

- ❖ Triggers once when encountered, prints the given format string and adds a new line:
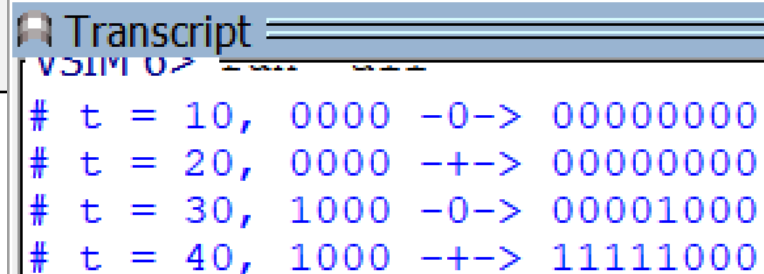
```
// define test inputs
int i;
initial begin
    for (i = 0; i < 2**2; i++) begin
        sign = i[0]; in = {i[1], {(M-1){1'b0}}}; #10;
        $display("t = %0t, %b %s %b",
                $time, in, sign ? "-+->" : "-0->", out);
    end // for
    $stop;
end // initial
```



Transcript

```
VSIM O> run -all
# t = 10, 0000 -0-> 00000000
# t = 20, 0000 -+-> 00000000
# t = 30, 1000 -0-> 00001000
# t = 40, 1000 -+-> 11111000
```

Format Specifiers

Table 5.7: Format Specifiers.

Specifier	Meaning
%h	Hexadecimal format
%d	Decimal format
%o	Octal format
%b	Binary format
%c	ASCII character format
%v	Net signalstrength
%m	Hierarchical name of current scope
%s	String
%t	Time
%e	Real in exponential format
%f	Real in decimal format
%g	Real in exponential or decimal format

Table 5.8: Special characters.

Symbol	Meaning
\n	New line
\t	Tab
\\	\character
\"	" character
\xyz	Where xyz is are octal digits - the character given by that octal code
%%	% character

- **Warning:** these differ from the specifiers for `printf`
- The *minimum* field width is specified by numbers between the '%' and specifier letter
 - e.g., %3d will pad out to 3 digits if necessary,
%0d will show just the minimum number of digits needed