



ECE TUTORING

**DROP-IN
TUTORING
AVAILABLE
FOR A SELECTION
OF EE
UNDERGRADUATE
CLASSES!**

**SCAN QR CODE TO VIEW THE
TUTORING SCHEDULE**



NOW LOCATED IN ECE RM 443!

**Take the elevator to floor 4R and
follow signage to 443.**



Design of Digital Circuits and Systems

ASM with Datapath I

Instructor: Vikram Iyer

Teaching Assistants:

Ariel Kao

Josh Wentzien

Selim Saridede

Jared Yoder


Derek Thorp

Adapted from material by Justin Hisa

Relevant Course Information



- ❖ Homework 2 late deadline tonight (4/17)
- ❖ Homework 3 due next Friday (4/25)
 - FIFO buffers & ASM charts
- ❖ Lab 2 reports due Friday (4/18), demos 4/21-25
- ❖ Lab 3 due 5/2
 - Lab 3 + 4 are really ~1.5 weeks long, so don't wait!
- ❖ Quiz 2 next Thursday (4/24)
 - Memory (ROM, RAM, reg files)

Review: ASM Chart

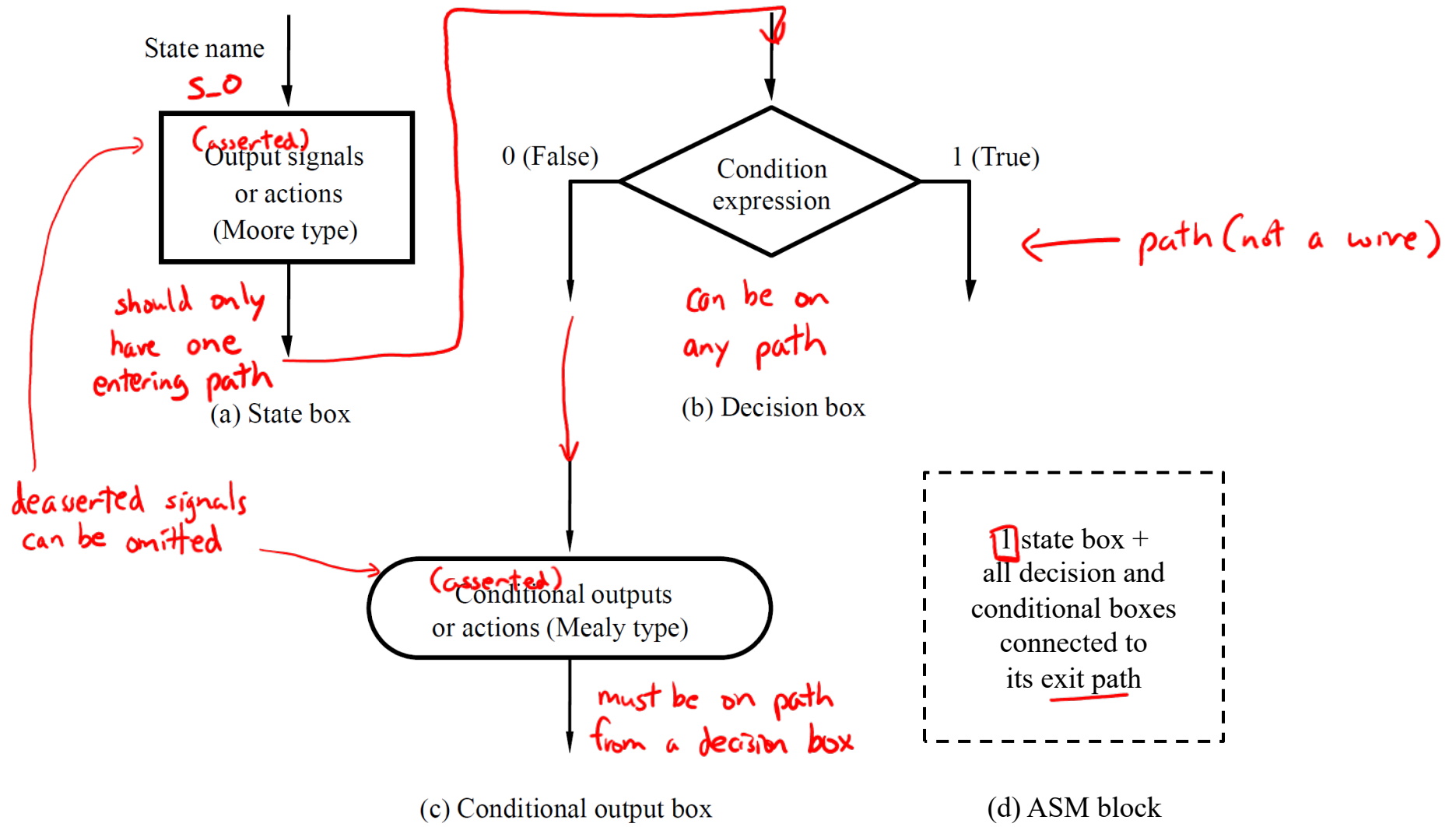


Review Question: 3-way Switch

  - ❖ Create an ASM chart for a 3-way switch system using Mealy-type output
 - LTog and RTog pulse 1 when switch is flipped/toggled, output called light




Moore

 


ASMD Charts

 - ❖ An **A**lgorithmic **S**tate **M**achine with a **D**atapath chart is created by adding RTL operations to an ASM chart
 - Timing of operations can be confusing – *NOT* a flowchart
- ❖ School of Thought #1:
 - RTL operations are triggered by control signals, so they can appear anywhere an output signal can:




ASMD Charts

 - ❖ An **A**lgorithmic **S**tate **M**achine with a **D**atapath chart is created by adding RTL operations to an ASM chart
 - Timing of operations can be confusing – *NOT* a flowchart
- ❖ School of Thought #2:
 - It's clearer to separate control signals (Control) from RTL operations (Datapath)
- ❖ There isn't a set standard
 - You may see both or variants
 - ***We use School of Thought #2***




ASMD Hardware

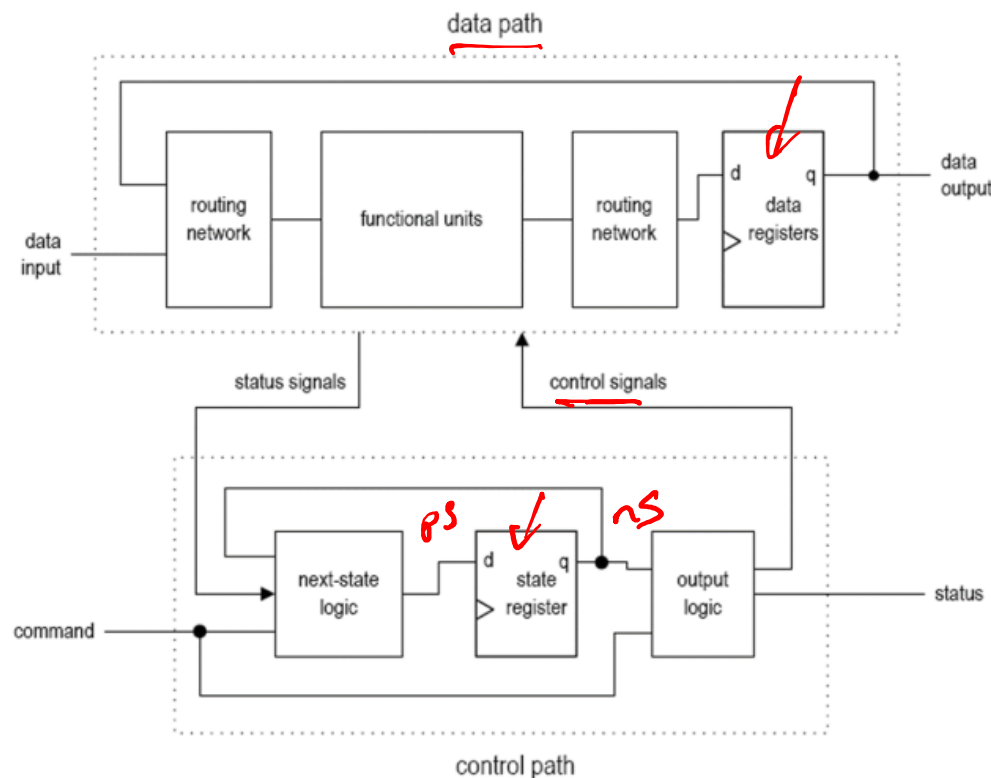- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





ASMD Hardware

 - ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!
- ❖ The behavior of both state and data registers depend on the current control state
 - Can conceptually think of as a MUX to the registers' inputs that uses the current state as its selector bits





Hardware Example #1

  - ❖ State transitions and RTL operations are both controlled by the clock
- It's often helpful to remember the underlying hardware – registers!





Hardware Example #1

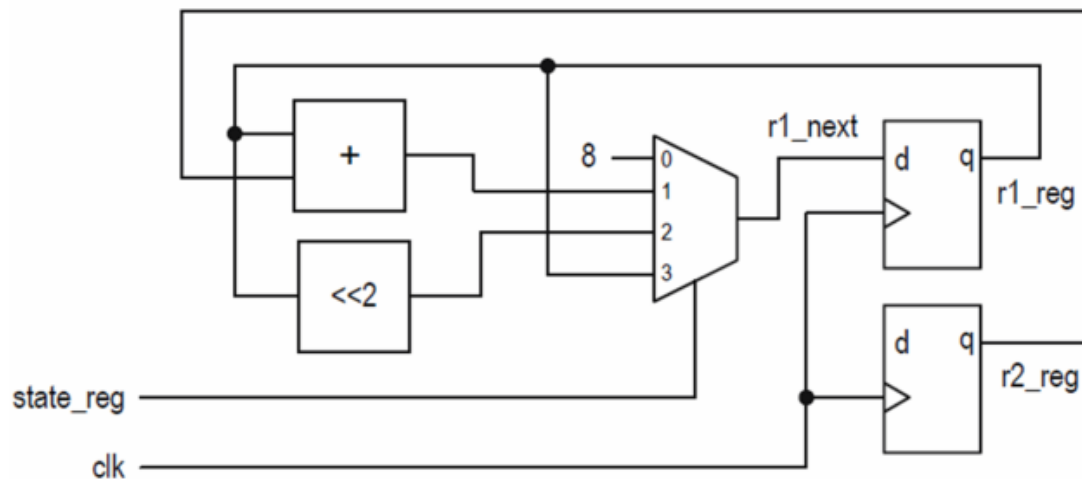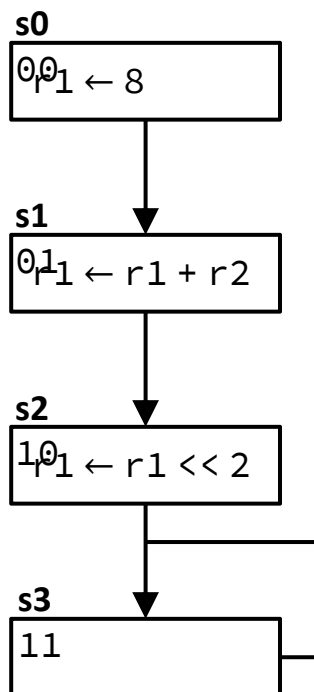- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





Hardware Example #2

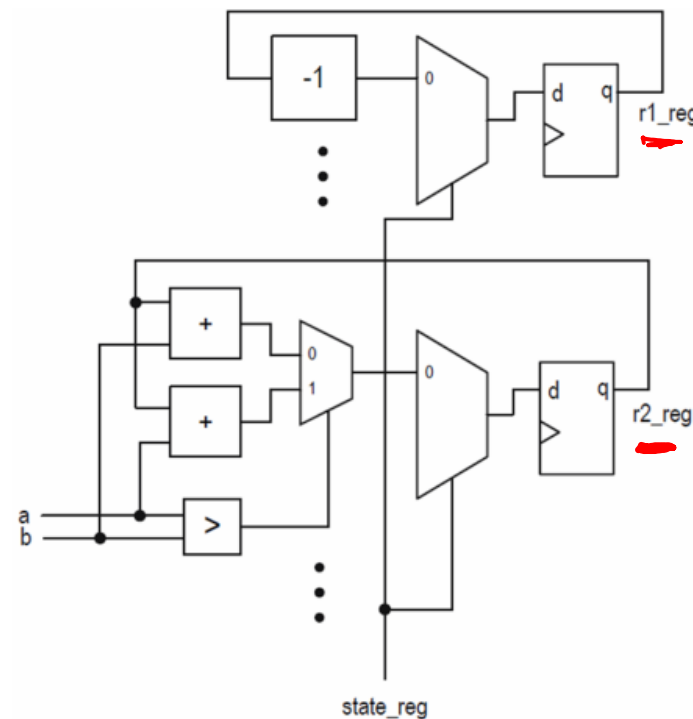 - ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers! *s - idle*





ASMD Timing

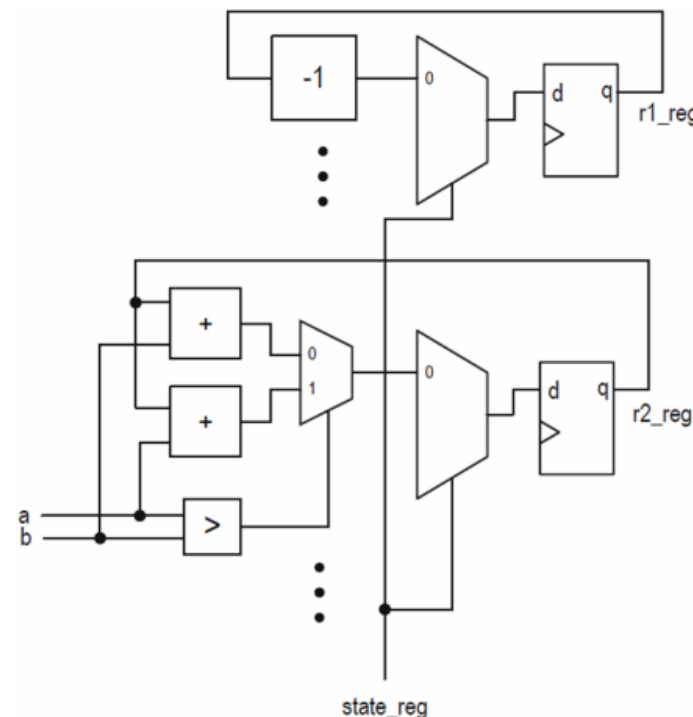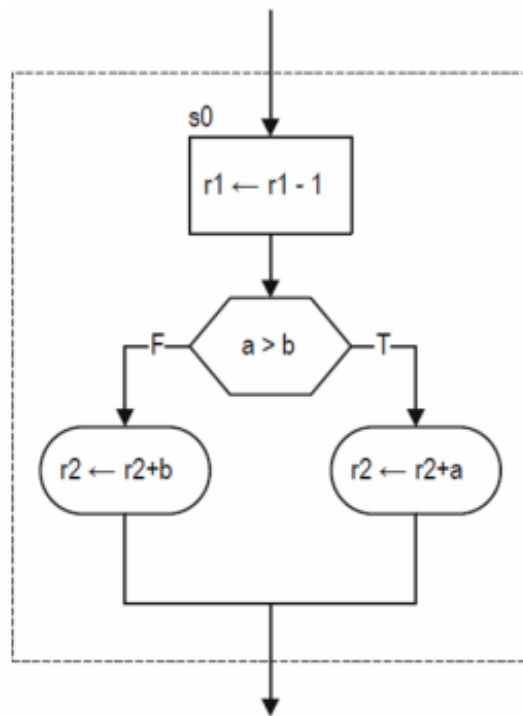- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than *entrance*



ASMD Timing

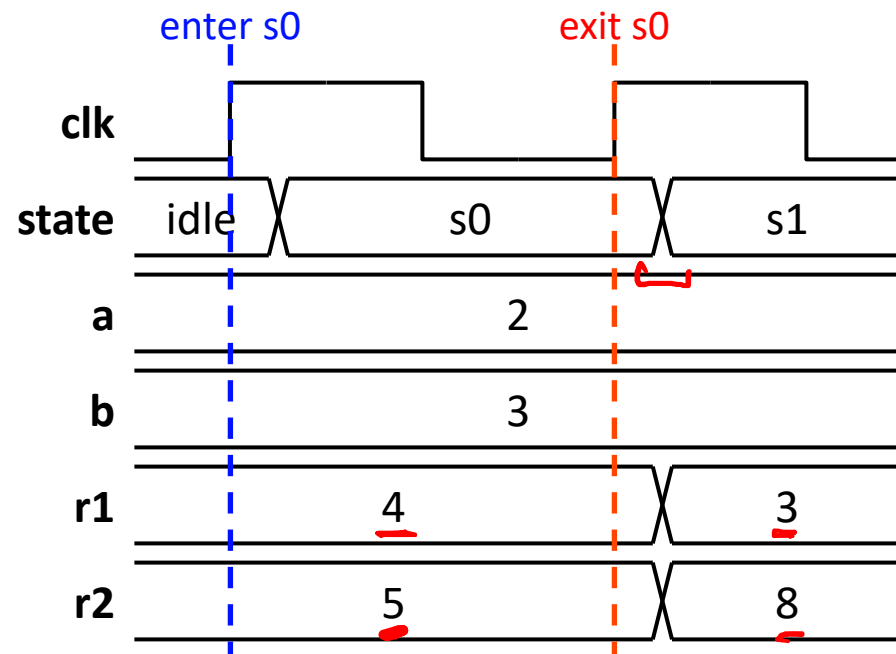 
- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than *entrance*



ASMD Timing Question


- ❖ What value will be stored in r when we transition from state $s1$ to the next state? -1, 0, 1

exit when $r = 0$
 $0 - 1 = -1$

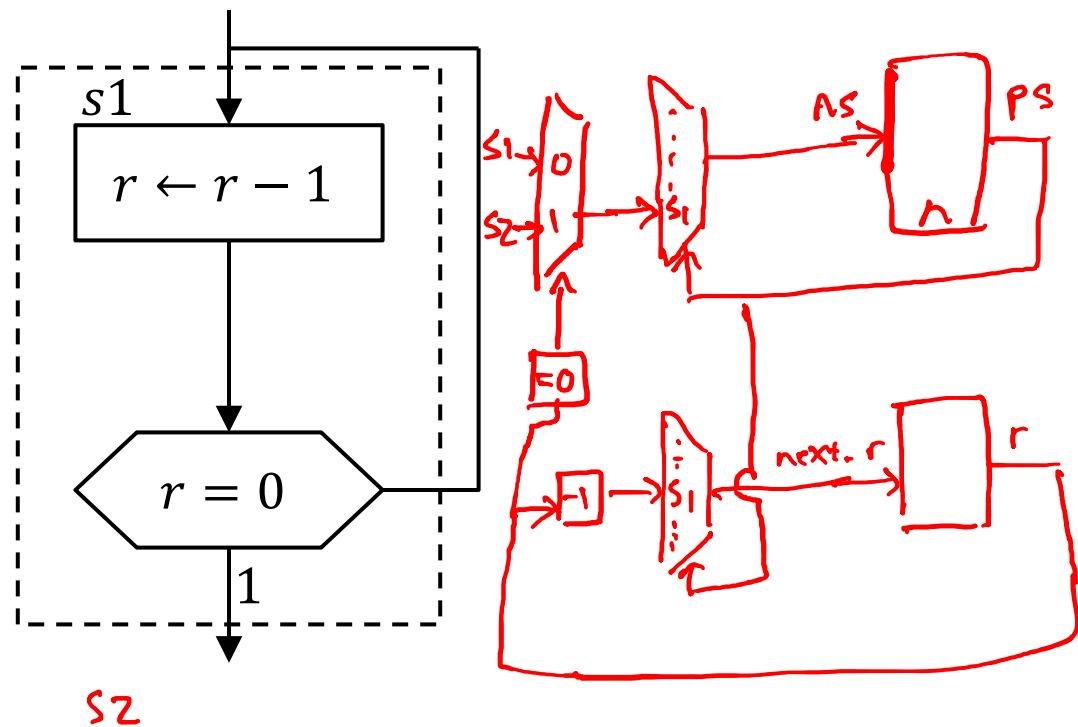


ASMD Timing

 
- ❖ When a registered output (e.g., r) is used in a decision box, its effect may appear to be delayed by one clock
- Can define a next-state value (e.g., r_next) to use instead



(a) Use old value of r

 

(b) Use new value of r

 

Short Tech

Break




ASMD Design Procedure

- ❖ From problem description or algorithm pseudocode:
 - 1) Identify necessary datapath components and operations
 - 2) Identify states and signals that cause state transitions (external inputs and status signals), based on the necessary sequencing of operations
 - 3) Name the control signals that are generated by the controller that cause the indicated operations in the datapath unit

$r_1 \leftarrow r_1 + 1$ — incr. r_1
 - 4) Form an ASM chart for your controller, using states, decision boxes, and signals determined above
 - 5) Add the datapath RTL operations associated with each control signal

Design Example #1


❖ System specification:

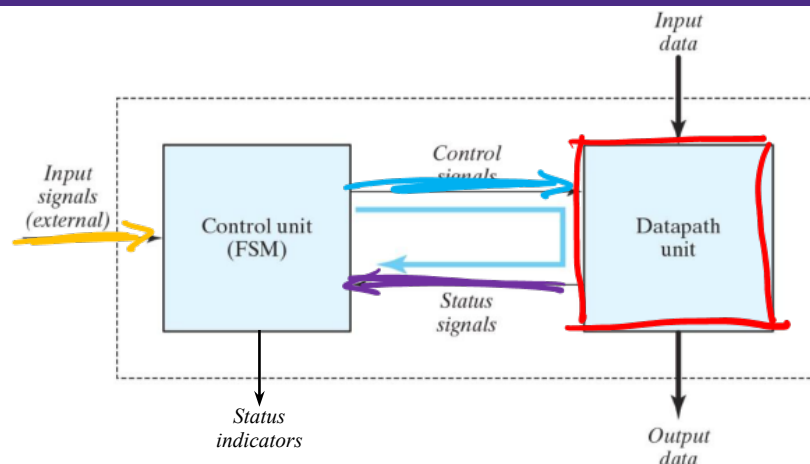

- datapath
 - Flip-flops E and F
 - 4-bit binary up-counter A = $0bA_3A_2A_1A_0$
- input to ctrl
 - Active-low reset signal $reset_b$ puts us in state S_idle , where we remain while signal $Start$ = 0
 - $Start = 1$ initiates the system's operation by clearing A and F . At each subsequent clock pulse, the counter is incremented by 1 until the operations stop.
- control signals
 - status
 - Bits A_2 and A_3 determine the sequence of operations:
 - If $A_2 = 0$, set E to 0 and the count continues ← clr_A
 - If $A_2 = 1$, set E to 1; additionally, if $A_3 = 0$, the count continues, otherwise, wait one clock pulse to set F to 1 and stop counting (i.e., back to S_idle) ← set_F

Design Example #1

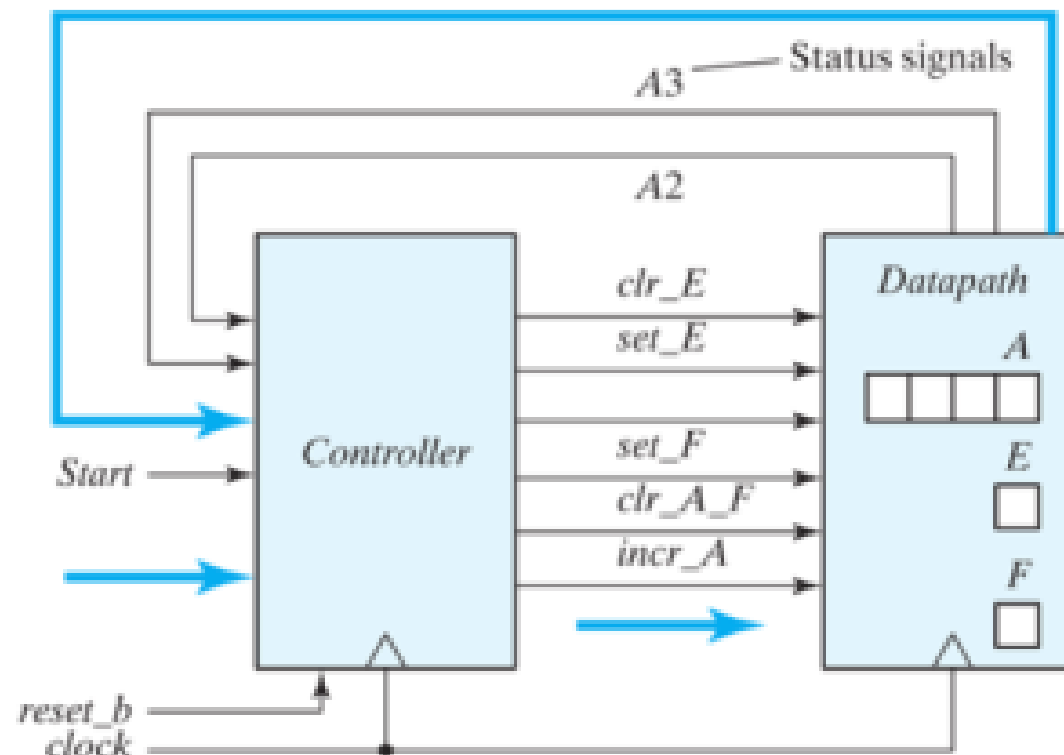
- ❖ The system can be represented by the following block diagram:



Design Example #1 (ASM → ASMD Chart)

1100

- ❖ Synchronous or asynchronous reset?

 

Design Example #1 (Timing)

❖ Sequence of operations:

Counter				Flip-Flops		Conditions	State
A_3	A_2	A_1	A_0	E	F		
X	X	X	X	1	X	Start	S_idle
0	0	0	0	1	0	$A_2 = 0, A_3 = 0$	S_count
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_2 = 1, A_3 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_2 = 0, A_3 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_2 = 1, A_3 = 1$	
1	1	0	1	1	0		S_F
1	1	0	1	1	1		S_idle

Design Example #1 (Logic)

❖ Controller:

■ State Table:

	Present State		Inputs			Next State		Outputs				
Present-State Symbol	P_1	P_0	Start	A_2	A_3	N_1	N_0	set_E	clr_E	set_F	clr_A_F	incr_A
S_idle	0	0	0	X	X	0	0	0	0	0	0	0
S_idle	0	0	1	X	X	0	1	0	0	0	1	0
S_count	0	1	X	0	X	0	1	0	1	0	0	1
S_count	0	1	X	1	0	0	1	1	0	0	0	1
S_count	0	1	X	1	1	1	1	1	0	0	0	1
S_F	1	1	X	X	X	0	0	0	0	1	0	0

■ Logic:

$$\begin{aligned}
 N_1 &= S_count \cdot A_2 A_3 & set_F &= S_F \\
 N_0 &= S_count + S_idle \cdot Start & clr_A_F &= S_idle \cdot Start \\
 set_E &= S_count \cdot A_2 & incr_A &= S_count \\
 clr_E &= S_count \cdot \bar{A}_2
 \end{aligned}$$

Short Tech Break

Design Example #1 (SV, Controller)

control signals (out)
status signals (in)
external inputs (in)

```
module controller (set_E, clr_E, set_F, clr_A_F,  
                  incr_A, A2, A3, Start, clk,  
                  reset_b);  
  
    // port definitions  
    input logic Start, clk, reset_b, A2, A3;  
    output logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // define state names and variables  
  
    // controller logic w/synchronous reset
```

Design Example #1 (SV, Controller)

control signals (out)
status signals (in)
external inputs (in)

```
module controller (set_E, clr_E, set_F, clr_A_F,  
                  incr_A, A2, A3, Start, clk,  
                  reset_b);  
  
    // port definitions  
    input logic Start, clk, reset_b, A2, A3;  
    output logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // define state names and variables  
    enum logic [1:0] {S_idle, S_count, S_F = 2'b11}  
    ps, ns;  
  
    // controller logic w/synchronous reset  
    always_ff @(posedge clk)  
        if (~reset_b)  
            ps <= S_idle;  
        else  
            ps <= ns;
```

Design Example #1 (SV, Controller)

```
// next state logic
```

```
// output assignments
```

```
endmodule // controller
```

Design Example #1 (SV, Controller)

```
// next state logic
always_comb
    case (ps)
        S_idle: ns = Start ? S_count : S_idle;
        S_count: ns = (A2 & A3) ? S_F : S_count;
        S_F:      ns = S_idle;
    endcase
```

```
// output assignments
assign set_E    = (ps == S_count) & A2;
assign clr_E    = (ps == S_count) & ~A2;
assign set_F    = (ps == S_F);
assign clr_A_F  = (ps == S_idle) & Start;
assign incr_A   = (ps == S_count);
```

```
endmodule // controller
```

control signals (in)
status signals (out)
external inputs (in)
external outputs (out)

29

Design Example #1 (SV, Datapath)

control signals (in)
status signals (out)
external inputs (in)
external outputs (out)

```
module datapath (A, E, F, clk, set_E, clr_E, set_F, clr_A_F,  
                incr_A);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input  logic clk, set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // datapath logic  
    always_ff @(posedge clk) begin  
        if (clr_E)      E <= 1'b0;  
        else if (set_E) E <= 1'b1;  
        if (clr_A_F)  
            begin  
                A <= 4'b0;  
                F <= 1'b0;  
            end  
        else if (set_F)  F <= 1'b1;  
        else if (incr_A) A <= A + 4'h1;  
    end // always_ff  
  
endmodule // datapath
```

Design Example #1 (SV, Top-Level Design)

```
module top_level (A, E, F, clk, Start, reset_b);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input  logic clk, Start, reset_b;  
  
    // internal signals  
    logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // instantiate controller and datapath  
    controller c_unit (.set_E, .clr_E, .set_F,  
                      .clr_A_F, .incr_A, .A2(A[2]),  
                      .A3(A[3]), .Start, .clk,  
                      .reset_b);  
    datapath d_unit (.*);  
  
endmodule // top_level
```