

Design of Digital Circuits and Systems

ASM with Datapath II

Instructor: Vikram Iyer

Teaching Assistants:

Ariel Kao

Josh Wentzien

Selim Saridede

Jared Yoder

Derek Thorp



Adapted from material by Justin Hisa

Relevant Course Information

- ❖ Homework 3 due Friday (4/25)
- ❖ Homework 4 released Thursday

- ❖ Quiz 2 (ROM, RAM, Reg files) this Thu at 11:50 am
 - Based heavily on Homework 2
 - Memory sizing, addressing, initialization, and implementation (*i.e.*, circuit diagram)


- ❖ Lab 3 reports due next Friday (5/2)
 - Ideally finish by early next week so you can start Lab 4, which will be released this Thursday

ASMD Design Procedure

- ❖ From problem description or algorithm pseudocode:
 - 1) Identify necessary datapath components and operations**
 - 2) Identify states and signals that cause state transitions**
(external inputs and status signals), based on the necessary sequencing of operations
 - 3) Name the control signals** that are generated by the controller that cause the indicated operations in the datapath unit
 - 4) Form an ASM chart for your controller**, using states, decision boxes, and signals determined above
 - 5) Add the datapath RTL operations** associated with each control signal

Design Example

❖ System specification:

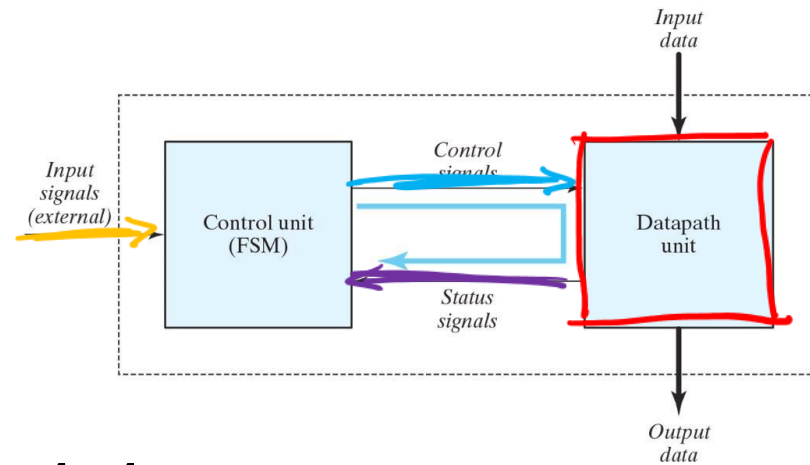

datapath ■ Flip-flops E and F

datapath ■ 4-bit binary counter A = $0bA_3A_2A_1A_0$

inputs to control ■ Active-low reset signal $reset_b$ puts us in state S_idle , where we remain while signal $Start$ = 0

control signals ■ $Start$ = 1 initiates the system's operation by clearing A and F . At each subsequent clock pulse, the counter is incremented by 1 until the operations stop. *clr_A-F*



status signals ■ Bits A_2 and A_3 determine the sequence of operations: *incr_A*

- If $A_2 = 0$, set E to 0 and the count continues *clr_E*
 - If $A_2 = 1$, set E to 1; additionally, if $A_3 = 0$, the count continues, otherwise, wait one clock pulse to set F to 1 and stop counting (i.e., back to S_idle) *set_E*
- set_F*

Design Example #1 (ASMD Chart)

❖ Synchronous or asynchronous reset?

  for synchronous reset, add decision box on reset-b out of every state box:



Design Example #1 (SV, Controller)

control signals (out)
status signals (in)
external inputs (in)

```
module controller (set_E, clr_E, set_F, clr_A_F,  
                  incr_A, A2, A3, Start, clk,  
                  reset_b);  
  
    // port definitions  
    input logic Start, clk, reset_b, A2, A3;  
    output logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // define state names and variables  
    enum logic [1:0] {S_idle, S_1, S_2 = 3} ps, ns;  
  
    // controller logic w/synchronous  
    always_ff @(posedge clk)  
        if (~reset_b)  
            ps <= S_idle;  
        else  
            ps <= ns;
```

```
    // next state logic  
    always_comb  
        case (ps)  
            S_idle: ns = Start ? S_1 : S_idle;  
            S_1:    ns = (A2 & A3) ? S_2 : S_1;  
            S_2:    ns = S_idle;  
        endcase  
  
    // output assignments  
    assign set_E = (ps == S_1) & A2;  
    assign clr_E = (ps == S_1) & ~A2;  
    assign set_F = (ps == S_2);  
    assign clr_A_F = (ps == S_idle) & Start;  
    assign incr_A = (ps == S_1);  
  
endmodule // controller
```

Design Example #1 (SV, Datapath)

control signals (in)
 status signals (out)
 external inputs (in)
 external outputs (out)

```

module datapath (A, E, F, clk, set_E, clr_E, set_F, clr_A_F,
                 incr_A);

  // port definitions
  output logic [3:0] A;
  output logic E, F;
  input  logic clk, set_E, clr_E, set_F, clr_A_F, incr_A;

  // datapath logic
  always_ff @(posedge clk) begin
    if (clr_E)      E <= 1'b0;
    else if (set_E)  E <= 1'b1;
    if (clr_A_F)
      begin
        A <= 4'b0;
        F <= 1'b0;
      end
    else if (set_F)  F <= 1'b1;
    else if (incr_A) A <= A + 4'h1;
  end // always_ff

endmodule // datapath
  
```




Design Example #1 (SV, Top-Level Design)

```
module top_level (A, E, F, clk, Start, reset_b);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input logic clk, Start, reset_b;  
  
    // internal signals (control signals and status signals that aren't outputs)  
    logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // instantiate controller and datapath  
    controller c_unit (.set_E, .clr_E, .set_F,  
                      .clr_A_F, .incr_A, .A2(A[2]),  
                      .A3(A[3]), .Start, .clk,  
                      .reset_b);  
  
    datapath d_unit (.*);  
  
endmodule // top_level
```


Design Example #2: Fibonacci

 - ❖ Design a sequential Fibonacci number circuit with the following properties:



- *i* is the desired sequence number
- *f* is the computed Fibonacci number:

$$fib(i) = \begin{cases} 0, & i = 0 \\ 1, & i = 1 \\ fib(i-1) + fib(i-2), & i > 1 \end{cases}$$

- ready means the circuit is idle and ready for new input
- *start* signals the beginning of a new computation
- *done_tick* is asserted for 1 cycle when the computation is complete

Design Example #2 (Pseudocode)

❖ Pseudocode analysis:

- Variables are part of **datapath**; assignments become RTL operations
- Chunks of related actions should be triggered by **control signals**
- Decision points become **status signals**

Design Example #2 (Control-Datapath)

i = 0
if ($i == 0$) return 0;

adder


init
 $f_{m1} = 1$;
 $f_{m2} = 0$;

n = i


for n from 2 to $i-1$ (inclusive)

iterate
temp = f_{m2}
 $f_{m2} = f_{m1}$
 $f_{m1} = \text{temp} + f_{m2}$

return $f_{m1} + f_{m2}$

 

Design Example #2 (ASMD Chart)

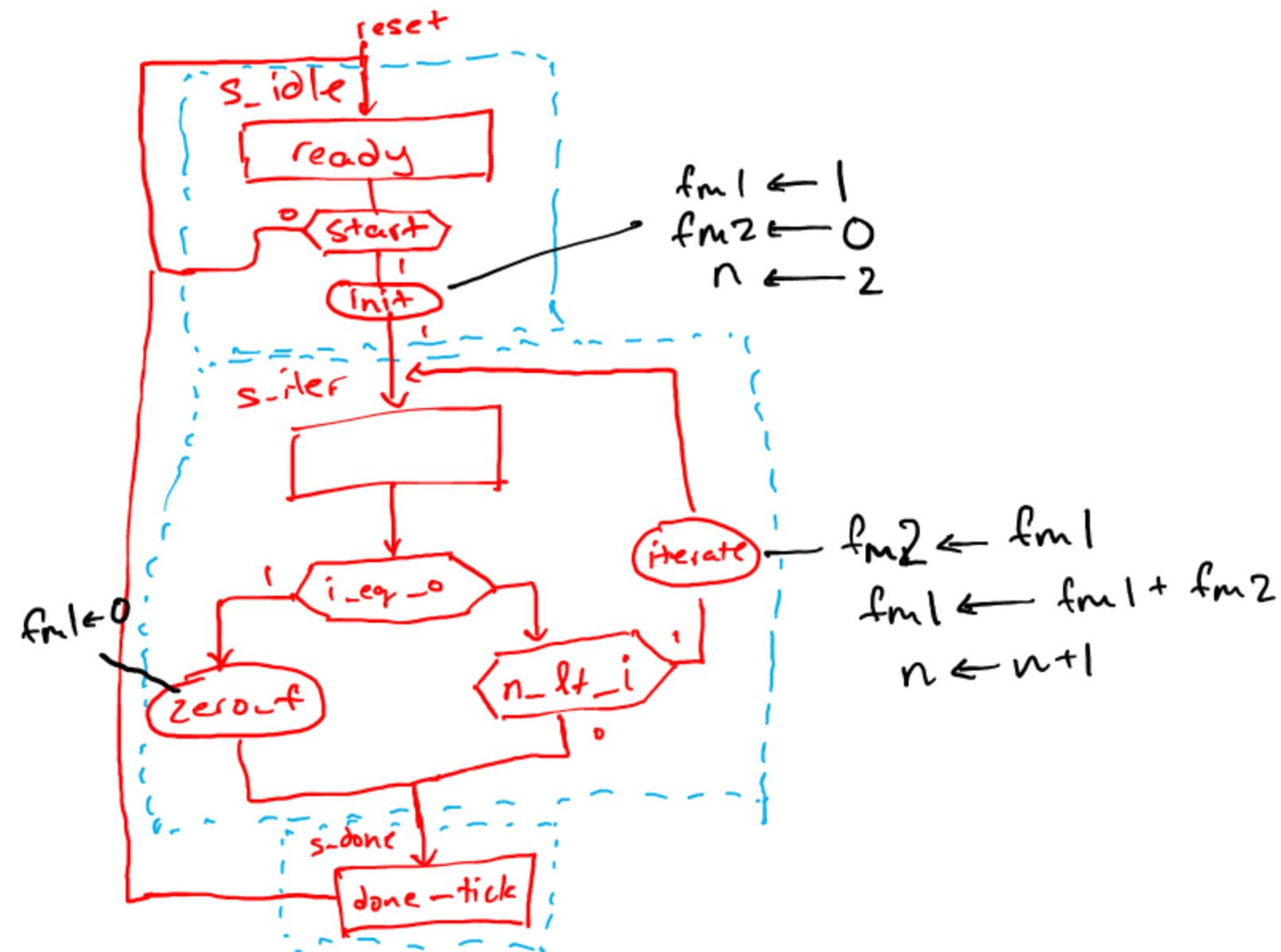

Design Example #2 (SV)

```
fib_control:
    // port definitions
    // define state names and variables
    // controller logic w/synchronous reset
    // next state logic
    // output assignments

fib_datapath:
    // port definitions
    // datapath logic

fib:
    // port definitions
    // define status and control signals
    // instantiate control and datapath
```

Other Hardware Algorithms

- ❖ Sequential binary multiplier or divider
- ❖ Arithmetic mean
- ❖ Lab 4: Bit counting
- ❖ Lab 4: Binary search
- ❖ Lab 5: Bresenham's line

Technology Break

Hardware Acceleration

- ❖ ASMD as a design process can be used to implement software algorithms
- ❖ Custom hardware can accelerate operation:
 - Hardware can better exploit parallelism
 - Hardware can implement more specialized operations
 - Hardware can reduce “processor overhead”
(*e.g.*, instruction fetch, decoding)
- ❖ “Hardware accelerators” are frequently used to complement processors to speed up common, computationally-intensive tasks
 - *e.g.*, encryption, machine vision, cryptocurrency mining

Binary Multiplication

❖ Multiplication of unsigned numbers

(a) Multiplication by hand

Multiplicand M (14)	1 1 1 0
Multiplier Q (11)	x 1 0 1 1

	1 1 1 0
	1 1 1 0
	0 0 0 0
	1 1 1 0

Product P (154)	1 0 0 1 1 0 1 0

(b) Using multiple adders

Multiplicand M (14)	1 1 1 0
Multiplier Q (11)	x 1 0 1 1

Partial product 0	1 1 1 0
	+ 1 1 1 0

Partial product 1	1 0 1 0 1
	+ 0 0 0 0

Partial product 2	0 1 0 1 0
	+ 1 1 1 0


Product P (154)	1 0 0 1 1 0 1 0

(c) Hardware implementation

		m_3	m_2	m_1	m_0	
	x	q_3	q_2	q_1	q_0	
Partial product 0		m_3q_0	m_2q_0	m_1q_0	m_0q_0	
		+ m_3q_1	m_2q_1	m_1q_1	m_0q_1	
Partial product 1		$PP1_5$	$PP1_4$	$PP1_3$	$PP1_2$	$PP1_1$
		+ m_3q_2	m_2q_2	m_1q_2	m_0q_2	
Partial product 2		$PP2_6$	$PP2_5$	$PP2_4$	$PP2_3$	$PP2_2$
		+ m_3q_3	m_2q_3	m_1q_3	m_0q_3	
Product P		p_7	p_6	p_5	p_4	p_3
						p_2
						p_1
						p_0

Parallel Binary Multiplier

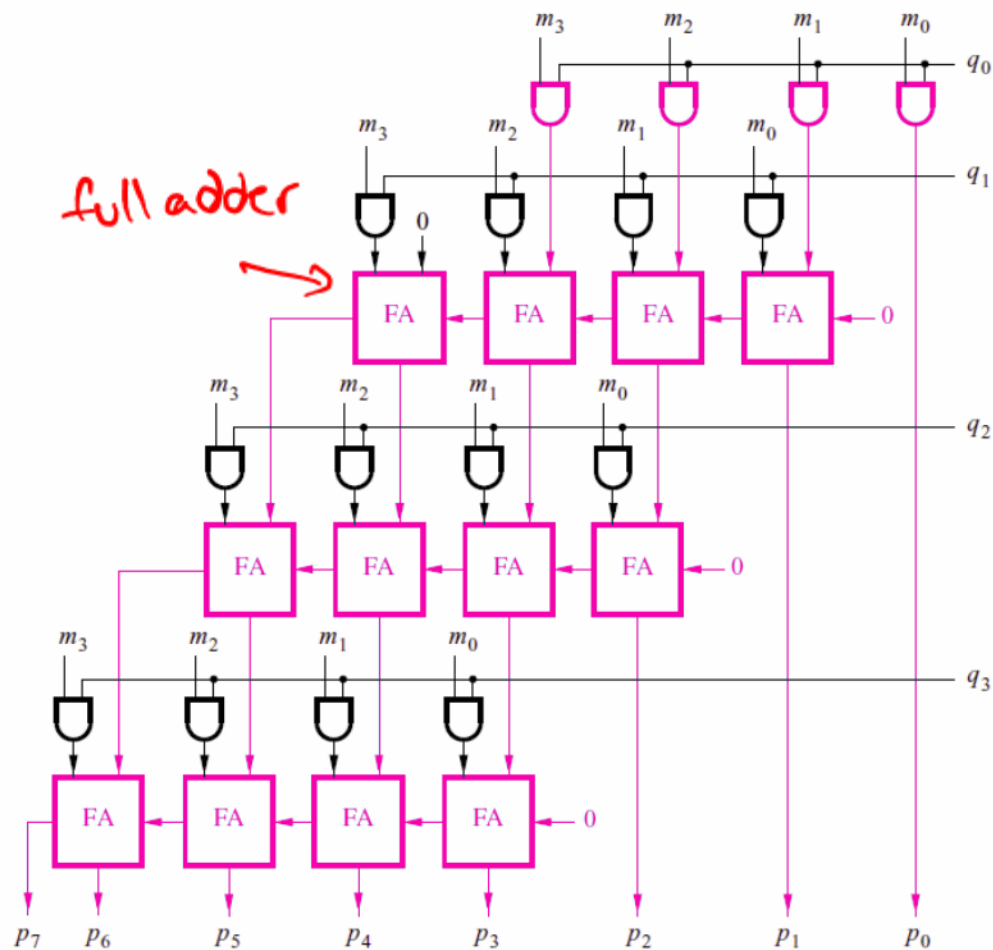- ❖ *Parallel* multipliers require a lot of hardware



Sequential Binary Multiplier

- ❖ Design a *sequential* multiplier that uses only one adder and a shift register
 - Assume one clock cycle to shift and one clock cycle to add
 - More efficient in hardware, less efficient in time
- ❖ Considerations:
 - n -bit **multiplicand** and **multiplier** yield a product at most how wide? $2n$
 - What are the ports for an n -bit adder? *carry out*
 - How many shift-and-adds do we do and how do we know when to stop? n *rounds*

Sequential Binary Multiplier


- ❖ Design a *sequential* multiplier that uses only one adder and a shift register
 - Assume one clock cycle to shift and one clock cycle to add
 - More efficient in hardware, less efficient in time
- ❖ Implementation Notes:
 - If current bit of **multiplier** is 0, then skip the adding step
 - Instead of shifting **multiplicand** to the left, we will shift the **partial sum** (and the **multiplier**) *to the right*
 - We will re-use the **multiplier** register for the lower half of the product
 - Treat **carry**, **partial sum**, and **multiplier** as one shift register $\{\underline{C}, \underline{A}, \underline{Q}\}$

Sequential Binary Multiplier Operation

❖ A few steps of:

$$\begin{array}{r} 11010111 \\ \times 00010111 \\ \hline \end{array}$$

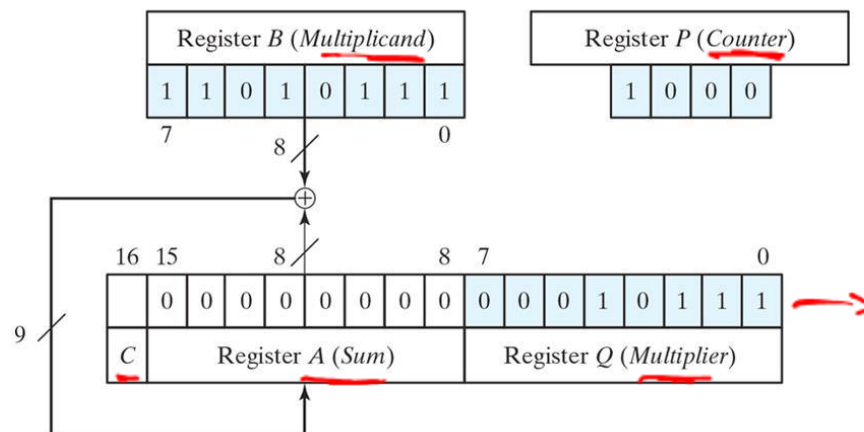In case this got confusing writing all the bits, all we're doing here is computing the partial products



Operation (completed)	C	A	Q	P
Initialize computation	0	00000000	00010111	1000
Add (Q[0]=1)	0	11010111	00010111	0111
Shift	0	01101011	10001011	0111
Add (Q[0]=1)	1	11010111	10001011	0110
Shift		10100001	01000101	0110

Binary Multiplier Specification

❖ Datapath

- $(2n+1)$ -bit *shift register* with bits split into 1-bit C , n -bit A , and n -bit Q
- Multiplicand stored in register B , multiplier stored in Q
- An n -bit *parallel adder* adds the contents of B to A and outputs to $\{C, A\}$
- A $\lceil \log_2(n + 1) \rceil$ -bit *counter* P


❖ Control

- Inputs $Start$ and $Reset$, outputs $Ready$ and $Done$
- Status signals: $Q[0]$ P_zero
- Control signals: $shift_regs$, $load_regs$, add_regs , dec_P


Binary Multiplier (ASMD Chart)

If it helps you can start by drawing an FSM to outline the states you need before creating the ASM chart

States:

 

ASMD:

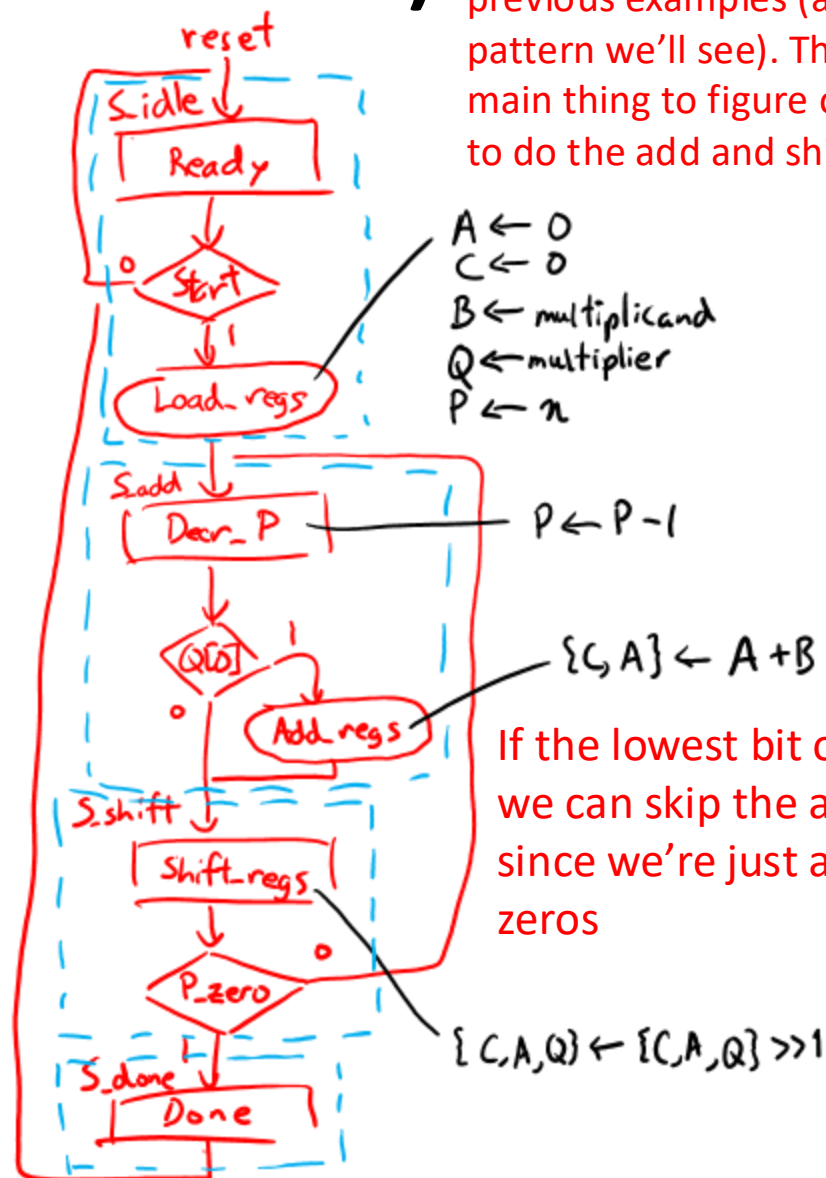

The start, init, and done logic are very similar to our previous examples (a common pattern we'll see). Then the main thing to figure out is how to do the add and shifting.

If the lowest bit of Q is a 0 we can skip the addition since we're just adding zeros

Binary Multiplier Implementation

❖ Controller Logic

$$\text{Load_regs} = S_idle \cdot \text{start}$$

Mealy type output that we assert in the idle stat if start is high

$$\text{Shift_regs} = S_shift$$

Moore type output we always assert in the shift state

$$\text{Add_regs} = S_add \cdot Q[0]$$

$$\text{Decr_P} = S_add$$

$$\text{Ready} = S_idle$$

$$\text{Done} = S_done$$

Binary Multiplier (SV, Datapath)

```
module datapath #(parameter WIDTH=8)
    (product, Q, P, multiplicand, multiplier, clk,
     Load_regs, Shift_regs, Add_regs, Decr_P);

    // port definitions
    output logic [2*WIDTH-1:0] product;
    output logic [WIDTH-1:0] Q, P; // note: unnecessary bits for P
    input  logic [WIDTH-1:0] multiplicand, multiplier;
    input  logic clk, Load_regs, Shift_regs, Add_regs, Decr_P;

    // internal logic
    logic C;
    logic [WIDTH-1:0] A, B;

    // datapath logic

endmodule
```

Binary Multiplier (SV, Datapath)

```
module datapath #(parameter WIDTH=8)
    (product, Q, P, multiplicand, multiplier, clk,
     Load_regs, Shift_regs, Add_regs, Decr_P);

    // port definitions
    ...

    // internal logic
    ...

    // datapath logic
    always_ff @(posedge clk) begin
        if (Load_regs) begin
            A <= 0; C <= 0; P <= WIDTH;
            B <= multiplicand;
            Q <= multiplier;
        end
        if (Decr_P)      P <= P - 1;
        if (Add_regs)    {C, A} <= A + B;
        if (Shift_regs) {C, A, Q} <= {C, A, Q} >> 1;
    end // always_ff

    assign product = {A, Q};
endmodule
```