

# Design of Digital Circuits and Systems

## ASM with Datapath III

**Instructor:** Vikram Iyer

**Teaching Assistants:**

Ariel Kao

Josh Wentzien

Selim Saridede

Jared Yoder


Derek Thorp


Adapted from material by Justin Hisa


# Relevant Course Information


- ❖ Homework 3 due tomorrow
- ❖ Homework 4 released today and due 5/5
  - ASMDs and algorithm implementation debugging
- ❖ Quiz 2 (ROM, RAM, Reg files) @ 11:50 am
- ❖ Lab 3 reports due next Friday (5/2)
  - Ideally finish by early next week so you can start Lab 4
- ❖ Lab 4 released today and due 5/9
  - Implementing bit counting and binary search algorithms

# ASMD Chart Review Questions

state box: 

decision box: 

conditional output: 

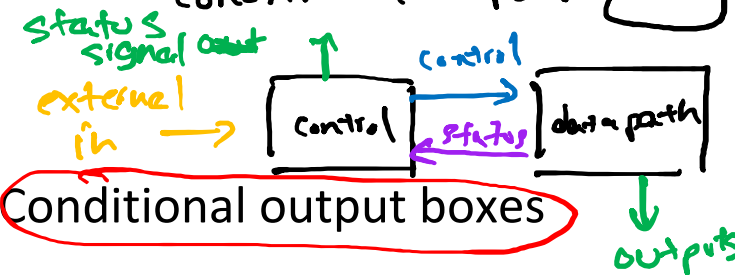

❖ Circle all that apply:

- Where can **control signals** be found?

State boxes      Decision boxes

- Where can **status signals** be found?

State boxes      Decision boxes

- Where can **external input signals** be found?

State boxes      Decision boxes

- What is the *first* thing a path should encounter in an **ASM block**?

State boxes      Decision boxes

- What can be found outside of **ASM blocks**? *none*

State boxes      Decision boxes

- What can **RTL operations** be attached to?

Control signals      Status signals

Conditional output boxes

Conditional output boxes

Conditional output boxes


Conditional output boxes

External output signals
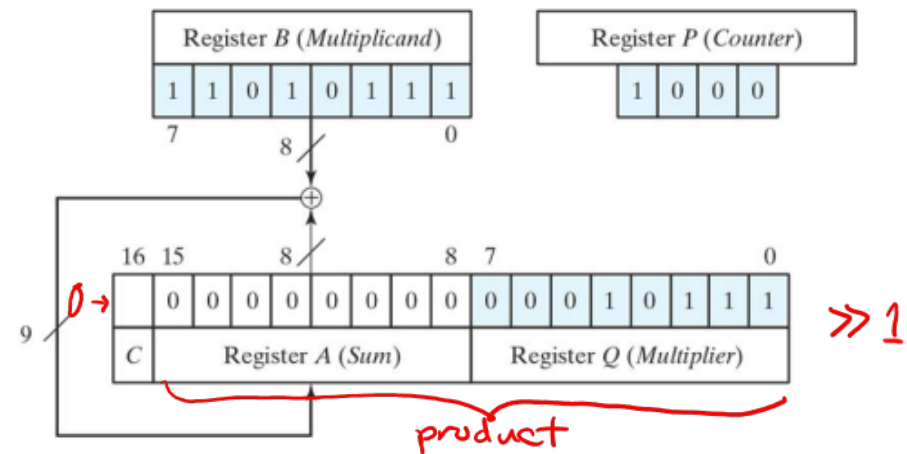
# Sequential Binary Multiplier Operation


❖ A few steps of:

$$\begin{array}{r} 11010111 \\ \times 00010111 \\ \hline \end{array}$$




| Operation (completed)  | C | A        | Q        | P    |
|------------------------|---|----------|----------|------|
| Initialize computation | 0 | 00000000 | 00010111 | 1000 |
| Add (Q[3] = 1)         | 0 | 11010111 | 00010111 | 0111 |
| Shift                  | 0 | 01101011 | 10001011 | 0111 |
| Add (Q[2] = 1)         | 1 | 01000010 | 10001011 | 0110 |
| Shift                  | 0 | 10100001 | 01000101 | 0110 |
| Add (Q[1] = 1)         | 1 | 01111000 | 01000101 | 0101 |
| Shift                  | 0 | 10111100 | 00100010 | 0101 |

# Binary Multiplier (ASMD Chart)

 

ASMD:

 

# ASMD Process Review

- 1) Identify datapath components, control signals, and status signals from description or pseudocode.
- 2) [*optional*] Create control-datapath circuit diagram.
- 3) [*optional*] Create state outline to plan out states and transitions between them.
- 4) Draw out ASM state boxes, decision boxes, and paths between them.
- 5) Augment state boxes with Moore-type outputs and add conditional output boxes with Mealy-type outputs.
- 6) Add ASM blocks to organize states.
- 7) Add RTL operations to control signals.
- 8) Double-check decision box edge cases and timing of operations (*i.e.*, debug).

# Short Tech Break

# Division Circuit

- ❖ Design a circuit that implements the long-division algorithm:

$$\begin{array}{r} 15 \\ 9 \overline{) 140} \\ \underline{9} \phantom{0} \\ 50 \\ \underline{45} \\ 5 \end{array}$$

(a) An example using decimal numbers

$$\begin{array}{r} \text{divisor} \rightarrow 1001 \quad \begin{array}{r} 00001111 \\ 1001 \overline{) 10001100} \\ \underline{1001} \phantom{00} \\ 10001 \phantom{00} \\ \underline{1001} \phantom{00} \\ 10000 \phantom{00} \\ \underline{1001} \phantom{00} \\ 1110 \\ \underline{1001} \\ 101 \end{array} \begin{array}{l} \leftarrow \text{quotient} \\ \leftarrow \text{dividend} \\ \leftarrow \text{remainder} \end{array} \end{array}$$

(b) Using binary numbers

- ❖ Considerations:


- Main operations? *shift, compare, subtract*
- Stop condition? *n iterations if divisor & dividend are n bits*



# Division Circuit

- ❖ Design a circuit that implements the long-division algorithm:
  - 1) Double the **dividend** width by appending 0's in front and align the **divisor** to the leftmost bit of the *extended dividend*.
  - 2) If the corresponding **dividend** bits are  $\geq$  the **divisor**, subtract the **divisor** from the **dividend** bits and make the corresponding **quotient** bit 1. Otherwise, keep the original **dividend** bits and make the **quotient** bit 0.
  - 3) Append one additional **dividend** bit to the previous result and shift the divisor to the right one position.
  - 4) Repeat steps 2 and 3 until all dividend bits are used.

# Division Circuit

 

## ❖ Implementation Notes:


- If current **dividend window** is smaller than the **divisor**, skip subtraction
- Instead of shifting **divisor** to the right, we will shift the **dividend** (and the **quotient**) *to the left*
- We will re-use the lower half of the **dividend** register to store the **quotient**

# Division Circuit Operation

❖ A few steps of:

$$\begin{array}{r} 0111 \\ (2) 0010 \overline{) 1111} \\ \underline{00} \end{array} \quad (15)$$

 $q\_bit = (R \geq B)$   
 $Q\_nxt = \{Q[n-2:0], q\_bit\}$   
 $R\_tmp = q\_bit ? R-B : R$   
 $R\_nxt = \{R\_tmp[n-2:0], Q[n-1]\}$



| Op (done)  | <u>B</u> | R               | Q               | q_bit | R_tmp      | R_nxt | Q_nxt | P   |
|------------|----------|-----------------|-----------------|-------|------------|-------|-------|-----|
| Initialize | 0010     | 0000<br>↓ R_nxt | 1111<br>↓ Q_nxt | 0     | 0000       | 0001  | 1110  | 100 |
| compute    | 0010     | 0001            | 110             | 0     | 0001 (R)   | 0011  | 1100  | 011 |
| compute    | 0010     | 0011            | 1100            | 1     | 0001 (R-B) | 0011  | 1001  | 010 |
| compute    | 0010     | 0011            | 1001            | 1     | 0001 (R-B) | 0011  | 0011  | 001 |
| compute    | 0010     | 0011            | 0011            | 1     | 0001 (R-B) | 0010  | 0111  | 000 |
| compute    | 0010     | 0001<br>↓ R_tmp | 0111            | 1     | X          | X     | X     | X   |

# Division Circuit Specification

## ❖ Datapath

- $2n$ -bit *register* with bits split into  $n$ -bit  $R$  and  $n$ -bit  $Q$
- Divisor stored in register  $B$ , dividend stored in  $Q$ ,  $R$  holds 0
- A “compare and subtract” module outputs  $\{R, 0\}$  if  $R < B$  and  $\{R - B, 1\}$  otherwise ( $\{R\_tmp, q\_bit\}$ )
- A *shifter* left shifts  $q\_bit$  into  $\{R\_tmp, Q\}$  and outputs to the inputs of  $R$  and  $Q$
- A  $\lceil \log_2(n + 1) \rceil$ -bit *counter*  $P$

## ❖ Control

- Inputs  $Start$  and  $Reset$ , outputs  $Ready$  and  $Done$
- Status signals:  $R\_zero$
- Control signals:  $Load\_regs, Decr\_P, Enable\_RQ, Finish\_RQ$

# Division Circuit (ASMD Chart)

# Division Circuit Implementation

## ❖ Controller Logic

*Load\_regs* =

*Enable\_RQ* =

*Finish\_RQ* =


*Decr\_P* =

*Ready* =


*Done* =

# Division Circuit (ASMD Chart)

States:

 

ASMD:

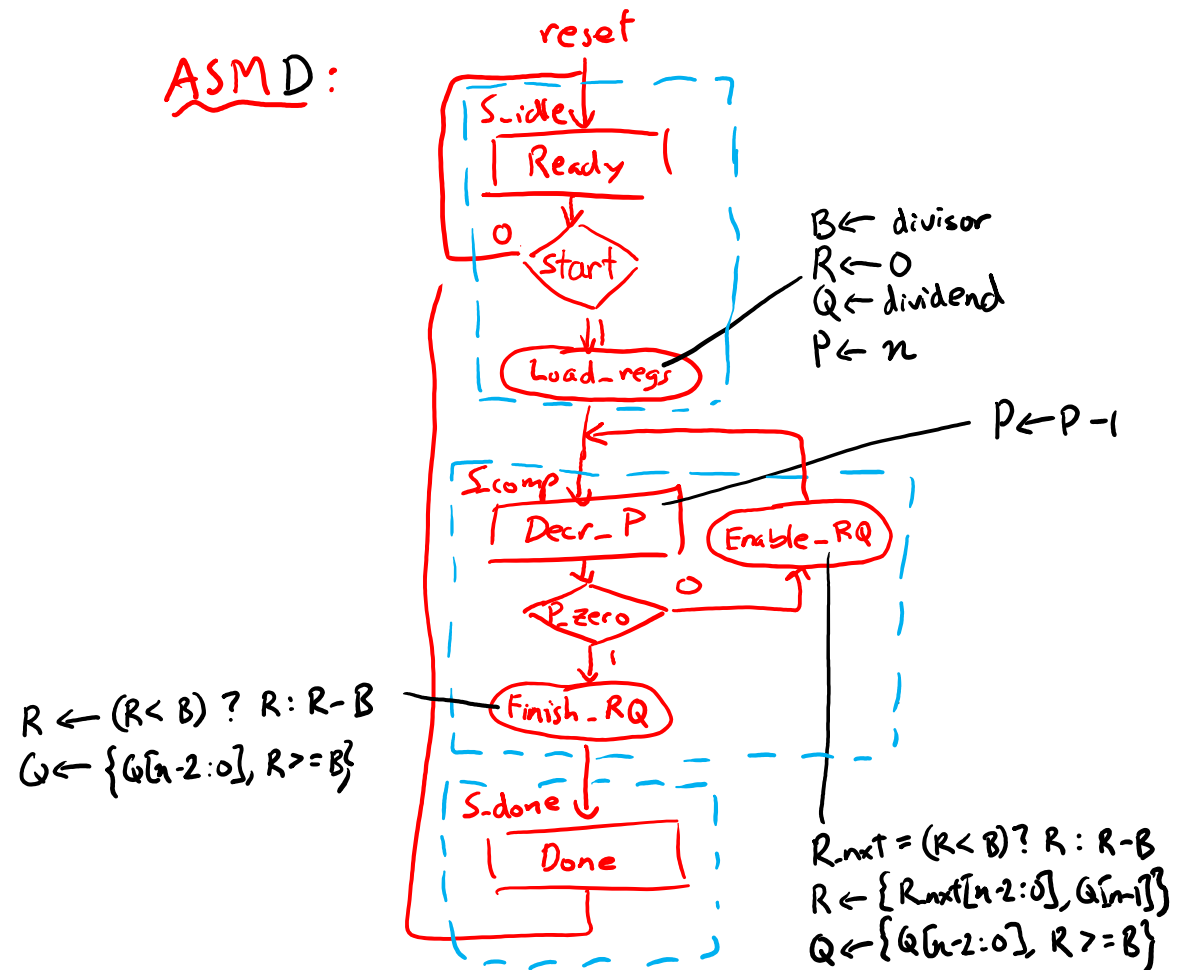

# Division Circuit Implementation

## ❖ Controller Logic

$$Load\_regs = S\_idle \cdot Start$$

$$Enable\_RQ = S\_comp \cdot \overline{P\_zero}$$

$$Finish\_RQ = S\_comp \cdot P\_zero$$

$$Decr\_P = S\_comp$$

$$Ready = S\_idle$$

$$Done = S\_done$$



# Division Circuit (SV, Datapath)

```
module datapath #(parameter WIDTH=4)
    (Q, P, divisor, dividend, clk,
     Load_regs, Enable_RQ, Enable_R, Decr_P);

    // port definitions
    output logic [2*WIDTH-1:0] product;
    output logic [WIDTH-1:0] Q, P; // note: unnecessary bits for P
    input logic [WIDTH-1:0] multiplicand, multiplier;
    input logic clk, Load_regs, Shift_regs, Add_regs, Decr_P;

    // internal logic
    logic [WIDTH-1:0] B, R, R_tmp, R_nxt;
    logic q_bit;

endmodule
```

# Division Circuit (SV, Datapath)

```
module datapath #(parameter WIDTH=4)
    (Q, P, divisor, dividend, clk,
     Load_regs, Enable_RQ, Enable_R, Decr_P);

    // port definitions & internal logic
    ...

    // assignments
    assign q_bit = (R >= B);
    assign R_tmp = (R < B) ? R : R-B;
    assign R_nxt = {R_tmp[WIDTH-2:0], Q[WIDTH-1]};
    assign Q_nxt = {Q[WIDTH-2:0], q_bit};

    // datapath logic
    always_ff @(posedge clk) begin
        if (Load_regs) begin
            R <= 0;      Q <= dividend;
            P <= WIDTH;  B <= divisor;
        end
        if (Decr_P)      P <= P - 1;
        if (Comp_regs)   {R, Q} <= {R_nxt, Q_nxt};
        if (Done_regs)   {R, Q} <= {R_tmp, Q_nxt};
    end // always_ff

endmodule
```

## Lab 4 Preview: Bit Counter

- ❖ Design a circuit that counts the number of bits in a register *A* that have the value 1
- ❖ Algorithm:

```
B = 0; // counter
while A != 0 do
    if A[0] = 1 then
        B = B + 1
    endif
    A = A >> 1
endwhile
```