

Design of Digital Circuits and Systems

Algorithms to Hardware I

Instructor: Vikram Iyer

Teaching Assistants:

Ariel Kao

Josh Wentzien

Selim Saridede

Jared Yoder

Derek Thorp

Adapted from material by Justin Hisa

Relevant Course Information

- ❖ Lab 3 reports due Friday (5/2)
- ❖ Lab 4 due next Friday (5/9)
- ❖ hw4 due on Wednesday (5/7)
- ❖ Anonymous mid-quarter survey on Canvas (due 5/5)
- ❖ Quiz 3 (ASM, ASMD) next Thursday (5/8)

Arithmetic Mean

- ❖ Design a sequential circuit that computes the mean M of k n -bit numbers stored in registers
 - *e.g.*, accessing a RAM or register file with k addresses
 - To save on hardware, you can only use one n -bit adder and have a single read port RAM
- ❖ Algorithm Pseudocode:

Aside: Counter Variable

- ❖ Many sequential hardware algorithms utilize counters
- ❖ If both work, is there a preference?
 - How to implement $C = k - 1$ check?

 - How to implement $C = 0$ check?

Arithmetic Mean Specification

❖ Datapath

- A k -address *register file* (only using `r_addr` and `r_data`)
- Reg file address stored in $\lceil \log_2(k) \rceil$ *down-counter* A
- Sum stored in register S
- An n -bit *divider* circuit, as discussed last lecture

❖ Control

- Inputs *Start* and *Reset*, outputs *Ready* and *Done*
- Status signals:
- Control signals:



Arithmetic Mean (ASMD Chart, Initial)

- ❖ For now, ignore the details of the divider circuit


```
S = 0
for A = k-1 to 0
    S = S + Reg[A]
endfor
M = S/k
```

Arithmetic Mean (ASMD Chart)

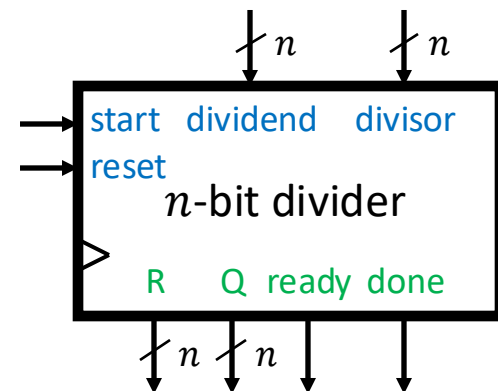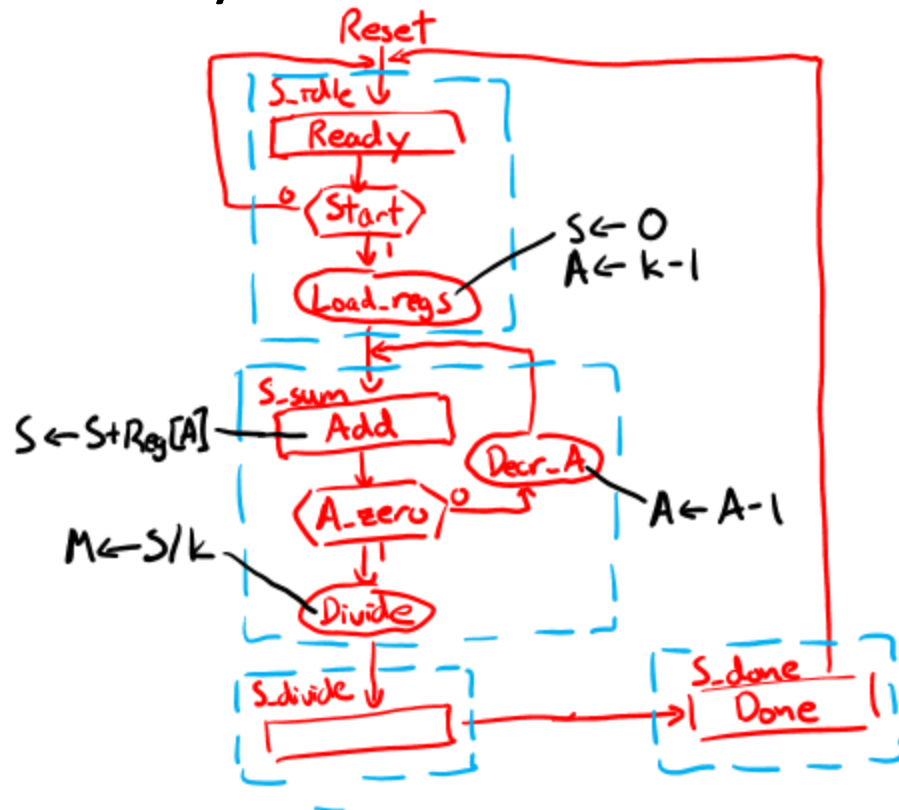- ❖ Fix your ASMD chart based on the divider circuit:





Arithmetic Mean Datapath

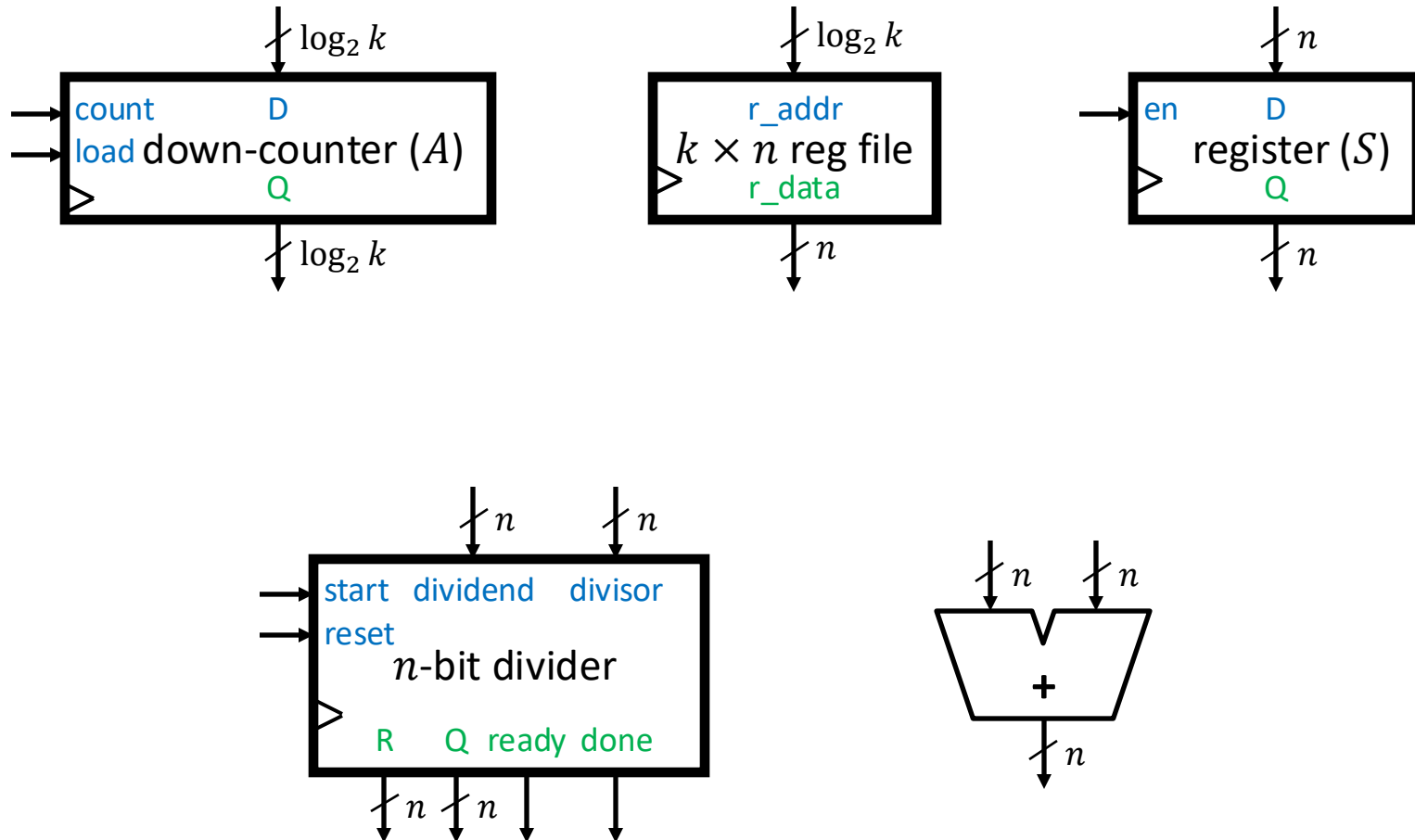

Technology Break

Aside: Load Loops

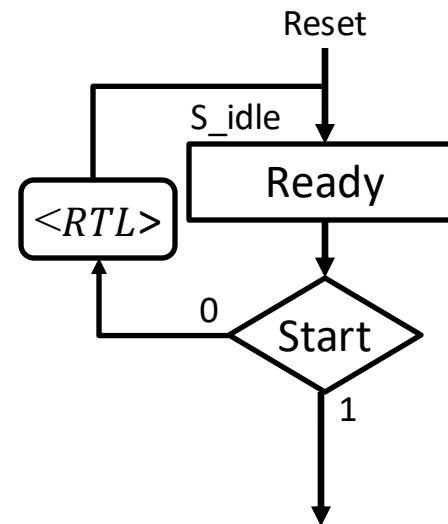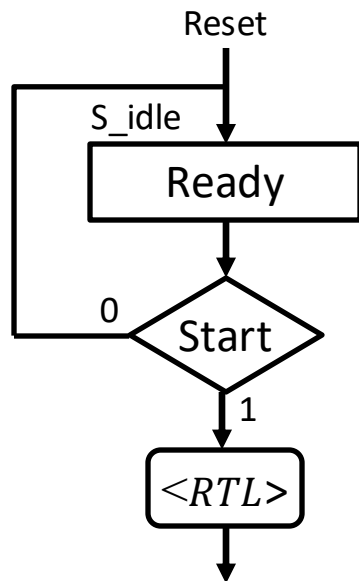
- ❖ For *some* initialization operations, you can get equivalent behavior from either the (1) outgoing edge or the (2) looping edge:



Aside: Start Loops

- ❖ What happens if we forget to de-assert *Start*?

- ❖ Fix:

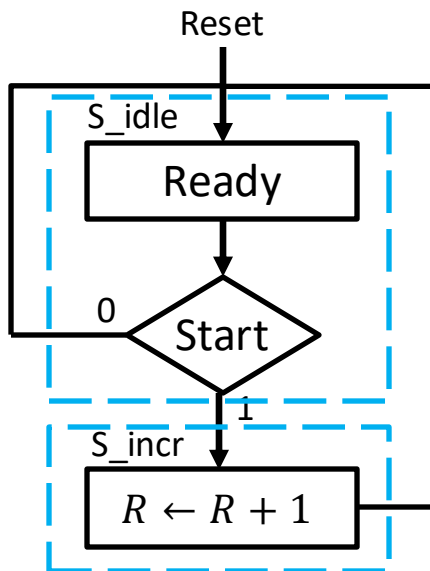

Sorting Algorithm

- ❖ Design a circuit to sort k n -bit numbers stored in a set of registers in ascending order

Algorithm:

```

for i = 0 to k-2 do
  A = Reg[i]
  for j = i+1 to k-1 do
    B = Reg[j]
    if B < A then
      Reg[i] = B
      Reg[j] = A
      A = Reg[i]
    endif
  endfor
endfor

```

Example ($k = 4$): i to 2, j to 3

i	j	A	B	R[0]	R[1]	R[2]	R[3]
0	1	3	7 _x	3	7	1	0
0	2	3	1 _✓	3	7	1	0
0	3	1	0 _✓	1	7	3	0
1	2 _(in)	7	3 _✓	0	7	3	1
1	3	3	1 _✓	0	3	7	1
2	3 _(in)	7	3 _✓	0	1	7	3
				0	1	3	7

Sorting Algorithm Specification

❖ Datapath

- A k -address *register file* (assume only 1 port)
- Two $\lceil \log_2(k) \rceil$ *up-counters* i and j
- Two registers A and B
- An n -bit *comparator* circuit to check for $B < A$

❖ Control

- Inputs *Start* and *Reset*, outputs *Ready* and *Done*
- Status signals:
- Control signals:

Sorting Algorithm Specification

❖ Datapath



- A k -address *register file* (assume only 1 port)
- Two $\lceil \log_2(k) \rceil$ *up-counters* i and j
- Two registers A and B
- An n -bit *comparator* circuit to check for $B < A$

❖ Timing Notes:

- RTL operations in a state occur on the *next* clock trigger
- Can $i \leftarrow x$ and $A \leftarrow \text{Reg}[i]$ be done simultaneously?
- Can $\text{Reg}[i] \leftarrow B$ and $\text{Reg}[j] \leftarrow A$ be done simultaneously?
- Swap operations *must* be done sequentially

Sorting Algorithm (ASMD Chart)

Sorting Algorithm (ASMD Chart)

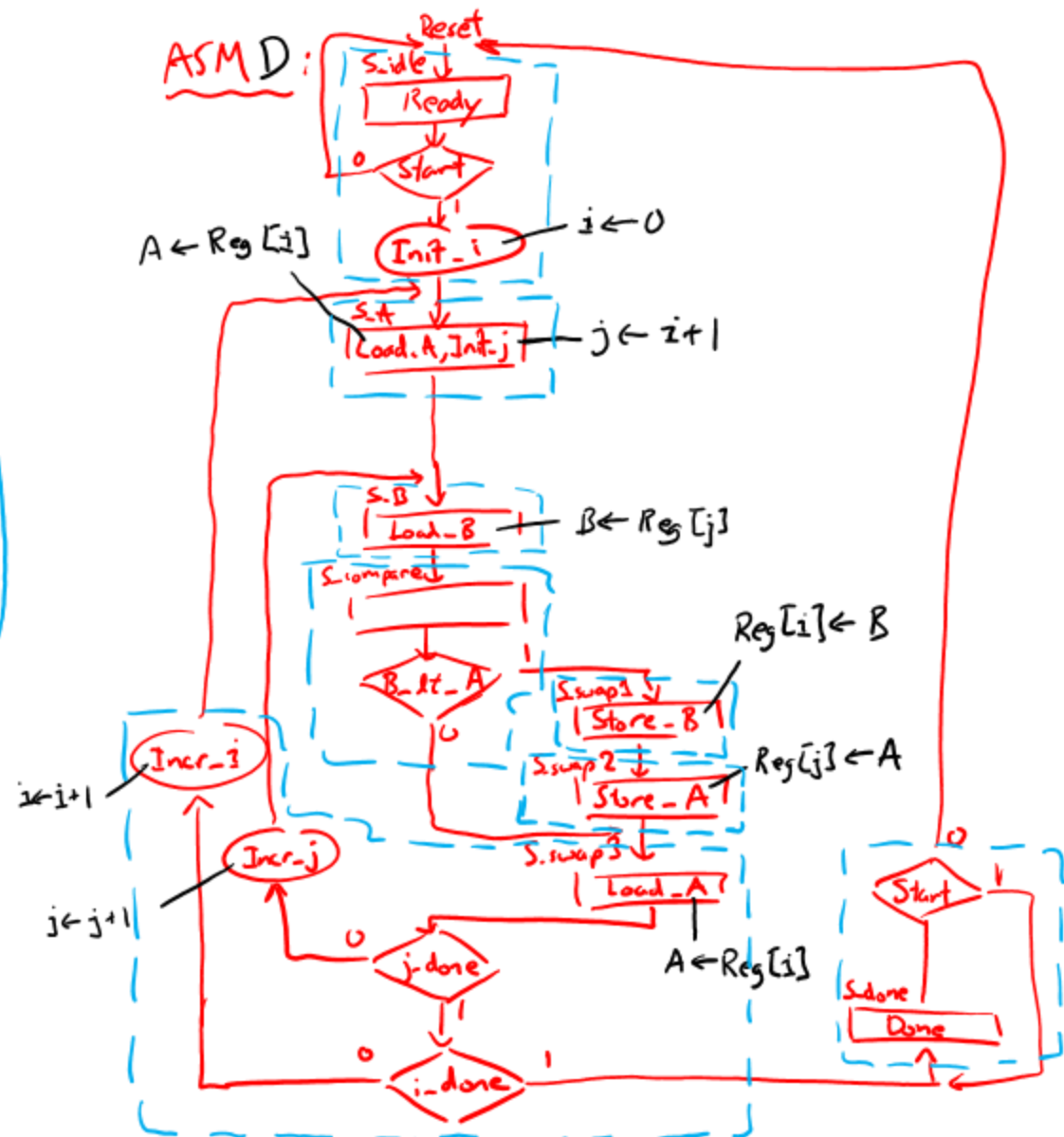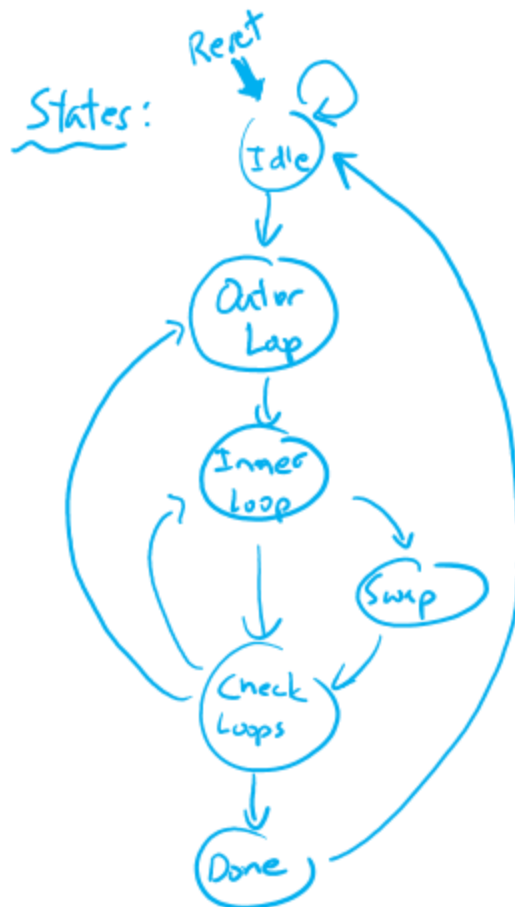


Sorting Algorithm Datapath

Control Signals:


Init- i , Incr- i
Init- j , Incr- j
Load- A , Store- A
Load- B , Store- B

Status Signals:


$B_{lt} A$
 i_done
 j_done

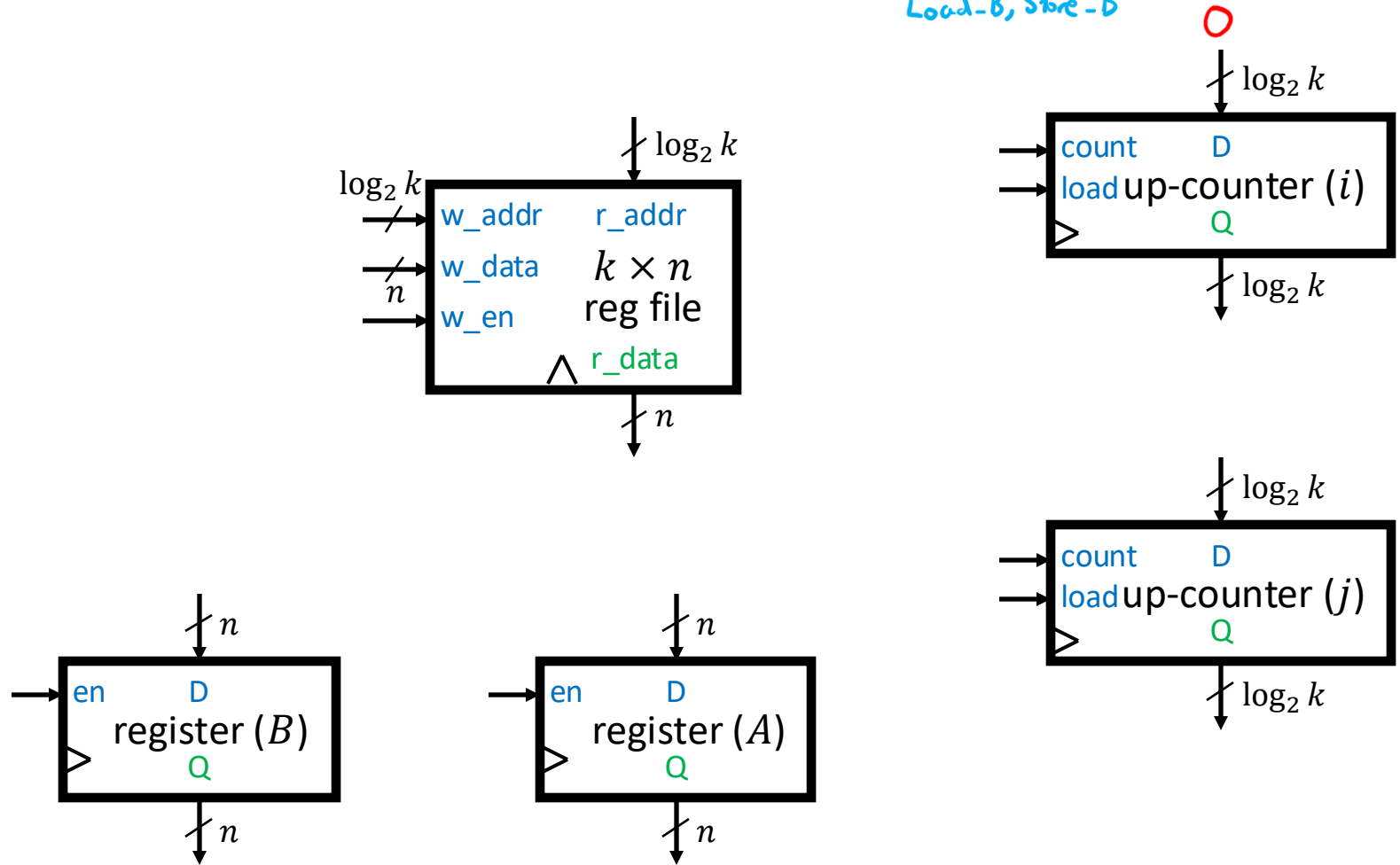


Sorting Algorithm Datapath

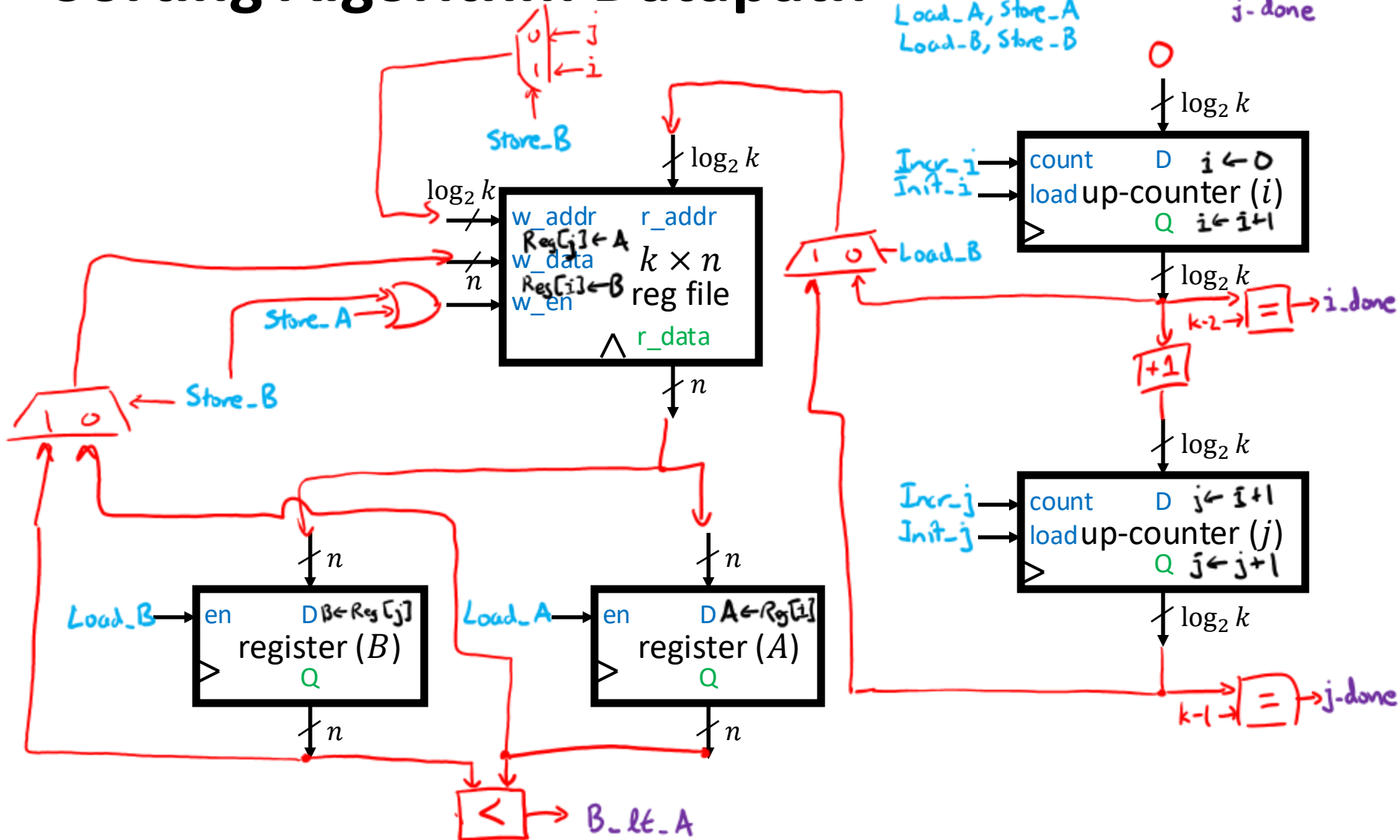

Alternate Sort Algorithm Datapath (1/2)

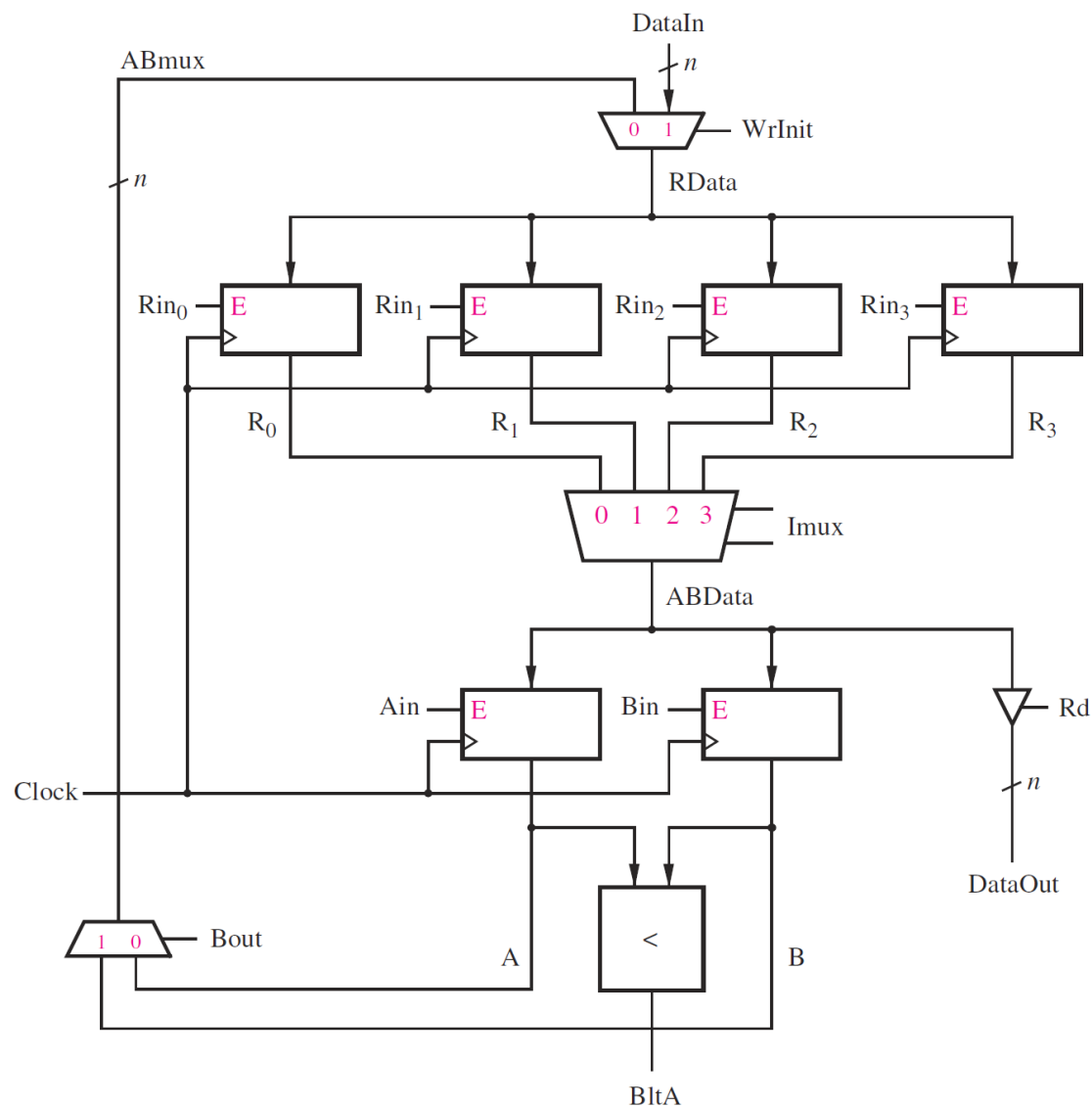

Alternate Sort Algorithm Datapath (2/2)

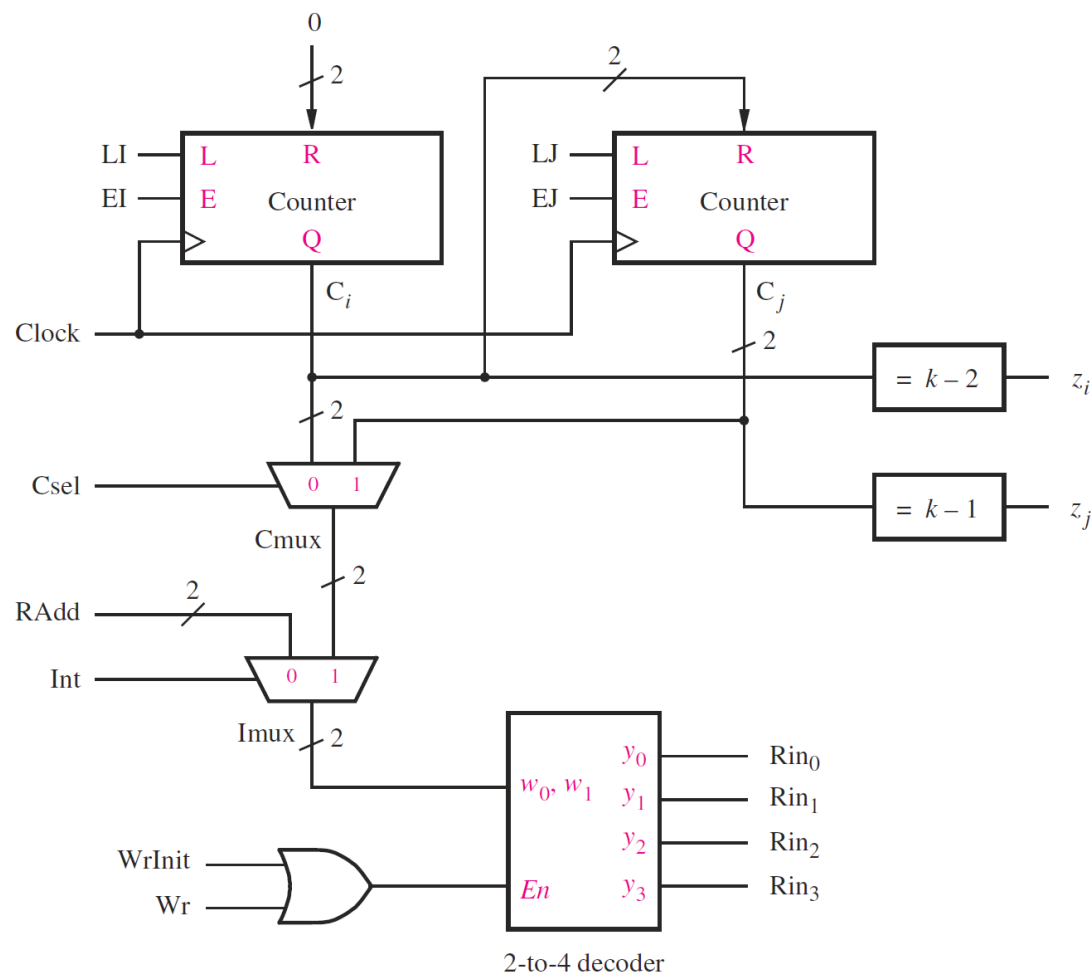

Lab 4 Preview: Binary Search

- ❖ Design a circuit that searches a *sorted* array for a given value by checking the middle element of the remaining portion of the array we would expect to find the given number:

```
L = 0
R = n - 1
while L <= R do
    m = floor((L + R)/2)
    if A[m] < T then
        L = m + 1
    else if A[m] > T then
        R = m - 1
    else
        return m
    endif
endwhile
return unsuccessful
```