

# Design of Digital Circuits and Systems

## Clock Domain Crossing

**Instructor:** Vikram Iyer

**Teaching Assistants:**

Ariel Kao

Josh Wentzien

Selim Saridede

Jared Yoder

Derek Thorp

Adapted from material by Justin Hisa


# Relevant Course Information

- ❖ Homework 5 due Friday (5/16)
  - Problem 4 looks long but it's more a walkthrough
  
- ❖ Lab 5 due next week (5/23)
  - Hardest/longest lab
    - Spend time planning and thinking through your design
  - You will need to use the VGA interface on LabsLand
 
# Review: Timing Slack

- ❖ *Slack* is how much wiggle room we have before we run into a potential timing violation (setup or hold)

- Can think of as worst-case analysis
- Setup slack =  $DRT_{su} - DAT_{su} = \text{clock path}_{\min} - \text{data path}_{\max}$
- Hold slack =  $DAT_h - DRT_h = \text{data path}_{\min} - \text{clock path}_{\max}$



- We looked specifically at the slack between a single source and destination register, but in reality, we'd want to know the minimum slack between *any two registers* in our system

# Review: Timing Slack


for destination register

$$\text{setup slack} = \text{clock path}_{\min} - \text{data path}_{\max}$$

$$\text{hold slack} = \text{data path}_{\min} - \text{clock path}_{\max}$$

need to analyze paths from:  $A \rightarrow A$ ,  $A \rightarrow B$ ,  $B \rightarrow A$ ,  $B \rightarrow B$

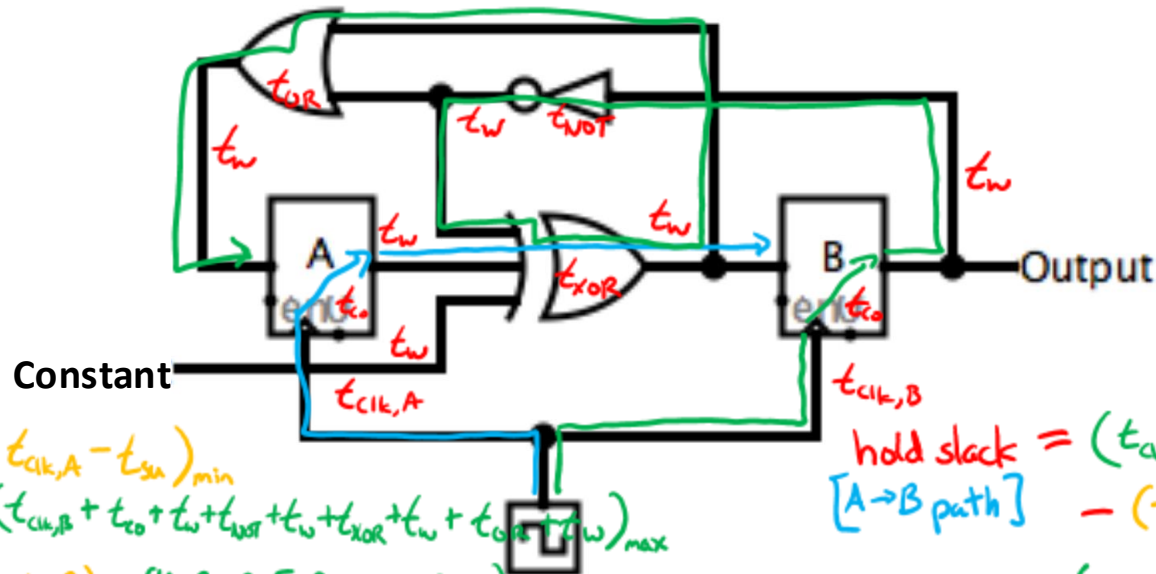- ❖ Solve for the min setup and hold slacks if  $T = 40$  ns
  - Registers:  $t_h = 1$  ns,  $t_{su} = 3$  ns,  $t_{co} \in [6, 9]$  ns
  - Delays:  $t_{\text{wire}} \in [1, 2]$  ns,  $t_{\text{clk}, A} \in [1, 2]$  ns,  $t_{\text{clk}, B} \in [2, 4]$  ns  
 $t_{\text{NOT}} \in [3, 5]$  ns,  $t_{\text{OR}} \in [6, 8]$  ns,  $t_{\text{XOR}} \in [9, 12]$  ns



$$\begin{aligned} \text{setup slack} &= (T + t_{\text{clk}, A} - t_{su})_{\min} \\ &\quad - (t_{\text{clk}, B} + t_{co} + t_w + t_{\text{NOT}} + t_w + t_{\text{XOR}} + t_w + t_{co} + t_w)_{\max} \\ &= (40 + 1 - 3) - (4 + 9 + 2 + 5 + 2 + 12 + 2 + 8 + 2) \\ &= 38 \text{ ns} - 46 \text{ ns} = \boxed{-8 \text{ ns (setup violation!)}} \end{aligned}$$


$$\begin{aligned} \text{hold slack} &= (t_{\text{clk}, A} + t_{co} + t_w + t_{\text{XOR}} + t_w)_{\min} \\ &\quad - (t_{\text{clk}, B} + t_h)_{\max} \\ &= (1 + 6 + 1 + 9 + 1) - (4 + 1) \\ &= 18 \text{ ns} - 5 \text{ ns} = \boxed{13 \text{ ns}} \end{aligned}$$

# Clock Domains

- ❖ A **clock domain** is all of the sequential logic that runs on the same clock/clock frequency
  - May have multiple clock domains in one device or different clock domains when communicating across devices
  - These can arise purposefully (*e.g.*, using multiple clocks) or inadvertently (*e.g.*, really bad clock skew and jitter)
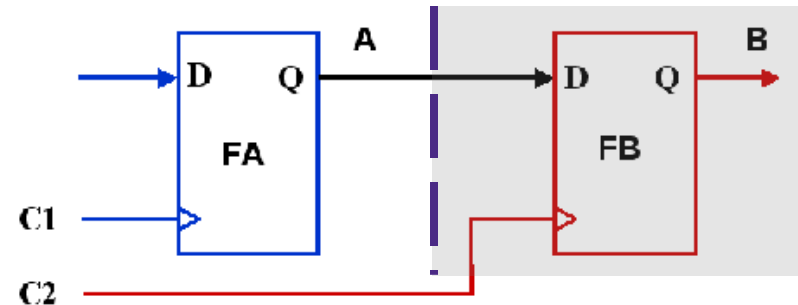
# Clock Domain Crossing (CDC)


- ❖ Sending data from one clock domain to another is called a **clock domain crossing**
  - Can cause timing issues: metastability, data loss, and data incoherence
  - The **sending clock domain** and **receiving clock domain** are separated by a **CDC boundary**



- ❖ The phase and frequency relationships between clock domains may be *known* (**synchronous CDC**) or *unknown* (**asynchronous CDC**)
 
# Synchronization


- ❖ **Synchronization:** coordination of events for proper transfer of data
  - *e.g.*, the two-flip-flop circuit recommended in 271



- We will discuss a number of other synchronizers today
 
# Metastability

- ❖ **Metastability** is the ability of a digital system to persist for an unbounded time in an unstable equilibrium or metastable state
  - Caused by timing constraint violations
  - [https://en.wikipedia.org/wiki/Metastability\\_in\\_electronics](https://en.wikipedia.org/wiki/Metastability_in_electronics)






# Metastability
 
## ❖ Why is metastability bad?

- Circuit may be unable to settle into a stable '0' or '1' logic level within the time required for proper circuit operation
  - Unstable signals can also cause current spikes
- Unpredictable behavior or random value
  - Metastable signal is passed to combinational logic



CL reacts immediately to changes in signal

- Metastable signal passed to multiple destinations



value might be read differently at different destinations

- Downstream timing issues




could violate timing constraints downstream


# Metastability and CDC

- ❖ Metastability is inevitable in a multi-clock design, but want to prevent it as much as possible
  - Caused by different frequencies, clock skew, clock jitter
- ❖ Signals in the **sending clock domain** should be *synchronized* before being passed to a CDC boundary

■ Bad:

 


■ Good:

 
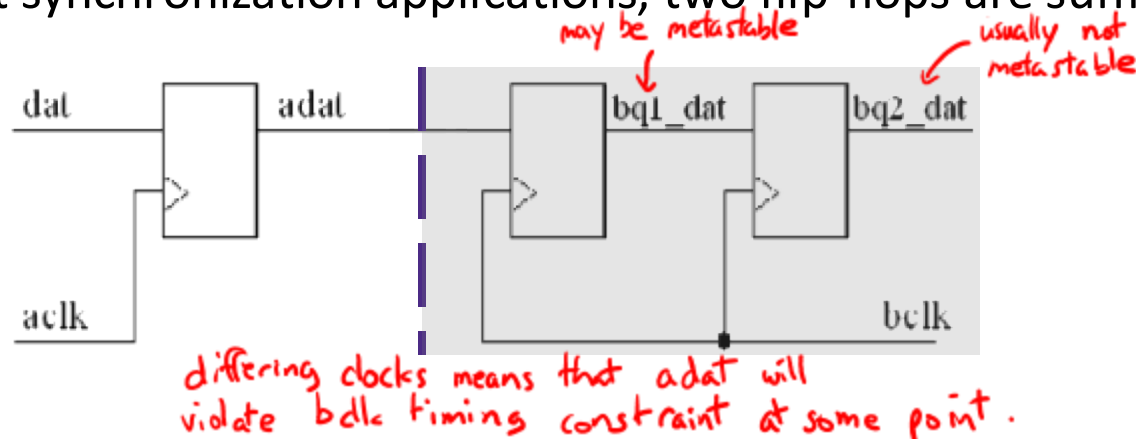
# Metastability and CDC


- ❖ Metastability is inevitable in a multi-clock design, but want to prevent it as much as possible
  - Caused by different frequencies, clock skew, clock jitter
- ❖ Signals in the **receiving clock domain** should be passed through a *synchronizer* before rest of system
  - Add flip-flops to give metastable signals time to settle so rest of system receives clean/valid signals
    - For most synchronization applications, two flip-flops are sufficient



# Technology Break
 
# Data Loss


- ❖ **Data loss** refers to information lost due to failures
- ❖ Data loss during CDC:
  - Typically means *incorrect reads* or *missed input changes*



Handwritten red scribbles.
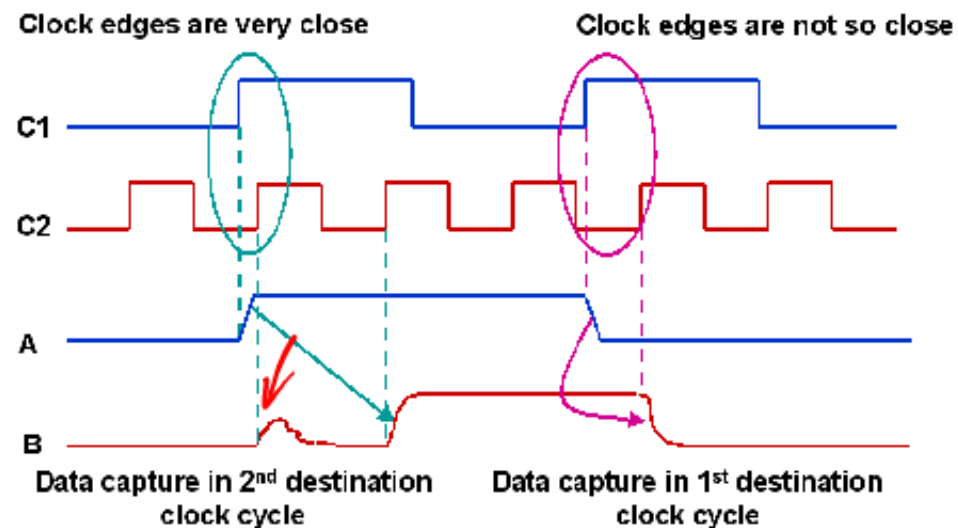
# Data Loss

- ❖ **Data loss** refers to information lost due to failures
- ❖ Data loss during CDC:
  - Typically means *incorrect reads* or *missed input changes*
  - Change in **sending domain** data may not be properly captured on first clock edge in **receiving domain** due to metastability:




# Dealing with Data Loss

- ❖ **Sending domain** data should be held constant long enough to be captured in the **receiving domain**
  - No longer a cycle-by-cycle correspondence between **sending** and **receiving** domain data
- ❖ Need to account for differences in clock speeds
  - Slower  $\rightarrow$  Faster (*synchronous*): holding input constant for one clock cycle is probably enough since  $T_{\text{sending}} > T_{\text{receiving}}$ 
    - Can do longer to be more sure


(no feedback)

 every change in *adat* needs to be held for a certain # of clock cycles


 
# Dealing with Data Loss


- ❖ **Sending domain** data should be held constant long enough to be captured in the **receiving domain**
  - No longer a cycle-by-cycle correspondence between **sending** and **receiving** domain data
- ❖ Need to account for differences in clock speeds
  - Faster → Slower (*synchronous*): “open loop” solution is to holding input constant for longer by “stretching” them




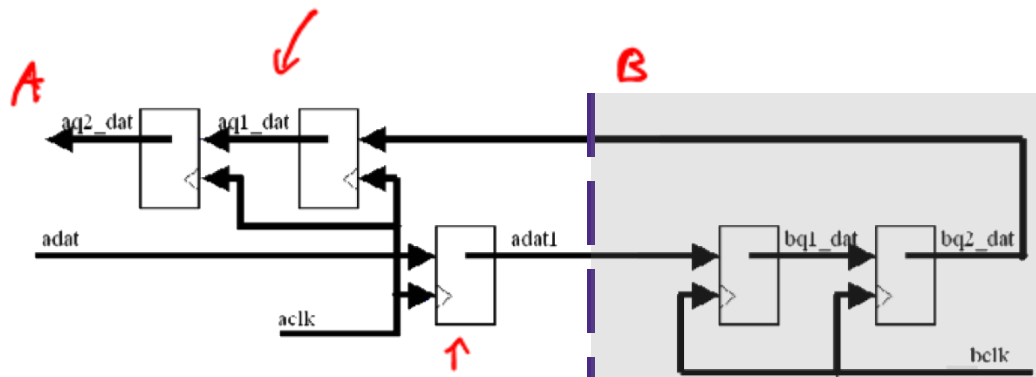
# Dealing with Data Loss

- ❖ **Sending domain** data should be held constant long enough to be captured in the **receiving domain**
  - No longer a cycle-by-cycle correspondence between **sending** and **receiving** domain data
- ❖ Need to account for differences in clock speeds
  - Faster → Slower (*synchronous*): “closed loop” solutions can check for proper receipt of signal before changing signal




# Dealing with Data Loss

- ❖ **Sending domain** data should be held constant long enough to be captured in the **receiving domain**
  - No longer a cycle-by-cycle correspondence between **sending** and **receiving** domain data
- ❖ Need to account for differences in clock speeds
  - For *asynchronous* CDC, will need to employ a more sophisticated synchronization technique
    - *e.g.*, handshake or FIFO buffer
 
# Data Incoherence

- ❖ **Data incoherence** is the invalid combination of values caused by differing outcomes when passing multiple signals (*e.g.*, a vector) through a CDC simultaneously
  - Depending on what the data represents, this invalid state may lead to functional errors



passing a bus through a register is really passing each bit through a FF:



each FF could experience metastability differently and at different times!

# Dealing with Data Incoherence

- ❖ Specifically trying to avoid *invalid states*
  - The issue of incorrect reads is metastability and data loss
- ❖ When possible, restrict data changes to 1 bit at a time
  - Even on failed transition, will remain in a valid state
  - e.g., a Gray code counter

Decimal	0	1	2	3	4	5	6	7
Binary	000	001	010	011	100	101	110	111
Gray	00 <u>0</u>	→ 00 <u>1</u>	→ 01 <u>1</u>	→ 01 <u>0</u>	→ 11 <u>0</u>	→ 11 <u>1</u>	→ 10 <u>1</u>	→ 10 <u>0</u>

only 1 bit changes  
at a time


- ❖ Ensure that system can recover from invalid states
  - May result in less optimized logic (fewer don't cares)
  - e.g., force transitions from invalid to valid states in FSM  
(make sure not a sink state)

# Synchronization of CDC Data Signals

- ❖ The previously mentioned techniques of adding synchronizing flip-flops and using Gray codes are not generally sufficient for data buses through a CDC
- ❖ Three common methods for synchronizing data between clock domains are:
  - MUX-based synchronizers
  - Handshake signals
  - FIFO buffers

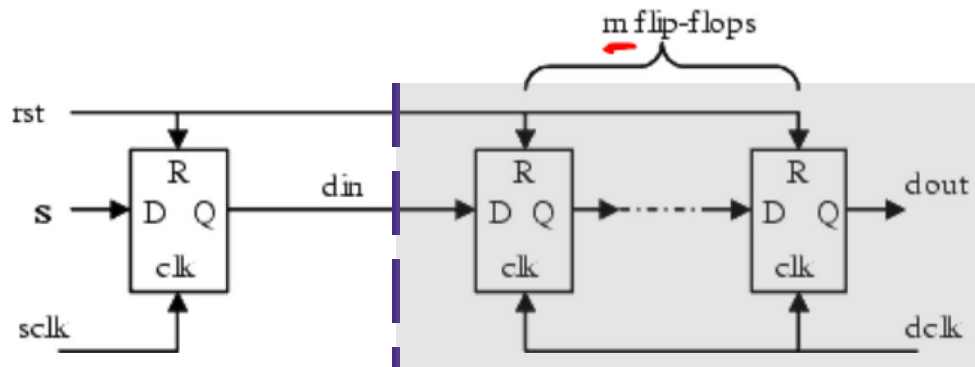
# Flip-Flop Synchronizer

- ❖ Add  $m$  flip-flops in the receiving domain
  - Generally want to hold input data stable for  $m+1$  receiving domain clock edges to ensure settling of data



 
# Recirculation MUX Synchronizer

- ❖ Control signals typically can sufficiently be handled by flip-flop synchronizers, so can use these to choose when to sample the data in the receiving domain


 
# Handshake Synchronizer

- ❖ A *request-and-acknowledge* scheme to guarantee the sampling of correct data
  - The relationship of the two clocks doesn't matter!
  - Best if data doesn't change very frequently because handshake takes so long





# Handshake Implementation

## ❖ Sender:

- Input data should be held stable ( $\overline{sLoad}$ ) until acknowledgement received
- Request ( $sreq$ ) signal should be stable for  $m+1$  cycles in the receiving clock domain to ensure transmission
- A new request should not be asserted until the acknowledgement from the previous data value has been de-asserted


# Handshake Implementation

## ❖ Receiver

- Input data should not be sampled (`dCtrl`) until request received
- Acknowledgement (dack) signal should be stable for  $m+1$  cycles in the sending clock domain to ensure transmission
- A new acknowledgement should not be asserted until the next request is received
 
# FIFO Synchronizer

- ❖ A dual-clock asynchronous FIFO can be used when the high latency of a handshake synchronizer cannot be tolerated



# FIFO Synchronizer

- ❖ The golden rules of FIFO buffers still apply:
  - The sender should never write when the FIFO is full
  - The receiver should never reads when the FIFO is empty
- ❖ Implementation details:
  - Have to deal with FF synchronizer delays, but not *every* time
  - Pointer (read and write) must be gray-coded at their source
    - Comparison of gray-coded positions is more complex
  - Determining full/empty signals on time is tricky
  - May need to slow data generation rate (or introduce breaks/pauses) if not being read fast enough

# Review Questions

- There are reasonable arguments for both → incorrect read counts as "lost" data  
 → 1-bit state can be incorrect/incoherent
- ❖ A 1-bit signal becomes metastable in the receiving domain and is read incorrectly. This is an example of:

Data loss

missed sending domain transitions

Data incoherence

Both

Neither

requires multiple bits

- ❖ What is the trade-off between using an open-loop and closed-loop CDC solution?

speed vs. certainty/feedback

open loop is quicker, but you are trusting that the signal is read properly

closed loop gives you the certainty of receipt via feedback but takes longer

- ❖ Which synchronizer is slowest (and why)?

Flip-flop

Recirculation MUX

Handshake

FIFO

uses both FF synch & recirculation MUX with feedback