

# DESIGN OF DIGITAL CIRCUITS AND SYSTEMS

## Memory I

**Instructor:** Justin Hsia

**Teaching Assistants:**

Colton Carroll

Hemil Patel

Rasya Fawwaz

Grace Zhou

Quinlyn Donohue

Rose Maresh

# Relevant Course Information



- ❖ HW1 can still be submitted tonight (1 late day)
  - Solution outline will be posted tomorrow (UW login)
- ❖ HW2 released today, due next Wednesday (4/15)
- ❖ Lab 1 reports due Friday (4/10), demos 4/12-17
- ❖ Lab 2 released today, due next Friday (4/17)
- ❖ Quiz 1 is Thursday, 4/9 in last 25 min of lecture
  - FSM design – state diagram, explain design decisions
  - Some past Quiz 1's available for practice on course website

# Review Question

- ❖ Design an FSM with 1-bit input and 1-bit output that will output two consecutive 1's any time it sees the string "010" and outputs 0 otherwise
  - Example inputs: 0 0 1 0 0 1 1 0 1 0 1 0 1 1 ...  
                  outputs: 0 0 0 1 1 0 0 0 0 1 1 1 1 0 ...
  - How many state bits do we need?
  - Which state should be your initial/reset state?
- ❖ If you have time, design both a **Moore** machine and **Mealy** machine "from scratch" (*i.e.*, don't convert between the two)
  - Which seems easier to implement? Can you name specific ways that the SystemVerilog implementation will be "easier"?
  
# Review Solution

- ❖ Design an FSM with 1-bit input and 1-bit output that will output two consecutive 1's any time it sees the string "010" and outputs 0 otherwise



# Aside: Powers of 2 and Prefixes

- ❖ Here focusing on large numbers (*i.e.*, exponents  $> 0$ )
- ❖ SI prefixes are *ambiguous* if base 10 or 2
  - Note that  $10^3 \approx 2^{10}$
- ❖ IEC prefixes are *unambiguously* base 2

**SIZE PREFIXES ( $10^x$  for Disk, Communication;  $2^x$  for Memory)**

SI Size	Prefix	Symbol	IEC Size	Prefix	Symbol
$10^3$	Kilo-	K	$2^{10}$	Kibi-	Ki
$10^6$	Mega-	M	$2^{20}$	Mebi-	Mi
$10^9$	Giga-	G	$2^{30}$	Gibi-	Gi
$10^{12}$	Tera-	T	$2^{40}$	Tebi-	Ti
$10^{15}$	Peta-	P	$2^{50}$	Pebi-	Pi
$10^{18}$	Exa-	E	$2^{60}$	Exbi-	Ei
$10^{21}$	Zetta-	Z	$2^{70}$	Zebi-	Zi
$10^{24}$	Yotta-	Y	$2^{80}$	Yobi-	Yi

$2^0 = 1$
$2^1 = 2$
$2^2 = 4$
$2^3 = 8$
$2^4 = 16$
$2^5 = 32$
$2^6 = 64$
$2^7 = 128$
$2^8 = 256$
$2^9 = 512$
$2^{10} = 1024$

# Large Powers of 2 and Units

- ❖ Because IEC prefixes are powers of  $2^{10}$ , we can convert any large power of 2 as follows:
  - Note that we are only changing the *quantity* and the *units* remain the same

$$2^{XY} \text{ "things"} = \left[ \begin{array}{l} Y=0 \rightarrow 1 \\ Y=1 \rightarrow 2 \\ Y=2 \rightarrow 4 \\ Y=3 \rightarrow 8 \\ Y=4 \rightarrow 16 \\ Y=5 \rightarrow 32 \\ Y=6 \rightarrow 64 \\ Y=7 \rightarrow 128 \\ Y=8 \rightarrow 256 \\ Y=9 \rightarrow 512 \end{array} \right] + \left[ \begin{array}{l} X=0 \rightarrow \\ X=1 \rightarrow \text{Kibi-} \\ X=2 \rightarrow \text{Mebi-} \\ X=3 \rightarrow \text{Gibi-} \\ X=4 \rightarrow \text{Tebi-} \\ X=5 \rightarrow \text{Pebi-} \\ X=6 \rightarrow \text{Exbi-} \\ X=7 \rightarrow \text{Zebi-} \\ X=8 \rightarrow \text{Yobi-} \end{array} \right] + \text{"things"}$$

## ❖ Examples:

- 2 GiB of memory?  $2 \text{ GiB} = 2^1 \times 2^{30} \text{ bytes} = 2^{31} \text{ bytes}$
- $2^{47}$  things into IEC:  $2^{47} \text{ things} = 2^7 \times 2^{40} = 128 \text{ Ti-things}$

# Memory

- ❖ Several forms of memory are available, which include:
  - ~~Secondary memory (e.g., hard disk, flash drive)~~ *not covered in 371*
  - Read-only memory (ROM)
  - Random-access memory (RAM)
  - Register files
    - Small, fast, fixed-sized memory that hold CPU data state
  - First in, first out (FIFO) buffers

# Embedded FPGA Memory

- ❖ An FPGA contains prefabricated memory modules
  - Intended for small or intermediate-sized storage
  - Contents of memory blocks can be configured via memory initialization files (*.mif*)
- ❖ The DE1-SoC's Cyclone V FPGA (Cyclone V SE A5) has:
  - 31k Adaptive Logic Modules (ALMs)
  - 4.45 Mbits of memory organized as 397 memory blocks, each with 10 kbits of storage (M10K)
    - Flexible, configurable memory storage available to the designer
    - Each M10K can act as single-port memory, dual-port RAM, shift register, ROM, or a FIFO buffer
  - More info on website: DE1-SoC → Cyclone V Handbook

# DE1-SoC Memory


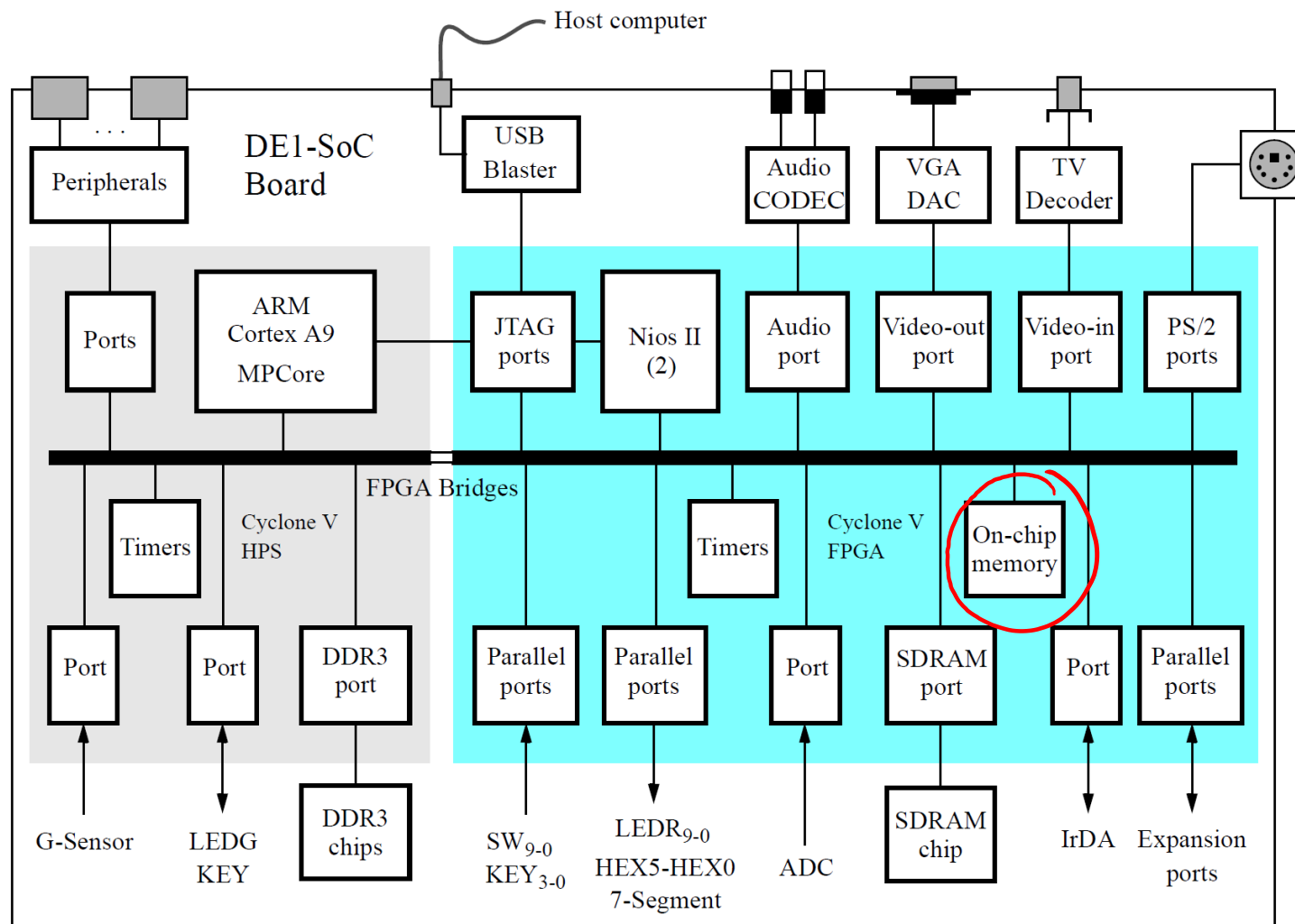


Figure 1. Block diagram of the DE1-SoC Computer.

# Cyclone V Adaptive Logic Modules

Figure 1-5: ALM High-Level Block Diagram for Cyclone V Devices

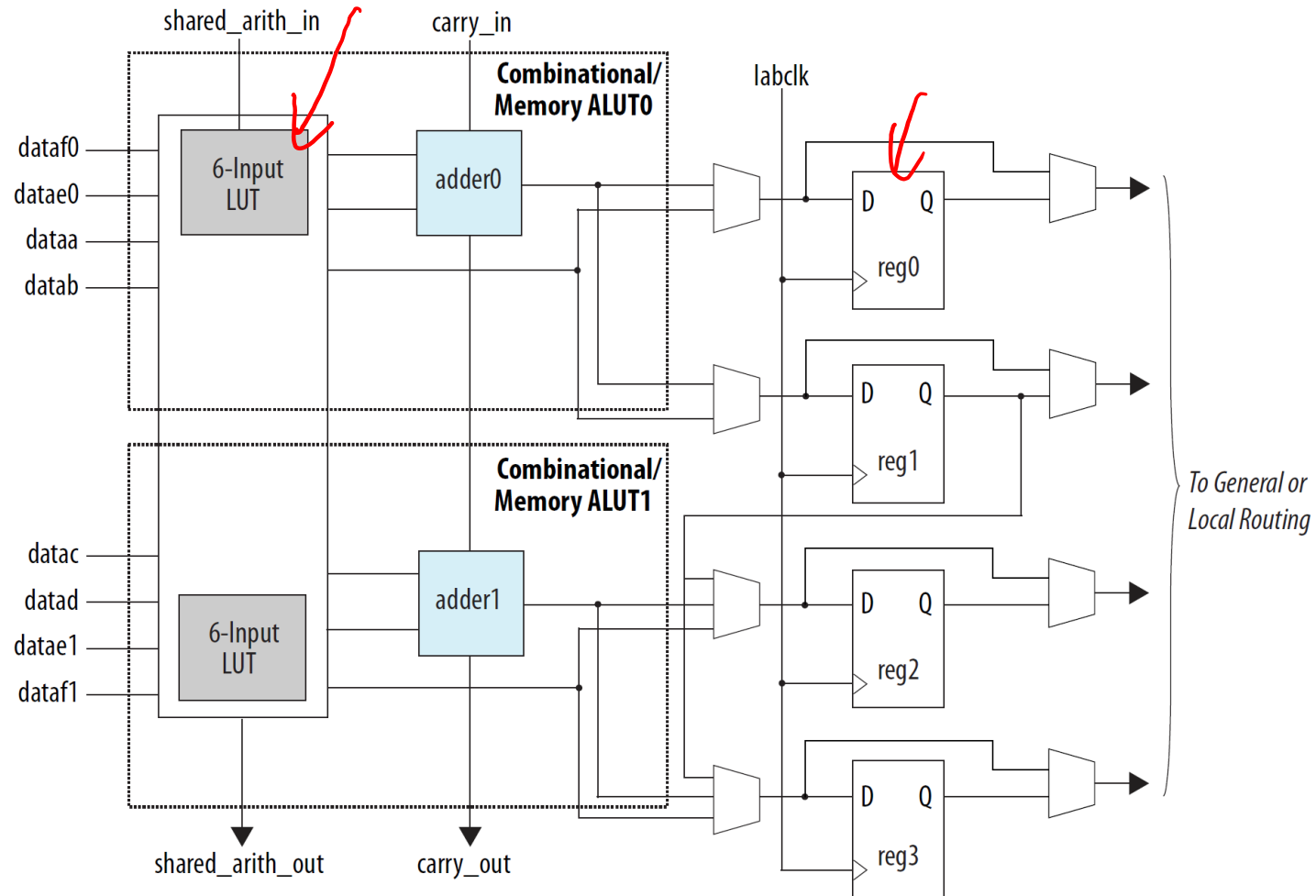


# Memory Modules


## ❖ Key characteristics of a simple memory module:

- Width – the number of **bits** in a word
- Depth – the number **words** in the module
- Number of ports
- Synchronicity of port access – whether or not accesses are controlled by a clock signal
- Simultaneous address access – can the same address be used for both read and write operations

} size of memory

 

## ❖ Example: WriteEnable Address

 

# Memory Characteristics

❖ Memory units are specified as depth × width.

*# of addresses* (pointing to depth)  
*size of word* (pointing to width)

❖ For the following memory units, answer:

- 1) Memory capacity (in bits and bytes using IEC prefixes) *depth × width*
- 2) Width of address bus ( $a$ )  *$\lceil \log_2(\text{depth}) \rceil$*
- 3) Width of data output bus ( $n$ ) *width*

❖ Memory 1: 8Ki × 32

*2<sup>3</sup>* ↓ *2<sup>10</sup>* ↓ *2<sup>5</sup>*

①  $2^{18}$  bits = 256 Ki-bits = 32 Ki-bytes

② 13 bits

③ 32 bits

❖ Memory 2: 2Gi × 8

*2<sup>1</sup>* ↓ *2<sup>30</sup>* ↓ *2<sup>3</sup>*

①  $2^{34}$  bits = 16 Gi-bits = 2 Gi-bytes

② 31 bits

③ 8 bits

TECHNOLOGY

BREAK

# Memory Type #1: ROM

## ❖ Read-Only Memory

- A purely *combinational* circuit (no internal state)
- Output is determined solely by address input

## ❖ In an FPGA:

- No actual embedded ROM, but can be emulated by a combinational circuit or a RAM with the write operation disabled
- Only practical for small tables

## ❖ In SystemVerilog:



- Define the ROM content as a 2-dimensional constant
- Oftentimes a selected assignment or case statement

# Example ROM

## ❖ Hex-to-7seg LED decoder:

### ■ Segments:

- Active low

  

## ❖ ROM size?

16 × 7 bits

depth (addresses)


B3	B2	B1	B0	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0
		⋮					⋮			
1	1	0	1	1	0	0	0	0	1	0
1	1	1	0	0	1	1	0	0	0	0
1	1	1	1	0	1	1	1	0	0	0

width (words)

# Example ROM: Case Implementation

```
module ROM_case(addr, data);  
    input logic [3:0] addr;  
    output logic [6:0] data;  
    always_comb  
        case (addr)  
            // L6543210  
            4'h0: data = 7'b1000000;  
            4'h1: data = 7'b1111001;  
            4'h2: data = 7'b0100100;  
            // ...  
            4'hD: data = 7'b0100001;  
            4'hE: data = 7'b0000110;  
            4'hF: data = 7'b0001110;  
        endcase  
endmodule // ROM_case
```

*watch the bit ordering!*



# Reading Data from a File

- ❖ Hard-coded values in your SV files can be tedious to format, debug, and swap out!
- ❖ Verilog provides *system tasks* to read data from a text file into an array:  
\$readmemb() and \$readmemh()
  - Basic usage: `$readmemb("file.txt", my_array);`
  - Reads in numerals (in **binary** or **hex**) from file separated by *whitespace* (i.e., spaces, tabs, newlines)
  - Can avoid some recompilation
  - File can have any extension (*.txt, .mem, .bit, .hex*)
- ★ Be very careful with dimensions of array and ordering of data in file!

# Example ROM: File Implementation

```

module ROM_file(addr, data);

  input logic [3:0] addr;
  output logic [6:0] data;

  logic [6:0] ROM [0:15]; // (!) unpacked dimension

  initial
    // reads binary values from file into array
    $readmemb("seg7decode.txt", ROM);

  assign data = ROM[addr];
endmodule // ROM_file

```

seg7decode.txt:  
read left to right, then  
top-to-bottom.

read as ROM[0]      white space      read as ROM[15]

<u>1000000</u>	1111001	0100100	0110000
0011001	0010010	0000010	1111000
0000000	0010000	0001000	0000011
1000110	0100001	0000110	<u>0001110</u>

# Dynamic Array Indexing Operation

- ❖ A signal can be used as an index to access an element in the array:


```
assign data = ROM[addr];
```

equivalent to

```
always_comb
case (addr)
  4'h0: data = ROM[0];
  4'h1: data = ROM[1];
  // ...
  4'hE: data = ROM[14];
  4'hF: data = ROM[15];
endcase
```
 
# Synchronicity Revisited

- ❖ To synchronize either the address input or ROM output, we can add a register as appropriate
  - Sometimes called “registering” the input or output to make your module “synchronous”
  - In SystemVerilog, can be done inside or outside of the module:



converted  
assign

```
initial
    $readmemb("seg7decode.txt", ROM);


// internally-registered ROM module
always_ff @(posedge clk)
    data <= ROM[addr];
```

# Memory Type #2: RAM

- ❖ **Random-Access Memory**
  - Can read and write to any address instead of having to read in sequence (*e.g.*, a magnetic disk)
- ❖ Can be implemented using different semiconductor technologies:
  - Static RAM (SRAM): Uses flip-flops to store data
  - Dynamic RAM (DRAM): Uses capacitors and transistors to store data that need to be periodically refreshed
  - SRAM is faster but more expensive than DRAM
- ❖ In a typical home computer:
  - CPU registers and caches are SRAM
  - “Memory” is *synchronous* DRAM (SDRAM)
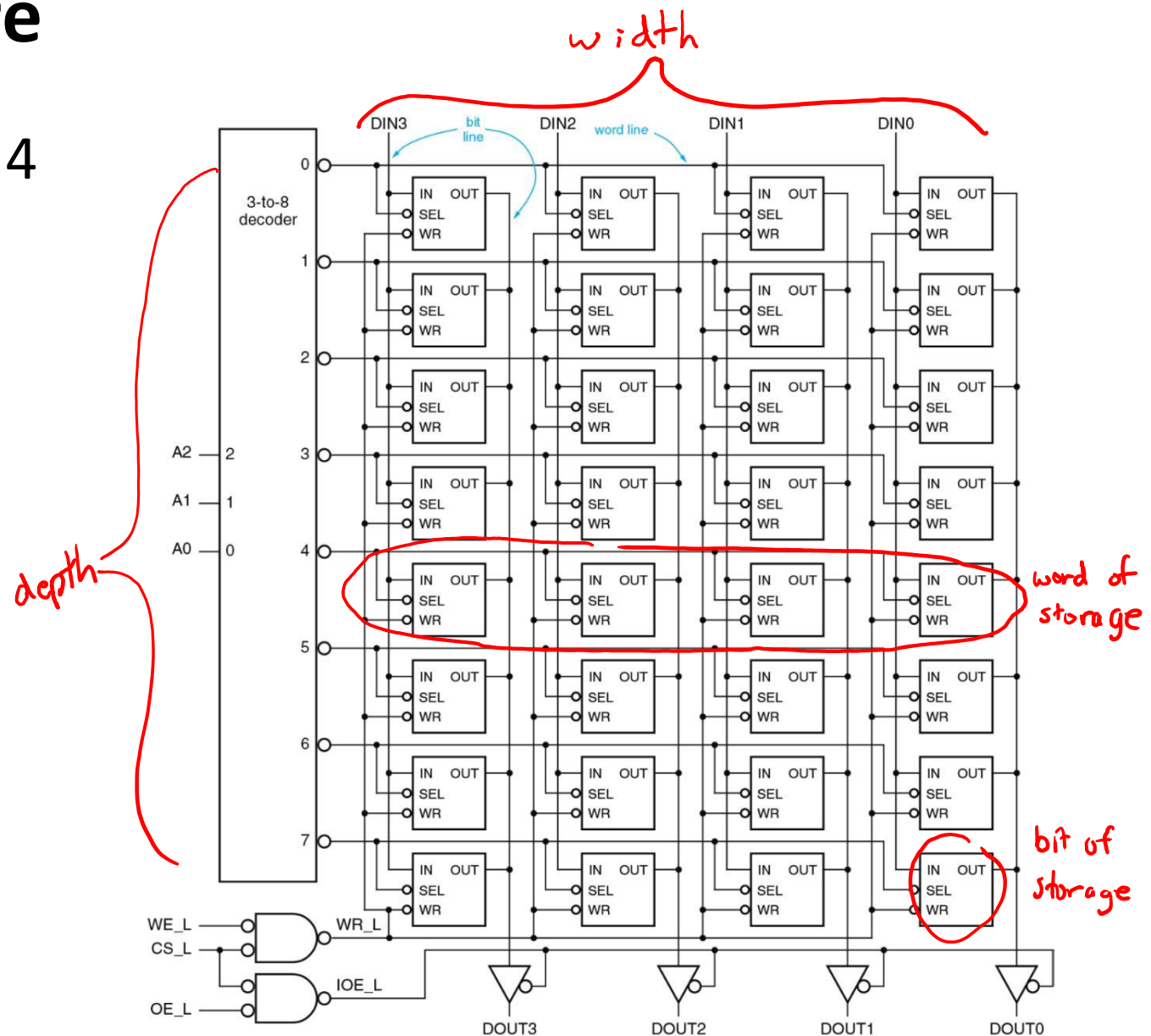
# Example RAM Hardware

- ❖ Internal structure of an  $8 \times 4$  static RAM:
  - Figure 15.18 from Wakerly



# RAM Variants

❖ Note that not all of the terminology used here is standardized:

## 1) Synchronicity

- Are the operations controlled by the clock?
- Can be applied to reading and writing independently

## 2) Number of ports''

- Not in the same sense as number of SV module ports
- Can roughly think of as "channels" (set of addr in, data in, write enable, and data out ports) – how many reads and writes can occur simultaneously?

## 3) Address independence

- Are the port's read and write operation based on the same or independent addr in buses?

# Synchronous Single-Port RAM

## ❖ Synchronous Inputs:


- wren (1 = write, 0 = read)
- addr ( $A$ -bit address)
- din ( $D$ -bit data)

## ❖ Synchronous Output:

- dout ( $D$ -bit data)
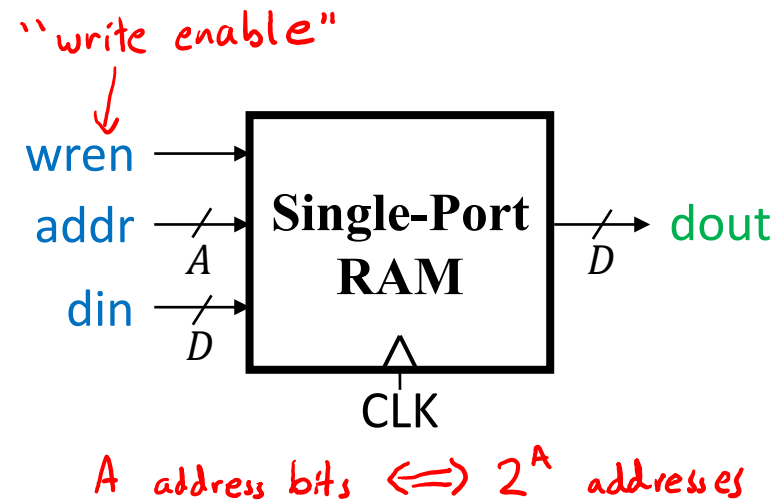
## ❖ Implementation hints:

- Will need an internal RAM array of what size?  $2^A \times D$
- To synchronize, should update on clock triggers *always-ff @ (posedge clk)*
- What should dout do when wren = 1? *also set to din*



# Synchronous Single-Port RAM: Implementation (1/2)

```
module RAM_single #(parameter A, D)
    (clk, wren, addr, din, dout);
```

```
endmodule // RAM_single
```

# Synchronous Single-Port RAM: Implementation (2/2)

```
module RAM_single #(parameter A, D)
    (clk, wren, addr, din, dout);

    input  logic clk, wren;
    input  logic [A-1:0] addr;
    input  logic [D-1:0] din;
    output logic [D-1:0] dout;

    logic [D-1:0] RAM [0:2**A-1];

    always_ff @(posedge clk) begin
        if (wren) begin // write
            RAM[addr] <= din;
            dout <= din;
        end
        else // read
            dout <= RAM[addr];
        end // always_ff
    endmodule // RAM_single
```

*could be either ordering since we aren't loading from a file*

*can't be RAM[addr] because non-blocking assignment*