

DESIGN OF DIGITAL CIRCUITS AND SYSTEMS

ASM with Datapath I

Instructor: Justin Hsia

Teaching Assistants:

Colton Carroll

Grace Zhou

Hemil Patel

Quinlyn Donohue


Rasya Fawwaz

Rose Maresh

Relevant Course Information




- ❖ Homework 2 late deadline tonight (4/16)
- ❖ Homework 3 due next Friday (4/24)
 - FIFO buffers & ASM charts
- ❖ Lab 2 reports due Friday (4/17), demos 4/20-24
 - Same lab demo slots for whole quarter
- ❖ Lab 3 due 5/1
 - Lab 3 + 4 are really ~1.5 weeks long, so don't wait!
- ❖ Quiz 2 next Thursday (4/23)
 - Memory (ROM, RAM, reg files)

Review: ASM Chart

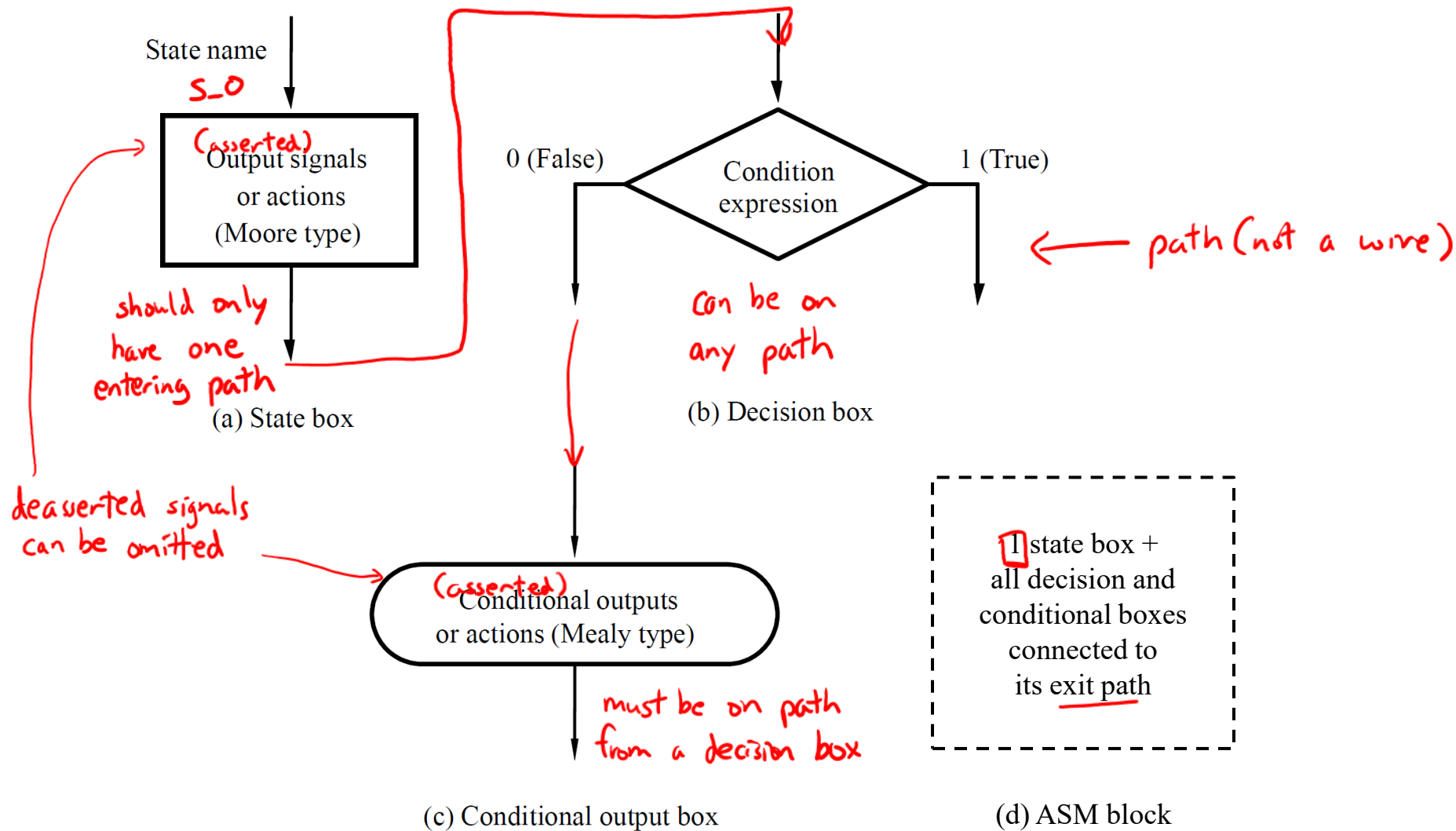


Review Question: 3-way Switch

 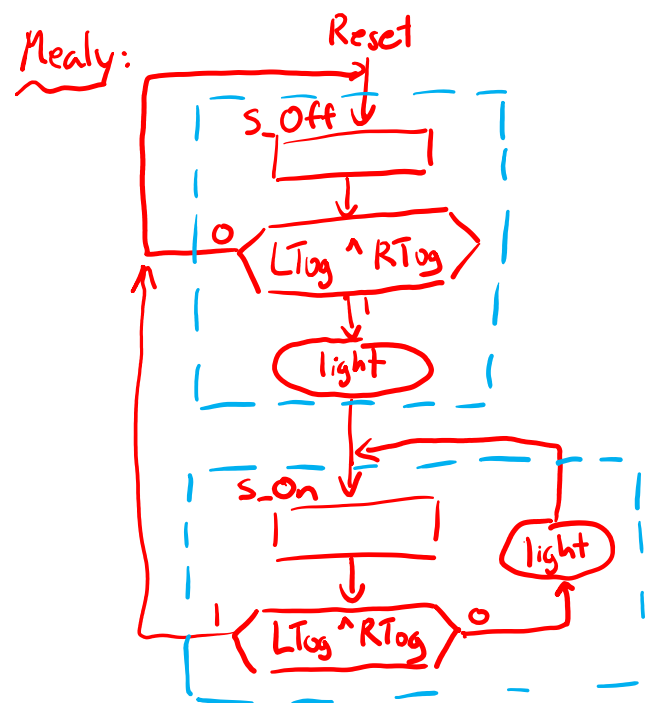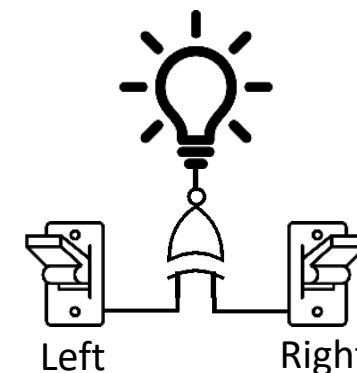- ❖ Create an ASM chart for a 3-way switch system using *Mealy*-type output
 - LTog and RTog pulse 1 when the switch is flipped/toggled
 - Output called light




ASMD Charts (1/2)

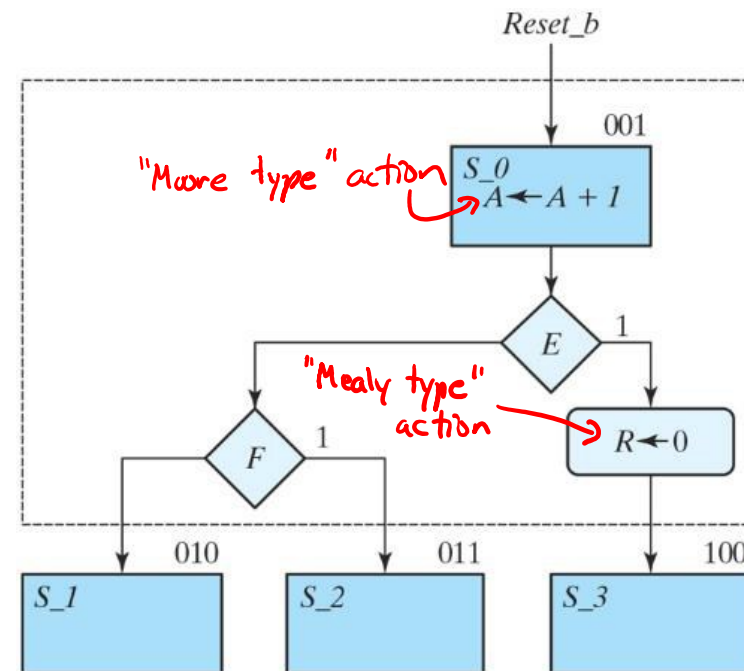- ❖ An **A**lgorithmic **S**tate **M**achine with a **D**atapath chart is created by adding RTL operations to an ASM chart
- ★ Timing of operations can be confusing – *NOT* a flowchart
- ❖ School of Thought #1:
 - RTL operations are triggered by control signals, so they can appear anywhere an output signal can:




ASMD Charts (2/2)

 - ❖ An **A**lgorithmic **S**tate **M**achine with a **D**atapath chart is created by adding RTL operations to an ASM chart
 - Timing of operations can be confusing – *NOT* a flowchart
- ❖ School of Thought #2:
 - It's clearer to separate control signals (Control) from RTL operations (Datapath)
- ❖ There isn't a set standard
 - You may see both or variants
 - ***We use School of Thought #2***




ASMD Hardware (1/2)

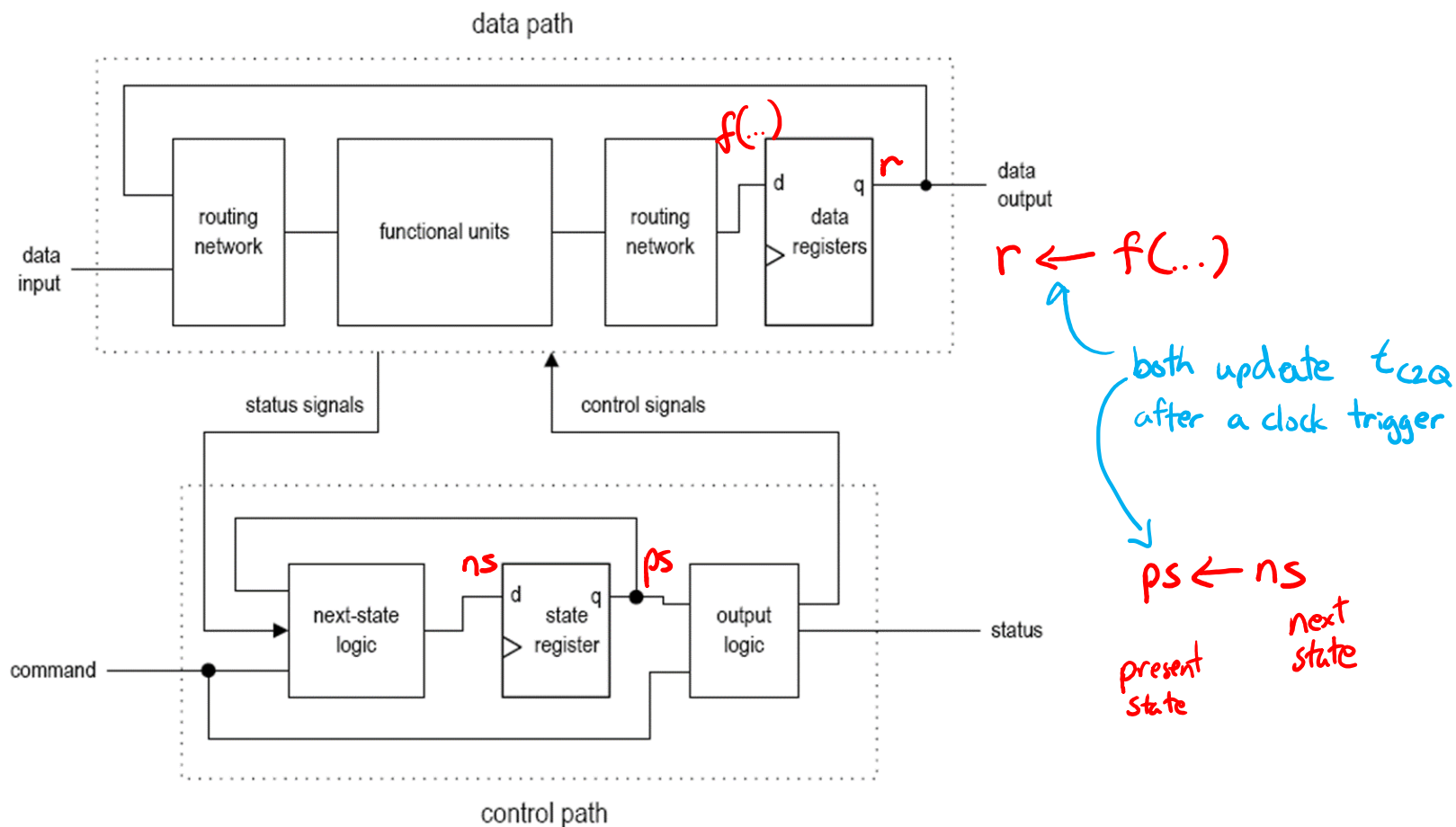- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





ASMD Hardware (2/2)

 - ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!
- ❖ The behavior of both state and data registers depend on the current control state
 - Can conceptually think of as a MUX to the registers' inputs that uses the current state as its selector bits





Hardware Example (1/2)

 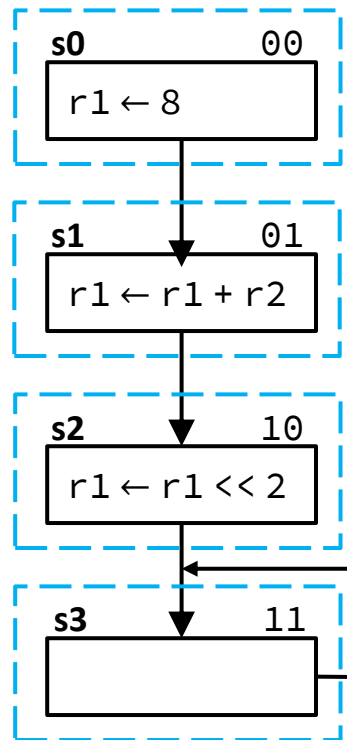- ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!





Hardware Example (2/2)

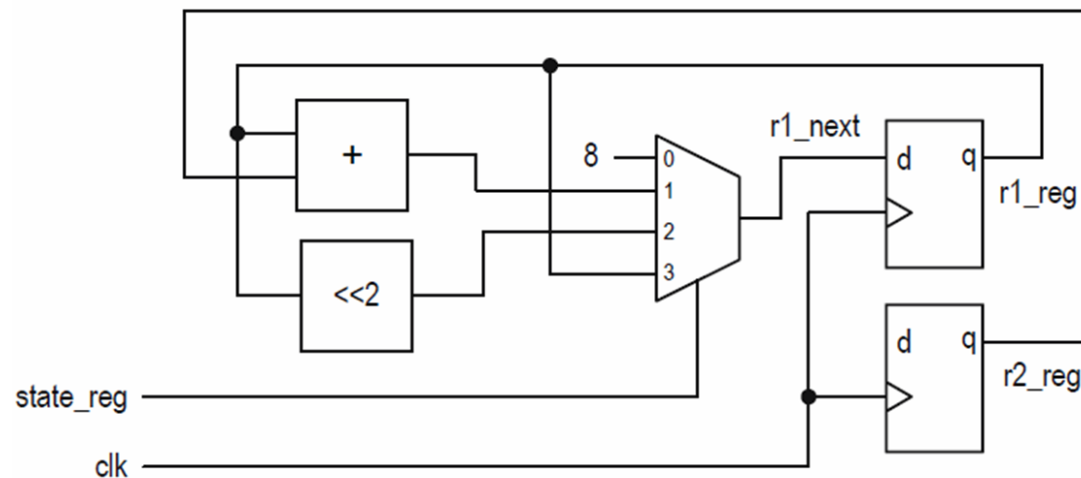 - ❖ State transitions and RTL operations are both controlled by the clock
 - It's often helpful to remember the underlying hardware – registers!



ASMD Timing (1/2)

 
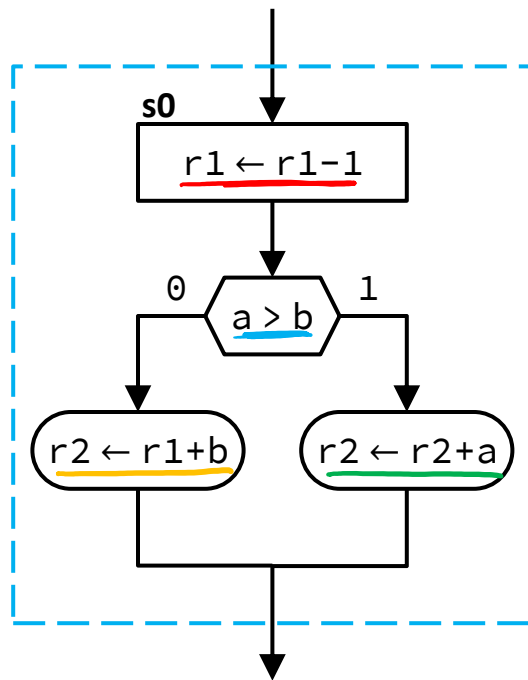
- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than *entrance*



this is only routed once we are in state $s0$, and $r1_reg$ reads that input on the next cycle

ASMD Timing (2/2)

 
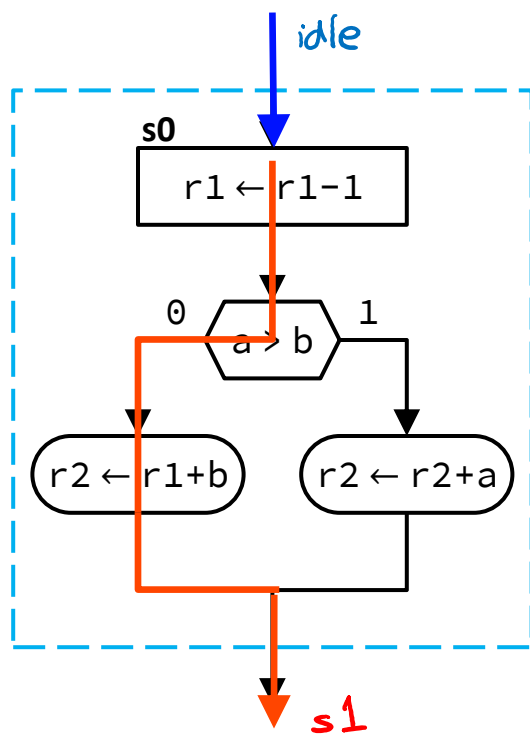
- ❖ Everything (registers!) within an ASM block occurs simultaneously at the next clock trigger
 - Differs from a flowchart – changes occur at state exit rather than *entrance*



ASMD Timing Question


- ❖ What value will be stored in r when we transition from state $s1$ to the next state? **-1**, 0, 1

  we exit when $r=0$, which means $0-1=-1$ is sitting on the input to r




ASMD Timing Tip

 
- ❖ When a registered output (e.g., r) is used in a decision box, its effect may appear to be delayed by one clock
 - Can define a next-state value (e.g., r_{next}) to use instead



(a) Use old value of r

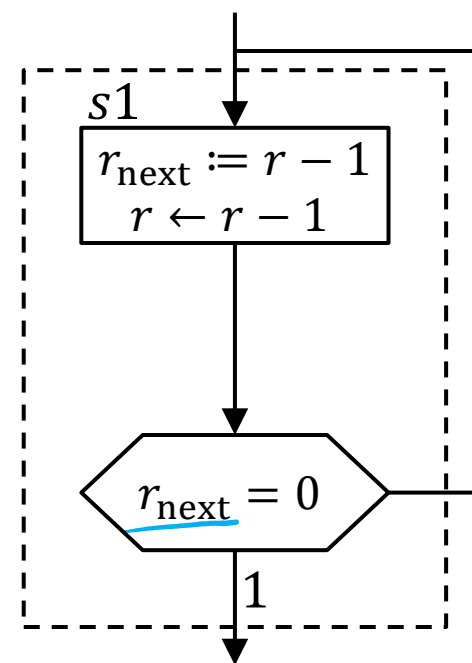

(b) Use new value of r

 

SHORT TECH

BREAK


ASMD Design Procedure

- ❖ From problem description or algorithm pseudocode:
 - 1) Identify necessary datapath components and operations**
 - 2) Identify states and signals that cause state transitions** (external inputs and status signals), based on the necessary sequencing of operations
 - 3) Name the control signals** that are generated by the controller that cause the indicated operations in the datapath unit
 - 4) Form an ASM chart for your controller**, using states, decision boxes, and signals determined above
 - 5) Add the datapath RTL operations** associated with each control signal

Design Example #1


❖ System specification:

- datapath ■ Flip-flops E and F
- datapath ■ 4-bit binary up-counter A = 0bA₃A₂A₁A₀
- inputs to control ■ Active-low reset signal reset_b puts us in state S_idle, where we remain while signal Start = 0
- control signals ■ Start = 1 initiates the system's operation by clearing A and F. At each subsequent clock pulse, the counter is incremented by 1 until the operations stop.
- status signals ■ Bits A₂ and A₃ determine the sequence of operations:
 - control signals • If A₂ = 0, set E to 0 and the count continues
 - If A₂ = 1, set E to 1; additionally, if A₃ = 0, the count continues, otherwise, wait one clock pulse to set F to 1 and stop counting (*i.e.*, back to S_idle)

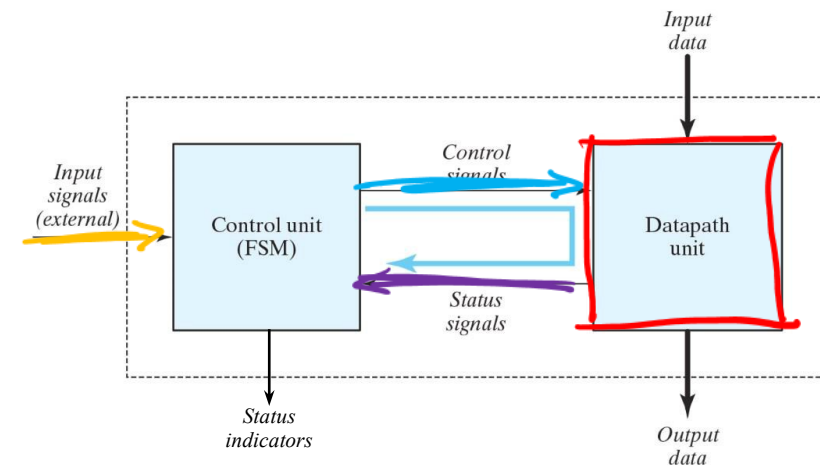


Design Example #1: Block Diagram

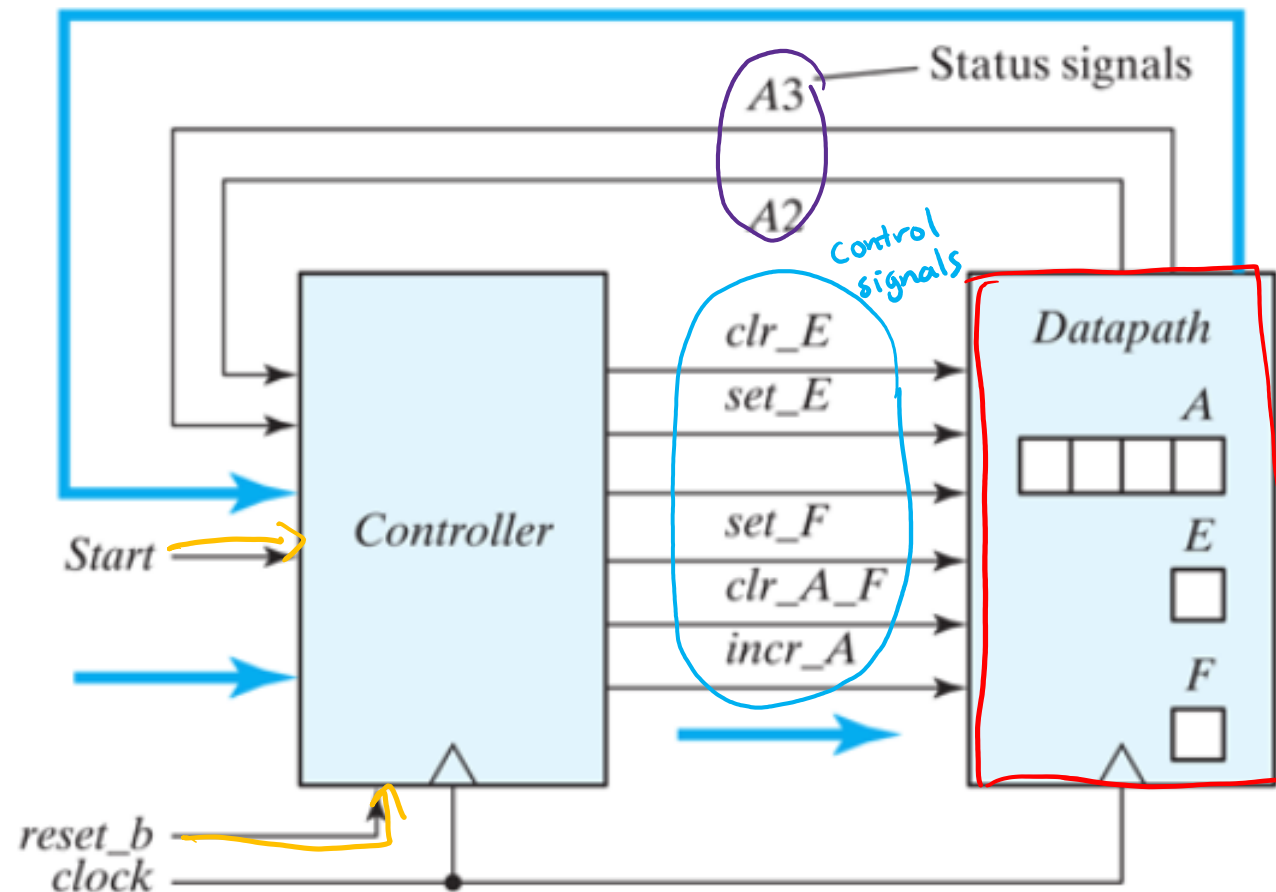- ❖ The system can be represented by the following block diagram:




Design Example #1: ASM → ASMD Chart

- ❖ Synchronous or asynchronous reset?

 

 for synchronous reset, add decision box on reset-b out of every state box:



Design Example #1: Timing

❖ Sequence of operations:

		Counter				Flip-Flops		Conditions	State
		A ₃	A ₂	A ₁	A ₀	E	F		
		X	X	X	X	1	X	Start	S_idle
clr_A-F ↻	↻	0	<u>0</u>	0	0	1	0	A ₂ = 0, A ₃ = 0	S_count
clr_E ↻	↻	0	0	0	1	0	0		
		0	0	1	0	0	0		
		0	0	1	1	0	0		
set_E ↻	↻	0	<u>1</u>	0	0	0	0	A ₂ = 1, A ₃ = 0	
		0	1	0	1	1	0		
		0	1	1	0	1	0		
		0	1	1	1	1	0		
clr_E ↻	↻	1	<u>0</u>	0	0	1	0	A ₂ = 0, A ₃ = 1	
		1	0	0	1	0	0		
		1	0	1	0	0	0		
		1	0	1	1	0	0		
set_E ↻	↻	1	<u>1</u>	0	0	0	0	A ₂ = 1, A ₃ = 1	
		1	1	0	1	1	0		
		1	1	0	1	1	1		S_idle

Design Example #1: Logic

❖ Controller:

■ State Table:

$$S_{idle} = \overline{P_1} \overline{P_0}$$

$$S_{count} = \overline{P_1} P_0$$

$$S_F = P_1 P_0$$

state logic inputs ← → state logic outputs

Present-State Symbol	Present State		Inputs			Next State		Outputs				
	P_1	P_0	Start	A_2	A_3	N_1	N_0	set_E	clr_E	set_F	clr_A_F	incr_A
S_{idle}	0	0	0	X	X	0	0	0	0	0	0	0
S_{idle}	0	0	1	X	X	0	1	0	0	0	1	0
S_{count}	0	1	X	0	X	0	1	0	1	0	0	1
S_{count}	0	1	X	1	0	0	1	1	0	0	0	1
S_{count}	0	1	X	1	1	1	1	1	0	0	0	1
S_F	1	1	X	X	X	0	0	0	0	1	0	0

■ Logic:

$$N_1 = S_{count} \cdot A_2 \cdot A_3$$

$$set_F = S_F$$

$$N_0 = S_{count} + S_{idle} \cdot Start \quad clr_{A_F} = S_{idle} \cdot Start$$

$$set_E = S_{count} \cdot A_2$$

$$incr_A = S_{count}$$

$$clr_E = S_{count} \cdot \overline{A_2}$$

SHORT TECH

BREAK

Design Example #1: Controller Outline (1/2)

control signals (out)
 status signals (in)
 external inputs (in)

```

module controller (set_E, clr_E, set_F, clr_A_F,
                  incr_A, A2, A3, Start, clk,
                  reset_b);
  // port definitions
  input logic Start, clk, reset_b, A2, A3;
  output logic set_E, clr_E, set_F, clr_A_F, incr_A;

  // define state names and variables
  enum logic [1:0] { S_idle, S_count, S_F = 2'b11 } ps, ns;

  // controller logic w/synchronous reset
  always_ff @(posedge clk)
    if (~reset_b)
      ps <= S_idle;
    else
      ps <= ns;

  // asynchronous reset:
  always_ff @(posedge clk, negedge reset_b)
    if (~reset_b)
      ps <= S_idle;
    else
      ps <= ns;
  
```

Design Example #1: Controller Code (1/2)

control signals (out)
status signals (in)
external inputs (in)

```
module controller (set_E, clr_E, set_F, clr_A_F,  
                 incr_A, A2, A3, Start, clk,  
                 reset_b);  
  
    // port definitions  
    input logic Start, clk, reset_b, A2, A3;  
    output logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // define state names and variables  
    enum logic [1:0] {S_idle, S_count, S_F = 2'b11} ps, ns;  
  
    // controller logic w/synchronous reset  
    always_ff @(posedge clk)  
        if (~reset_b)  
            ps <= S_idle;  
        else  
            ps <= ns;
```

Design Example #1: Controller Outline (2/2)

```
// next state logic
```

```
always-comb  
case (ps)
```

```
  S_idle:    ns = Start ? S_count : S_idle;
```

```
  S_count:   ns = (A3 & A2) ? S_F : S_count;
```

```
  S_F:      ns = S_idle;
```

```
end case
```

```
// output assignments
```

```
assign set_E = (ps == S_count) & A2;
```

```
  ⋮  
  ⋮  
  ⋮
```

```
endmodule // controller
```

Design Example #1: Controller Code (2/2)

```
// next state logic
always_comb
  case (ps)
    S_idle: ns = Start ? S_count : S_idle;
    S_count: ns = (A2 & A3) ? S_F : S_count;
    S_F:      ns = S_idle;
  endcase

// output assignments
assign set_E   = (ps == S_count) & A2;
assign clr_E   = (ps == S_count) & ~A2;
assign set_F   = (ps == S_F);
assign clr_A_F = (ps == S_idle) & Start;
assign incr_A  = (ps == S_count);

endmodule // controller
```

Design Example #1: Datapath Outline

control signals (in)
 status signals (out)
 external inputs (in)
 external outputs (out)

```

module datapath (A, E, F, clk, set_E, clr_E, set_F, clr_A_F,
                incr_A);

  // port definitions
  output logic [3:0] A;
  output logic E, F;
  input  logic clk, set_E, clr_E, set_F, clr_A_F, incr_A;

  // datapath logic
  always_ff@ (posedge clk) begin
    if (set_E)   E <= 1;
    else if (clr_E) E <= 0;
    if (set_F)   F <= 1;
    else if (clr_A_F) begin
      A <= 4'h0;
      F <= 0;
    end
    else if (incr_A) A <= A + 4'h1;
  end
endmodule // datapath
  
```

} watch for potential conflicts!

Design Example #1: Datapath Code

control signals (in)
status signals (out)
external inputs (in)
external outputs (out)

```
module datapath (A, E, F, clk, set_E, clr_E, set_F, clr_A_F,  
                incr_A);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input  logic clk, set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // datapath logic  
    always_ff @(posedge clk) begin  
        if (clr_E)      E <= 1'b0;  
        else if (set_E) E <= 1'b1;  
        if (clr_A_F)  
            begin  
                A <= 4'h0;  
                F <= 1'b0;  
            end  
        else if (set_F) F <= 1'b1;  
        else if (incr_A) A <= A + 4'h1;  
    end // always_ff  
  
endmodule // datapath
```

Design Example #1: Top-Level Code

```
module top_level (A, E, F, clk, Start, reset_b);  
  
    // port definitions  
    output logic [3:0] A;  
    output logic E, F;  
    input logic clk, Start, reset_b;  
  
    // internal signals (control signals and status signals that aren't outputs)  
    logic set_E, clr_E, set_F, clr_A_F, incr_A;  
  
    // instantiate controller and datapath  
    controller c_unit (.set_E, .clr_E, .set_F,  
                      .clr_A_F, .incr_A, .A2(A[2]),  
                      .A3(A[3]), .Start, .clk,  
                      .reset_b);  
  
    datapath d_unit (.*);  
  
endmodule // top_level
```