

# DESIGN OF DIGITAL CIRCUITS AND SYSTEMS

## Algos to Hardware II, Timing Review

**Instructor:** Justin Hsia

**Teaching Assistants:**

Colton Carroll

Grace Zhou

Hemil Patel

Quinlyn Donohue

Rasya Fawwaz

Rose Maresh



# Relevant Course Information

- ❖ Anonymous mid-quarter survey on Canvas (due 5/4)
- ❖ Homework 4 due on Monday (5/4)
- ❖ Lab 3 due Friday (5/1)
- ❖ Lab 4 due next Friday (5/8)
- ❖ Lab 5 will be released next week, due 5/22
- ❖ Quiz 3 (ASM, ASMD) next Thursday (5/7)

# Lecture Outline (1/2)

- ❖ **Algorithm → Hardware Wrap-up**
- ❖ Timing Constraints Review


# Sorting Algorithm: ASMD Chart

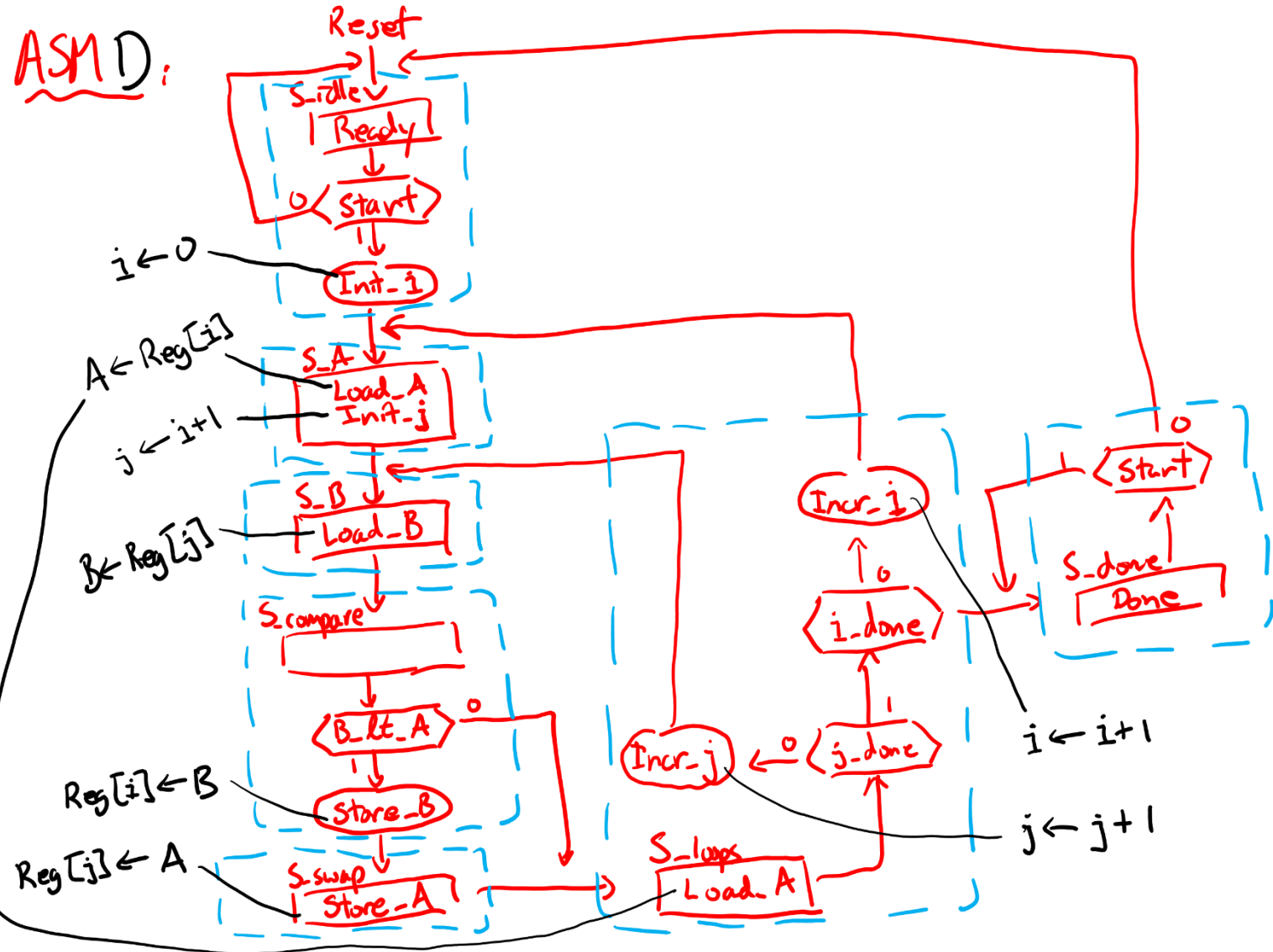 
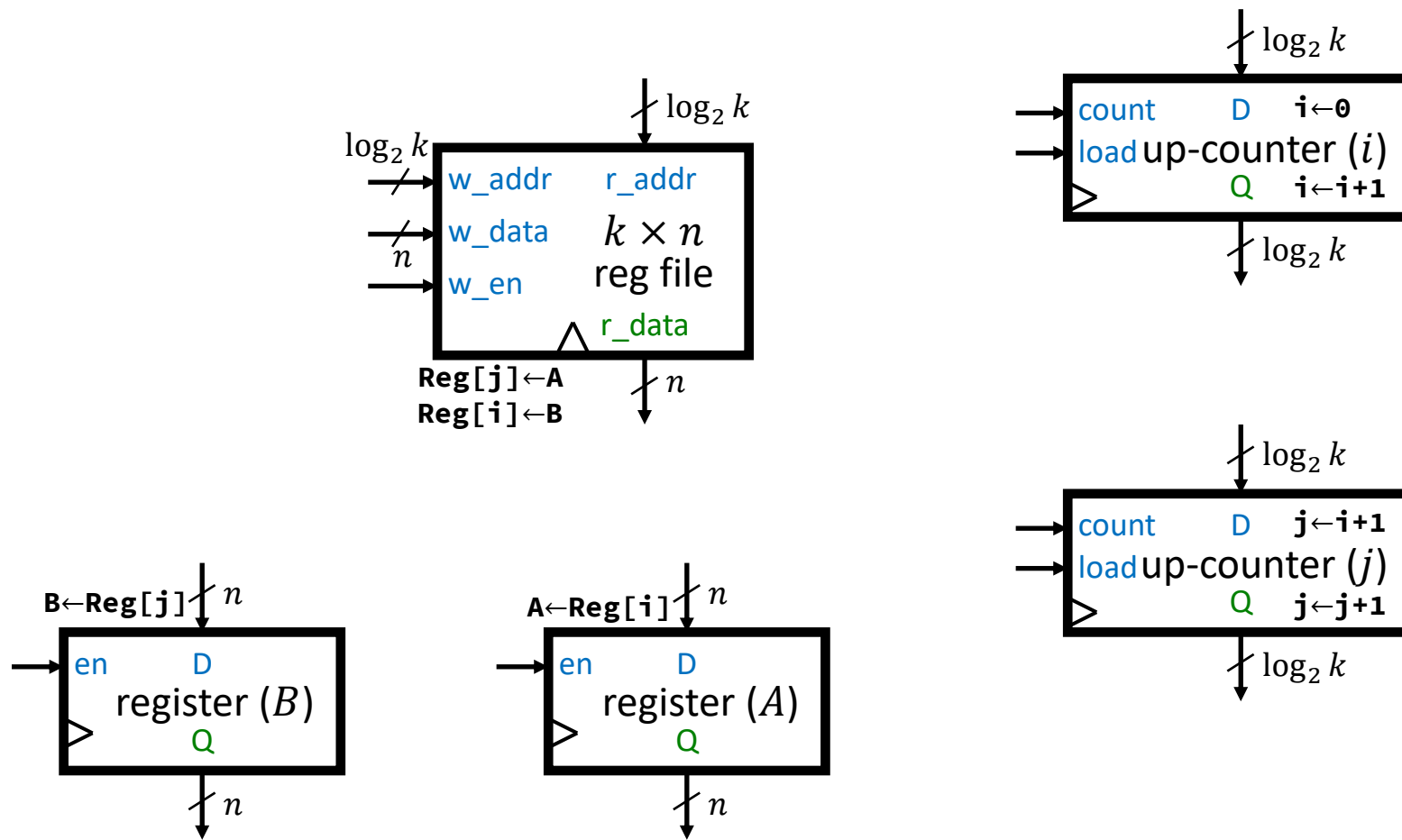
# Sorting Algorithm Datapath

**Control Signals:**  
 Init\_i, Incr\_i  
 Init\_j, Incr\_j  
 Load\_A, Store\_A  
 Load\_B, Store\_B

**Status Signals:**  
 B\_lt\_A  
 i\_done  
 j\_done




# isPrime Algorithm

- ❖ Design a sequential circuit that determines if an input **Num** is a prime number (e.g., 2, 3, 5, 7) or not
  - **Num** has width **W**, output **P** is **1** (prime) or **0** (not prime)
  - Assume the usual **Ready**, **Done**, **Start**, **Reset**
- ❖ Algorithm:

```
N = Num
if N < 3 do           // handle special cases
    return (N == 2)
for F = 2 to N/2 do // factor to check
    if (N % F == 0) do
        return 0
    endif
endfor
return 1
```

# isPrime: ASMD Chart

# isPrime: Block Diagram

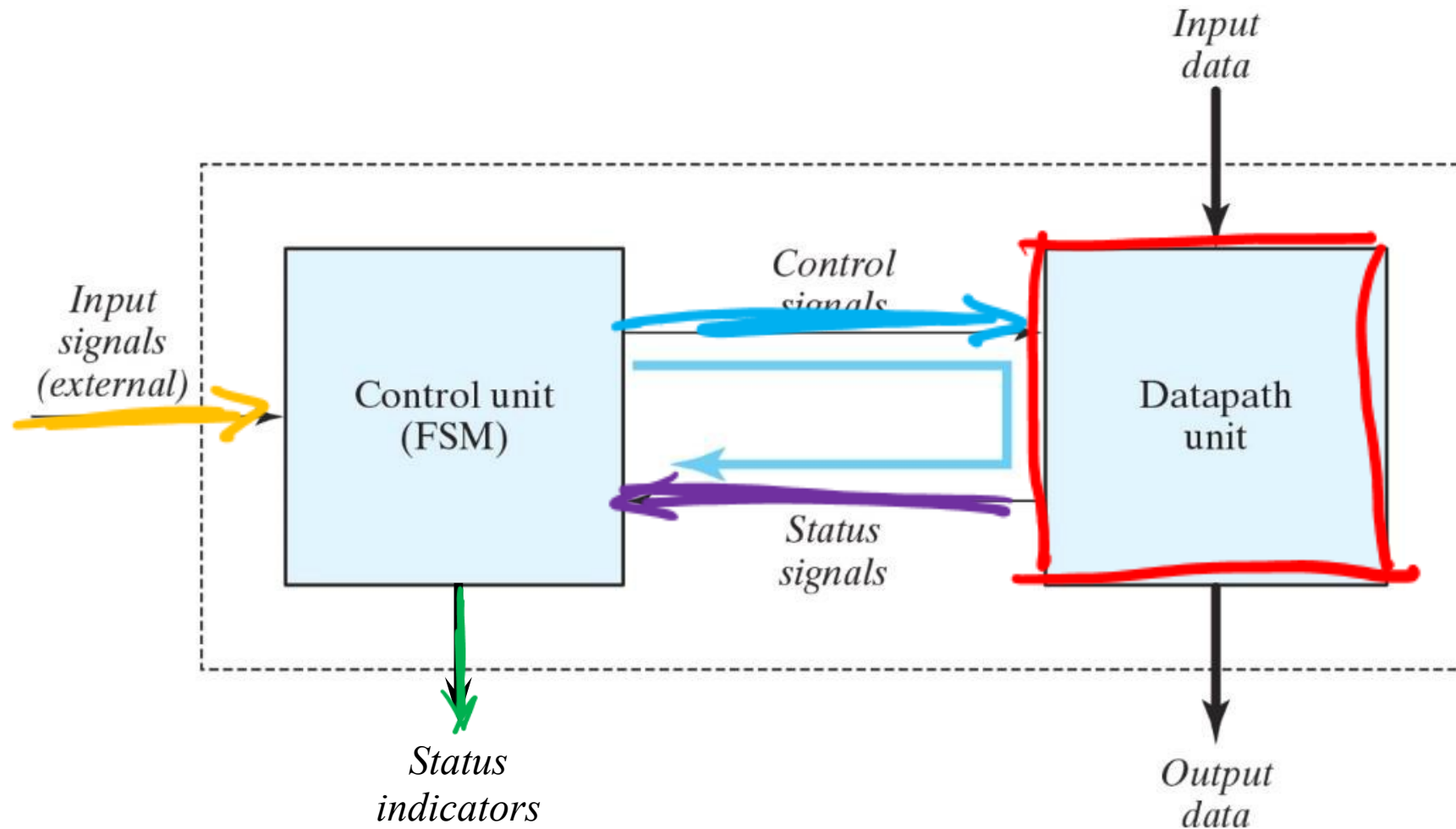

SHORT TECH

BREAK

Download starter code for live coding from [the course schedule!](#)

# isPrime Live Coding Demo

```
isPrime_control:  
    // port definitions  
    // define state names and variables  
    // controller logic w/synchronous reset  
    // next state logic  
    // output assignments  
  
isPrime_datapath:  
    // port definitions  
    // internal datapath signals and registers  
    // datapath logic  
    // output assignments  
  
isPrime:  
    // port definitions  
    // define status and control signals  
    // instantiate control and datapath
```

# Basic Testbench Review

## ❖ How to start a testbench:

- 1) Create a `<name>_tb` module with no ports
- 2) Create variables that match the module's ports
- 3) Instantiate an instance of the module can call it `dut` or `uut`
- 4) If needed, create a simulated clock
- 5) Create an `initial` block to define your test inputs

## ❖ Tools we know about:

- Timing controls: `#<time>;`, `@(posedge <signal>);`
- Loops: `integer i; for (i = 0; i < 2**3; i++)`  
`repeat (2**4)`

# Testing Your Algorithm

- ❖ Create a testbench for our isPrime module:

```
module isPrime_tb ();  
    // define parameters  
  
    // define module port connections  
  
    // instantiate module  
  
    // create simulated clock  
  
    // define test inputs  
  
endmodule
```

# Testing Your Algorithm

- ❖ Create a testbench for our isPrime module:
  - Single Num value (arbitrary wait):

```
// define test inputs

initial begin
    Num = 3;
    Reset = 1; Start = 0; @(posedge clk);
    Reset = 0;           @(posedge clk);
    Start = 1;           @(posedge clk);
    Start = 0;

    repeat (2**4)        // wait 16 clock cycles
        @(posedge clk);

    @(posedge clk); // extra cycle of output
    $stop();
end
```

# Testing Your Algorithm

- ❖ Create a testbench for our isPrime module:
  - Single Num value (check Ready):

```
// define test inputs

initial begin
    Num = 3;
    Reset = 1; Start = 0; @(posedge clk);
    Reset = 0;           @(posedge clk);
    Start = 1;           @(posedge clk);
    Start = 0;

    @(posedge Ready); // wait until module says it's ready

    @(posedge clk); // extra cycle of output
    $stop();
end
```

# Testing Your Algorithm

- ❖ Create a testbench for our isPrime module:
  - All Num values:

```
// define test inputs
integer i;
initial begin
    Reset = 1; Start = 0; @(posedge clk);
    Reset = 0;           @(posedge clk);

    for (i = 0; i < 2**W; i++) begin
        Start = 1; Num = i; @(posedge clk);
        Start = 0;         @(posedge Ready);
    end

    @(posedge clk); // extra cycle of output
    $stop();
end
```


# Testing Your Algorithm: \$display

- ❖ Triggers once when encountered, prints the given format string and adds a new line:

```
// define test inputs
integer i;
initial begin
  Reset = 1; Start = 0; @(posedge clk);
  Reset = 0;          @(posedge clk);
  for (i = 0; i < 2**W; i++) begin
    Start = 1; Num = i; @(posedge clk);
    Start = 0;          @(posedge Ready);

    $display("T = %4t, isPrime(%2d) = %s",
             $time, Num, P ? "Yes" : "No ");

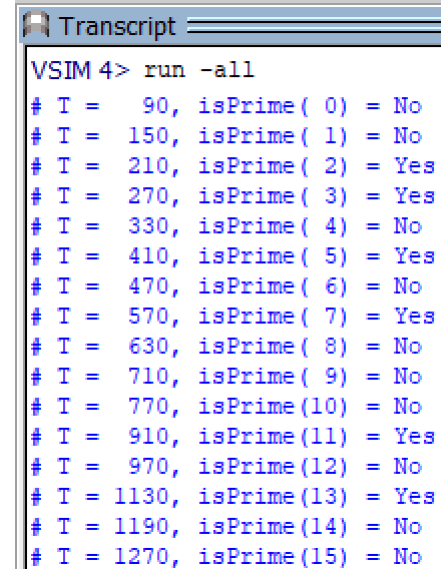  end
  @(posedge clk); // extra cycle of output
  $stop();
end
```



```
Transcript
VSIM 4> run -all
# T = 90, isPrime( 0) = No
# T = 150, isPrime( 1) = No
# T = 210, isPrime( 2) = Yes
# T = 270, isPrime( 3) = Yes
# T = 330, isPrime( 4) = No
# T = 410, isPrime( 5) = Yes
# T = 470, isPrime( 6) = No
# T = 570, isPrime( 7) = Yes
# T = 630, isPrime( 8) = No
# T = 710, isPrime( 9) = No
# T = 770, isPrime(10) = No
# T = 910, isPrime(11) = Yes
# T = 970, isPrime(12) = No
# T = 1130, isPrime(13) = Yes
# T = 1190, isPrime(14) = No
# T = 1270, isPrime(15) = No
```

SHORT TECH


BREAK

# Lecture Outline (2/2)

- ❖ Algorithm → Hardware Wrap-up
- ❖ **Timing Constraints Review**
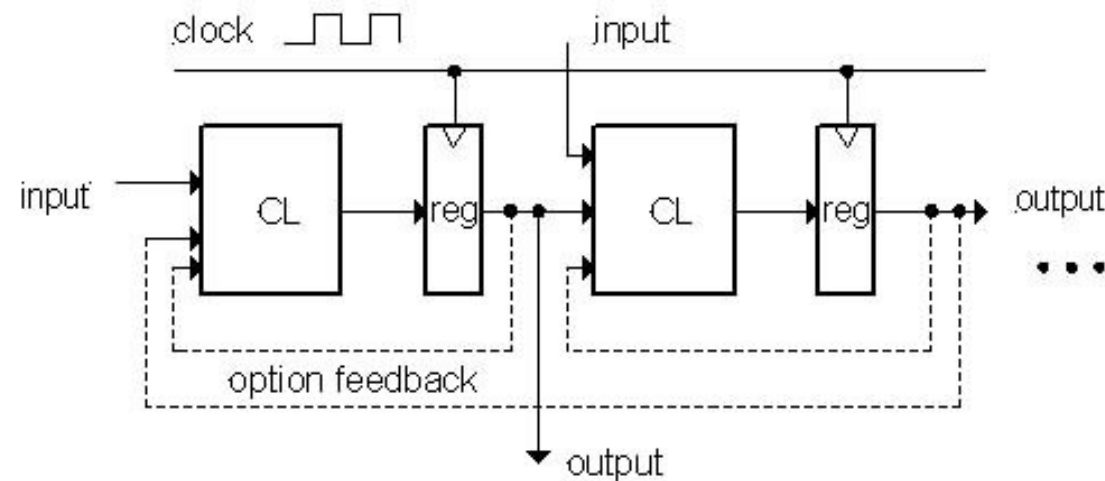
# Why Are Timing Constraints Important?

- ❖ Our model of synchronous digital systems relies on timing behavior of the clock and logic stages
  - Combinational logic blocks separated by registers




- Violations can cause incorrect behavior or can cause produced semiconductor circuits to fail!
- Timing considerations can limit how fast our system/clock can run



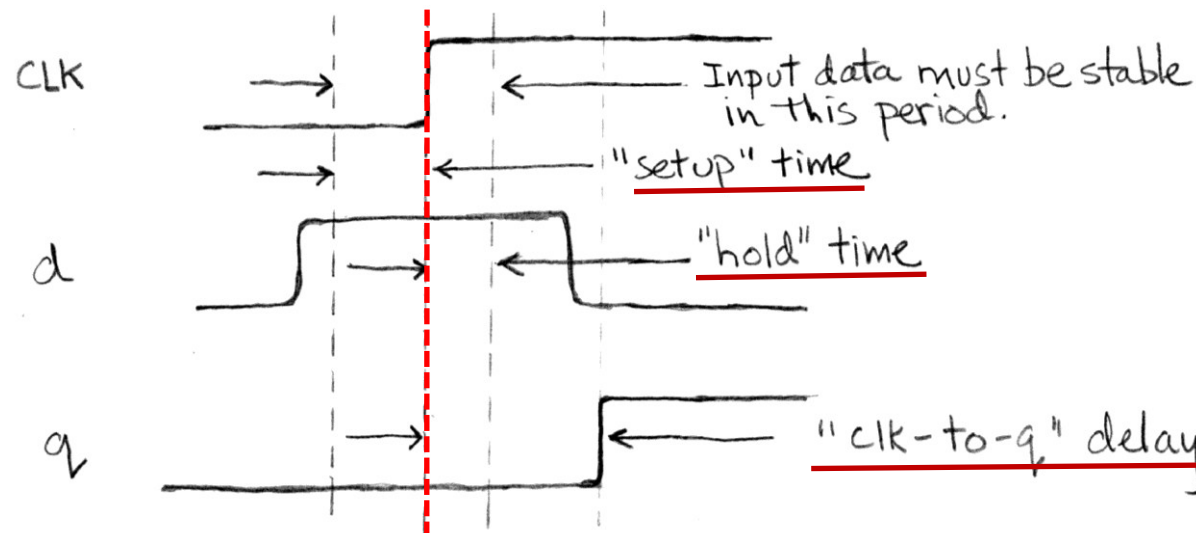
# Review: Sequential Timing Constraints

- ❖ **Setup Time ( $t_s$  or  $t_{su}$ ):** How long the input must be stable *before* the CLK trigger for proper input read
- ❖ **Hold Time ( $t_h$ ):** How long the input must be stable *after* the CLK trigger for proper input read
- ❖ **"CLK-to-Q" Delay ( $t_{c2q}$  or  $t_{co}$ ):** How long it takes the output to change, measured from the CLK trigger



# Where Do Timing Terms Come From?

- ❖ Edge-triggered D flip-flop:

 

By Nolanjshettle at English Wikipedia, CC BY-SA 3.0,  
<https://commons.wikimedia.org/w/index.php?curid=40852354>

# When Can the Input Change?

- ❖ When a register input changes shouldn't violate hold time ( $t_h$ ) or setup time ( $t_{su}$ ) constraints within a clock period ( $T$ )
- ❖ Let  $t_{input,i}$  be the time it takes for the input of a register to change for the  $i$ -th time in a single clock cycle, measured from the CLK trigger:
  - Then we need  $t_h \leq t_{input,i} \leq T - t_{su}$  for all  $i$
  - Two separate constraints!


# Timing Constraint Considerations

- ❖ Use *worst-case analysis*
  - Asynchronous inputs are *really* problematic
  - Use the **critical path** – the longest delay between *any* two registers in a circuit – for setup time constraint
  - Use the shortest path for the hold time constraint
- ❖ A timing violation could be caused by a signal change from the *previous* clock cycle
  - *i.e.*, a really late input change could violate the hold time constraint in the *next* clock cycle
- ❖ Setup time constraint helps determine feasibility of clock frequency:  
max freq =  $1/(\text{min period})$
 
# Timing Constraint Worked Example

❖  $t_{su} = 12 \text{ ns}$ ,  $t_h = 18 \text{ ns}$ ,  $t_{CO} = 8 \text{ ns}$ ,  
 $t_{AND} = 25 \text{ ns}$ , and  $t_{NOR} = 20 \text{ ns}$

- If In changes  $t_{CO}$  after each clock trigger, what is the **minimum clock period** we can use?



- If we use the minimum clock period, when within a clock period  $[0, T]$  can In change without causing a timing violation?