

DESIGN OF DIGITAL CIRCUITS AND SYSTEMS

Algos to Hardware II, Timing Review

Instructor: Justin Hsia

Teaching Assistants:

Colton Carroll

Grace Zhou

Hemil Patel

Quinlyn Donohue

Rasya Fawwaz

Rose Maresh



Relevant Course Information

- ❖ Anonymous mid-quarter survey on Canvas (due 5/4)
- ❖ Homework 4 due on Monday (5/4)
- ❖ Lab 3 due Friday (5/1)
- ❖ Lab 4 due next Friday (5/8)
- ❖ Lab 5 will be released next week, due 5/22
- ❖ Quiz 3 (ASM, ASMD) next Thursday (5/7)

Lecture Outline (1/2)

- ❖ **Algorithm → Hardware Wrap-up**
- ❖ Timing Constraints Review


Sorting Algorithm: ASMD Chart

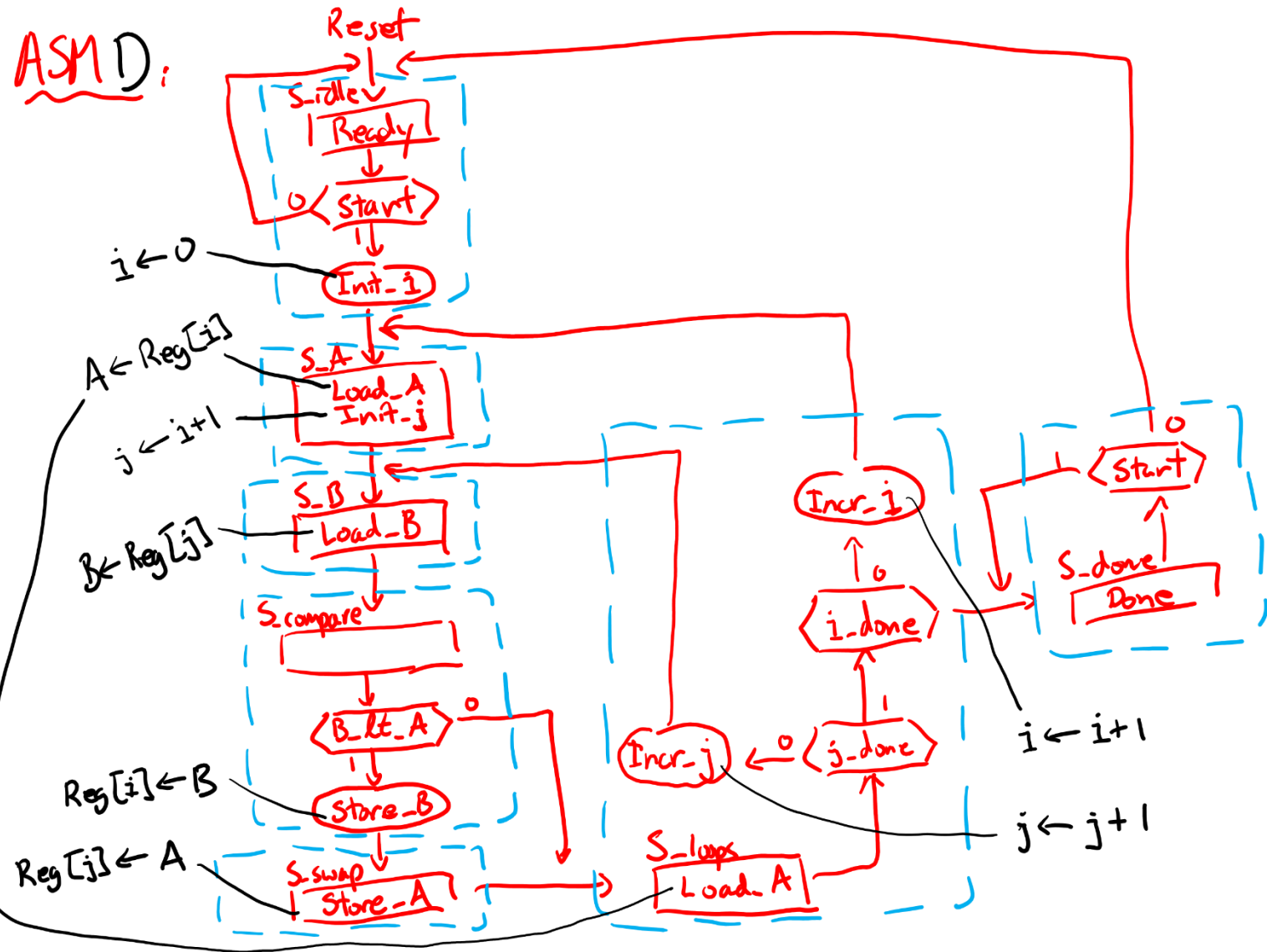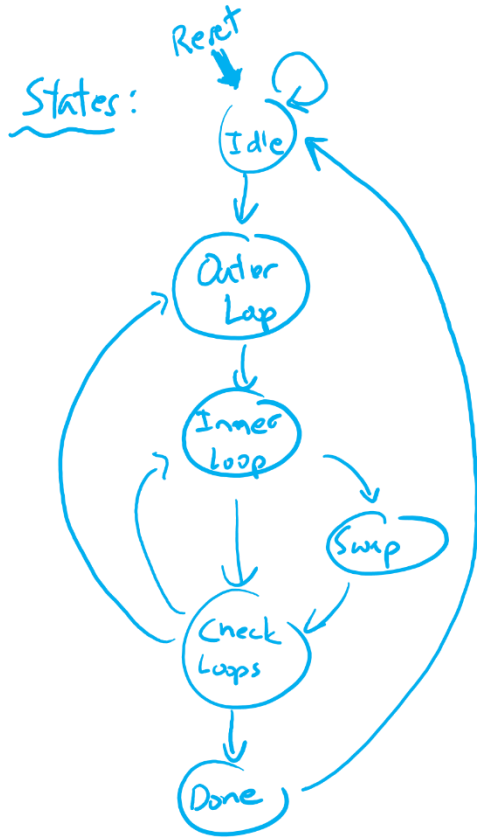

Sorting Algorithm Datapath

Control Signals:
 Init_i, Incr_i
 Init_j, Incr_j
 Load_A, Store_A
 Load_B, Store_B

Status Signals:
 B_lt_A
 i_done
 j_done

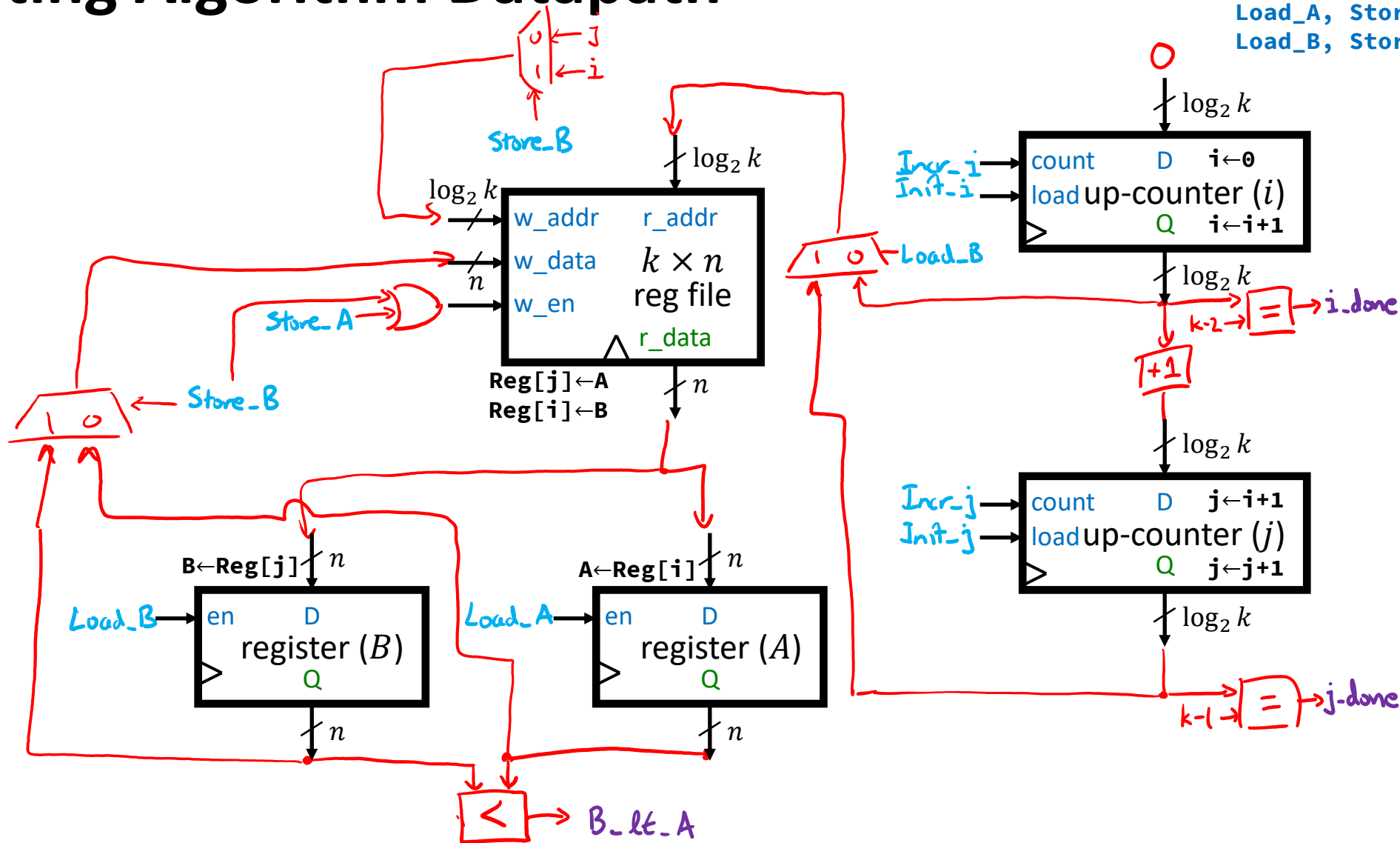


isPrime Algorithm

- ❖ Design a sequential circuit that determines if an input **Num** is a prime number (e.g., 2, 3, 5, 7) or not
 - **Num** has width **W**, output **P** is **1** (prime) or **0** (not prime)
 - ↳ parameter
 - Assume the usual **Ready**, **Done**, **Start**, **Reset**
- ❖ Algorithm:

copy of
input Num
so we can't
change it during
the algorithm

```
N = Num
if N < 3 do // handle special cases
    return (N == 2)
for F = 2 to N/2 do // factor to check
    if (N % F == 0) do
        return 0 // factor found, not a prime
    endif
endfor
return 1 // no factors found, is prime
```


isPrime: ASMD Chart

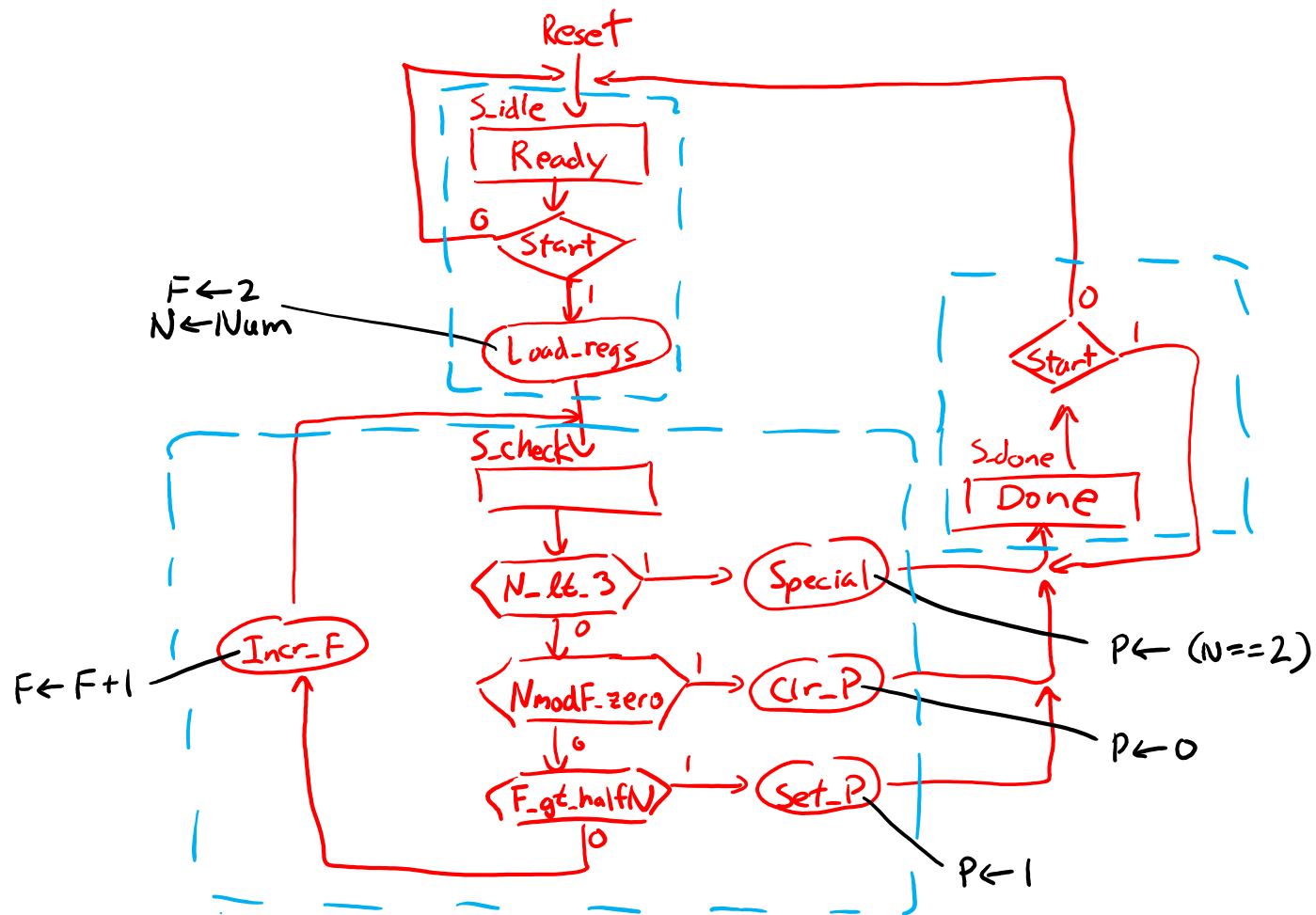

Alternatives:

- `Incr-F` could be Moore output on `S-check`
- `Special` could be extra decision box on `N=2` that uses `Clr_P` & `Set_P` on its outbound paths
- `N < 3` check could be done in `S_idle`

isPrime: Block Diagram

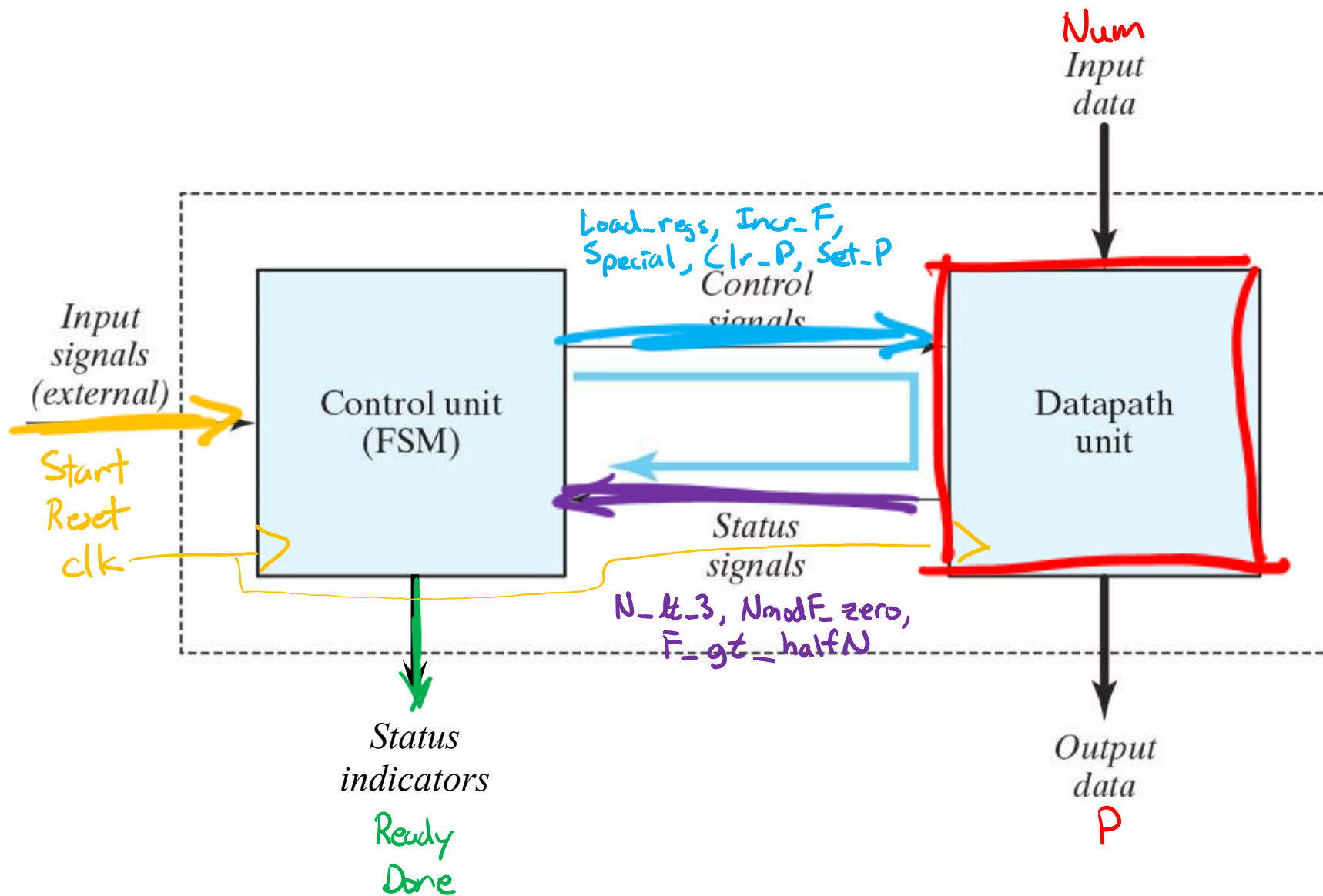

SHORT TECH

BREAK

Download/copy the code skeletons from [the course schedule](#)

isPrime Live Coding Demo

```
isPrime_control:  
    // port definitions  
    // define state names and variables  
    // controller logic w/synchronous reset  
    // next state logic  
    // output assignments  
  
isPrime_datapath:  
    // port definitions  
    // internal datapath signals and registers  
    // datapath logic  
    // output assignments  
  
isPrime:  
    // port definitions  
    // define status and control signals  
    // instantiate control and datapath
```

Basic Testbench Review

❖ How to start a testbench:

- 1) Create a `<name>_tb` module with no ports
- 2) Create variables that match the module's ports
- 3) Instantiate an instance of the module can call it `dut` or `uut`
- 4) If needed, create a simulated clock
- ★ 5) Create an `initial` block to define your test inputs

❖ Tools we know about:

- Timing controls: `#<time>;`, `@(posedge <signal>);`
- Loops: `integer i; for (i = 0; i < 2**3; i++)`
`repeat (2**4)`

Testing Your Algorithm

- ❖ Create a testbench for our isPrime module:

```
module isPrime_tb ();  
    // define parameters  
  
    // define module port connections  
  
    // instantiate module  
  
    // create simulated clock  
  
    ★ // define test inputs  
  
endmodule
```

Testing Your Algorithm

- ❖ Create a testbench for our isPrime module:
 - Single Num value (arbitrary wait):

```
// define test inputs

initial begin
  Num = 3; // test value
  Reset = 1; Start = 0; @(posedge clk); // reset system
  Reset = 0; @(posedge clk); // idle
  Start = 1; @(posedge clk); // start computation
  Start = 0; // make sure we don't get stuck in S_done

  repeat (2**4) // wait 16 clock cycles
    @(posedge clk);

  @(posedge clk); // extra cycle of output
  $stop();
end
```

Testing Your Algorithm

❖ Create a testbench for our isPrime module:

- Single Num value (check Ready):

Done also works, but detects 1 cycle earlier

```
// define test inputs

initial begin
    Num = 3;
    Reset = 1; Start = 0; @(posedge clk);
    Reset = 0;           @(posedge clk);
    Start = 1;           @(posedge clk);
    Start = 0;

    @(posedge Ready); // wait until module says it's ready

    @(posedge clk); // extra cycle of output
    $stop();
end
```

Testing Your Algorithm

- ❖ Create a testbench for our isPrime module:
 - All Num values:

```
// define test inputs
integer i;
initial begin
  Reset = 1; Start = 0; @(posedge clk);
  Reset = 0;           @(posedge clk);

  for (i = 0; i < 2**W; i++) begin
    Start = 1; Num = i; @(posedge clk);
    Start = 0;         @(posedge Ready);
  end

  @(posedge clk); // extra cycle of output
  $stop();
end
```

// reset system
// idle

// loop through all Num's
// set Num & start computation
// wait until Ready again

Testing Your Algorithm: \$display

- ❖ Triggers once when encountered, prints the given format string and adds a new line:

```
// define test inputs
integer i;
initial begin
  Reset = 1; Start = 0; @(posedge clk);
  Reset = 0;          @(posedge clk);
  for (i = 0; i < 2**W; i++) begin
    Start = 1; Num = i; @(posedge clk);
    Start = 0;          @(posedge Ready);

    { $display("T = %4t, isPrime(%2d) = %s",
              $time, Num, P ? "Yes" : "No ");
      }
  end
  @(posedge clk); // extra cycle of output
  $stop();
end
```

current simulation time

```
Transcript
VSIM 4> run -all
# T = 90, isPrime( 0) = No
# T = 150, isPrime( 1) = No
# T = 210, isPrime( 2) = Yes
# T = 270, isPrime( 3) = Yes
# T = 330, isPrime( 4) = No
# T = 410, isPrime( 5) = Yes
# T = 470, isPrime( 6) = No
# T = 570, isPrime( 7) = Yes
# T = 630, isPrime( 8) = No
# T = 710, isPrime( 9) = No
# T = 770, isPrime(10) = No
# T = 910, isPrime(11) = Yes
# T = 970, isPrime(12) = No
# T = 1130, isPrime(13) = Yes
# T = 1190, isPrime(14) = No
# T = 1270, isPrime(15) = No
```

SHORT TECH


BREAK

Lecture Outline (2/2)

- ❖ Algorithm → Hardware Wrap-up
- ❖ **Timing Constraints Review**

Why Are Timing Constraints Important?

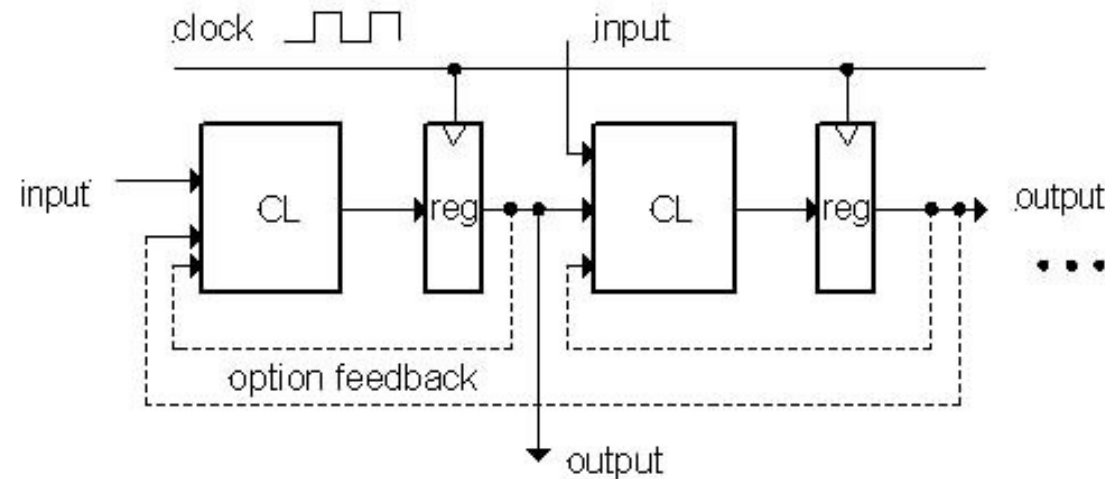
- ❖ Our model of synchronous digital systems relies on timing behavior of the clock and logic stages
 - Combinational logic blocks separated by registers



- Violations can cause incorrect behavior or can cause produced semiconductor circuits to fail!
- Timing considerations can limit how fast our system/clock can run


Review: Sequential Timing Constraints

 - ❖ **Setup Time (t_s or t_{su}):** How long the input must be stable *before* the CLK trigger for proper input read
- ❖ **Hold Time (t_h):** How long the input must be stable *after* the CLK trigger for proper input read
- ❖ **"CLK-to-Q" Delay (t_{c2Q} or t_{co}):** How long it takes the output to change, measured from the CLK trigger



Where Do Timing Terms Come From?

- ❖ Edge-triggered D flip-flop:

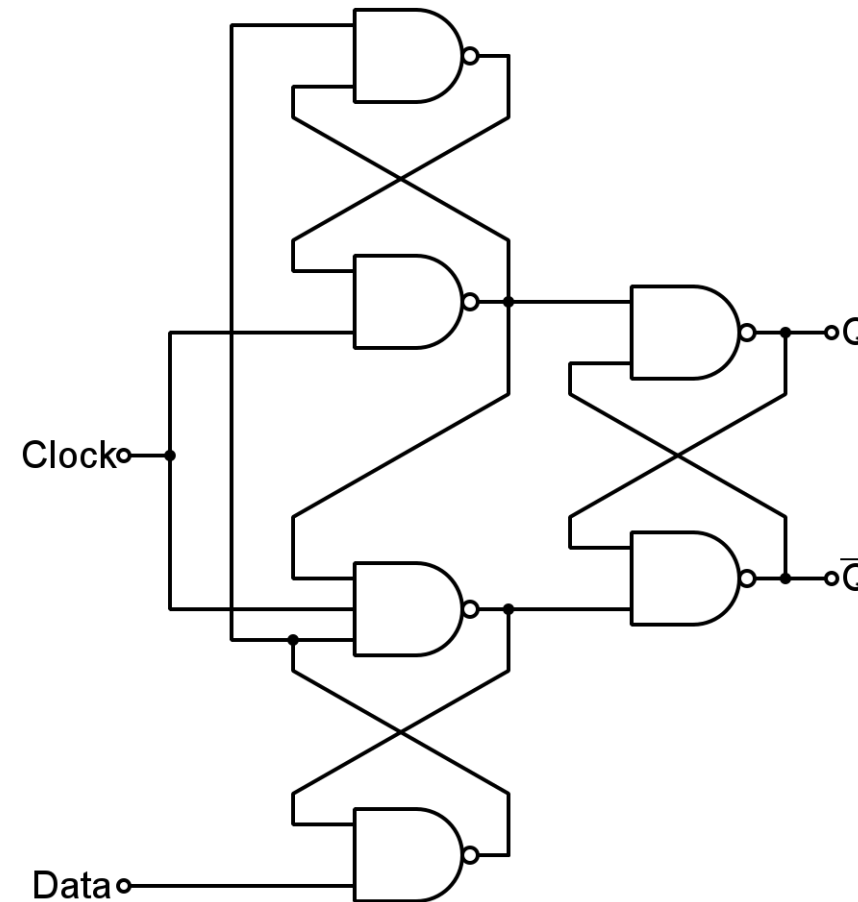


By Nolanjshettle at English Wikipedia, CC BY-SA 3.0,
<https://commons.wikimedia.org/w/index.php?curid=40852354>

When Can the Input Change?

- ❖ When a register input changes shouldn't violate hold time (t_h) or setup time (t_{su}) constraints within a clock period (T)
- ❖ Let $t_{input,i}$ be the time it takes for the input of a register to change for the i -th time in a single clock cycle, measured from the CLK trigger:
 - Then we need $t_h \stackrel{\textcircled{1}}{\leq} t_{input,i} \stackrel{\textcircled{2}}{\leq} T - t_{su}$ for all i
 - Two separate constraints!

$$\textcircled{1} \quad t_{input,i} \geq t_h$$
 
$$\textcircled{2} \quad t_{input,n} \leq T - t_{su}$$



Timing Constraint Considerations

- ❖ Use *worst-case analysis*
 - Asynchronous inputs are *really* problematic
 - Use the **critical path** – the longest delay between *any* two registers in a circuit – for setup time constraint
 - Use the shortest path for the hold time constraint
- ❖ A timing violation could be caused by a signal change from the *previous* clock cycle
 - *i.e.*, a really late input change could violate the hold time constraint in the *next* clock cycle
- ❖ Setup time constraint helps determine feasibility of clock frequency:
max freq = $1/(\text{min period})$

Timing Constraint Worked Example

- ❖ $t_{su} = 12 \text{ ns}$, $t_h = 18 \text{ ns}$, $t_{CO} = 8 \text{ ns}$,
 $t_{AND} = 25 \text{ ns}$, and $t_{NOR} = 20 \text{ ns}$

- If In changes t_{CO} after each clock trigger ²⁵/₄₅ what is the **minimum clock period** we can use?

critical path(s) shown in red.

$$t_{CO} + t_{AND} + t_{NOR} \leq T - t_{su}$$

$$8 + 25 + 20 \leq T - 12 \quad \boxed{T \geq 65 \text{ ns}}$$

- If we use the minimum clock period, when within a clock period $[0, T]$ can In change without causing a timing violation?

In changes propagate to register inputs along 2 paths (— and —).

$$t_h \leq t_{in} + t_{AND} \leq T - t_{su} \Rightarrow -7 \text{ ns} \leq t_{in} \leq 28 \text{ ns}$$

$$t_h \leq t_{in} + t_{AND} + t_{NOR} \leq T - t_{su} \Rightarrow -27 \text{ ns} \leq t_{in} \leq 8 \text{ ns}$$

intersect $\Rightarrow -7 \text{ ns} \leq t_{in} \leq 8 \text{ ns}$

$[0, 8) \text{ ns}$
 or
 $(58, 65] \text{ ns}$

