

# DESIGN OF DIGITAL CIRCUITS AND SYSTEMS

## Static Timing Analysis

**Instructor:** Justin Hsia

**Teaching Assistants:**

Colton Carroll

Hemil Patel

Rasya Fawwaz

Grace Zhou

Quinlyn Donohue


Rose Maresh

# Relevant Course Information

- ❖ Lab 4 due Friday (5/8)
- ❖ Quiz 3 is this Thursday at **11:50** am (30 min)
  - ASM and ASMD charts
- ❖ Homework 5 (5/15) and Lab 5 (5/22) will be released on Thursday
  - Lab 5 is the longest “regular” lab, mostly because of debugging – careful with number representation
- ❖ Rest of course material will NOT show up in labs
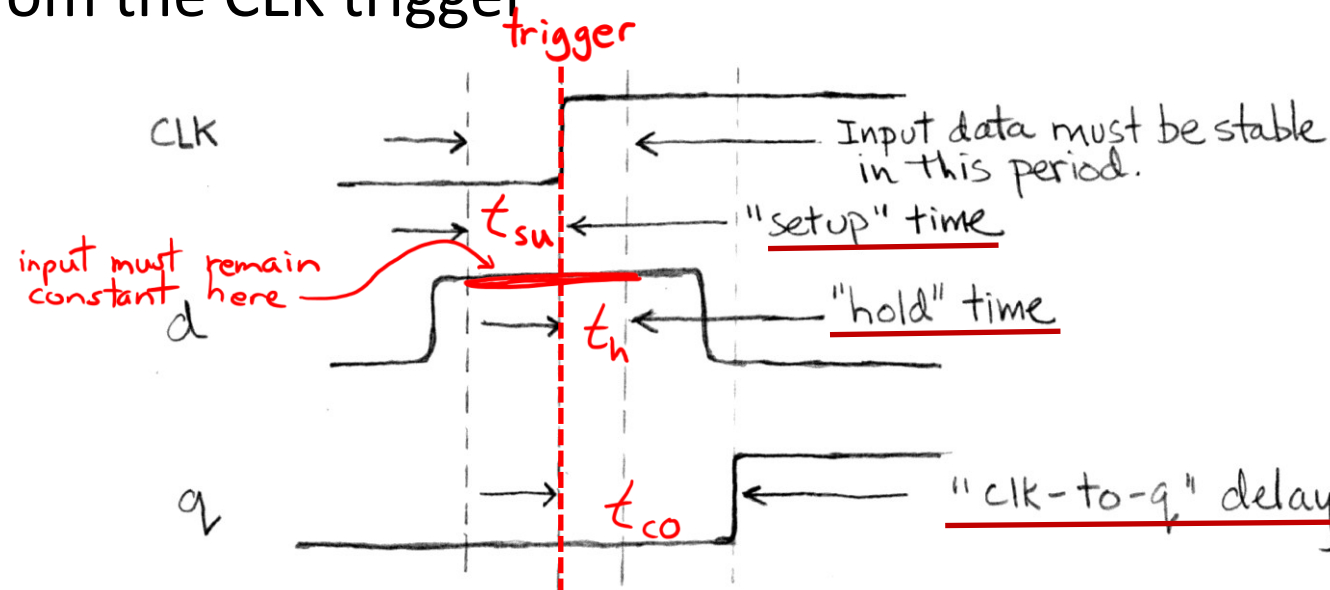
# Review: Sequential Timing Constraints

- ❖ **Setup Time ( $t_s$  or  $t_{su}$ ):** How long the input must be stable *before* the CLK trigger for proper input read
- ❖ **Hold Time ( $t_h$ ):** How long the input must be stable *after* the CLK trigger for proper input read
- ❖ **"CLK-to-Q" Delay ( $t_{c2Q}$  or  $t_{co}$ ):** How long it takes the output to change, measured from the CLK trigger




# When Can the Input Change?

- ❖ When a register input changes shouldn't violate hold time ( $t_h$ ) or setup time ( $t_{su}$ ) constraints within a clock period ( $T$ )
- ❖ Let  $t_{input,i}$  be the time it takes for the input of a register to change for the  $i$ -th time in a single clock cycle, measured from the CLK trigger:
  - Then we need  $t_h \stackrel{\textcircled{1}}{\leq} t_{input,i} \stackrel{\textcircled{2}}{\leq} T - t_{su}$  for all  $i$
  - Two separate constraints!

$$\textcircled{1} \quad t_{input,1} \geq t_h$$
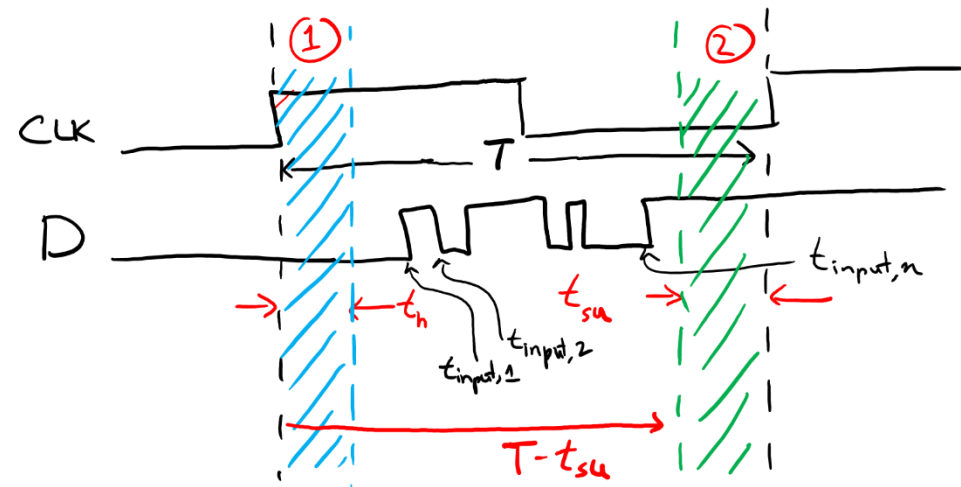
$$\textcircled{2} \quad t_{input,n} \leq T - t_{su}$$




# Timing Constraint Questions

- 1) What are you solving for? Which constraint/inequality is relevant?
  - $t_h$  → hold time constraint
  - $t_{su}$  or  $T$  → setup time constraint
  - Combinational logic delay → “max” means setup time constraint, “min” means hold time constraint
- 2) Find the most relevant pathway to a register input
  - Hold time constraint → shortest pathway
  - Setup time constraint → longest pathway
- 3) Solve the inequality for chosen path using the given constants
 
# Practice Timing Constraint Question

- Let  $T = 300$  ps,  
 $t_{su} = 80$  ps,  $t_h = 50$  ps,  
 $t_{co} = 100$  ps.




- If In changes exactly on clock triggers, what are the limits on the XOR gate delay that ensure proper behavior?

$$0 + t_{xor} \geq t_h$$

$$t_{co} + t_{xor} \leq T - t_{su}$$

$$t_{XOR} \in (50, 120) \text{ ps}$$

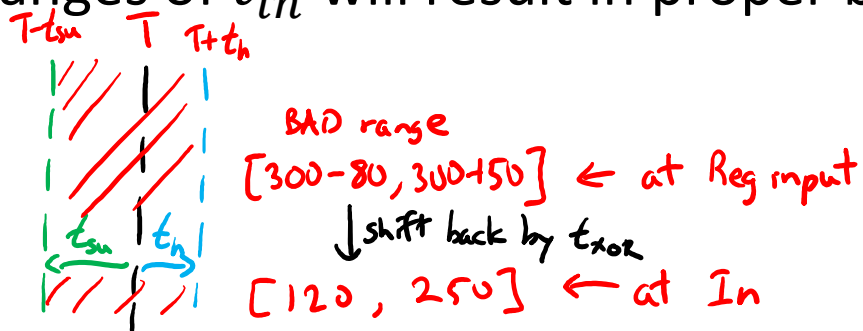- Now let  $t_{XOR} = 100$  ps and In change a fixed  $t_{in}$  after each clock trigger, what ranges of  $t_{in}$  will result in proper behavior? Answer within a single clock cycle:




$$t_{in} \in [0, 120) \cup (250, 300] \text{ ps}$$

 
# What Affects Circuit Timing?

❖ A more realistic picture:

- **Logic depth of circuit pathways** } *part of design process*
- **Length, resistance, and capacitance of wire** } *baseline physical properties*
- **Size of the transistors**
- **Operating conditions: Voltage & Temperature** } *fluctuations based on conditions*




# Review: FPGA-Based Design Flow

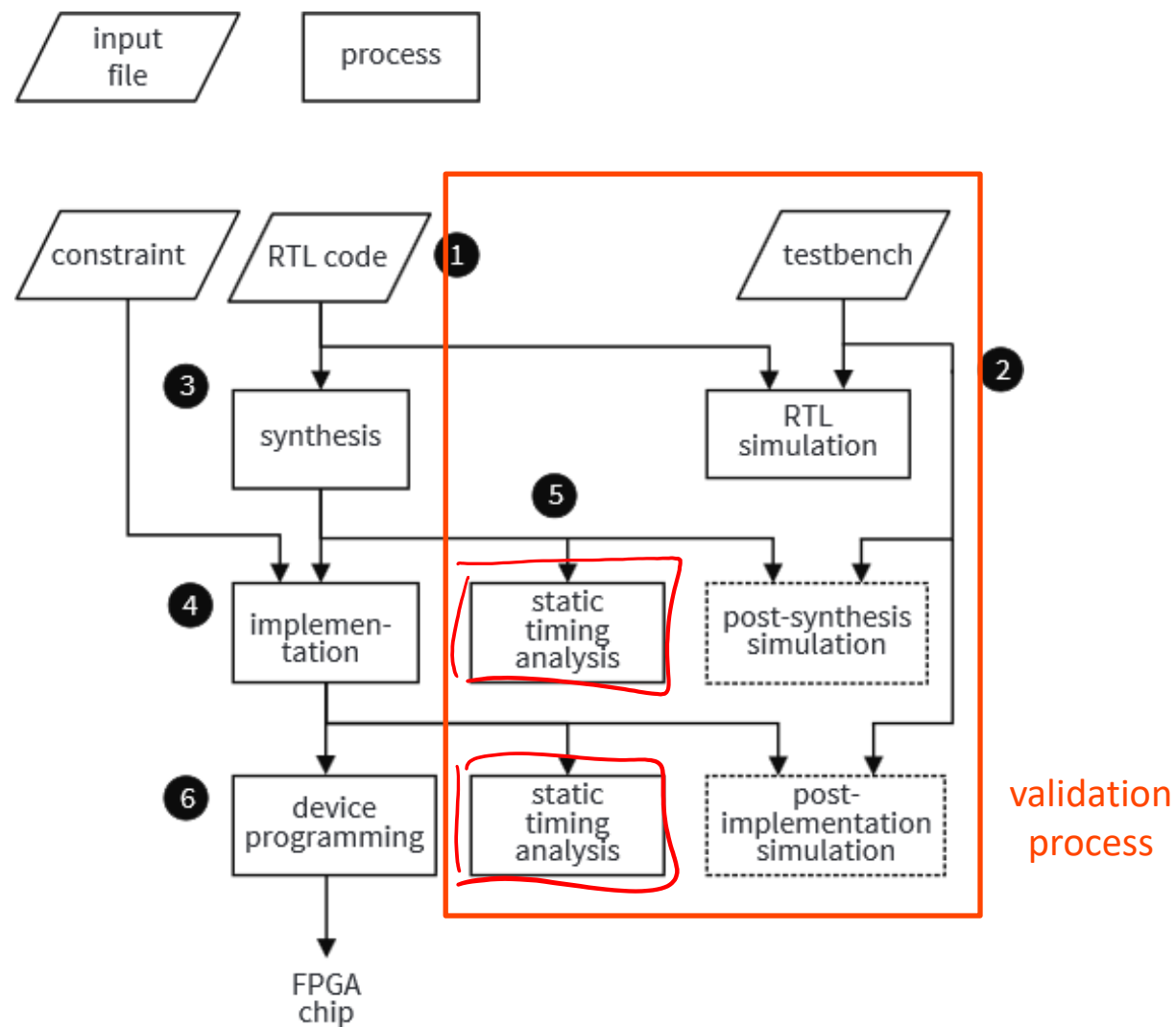

Source: Figure 2.3 from "FPGA Prototyping" by P. Chu

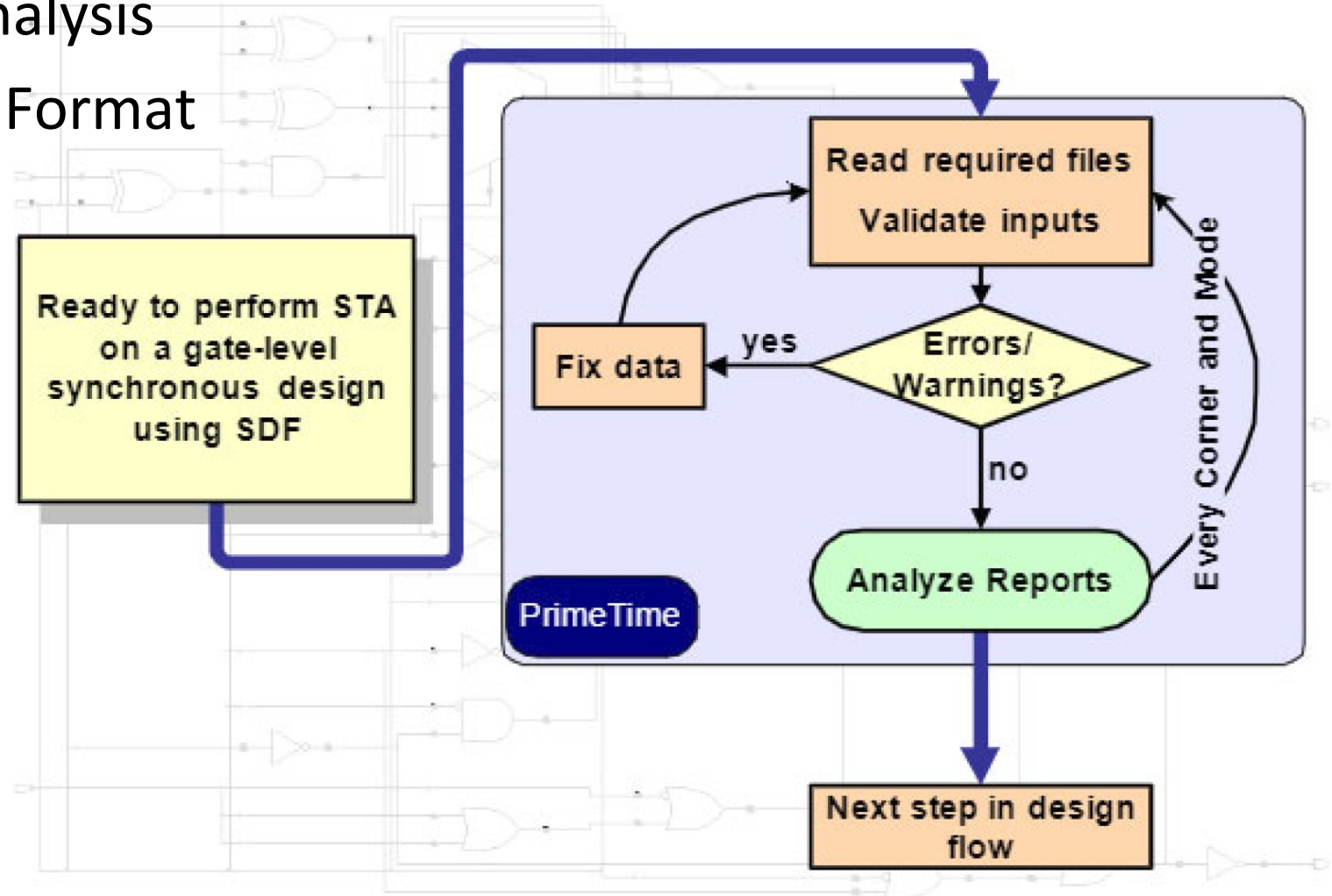
# Static Timing Analysis Flow

- ❖ STA = Static Timing Analysis
- ❖ SDF = Standard Delay Format



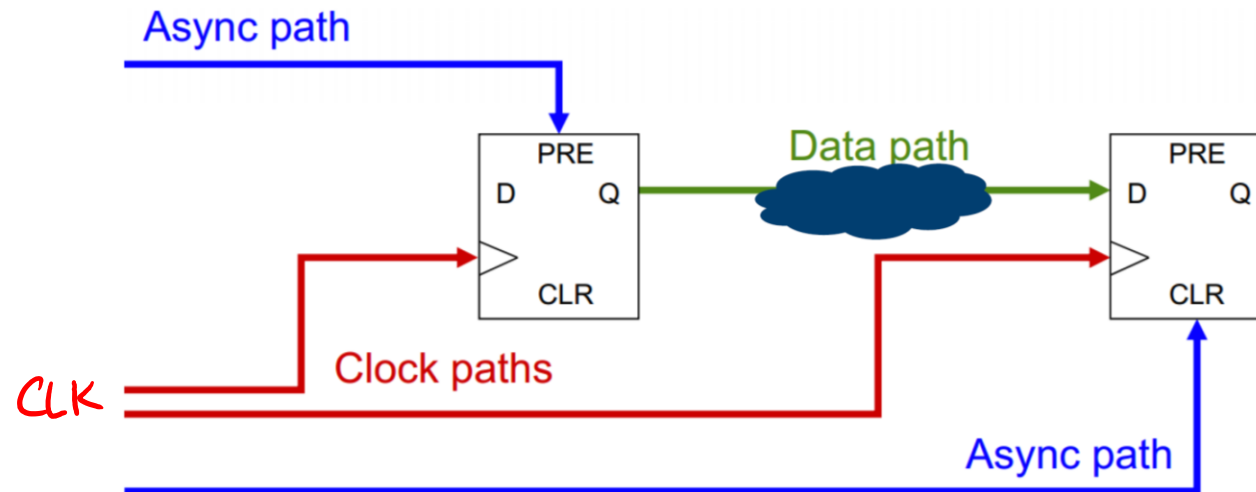
# Circuit Path Categorization

- ❖ **Data paths** are between inputs, sequential elements, and outputs
- ❖ **Clock paths** are from device ports or internally-generated clocks to the clock pins of sequential elements
- ❖ **Asynchronous paths** are between inputs and asynchronous set and clear pins of sequential elements



 
# Data Path Validity

- ❖ A data signal is considered **valid** when it has finished computing and is stable
  - Note that this remains true until the next round of computation begins, which can cross clock cycle boundaries
- ❖ For proper behavior (*i.e.*, correct reads), the input to a register must remain valid throughout the setup and hold time constraints


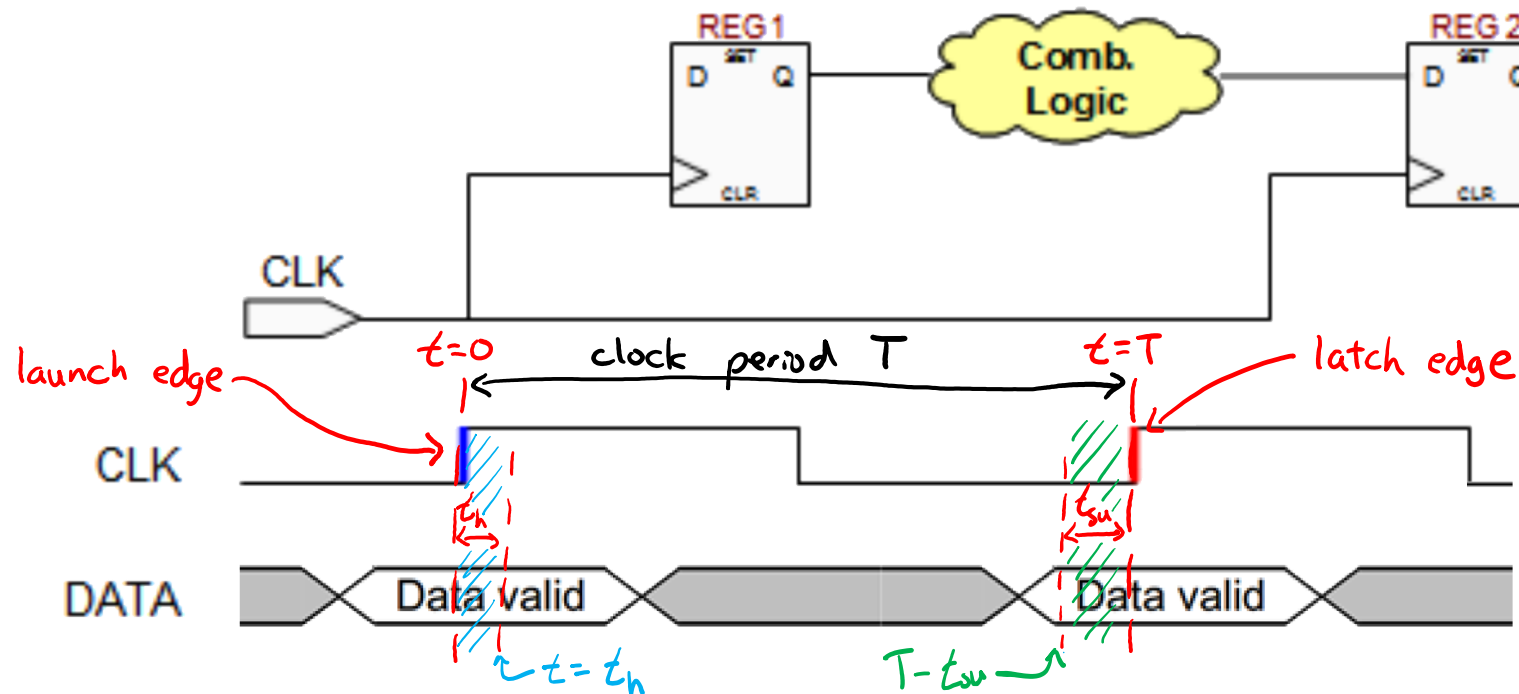
# Clock Edges

- ❖ Looking at a single clock cycle
  - **Launch Edge**: the clock edge that activates/launches the **source register**
  - **Latch Edge**: the clock edge that latches the data into the **destination register**




# Timing Delays and Points of Interest: Definitions

- ❖ **Clock Network Delay** ( $t_{clk}$ )
  - How long it takes for changes in the clock signal to arrive at the register – the cause of *clock skew*
- ❖ **Clock-to-Q or Clock-to-out Delay** ( $t_{C2Q}$ ,  $t_{CQ}$ , or  $t_{CO}$ )
  - How long it takes the output to change, measured from the register's *received* clock edge – a property of the FF/register
- ❖ **Data Arrival Time** (DAT)
  - The time at which the destination register's input is settled
- ❖ **Clock Arrival Time** (CAT)
  - The time at which a clock edge arrives at the destination register

# Timing Delays and Points of Interest: Formulas

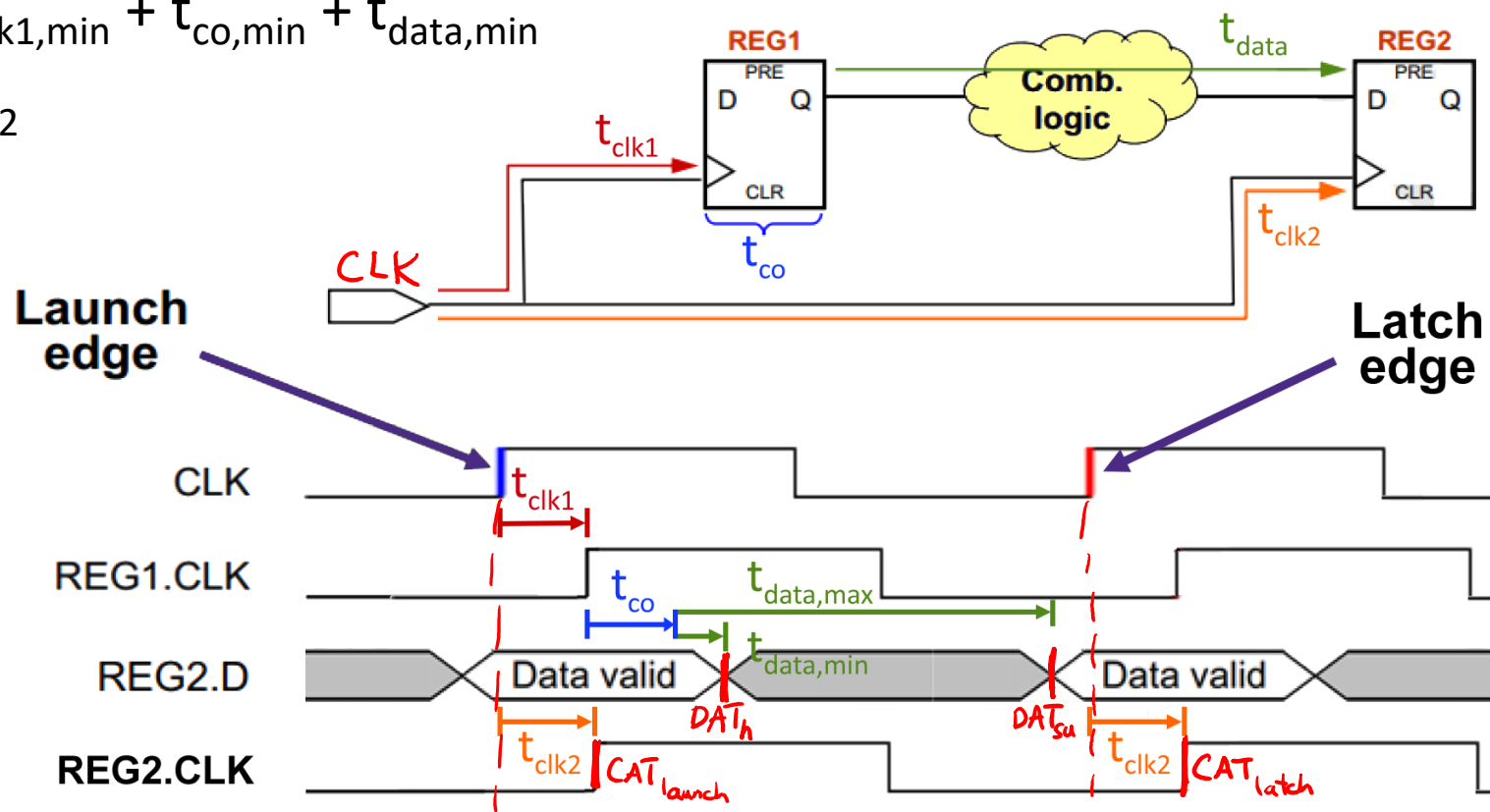
## ❖ Data Arrival Times (DAT) and Clock Arrival Times (CAT)

- $DAT_{su} = \text{launch edge} + t_{clk1,max} + t_{co,max} + t_{data,max}$
- $DAT_h = \text{launch edge} + t_{clk1,min} + t_{co,min} + t_{data,min}$
- $CAT_{latch/launch} = \text{edge} + t_{clk2}$



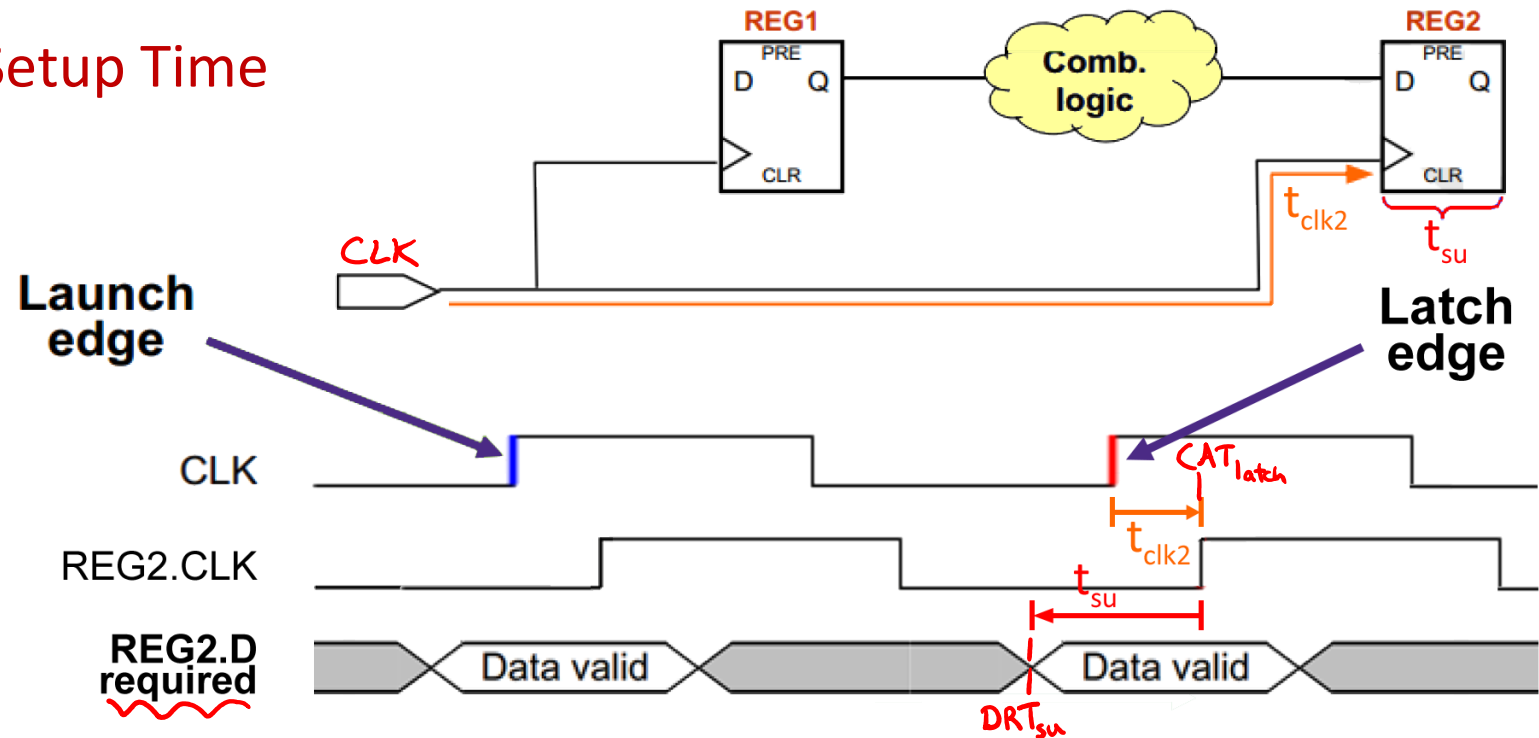
# Data Required Time (DRT): Setup

- ❖ Data Required Time for Setup ( $DRT_{su}$ )
  - The minimum time required *before* the *latch* edge for data to get latched into the destination register
  - Clock Arrival Time<sub>latch</sub> – Setup Time


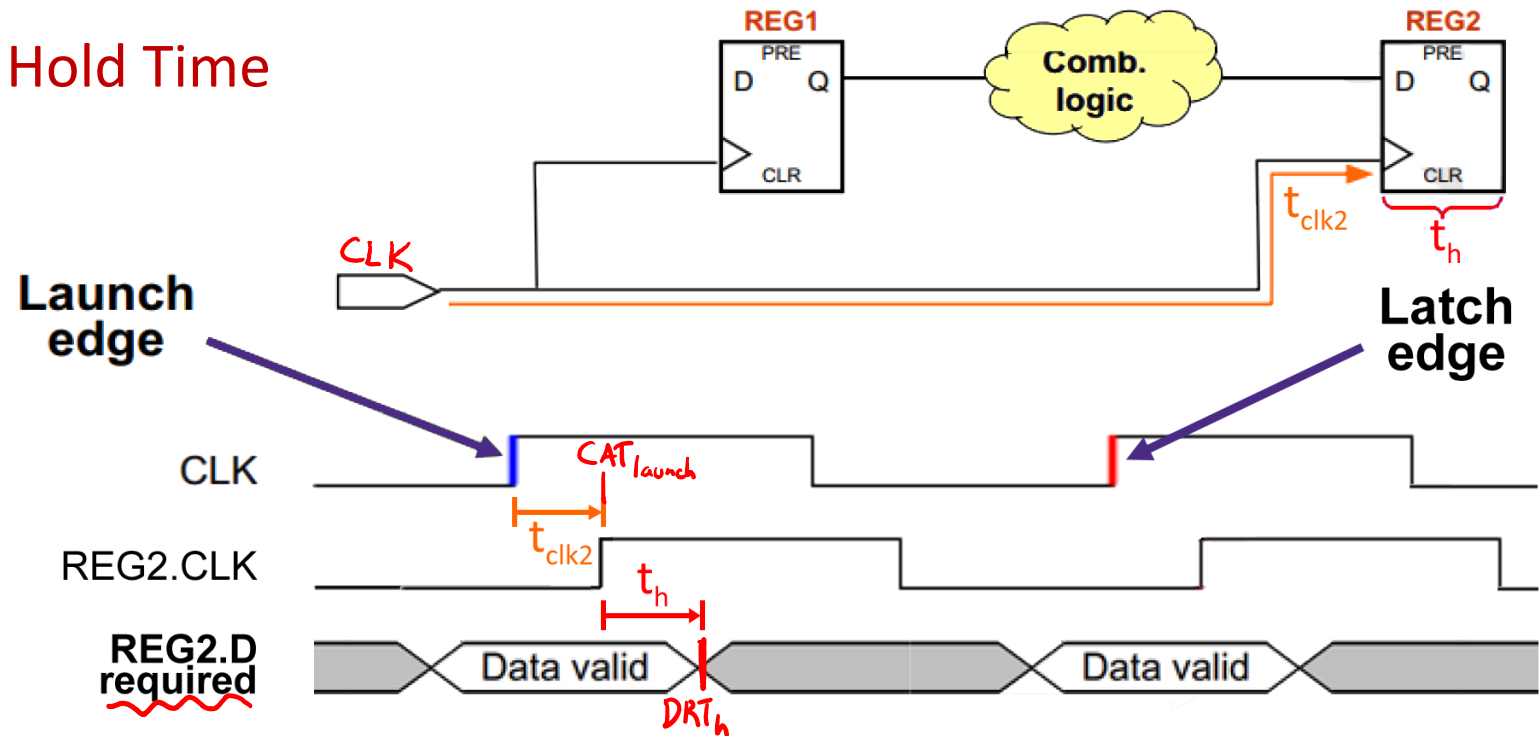
# Data Required Time (DRT): Hold


- ❖ Data Required Time for Hold ( $DRT_h$ )
  - The minimum time required *after* the *launch* edge for the data to remain valid for successful latching
  - Clock Arrival Time<sub>launch</sub> + Hold Time


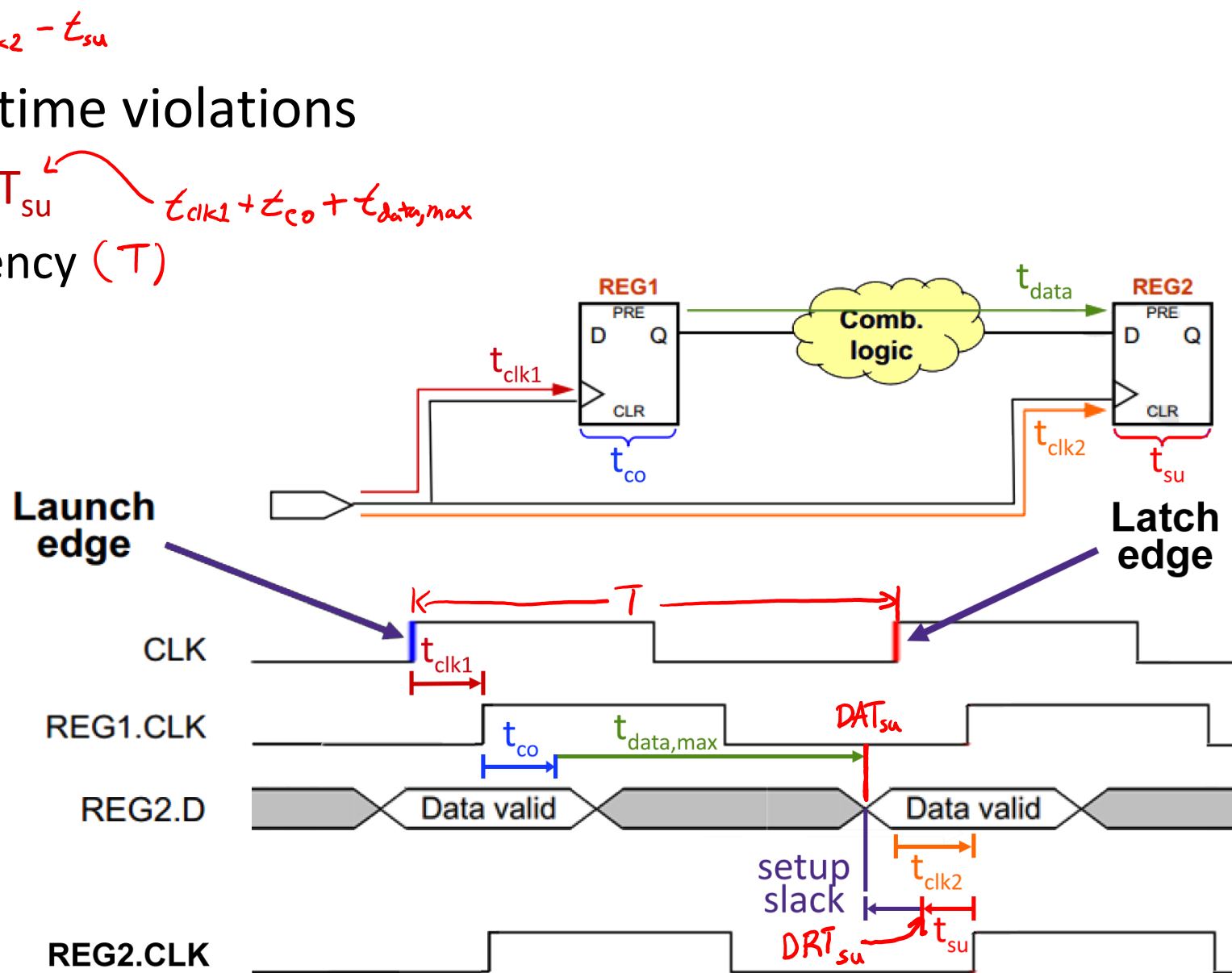
# Setup Slack


❖ Wiggle room for setup time violations

- Setup slack =  $DRT_{su} - DAT_{su}$
- Depends on clock frequency ( $T$ )


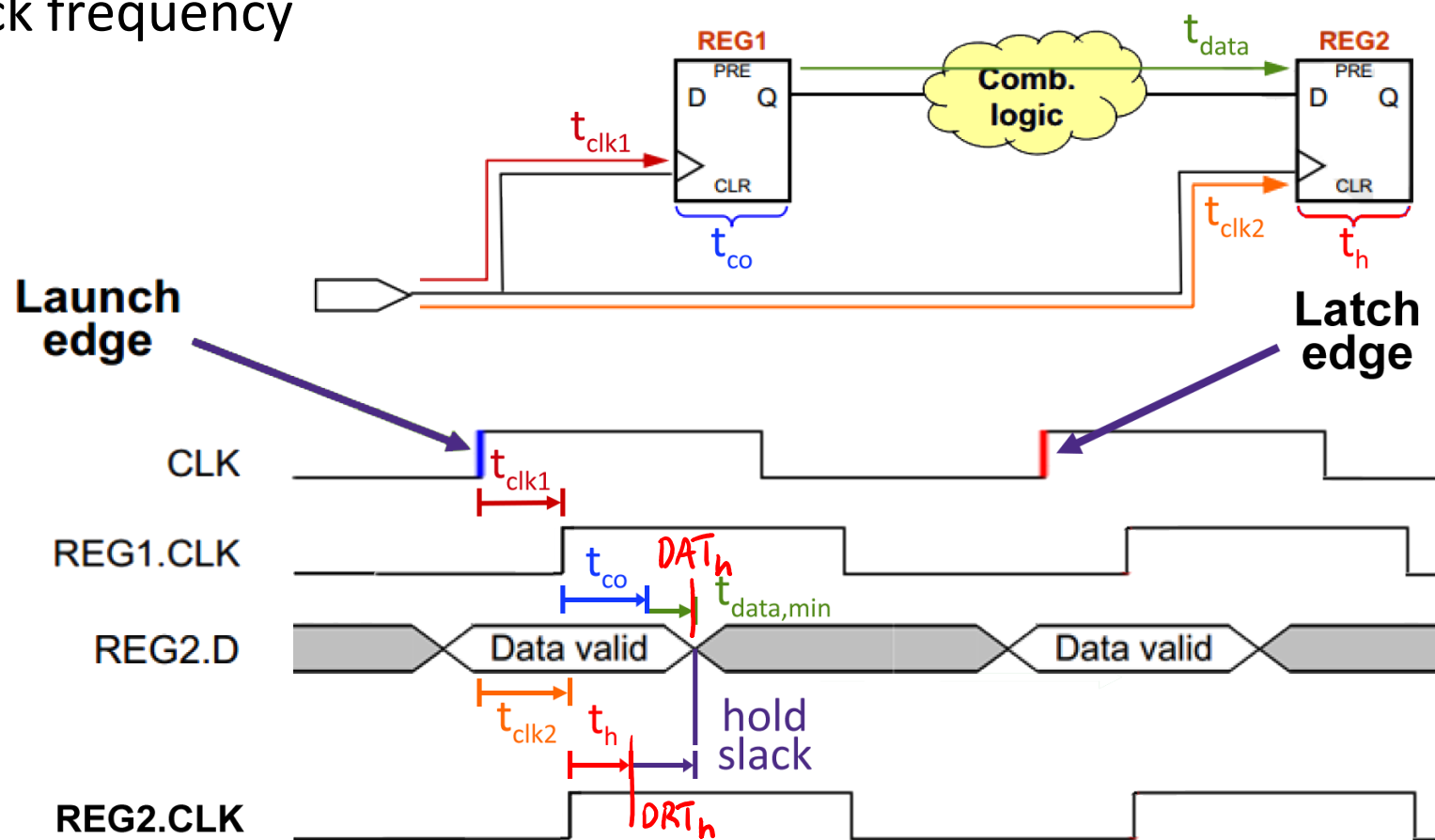
# Hold Slack


- ❖ Wiggle room for hold time violations
  - Hold slack =  $DAT_h - DRT_h$ 
    - (Handwritten:  $t_{clk1} + t_{co} + t_{data,min}$  points to  $DAT_h$ )*
    - (Handwritten:  $t_{clk2} + t_h$  points to  $DRT_h$ )*
  - Does not depend on clock frequency



TECHNOLOGY

BREAK

# Setup Slack Example

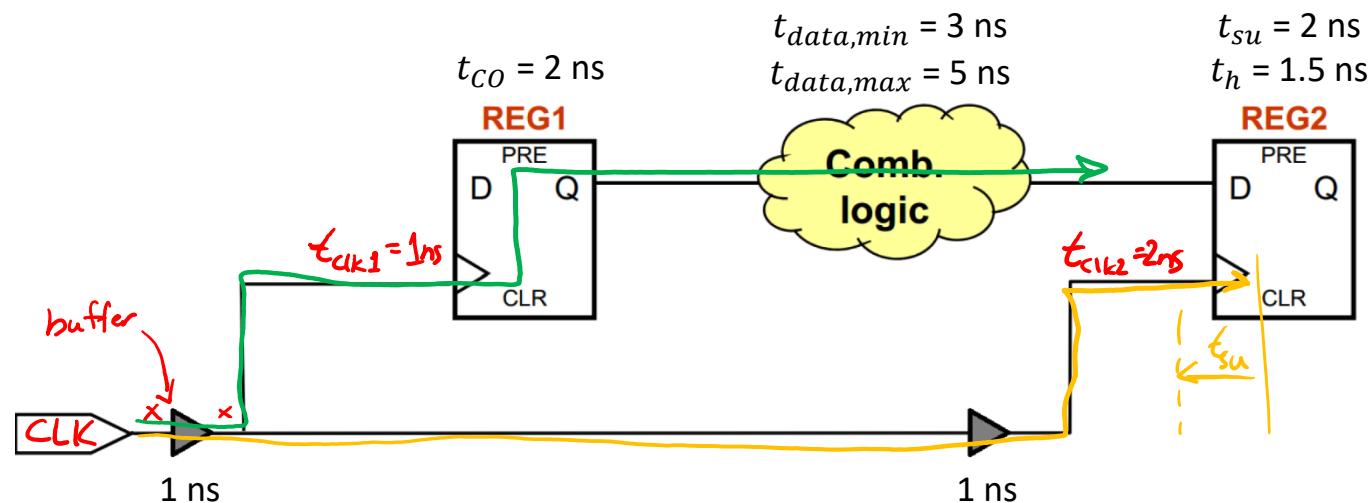

❖ Assume 100 MHz clock; clock period  $T = 10 \text{ ns}$

❖ Setup slack =  $DRT_{su} - DAT_{su}$


$$= \overset{\text{latch edge}}{\text{min clock path}} - \text{max data path}$$

$$= (T + t_{clk,2,min} - t_{su,max}) - (t_{clk,1,max} + t_{co,max} + t_{data,max})$$

$$= (10 + 2 - 2) - (1 + 2 + 5)$$

**setup slack = 2 ns**  $> 0$ , so no timing violation

# Hold Slack Example


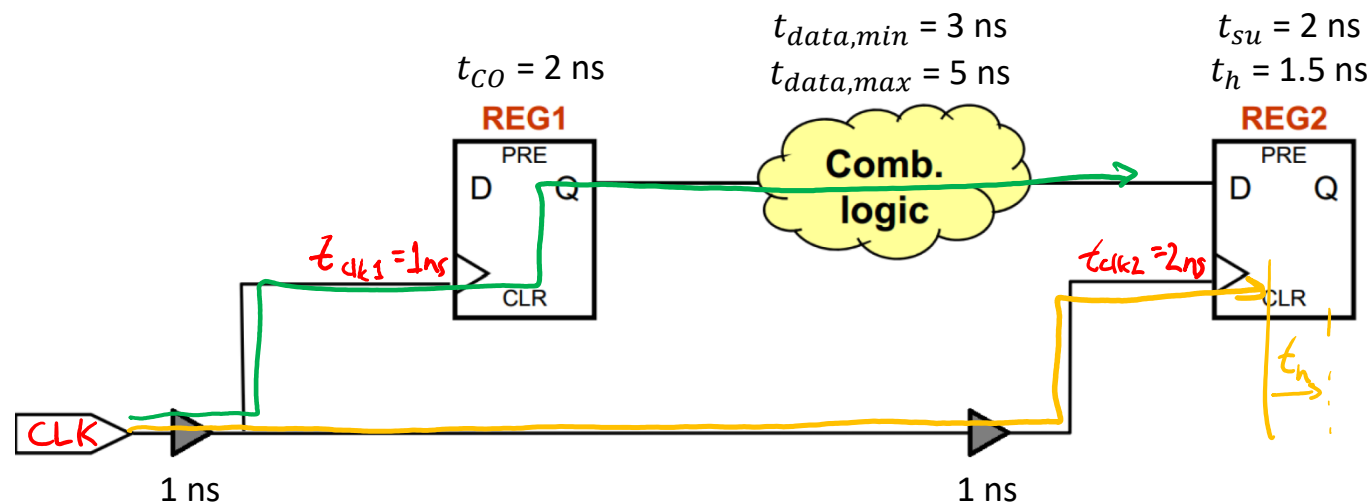


❖ Assume 100 MHz clock; clock period  $T = 10 \text{ ns}$

❖ Hold slack =  $DAT_h - DRT_h$

$= \text{min data path} - \text{max clock path}$   
 $(t_{clk1,min} + t_{CO,min} + t_{data,min}) - (0 + t_{clk2,max} + t_{h,max})$   
 $(1 + 2 + 3) - (2 + 1.5)$   
hold slack = 2.5 ns  $> 0$ , so no timing violation

# Slack Exercise (1/2)

 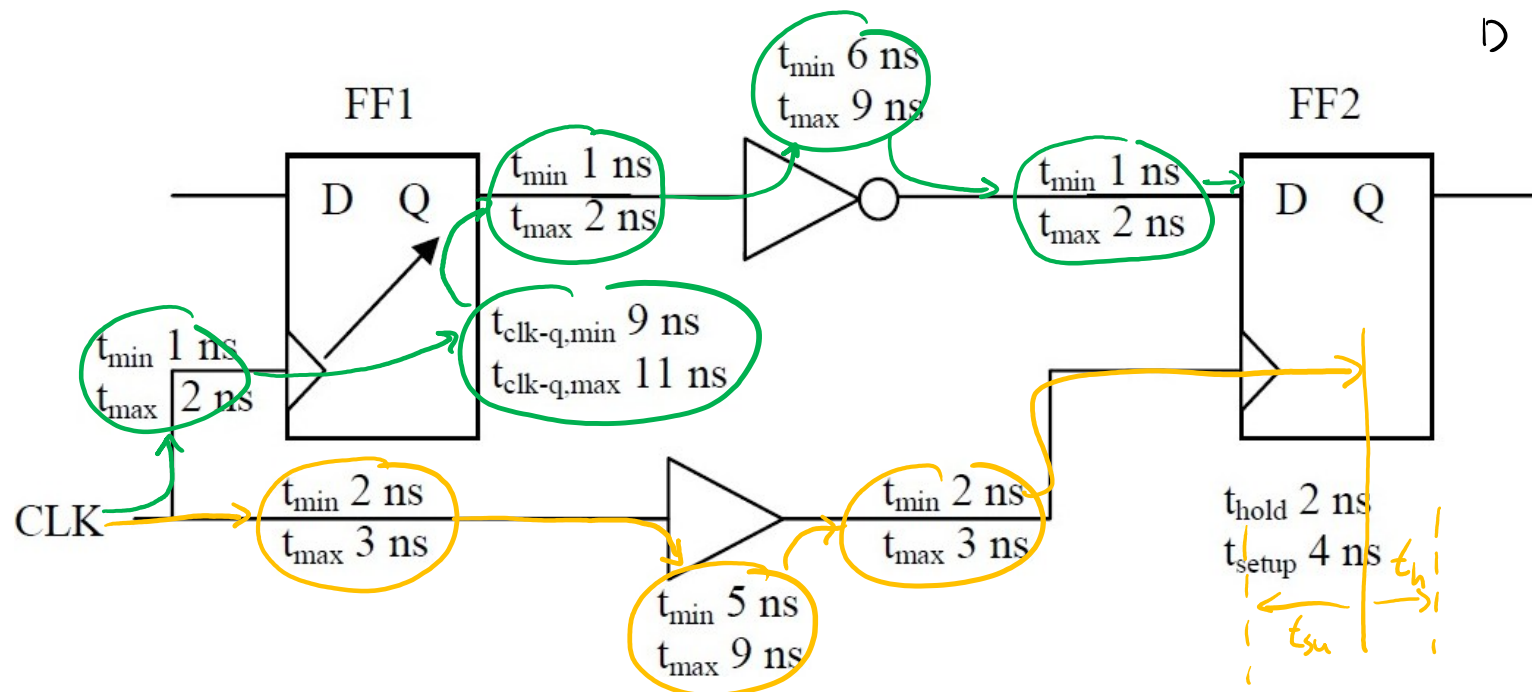

❖ Calculate the setup and hold slacks:


- Assume 50 MHz clock; clock period  $T = 20 \text{ ns}$
- setup slack =  $\text{min clock path} - \text{max data path}$   
 $(20 + 2 + 5 + 2 - 4) = 25 \quad (2 + 11 + 2 + 9 + 2) = 26$
- hold slack =  $\text{min data path} - \text{max clock path}$   
 $(1 + 9 + 1 + 6 + 1) = 18 \quad (3 + 9 + 3 + 2) = 17$

timing violation!

$$= \boxed{-1 \text{ ns}}$$

$$= \boxed{1 \text{ ns}}$$

# Slack Exercise (2/2)

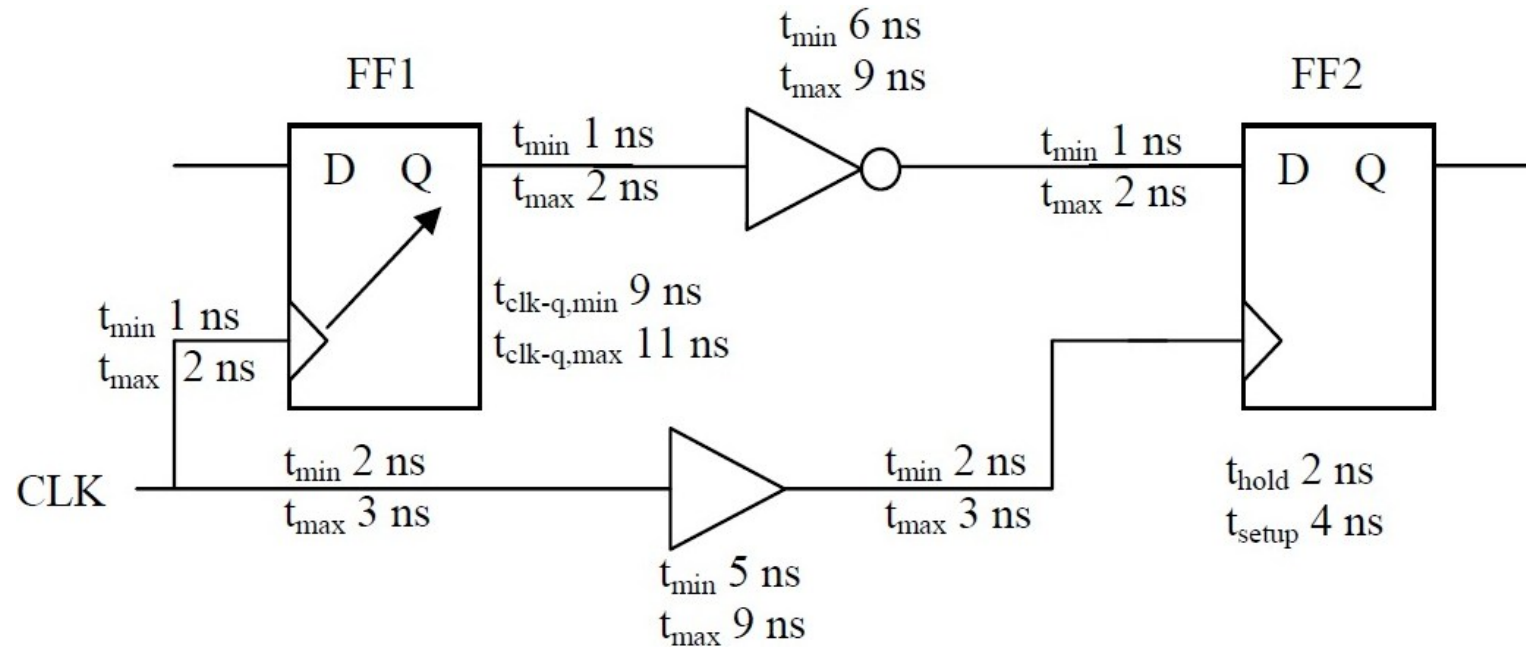

- ❖ What is the fastest clock we can use with this circuit?

need setup slack  $\geq 0$  by changing clock speed/period (T)  
 so need  $T \geq 21 \text{ ns}$ , which means  $f \leq 47.6 \text{ MHz}$


# Synopsys Design Constraints (SDC)

- ❖ Synopsys Design Constraints describe timing constraints and exceptions
  - Quartus uses `.sdc` files to define clocks, I/O constraints, and other information that the fitter needs to make the best decisions
  - You can make and edit these using the TimeQuestGUI or by editing the `.sdc` file in a text editor (see Homework 5)

# I/O Constraints: Input Delays
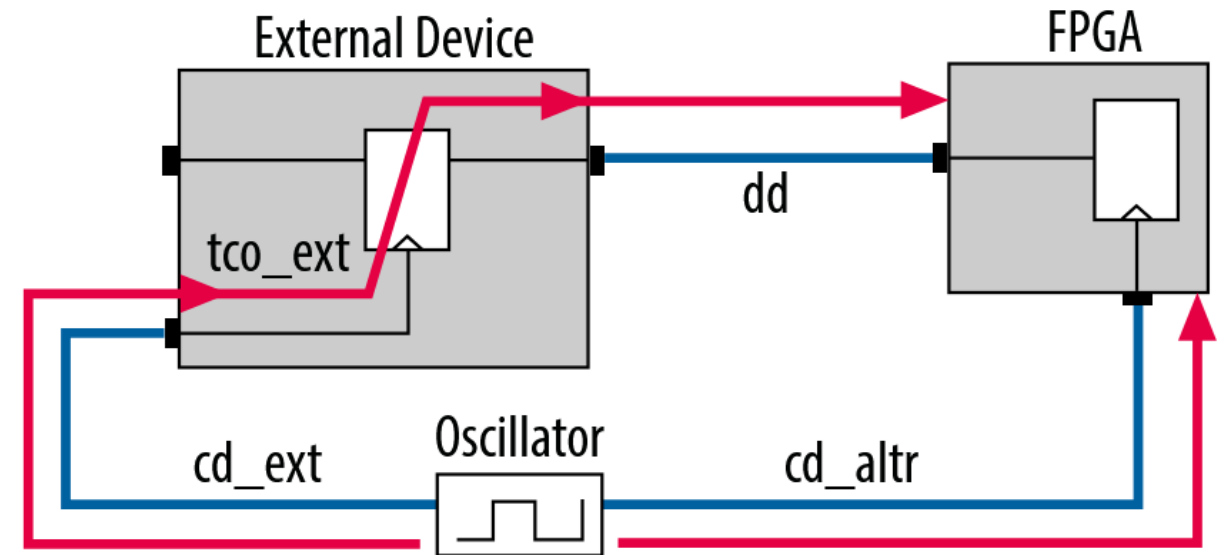
## ❖ set\_input\_delay

- Command to specify external delays feeding into the FPGA's input ports
- <https://docs.altera.com/r/docs/683243/25.3/quartus-prime-pro-edition-user-guide-timing-analyzer/input-constraints-set-input-delay>




## ❖ Applied to this setup: *clock skew*

- $\text{input delay}_{\min} = (\text{cd\_ext}_{\min} - \text{cd\_altr}_{\max}) + \text{tco\_ext}_{\min} + \text{dd}_{\min}$
- $\text{input delay}_{\max} = (\text{cd\_ext}_{\max} - \text{cd\_altr}_{\min}) + \text{tco\_ext}_{\max} + \text{dd}_{\max}$ 
  - “cd” = clock delay, “dd” = data delay, “altr” = Altera FPGA

# I/O Constraints: Output Delays
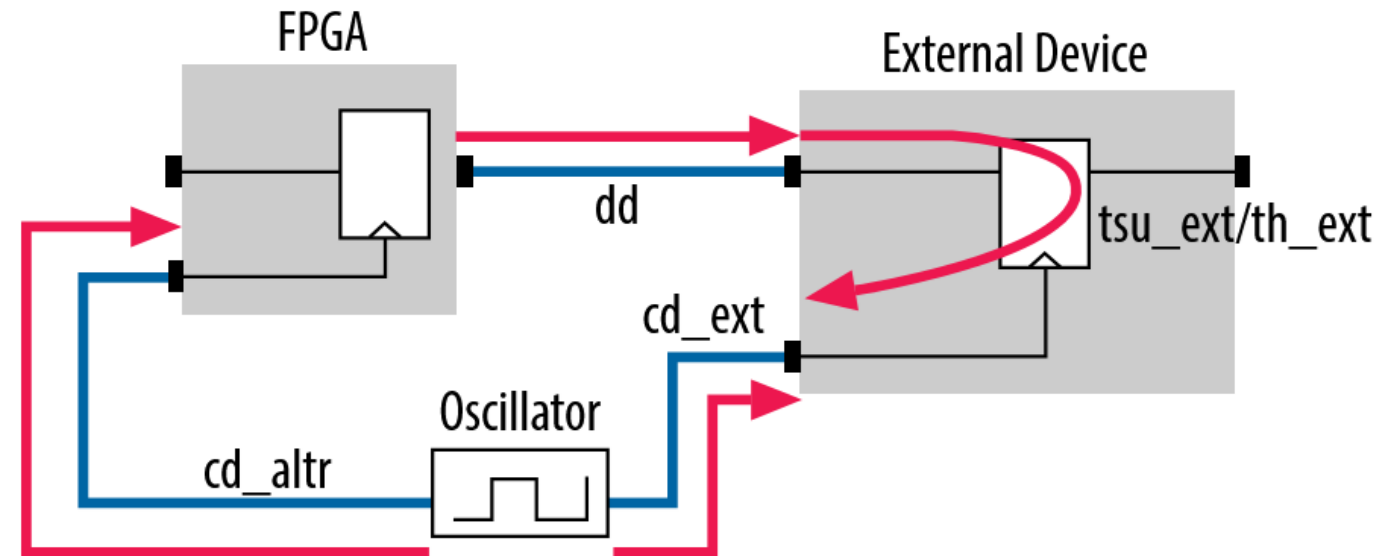
## ❖ set\_output\_delay

- Command to specify external delays leaving the FPGA's output ports
- <https://docs.altera.com/r/docs/683243/25.3/quartus-prime-pro-edition-user-guide-timing-analyzer/output-constraints-set-output-delay>



## ❖ Applied to this setup: *clock skew*

- $\text{output delay}_{\min} = (\text{cd\_altr}_{\min} - \text{cd\_ext}_{\max}) + \text{dd}_{\min} - \text{th\_ext}_{\max}$
- $\text{output delay}_{\max} = (\text{cd\_altr}_{\max} - \text{cd\_ext}_{\min}) + \text{dd}_{\max} + \text{tsu\_ext}_{\max}$ 
  - “cd” = clock delay, “dd” = data delay, “altr” = Altera FPGA


# I/O Constraints: Datasheets

❖ Check the datasheet!

READ/WRITE CYCLE SWITCHING CHARACTERISTICS (Over Operating Range)						
Symbol	Parameter	-166		-133		Unit
		Min.	Max.	Min.	Max.	
f <sub>MAX</sub> <sup>(3)</sup>	Clock Frequency	—	166	—	133	MHz
t <sub>CC</sub> <sup>(3)</sup>	Cycle Time	6	—	7.5	—	ns
t <sub>KH</sub>	Clock High Time	2.4	—	2.8	—	ns
t <sub>KL</sub> <sup>(3)</sup>	Clock Low Time	2.4	—	2.8	—	ns
t <sub>CA</sub> <sup>(3)</sup>	Clock Access Time	—	3.5	—	4	ns
t <sub>COX</sub> <sup>(1)</sup>	Clock High to Output Invalid	3	—	3	—	ns
t <sub>COLZ</sub> <sup>(1,2)</sup>	Clock High to Output Low-Z	0	—	0	—	ns
t <sub>COHZ</sub> <sup>(1,2)</sup>	Clock High to Output High-Z	1.5	3.5	1.5	3.5	ns
t <sub>OEQ</sub> <sup>(3)</sup>	Output Enable to Output Valid	—	3.5	—	3.8	ns
t <sub>EOX</sub> <sup>(1)</sup>	Output Disable to Output Invalid	0	—	0	—	ns
t <sub>ELZ</sub> <sup>(1,2)</sup>	Output Enable to Output Low-Z	0	—	0	—	ns
t <sub>EHZ</sub> <sup>(1,2)</sup>	Output Disable to Output High-Z	2	4.5	2	5	ns
t <sub>AS</sub> <sup>(3)</sup>	Address Setup Time	2.1	—	2.1	—	ns
t <sub>SS</sub> <sup>(3)</sup>	Address Status Setup Time	1.5	—	1.5	—	ns
t <sub>WS</sub> <sup>(3)</sup>	Write Setup Time	1.5	—	1.5	—	ns
t <sub>CS</sub> <sup>(3)</sup>	Chip Enable Setup Time	1.5	—	1.5	—	ns
t <sub>AVS</sub> <sup>(3)</sup>	Address Advance Setup Time	1.5	—	1.5	—	ns
t <sub>AH</sub> <sup>(3)</sup>	Address Hold Time	1.0	—	1.0	—	ns
t <sub>SH</sub> <sup>(3)</sup>	Address Status Hold Time	0.5	—	0.5	—	ns
t <sub>WH</sub> <sup>(3)</sup>	Write Hold Time	0.5	—	0.5	—	ns
t <sub>CEH</sub> <sup>(3)</sup>	Chip Enable Hold Time	0.5	—	0.5	—	ns
t <sub>AVH</sub> <sup>(3)</sup>	Address Advance Hold Time	0.5	—	0.5	—	ns

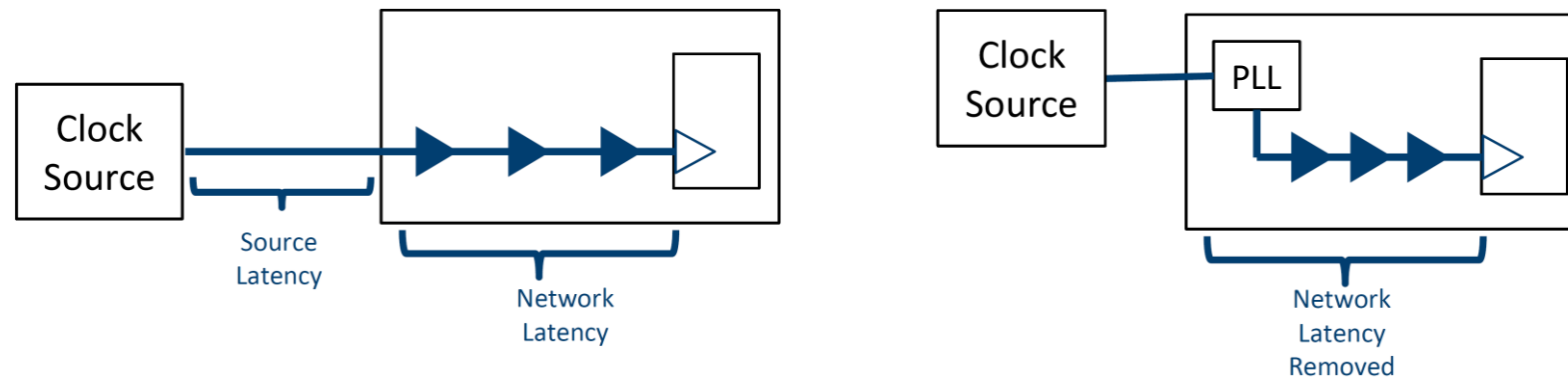
# Clock Effects: Latency

- ❖ **Clock Latency:** Delay for clock signal to reach components
  - Source latency: The delay between the clock definition and its source
  - Network latency: The delay between the clock definition and register clock pins
    - [extra] Often dealt with using an onboard phase-locked loop (PLL) – see `derive_pll_clocks` command


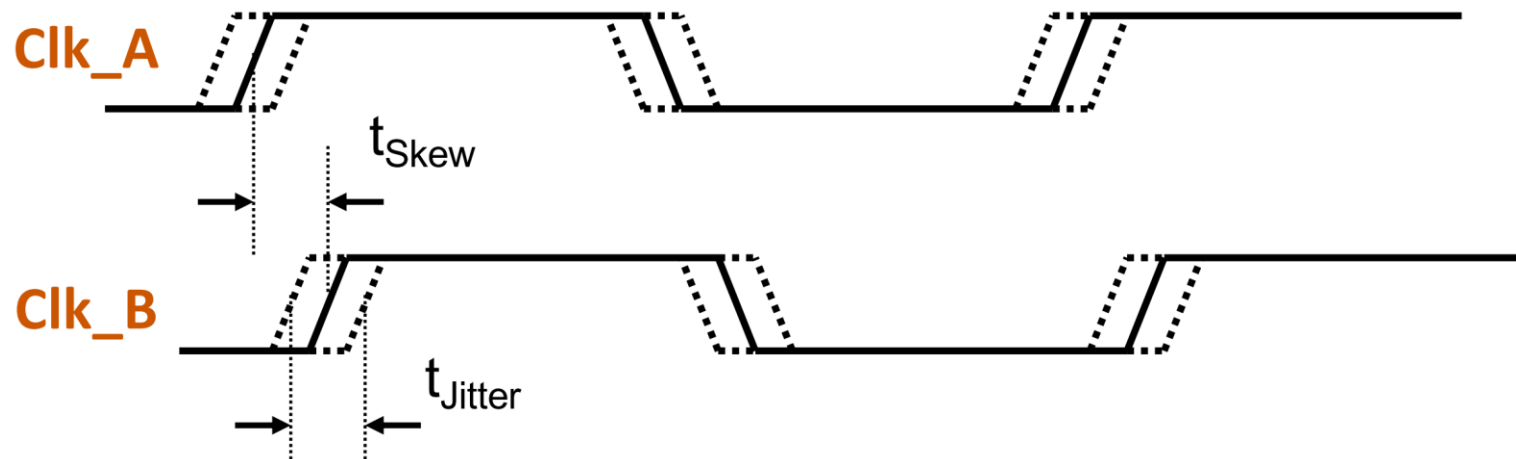
# Clock Effects: Uncertainty

- ❖ **Clock Uncertainty:** Clock signal does not arrive at every clock pin simultaneously
  - Skew: Differences in arrival time of a clock signal to different components
  - Jitter: Deviations from defined period
  - Synchronous clock domain crossings (future lecture)



# Timing Closure

- ❖ Timing constraints need to be met *simultaneously*
  - Sometimes fixing one violation will introduce another 🤪
- ❖ **Hold violations:** Fast data path and/or destination register's clock latency
  - Fix: Add delay in data path with buffers or pairs of inverters (Quartus does this automatically!)
- ❖ **Setup violations:** Data arrives too late compared to the destination register's clock speed
  - Slow down the clock (undesirable)
  - Tell fitter to try harder or confine logic to a smaller area
  - Rewrite code to simplify logic
  - Add *pipelining* (next lecture)