

# EE/CSE371 QUIZ 2

Name: \_\_\_\_\_

Student ID  
Number: \_\_\_\_\_

**Please do not turn the page until 11:50.**

## Instructions

- This quiz contains 4 pages, including this cover page. The 4<sup>th</sup> page is just for scratch work and won't be graded, but should still be turned in. You may additionally use the backs of the pages for scratch work.
- Please clearly indicate (*e.g.*, box, circle) your final answers if a specific box isn't provided.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all headphones and watches.
- You have 30 (+5) minutes to complete this quiz.

## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax.
- Powers of 2, for your reference:

$2^0$	$2^1$	$2^2$	$2^3$	$2^4$	$2^5$	$2^6$	$2^7$	$2^8$	$2^9$	$2^{10}$
1	2	4	8	16	32	64	128	256	512	1024

## Memory Size

Specify the size of a ROM (number of words and number of bits per word) that will accommodate the truth table representing the following combinational circuit component:

A circuit component that counts the number of "0" bits in a 4-bit input (e.g., 4'b0001 outputs 3, 4'b1010 outputs 2). Assume that the output width is the minimum required.

Depth (in words):

Width (in bits):

## Memory Addressing

We need a memory with a **256 byte** (not bits) capacity but only have access to **16 × 8 RAM chips**.


(A) How many of these chips are needed to provide the desired memory capacity?

(B) How many address bits/lines will our memory require to decode our chip select (i.e., how many address bits are needed for us to know which RAM chip we need to access)?
 
## Memory Implementation


For reference, the implementation of a 1-port, 2 × 8 register file/RAM is given here:

- D and Q are the register input/output ports
- en is the register enable port
- clk input assumed, but not shown
- MUX and DMX stand for (de)multiplexor




We now examine a dual-port RAM module, as introduced in lecture. This configuration allows for either reading or writing from ports a and b simultaneously.

 (A) Complete the implementation of a 2x8 dual-port RAM as a register file on the next page. Make sure to label your signals and signal widths and what selector combinations correspond to which MUX/DEMUX lines.



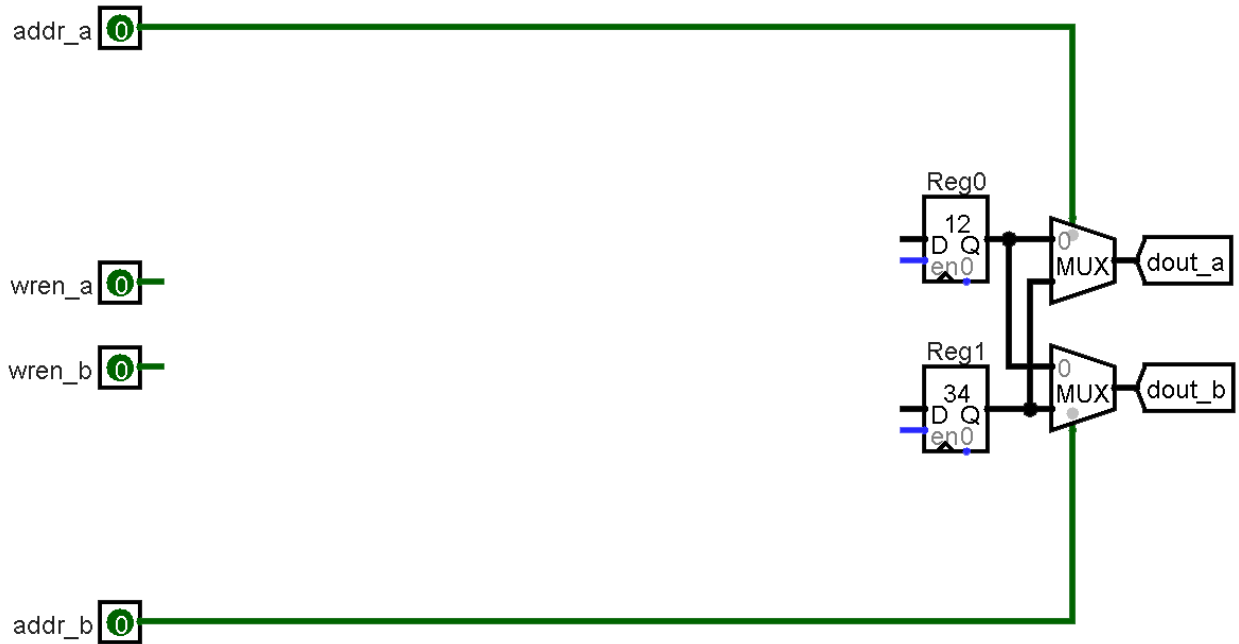- For the ports not shown (din\_a, din\_b), you can write their names next to any wire you want to connect them to (as shown with dout\_a and dout\_b).



- (B) *Briefly* explain how you chose to handle **write conflicts** (*i.e.*, when both ports simultaneously write to the same address).

---

Space for scratch work. Anything below this line won't be graded.

This page intentionally left blank for scratch work.