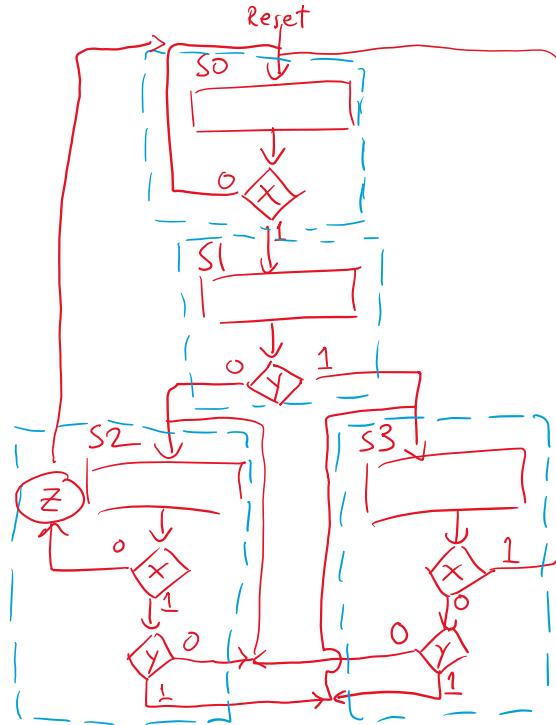


Design of Digital Circuits and Systems, Quiz 3

ASM and ASMD

Solution Outlines

Question 1:



Question 2:

- Alternate names could have been chosen for the data registers and control signals.
- Counter could have gone up instead of down from 0 to n-1.

