

EE/CSE371 QUIZ 5

Name: _____
Student ID
Number: _____

Please do not turn the page until 11:30.

Instructions

- This quiz contains 4 pages, including this cover page. You may use the backs of the pages for scratch work.
- The quiz is closed book and closed notes, though calculators are allowed.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all headphones and watches.
- You have 50 (+5) minutes to complete this quiz.

Advice


- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax.

Static Timing Analysis [10 pts]

setup slack = $DRT_{su} - DAT_{su}$ = min clock path - max data path

hold slack = $DAT_h - DRT_h$ = min data path - max clock path

 We will analyze the following circuit with the indicated timing constants:




- $T = 200$ ns (period), $t_{su} = 13$ ns (all regs)
- $t_{wire} = 0$ (all wires), $t_h = 9$ ns (all regs)
- $t_{clk1} \in [3, 7]$ ns (Reg1), $t_{CO} \in [12, 16]$ ns (all regs)
- $t_{clk2} \in [2, 6]$ ns (Reg2), $t_{AND} \in [45, 50]$ ns
- $t_{clk3} \in [1, 5]$ ns (Reg3), $t_{NOT} \in [15, 20]$ ns
- $t_{clk4} \in [4, 8]$ ns (Reg4), $t_{OR} \in [55, 60]$ ns

Solve for the setup slack and hold slack for this circuit and put your answers in the boxes below. You are allowed to use a calculator on this problem, but no credit will be given without work.

Setup Slack:	ns
Hold Slack:	ns

Pipelining [12 pts]

 We will look at a simplified version of the same circuit:



$$t_{su} = t_h = t_{wire} = t_{clk} = 0$$

$$t_{CO} = 10 \text{ ns (all regs)}$$


$$t_{AND} = 50 \text{ ns}$$

$$t_{NOT} = 20 \text{ ns}$$

$$t_{OR} = 60 \text{ ns}$$


- 1) Complete *both copies* of the Data Flow Graph (DFG) for the circuit by adding nodes labeled with their delays and edges. Note that A, B, C, and X correspond to the labeled nets in the circuit above. One node, corresponding to the lower OR gate, has been provided for you.
- 2) Draw cutsets on your two DFGs to make a 2-stage pipelined and a 3-stage pipelined version of this circuit with *minimal clock period*.
- 3) Assuming we use the minimum clock periods, compute the latency for both pipelined versions of this circuit and write them into the boxes below. No credit will be given without work.

2-stage pipeline:

 

Latency: ns


3-stage pipeline:

 

Latency: ns

Clock Domain Crossing [4 pts]

 We tweaked the circuit so that Reg4 is now controlled by a separate clock with $T_1 = 2 \times T_2$ (i.e., clk1 has a longer period):



Predictably, the output of Reg4 is suffering from lots of timing issues. Assuming we cannot change the clocks, **name two changes to this circuit we could do to improve its behavior.** Provide a brief explanation for why each change helps.

Change #1:

Change #2: