 


# Design of Digital Circuits and Systems, Quiz 5

## Timing: STA, Pipelining, CDC

### Solution Outlines

#### Static Timing Analysis:



**Longest data path** and **shortest data path** are shown on the circuit diagram above. Note that the clock network delays are ordered  $t_{clk1} > t_{clk2} > t_{clk3}$  and that  $t_{XOR} > t_{NOT} + t_{AND}$ . The **longest path** has Reg5 and the **shortest path** has Reg4 as the destination registers for the clock paths.

**setup slack** = min clock path – max data path

$$= (T + t_{clk5,min} - t_{su,max}) - (t_{clk1,max} + t_{CO,max} + 3 \cdot t_{wire,max} + t_{XOR,max} + t_{OR,max})$$

$$= (160 + 3 - 15) - (7 + 16 + 3 \cdot 0 + 70 + 50) = \mathbf{5 \text{ ns}}$$


**hold slack** = min data path – max clock path

$$= (t_{clk2,min} + t_{CO,min} + 2 \cdot t_{wire} + t_{NOT,min}) - (0 + t_{clk4,max} + t_{h,max})$$

$$= (2 + 12 + 2 \cdot 0 + 9) - (0 + 8 + 11) = \mathbf{4 \text{ ns}}$$
 
#### Pipelining:

The DFG and example cutsets (for **2-stage** and **3-stage** pipelines; multiple exist) might look like:



The key is to separate the OR delay from the XOR and AND delays; no stage should exceed the 70 delay of the XOR. The middle NOT delay can be placed in any stage with another node.

The 2-stage critical path gives us a  $T_{min}$  of  $t_{CO} + t_{XOR} = 16 + 70 = 86 \text{ ns}$ . Since it takes 2 clock cycles for the inputs to reach the output, latency =  $2 \cdot T_{min} + t_{CO} = 188 \text{ ns}$ .

The 3-stage critical path is the same as the 2-stage one =  $86 \text{ ns}$ . Since it takes 3 clock cycles for the inputs to reach the output, latency =  $3 \cdot T_{min} + t_{CO} = 274 \text{ ns}$ .

**Here, a 3-stage pipeline is unnecessary and increases our latency for no gain in throughput.**

### **Clock Domain Crossing:**

We have a *synchronous* clock domain crossing from a faster sending clock domain to a slower receiving clock domain.

For **data loss**, this would happen if a quick change in the sending domain (e.g.,  $0 \rightarrow 1 \rightarrow 0$ ) **gets missed** in the receiving domain (e.g., read 0 the whole time) because it is sampling 3 times slower than the sending domain can generate changes. Mentions of a change at the input of Reg4 or Reg5 causing metastability that results in **a bad/incorrect read** were also accepted.

For **data incoherence**, this means that a *multi-bit signal* passed across a CDC is read in an invalid state (i.e., **the signals no longer accurately reflect the logic of the circuit/inputs**). We mainly accepted two answers: (1) the two signals being sent across the clock domain crossing experience metastability differently (or at different times) and (2) the clk2 trigger falls in-between the times that the Reg4 and Reg5 inputs update due to the difference in path delays.