

Levels in Processor Design

Circuit design

- build gates (AND,OR, NAND, NOR, etc.), flip-flops, etc. from transistors

Logical design

- put gates together to form registers, adders, etc. (CSE370)

Register transfer level

- describes the execution of instructions by showing how information is transferred and manipulated between adders, registers, etc.
 - combinational: the output is a function of the input, e.g., an adder
 - sequential: state is remembered, e.g., registers

Architectural description

- ISA, software conventions

System description

- memory hierarchy, I/O, number of processors, etc.

Execution Cycle

What happens when an instruction executes

(1) **fetch**

- sent the PC to memory
- transfer an instruction from memory to the CPU
- increment the PC

(2) **decode** & read the ALU sources

- registers
- immediate from the instruction


(3) **execute**

- an ALU operation
- **effective address** calculation
 - address to memory
 - memory access
 - data to memory (if a store)
 - data from memory (if a load)
- branch target calculation
 - condition check
 - change the PC
 - save the return address on a **jal**

(4) **store** the result in a register

- from the ALU
- from memory

Processor Datapath & Control Unit

 


Datapath:

- **combinational** & **sequential** logic
- hardware that implements the operations: ALU, incrementer
- storage for the program (**processor state**): GPRs, PC, status
- wires & buses: data flow between the components

Control

- sends signals to the datapath elements
- specifies what operations to perform, what data to move, when to move it, where to move it


Datapath Building Blocks: Sequential

 

Register

- holds 32 bits
- can be read or written


Datapath Building Blocks: Sequential

 

Register File

- always reads
- writes controlled by enable
- can both read and write in the same cycle
 - write first, read second
- can read two register values in the same cycle

Datapath Building Block: Sequential

 


Memory

- can only read or write one location in a cycle
- both reads & writes controlled by an enable line

Datapath Building Block: Combinational


Multiplexor (MUX):

 - selects one of its inputs for output
- input selected depends on **select** signal




Demultiplexor (selector)

 - routes the input to one of the outputs
- the output chosen depends **select**



Datapath Building Block: Combinational

 

ALU

- Computes arithmetic & logical functions

Single-cycle Datapath

No hardware can be reused by the same instruction

(memory units not really on the CPU)