


Lecture 8

- Today
 - Finish single-cycle datapath/control path
 - Look at its performance and how to improve it.

now high tech! V2.9



The final datapath

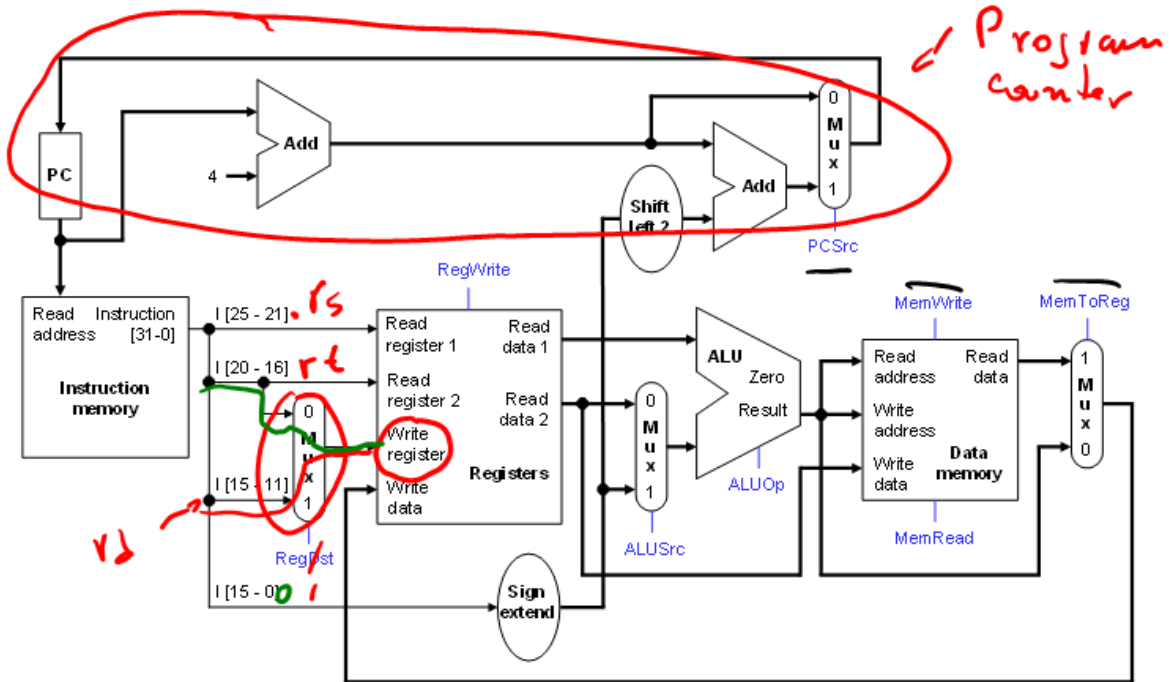


Control


- The control unit is responsible for setting all the control signals so that each instruction is executed properly.
 - The control unit's input is the 32-bit instruction word. †
 - The outputs are values for the blue control signals in the datapath.
- Most of the signals can be generated from the instruction opcode alone, and not the entire 32-bit word.
- To illustrate the relevant control signals, we will show the route that is taken through the datapath by R-type, lw, sw and beq instructions.

R-type instruction path

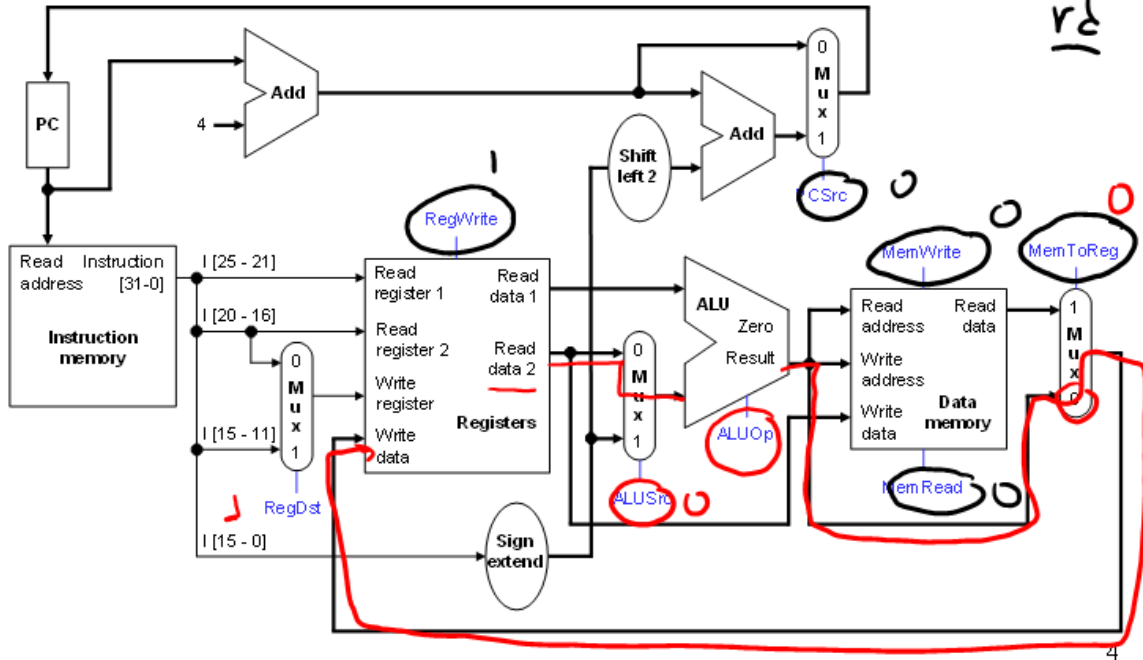- The R-type instructions include add, sub, and, or, and slt. write
- The ALUOp is determined by the instruction's "func" field. rd




lw instruction path

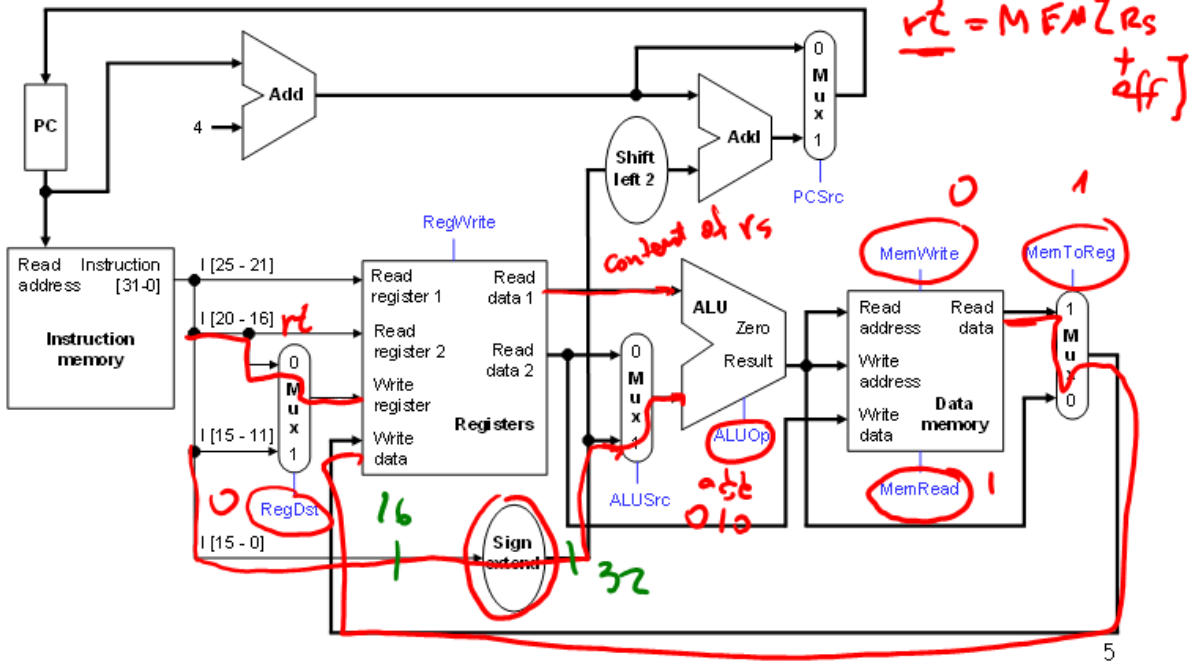


sw instruction path

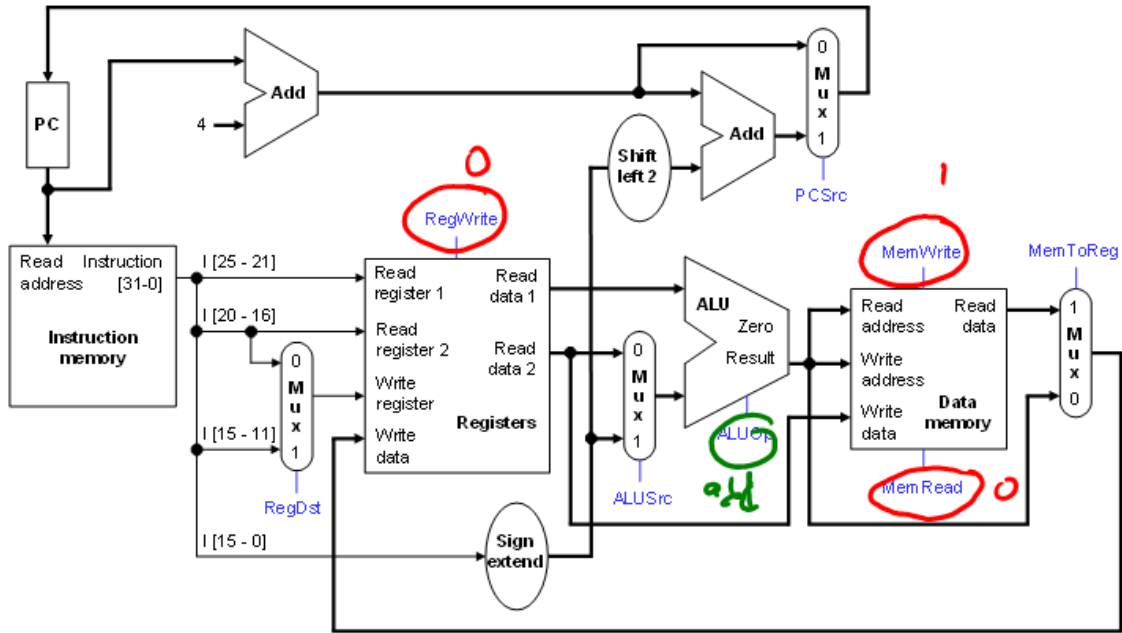- An example store instruction is `sw $a0, 16($sp)`.
- The `ALUOp` must be 010 (add), again to compute the effective address.



beq instruction path

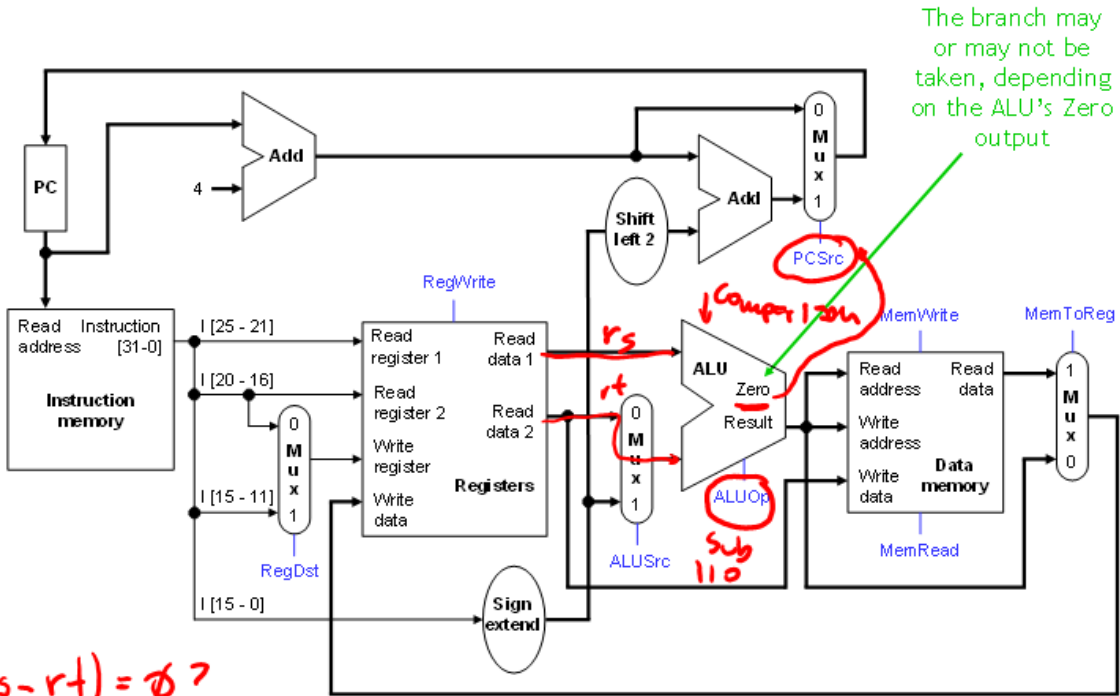


Control signal table

Operation	RegDst	RegWrite	ALUSrc	ALUOp	MemWrite	MemRead	MemToReg
add	1	1	0	010	0	0	0
sub	1	1	0	110	0	0	0
and	1	1	0	000	0	0	0
or	1	1	0	001	0	0	0
slt	1	1	0	111	0	0	0
lw	0	1	1	010	0	1	1
sw	X	0	1	010	1	0	X
beq	X	0	0	110	0	0	X

- sw and beq are the only instructions that do not write any registers.
- lw and sw are the only instructions that use the constant field. They also depend on the ALU to compute the effective memory address.
- ALUOp for R-type instructions depends on the instructions' func field.
- The PCSrc control signal (not listed) should be set if the instruction is beq and the ALU's Zero output is true.

Generating control signals

- The control unit needs 13 bits of inputs.
 - Six bits make up the instruction's opcode.
 - Six bits come from the instruction's func field.
 - It also needs the Zero output of the ALU.
- The control unit generates 10 bits of output, corresponding to the signals mentioned on the previous page.
- You can build the actual circuit by using big K-maps, big Boolean algebra, or big circuit design programs.
- The textbook presents a slightly different control unit.

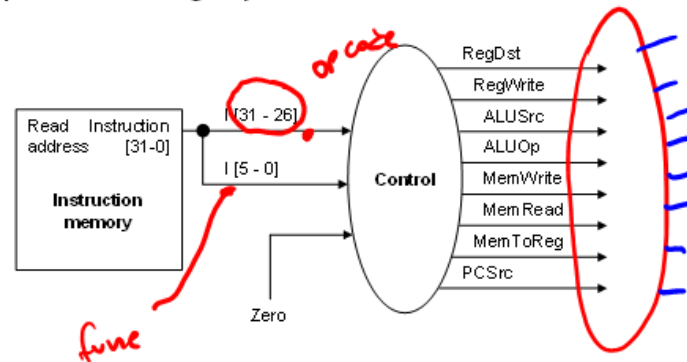

Summary of Single-Cycle Implementation

- A **datapath** contains all the functional units and connections necessary to implement an instruction set architecture.
 - For our **single-cycle implementation**, we use two separate memories, an ALU, some extra adders, and lots of multiplexers.
 - MIPS is a 32-bit machine, so most of the buses are 32-bits wide.
- The **control unit** tells the datapath what to do, based on the instruction that's currently being executed.
 - Our processor has ten **control signals** that regulate the datapath.
 - The control signals can be generated by a combinational circuit with the instruction's 32-bit binary encoding as input.
- Next, we'll see the performance limitations of this single-cycle machine and try to improve upon it.



Single-Cycle Performance



- We just saw a MIPS single-cycle datapath and control unit.
- Now we'll explore **factors** that contribute to a processor's **execution time**, and specifically at the performance of the single-cycle machine.
- Next time, we'll explore how to improve on the single cycle machine's performance using pipelining.

Three Components of CPU Performance

$$\text{CPU time}_{x,p} = \underbrace{\text{Instructions executed}_p}_{\text{Program}} * \underbrace{\text{CPI}_{x,p}}_{\text{Cycles Per Instruction}} * \underbrace{\text{Clock cycle time}_x}_{\text{Clock}}$$

The equation is annotated with red handwritten marks: a checkmark above 'Instructions executed_p', a double underline under 'CPI_{x,p}', a circle around 'CPI_{x,p}', a circle around 'Clock cycle time_x', and a star-in-a-circle symbol to the right of the equation. A red arrow points from the word 'Program' to 'Instructions executed_p', and another red arrow points from 'Cycles Per Instruction' to 'CPI_{x,p}'. There are also several red arrows pointing to the terms in the equation.



Instructions Executed

- Instructions executed:
 - We are not interested in the static instruction count, or how many lines of code are in a program. 200'
 - Instead we care about the dynamic instruction count, or how many instructions are actually executed when the program runs.
- There are three lines of code below, but how many instructions are actually executed?

```
→ li    $a0, 1000
Ostrich: sub  $a0, $a0, 1
          bne $a0, $0, Ostrich
```


3 static

1 x 1
1000 x
1000 x




Clock cycle time
 
$$\text{Clock rate} = \frac{1}{\text{period}}$$




- One “cycle” is the minimum time it takes the CPU to do any work.
 - The clock cycle time or clock period is just the length of a cycle.
 - The clock rate, or frequency, is the reciprocal of the cycle time.
- Generally, a higher frequency is better.
- Some examples illustrate some typical frequencies.
 - A 500MHz processor has a cycle time of ? 2 ns
 - A 2GHz (2000MHz) CPU has a cycle time of just 0.5ns (500ps).

How the add goes through the datapath

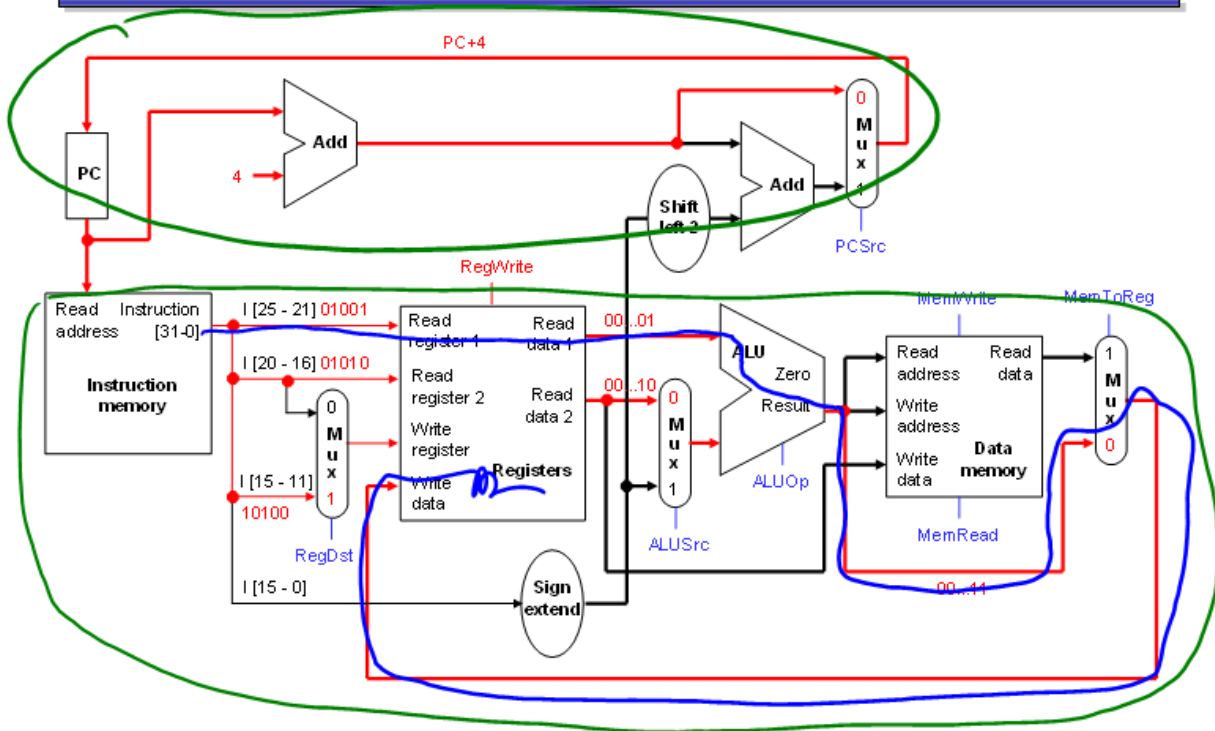

⇒ Edge-triggered state elements

- In an instruction like `add $t1, $t1, $t2`, how do we know `$t1` is not updated until *after* its original value is read?
- We'll assume that our state elements are positive edge triggered, and are updated only on the positive edge of a clock signal.
 - The register file and data memory have explicit write control signals, RegWrite and MemWrite. These units can be written to only if the control signal is asserted *and* there is a positive clock edge.
 - In a single-cycle machine the PC is updated on each clock cycle, so we don't bother to give it an explicit write control signal.

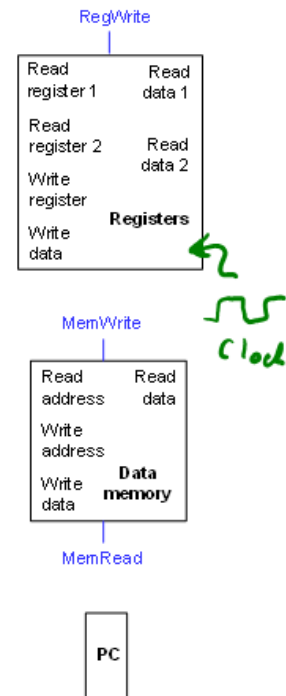

The datapath and the clock


1. On a positive clock edge, the PC is updated with a new address.
 2. A new instruction can then be loaded from memory. The control unit sets the datapath signals appropriately so that
 - registers are read, ✓
 - ALU output is generated, ✓
 - data memory is read or written, and ✓
 - branch target addresses are computed. ✓
 3. Several things happen on the next positive clock edge.
 - The register file is updated for arithmetic or lw instructions.
 - Data memory is written for a sw instruction. ✓
 - The PC is updated to point to the next instruction. ✓
- In a **single-cycle datapath** everything in Step 2 must complete within one clock cycle, before the next positive clock edge.

1
cycle



How long is that clock cycle?

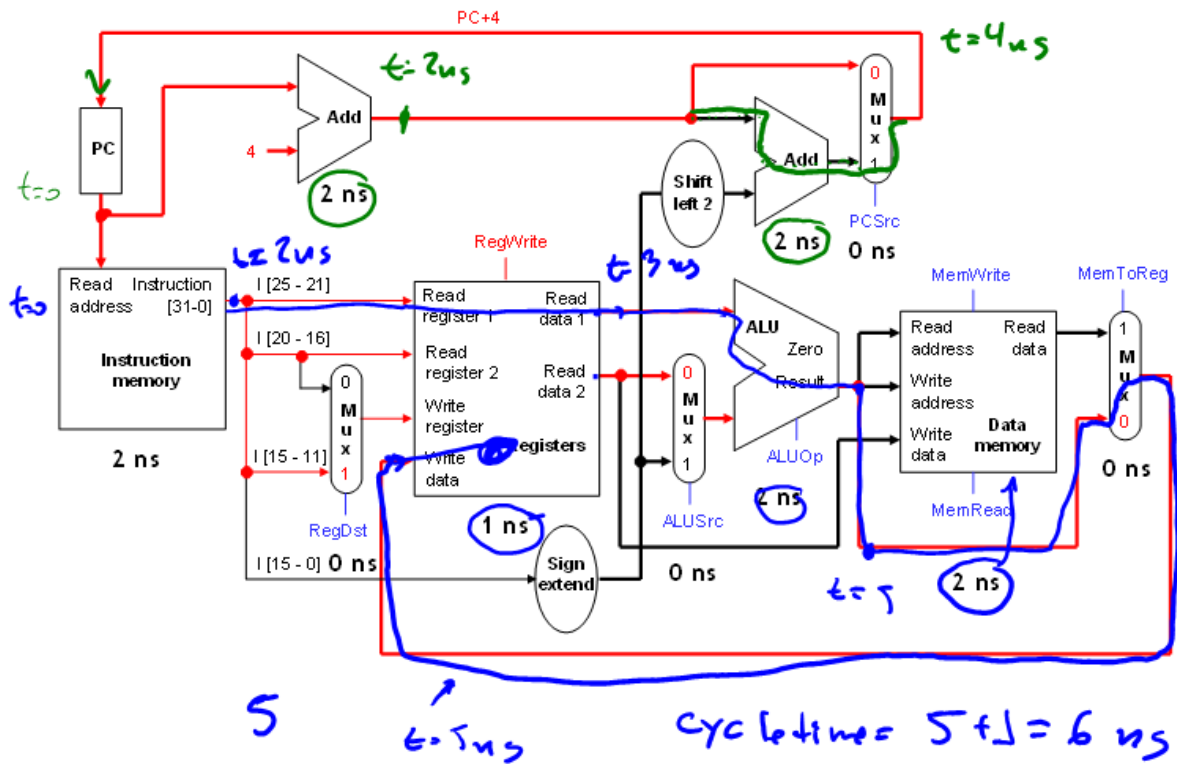
Compute the longest path in the add instruction



The slowest instruction...

- If all instructions must complete within one clock cycle, then the cycle time has to be large enough to accommodate the *slowest* instruction.
- For example, `lw $t0, -4($sp)` is the slowest instruction needing 8 ns.
 - Assuming the circuit latencies below.


cycle time = 7 + 1 = 8 ns

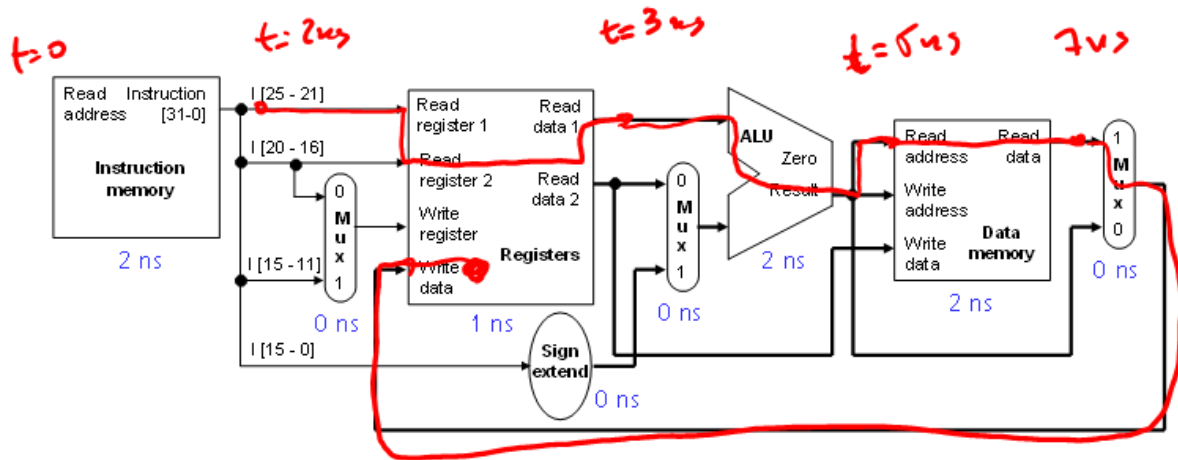

The slowest instruction...

- If all instructions must complete within one clock cycle, then the cycle time has to be large enough to accommodate the *slowest* instruction.
- For example, `lw $t0, -4($sp)` needs 8ns, assuming the delays shown here.


reading the instruction memory	2ns	}	8ns
reading the base register \$sp	1ns		
computing memory address \$sp-4	2ns		
reading the data memory	2ns		
storing data back to \$t0	1ns		

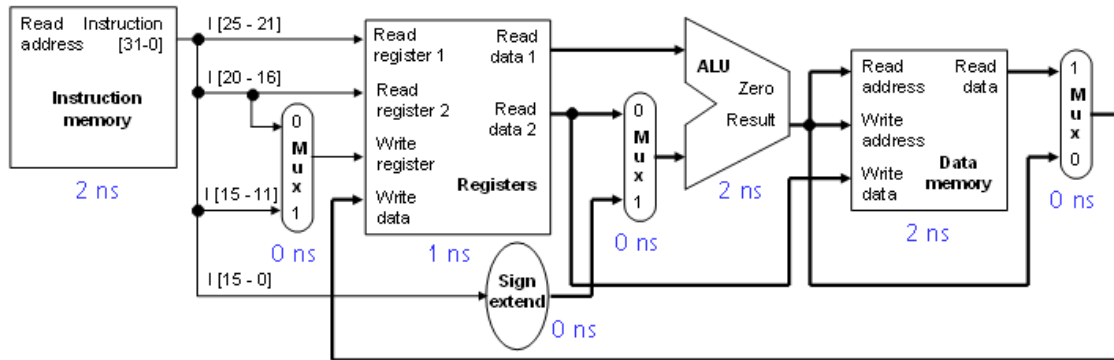

...determines the clock cycle time

- If we make the cycle time 8ns then *every* instruction will take 8ns, even if they don't need that much time.
- For example, the instruction `add $s4, $t1, $t2` really needs just 6ns.

reading the instruction memory	2 ns	} 6 ns
reading registers \$t1 and \$t2	1 ns	
computing \$t1 + \$t2	2 ns	
storing the result into \$s0	1 ns	

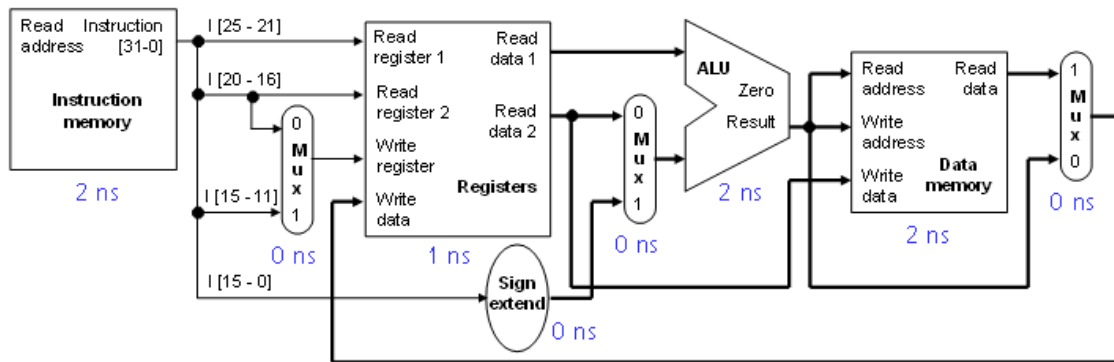

Performance of Single-cycle Design

$$\text{CPU time}_{x,p} = \frac{\text{Instructions executed}_p}{N} * \text{CPI}_{x,p} * \text{Clock cycle time}_x$$

$$\text{CPU time} = N \times 1 \times 8 \times 10^{-9}$$

$$N = 1 \text{ billion instrs} \Rightarrow 8 \text{ seconds}$$

How bad is this?

- With these same component delays, a sw instruction would need 7ns, and beq would need just 5ns.
- Let's consider the gcc instruction mix from p. 189 of the textbook.

→

Instruction	Frequency
Arithmetic	<u>48%</u>
Loads	<u>22%</u>
Stores	<u>11%</u>
Branches	<u>19%</u>



- With a single-cycle datapath, each instruction would require 8ns.
- But if we could execute instructions as fast as possible, the average time per instruction for gcc would be:

$$\underline{(48\% \times 6\text{ns})} + (22\% \times 8\text{ns}) + (11\% \times 7\text{ns}) + (19\% \times 5\text{ns}) = \underline{6.36\text{ns}}$$

- The single-cycle datapath is about 1.26 times slower!

It gets worse...

- We've made very optimistic assumptions about memory latency:
 - Main memory accesses on modern machines is >50ns.
 - For comparison, an ALU on an AMD Opteron takes ~0.3ns.
- Our worst case cycle (loads/stores) includes 2 memory accesses
 - A modern single cycle implementation would be stuck at <10Mhz.
 - Caches will improve common case access time, not worst case.
- Tying frequency to worst case path violates first law of performance!!
 - “Make the common case fast” (we'll revisit this often)

3.33GHz



Summary

- **Performance** is one of the most important criteria in judging systems.
 - Here we'll focus on Execution time.
- Our main performance equation explains how performance depends on several factors related to both hardware and software.

$$\text{CPU time}_{x,p} = \text{Instructions executed}_p * \text{CPI}_{x,p} * \text{Clock cycle time}_x$$

- It can be hard to measure these factors in real life, but this is a useful guide for comparing systems and designs.
- A single-cycle CPU has two main disadvantages.
 - The cycle time is limited by the worst case latency.
 - It isn't efficiently using its hardware.
- Next time, we'll see how this can be rectified with pipelining.

