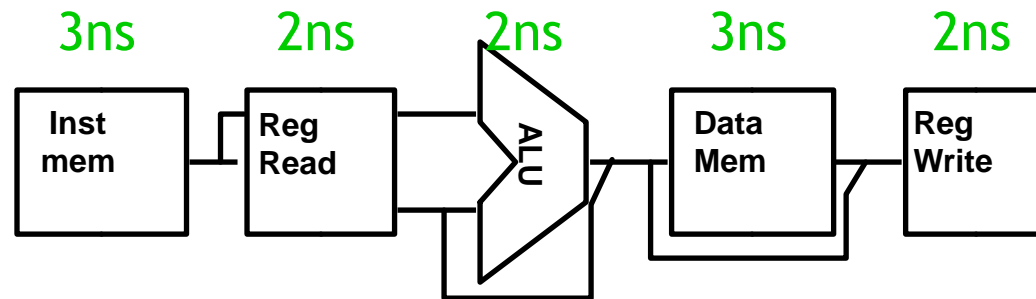


Lecture 11

- Today's topics:
 - More pipelining...

Performance Revisited

- Assuming the following functional unit latencies:



- What is the cycle time of a **single-cycle implementation**?
 - What is its throughput?

12ns


- What is the cycle time of an ideal **pipelined implementation**?
 - What is its steady-state throughput?

3ns, 1 inst per cycles (3ns)

- How much faster is pipelining?

~4x - Why not ~5?

Ideal speedup

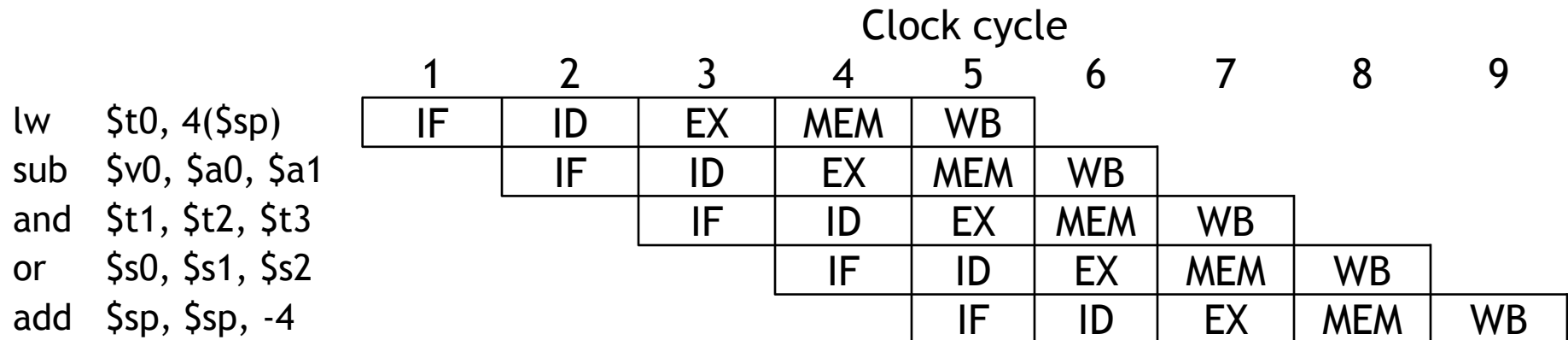


- In our pipeline, we can execute up to five instructions simultaneously.
 - This implies that the maximum speedup is 5 times.
 - In general, the **ideal speedup** equals the pipeline depth.
- Why was our speedup on the previous slide “only” 4 times?
 - The pipeline stages are imbalanced: a register file and ALU operations can be done in 2ns, but we must stretch that out to 3ns to keep the ID, EX, and WB stages synchronized with IF and MEM.
 - Balancing the stages is one of the many hard parts in designing a pipelined processor.

The pipelining paradox

	Clock cycle								
	1	2	3	4	5	6	7	8	9
lw \$t0, 4(\$sp)	IF	ID	EX	MEM	WB				
sub \$v0, \$a0, \$a1		IF	ID	EX	MEM	WB			
and \$t1, \$t2, \$t3			IF	ID	EX	MEM	WB		
or \$s0, \$s1, \$s2				IF	ID	EX	MEM	WB	
add \$sp, \$sp, -4					IF	ID	EX	MEM	WB

- Pipelining does *not* improve the **execution time** of any single instruction. Each instruction here actually takes *longer* to execute than in a single-cycle datapath (15ns vs. 12ns)!
- Instead, pipelining increases the **throughput**, or the amount of work done per unit time. Here, several instructions are executed together in each clock cycle.
- Why does this help us?
- The result is improved execution time for a *sequence* of instructions, such as an entire program.

Pipeline diagram review

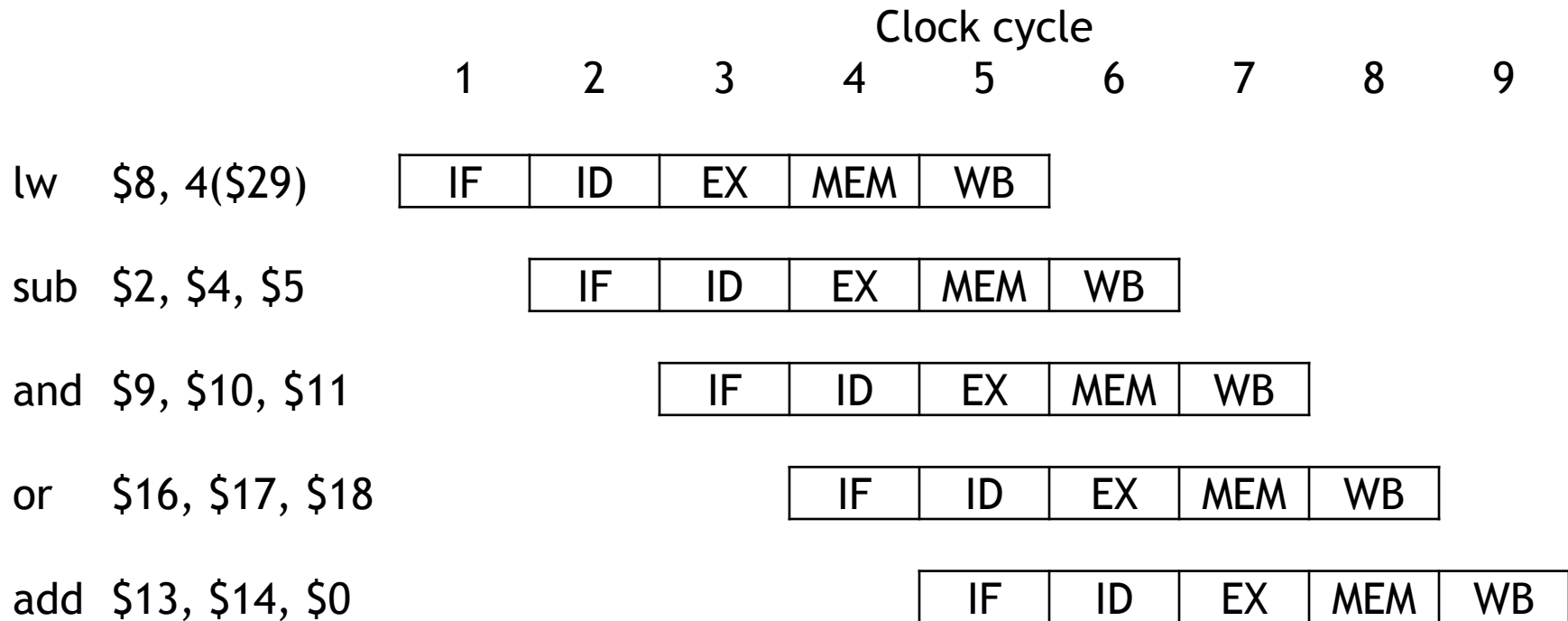

- This diagram shows the execution of an ideal code fragment.
 - Each instruction needs a total of five cycles for execution.
 - One instruction begins on every clock cycle for the first five cycles.
 - One instruction completes on each cycle from that time on.

Our examples are too simple

- Here is the example instruction sequence used to illustrate pipelining

```
lw    $8, 4($29)
sub   $2, $4, $5
and   $9, $10, $11
or    $16, $17, $18
add   $13, $14, $0
```

- The instructions in this example are **independent**.
 - Each instruction reads and writes completely different registers.
 - Our datapath handles this sequence easily, as we saw last time.
- But most sequences of instructions are *not* independent!

An example with dependencies

	sub	\$2, \$1, \$3
and	\$12, \$2, \$5	
or	\$13, \$6, \$2	
add	\$14, \$2, \$2	
sw	\$15, 100(\$2)	


This is not a problem for the single-cycle and multicycle datapaths.

Each instruction is executed completely before the next one begins.

This ensures that instructions 2 through 5 above use the new value of \$2 (the sub result), just as we expect.


How would this code sequence fare in our pipelined datapath?

Data hazards in the pipeline diagram

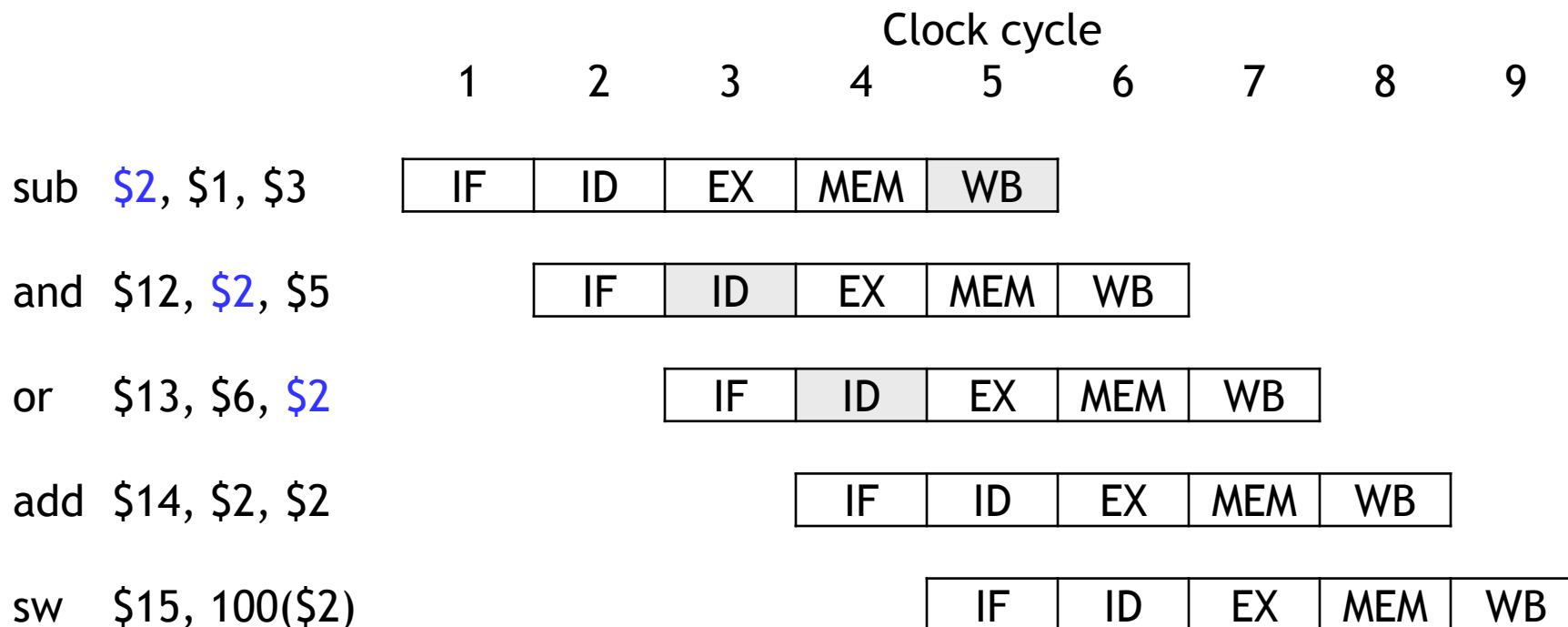


- The SUB instruction does not write to register \$2 until clock cycle 5. This causes two **data hazards** in our current pipelined datapath.
 - The AND reads register \$2 in cycle 3. Since SUB hasn't modified the register yet, this will be the *old* value of \$2, not the new one.
 - Similarly, the OR instruction uses register \$2 in cycle 4, again before it's actually updated by SUB.

Things that are okay

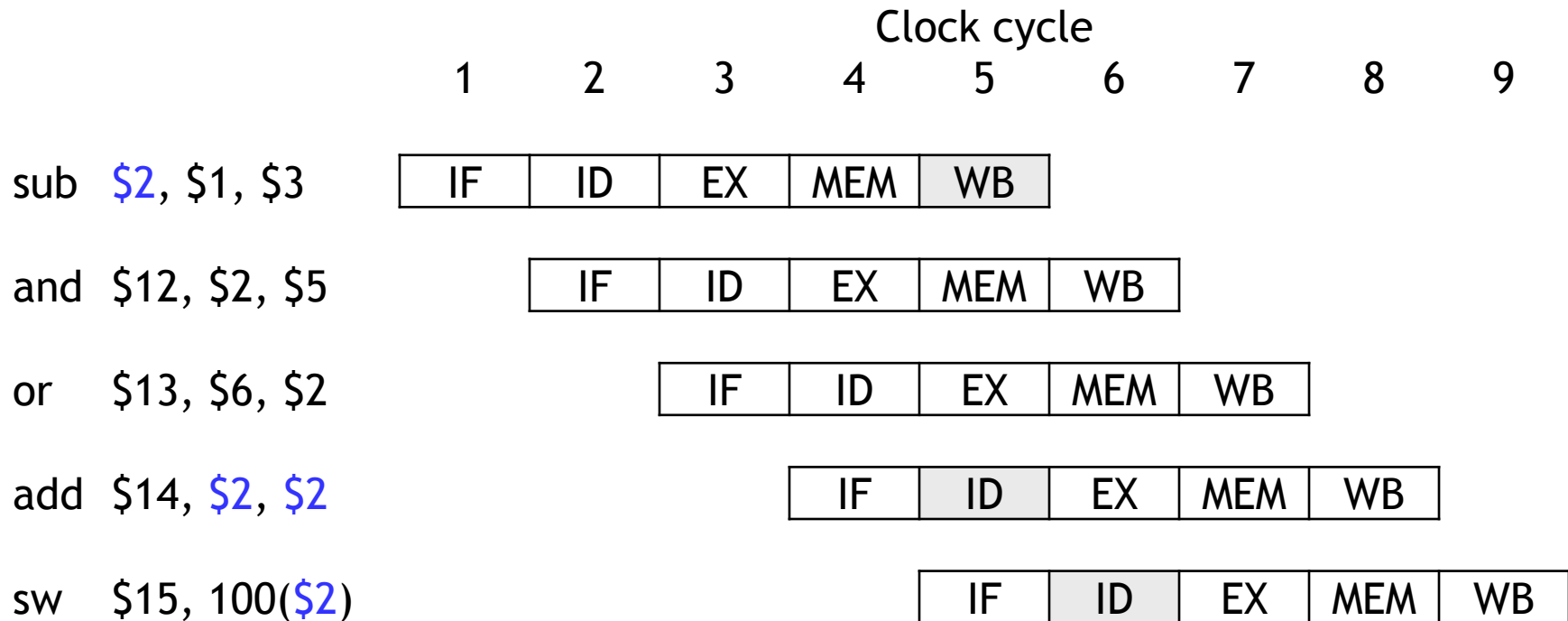


- The ADD instruction is okay, because of the register file design.
 - Registers are written at the beginning of a clock cycle.
 - The new value will be available by the end of that cycle.
- The SW is no problem at all, since it reads \$2 after the SUB finishes.

Dependency arrows

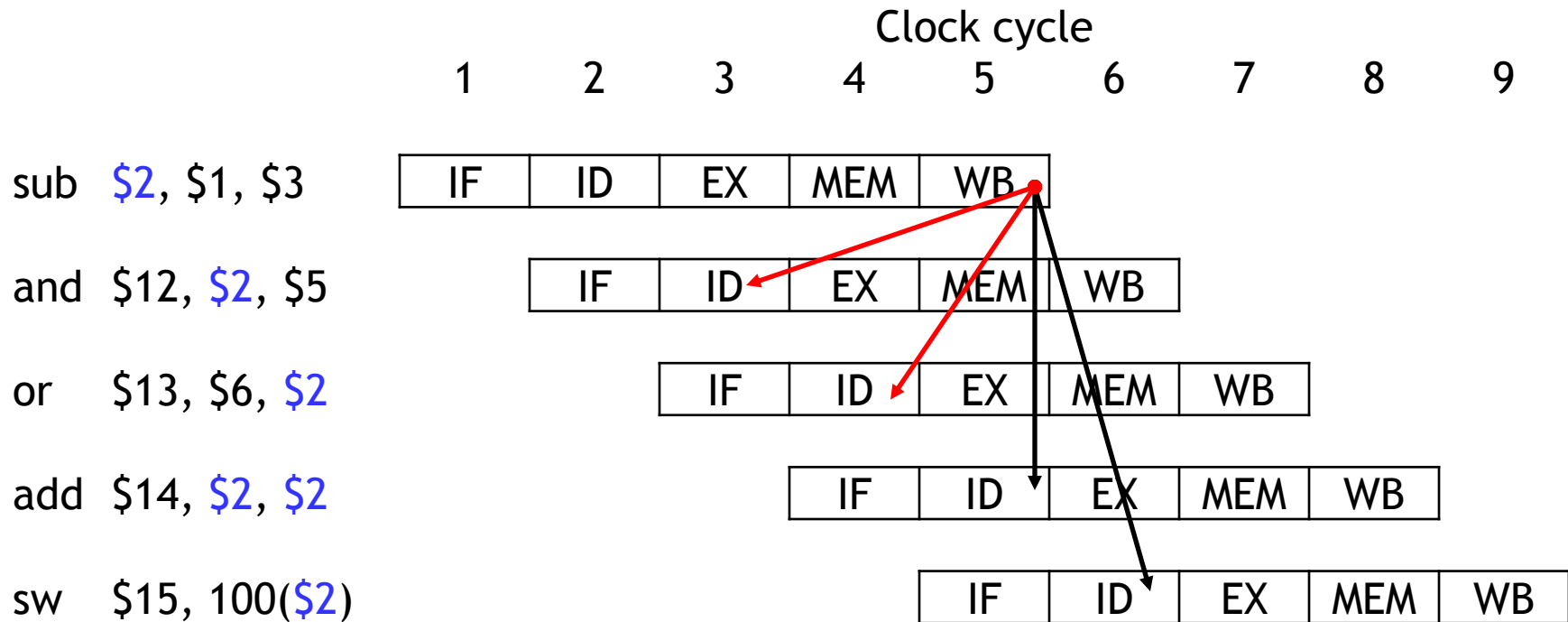


- Arrows indicate the flow of data between instructions.
 - The tails of the arrows show when register \$2 is written.
 - The heads of the arrows show when \$2 is read.
- Any arrow that points backwards in time represents a **data hazard** in our basic pipelined datapath. Here, hazards exist between instructions 1 & 2 and 1 & 3.

A fancier pipeline diagram

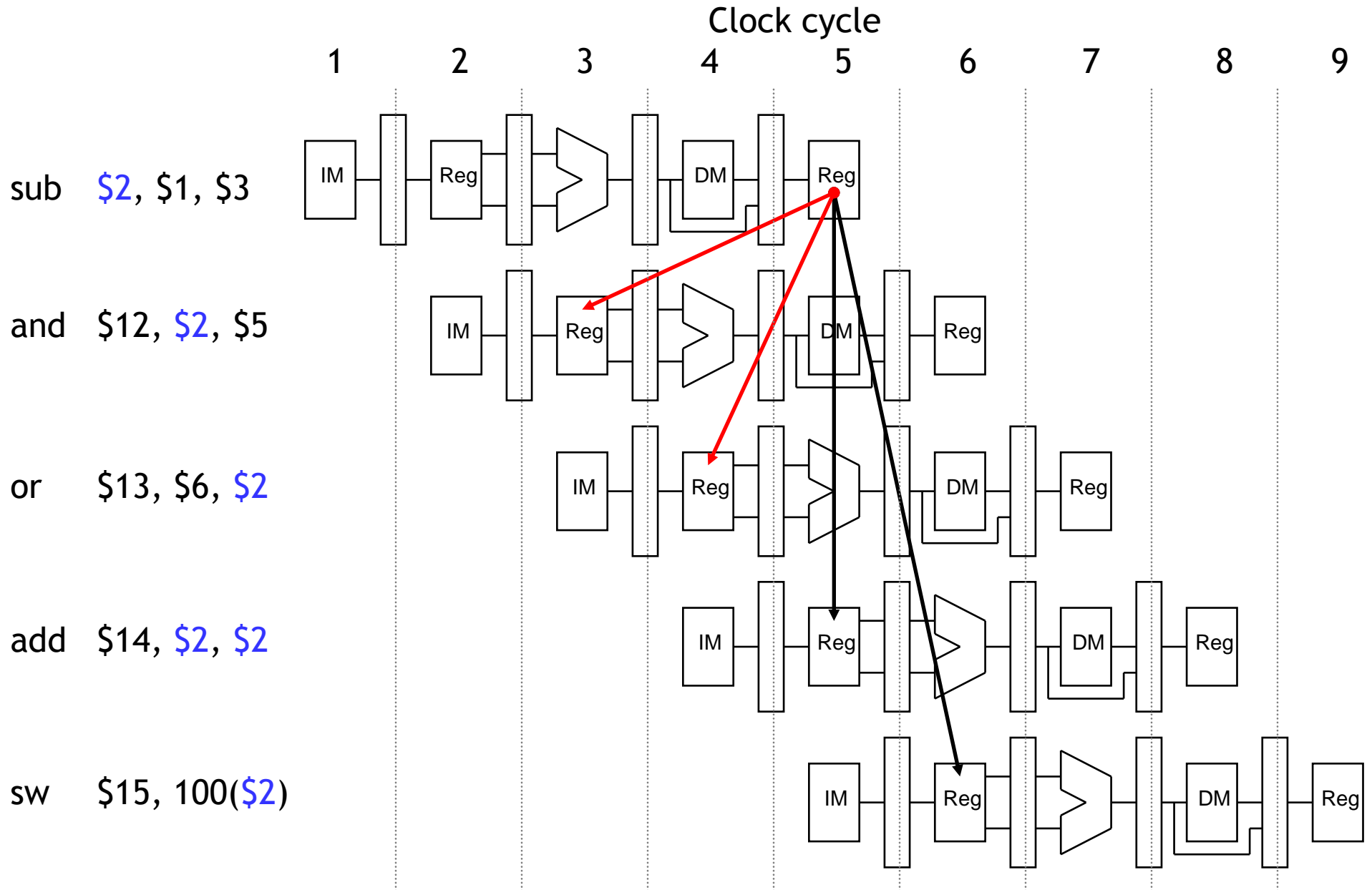


A more detailed look at the pipeline

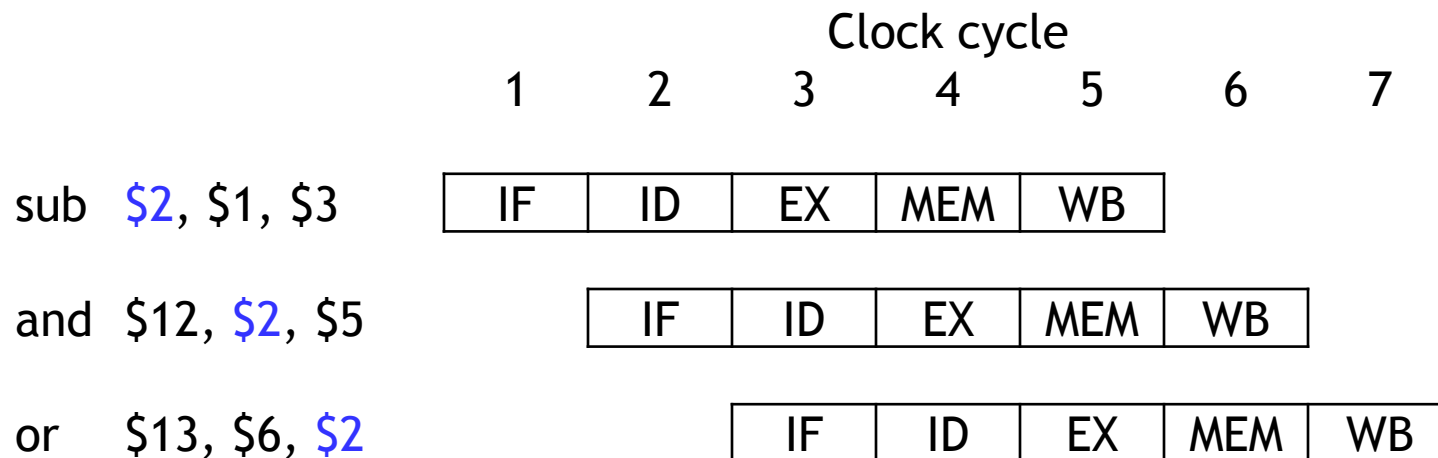- We have to eliminate the hazards, so the AND and OR instructions in our example will use the correct value for register \$2.
- When is the data actually produced and consumed?
- What can we do?




A more detailed look at the pipeline

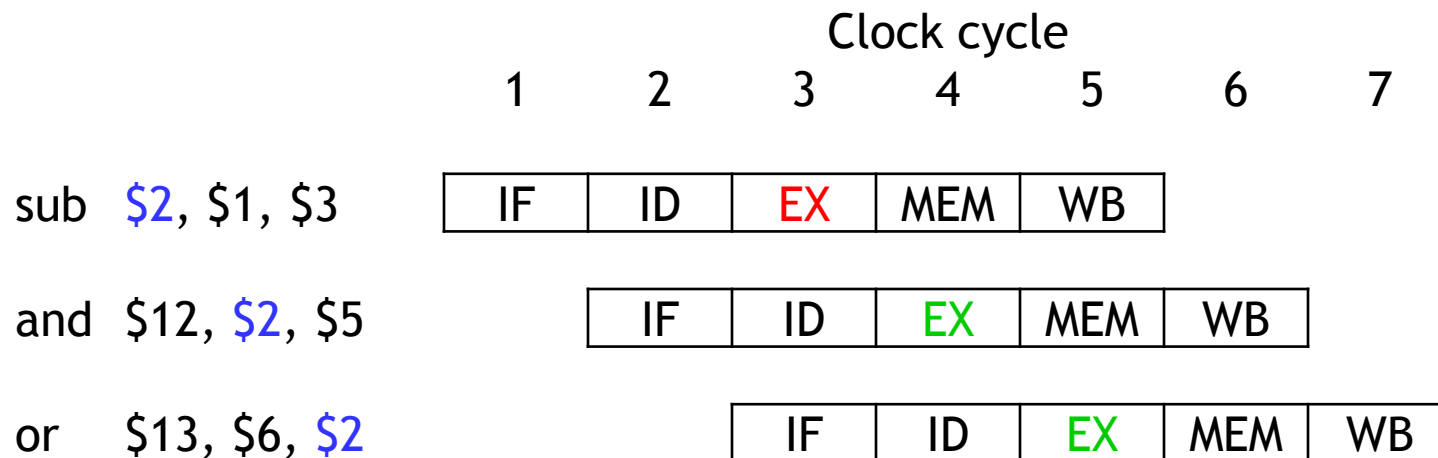- We have to eliminate the hazards, so the AND and OR instructions in our example will use the correct value for register \$2.
- Let's look at when the data is actually produced and consumed.
 - The SUB instruction produces its result in its **EX** stage, during cycle 3 in the diagram below.
 - The AND and OR need the new value of \$2 in their **EX** stages, during clock cycles 4-5 here.




Bypassing the register file

- The actual result \$1 – \$3 is computed in clock cycle 3, *before* it's needed in cycles 4 and 5.
- If we could somehow bypass the writeback and register read stages when needed, then we can eliminate these data hazards.
 - Today we'll focus on hazards involving arithmetic instructions.
 - Next time, we'll examine the lw instruction.
- Essentially, we need to pass the ALU output from SUB directly to the AND and OR instructions, without going through the register file.

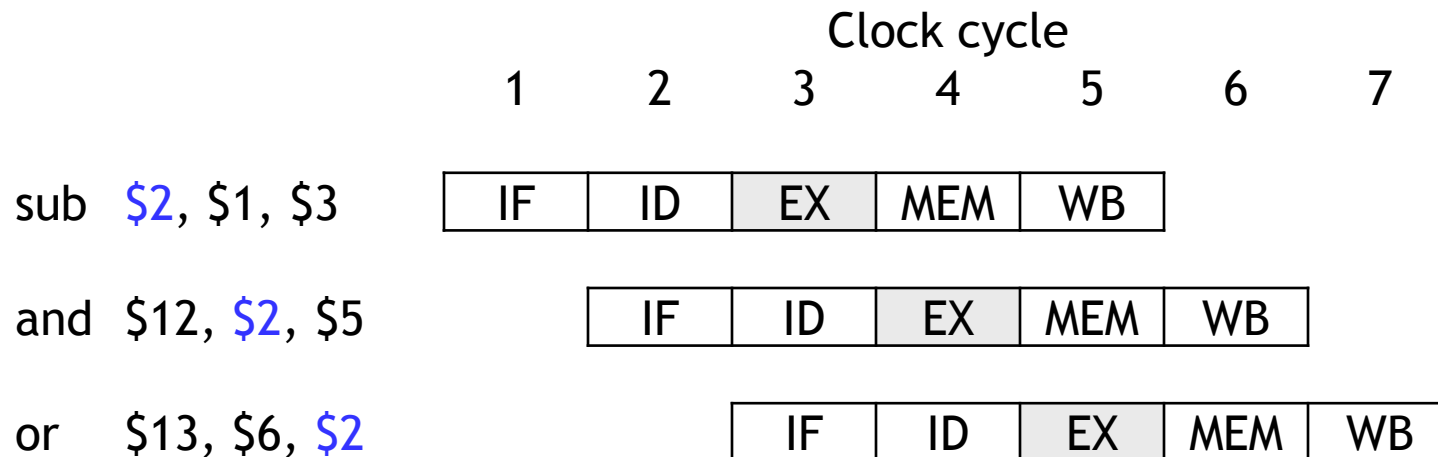


Where to find the ALU result

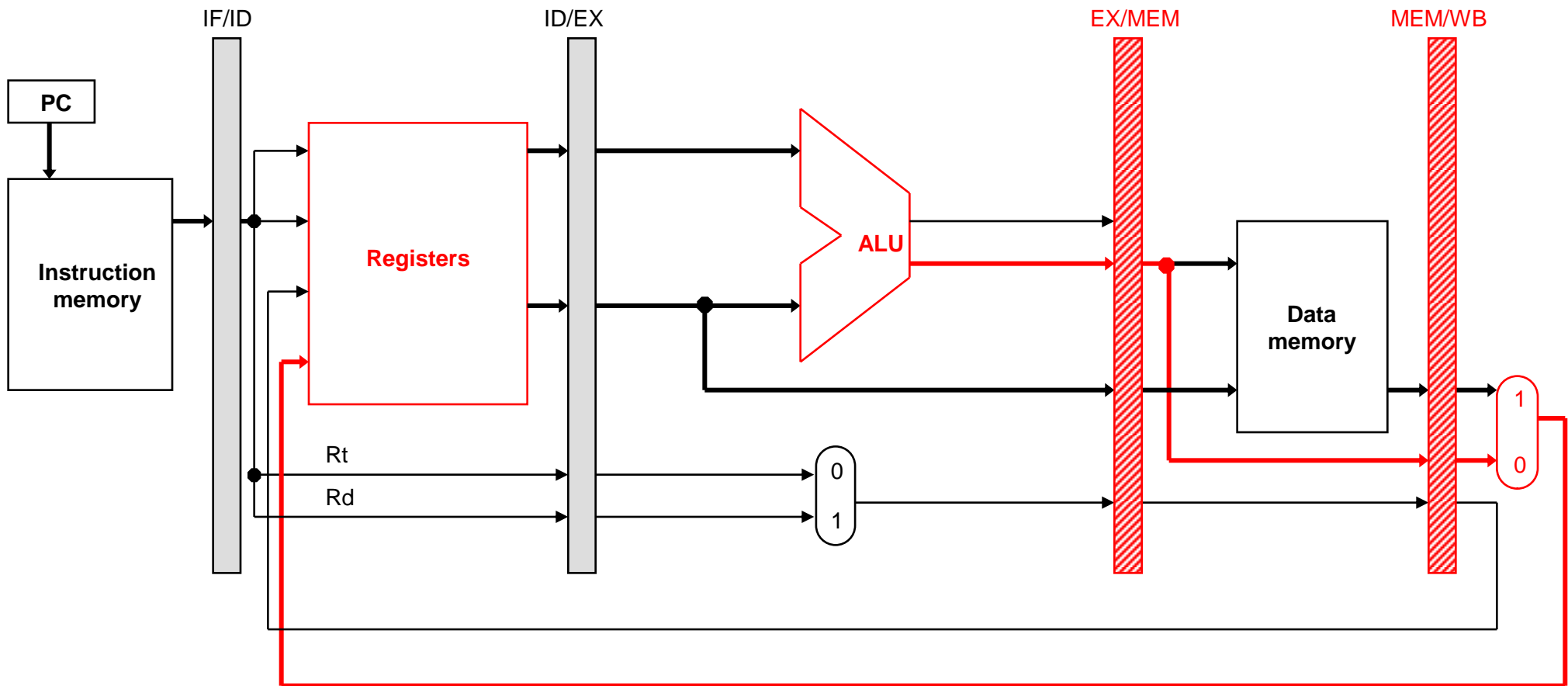- The ALU result generated in the EX stage is normally passed through the pipeline registers to the MEM and WB stages, before it is finally written to the register file.
- This is an abridged diagram of our pipelined datapath.




Forwarding

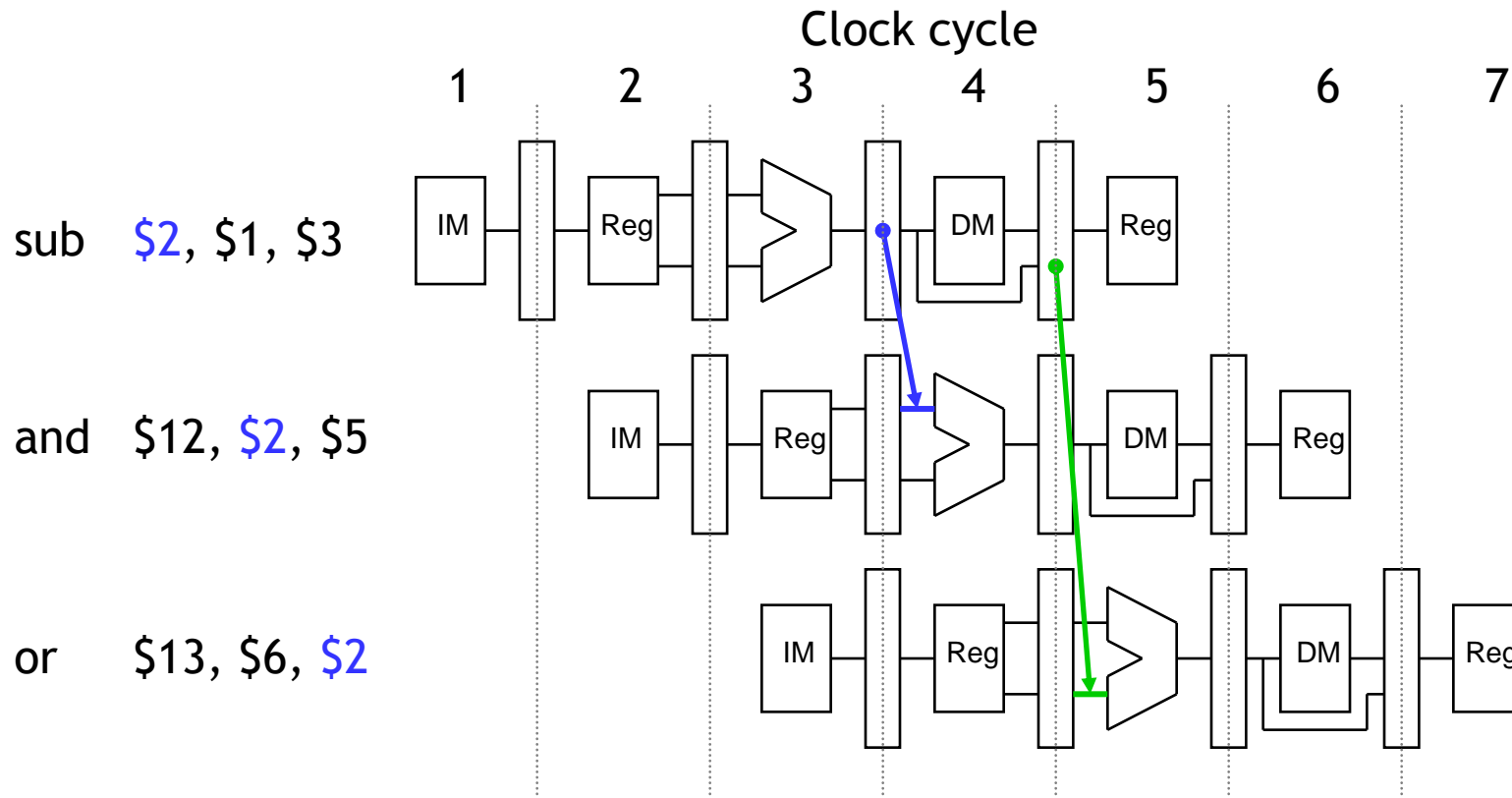- Since the pipeline registers already contain the ALU result, we could just **forward** that value to subsequent instructions, to prevent data hazards.
 - In clock cycle 4, the AND instruction can get the value \$1 - \$3 from the **EX/MEM** pipeline register used by sub.
 - Then in cycle 5, the OR can get that same result from the **MEM/WB** pipeline register being used by SUB.




Outline of forwarding hardware

- A **forwarding unit** selects the correct ALU inputs for the EX stage.
 - If there is no hazard, the ALU's operands will come from the **register file**, just like before.
 - If there is a hazard, the operands will come from either the **EX/MEM** or **MEM/WB** pipeline registers instead.
- The ALU sources will be selected by two new multiplexers, with control signals named **ForwardA** and **ForwardB**.

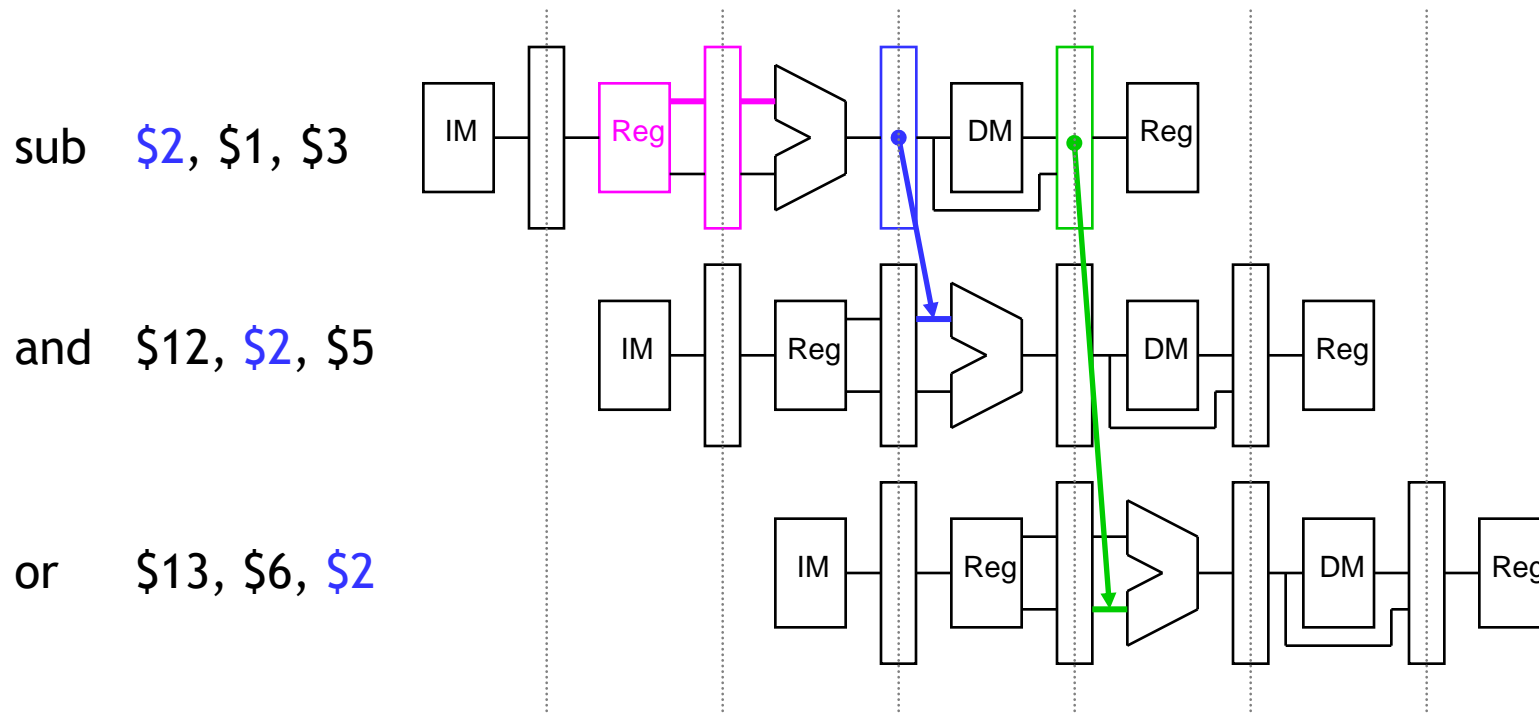

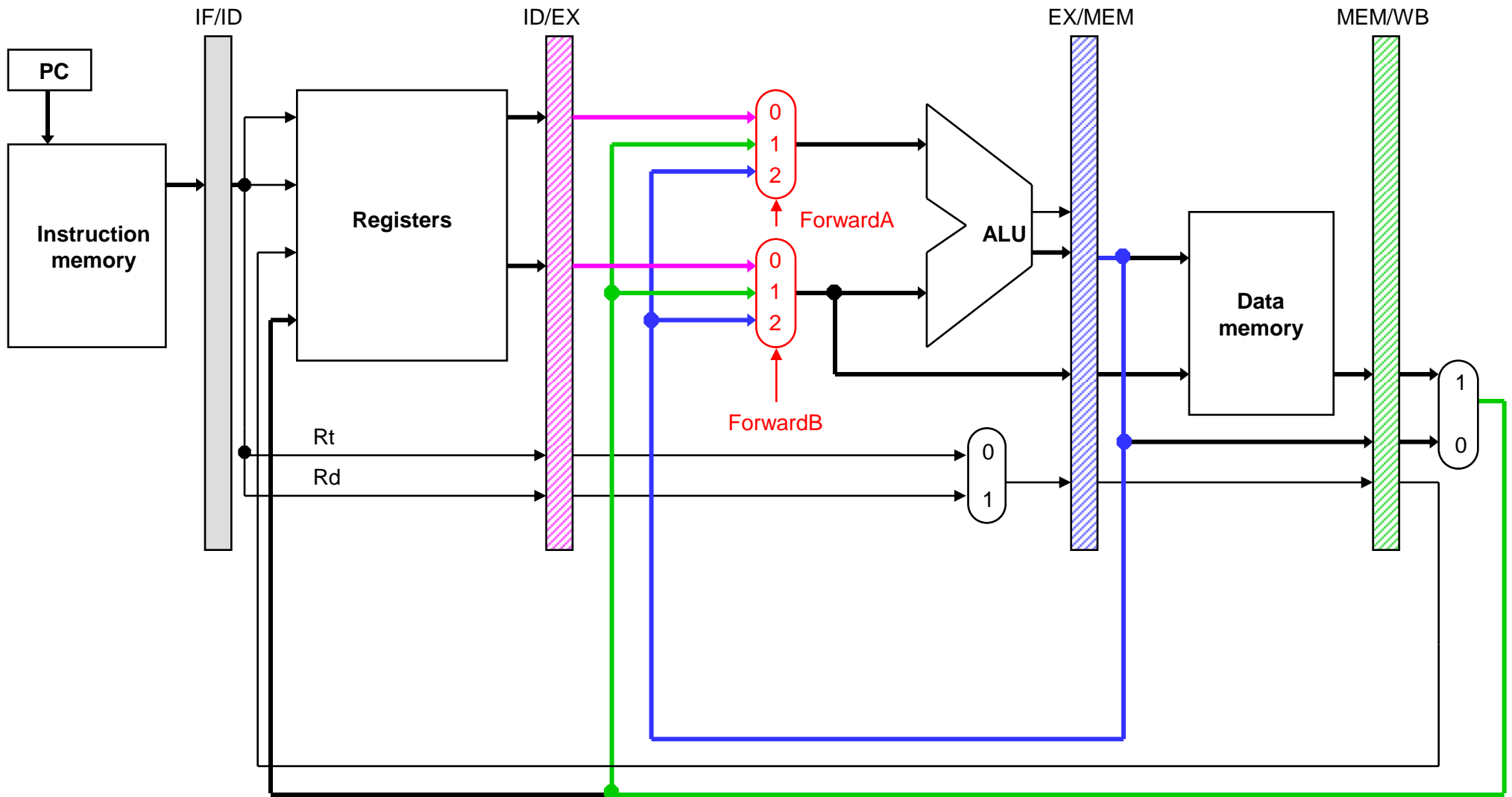Simplified datapath with forwarding muxes




Detecting EX/MEM data hazards

- So how can the hardware determine if a hazard exists?


sub \$2, \$1, \$3

and \$12, \$2, \$5

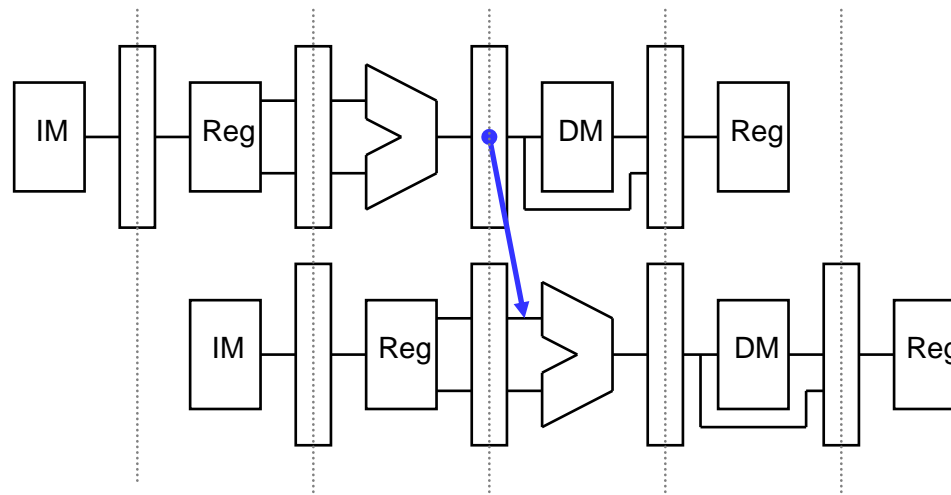

Detecting EX/MEM data hazards

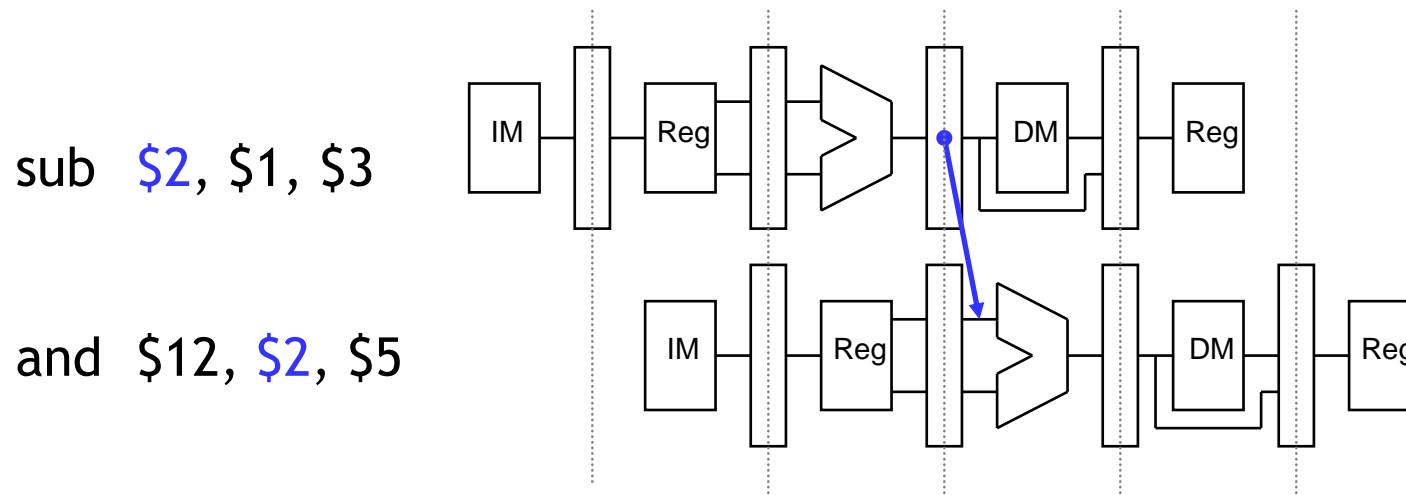- So how can the hardware determine if a hazard exists?
- An **EX/MEM hazard** occurs between the instruction currently in its EX stage and the previous instruction if:
 1. The previous instruction will write to the register file, *and*
 2. The destination is one of the ALU source registers in the EX stage.
- There is an EX/MEM hazard between the two instructions below.



- Data in a pipeline register can be referenced using a class-like syntax. For example, `ID/EX.RegisterRt` refers to the `rt` field stored in the ID/EX pipeline.


EX/MEM data hazard equations

- The first ALU source comes from the pipeline register when necessary.

if ($EX/MEM.RegWrite = 1$
and $EX/MEM.RegisterRd = ID/EX.RegisterRs$)
then $ForwardA = 2$

- The second ALU source is similar.

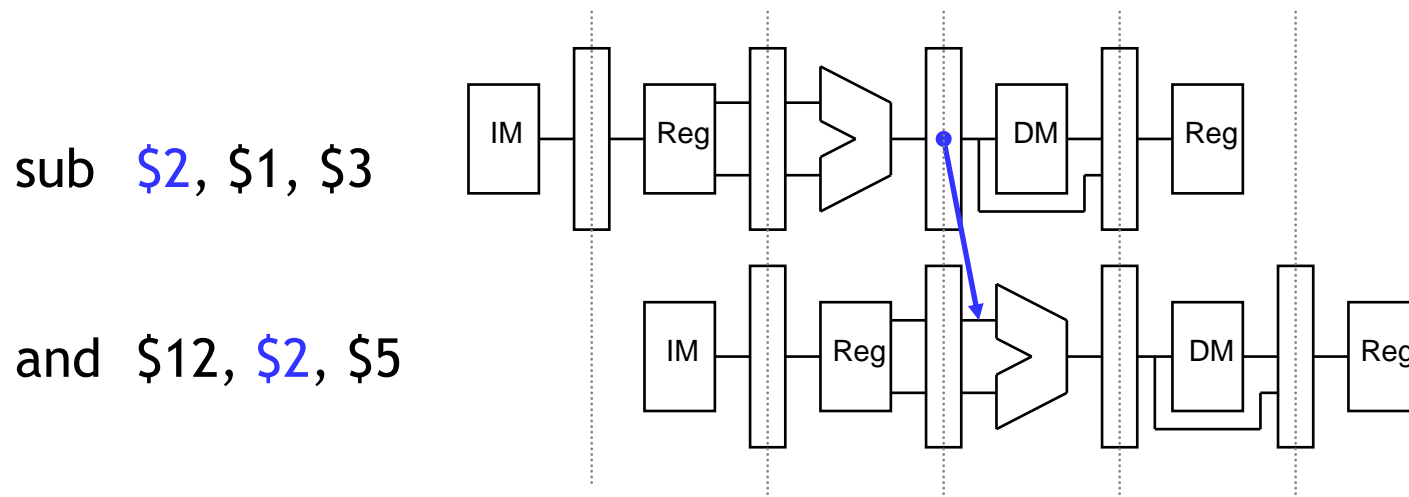if ($EX/MEM.RegWrite = 1$
and $EX/MEM.RegisterRd = ID/EX.RegisterRt$)
then $ForwardB = 2$




Detecting MEM/WB data hazards

- A **MEM/WB hazard** may occur between an instruction in the EX stage and the instruction from *two* cycles ago.
- One new problem is if a register is updated twice in a row.

```
add  $1, $2, $3
add  $1, $1, $4
sub  $5, $5, $1
```

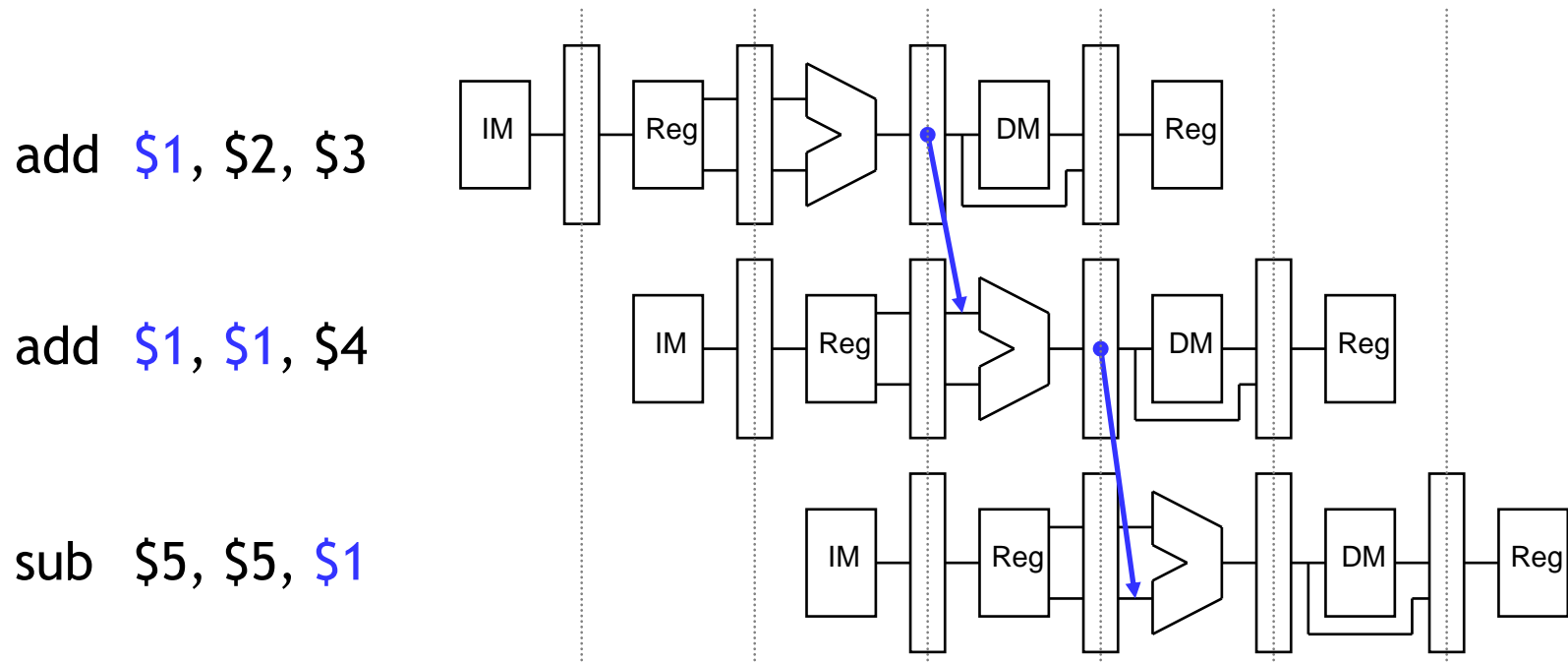- Register \$1 is written by *both* of the previous instructions, but only the most recent result (from the second ADD) should be forwarded.



MEM/WB hazard equations


- Here is an equation for detecting and handling MEM/WB hazards for the first ALU source.

if ($\text{MEM/WB.RegWrite} = 1$
and $\text{MEM/WB.RegisterRd} = \text{ID/EX.RegisterRs}$
and ($\text{EX/MEM.RegisterRd} \neq \text{ID/EX.RegisterRs}$ or $\text{EX/MEM.RegWrite} = 0$)
then $\text{ForwardA} = 1$

- The second ALU operand is handled similarly.

if ($\text{MEM/WB.RegWrite} = 1$
and $\text{MEM/WB.RegisterRd} = \text{ID/EX.RegisterRt}$
and ($\text{EX/MEM.RegisterRd} \neq \text{ID/EX.RegisterRt}$ or $\text{EX/MEM.RegWrite} = 0$)
then $\text{ForwardB} = 1$

Simplified datapath with forwarding

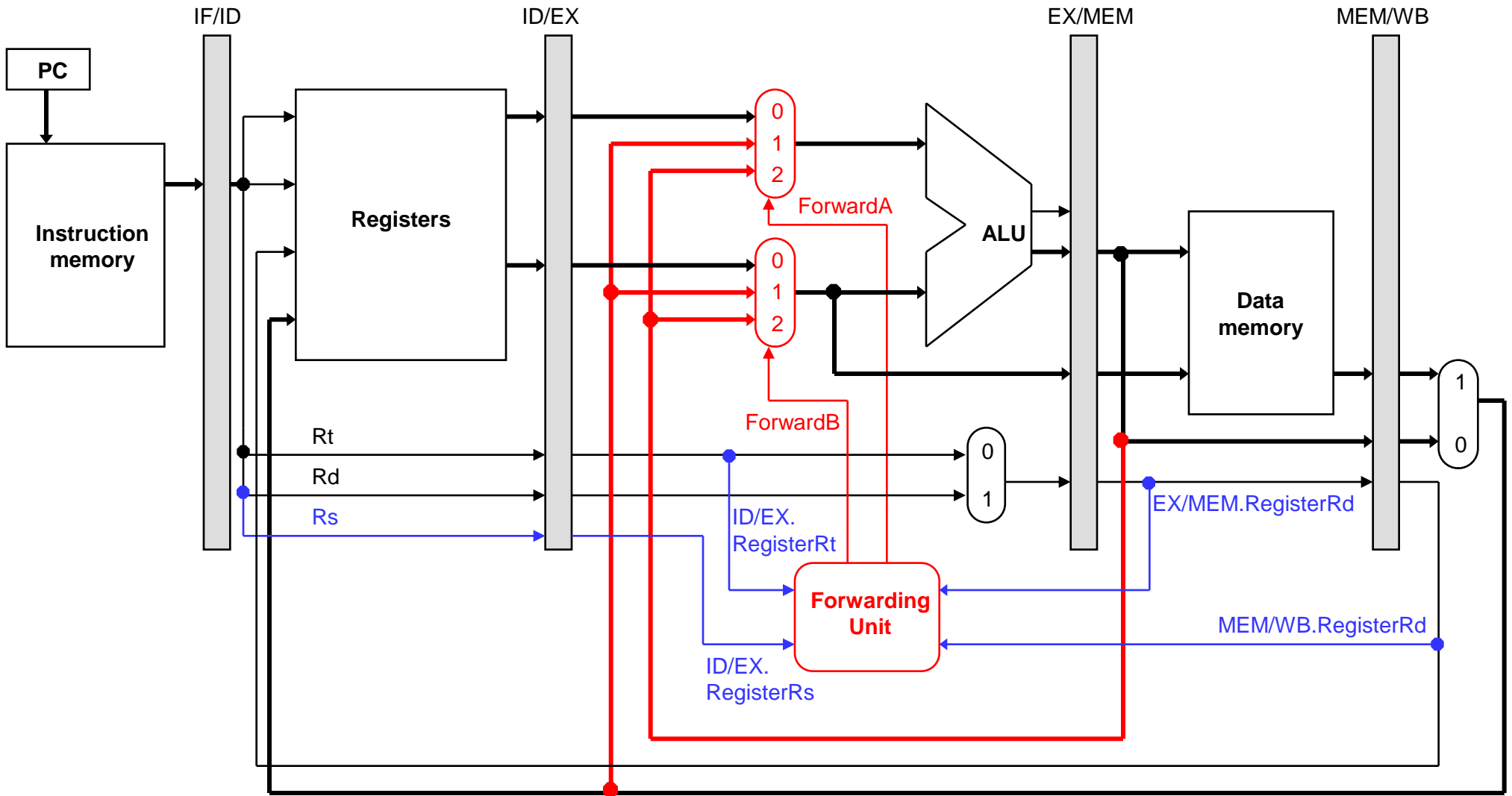

The forwarding unit

- The forwarding unit has several control signals as inputs.

ID/EX.RegisterRs

EX/MEM.RegisterRd

MEM/WB.RegisterRd

ID/EX.RegisterRt

EX/MEM.RegWrite

MEM/WB.RegWrite

(The two RegWrite signals are not shown in the diagram, but they come from the control unit.)


- The forwarding unit outputs are selectors for the **ForwardA** and **ForwardB** multiplexers attached to the ALU. These outputs are generated from the inputs using the equations on the previous pages.
- Some new buses route data from pipeline registers to the new muxes.

Example


```
sub    $2, $1, $3
and    $12, $2, $5
or     $13, $6, $2
add    $14, $2, $2
sw     $15, 100($2)
```

- Assume again each register initially contains its number plus 100.
 - After the first instruction, \$2 should contain -2 (101 - 103).
 - The other instructions should all use -2 as one of their operands.
- We'll try to keep the example short.
 - Assume no forwarding is needed except for register \$2.
 - We'll skip the first two cycles, since they're the same as before.


Clock cycle 3

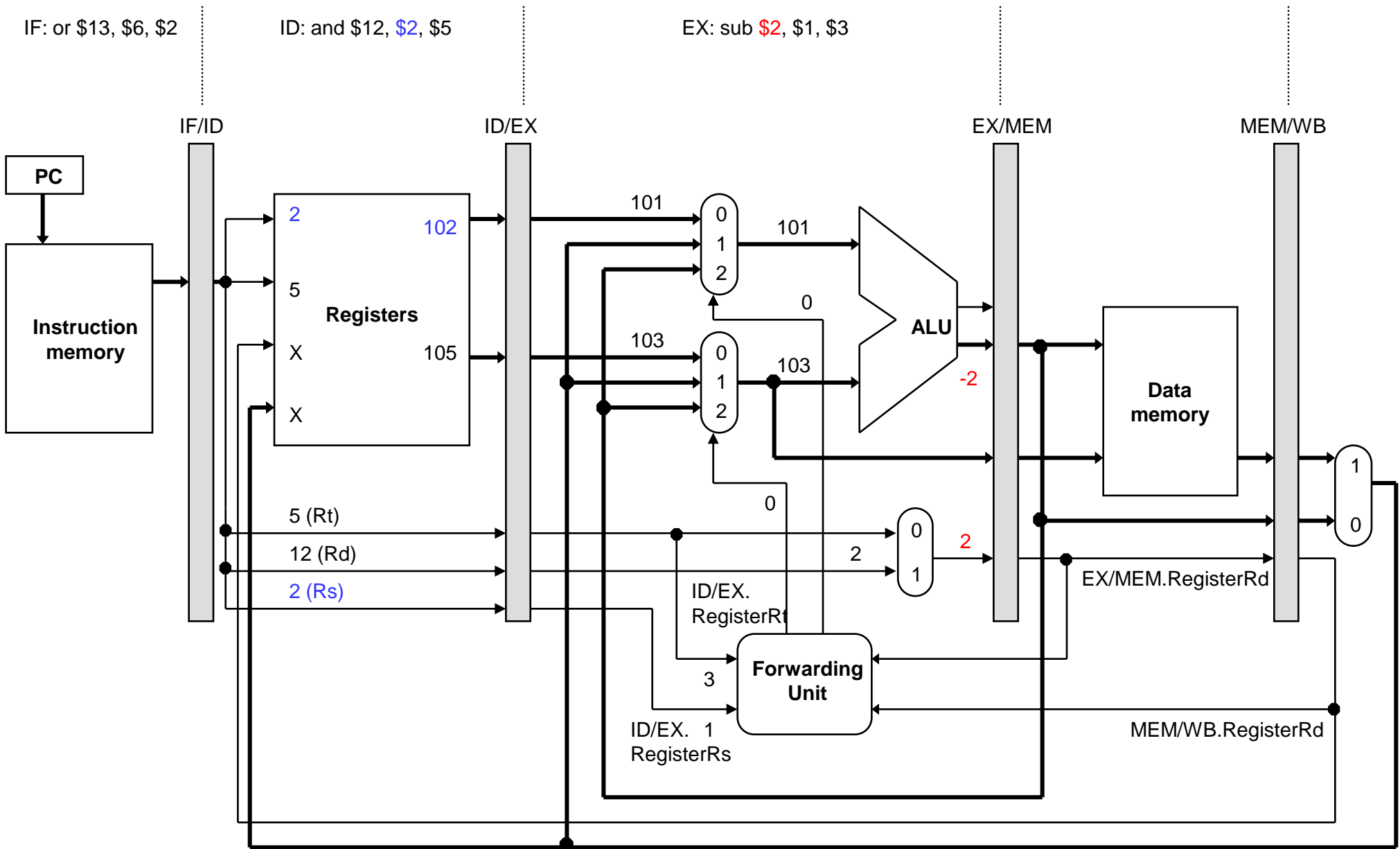

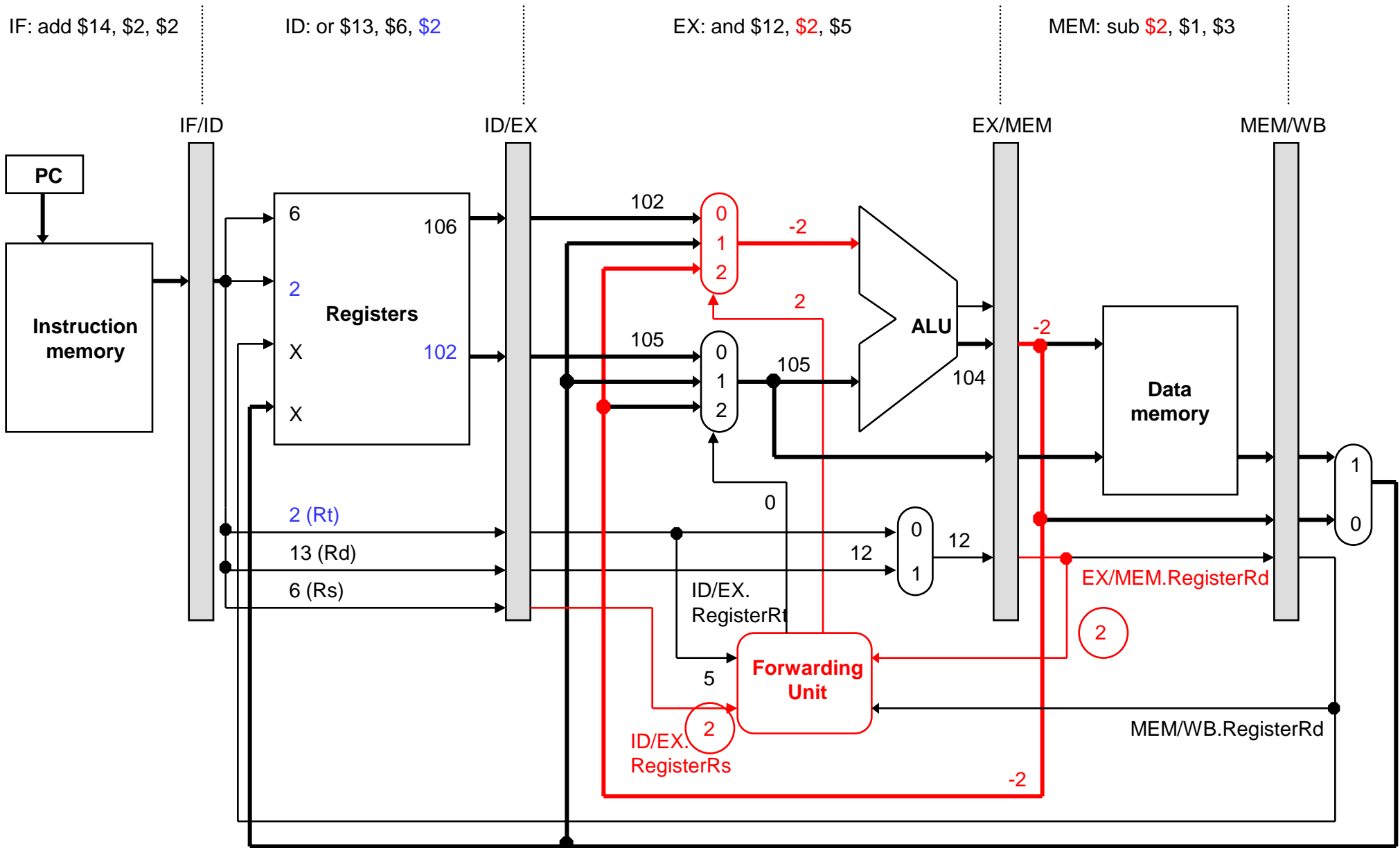Clock cycle 4: forwarding \$2 from EX/MEM



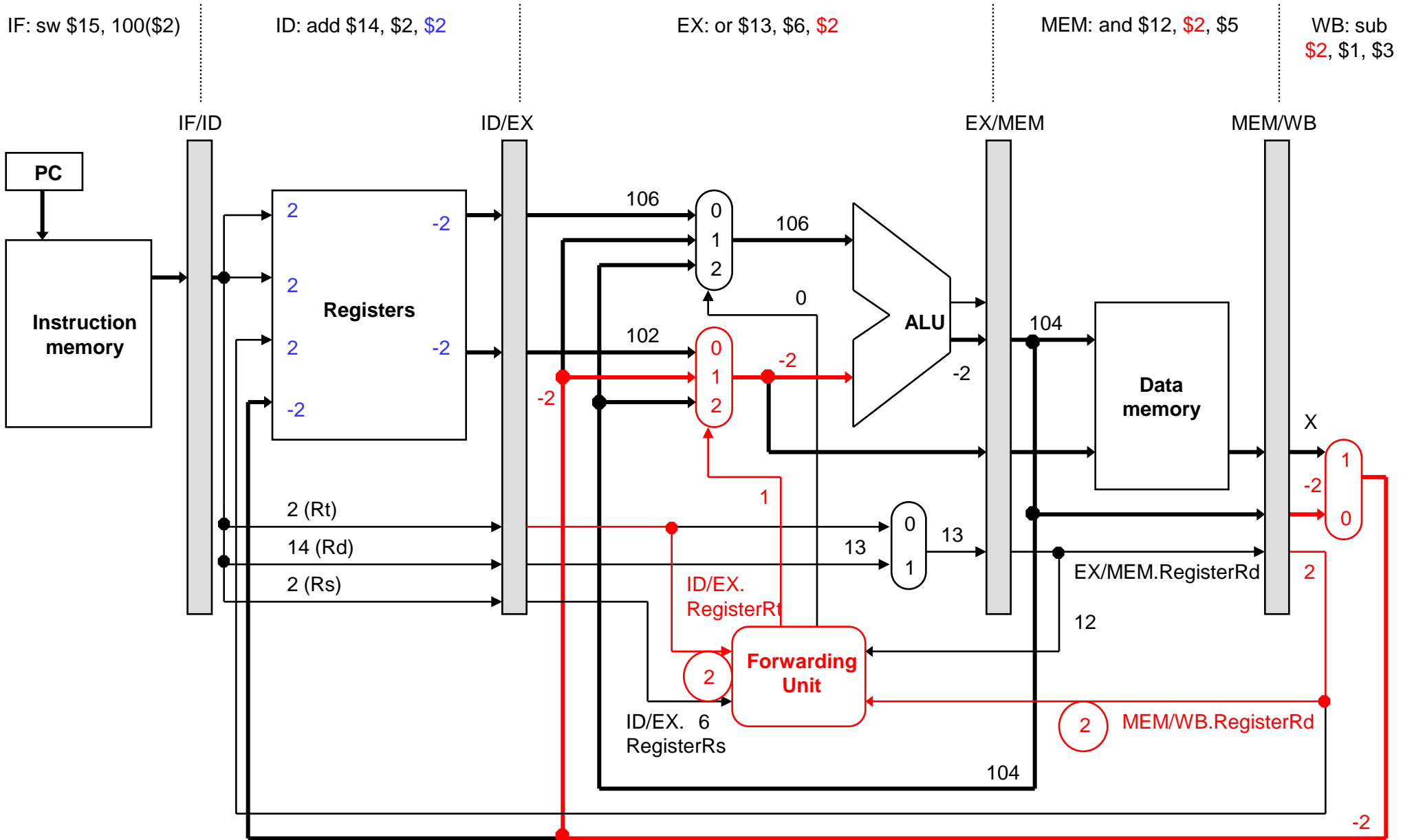
Clock cycle 5: forwarding \$2 from MEM/WB



Lots of data hazards



- The first data hazard occurs during cycle 4.
 - The forwarding unit notices that the ALU's first source register for the AND is also the destination of the SUB instruction.
 - The correct value is forwarded from the EX/MEM register, overriding the incorrect old value still in the register file.
- A second hazard occurs during clock cycle 5.
 - The ALU's second source (for OR) is the SUB destination again.
 - This time, the value has to be forwarded from the MEM/WB pipeline register instead.
- There are no other hazards involving the SUB instruction.
 - During cycle 5, SUB writes its result back into register \$2.
 - The ADD instruction can read this new value from the register file in the same cycle.

Complete pipelined datapath...so far

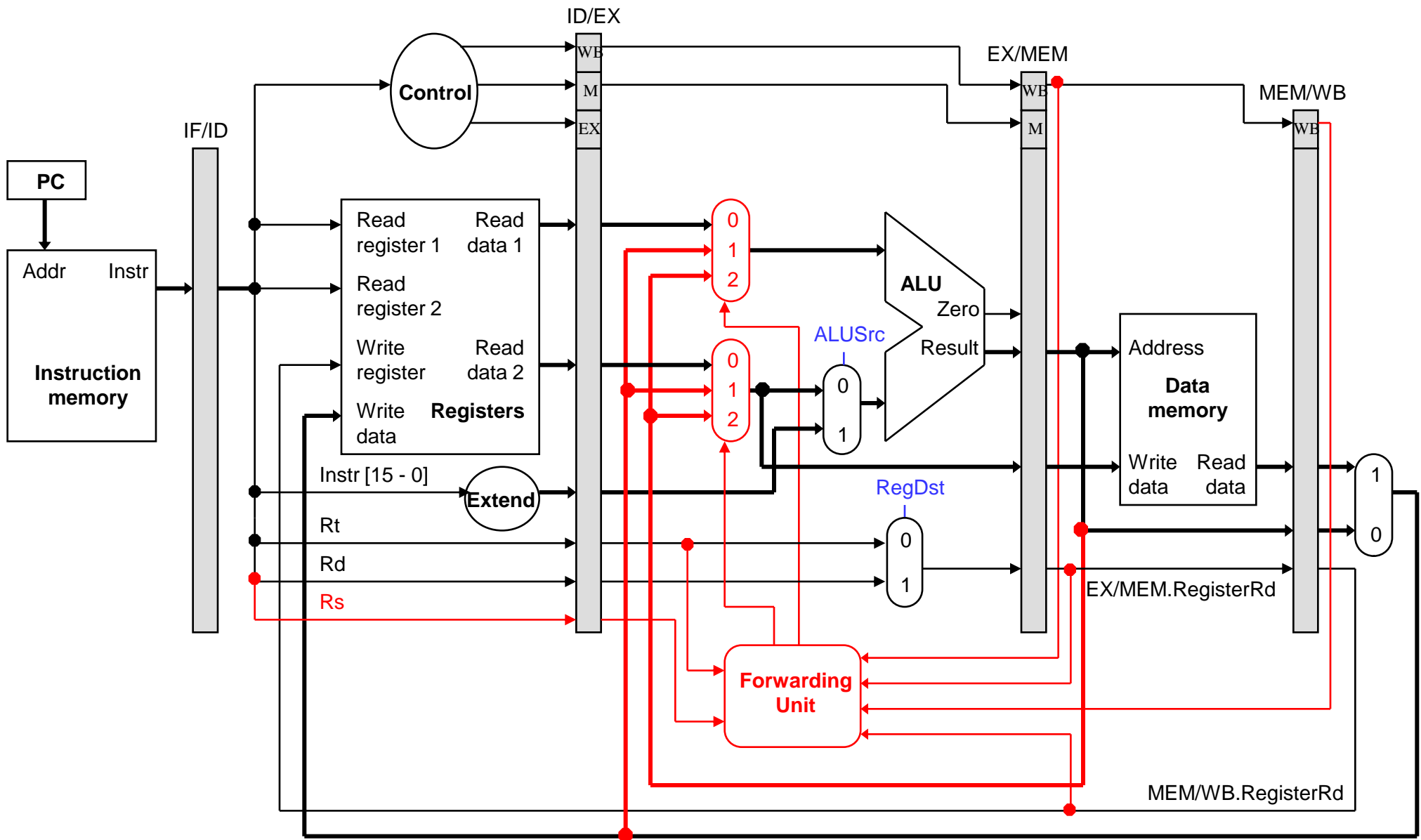


What about stores?


- Two “easy” cases:

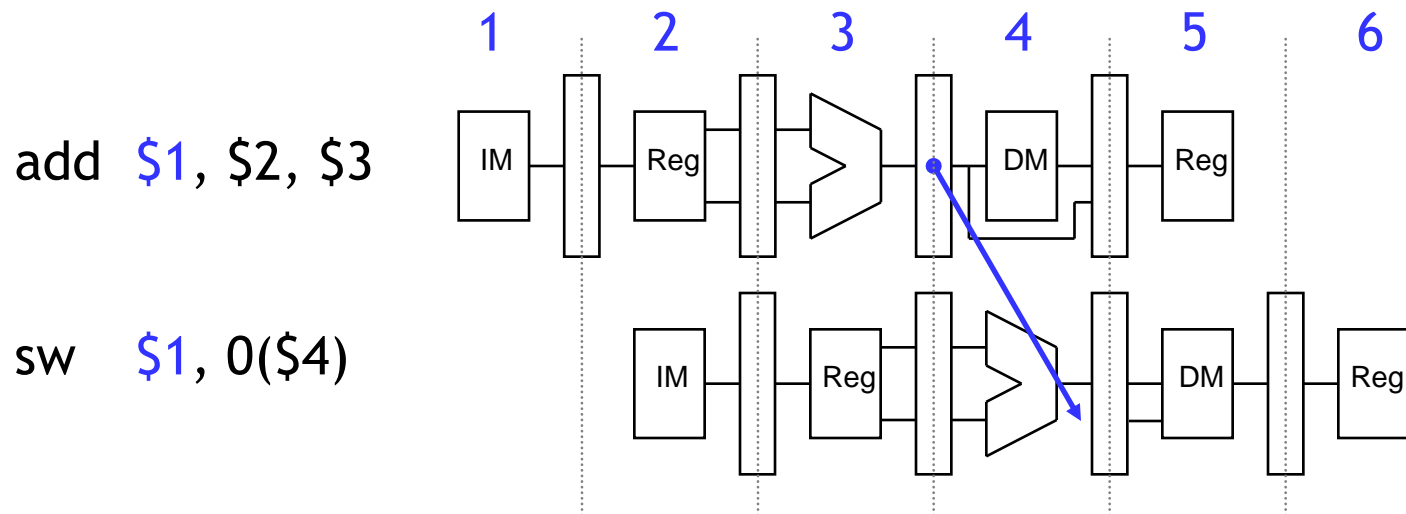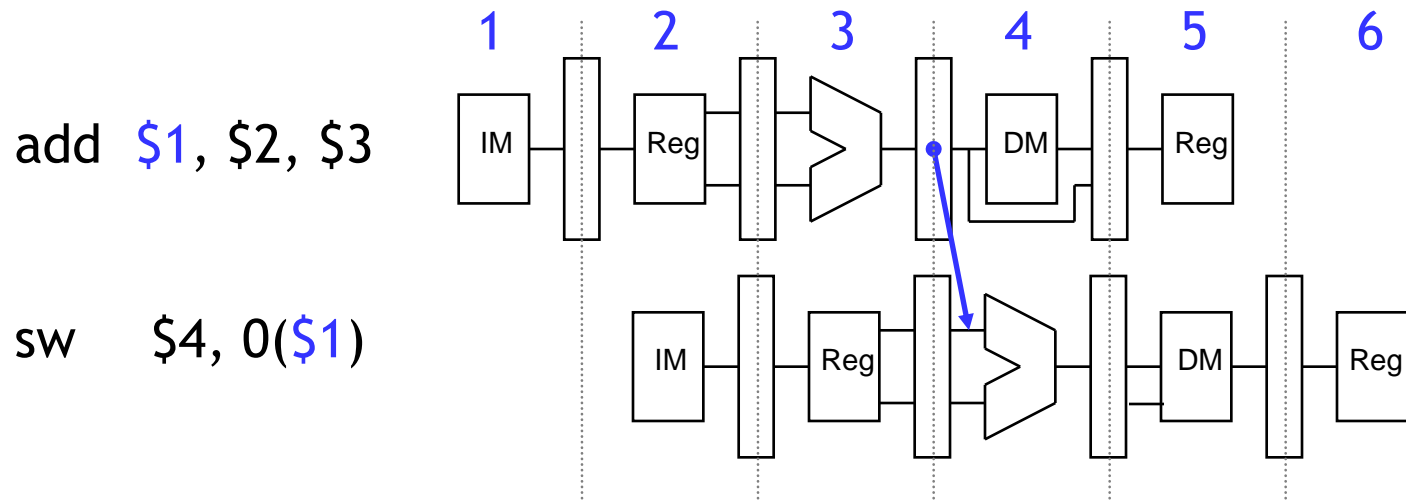

Store Bypassing: Version 1

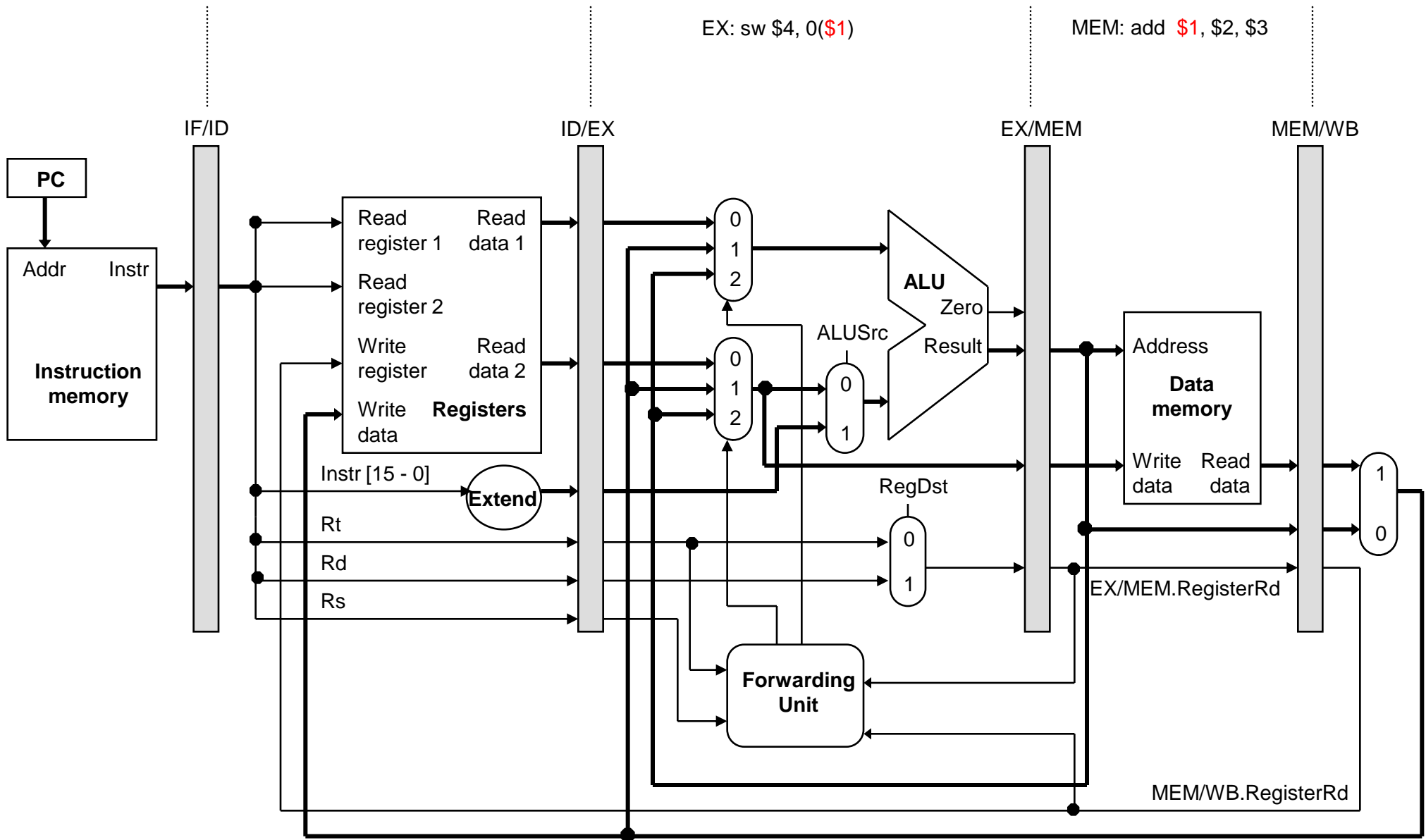


Store Bypassing: Version 2

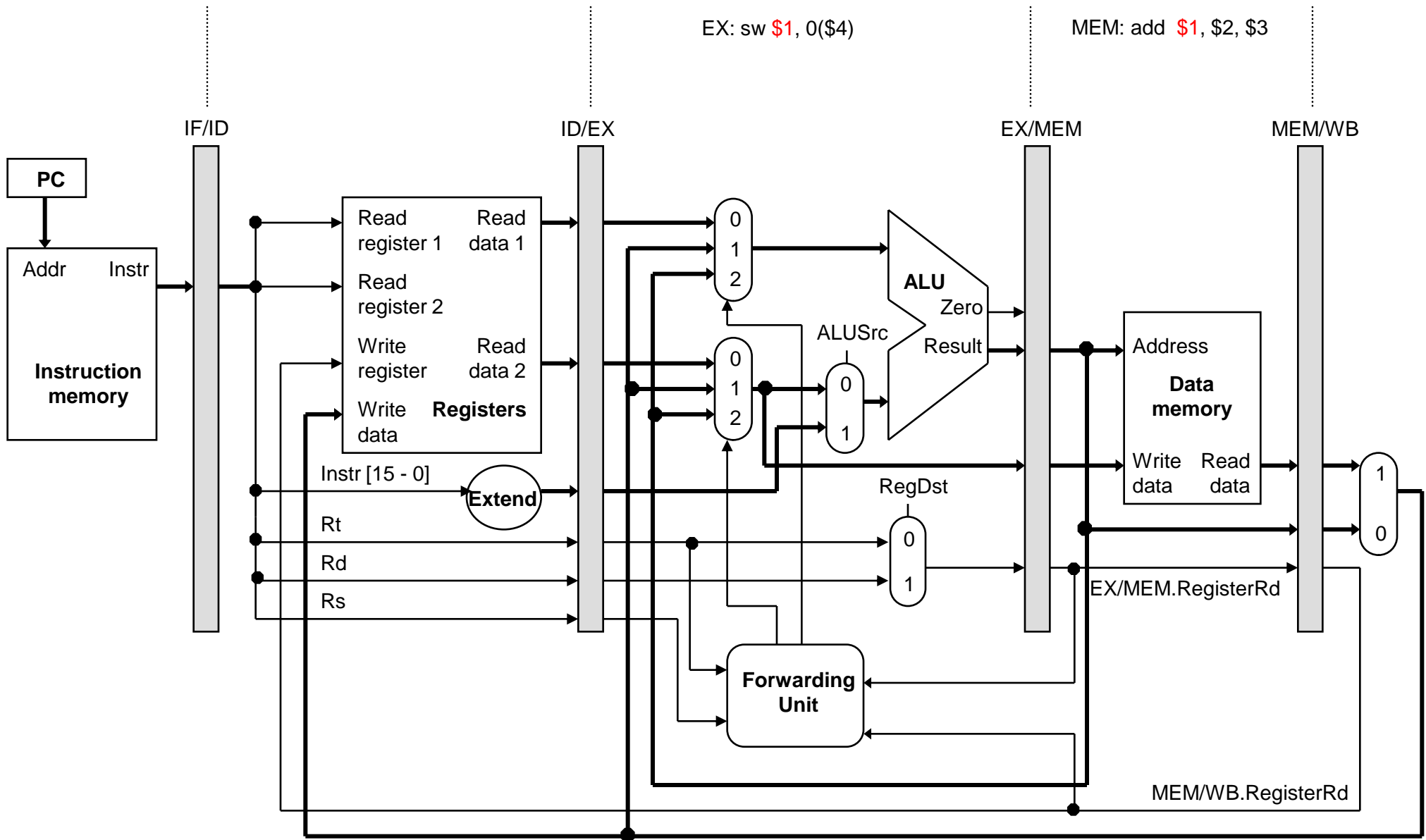


What about stores?

- A harder case:

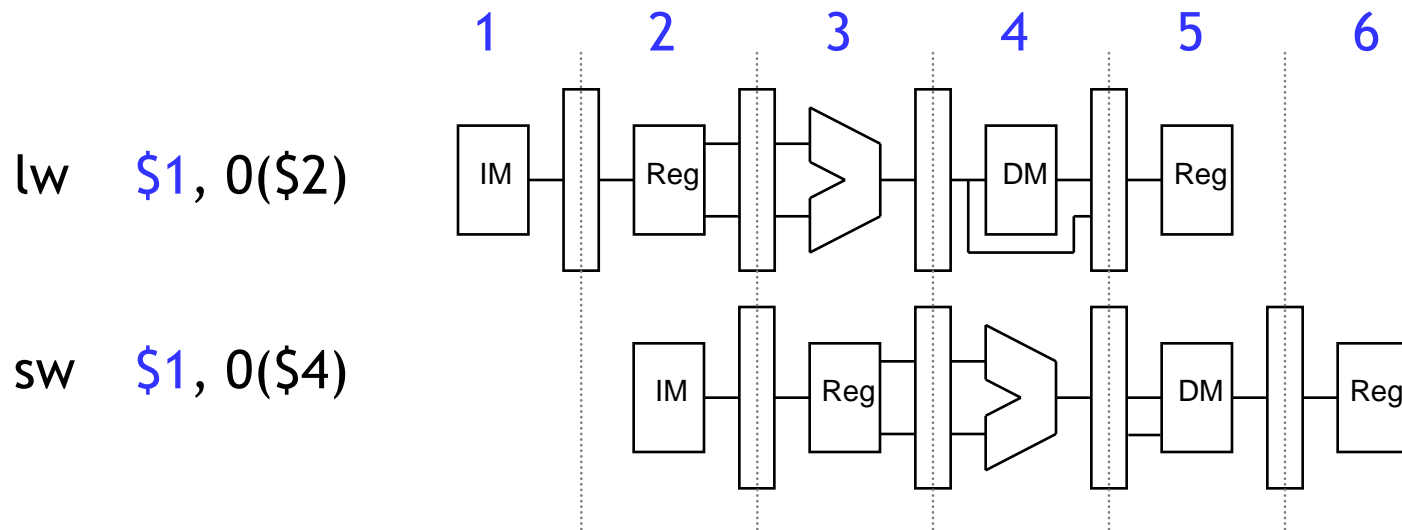

- In what cycle is:
 - The load value available?
 - The store value needed?
- What do we have to add to the datapath? (handout)

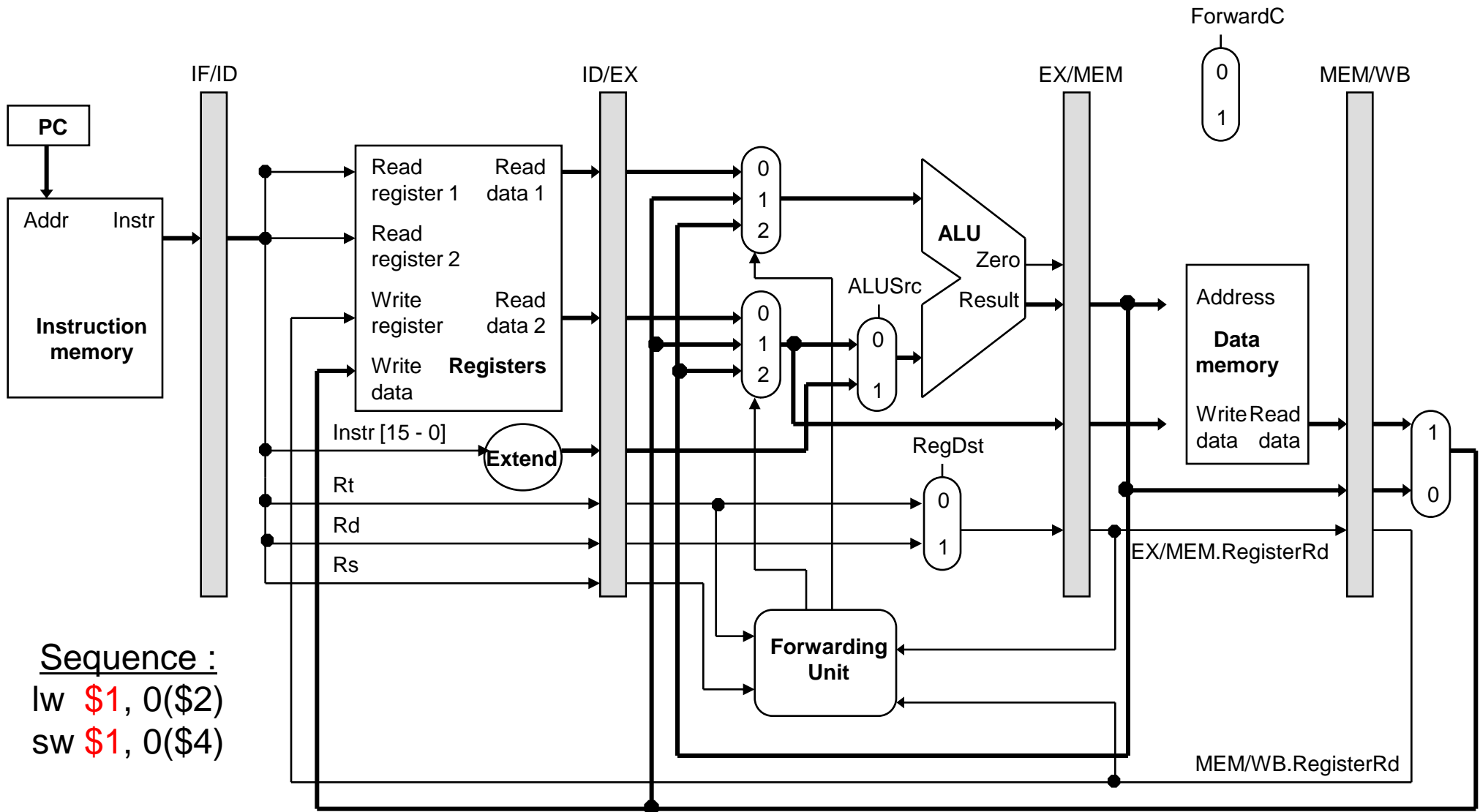Load/Store Bypassing: Extend the Datapath



Miscellaneous comments

- Each MIPS instruction writes to at most one register.
 - This makes the forwarding hardware easier to design, since there is only one destination register that ever needs to be forwarded.
- Forwarding is especially important with deep pipelines like the ones in all current PC processors.
- Section 6.4 of the textbook has some additional material not shown here.
 - Their hazard detection equations also ensure that the source register is not \$0, which can never be modified.
 - There is a more complex example of forwarding, with several cases covered. Take a look at it!

Summary

- In real code, most instructions are dependent upon other ones.
 - This can lead to **data hazards** in our original pipelined datapath.
 - Instructions can't write back to the register file soon enough for the next two instructions to read.
- **Forwarding** eliminates data hazards involving arithmetic instructions.
 - The forwarding unit detects hazards by comparing the destination registers of previous instructions to the source registers of the current instruction.
 - Hazards are avoided by grabbing results from the pipeline registers *before* they are written back to the register file.
- Next, we'll finish up pipelining.
 - Forwarding can't save us in some cases involving lw.
 - We still haven't talked about branches for the pipelined datapath.

