

CSE 390 B Spring 2021

# Sequential Logic & Bloom's Taxonomy

Project 1 Reflection, Introduction to Bloom's Taxonomy,  
Cornell Note-Taking, Continuation of Circuit Design, &  
Physical Timekeeping



# Agenda

- ❖ **Project 1 Reflection**
- ❖ Bloom's Taxonomy
- ❖ Cornell Note-Taking Method
- ❖ Representing Time in Hardware
- ❖ Sequential Logic


# Project 1 Discussion

- ❖ What was the most frustrating or difficult part of the Boolean Logic assignment?
- ❖ What tools, questions, strategies did you utilize to persist through the assignment?
- ❖ What discrepancy did you have between your *estimated* time to complete the assignment and your *actual* time? Why?


# Agenda

- ❖ Project 1 Reflection
- ❖ **Bloom's Taxonomy**
- ❖ Cornell Note-Taking Method
- ❖ Representing Time in Hardware
- ❖ Sequential Logic

# Bloom's Taxonomy

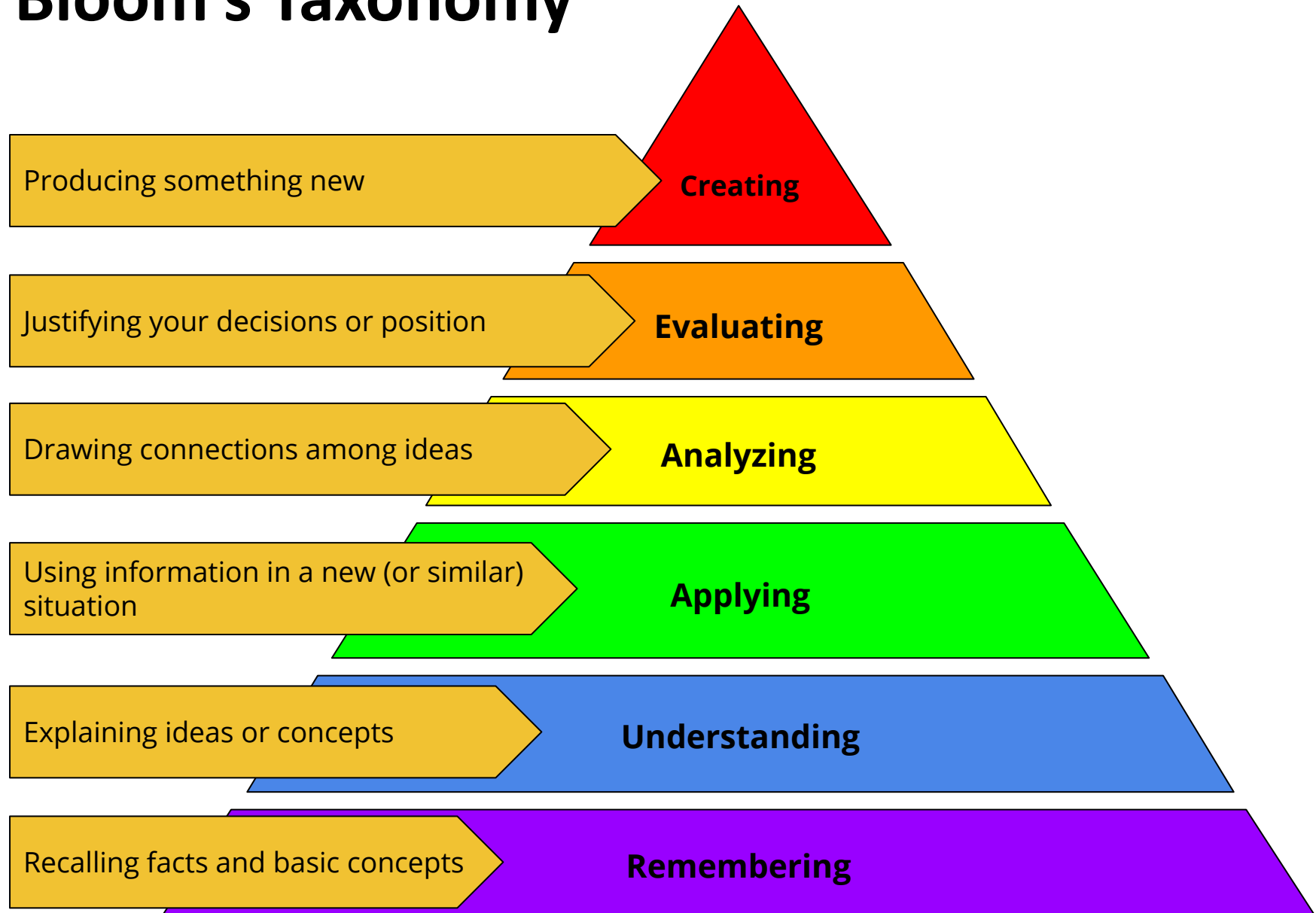

# Bloom's Taxonomy in Action

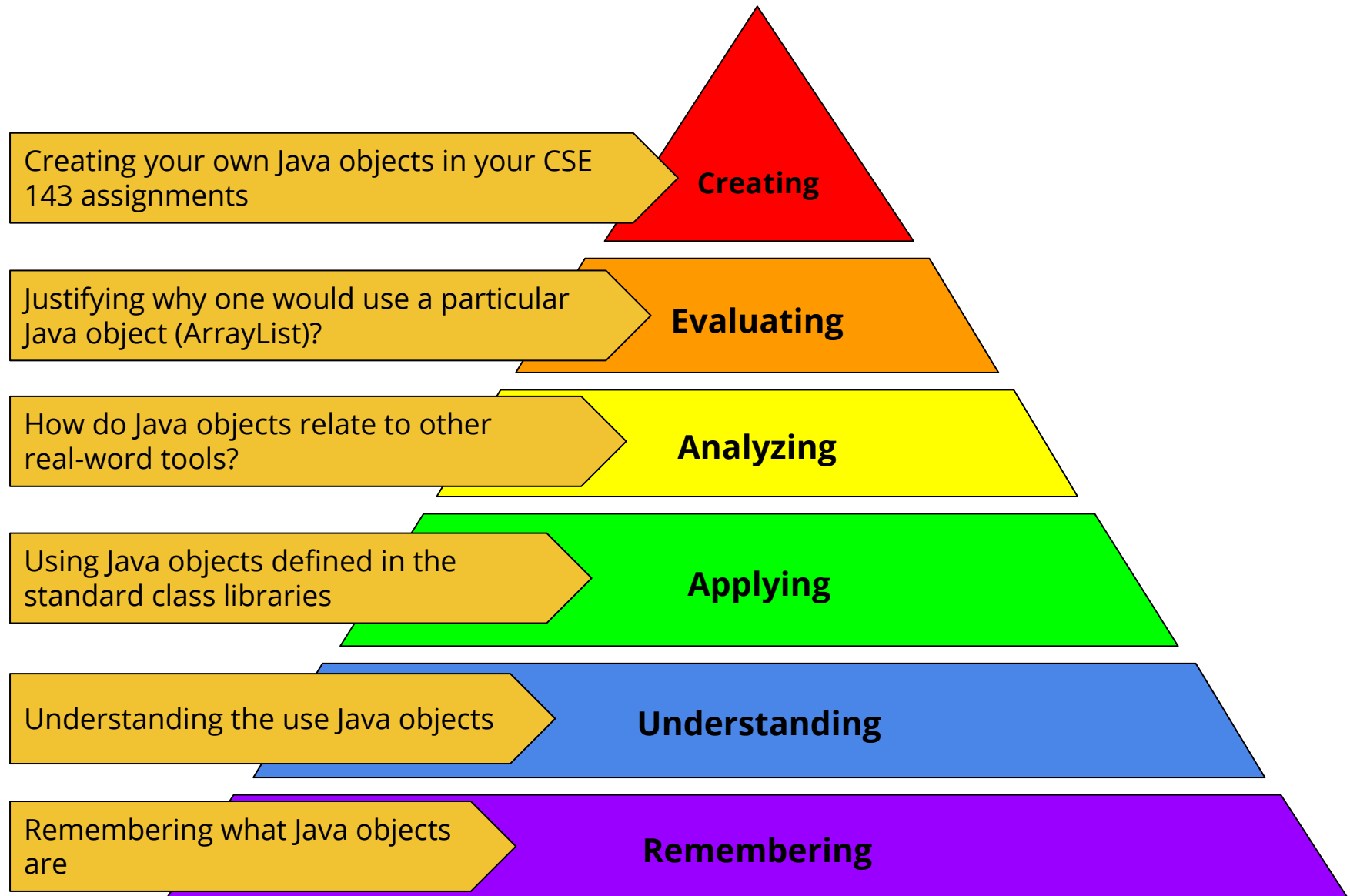


# Agenda

- ❖ Project 1 Reflection
- ❖ Bloom's Taxonomy
- ❖ **Cornell Note-Taking Method**
- ❖ Representing Time in Hardware
- ❖ Sequential Logic

# Cornell Note-Taking Method

Questions	Notes
Compose a question that corresponds to the notes you took	I. Main Topic <ul style="list-style-type: none"><li>○ Sub point</li><li>○ <u>definition</u></li><li>○ example **</li></ul>
In what ways is object-oriented programming more extensible than functional programming?	II. Object-Oriented Programming <ul style="list-style-type: none"><li>○ Encapsulates the data and the operations for a given data type</li><li>○ Provides abstractions - you don't need to know how a car is implemented in order to use it</li><li>○ Extensibility - easier to <u>add new data types</u></li></ul>
	III. Functional Programming <ul style="list-style-type: none"><li>○ Extensibility - easier to <u>add new operations</u></li></ul>
<hr/> <b>Summary</b>	
Object-oriented programming and functional programming are two types of programming paradigms...	

# Cornell Note-Taking Method

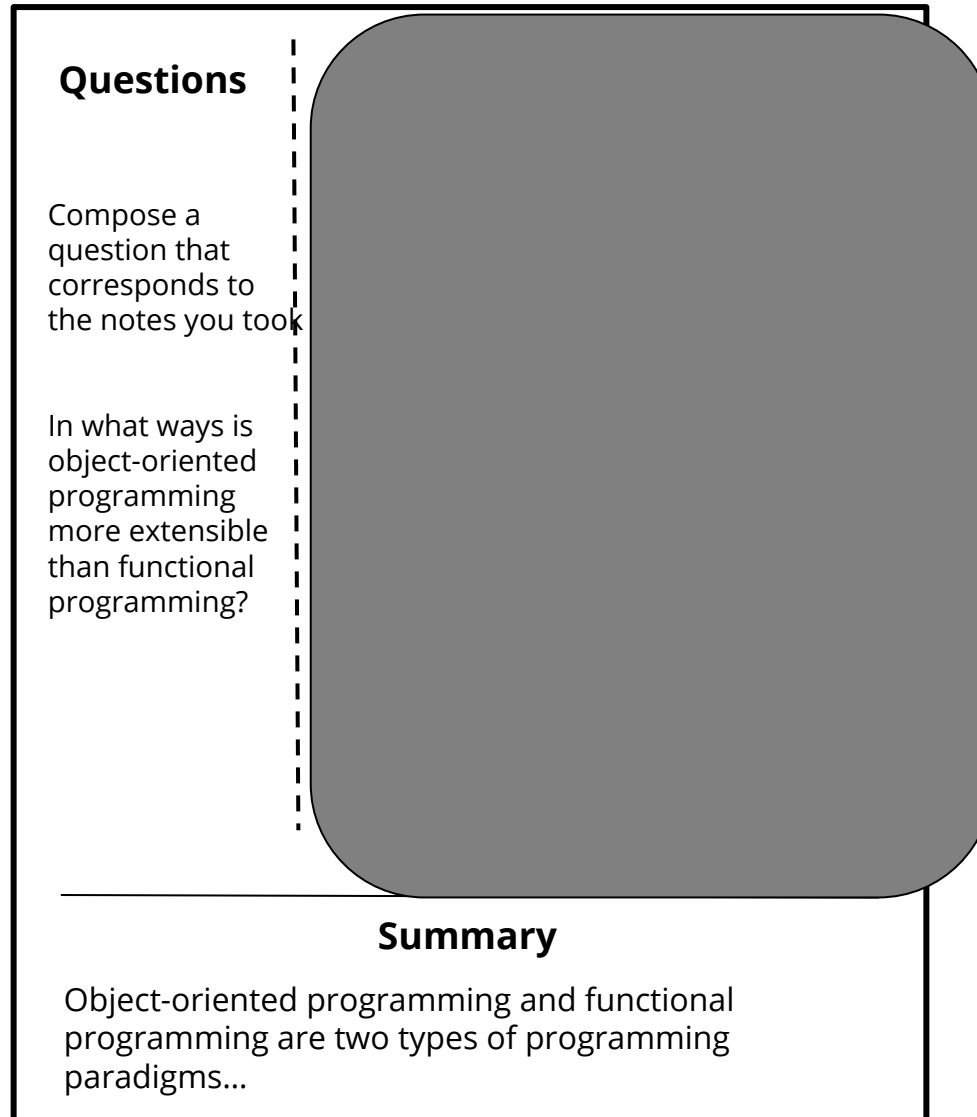

# Applying the Cornell Note-Taking Method

- ❖ You are going to try it... TODAY!
- ❖ Thursday you will come & contrast cornell notes with your classmates
- ❖ You are also going to try it with one of your other classes as part of Project 3 (more on Thursday)

# Agenda


- ❖ Project 1 Reflection
- ❖ Bloom's Taxonomy
- ❖ Cornell Note-Taking Method
- ❖ **Representing Time in Hardware**
- ❖ Sequential Logic

# Combinational Logic vs. Sequential Logic

- So far, we ignored “time” in our circuits
- Our chips use **combinational logic**
  - When given inputs, the chip computes its output “instantaneously”
  - The output is a pure function of the current inputs, no memory of previous events
- Today, we’ll start exploring what happens when we consider time, ultimately building to **sequential logic**
 
# Why Consider Time Now?

- Needed for Our Abstraction:
  - For memory, we need to talk about hardware maintaining state. To do so, we need a vocabulary to talk about time.
- Needed for Implementation:
  - Physical implementations of chips **cannot be instantaneous**. We need to account for physical delays in signal propagation.




# Physical Timekeeping

- In hardware, keep track of time with an alternating signal
  - Creates idea of **discrete time** -- state changes only occur in discrete intervals, right when signal alternates



 
# Physical Timekeeping

- In hardware, keep track of time with an alternating signal
  - Creates idea of **discrete time** -- state changes only occur in discrete intervals, right when signal alternates



 
# Adding a Clock: Ideal

- We want this behavior from a simple, combinational Not gate:



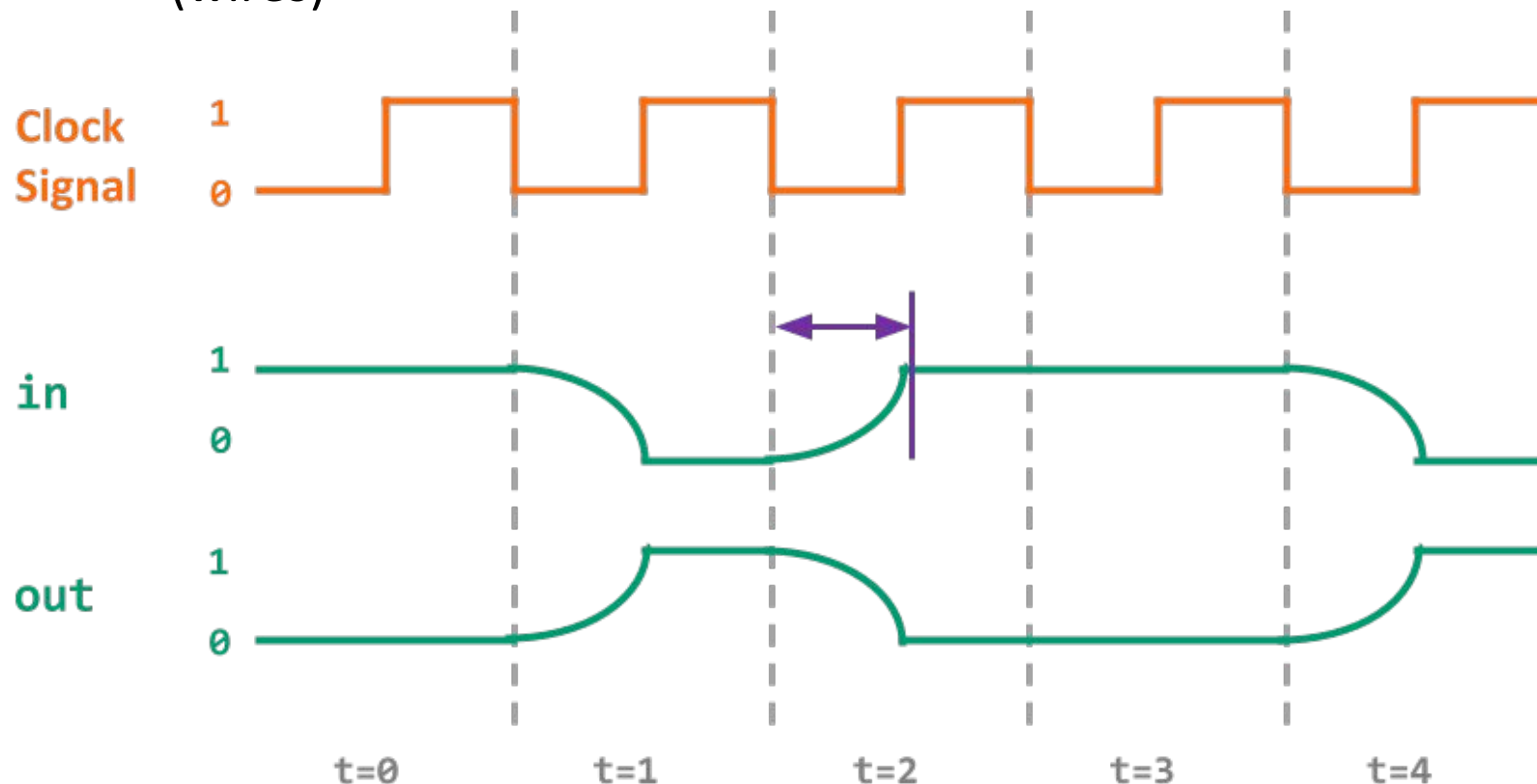
# Adding a Clock: Reality

- Combinational logic may be incorrect for a period immediately after inputs change
  - **computation delays** (logic gates) and **propagation delays** (wires)



 
# Adding a Clock: Clock Cycles

Choose a clock cycle length slightly longer than the delays



 
# Adding a Clock: Abstraction

- If we use a long enough clock cycle, we can *pretend* that combinational chips (like Not) work instantly



 
# Combinational vs. Sequential Abstraction



**Combinational:** a function of the inputs from the current time cycle



 **Sequential:** a function of inputs from the previous cycle (has “memory”)




# Agenda


- ❖ Project 1 Reflection
- ❖ Bloom's Taxonomy
- ❖ Cornell Note-Taking Method
- ❖ Representing Time in Hardware
- ❖ **Sequential Logic**
 
# A New Primitive: Flip Flop

- Simplest state-keeping component
  - 1-bit input, 1-bit output
  - Wired to the clock signal
  - Always outputs its previous input:  $out(t) = in(t-1)$
- Implementation: a gate that can flip between two stable states (remembering 0 vs. remembering 1)
  - Gates with this behavior are “Data Flip Flops”



# Flip-Flop Time Series

 

pin	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...
in	0	0	1	1	0	1	0	...
out	0	0	0	1	1	0	1	...

Example:

$$\text{out}(t=3) = \text{in}(t=2)$$

# Aside: Treating Flip-Flop as Primitive


- Disclaimer: CAN be made from Nand gates exclusively!
  - BUT requires wiring them together in a “messy” loop that the hardware simulator can't simulate and isn't very educational
- For simplicity, we'll treat Flip-Flop as primitive in homeworks
  - Just like Nand, you can use the built-in implementation

# Sequential Chips

- A category of chips that utilize the clock signal, in addition to any combinational logic
- Capable of:
  - Maintaining state
  - Optionally, acting on that state & current inputs
    - Can incorporate combinational logic as well!
- Constructed from:
  - DFFs
  - Combinational logic (which is entirely constructed from Nand)
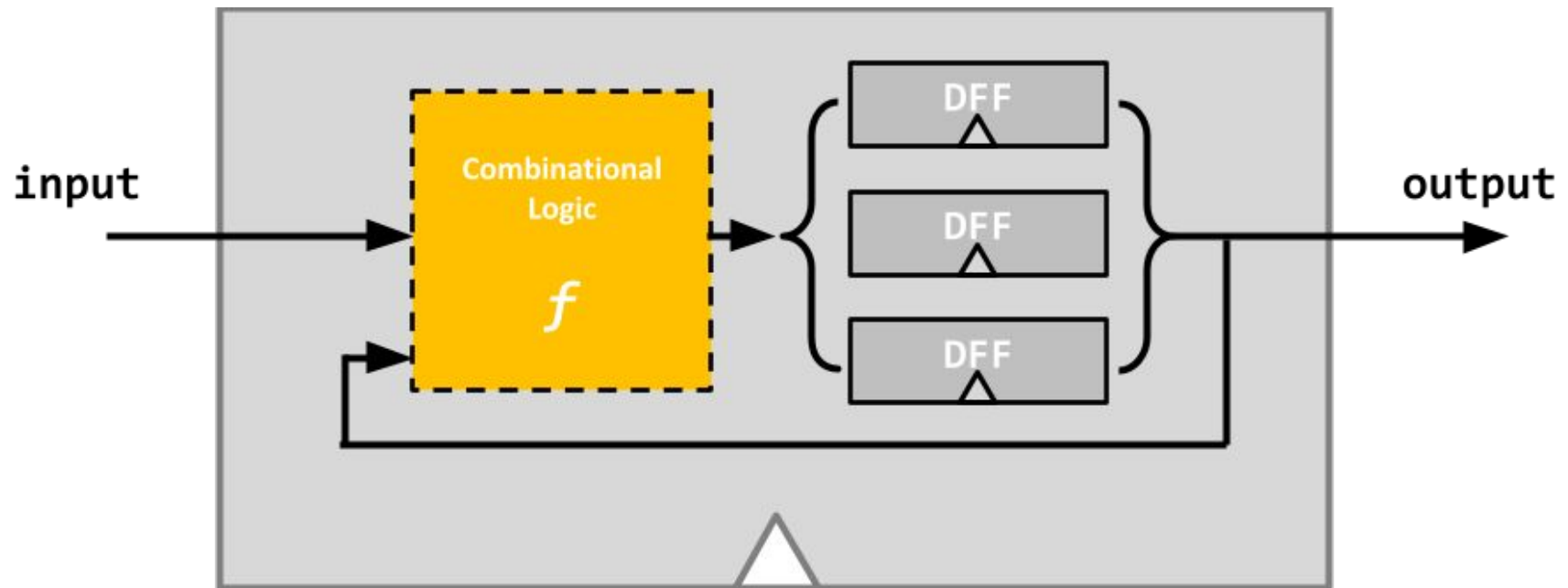
# Sequential Chips

$$\text{output}(t) = f(\text{state}(t-1), \text{input}(t-1))$$



# DFF Example 1 Specification

- Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$


- Takes two inputs, a and b, and outputs the Xor of them
  - Note that out at time t is determined by a and b at time t-1
  - We will need to use a DFF!

# DFF Example 1 Circuit Diagram


- Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

- Circuit diagram:

 

# DFF Example 1 Time Series

 


pin	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...
a	0	0	1	1	1	0	0	...
b	0	1	0	1	1	1	0	...
out	0	0	1	1	0	0	1	...

Example:

$$\text{out}(t=3) = \text{Xor}(a(t=2), b(t=2))$$

# DFF Example 1 HDL Implementation

 

```
CHIP Example1 {
```

```
  IN a, b;
```

```
  OUT out;
```

```
  PARTS :
```

```
  Xor(a=a, b=b, out=xorout);
```

```
  DFF(in=xorout, out=out);
```

```
}
```

# DFF Example 2 Specification

- Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$


- Notice how the specification uses  $\text{out}(t-1)$  as an input for  $\text{out}(t)$ 
  - Need some sort of circular wiring, separated by a DFF

# DFF Example 2 Circuit Diagram


- Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- Circuit diagram:

 

# DFF Example 2 Time Series

 


pin	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...
in	0	0	1	1	1	0	0	...
out	0	0	0	1	0	1	1	...

Example:

$$\text{out}(t=1) = \text{Xor}(\text{in}(t=0), \text{out}(t=0))$$

# DFF Example 2 HDL Implementation

 

```
CHIP Example2 {
```

```
  IN in;
```

```
  OUT out;
```

```
  PARTS:
```

```
  Xor(a=in, b=prevout, out=xorout);
```

```
  DFF(in=xorout, out=prevout, out=out);
```

```
}
```

# DFF Example 3 Specification

- Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

# DFF Example 3 Time Series

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

pin	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...
in	1	1	0	1	1	0	0	...
out	0	1	0	0	1	0	0	...

Example:


$$\text{out}(t=1) = \text{And}(\text{Not}(\text{out}(t=0)), \text{in}(t=0))$$

# DFF Example 3 Circuit Diagram

- Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

- Circuit diagram:

 

# DFF Example 3 HDL Implementation

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

```
CHIP Example3 {
```

```
    IN in;
```

```
    OUT out;
```

```
    PARTS :
```

```
    Not(in=prevout, out=notprevout);
```

```
    And(a=in, b=notprevout, out=andout);
```

```
    DFF(in=andout, out=prevout, out=out);
```

```
}
```

# Reminders

- ❖ Project 2 is due Thursday 11:59PM PDT
- ❖ Margot and Eric have office hours NOW(!) 2:00 - 3:00PM on Tuesdays!
- ❖ Message board! Discord!