

CSE 390B, Autumn 2022

Building Academic Success Through Bottom-Up Computing

Test-taking Strategies & Midterm Practice Exam

Hack CPU Logic, Test-taking Strategies, Midterm Practice
Exam, Practice Exam Walkthrough and Rubric

Week 7 Announcements

- ❖ CSE 390B final is Tuesday of finals (12/13), 4:30-6:20pm
 - Please let the course staff know if you have a conflicting final

- ❖ Project reminders
 - First check specification and textbook when you have a question
 - Please avoid submitting a link on the project documents
 - Please assign problems to the pages when submitting the project document on Gradescope
 - Please find a time for the Project 6 mock exam problem and update [the spreadsheet](#) (if your group has not already)

- ❖ Andres' office hours now on Mondays from 3:30-4:30pm
 - Location: CSE2 153

Lecture Outline

❖ Hack CPU Logic

- Implementation and Operations

❖ Test-taking Strategies

- Maximizing Success on Exam Day


❖ Midterm Practice Exam

- Mock Exam, Debrief, and Reflection

❖ Practice Exam Solutions and Rubric


- Walkthrough of Solutions and Exploring Sample Rubrics

Hack CPU

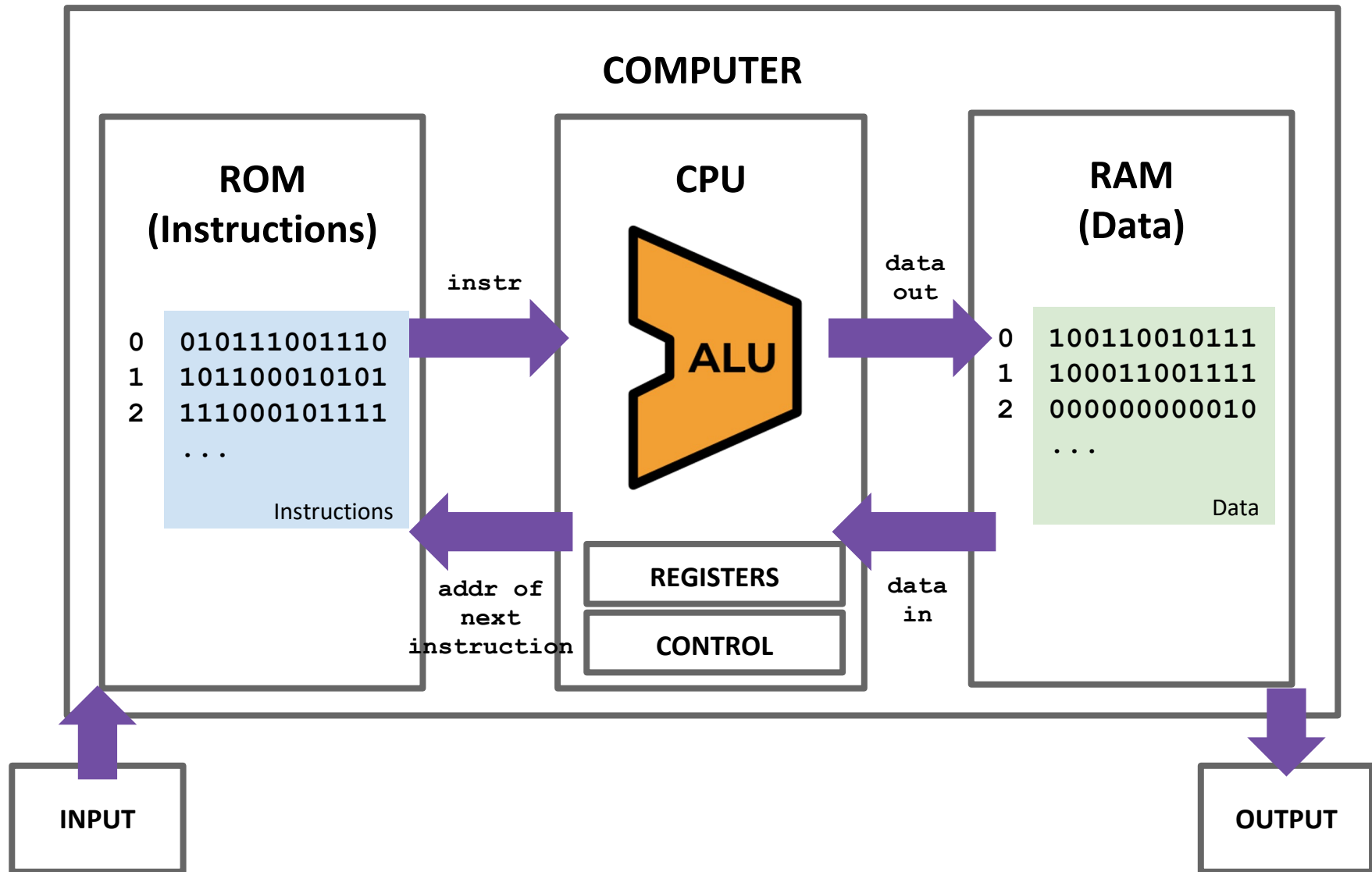


Hack CPU Interface Inputs

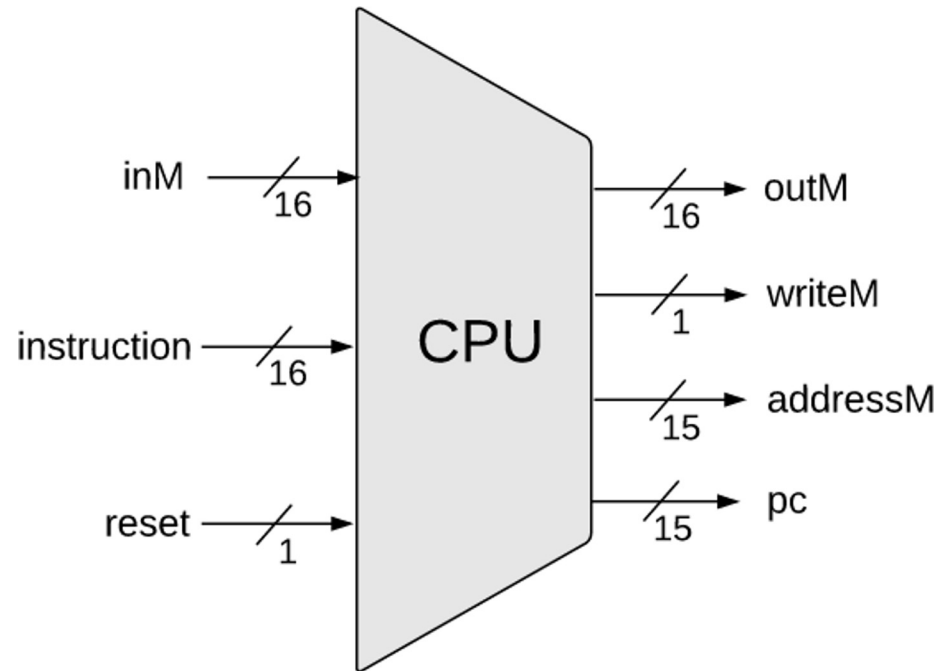- ❖ **inM**: Value coming from memory
- ❖ **instruction**: 16-bit instruction
- ❖ **reset**: if 1, reset the program




Hack CPU Interface Outputs

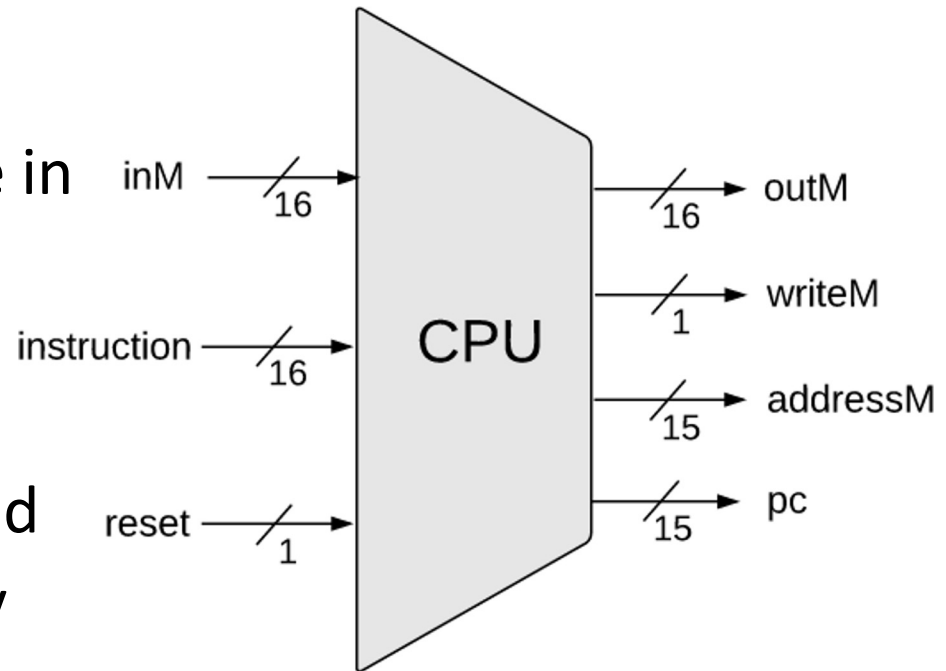
- ❖ **outM**: value used to update memory if writeM is 1
- ❖ **writeM**: if 1, update value in memory at addressM with outM
- ❖ **addressM**: address to read from or write to in memory
- ❖ **pc**: address of next instruction to be fetched from memory



Hack CPU Implementation

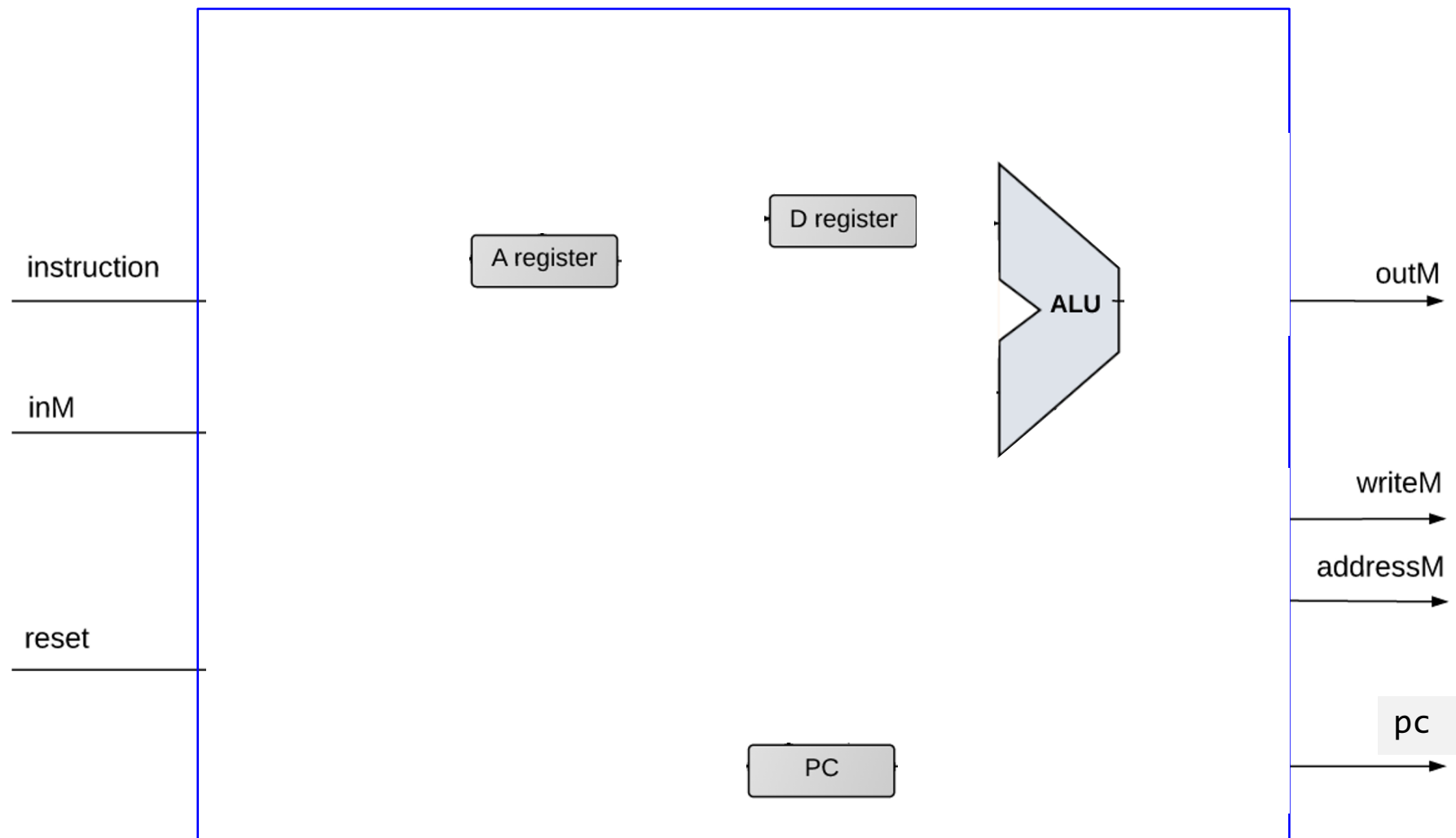


Hack CPU Implementation

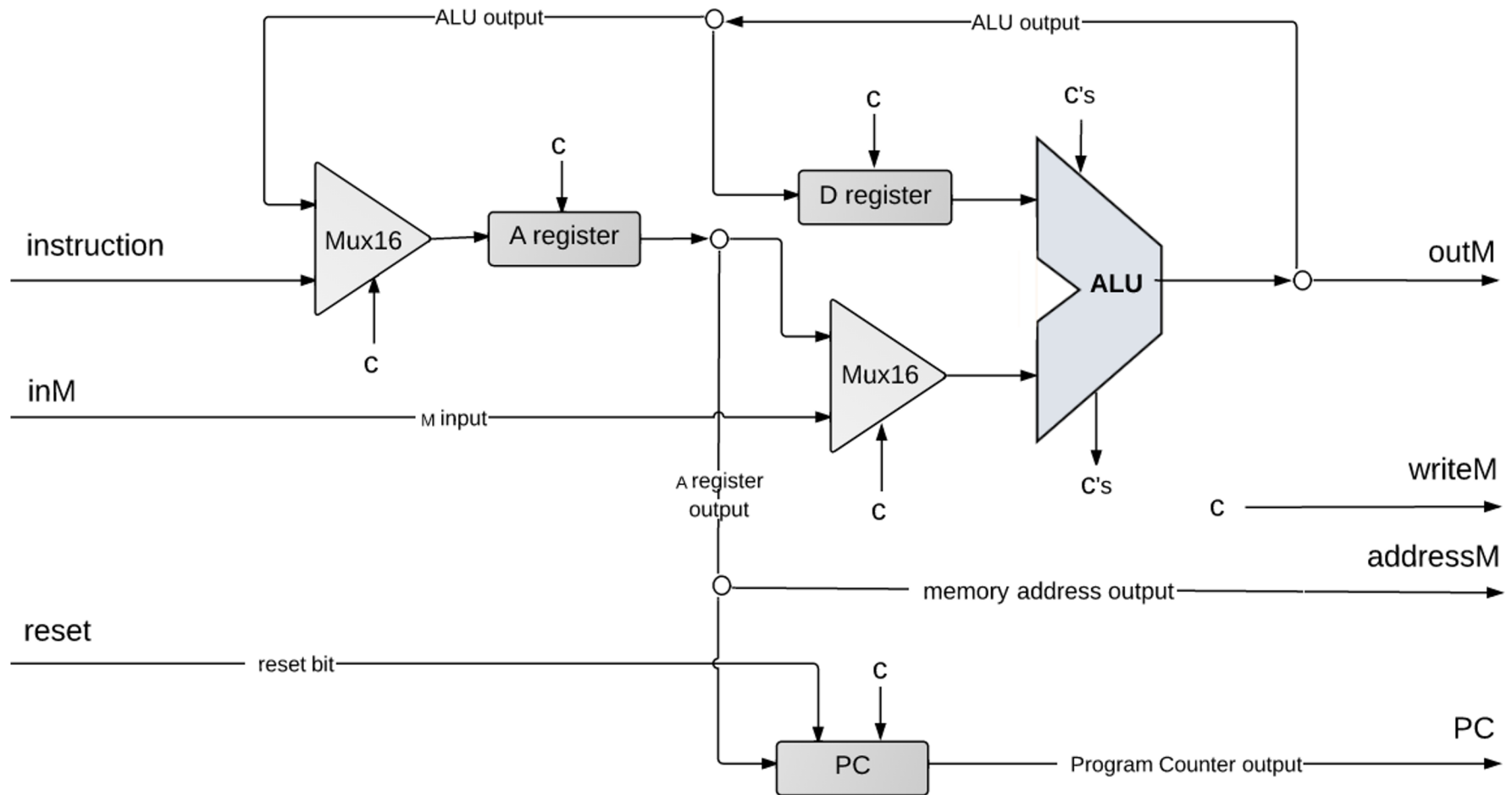


(each "c" symbol represents a control bit)

CPU Operation: Instruction Handling

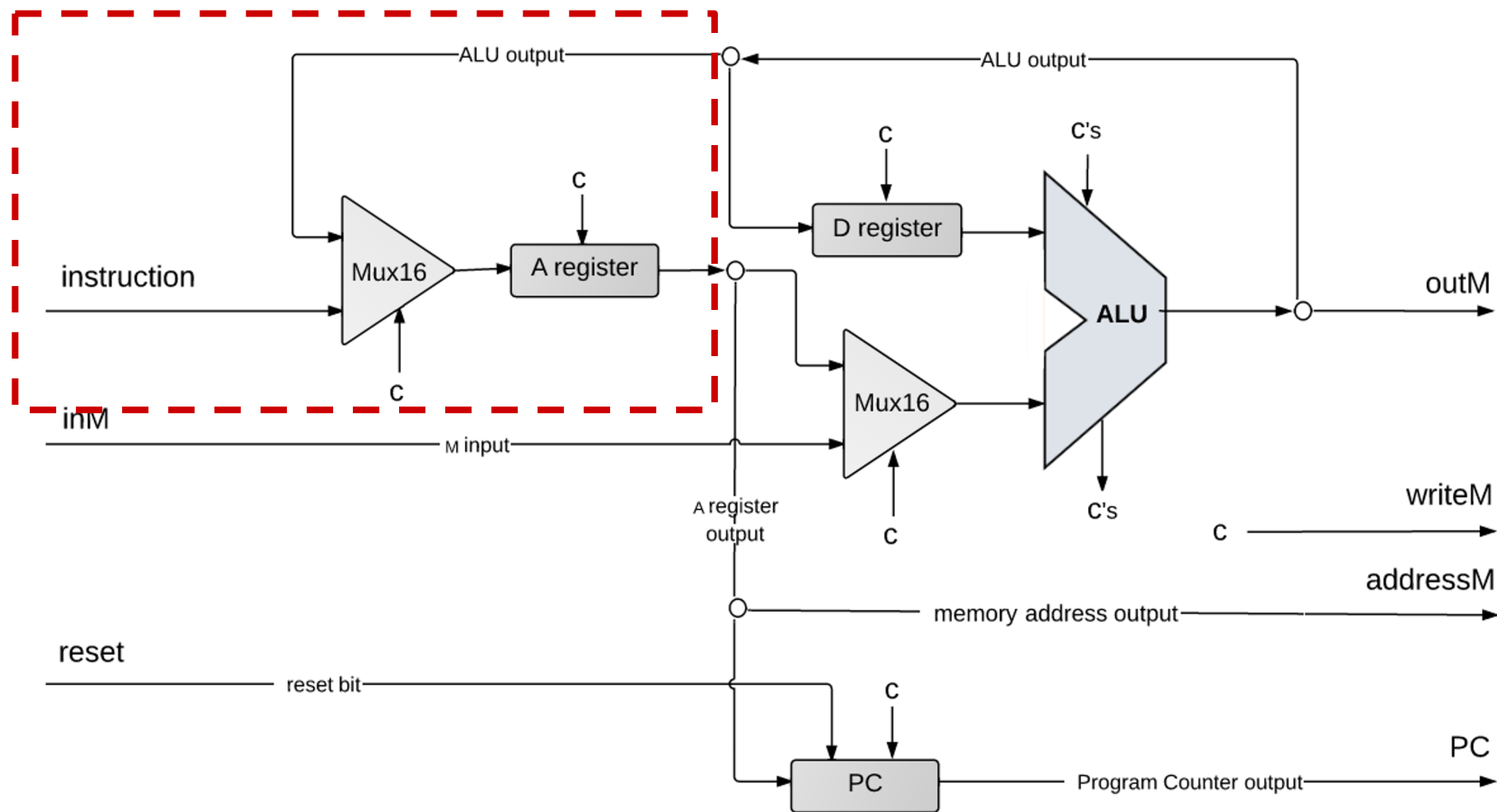


(each "c" symbol represents a control bit)

CPU Operation: Instruction Handling

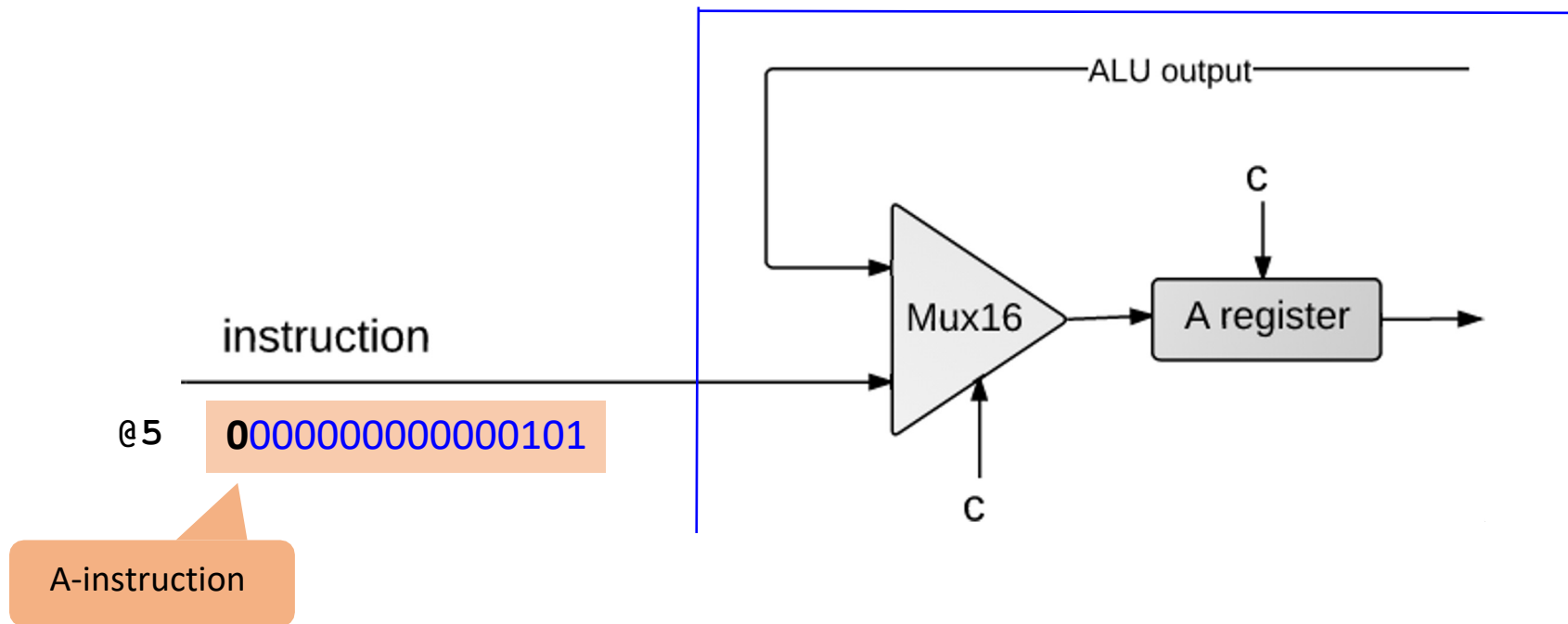


CPU Operation: Instruction Handling

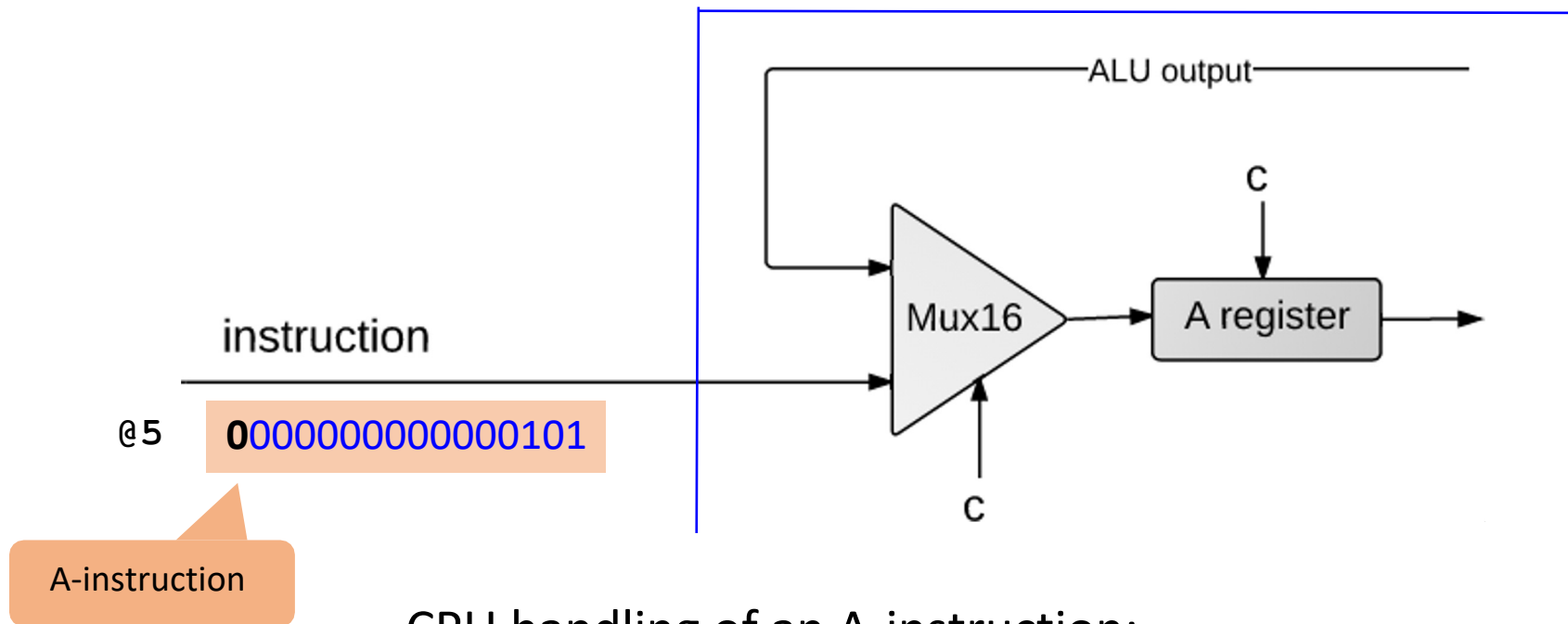

CPU handling of an A-instruction:

- ❖ Decodes the instruction into:
 - op-code
 - 15-bit value
- ❖ Stores the value in the A-register
- ❖ Outputs the value (not shown in this diagram)

CPU Operation: Instruction Handling

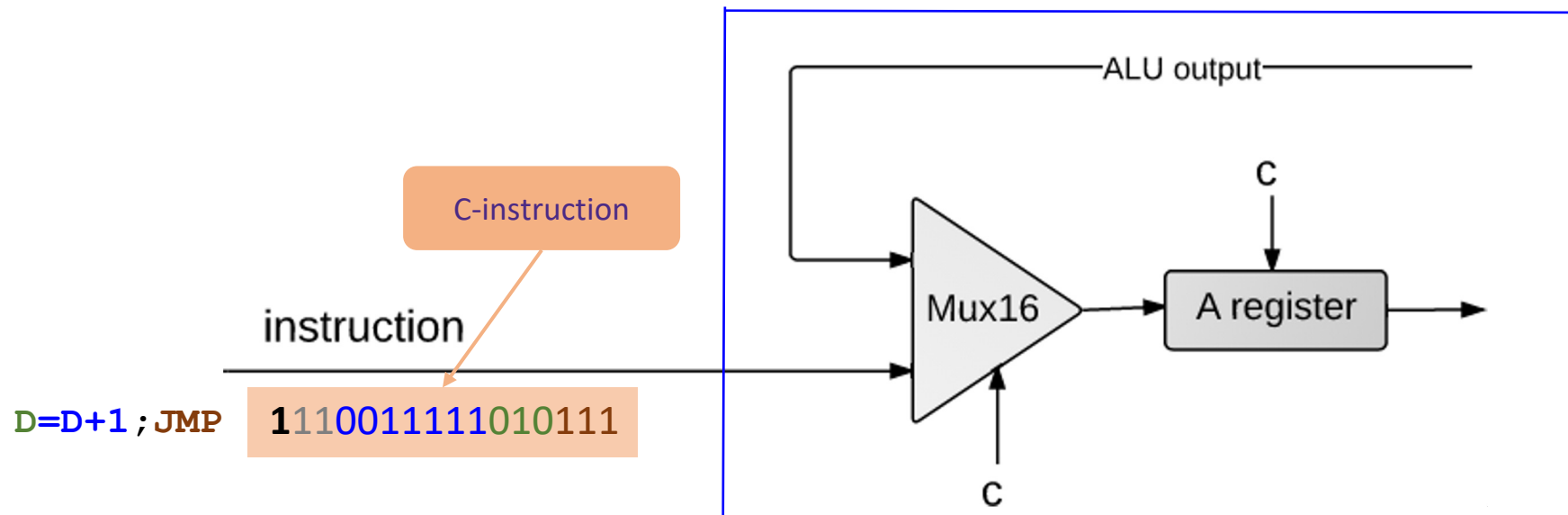

Hack: C-Instructions

❖ Symbolic: `dest = comp ; jump`

❖ Binary: 1 1 1 a c1 c2 c3 c4 c5 c6 d1 d2 d3 j1 j2 j3

Family:
C-Instruction


Unused

Comp:
ALU Operation (a bit chooses
between A and M)

Dest:
Where to store
result

Jump:
Condition for
jumping

CPU Operation: Instruction Handling

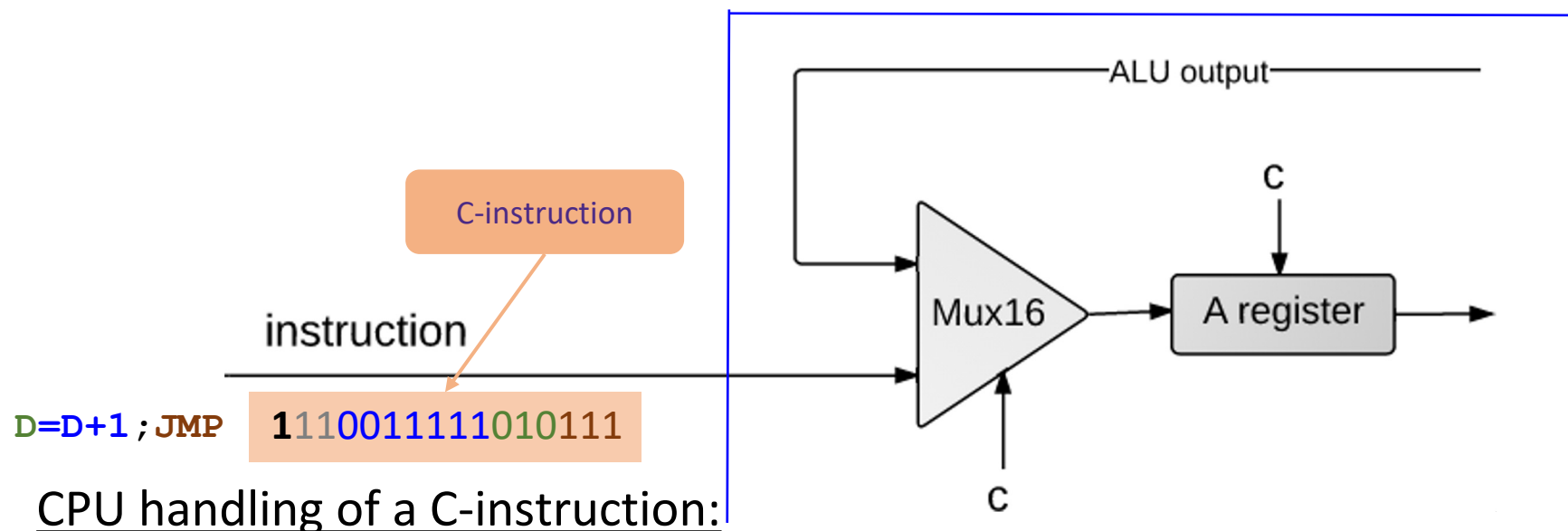

CPU handling of a C-instruction:

- ❖ Decodes the instruction bits into:
 - Op-code
 - ALU control bits
 - Destination load bits
 - Jump bits
- ❖ Routes these bits to their chip-part destinations
- ❖ The chip-parts (most notably, the ALU) execute the instruction

Hack: C-Instructions

❖ Symbolic: **dest** = **comp** ; **jump**

❖ Binary: 1 1 1 a c1 c2 c3 c4 c5 c6 d1 d2 d3 j1 j2 j3

(when a=0) <i>comp mnemonic</i>	c1	c2	c3	c4	c5	c6	(when a=1) <i>comp mnemonic</i>
0	1	0	1	0	1	0	
1	1	1	1	1	1	1	
-1	1	1	1	0	1	0	
D	0	0	1	1	0	0	
A	1	1	0	0	0	0	M
!D	0	0	1	1	0	1	
!A	1	1	0	0	0	1	!M
-D	0	0	1	1	1	1	
-A	1	1	0	0	1	1	-M
D+1	0	1	1	1	1	1	M+1
A+1	1	1	0	1	1	1	
D-1	0	0	1	1	1	0	
A-1	1	1	0	0	1	0	M-1
D+A	0	0	0	0	1	0	D+M
D-A	0	1	0	0	1	1	D-M
A-D	0	0	0	1	1	1	M-D
D&A	0	0	0	0	0	0	D&M
D A	0	1	0	1	0	1	D M

Comp:


ALU Operation (a bit chooses between A and M)

Chapter 4

Important: just pattern matching text!

Cannot have "1+M"

CPU Operation: Handling C-Instructions

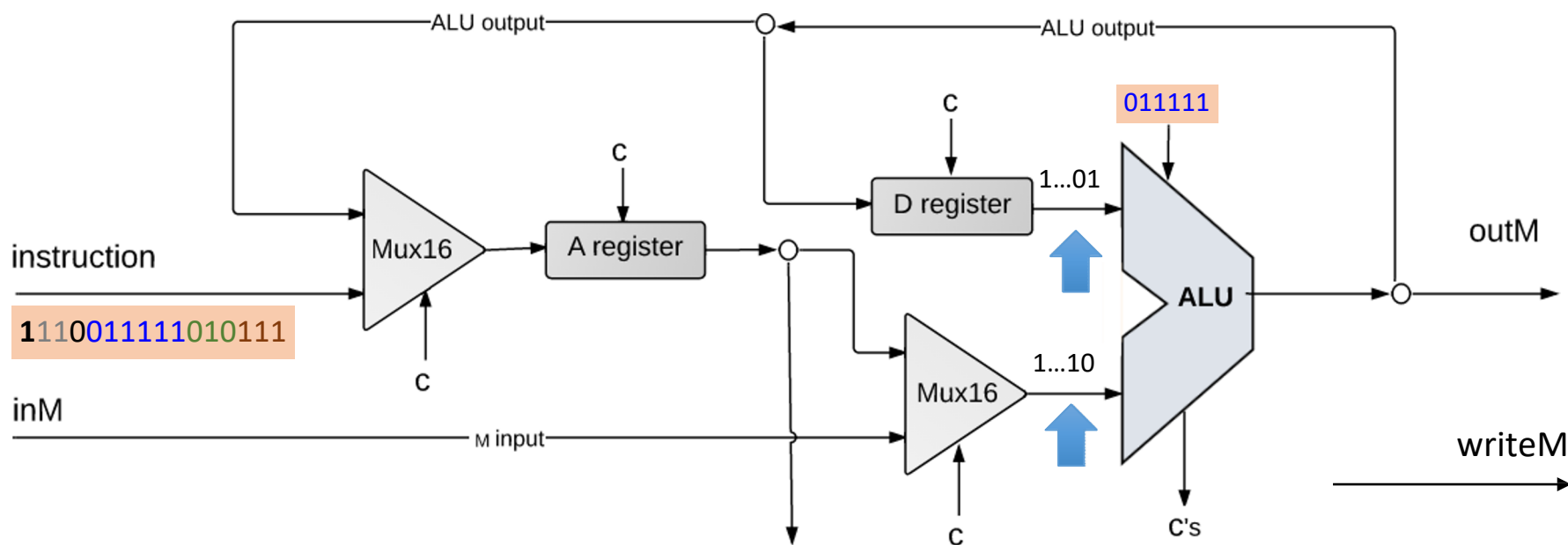

ALU data inputs:

- ❖ Input 1: from the D-register
- ❖ Input 2: from either:
 - A-register, or
 - data memory

ALU control inputs:

- ❖ Control bits (from the instruction)

Hack: C-Instructions

❖ Symbolic: `dest = comp ; jump`


❖ Binary: `1 1 1 a c1 c2 c3 c4 c5 c6 d1 d2 d3 j1 j2 j3`

Dest:
Where to store
result

Chapter 4

d1	d2	d3	Mnemonic	Destination (where to store the computed value)
0	0	0	null	The value is not stored anywhere
0	0	1	M	Memory[A] (memory register addressed by A)
0	1	0	D	D register
0	1	1	MD	Memory[A] and D register
1	0	0	A	A register
1	0	1	AM	A register and Memory[A]
1	1	0	AD	A register and D register
1	1	1	AMD	A register, Memory[A], and D register


CPU Operation: Handling C-Instructions

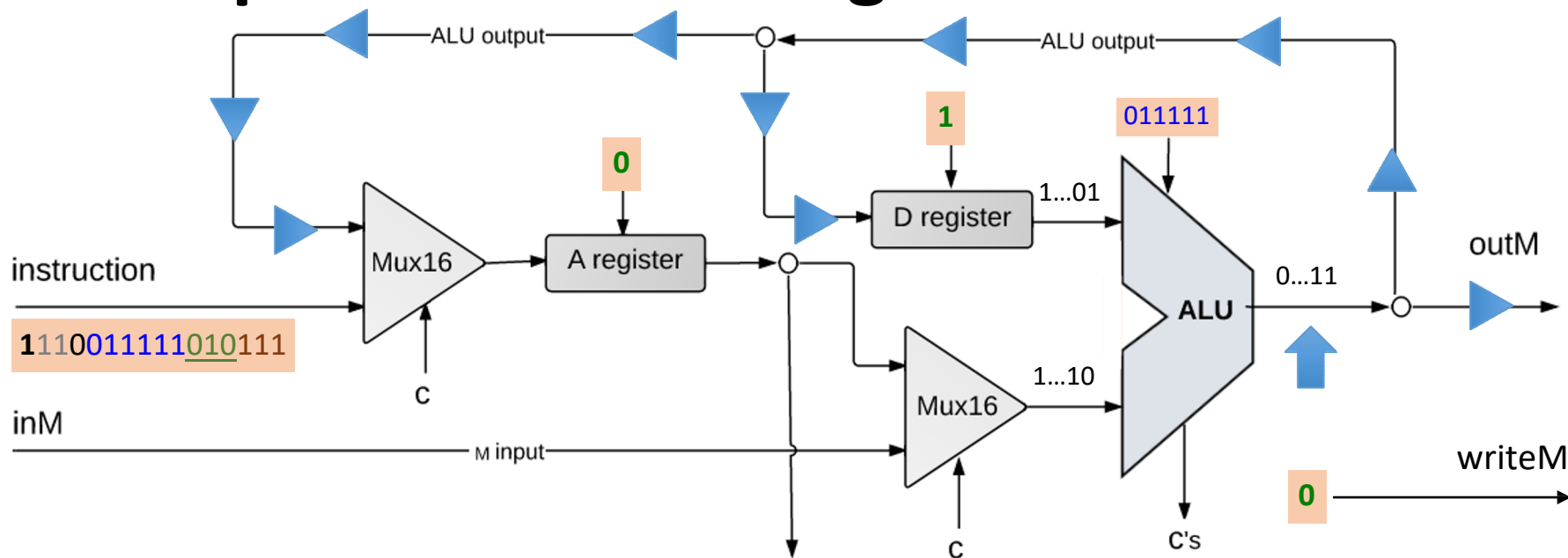

ALU data output:

- ❖ Result of ALU calculation
- ❖ Fed simultaneously to: D-register, A-register, data memory
- ❖ Which destination *actually* commits to the ALU output is determined by the instruction's **destination bits**


CPU Operation: Handling C-Instructions

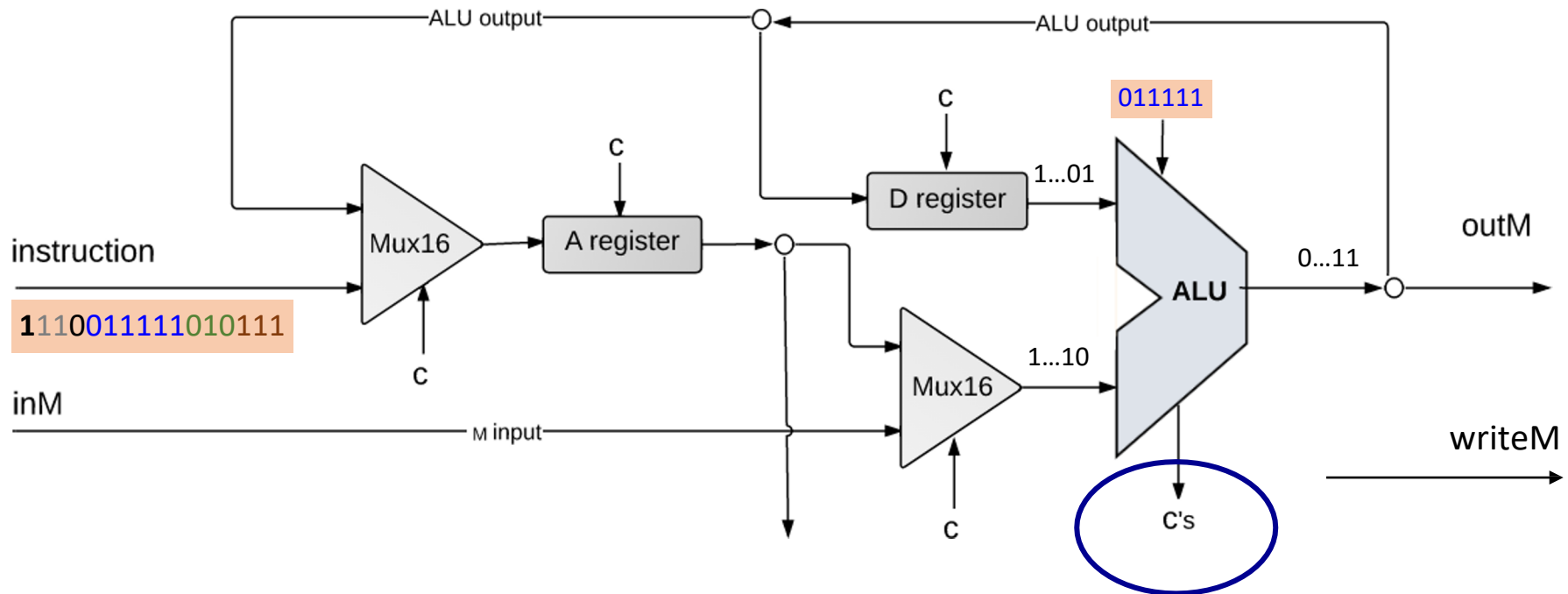


ALU control outputs:

- ❖ Is the output negative?
- ❖ Is the output zero?


CPU Operation: Control

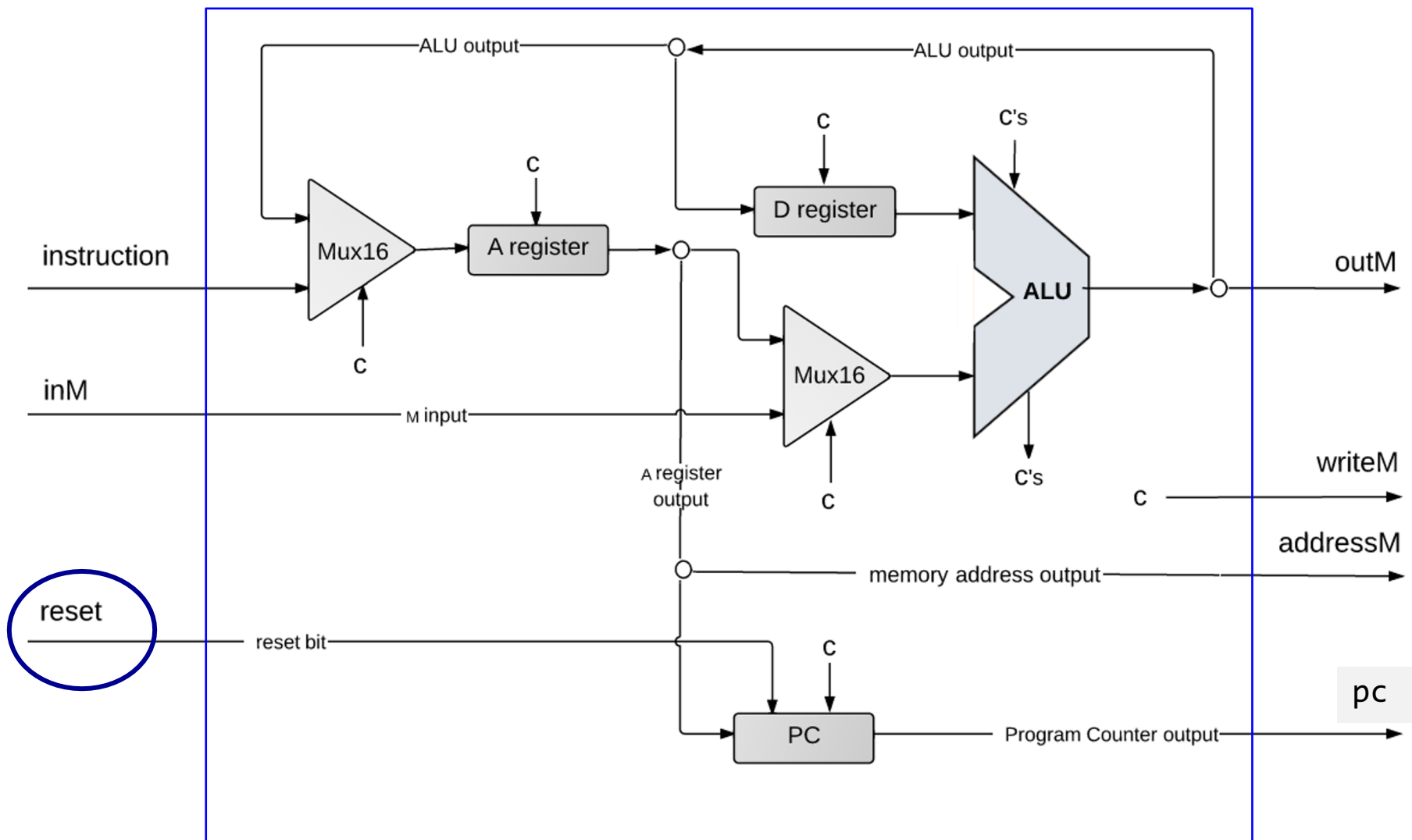

CPU Operation: Control

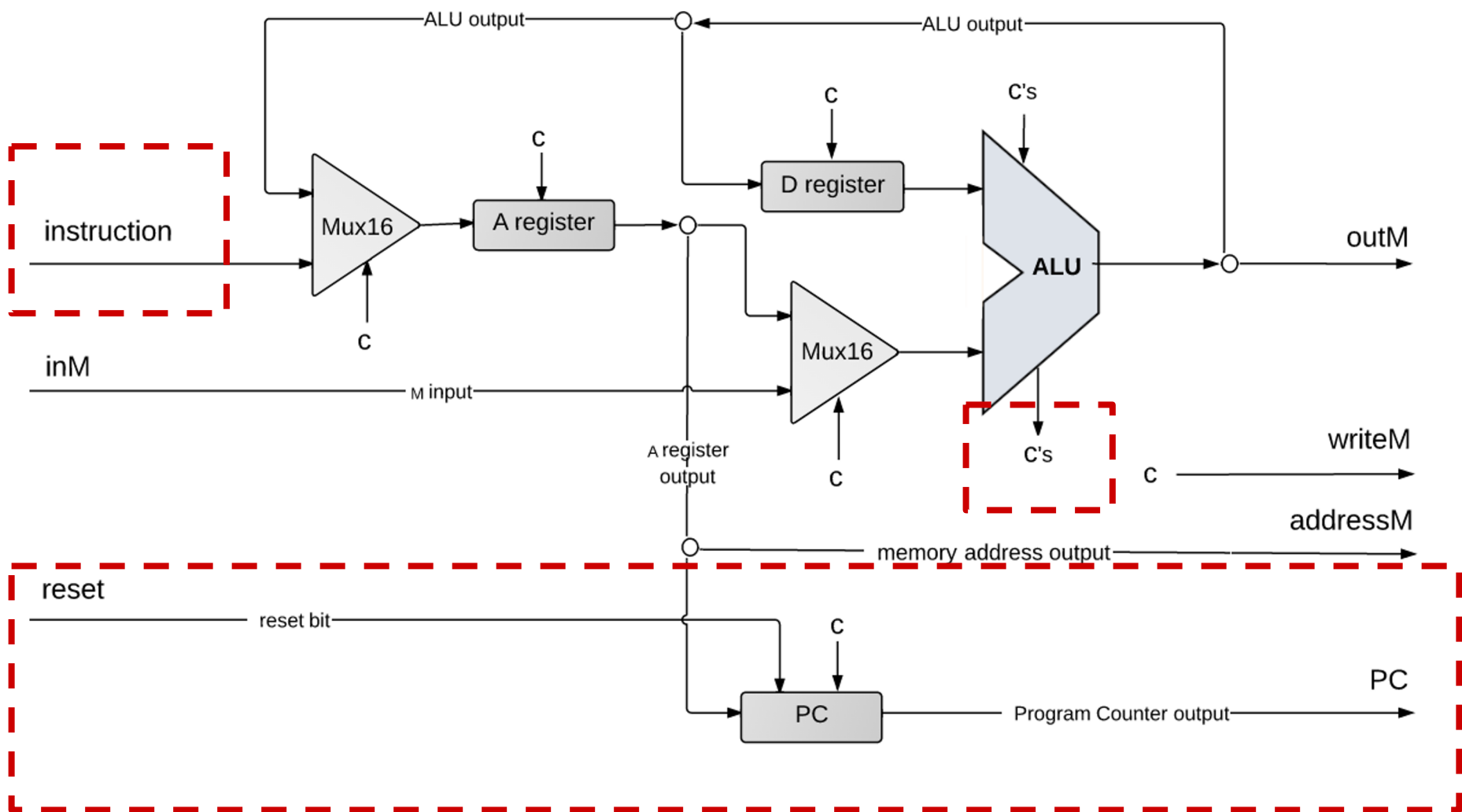

CPU Operation: Control

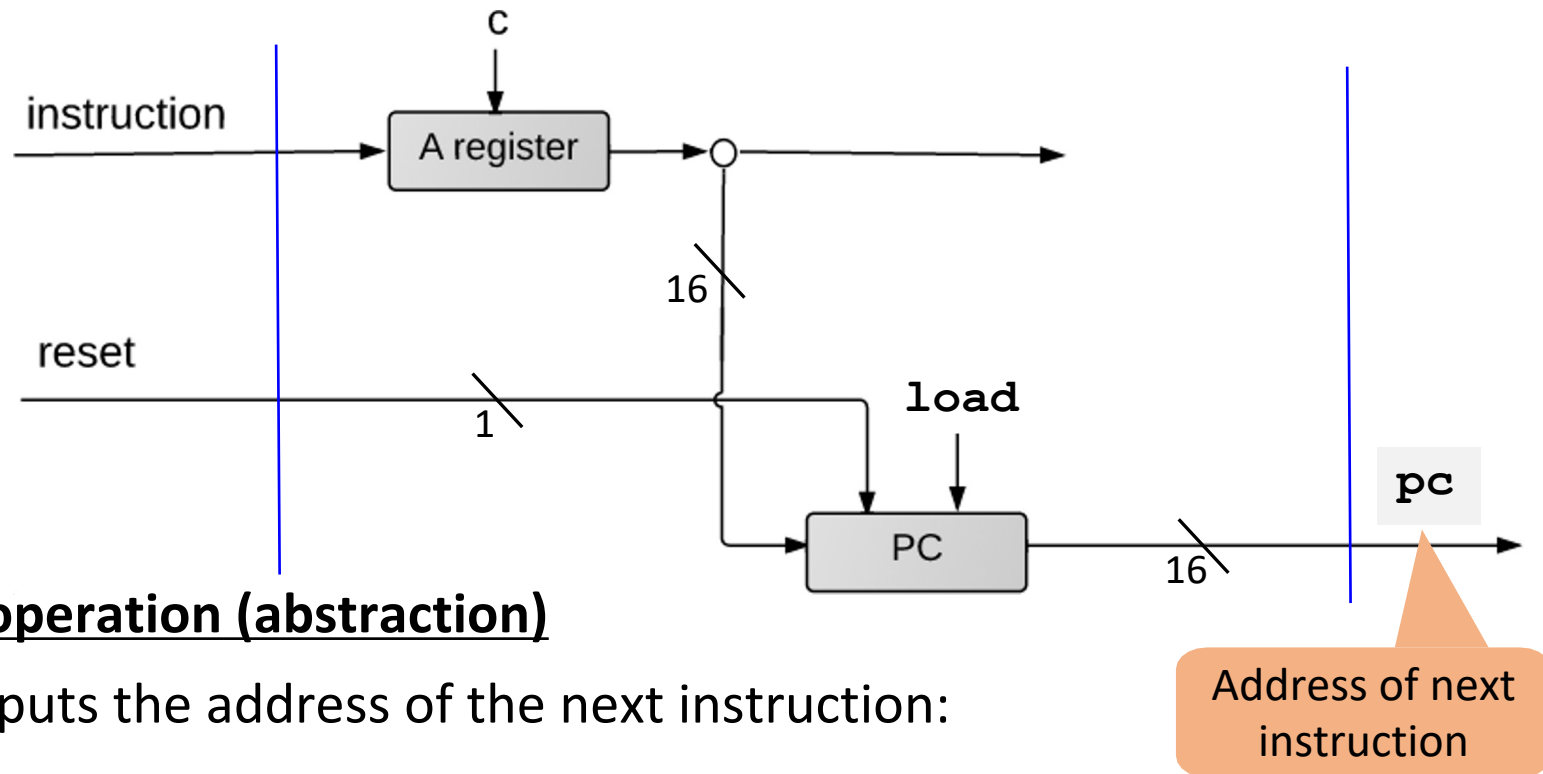

PC operation (abstraction)

Outputs the address of the next instruction:

- ❖ Restart: $PC = 0$
- ❖ No jump: $PC++$
- ❖ Go to: $PC = A$
- ❖ Conditional go to:

if (condition)	$PC = A$
else	$PC++$

Hack: C-Instructions

❖ Symbolic: **dest** = **comp** ; **jump**


❖ Binary: 1 1 1 a c1 c2 c3 c4 c5 c6 d1 d2 d3 j1 j2 j3

Jump:
Condition for
jumping


Chapter 4

j1 (<i>out</i> < 0)	j2 (<i>out</i> = 0)	j3 (<i>out</i> > 0)	Mnemonic	Effect
0	0	0	null	No jump
0	0	1	JGT	If <i>out</i> > 0 jump
0	1	0	JEQ	If <i>out</i> = 0 jump
0	1	1	JGE	If <i>out</i> ≥ 0 jump
1	0	0	JLT	If <i>out</i> < 0 jump
1	0	1	JNE	If <i>out</i> ≠ 0 jump
1	1	0	JLE	If <i>out</i> ≤ 0 jump
1	1	1	JMP	Jump

CPU Operation: Control

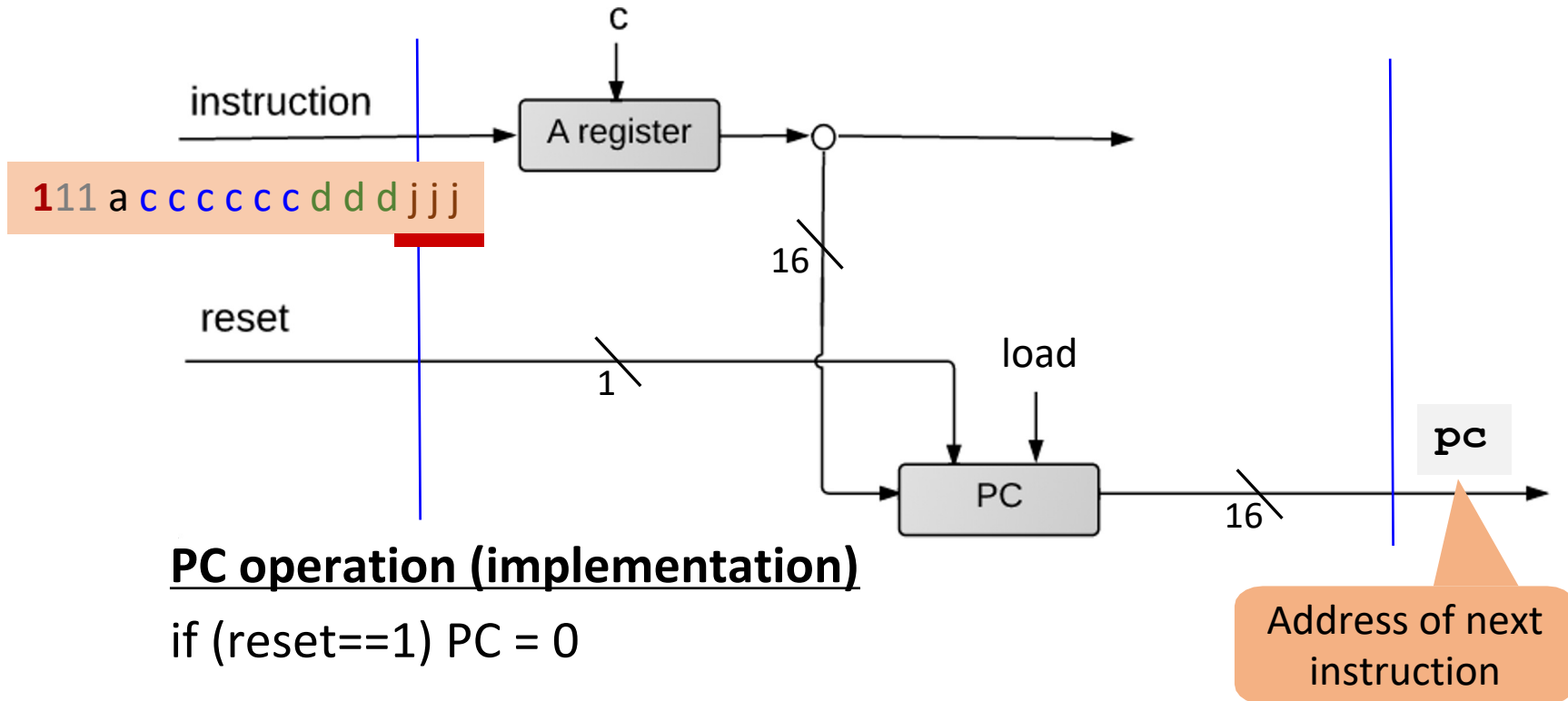

Hack CPU Implementation: That's It!

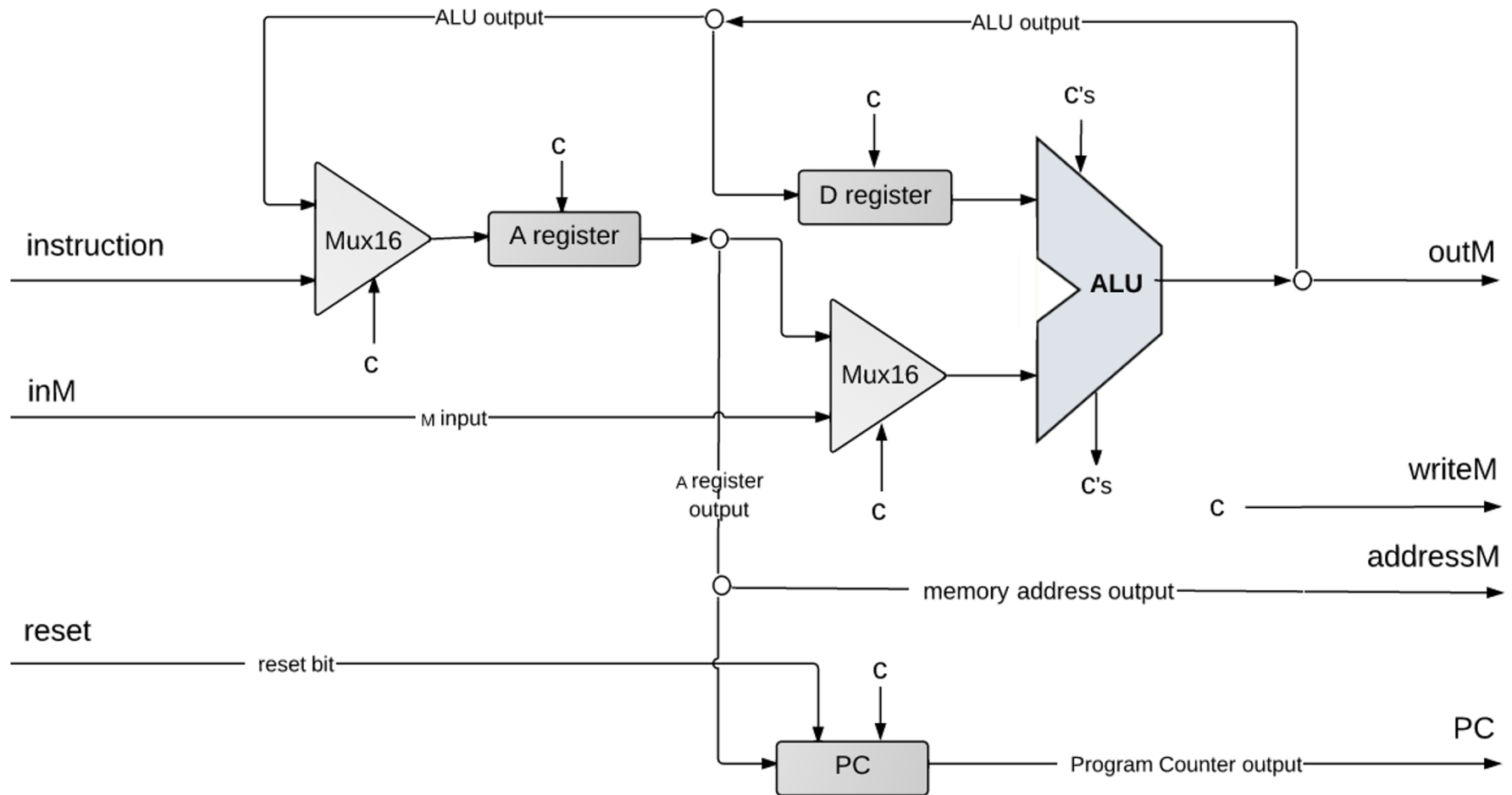

Lecture Outline

- ❖ Hack CPU Logic
 - Implementation and Operations
- ❖ **Test-taking Strategies**
 - **Maximizing Success on Exam Day**
- ❖ Midterm Practice Exam
 - Mock Exam, Debrief, and Reflection
- ❖ Practice Exam Solutions and Rubric
 - Walkthrough of Solutions and Exploring Sample Rubrics

Test-taking Strategies Discussion

- ❖ What are some test-taking strategies you have previously utilized in taking your exams?
- ❖ Were those strategies you tried effective or not? Why?
- ❖ How might you try a new test-taking strategy on the CSE 390B midterm or any other upcoming exam?

Test-taking Strategies

- ❖ Survey the entire exam before beginning
 - Helps plan how much time to allocate for each problem
- ❖ Read exam directions and question statements carefully
 - Use **highlights**, underlines, circles on important details
- ❖ Answer the questions you feel the most confident in first
- ❖ If stuck on a problem, make a mark on the problem and revisit the question later

Test-taking Strategies

- ❖ Prioritize how you will answer questions
 - Do this based on confidence level for each type of question or how long you think each will take
- ❖ Rely on a methodological approach for each question
 - Helps make taking the test feel more systematic
- ❖ If stuck on a question, demonstrate what you know
 - Many exams reward partial credit
- ❖ If time allows, double check your answers
 - Catches any small mistakes that may have been made earlier

Lecture Outline

- ❖ Hack CPU Logic
 - Implementation and Operations
- ❖ Test-taking Strategies
 - Maximizing Success on Exam Day
- ❖ **Midterm Practice Exam**
 - **Mock Exam, Debrief, and Reflection**
- ❖ Practice Exam Solutions and Rubric
 - Walkthrough of Solutions and Exploring Sample Rubrics

Midterm Practice Exam

- ❖ The exam is closed-note, closed-book
 - You may only use the midterm reference sheet
- ❖ Questions are not necessarily in order of difficulty
- ❖ You will have 25 minutes to complete the mock exam
 - We will give you a 5-minute warning
- ❖ Remember to relax and take deep breaths

Mock Exam Debrief & Reflection

- ❖ What did you learn about yourself through this process?
About your test-taking practices?
- ❖ What are two test-taking strategies that you would like to engage with in your next exam? Why?
- ❖ What is one thing that can help you relax and calm down before or during your exam?

Lecture Outline

- ❖ Hack CPU Logic
 - Implementation and Operations
- ❖ Test-taking Strategies
 - Maximizing Success on Exam Day
- ❖ Midterm Practice Exam
 - Mock Exam, Debrief, and Reflection
- ❖ Practice Exam Solutions and Rubric
 - Walkthrough of Solutions and Exploring Sample Rubrics

Question 1: Circuit Design

Part a: Truth Table

A_t	B_t	A_{t+1}	B_{t+1}
1	1	1	0
1	0	0	1
0	1	0	0
0	0	1	1

11 $\rightarrow$ 10 $\rightarrow$ 01 $\rightarrow$ 00 $\rightarrow$ 11

Question 1: Circuit Design

Part a: Truth Table

A_t	B_t	A_{t+1}	B_{t+1}
1	1	1	0
1	0	0	1
0	1	0	0
0	0	1	1

11 → 10 → 01 → 00 → 11

Question 1: Circuit Design

Part a: Truth Table

A_t	B_t	A_{t+1}	B_{t+1}
1	1	1	0
1	0	0	1
0	1	0	0
0	0	1	1

$$A_{t+1} = (A_t \& B_t)$$

$$A_{t+1} = (\sim A_t \& \sim B_t)$$

Part b: Boolean Expressions

Question 1: Circuit Design

Part a: Truth Table

A_t	B_t	A_{t+1}	B_{t+1}
1	1	1	0
1	0	0	1
0	1	0	0
0	0	1	1

$$A_{t+1} = (A_t \& B_t)$$

$$A_{t+1} = (\sim A_t \& \sim B_t)$$

Part b: Boolean Expressions

$$A_{t+1} = (A_t \& B_t) \mid (\sim A_t \& \sim B_t)$$

Question 1: Circuit Design

Part a: Truth Table

A_t	B_t	A_{t+1}	B_{t+1}
1	1	1	0
1	0	0	1
0	1	0	0
0	0	1	1

$$A_{t+1} = (A_t \& B_t)$$

$$B_{t+1} = (A_t \& \sim B_t)$$

$$A_{t+1} = (\sim A_t \& \sim B_t)$$

$$B_{t+1} = (\sim A_t \& \sim B_t)$$

Part b: Boolean Expressions

$$A_{t+1} = (A_t \& B_t) \mid (\sim A_t \& \sim B_t)$$

$$B_{t+1} = (A_t \& \sim B_t) \mid (\sim A_t \& \sim B_t)$$

$$= \sim B_t \& (A_t \mid \sim A_t)$$

[Factor out $\sim B_t$]

$$= \sim B_t$$

$$[A_t \mid \sim A_t = 1]$$

Question 1: Circuit Design

Part a: Truth Table

A_t	B_t	A_{t+1}	B_{t+1}
1	1	1	0
1	0	0	1
0	1	0	0
0	0	1	1

Part c: Drawing the Circuit

Part b: Boolean Expressions

$$A_{t+1} = (A_t \& B_t) \mid (\sim A_t \& \sim B_t)$$

$$B_{t+1} = (A_t \& \sim B_t) \mid (\sim A_t \& \sim B_t)$$

$$= \sim B_t \& (A_t \mid \sim A_t)$$

$$= \sim B_t$$

$$[\text{Factor out } \sim B_t]$$

$$[A_t \mid \sim A_t = 1]$$

Question 1: Circuit Design Sample Rubric

Category	Points	Criteria
Truth Table	4 points	1 point for each row in the truth table that is correct
Boolean Expressions	6 points	❖ 4 points for correct expression for A_{t+1} ▪ 2 points if truth table is wrong but expression matches truth table ❖ 2 points for correct expression for B_{t+1} ▪ 1 point if truth table is wrong but expression matches truth table
Circuit Diagram	5 points	❖ 3 points for having circuits that match the Boolean expressions in part b ❖ 2 points for fully correct diagram
Total	15 points	

Question 2: Math Puzzle

Dana needs 300 pickets for her colorful picket fence. She wants equal amounts of each of her 4 selected colors. She already has 32 red, 26 green, 9 yellow, and no blue. If the pickets cost 25 cents and you get 20% off if you purchase 50 or more of the same color, and 30% off if you purchase 60 or more of one color, how much does Dana need to spend? List your answer to two decimal places. You may use a calculator application on your computer to solve this problem.

Question 2: Math Puzzle

Dana needs 300 pickets for her colorful picket fence. She wants equal amounts of each of her 4 selected colors. She already has 32 red, 26 green, 9 yellow, and no blue. If the pickets cost 25 cents and you get 20% off if you purchase 50 or more of the same color, and 30% off if you purchase 60 or more of one color, how much does Dana need to spend? List your answer to two decimal places. You may use a calculator application on your computer to solve this problem.

Solution

$$75 - 32 = 43 \text{ red}$$

$$75 - 26 = 49 \text{ green}$$

$$75 - 9 = 66 \text{ yellow}$$

$$75 - 0 = 75 \text{ blue}$$

$$\begin{aligned} &43 \times 0.25 + 49 \times 0.25 + 0.7 \times 66 \times 0.25 + 0.7 \times 75 \times 0.25 \\ &= \$47.675 \end{aligned}$$

$$= \$47.68 \quad (\text{Rounding down is also acceptable})$$

Question 3: Hack Assembly Programming

Write a Hack assembly program that stores -1, 0, or 1 in R1 based on the sign of R0. To be more specific, your program should store a -1 in R1 if R0 is negative, a 0 in R1 if R0 is 0, and a 1 in R1 if R0 is positive.

j1 (<i>out</i> < 0)	j2 (<i>out</i> = 0)	j3 (<i>out</i> > 0)	Mnemonic	Effect
0	0	0	null	No jump
0	0	1	JGT	If <i>out</i> > 0 jump
0	1	0	JEQ	If <i>out</i> = 0 jump
0	1	1	JGE	If <i>out</i> ≥ 0 jump
1	0	0	JLT	If <i>out</i> < 0 jump
1	0	1	JNE	If <i>out</i> ≠ 0 jump
1	1	0	JLE	If <i>out</i> ≤ 0 jump
1	1	1	JMP	Jump

Question 3: Hack Assembly Programming

Write a Hack assembly program that stores -1, 0, or 1 in R1 based on the sign of R0. To be more specific, your program should store a -1 in R1 if R0 is negative, a 0 in R1 if R0 is 0, and a 1 in R1 if R0 is positive.

Equivalent pseudocode:

```
if (R0 < 0) {
    R1 = -1;
} else if (R0 > 0) {
    R1 = 1;
} else { //R0 == 0
    R1 = 0;
}
```

j1 (out < 0)	j2 (out = 0)	j3 (out > 0)	Mnemonic	Effect
0	0	0	null	No jump
0	0	1	JGT	If <i>out</i> > 0 jump
0	1	0	JEQ	If <i>out</i> = 0 jump
0	1	1	JGE	If <i>out</i> ≥ 0 jump
1	0	0	JLT	If <i>out</i> < 0 jump
1	0	1	JNE	If <i>out</i> ≠ 0 jump
1	1	0	JLE	If <i>out</i> ≤ 0 jump
1	1	1	JMP	Jump

Question 3: Hack Assembly Programming

Write a Hack assembly program that stores -1, 0, or 1 in R1 based on the sign of R0. To be more specific, your program should store a -1 in R1 if R0 is negative, a 0 in R1 if R0 is 0, and a 1 in R1 if R0 is positive.

Equivalent pseudocode:

```
if (R0 < 0) {
    R1 = -1;
} else if (R0 > 0) {
    R1 = 1;
} else { //R0 == 0
    R1 = 0;
}
```

j1 (out < 0)	j2 (out = 0)	j3 (out > 0)	Mnemonic	Effect
0	0	0	null	No jump
0	0	1	JGT	If out > 0 jump
0	1	0	JEQ	If out = 0 jump
0	1	1	JGE	If out ≥ 0 jump
1	0	0	JLT	If out < 0 jump
1	0	1	JNE	If out ≠ 0 jump
1	1	0	JLE	If out ≤ 0 jump
1	1	1	JMP	Jump

One solution:

```
@R0
D = M
@NEGATIVE
D; JLT
@POSITIVE
D; JGT
// R0 == 0 case
@R1
M = 0
@END
0; JMP
(NEGATIVE)
// R0 < 0 case
@R1
M = -1
@END
0; JMP
(POSITIVE)
// R0 > 0 case
@R1
M = 1
(END)
@END
0; JMP
```

Question 3: Hack Assembly Sample Rubric

Category	Points	Criteria
Has Infinite End Loop	1 point	❖ 1 point if program has an Infinite End Loop
Conditional Checks	4 points	❖ 2 points for having at least two checks for cases. Almost all solutions will need a check for 2 of the three cases (negative, zero, positive). ❖ 2 points for correctly matching jump condition to cases (e.g. jump to negative case when negative, etc.)
Assigns Correct R1 Value	3 points	❖ One point for each case: ▪ negative: $R1 = -1$ ▪ zero: $R1 = 0$ ▪ positive: $R = 1$
Fully Correct Implementation	2 points	❖ Covers any little mistakes that may result in an incorrect implementation (e.g., forgetting to jump to the end when a case is done)
Total	10 points	

Question 4: Metacognitive Skills

- ❖ Name two metacognitive skills that we have covered in CSE 390B thus far.

Post-Lecture 12 Reminders

- ❖ CSE 390B midterm this Thursday (11/10) during lecture at 2:30pm
- ❖ Project 6: Mock Exam Problem & Building a Computer due next Thursday (11/17) at 11:59pm
- ❖ Preston has office hours after class in CSE2 153
 - Feel free to post your questions on the Ed board as well