

CSE 390B, Autumn 2022

Building Academic Success Through Bottom-Up Computing

# Study Environment, Boolean Logic, & HDL

Study Environment Discussion, Boolean Logic and Functions,  
Hardware Descriptive Language, Implementing an **Xor** Gate

# Checking in on Project 1

- ❖ Eric made a typo on the Project 1 document
  - Fixed as of yesterday (10/3), please redownload document from Canvas if necessary
- ❖ Remember to double-check your submission on GitLab
  - Navigate to GitLab, open tags, and verify that the associated commit includes your expected changes
- ❖ How has Project 1 been coming along?
- ❖ What questions do you have about Project 1?

# Lecture Outline

## ❖ Study Environment Discussion

## ❖ Boolean Logic and Functions

- Boolean Expressions, Circuit Diagrams, Truth Tables
- Boolean Function Synthesis Strategy

## ❖ Hardware Descriptive Languages (HDL)

- HDL Syntax, **And** Gate Example

## ❖ Implementing an **Xor** gate in HDL

# Study Environment Discussion

In groups of 3-4, discuss the following questions about study environments:

- ❖ On a typical day, what does your study environment look like? Be specific!
- ❖ What contributes to an effective study environment? Why?
  - What changes can you make to introduce some of these factors?
- ❖ What factors hinder a study environment from being effective? Why?
  - What changes can you make to remove some of these factors?

# Lecture Outline

- ❖ Study Environment Discussion
- ❖ **Boolean Logic and Functions**
  - Boolean Expressions, Circuit Diagrams, Truth Tables
  - Boolean Function Synthesis Strategy
- ❖ Hardware Descriptive Languages (HDL)
  - HDL Syntax, **And** Gate Example
- ❖ Implementing an **Xor** gate in HDL

# Boolean Values

- ❖ A binary choice: **True** or **False**
- ❖ Also known as a “low” signal (false, “off,” or 0) and a “high” signal (true, “on”, or 1)



“Off”

False

0



“On”

True

1

# Boolean Operations

- ❖ Use logical operations to combine Boolean values
  - **Truth table:** A table that lists every possible set of inputs and the corresponding output of the operation
  - Operations correspond to physical hardware gates

- ❖ Examples:

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

$$F = A \text{ OR } B$$

A	F
0	1
1	0

$$F = \text{NOT } A$$

# Boolean Functions

❖ Combinations of Boolean inputs resulting in single output


❖ Multiple ways to specify a Boolean function:

- Boolean expression:  $F = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$

- Circuit diagram with logic gates:

- Truth table:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 



# Boolean Expression $\rightarrow$ Truth Table

- ❖ We can build a truth table from an expression
  - Evaluate the Boolean expression on all possible inputs

$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$



A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Boolean Expression $\rightarrow$ Truth Table

- ❖ We can build a truth table from an expression
  - Evaluate the Boolean expression on all possible inputs

$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$




A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1
 
# Boolean Expression $\leftarrow$ Truth Table

❖ But can we do it in reverse?

$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

# Boolean Expression $\leftarrow$ Truth Table

❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

# Boolean Expression $\leftarrow$ Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

# Boolean Expression $\leftarrow$ Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

# Boolean Expression $\leftarrow$ Truth Table

❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

# Boolean Expression $\leftarrow$ Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

A AND B AND C



# Boolean Expression $\leftarrow$ Truth Table

❖ Then, we can combine the rows using OR operations

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C


A AND B AND C

$F = \text{NOT}(A) \text{ AND } \text{NOT}(B) \text{ AND } C \text{ OR } \text{NOT}(A) \text{ AND } B \text{ AND } C \text{ OR } A \text{ AND } B \text{ AND } \text{NOT } C \text{ OR } A \text{ AND } B \text{ AND } C$
 
# Boolean Expression ← Truth Table

- ❖ But can we do it in reverse?
  - Yes, we can! The strategy we used is **Boolean Function Synthesis**

$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

# Five-minute Break!

- ❖ Feel free to stand up, stretch, use the restroom, drink some water, review your notes, or ask questions
- ❖ We'll be back at:





Vote at <https://pollev.com/cse390b>

## Which of the following statements is FALSE?

- A. The Boolean Function Synthesis strategy works on every truth table
- B. In CSE 390B, we will be asking you to write Boolean expressions that must be simplified
- C. The abstraction of voltages on a physical wire represents two values
- D. A truth table lists every possible combination of inputs for a Boolean operation
- E. We're lost...

# Lecture Outline

- ❖ Study Environment Discussion
- ❖ Boolean Logic and Functions
  - Boolean Expressions, Circuit Diagrams, Truth Tables
  - Boolean Function Synthesis Strategy
- ❖ **Hardware Descriptive Languages (HDL)**
  - **HDL Syntax, And Gate Example**
- ❖ Implementing an **Xor** gate in HDL

# Hardware Design Language (HDL)

- ❖ HDL is a programming language to specify hardware components and how they're connected
  - Another way of describing a Boolean function!
  
- ❖ Many Hardware Design Languages are used today
  - E.g., VHDL, Verilog, SystemVerilog
  - In this course, we'll use a simple HDL language called "HDL"
  
- ❖ Unlike Java, HDL is a **declarative** language. This means the following:
  - The order of statements (lines of code) doesn't matter
  - We are describing a physical system

# Hardware Design Language (HDL)

## ❖ Format of an HDL file

- File comment describes expected behavior
- **IN** names chip inputs, **OUT** names chip outputs
- **PARTS** specify the components (i.e., other gates) that implement the chip

```
/**  
 * And gate:  
 * out = 1 only if both a and b are 1  
 */  
CHIP And {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
    // Put your code here:  
}
```

# Reusing Components

- ❖ You can (and should!) use chips you have already implemented to implement subsequent chips
- ❖ We give you one gate, **Nand**, to start out with
  - Implication: The entire computer you will be building will be use **Nand** gates as its foundation
- ❖ We also provide you with some chips you can use without implementing
  - More details this Thursday when Project 2 is released




# HDL Component Example: AND

- ❖ The chip specification tells us the name of the input and output wires

```
CHIP And {  
    IN a, b;  
    OUT out;  
  
    ...  
}
```

- ❖ Goal: Implement  $w1 \text{ AND } w2$

 - HDL Syntax for using (being a client of the **And** gate):  
**And(a=w1, b=w2, out=w3);**
- Equivalent circuit diagram:



# Multi-bit Buses in HDL

- ❖ It can be useful to manipulate groups of wires
  - Called a “bus” of wires
- ❖ HDL provides array like syntax for manipulating buses
  - **And4** chip example:

```
/**
 * Bit-wise And of two 4-bit inputs
 */
CHIP And4 {
    IN a[4], b[4];
    OUT out[4];

    PARTS:
    And (a=a[0], b=b[0], out=out[0]);
    And (a=a[1], b=b[1], out=out[1]);
    And (a=a[2], b=b[2], out=out[2]);
    And (a=a[3], b=b[3], out=out[3]);
}
```

# HDL Resources

- ❖ HDL will feel unfamiliar at first, and that's okay
- ❖ Resources for helping you navigate HDL linked under the [Resources page](#) on the course website
  - HDL Survival guide
  - Appendix A (HDL Spec)
  - Chip Set Overview (to help you remember the inputs/outputs for various chips)
  - Chapter readings

# Lecture Outline

- ❖ Study Environment Discussion
- ❖ Boolean Logic and Functions
  - Boolean Expressions, Circuit Diagrams, Truth Tables
  - Boolean Function Synthesis Strategy
- ❖ Hardware Descriptive Languages (HDL)
  - HDL Syntax, **And** Gate Example
- ❖ **Implementing an Xor gate in HDL**

# The Foundational Building Block

- ❖ It all starts with the NAND gate
- ❖ NAND is short for “Not And”
  - The same output as the AND gate, but every output bit is negated (flipped)

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

$$F = A \text{ NAND } B$$

# Building Gates From Nand

- ❖ Recall the **Boolean Function Synthesis** strategy from today's reading
  - We saw how we can represent any truth table in terms of three gates: **Not**, **And**, **Or**
- ❖ First, we can represent **Not** directly from **Nand**
  - $\text{Not } a = a \text{ Nand } a$
- ❖ Then, we can represent **And** in terms of **Not** and **Nand**
  - $a \text{ And } b = \text{Not}(a \text{ Nand } b)$
- ❖ Represent **Or** in terms of **Not** and **And**
  - Apply De Morgan's Law
  - $a \text{ Or } b = \text{Not}(\text{Not}(a) \text{ And } \text{Not}(b))$  [De Morgan's Law]

# Implementing an **Xor** gate: Overview

- ❖ Let's walk through an example of building a gate that you will work on in Project 2, the **Xor** gate
- ❖ Together, we'll implement the **Xor** gate

```
/**  
 * Xor gate:  
 * out = not(a == b)  
 */  
CHIP Xor {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
    // Put your code here:  
}
```

# Implementing an Xor gate: Overview

## ❖ Plan of action:

- Step 1: Create the logic operation's **truth table**
- Step 2: Use truth table to generate a **Boolean function** using strategies we've learned, such as the Boolean Function Synthesis
- Step 3: Convert Boolean function to **HDL**

```
/**  
 * Xor gate:  
 * out = not(a == b)  
 */  
CHIP Xor {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
    // Put your code here:  
}
```



# Implementing an Xor gate: Step 1

- ❖ Step 1: Create the truth table for **Xor**
  - Interpret the specification:  $F = \text{NOT}(A == B)$

A	B	F
0	0	
0	1	
1	0	
1	1	

$$F = A \text{ XOR } B$$

# Implementing an **Xor** gate: Step 1

## ❖ Step 1: Create the truth table for **Xor**

- Interpret the specification:  $F = \text{NOT}(A == B)$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

$$F = A \text{ XOR } B$$

# Implementing an Xor gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
  - Let's use the **Boolean Function Synthesis** strategy from the reading
  - **Row 2 = NOT(A) AND B**

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

# Implementing an Xor gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
  - Let's use the **Boolean Function Synthesis** strategy from the reading
  - Row 2 = NOT(A) AND B
  - Row 3 = A AND NOT(B)

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

# Implementing an Xor gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
  - Let's use the **Boolean Function Synthesis** strategy from the reading
  - Row 2 = NOT(A) AND B
  - Row 3 = A AND NOT(B)
  - $F = ?$

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$



Vote at <https://pollev.com/cse390b>

**What is the unsimplified Boolean expression result from performing Boolean function synthesis on  $F = A \text{ XOR } B$ ?**

- A.  $(A \text{ AND NOT}(B)) \text{ AND } (\text{NOT}(A) \text{ AND } B)$
- B.  $(\text{NOT}(A) \text{ AND } B) \text{ AND } (A \text{ AND } B)$
- C.  $(A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND NOT}(B))$
- D.  $(\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND NOT}(B))$
- E. **We're lost...**

- Row 2 =  $\text{NOT}(A) \text{ AND } B$
- Row 3 =  $A \text{ AND NOT}(B)$

A	B	F = A XOR B	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

# Implementing an Xor gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
  - Let's use the Boolean function synthesis strategy from the reading
  - Row 2 = NOT(A) AND B
  - Row 3 = A AND NOT(B)
  - $F = \text{Row 2 OR Row 3}$   
 $= (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND NOT}(B))$


A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$
 
# Implementing an Xor gate: Step 3

- ❖ Now that we have a Boolean expression, we can implement the **Xor** gate in HDL
- ❖ Optionally, it can help to express the Boolean expression as a circuit diagram

$$A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$$





 
# Implementing an Xor gate: Step 3

- ❖ Step 3: Convert Boolean function to HDL syntax
  - $A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$
  - Assumes **Not**, **And**, and **Or** are already implemented
  - Note the use of intermediary wires: **nota**, **notb**, **x**, and **y**

```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
    Not (in=a, out=nota);  
    Not (in=b, out=notb);  
    And (a=a, b=notb, out=x);  
    And (a=nota, b=b, out=y);  
    Or (a=x, b=y, out=out);  
}
```



# Wrapping Up

- ❖ Exciting lecture topics this Thursday!
  - Metacognitive Subject: Time Management
  - Technical Subject: Making Decisions in Hardware, Project 2 Overview
- ❖ **Project 1 due this Thursday (10/6) at 11:59pm**
- ❖ Preston has office hours after class in CSE2 153
- ❖ First Student-TA meetings starting this week
  - Your TA will be in contact with you about the first meeting (if not already)