

CSE 390B, Autumn 2022

Building Academic Success Through Bottom-Up Computing

Bloom's Taxonomy & Sequential Logic

Bloom's Taxonomy, Introduction to Sequential Logic,
Representing Time in Hardware, The Data Flip-Flop (DFF)

Lecture Outline

❖ Bloom's Taxonomy

- Applying Higher Levels of Cognition to Learning

❖ Introduction to Sequential Logic

- The Problem with Combinational Logic


❖ Representing Time in Hardware

- Clock Signals and Units of Time in Hardware


❖ The Data Flip-Flop (DFF)

- Implementation and Examples

Bloom's Taxonomy

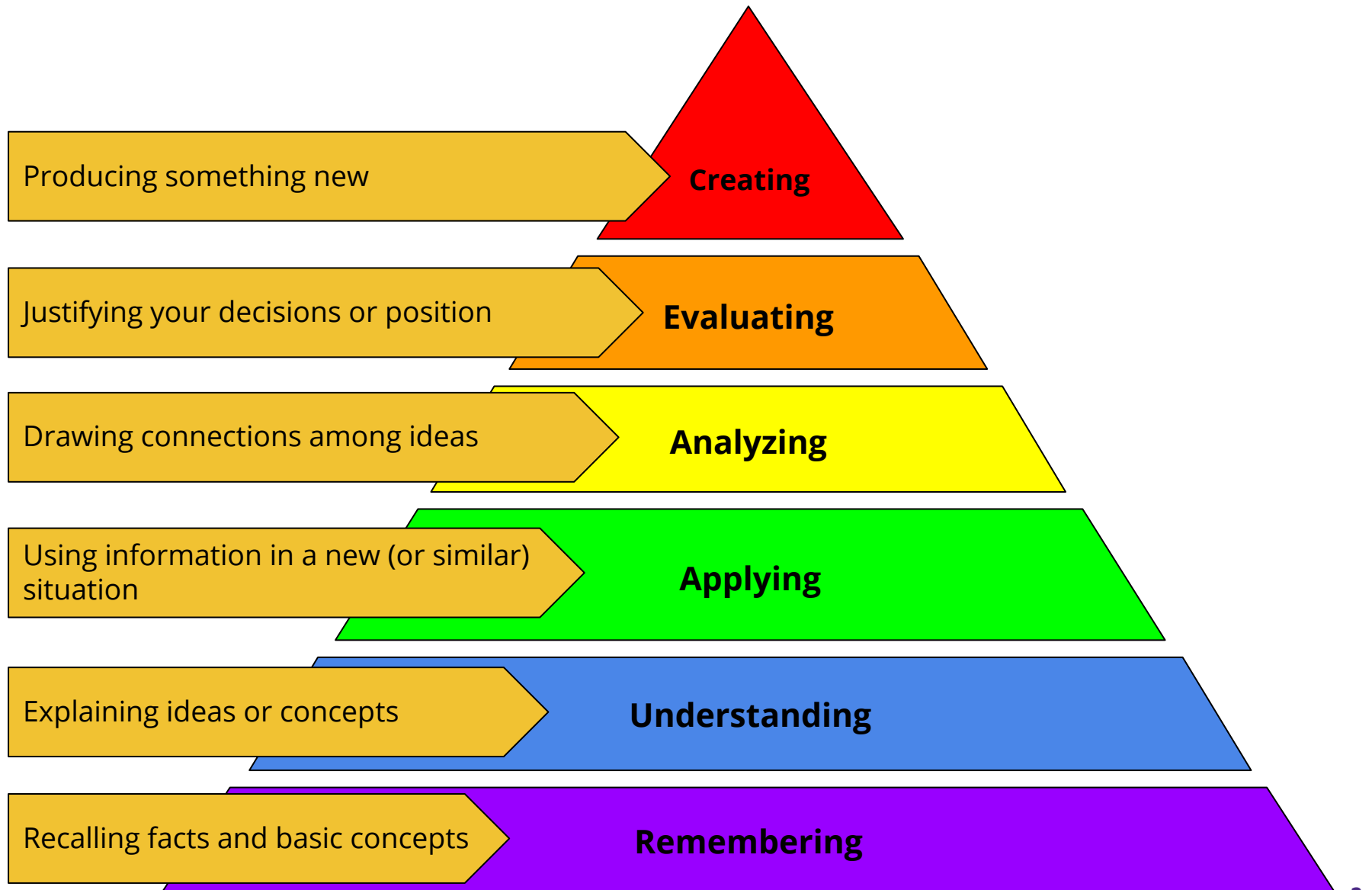

Bloom's Taxonomy in Action

 


Bloom's Taxonomy Discussion

In groups of 3-4, discuss the following points:

- ❖ Identify various aspects of your academic responsibilities as a UW student (e.g., attending lecture) and categorize them in one of the levels on Bloom's Taxonomy

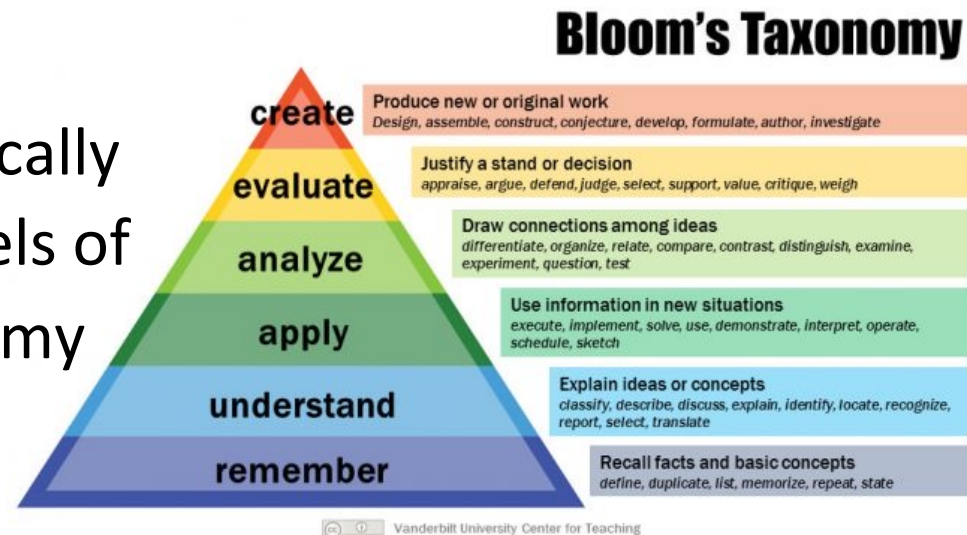- ❖ Discuss how you can practically engage in higher-order levels of thinking in Bloom's Taxonomy




Lecture Outline

- ❖ Bloom's Taxonomy
 - Applying Higher Levels of Cognition to Learning
- ❖ Introduction to Sequential Logic
 - The Problem with Combinational Logic
- ❖ Representing Time in Hardware
 - Clock Signals and Units of Time in Hardware
- ❖ The Data Flip-Flop (DFF)
 - Implementation and Examples


Why Consider Time Now?

 - ❖ Needed for our **abstraction**
 - We need to talk about hardware maintaining state for memory
 - We need vocabulary to talk about time
- ❖ Needed for our **implementation**
 - Physical implementations of chips cannot be instantaneous
 - We need to account for physical delays in signal propagation



The Problem with Combinational Logic


- ❖ Consider the following circuit:

 

- ❖ Let's assume that $a=0$, $b=1$, and $c=0$
 - The output should be 1
- ❖ What's the result if we change $b=0$ and $c=1$?
 - The result should still be 1
 - However, `out` is briefly 0 if we change c first


Autopilot Control Circuit Example

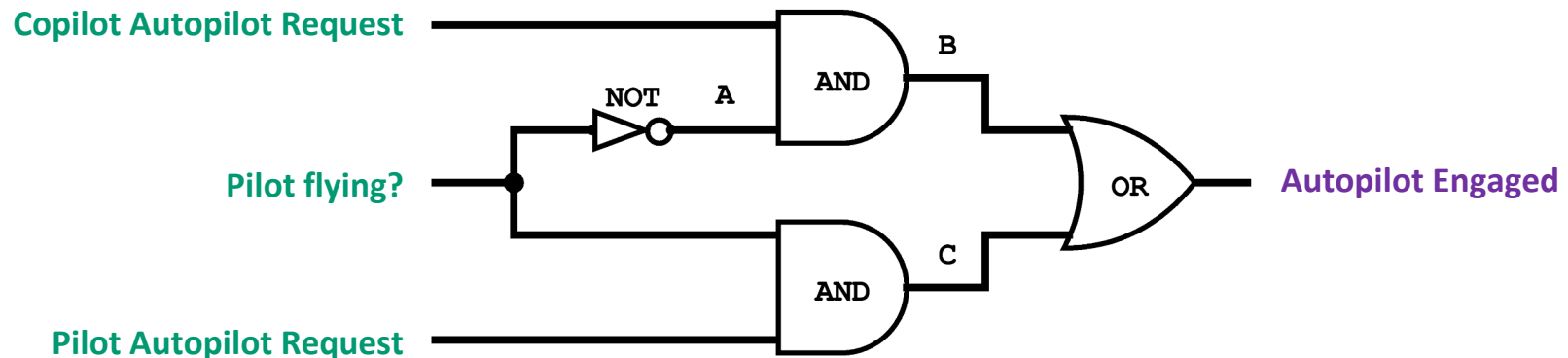- ❖ Consider this autopilot control circuit:
 - Either the pilot or copilot is flying at any time
 - The pilot and copilot can separately request autopilot
 - Only the person flying can request autopilot





Autopilot Control Circuit Example

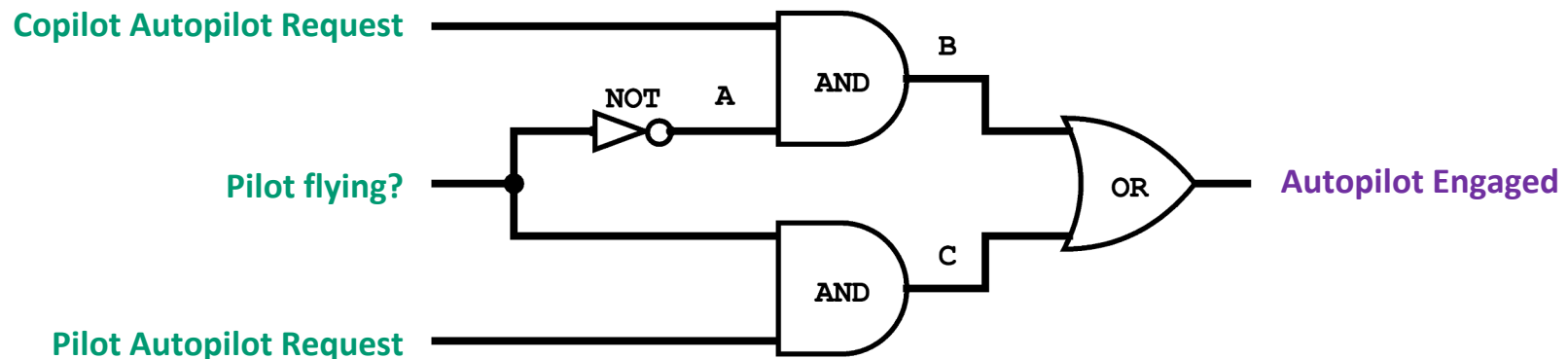- ❖ Consider this autopilot control circuit:
 - Either the pilot or copilot is flying at any time
 - The pilot and copilot can separately request autopilot
 - Only the person flying can request autopilot





- ❖ Let's assume every logic gate takes 1ms to compute
 - For example, if an input changes at $t=4\text{ms}$, the gate will only output the new result at $t=5\text{ms}$



Autopilot Control Circuit Example

  



Autopilot Control Circuit Example

 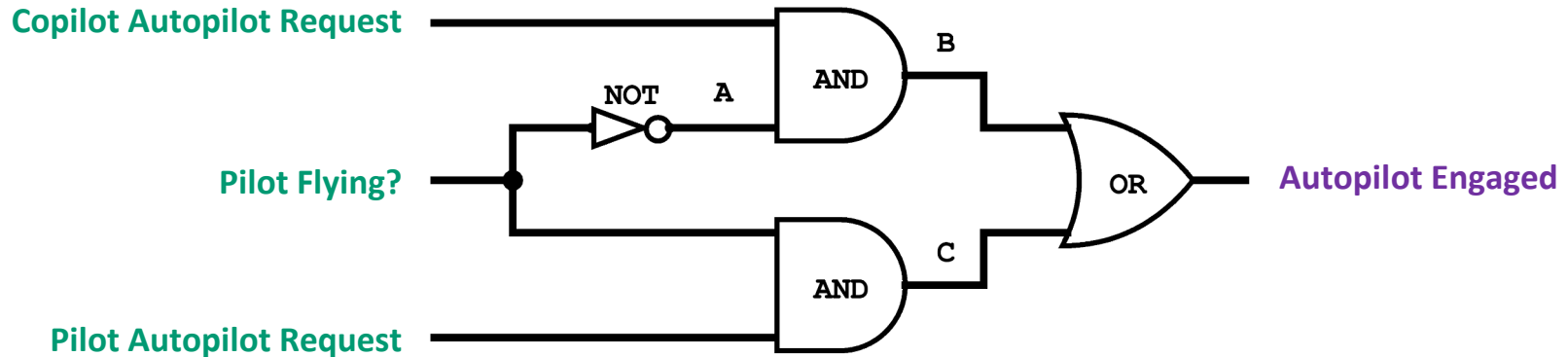



Autopilot Control Circuit Example

 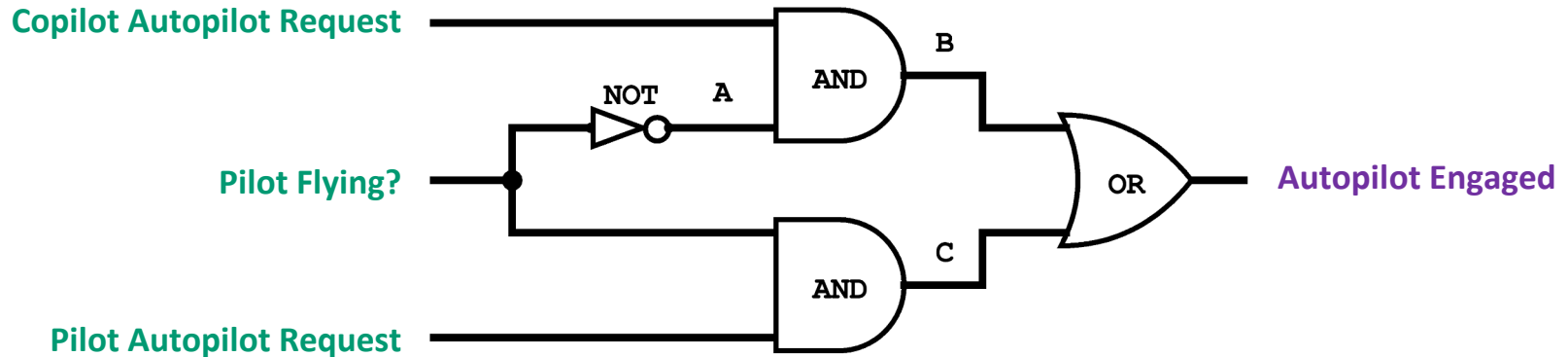

Autopilot Control Circuit Example

  



Autopilot Control Circuit Example

  



Vote at <https://pollev.com/cse390b>

 
 
Describe the behavior of the Autopilot Engaged (**AE**) output between 1ms to 6ms.







Vote at <https://pollev.com/cse390b>

  Describe the behavior of the Autopilot Engaged (AE) output between 1ms to 6ms.



Autopilot Control Circuit Example

 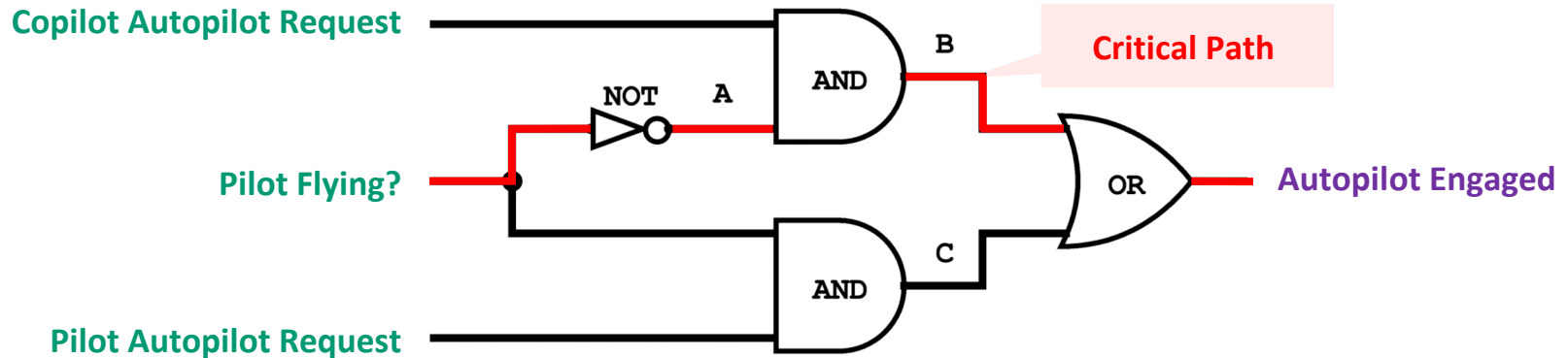


Combinational vs. Sequential Logic

- ❖ So far, we have ignored “time” in our circuits
- ❖ Our chips used **combinational logic**
 - When given inputs, the chip computes its output instantaneously
 - The output is a function of the current inputs, with no memory of previous events
- ❖ Today, we'll start exploring what happens when we consider time, ultimately building to **sequential logic**


What is Sequential Logic?

- ❖ Sequential logic incorporates time in hardware
- ❖ Output depends on present value of its input signals *and* a sequence of past inputs
- ❖ Sequential logic resolves the problem introduced with combinational logic
 - Does so by adding a **delay** for the entire circuit before evaluating the result
 - All the circuits will be evaluated between one **clock cycle** and the output will be evaluated at the end of the clock cycle


Combinational vs. Sequential Abstraction

 

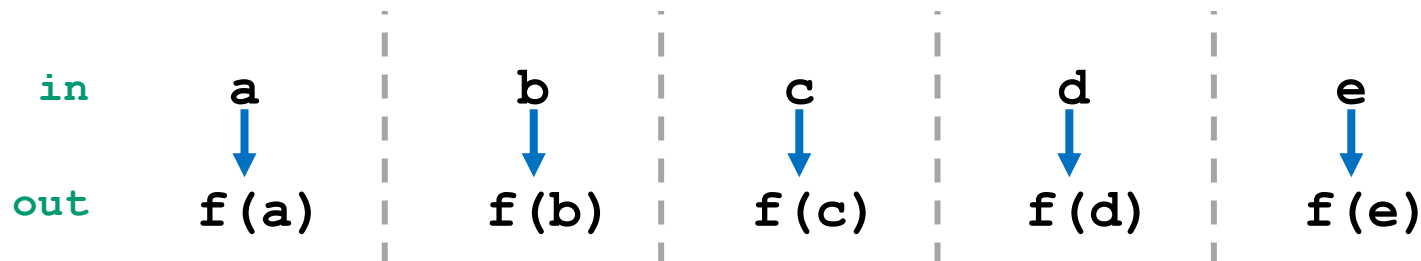Combinational: a function of the current inputs



 Sequential: a function of previous inputs (has “memory”)




Lecture Outline

- ❖ Bloom's Taxonomy
 - Applying Higher Levels of Cognition to Learning
- ❖ Introduction to Sequential Logic
 - The Problem with Combinational Logic
- ❖ **Representing Time in Hardware**
 - **Clock Signals and Units of Time in Hardware**
- ❖ The Data Flip-Flop (DFF)
 - Implementation and Examples

Representing Time: Clock Signals

- ❖ We physically represent time in hardware with a **clock signal**
 - A clock signal changes its frequency at a set time rate
 - Alternates between a low signal and a high signal of equal length
- ❖ A **cycle** is a period of time between a low and high signal
 - Represents one unit of time in hardware
 - We can change how long a unit of time is by alternating the length of the low and high signals

 

Physical Timekeeping

- ❖ Hardware keeps track of time using an alternating signal
 - Creates the idea of **discrete time**: state changes only occur in discrete intervals, right when signal alternates

Physical
Time




Clock
Signal

1
0




Physical Timekeeping

 
- ❖ Hardware keeps track of time using an alternating signal
 - Creates the idea of **discrete time**: state changes only occur in discrete intervals, right when signal alternates



Adding a Clock: Ideal

 


 - ❖ We want this behavior from a simple, combinational Not gate:




Adding a Clock: Reality

 - ❖ Combinational logic may be incorrect for a period immediately after inputs change
 - **Computation delays** (logic gates) and **propagation delays** (wires)




Adding a Clock: Clock Cycles

 - ❖ Choose a clock cycle length slightly longer than the delays



Adding a Clock: Abstraction

 - ❖ If we use a long enough clock cycle, we can *pretend* that combinational chips (like Not) work instantly



Five-minute Break!

- ❖ Feel free to stand up, stretch, use the restroom, drink some water, review your notes, or ask questions
- ❖ We'll be back at:





Vote at <https://pollev.com/cse390b>

Which of the following statements about sequential logic is FALSE?


- A. We represent time with a clock signal that alternates between high and low signals**
- B. The DFF allows us to reuse outputs as inputs in a circuit**
- C. The outputs for a DFF at time $t=2$ is determined by the inputs at time $t=3$**
- D. Sequential logic is important because it addresses slight delays caused in circuit gates**
- E. We're lost...**

Lecture Outline

- ❖ Bloom's Taxonomy
 - Applying Higher Levels of Cognition to Learning
- ❖ Introduction to Sequential Logic
 - The Problem with Combinational Logic
- ❖ Representing Time in Hardware
 - Clock Signals and Units of Time in Hardware
- ❖ **The Data Flip-Flop (DFF)**
 - **Implementation and Examples**

The Data Flip-Flop Gate

 - ❖ Simplest state-keeping component
 - 1-bit input, 1-bit output
 - Wired to the clock signal
 - Always outputs its previous input: $\text{out}(t) = \text{in}(t-1)$
- ❖ Implementation: a gate that can flip between two stable states (remembering 0 vs. remembering 1)
 - Gates with this behavior are “Data Flip Flops” (DFFs)





Aside: Treating the DFF as a Primitive

- ❖ Disclaimer: DFFs can be made from Nand gates exclusively
 - But requires wiring them together in a “messy” loop that the hardware simulator can't simulate and isn't very educational

- ❖ For simplicity, we will treat the DFF as a primitive in the projects
 - Just like Nand, you can use the built-in implementation

Data Flip-Flop (DFF) Behavior

  

Sequential Chips


- ❖ A category of chips that utilize the clock signal, in addition to any combinational logic

- ❖ Capable of:
 - Maintaining state
 - Optionally, acting on that state and the current inputs
 - Can incorporate combinational logic as well

- ❖ Constructed from:
 - DFFs
 - Combinational logic (which is entirely constructed from Nand)


Sequential Chips
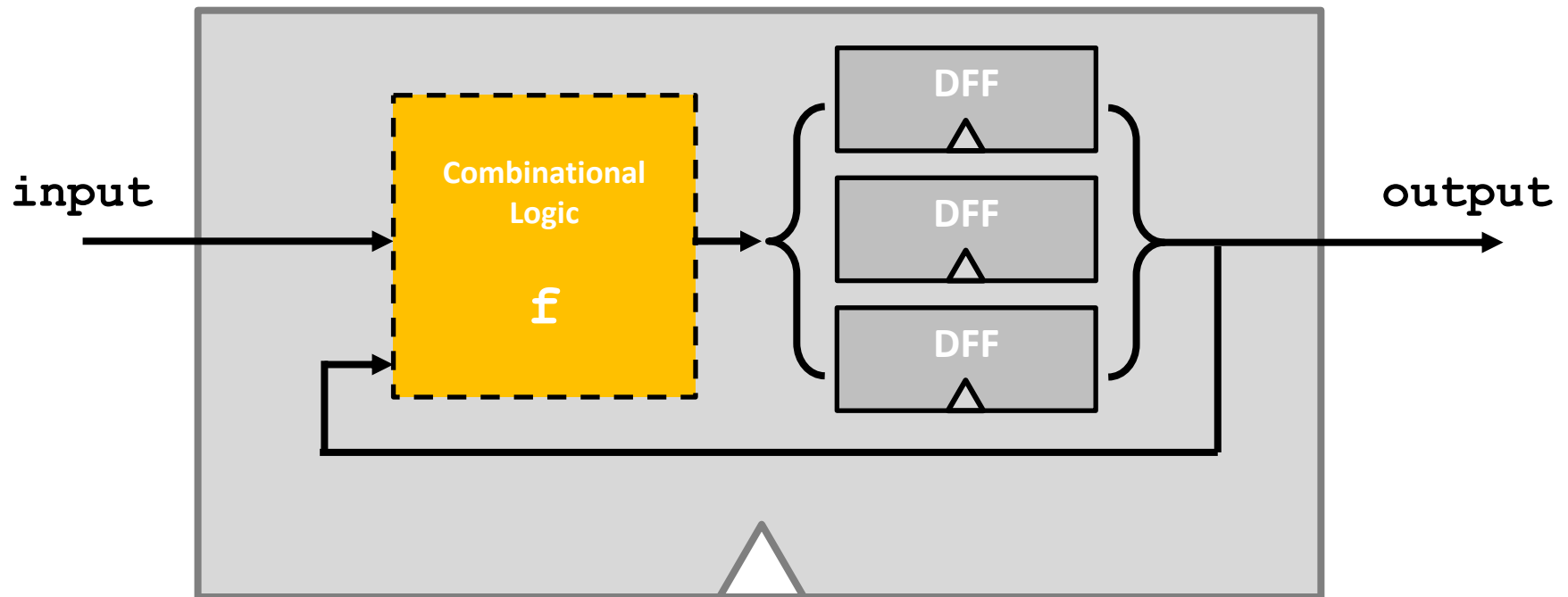
$$\text{output}(t) = f(\text{state}(t-1), \text{input}(t))$$



D Flip-Flop: Time Series

❖ DFF Specification:

 

$$\text{out}(t) = \text{in}(t-1)$$

in	0	0	1	1	0	1	0	...
out	0	0	0	1	1	0	1	...
time	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

Example: $\text{out}(t=3) = \text{in}(t=2)$

DFF Example 1: Specification

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

- ❖ Takes two inputs, a and b , and outputs the Xor of them
 - Note that out at time t is determined by a and b at time $t-1$
 - We will need to use a DFF
- ❖ Exercise: Draw out the corresponding circuit diagram and HDL implementation

DFF Example 1: Time Series

❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

a	0	0	1	1	1	0	0	...
b	0	1	0	1	1	1	0	...
out	0	0	1	1	0	0	1	...
time	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

❖ Example: $\text{out}(t=3) = \text{Xor}(a(t=2), b(t=2))$

DFF Example 1: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

- ❖ Circuit diagram:


- ❖ HDL:

DFF Example 1: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

- ❖ Circuit diagram:

 

- ❖ HDL:

```
CHIP Example1 {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
    Xor(a=a, b=b, out=xorout);  
    DFF(in=xorout, out=out);  
}
```

DFF Example 2: Specification

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Notice how the specification uses $\text{out}(t-1)$ as an input for $\text{out}(t)$
 - Implies the necessity of circular wiring, separated by a DFF
- ❖ Exercise: Draw out the corresponding circuit diagram and HDL implementation

DFF Example 2: Time Series

❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

in	0	0	1	1	1	0	0	...
out	0	0	0	1	0	1	1	...
time	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

❖ Example: $\text{out}(t=1) = \text{Xor}(\text{in}(t=0), \text{out}(t=0))$

DFF Example 2: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Circuit diagram:


- ❖ HDL:

DFF Example 2: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Circuit diagram:

 

- ❖ HDL:

```
CHIP Example2 {
```

```
  IN in;
```

```
  OUT out;
```

```
  PARTS:
```

```
    Xor(a=in, b=prevout, out=xorout);
```

```
    DFF(in=xorout, out=prevout, out=out);
```

```
}
```

DFF Example 3: Specification

- ❖ Example specification:

$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$

- ❖ Exercise: Draw out the corresponding circuit diagram and HDL implementation

DFF Example 3: Time Series

❖ Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

in	1	1	0	1	1	0	0	...
out	0	1	0	0	1	0	0	...
time	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

❖ Example:

$$\text{out}(t=1) = \text{And}(\text{Not}(\text{out}(t=0)), \text{in}(t=0))$$

DFF Example 3: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

- ❖ Circuit diagram:


- ❖ HDL:

DFF Example 3: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

- ❖ Circuit diagram:

 

- ❖ HDL:

```
CHIP Example3 {
```

```
    IN in;
```

```
    OUT out;
```

```
    PARTS:
```

```
    Not(in=prevout, out=notprevout);
```

```
    And(a=in, b=notprevout, out=andout);
```

```
    DFF(in=andout, out=prevout, out=out);
```

```
}
```

Post-Lecture 6 Reminders

- ❖ Exciting lecture topics this Thursday!
 - Metacognitive Subject: Cornell Note-taking Method
 - Technical Subject: Computer Memory

- ❖ **Project 3 due this Thursday (10/20) at 11:59pm**

- ❖ Preston has office hours after class in CSE2 153
 - Feel free to post your questions on the Ed board as well