CSE 390B, Autumn 2022 Building Academic Success Through Bottom-Up Computing **Cornell Note-taking & Building Memory**

Cornell Note-taking Method, Storing Data, Representing and Building Memory, Program Counter Overview

W UNIVERSITY of WASHINGTON

Lecture Outline

- Cornell Note-taking Method
 - System for Taking, Organizing, and Reviewing Notes
- Review of Sequential Logic and DFFs
- Storing Data: Bit
 - Bit Overview and Implementation
- Representing and Building Memory
 - Array Abstraction, Building From the Bit
- Program Counter (PC) Overview
 - Control Flow of Computer Programs





Cornell Note Taking Method

| Questions | Notes | | | | | | |
|---|---|--|--|--|--|--|--|
| Compose a question that corresponds to | I. Main Topic ○ Sub point ○ <u>definition</u> ○ example ** | | | | | | |
| the notes you took | II. Object-Oriented Programming Encapsulates the data and the operations for a | | | | | | |
| In what ways is object-oriented programming more extensible than functional programming? | given data type Provides abstractions - you don't need to know how a car is implemented in order to use it Extensibility - easier to add new data types | | | | | | |
| | III. Functional Programming ○ Extensibility - easier to <u>add new operations</u> | | | | | | |
| Summary | | | | | | | |
| Object-oriented programming and functional | | | | | | | |

Object-oriented programming and functional programming are two types of programming paradigms...

Cornell Note Taking Method



Applying the Cornell Note-Taking Method

- Try it during today's technical lecture!
- Next week, we'll provide you with an opportunity to discuss your notes with your classmates
- You will also practice it with one of your other classes as part of Project 4

Lecture Outline

- Cornell Note-taking Method
 - System for Taking, Organizing, and Reviewing Notes

Review of Sequential Logic and DFFs

- Storing Data: Bit
 - Bit Overview and Implementation
- Representing and Building Memory
 - Array Abstraction, Building From the Bit
- Program Counter (PC) Overview
 - Control Flow of Computer Programs

Poll Everywhere

Vote at https://pollev.com/cse390b

Describe the behavior of the Autopilot Engaged (AE) output between 1ms to 6ms.





Autopilot Control Circuit Example



Physical Timekeeping

Hardware keeps track of time using an alternating signal

 Creates the idea of discrete time: state changes only occur in discrete intervals, right when signal alternates



Discrete Time Intervals

Adding a Clock: Clock Cycles

Choose a clock cycle length slightly longer than the delay length of the critical path > 3ms



The Data Flip-Flop Gate

- Simplest state-keeping component
 - 1-bit input, 1-bit output
 - Wired to the clock signal
 - Always outputs its previous input: out(t) = in(t-1)
- Implementation: a gate that can flip between two stable states (remembering 0 vs. remembering 1)
 - Gates with this behavior are "Data Flip Flops" (DFFs)



Data Flip-Flop (DFF) Behavior



Sequential Chips

output(t) = f(state(t-1), input(t))



D Flip-Flop: Time Series



DFF Specification:

out(t) = in(t-1)

| in | 0 | 0 | 1 | 1 | 0 | 1 | 0 | ••• |
|------|-----|-----|-----|-----|-----|-----|-----|-------|
| out | 0 | 0 | 0 | 1 | 1 | 0 | 1 | • • • |
| time | t=0 | t=1 | t=2 | t=3 | t=4 | t=5 | t=6 | ••• |

Example:
$$out(t=3) = in(t=2)$$

DFF Example 1: Specification

Example specification:

```
out(t) = Xor(a(t-1), b(t-1))
```

- Takes two inputs, a and b, and outputs the Xor of them
 - Note that out at time t is determined by a and b at time t-1
 - We will need to use a DFF
- Exercise: Draw out the corresponding circuit diagram and HDL implementation

DFF Example 1: Time Series

Example specification:

out(t) = Xor(a(t-1), b(t-1))



* Example: out(t=3) = Xor(a(t=2), b(t=2))

DFF Example 1: Circuit Diagram & HDL

Example specification:

```
out(t) = Xor(a(t-1), b(t-1))
```

Circuit diagram:



DFF Example 1: Circuit Diagram & HDL

Example specification:

out(t) = Xor(a(t-1), b(t-1))

Circuit diagram:



CHIP Example1 {
 * HDL: IN a, b;
 OUT out;

}

PARTS: Xor(a=a, b=b, out=xorout); DFF(in=xorout, out=out);

Lecture Outline

- Cornell Note-taking Method
 - System for Taking, Organizing, and Reviewing Notes
- Review of Sequential Logic and DFFs
- Storing Data: Bit
 - Bit Overview and Implementation
- Representing and Building Memory
 - Array Abstraction, Building From the Bit
- Program Counter (PC) Overview
 - Control Flow of Computer Programs

Computer Overview

- CPU is the "brain" of our computer
 - Does necessary computations (add, subtract, multiply, etc.)
- Memory is used to store values for later use
 - Requires persistence across multiple computations
 - Needs to change values at our discretion



Storing Data: Bit

A Flip-Flop changes state *every* clock cycle

We will build the abstraction of a "Bit" that only changes when we instruct it to



Bit Behavior



Bit Behavior



Bit Time Series

Bit Specification:

if
$$(load(t-1))$$
: $out(t) = in(t-1)$
else: $out(t) = out(t-1)$

| | | t=1 | | | | | | |
|------|---|-----|---|---|---|---|---|-------|
| out | 0 | 1 | 1 | 1 | 0 | 1 | 0 | • • • |
| in | 1 | 0 | 0 | 0 | 1 | 0 | 1 | ••• |
| load | 1 | 0 | 0 | 1 | 1 | 1 | 0 | • • • |

Example 1: load (t=0) == 1 so out(t=1) = in(t=0)

Bit Time Series

Bit Specification:

if
$$(load(t-1))$$
: $out(t) = in(t-1)$
else: $out(t) = out(t-1)$

| | 1 | | | | | | | |
|------|-----|-----|-----|-----|-----|-----|-----|-----|
| | 0 | | | | | | | |
| time | t=0 | t=1 | t=2 | t=3 | t=4 | t=5 | t=6 | ••• |

* Example 1: load(t=0) == 1, so out(t=1) = in(t=0)

Example 2: load(t=2) == 0, so out(t=3) = out(t=2)



Vote at https://pollev.com/cse390b

Which gates will we need to implement a Bit? Select all that apply.

- A. Mux
- B. Xor
- C. And
- D. DFF
- E. We're lost...



if load(t-1) out(t) = in(t-1) else out(t) = out(t-1)

Implementing a Bit

- Bit Specification:
 if load(t-1) out(t) = in(t-1)
 else out(t) = out(t-1)
- Exercise: fill in the connections to the gates to create a circuit diagram of Bit

Implementing a Bit

- Bit Specification:
 if load(t-1) out(t) = in(t-1)
 else out(t) = out(t-1)
- Exercise: fill in the connections to the gates to create a circuit diagram of Bit



Five-minute Break!

- Feel free to stand up, stretch, use the restroom, drink some water, review your notes, or ask questions
- We'll be back at:



Lecture Outline

- Cornell Note-taking Method
 - System for Taking, Organizing, and Reviewing Notes
- Review of Sequential Logic and DFFs
- Storing Data: Bit
 - Bit Overview and Implementation
- Representing and Building Memory
 - Array Abstraction, Building From the Bit
- Program Counter (PC) Overview
 - Control Flow of Computer Programs

Memory Representation

Memory can be abstracted as one huge array

Addresses are indices into different memory slots

- The width of an address is fixed for the system
- The nand2tetris project will use 16-bit addresses
- Each value in memory takes up a fixed width
 - Not the same as address width
 - The nand2tetris project uses 16-bit slots (values) in memory

Memory Representation

Can read and write to memory by specifying an address

- More details next week
- * Example: x = memory[01...00]
 - Reads the value in memory at address 01...00 and stores it in x
- * Example: memory[01...00] = 7
 - Writes the value 7 in the memory slot at address 01...00

Building Memory: Register

Bits store a single value (0 or 1)

- In memory, we need to store 16-bit values
- Registers are conceptually the same as a Bit
 - Allows us to store and change 16-bit values
 - Groups together 16 individual bits that share a load signal

RAM: Random Access Memory

- Abstraction of Computer Memory: just a giant array
- Goal: create hardware that can provide that abstraction

| | 24 11000 | 25 11001 | 26 11010 | | 29 11101 | 30 11110 | 31 11111 | |
|-----|---------------------|--------------------|----------------------|-----------------------|---------------------|--------------------|--------------------|-----|
| ••• | 0 0000000 | | -1 1111111 | 124 1111100 | 0 0000000 | | | ••• |

Key attribute of arrays: "random access" lets us index into them at any point

$$memory[26] = -1;$$

Building Memory: RAM8 From Registers

RAM interface:

- address: address used to specify memory slot
- in: 16-bit input used to update specified memory slot if load is 1
- load: if 1, then in should be written to specified memory slot
- out: 16-bit output from the slot specified by address



- RAM8 can be built from 8 registers
 - address width is log₂(8) = 3 bits

Building Memory: RAM8 From Registers



- We don't want to update every register, however
- Solution: choose which register to enable with address
- Step 2: Choose which register to use for the output



When we think about making choices in hardware, we want to think about Mux and DMux

Building Memory: The Rest of RAM

- After RAM8, can build larger RAM chips from a combination of smaller RAM chips
 - For example, RAM64 can be built using eight RAM8 chips
- Technique is similar to RAM8 but will have to use different portions of the address
- The blocks section of the reading will be helpful
 - For example, can think of each RAM8 as a block of RAM64

Lecture Outline

- Cornell Note-taking Method
 - System for Taking, Organizing, and Reviewing Notes
- Review of Sequential Logic and DFFs
- Storing Data: Bit
 - Bit Overview and Implementation
- Representing and Building Memory
 - Array Abstraction, Building From the Bit
- Program Counter (PC) Overview
 - Control Flow of Computer Programs

Program Counter (PC)

- Memory is used to store data as well as code
- Instructions and operations are stored at different addresses in memory
- Program Counter in the CPU keeps track of which address contains the instruction that should be executed next



Program Counter (PC)

Keeps track of what instruction we are executing

 If the PC outputs 24, on the next clock cycle the computer runs the instruction at address 24 in the code segment

Program counter specification:

if (reset[t] == 1) out[t+1] = 0
else if (load[t] == 1) out[t+1] = in[t]
else if (inc[t] == 1) out[t+1] = out[t] + 1
else out[t+1] = out[t]



Project 4 Overview

Part I: Cornell Note Taking

- Practice taking detailed notes in another class
- Think critically about the technique
- Part II: Building Memory
 - Memory & Sequential Logic: Build our first sequential chips, from a 1-bit register to a 16K RAM module
 - Program Counter: Build counter that tracks where we are in a program, with support for several operations we'll need later
 - Note: Folder split for performance reasons only

Part III: Project 4 Reflection

Post-Lecture 7 Reminders

- Project 3 due tonight (10/20) at 11:59pm
- Project 4 (Cornell Note Taking & Building Memory) released today, due next Thursday (10/27) at 11:59pm
- Course Staff Support
 - Eric has office hours in CSE2 153 today after lecture
 - Post your questions on the Ed discussion board