

CSE 390B, Spring 2022

Building Academic Success Through Bottom-Up Computing

Study Environment, HDL, & Boolean Logic

Study Environment Discussion, Boolean Logic and Functions,
Hardware Descriptive Language, Project 2 Overview

Course Staff Introductions



Eric Fan

Audrey Ma

Sean Le

Ghislaine Ng

Preston Rivas

privas@cs.washington.edu

I'm currently a second year student and I can't wait to be your TA for CSE 390B! I grew up in La Conner Washington, which is about an hour north of Seattle, but I was born in San Diego, California. When not doing school work I enjoy running, hiking, kayaking, paddle boarding and hammocking (if you know any cool spots around UW to hang a hammock let me know!). I'm also a big fan of indie music and especially love listening to Peach Pit. If you find yourself stuck don't hesitate to reach out for help! I'm always willing to lend a hand, even if its something not related to CS/UW!

Project 1 Check-in

- ❖ The specification says Project 1 will take 30-60 minutes
 - Likely an underestimation
 - It may be taking longer for you, and that's okay
- ❖ Seeing some **GREAT** questions and answers on Ed!
- ❖ Your terminal setup will unlikely look the same as mine, and that's okay
 - Just ensure that the commands are correct
- ❖ **Double-check** your submission on GitLab!
 - Navigate to GitLab, open tags, and verify that the associated commit includes your expected changes

Lecture Outline

- ❖ **Study Environment Discussion**
- ❖ **Boolean Logic and Functions**
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
 - The Foundational Gate: NAND
- ❖ **Hardware Descriptive Languages (HDL)**
 - HDL Syntax, **And** Gate Example
- ❖ **Project 2 Overview**
 - **Xor** Implementation Example in HDL

Study Environment Discussion

In groups of 3-4, discuss the following questions about study environments:

- ❖ On a typical day, what does your study environment look like? **Be specific!**

- ❖ What contributes to an effective study environment? Why?
 - What changes can you make to introduce some of these factors?

- ❖ What factors hinder a study environment from being effective? Why?
 - What changes can you make to remove some of these factors?

Lecture Outline

- ❖ Study Environment Discussion
- ❖ **Boolean Logic and Functions**
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
 - The Foundational Gate: NAND
- ❖ Hardware Descriptive Languages (HDL)
 - HDL Syntax, **And** Gate Example
- ❖ Project 2 Overview
 - **Xor** Implementation Example in HDL



Vote at <https://pollev.com/cse390b>

Pre-lecture Reading Question: Which of the following statements is FALSE?

- A. The Boolean Function Synthesis strategy works on every truth table
- B. In CSE 390B, we will be asking you to write Boolean expressions that are simplified
- C. The abstraction of voltages on a physical wire represents two values
- D. A truth table lists every possible combination of inputs for a Boolean operation
- E. We're lost...

Boolean Values

- ❖ A binary choice: **True** or **False**
- ❖ Also known as a “low” signal (false, “off,” or 0) and a “high” signal (true, “on”, or 1)



“Off”

False

0



“On”

True

1

Boolean Operations

- ❖ Use logical operations to combine Boolean values
 - **Truth table:** A table that lists every possible set of inputs and the corresponding output of the operation
 - Operations correspond to physical hardware gates

- ❖ Examples:

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

$$F = A \text{ OR } B$$


A	F
0	1
1	0

$$F = \text{NOT } A$$

Boolean Operations

- ❖ Combinations of Boolean inputs
- ❖ Three ways to specify a Boolean function:
 - Boolean expression: $F = \text{NOT} ((A \text{ OR } B) \text{ AND } C)$
 - Circuit diagram with logic gates:
 - Truth table:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Boolean Expression \rightarrow Truth Table

- ❖ We know how to build a truth table from an expression
 - Evaluate the Boolean expression on all possible inputs

$$F(A, B, C) = \text{NOT} ((A \text{ OR } B) \text{ AND } C)$$



A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Boolean Expression \rightarrow Truth Table

- ❖ We know how to build a truth table from an expression
 - Evaluate the Boolean expression on all possible inputs

$$F(A, B, C) = \text{NOT} ((A \text{ OR } B) \text{ AND } C)$$




A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression \leftarrow Truth Table

❖ But can we do it in reverse?

$$F(A, B, C) = ?$$

 

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression ← Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

A AND B AND C

Boolean Expression ← Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C


A AND B AND C

$F = \text{NOT}(A) \text{ AND NOT}(B) \text{ AND } C \text{ OR NOT}(A) \text{ AND } B \text{ AND } C \text{ OR } A \text{ AND } B \text{ AND NOT } C \text{ OR } A \text{ AND } B \text{ AND } C$

Boolean Expression ← Truth Table

- ❖ But can we do it in reverse?
 - Yes, we can! The strategy we used is **Boolean Function Synthesis**
 
$$F(A, B, C) = \text{NOT} ((A \text{ OR } B) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

The Foundational Gate: Nand

- ❖ It all starts with the NAND gate
- ❖ NAND is short for “Not And”
 - The same output as the AND gate, but every output bit is negated (flipped)

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

$$F = A \text{ NAND } B$$

Building Gates From Nand

- ❖ Recall the **Boolean Function Synthesis** strategy from today's reading
 - We saw how we can represent any truth table in terms of three gates: **Not**, **And**, **Or**
- ❖ First, we can represent **Not** directly from **Nand**
 - $\text{Not } a = a \text{ Nand } a$
- ❖ Then, we can represent **And** in terms of **Not** and **Nand**
 - $a \text{ And } b = \text{Not } (a \text{ Nand } b)$
- ❖ Represent **Or** in terms of **Not** and **And**
 - Apply De Morgan's Law
 - $a \text{ Or } b = \text{Not } (\text{Not } (a) \text{ And } \text{Not } (b))$ [De Morgan's Law]

Lecture Outline

- ❖ Study Environment Discussion

- ❖ Boolean Logic and Functions
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
 - The Foundational Gate: NAND

- ❖ **Hardware Descriptive Languages (HDL)**
 - **HDL Syntax, And Gate Example**

- ❖ Project 2 Overview
 - **Xor** Implementation Example in HDL

Hardware Design Language (HDL)

- ❖ HDL is a programming language to specify hardware components and how they're connected
 - *Yet another* way of writing a Boolean function
- ❖ Many Hardware Design Languages are use today
 - E.g., VHDL, Verilog, SystemVerilog
 - In this course, we'll use a simple HDL language called "HDL"
- ❖ Unlike Java, HDL is a **declarative** language. This means...
 - The order of statements (lines of code) doesn't matter
 - We are describing a physical system

Hardware Design Language (HDL)

❖ Makeup of an HDL file

- File comment describes expected behavior
- **IN** names chip inputs, **OUT** names chip outputs
- **PARTS** specify the components that implement the chip
 - For Project 2, this will mostly be specifying Boolean functions

```
/**
 * And gate:
 * out = 1 only if both a and b are 1
 */
CHIP And {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Reusing Components

- ❖ You can use chips you have already implemented to implement subsequent chips
- ❖ We give you one gate, **Nand**, to start out with
 - Implication: Your entire computer is essentially built on **Nand** gates
- ❖ We also give you some chips you can use without implementing
 - See project specification for more details


HDL Component Example: AND

- ❖ The chip specification tells us the name of the input and output wires

```
CHIP And {  
    IN a, b;  
    OUT out;  
  
    ...  
}
```

- ❖ Goal: Implement $w1$ AND $w2$

 - HDL Syntax: `And (a=w1, b=w2, out=w3);`
- Equivalent circuit diagram:



Multi-bit Buses in HDL

- ❖ It can be useful to manipulate groups of wires
 - Called a “bus” of wires
- ❖ HDL provides array like syntax for manipulating buses
 - **And4** chip example:

```
/**
 * Bit-wise And of two 4-bit inputs
 */
CHIP And4 {
    IN a[4], b[4];
    OUT out[4];

    PARTS:
    And (a=a[0], b=b[0], out=out[0]);
    And (a=a[1], b=b[1], out=out[1]);
    And (a=a[2], b=b[2], out=out[2]);
    And (a=a[3], b=b[3], out=out[3]);
}
```

HDL Resources

- ❖ HDL will feel unfamiliar at first, and that's okay
- ❖ Some resources for helping you navigate HDL (these are all linked under the [Resources page](#) on the course website)
 - HDL Survival guide
 - Appendix A (HDL Spec)
 - Chip Set Overview (to help you remember the inputs/outputs for various chips)
 - Chapter readings

Five-minute Break!

- ❖ Feel free to stand up, stretch, use the restroom, drink some water, review your notes, or ask questions
- ❖ We'll be back at:
- ❖ Please sign up for your first 1:1 Student-TA meeting now if you have not already (signup sheet linked [here](#))
- ❖ Any song recommendations? Respond on Poll Everywhere at <https://pollev.com/cse390b>

Lecture Outline

- ❖ Study Environment Discussion
- ❖ Boolean Logic and Functions
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
 - The Foundational Gate: NAND
- ❖ Hardware Descriptive Languages (HDL)
 - HDL Syntax, **And** Gate Example
- ❖ **Project 2 Overview**
 - **Xor** Implementation Example in HDL

Project 2 Overview

- ❖ Part I: Study Skills Inventory
 - Self-assessing your skill level in various study practices and habits
- ❖ Part II: Boolean Logic
 - Clone your GitLab repository, write and test your code
- ❖ Part III: Project 2 Reflection
 - Reflect on your experience working through Project 2
- ❖ **Due next Thursday (4/7) at 11:59pm PDT**

Project 2 Overview

- ❖ Every logic gate in our computer can be implemented in terms of **Nand**
- ❖ We provide you only **Nand** to start Project 2
- ❖ You will build other basic gates (**Not**, **And**, etc.) in terms of **Nand** and then build increasingly complex gates
- ❖ Culminates to building a computer that, at its core, is entirely based on **Nand** gates

Project 2 Example: Xor

- ❖ Let's walk through an example of a gate that you will be implementing in Project 2
- ❖ Together, we'll implement the **Xor** gate

```
/**
 * Xor gate:
 * out = not(a == b)
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Project 2 Example: Xor

❖ Plan of action:

- Step 1: Create the logic operation's **truth table**
- Step 2: Use truth table to generate a **Boolean function** using strategies we've learned, such as the Boolean Function Synthesis
- Step 3: Convert Boolean function to **HDL**

```
/**  
 * Xor gate:  
 * out = not(a == b)  
 */  
CHIP Xor {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
    // Put your code here:  
}
```

Project 2 Example: Xor

- ❖ Step 1: Create the truth table for **Xor**
 - Interpret the specification: $F = \text{NOT}(A == B)$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

$$F = A \text{ XOR } B$$

Project 2 Example: Xor

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Project 2 Example: Xor

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading
 - Row 2 = NOT(A) AND B

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Project 2 Example: Xor

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading
 - Row 2 = NOT(A) AND B
 - Row 3 = A AND NOT(B)
 - $F = ?$

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$



Vote at <https://pollev.com/cse390b>

What is the unsimplified Boolean expression result from performing Boolean function synthesis on $F = A \text{ XOR } B$?

- A. $(A \text{ AND } \text{NOT}(B)) \text{ AND } (\text{NOT}(A) \text{ AND } B)$
- B. $(\text{NOT}(A) \text{ AND } B) \text{ AND } (A \text{ AND } B)$
- C. $(A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } \text{NOT}(B))$
- D. $(\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$
- E. We're lost...

- Row 2 = $\text{NOT}(A) \text{ AND } B$
- Row 3 = $A \text{ AND } \text{NOT}(B)$

A	B	F = A XOR B	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

Project 2 Example: Xor

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the Boolean function synthesis strategy from the reading
 - Row 2 = NOT(A) AND B
 - Row 3 = A AND NOT(B)
 - $A \text{ XOR } B = \text{Row 2 OR Row 3}$
 $= (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND NOT}(B))$


A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Project 2 Example: Xor

- ❖ May be helpful to convert a Boolean expression to a circuit diagram
 
$$A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$$



Project 2 Example: Xor


- ❖ Step 3: Convert Boolean function to HDL syntax
 - $A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$
 - Assumes **Not**, **And**, and **Or** are already implemented
 - Note the use of intermediary wires: **nota**, **notb**, **x**, and **y**

```
CHIP Xor {  
  IN a, b;  
  OUT out;
```

PARTS:

```
Not (in=a, out=nota);  
Not (in=b, out=notb);  
And (a=a, b=notb, out=x);  
And (a=nota, b=b, out=y);  
Or (a=x, b=y, out=out);
```

```
}
```

 

Project 2 Demonstration



- ❖ Work through the tools you will use in Project 2
- ❖ Today's goal: Tinker with all the tools for Project 2
- ❖ Stretch goal: Implement the first gate in Project 2, **Not**
 - Interacting with the tools and implementing the gates will help you become familiar with the interface and address any confusion

Project 2 Group Work

- ❖ Group time to work on the first gate, **Not**, in Project 2

- ❖ Complete the following tasks in groups:
 1. Read the **Overview** section of the specification
 2. Estimate how much time you think it will take to finish Project 2
 3. Clone your GitLab repository (instructions in Project 1)
 4. Open the HardwareSimulator (see instructions in the **Tools** section of the specification)
 5. Dive into it! Implement and test the **Not** gate

Wrapping Up

- ❖ Exciting topics for Week 2!
 - Metacognitive Subject: Time Management 
 - Technical Subject: Boolean Arithmetic & ALU
- ❖ Project Reminders:
 - **Project 1 due tonight (Thursday, 3/31) at 11:59pm PDT**
 - Projects will generally be graded two days after the due date
 - Project 2 (Study Skills Inventory & Boolean Logic) released, due next Thursday (4/7) at 11:59pm PDT
- ❖ First Student-TA meetings starting this week! 
 - If you haven't yet, sign up for your first meeting in the [signup spreadsheet](#)
 - Your TA will be in contact with you about the first meeting