





CSE 390B, Spring 2022

Building Academic Success Through Bottom-Up Computing

Time Management & Boolean Arithmetic

Time Management, Binary and Boolean Arithmetic, Circuits for Adding Binary Numbers, Making Decisions in Hardware

Connect With Your CSE 390B Peers

- ❖ Download Discord from <https://discord.com/download>
- ❖ Log in or create an account
- ❖ Click on  icon in left-most column to create channel
 - Select “Create My Own”
 - Select “For me and my friends”
 - Give your server a name! (e.g., “CSE 390B 22sp”)
- ❖ Use the  button to invite peers
- ❖ Create some text and voice channels. Some ideas:
 - Text: #projects, #questions, #chill, #random
 - Voice:  Study Room,  Lounge
- ❖ Feel free to connect via Slack, Messenger, etc. too

Project 2 Check-in

- ❖ How has Project 2 been going?
- ❖ What questions do you have about Project 2?
 - HardwareSimulator or GitLab setup-related issues?
- ❖ You'll discuss with your TA about the Study Skills Inventory and revisit it at the end of the quarter
- ❖ Read Part II Tips for guidance on how to begin technical portion

Lecture Outline

❖ Time Management

- Weekly Time Commitments

❖ Binary and Boolean Arithmetic

- Addition Operator and Overflow

❖ Circuits For Adding Binary Numbers

- Half Adder, Full Adder

❖ Making Decisions in Hardware

- Multiplexer (Mux) Logical Gate

Time Management



**One of your most precious resources is
your time.**

WHAT TYPICALLY FILLS UP YOUR TIME DURING THE QUARTER?

**CLASS LECTURES &
QUIZ SECTIONS**

**FAMILY
COMMITMENTS**

COMMUTING

**ADMINISTRATIVE
WORK**

WORKING

OFFICE HOURS

HOME CHORES

**PHYSICAL / MENTAL
ACTIVITIES**

STUDYING

**EXTRACURRICULAR
INVOLVEMENT**

FRIENDS/PARTNERS

AND MORE!

Weekly Time Commitments

Weekly Time Commitments

Time	Sunday	Monday	Tuesday	Wednesday	Thursday	Friday	Saturday
7:30 AM							
8:00 AM							
8:30 AM							
9:00 AM							
9:30 AM							
10:00 AM							
10:30 AM							
11:00 AM							
11:30 AM							
12:00 PM							
12:30 PM							
1:00 PM							
1:30 PM							
2:00 PM							
2:30 PM							
3:00 PM							
3:30 PM							
4:00 PM							
4:30 PM							
5:00 PM							
5:30 PM							
6:00 PM							
6:30 PM							
7:00 PM							
7:30 PM							
8:00 PM							
8:30 PM							
9:00 PM							
9:30 PM							
10:00 PM							
10:30 PM							
11:00 PM							
11:30 PM							

Weekly Time Commitments

- ❖ Class meeting times and quiz sections
- ❖ Family, friends, community, extracurricular commitments
- ❖ Physical and Mental Activities
- ❖ Studying for each of your classes
 - The number of credits for a course reflects the number of hours the class meets
 - In general, courses require two hours of homework for every one hour of class
- ❖ What else is not reflected given your specific situation?

Time Management Group Discussion

- ❖ Now that you've filled out your weekly time commitments, discuss in groups of 3-4:
 - What is one thing that is most surprising to you?
 - What is one thing you might change?
 - How might you use this time commitments sheet in the future?

Lecture Outline

- ❖ Time Management
 - Weekly Time Commitments
- ❖ **Binary and Boolean Arithmetic**
 - **Addition Operator and Overflow**
- ❖ Circuits For Adding Binary Numbers
 - Half Adder, Full Adder
- ❖ Making Decisions in Hardware
 - Multiplexer (Mux) Logical Gate



Vote at <https://pollev.com/cse390b>

What is the binary representation of the decimal value of 29?

A. **0b011011**

B. 0b011101

C. **0b100011**

D. **0b100111**

E. **We're lost...**

What is Binary?

- ❖ A **base n** number system is a system of number representation with **n symbols**
- ❖ Decimal system is a **base 10** number system
 - Base 10 symbols: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9 (each called a **digit**)
 - Increase a number by moving to the next greatest symbol
 - Add another digit when we run out of symbols
- ❖ Binary is a **base 2** number system
 - Base 2 symbols: 0, 1 (each called a **bit**)
 - Often prefixed with 0b (e.g., 0b1101, 0b10)
 - **Least-significant bit (LSB)**: Lowest-order position of a binary value
 - **Most-significant bit (MSB)**: Highest-order position of a binary value

Representing Numbers in Base 2

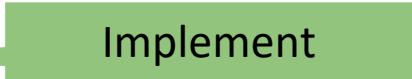

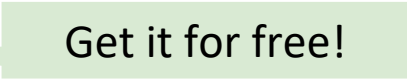
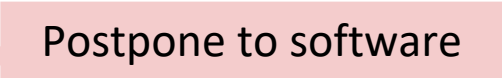
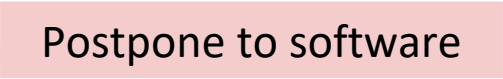
- ❖ Binary numbers are identical, except in base 2
 - Describe a value by specifying multiples of powers of 2
 - For example, a breakdown of 0b1101 in binary (13 in decimal)

Binary	Power of 2	Decimal	Power of 10
0b0001	1×2^0	1	1×10^0
0b0010	1×2^1	2	2×10^0
0b0100	1×2^2	4	4×10^0
0b1000	1×2^3	8	8×10^0

Representing Numbers in Binary

Binary	Decimal
0b000	0
0b001	1
0b010	2
0b011	3
0b100	4
0b101	5
0b110	6
0b111	7
...	...

Roadmap: Boolean Arithmetic

- ❖ Addition  Implement
- ❖ Subtraction  Get it for free!
- ❖ Comparison ($<$, $>$, $==$, $!=$)  Get it for free!
- ❖ Multiplication  Postpone to software
- ❖ Division  Postpone to software

Binary Addition

- ❖ How do we add two binary numbers?
 - As humans, we could convert to decimal and then back
- ❖ Example: $0b101 + 0b010$
 - First convert $0b101$ to decimal (result is 5)
 - Next convert $0b010$ to decimal (result is 2)
 - Add the decimal numbers and convert back to binary
 - $5 + 2 = 7$, which is $0b111$ in binary
- ❖ What's more useful is understanding the rules of binary addition so we can teach them to a computer

Case Study: Decimal Addition

- ❖ Consider how we perform decimal addition
 - Right to left (least significant place to most significant place)
 - When a result is more than one digit, carry the “overflow”

carry				
a	5	7	8	3
b	2	4	5	6
sum				

Binary Addition

- ❖ Binary addition is conceptually the same as decimal addition
 - Right to left (least significant place to most significant place)
 - When a result is more than one digit, carry the “overflow”

carry				
a	0	1	1	1
b	0	1	0	1
sum				

Binary Overflow

- ❖ What if there's a carry bit in the last column?

carry				
a	0	1	1	0
b	1	0	1	0
sum				

Binary Overflow

- ❖ What if there's a carry bit in the last column?
- ❖ We can't represent it in our fixed-width numbers
 - We are going to “drop” or ignore the extra carry bit

carry					
a		0	1	1	0
b		1	0	1	0
sum					

Five-minute Break!


- ❖ Feel free to stand up, stretch, use the restroom, drink some water, review your notes, or ask questions
- ❖ We'll be back at:
- ❖ Any song recommendations? Respond on Poll Everywhere at <https://pollev.com/cse390b>
- ❖ Research shows mid-lecture breaks reduce the decline of attention (Olmsted, 1999)

Lecture Outline

- ❖ Time Management
 - Weekly Time Commitments
- ❖ Binary and Boolean Arithmetic
 - Addition Operator and Overflow
- ❖ **Circuits For Adding Binary Numbers**
 - **Half Adder, Full Adder**
- ❖ Making Decisions in Hardware
 - Multiplexer (Mux) Logical Gate

Half Adder

 - ❖ Circuit for adding two bits together
- ❖ Takes in two inputs: `a`, `b`
 - `a` is the first bit being added
 - `b` is the corresponding bit to be added
- ❖ Produces two outputs: `sum`, `carry`
 - `sum` is the value to be put for this column in the result
 - `carry` is the value to be carried over to the next column



carry				
a	0	1	1	0
b	1	0	1	0
sum				

```
/**  
 * Computes the sum of 2 bits  
 */  
  
CHIP HalfAdder {  
    IN a, b;  
    OUT sum, carry;  
  
    PARTS:  
    // Put your code here:  
  
}
```

Half Adder Example

❖ Example: $0b0111 + 0b0101$

❖ For the right-most (least significant) column:

- $a = 1$
- $b = 1$
- $\text{sum} =$
- $\text{carry} =$

carry				
<hr/>				
a	0	1	1	1
b	0	1	0	1
sum				

Half Adder Example

❖ Boolean expressions:

- $\text{sum} =$
- $\text{carry} =$

a	b	sum	carry
0	0		
0	1		
1	0		
1	1		


Half Adder Example

❖ Boolean expressions:

- $\text{sum} = a \text{ XOR } b$
- $\text{carry} = a \text{ AND } b$

a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full Adder

 

- ❖ Circuit for adding three bits together (two bits *and* carry bit together from previous column)

- `a` is the first bit being added
- `b` is the corresponding bit to be added
- `c` is the carry bit from the right column

carry				
a	0	1	1	0
b	1	0	1	0
sum				

- ❖ Produces two outputs: `sum`, `carry`

- `sum` is the value to be put for this column in the result
- `carry` is the value to be carried over to the next column

```
/**
 * Computes the sum of 3 bits
 */

CHIP FullAdder {
    IN a, b, c;
    OUT sum, carry;

    PARTS:
        // Put your code here:

}
```

Full Adder

❖ Example: $0b0111 + 0b0101$

❖ For the second (second least significant) column:

- $a = 1$
- $b = 0$
- $c = 1$

▪ $\text{sum} =$

▪ $\text{carry} =$

carry			1	
<hr style="border-top: 1px dashed black;"/>				
a	0	1	1	1
b	0	1	0	1
sum				0

Full Adder Truth Table

a	b	c	sum	carry
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



Vote at <https://pollev.com/cse390b>

What are the sum and carry bits when $a=0$, $b=1$, and $c=1$?

- A. sum = 0, carry = 0
- B. sum = 0, carry = 1
- C. sum = 1, carry = 0
- D. sum = 1, carry = 1
- E. We're lost...

a	b	c	sum	carry
0	0	0		
0	0	1		
0	1	0		
0	1	1	?	?
1	0	0		
1	0	1		
1	1	0		
1	1	1		



Vote at <https://pollev.com/cse390b>

What are the sum and carry bits when $a=0$, $b=1$, and $c=1$?

A. sum = 0, carry = 0

B. sum = 0, carry = 1

C. sum = 1, carry = 0

D. sum = 1, carry = 1

E. We're lost...


a	b	c	sum	carry
0	0	0		
0	0	1		
0	1	0		
0	1	1	0	1
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Full Adder Truth Table

a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Multi-Bit Adder

 - ❖ Adds two 16-bit numbers
- ❖ Connects the full adders for each column together (wires the out carry from one column to the in carry of the next)



```
/**
 * Adds two 16-bit Two's Complement
 * values. Overflow is ignored.
 */
```

```
CHIP Add16 {
  IN a[16], b[16];
  OUT sum[16];
```

PARTS:

```
// Put your code here:
```

```
}
```

...	0	0	1	1	1	0	
...	0	0	1	0	1	0	1
+	...	1	0	1	1	0	0
...	1	1	1	0	0	0	1

Lecture Outline

- ❖ Time Management
 - Weekly Time Commitments
- ❖ Binary and Boolean Arithmetic
 - Addition Operator and Overflow
- ❖ Circuits For Adding Binary Numbers
 - Half Adder, Full Adder
- ❖ **Making Decisions in Hardware**
 - **Multiplexer (Mux) Logical Gate**

Making Decisions in Hardware

- ❖ We write if / else statements in Java with the understanding that *only one* of the branches will run
 - For example, in the following code, we expect to compute one of $a \ \& \ b$ or $a \ | \ b$ (not both)


```
if (c == 0) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

- ❖ In hardware, all circuits are always executing
 - We can't "turn off" a circuit based on a condition
 - Instead, we create circuits for different conditions and choose which output based on a condition instead

Making Decisions in Hardware


❖ We can use a **Multiplexer (Mux)** gate to choose which singular input to output

 - Takes three inputs: a , b , and sel
- If $sel == 0$, then $out = a$
- Otherwise, $out = b$



❖ A **Demultiplexer (DMux)** gate passes one input to one of several outputs and 0 to the rest of the outputs

 - Takes two inputs: in and sel
- If $sel == 0$, then $a = in$ and $b = 0$
- Otherwise, $a = 0$ and $b = in$



Mux Gate Implementation Example


- ❖ Example of converting pseudocode into a hardware circuit diagram:

```
if (c == 0) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

Mux Gate Implementation Example

- ❖ Example of converting pseudocode into a hardware circuit diagram:

```
if (c == 0) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

 

Mux Gate Practice Problem 1


- ❖ Draw out the hardware circuit diagram that corresponds to the following pseudocode:

```
if (c == 0) {  
    out = ~a | ~b;  
} else {  
    out = a | b;  
}
```

Mux Gate Practice Problem 1

- ❖ Draw out the hardware circuit diagram that corresponds to the following pseudocode:

```
if (c == 0) {  
    out = ~a | ~b;  
} else {  
    out = a | b;  
}
```

 

Mux Gate Practice Problem 2


- ❖ Draw out the hardware circuit diagram that corresponds to the following pseudocode:

```
if (a == b) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

Mux Gate Practice Problem 2

- ❖ Draw out the hardware circuit diagram that corresponds to the following pseudocode:

```
if (a == b) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

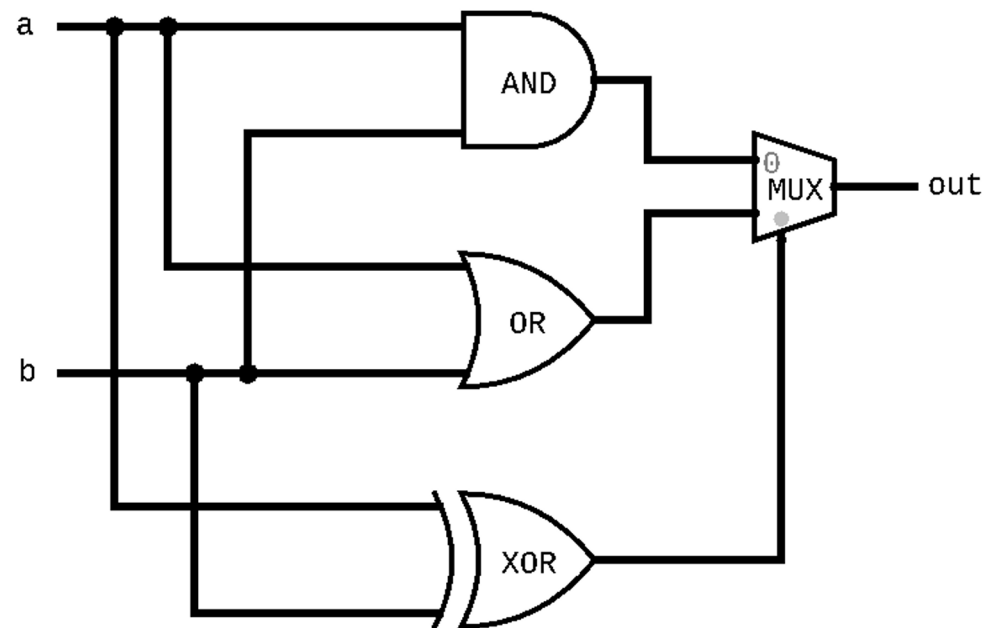

Lecture 3 Wrap-up

❖ Project Reminders

- Project 1 feedback released on Gradescope
- **Project 2 due this Thursday (4/7) at 11:59pm PDT**

❖ Lecture 4 Reading: [Negative Numbers in Binary](#)

❖ Course Staff Support

- Eric has office hours in CSE2 153 today after lecture until 5pm
- You can also post your questions on the Ed discussion board