

CSE 390B, Spring 2022

Building Academic Success Through Bottom-Up Computing

Growth Mindset & Arithmetic Logic Unit

Growth vs. Fixed Mindset, Negative Numbers in Binary,
Arithmetic Logic Unit (ALU), Project 3 Overview

Project 2 Check-in

- ❖ How has Project 2 been going?
 - 👍 If you're feeling **great** about completing Project 2 by tonight
 - 👎 If you're feeling **decent** about where you are right now
 - 🙄 If you're feeling **behind** or unlikely to submit on time
- ❖ A few common questions about Project 2:
 - Can't see message at bottom of Hardware Simulator? Try reducing window size (Settings → Displays → Change size to < 150%)
 - Can't use typical Boolean Function Synthesis on **Or.hdl**
 - **DMux.hdl**: Follow same implementation strategy as other gates
- ❖ **Double-check** your submission on GitLab
 - Navigate to GitLab, open tags, and verify that the associated commit includes your expected changes

Lecture Outline

- ❖ **Growth vs. Fixed Mindset**
 - **Setting SMART Goals**
- ❖ **Negative Numbers in Binary**
 - **Unsigned, Signed, and Two's Complement Representations**
- ❖ **Arithmetic Logic Unit (ALU)**
 - **Overview and Examples of ALU Functions**
- ❖ **Project 3 Overview**
 - **ALU Implementation Strategy**
 - **HDL Tips and Tricks**

Growth vs. Fixed Mindset



FIXED



GROWTH

MINDSETS

Setting SMART Goals

- ❖ **S** – Be specific, simple and significant.
- ❖ **M** – Make sure your goals are measurable. How many times within a week, month, the quarter do you want to do x goal?
- ❖ **A** – Make sure your goals are achievable. Is your goal within your scope of control?
- ❖ **R** – Be realistic and reasonable.
- ❖ **T** – Be time-bound. When will you accomplish your goal?

SMART Goals Group Discussion

SPRING QUARTER
GOALS

What are skills, practices
or habits that are not
strengths YET?

SPHERE OF CONTROL

Getting a 4.0 in a course

VS.

Attending course
office hours

SMART GOAL
FRAMEWORK

S — Specific

M — Measurable

A — Achievable

R — Realistic

T — Timebound

Attending CSE 390B
office hours at least
5x this quarter
(or once every other week)

Lecture Outline

- ❖ Growth vs. Fixed Mindset
 - Setting SMART Goals
- ❖ **Negative Numbers in Binary**
 - **Unsigned, Signed, and Two's Complement Representations**
- ❖ Arithmetic Logic Unit (ALU)
 - Overview and Examples of ALU Functions
- ❖ Project 3 Overview
 - ALU Implementation Strategy
 - HDL Tips and Tricks



Vote at <https://pollev.com/cse390b>

What are the Sign and Magnitude (signed) and Two's Complement binary representations of the number -7?

- A. Signed: 0b1001, Two's Complement: 0b1111**
- B. Signed: 0b0111, Two's Complement: 0b1001**
- C. Signed: 0b1111, Two's Complement: 0b0111**
- D. Signed: 0b1111, Two's Complement: 0b1001**
- E. We're lost...**

Two's Complement

- ❖ One binary interpretation to represent negative values
- ❖ Most significant bit (MSB) has a negative weight
 - Add the remaining bits as usual (with positive weights)
- ❖ Example: 0b1101 in Two's Complement
 - $-(1 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) = -8 + 4 + 0 + 1$
 $= -3$
- ❖ Negation procedure: Take bitwise complement and add one
 - $-x = \sim x + 1$
 - Example: Negate $x = 4$

Two's Complement

- ❖ One binary interpretation to represent negative values
- ❖ Most significant bit (MSB) has a negative weight
 - Add the remaining bits as usual (with positive weights)
- ❖ Example: 0b1101 in Two's Complement
 - $-(1 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) = -8 + 4 + 0 + 1$
 $= -3$
- ❖ Negation procedure: Take bitwise complement and add one
 - $-x = \sim x + 1$
 - Example: Negate $x = 4$
 - $-4 = \sim 0b0100 + 1 = 0b1011 + 0b1 = 0b1100 = -8 + 4 = -4$

Four-bit Values in Various Representations

Binary Value	Unsigned Binary	Signed Binary	Two's Complement
0b0000	0	0	0
0b0001	1	1	1
0b0010	2	2	2
0b0011	3	3	3
0b0100	4	4	4
0b0101	5	5	5
0b0110	6	6	6
0b0111	7	7	7
0b1000	8	-0	-8
0b1001	9	-1	-7
0b1010	10	-2	-6
0b1011	11	-3	-5
0b1100	12	-4	-4
0b1101	13	-5	-3
0b1110	14	-6	-2
0b1111	15	-7	-1

Two's Complement Addition

❖ The process for adding binary in Two's Complement is the same as that of unsigned binary

❖ Hardware performs the exact same calculations

- It doesn't need to know the sign of the values, it performs the same calculation
- The only difference is representation of sum

❖ Example: $0b1001 + 0b0010$

- Unsigned interpretation:
- Signed interpretation:
- Two's Complement interpretation:

carry				
a	1	0	0	1
b	0	0	1	0
sum				

Two's Complement Addition

❖ The process for adding binary in Two's Complement is the same as that of unsigned binary

❖ Hardware performs the exact same calculations

- It doesn't need to know the sign of the values, it performs the same calculation
- The only difference is representation of sum

❖ Example: $0b1001 + 0b0010 = 0b1011$


- Unsigned interpretation: $9 + 2 = 11$
- Signed interpretation: $-1 + 2 = -3$ (?)
- Two's Complement interpretation: $-7 + 2 = -5$

carry				
a	1	0	0	1
b	0	0	1	0
sum	1	0	1	1

Lecture Outline

- ❖ Growth vs. Fixed Mindset
 - Setting SMART Goals
- ❖ Negative Numbers in Binary
 - Unsigned, Signed, and Two's Complement Representations
- ❖ **Arithmetic Logic Unit (ALU)**
 - **Overview and Examples of ALU Functions**
- ❖ Project 3 Overview
 - ALU Implementation Strategy
 - HDL Tips and Tricks


The Von Neumann Architecture

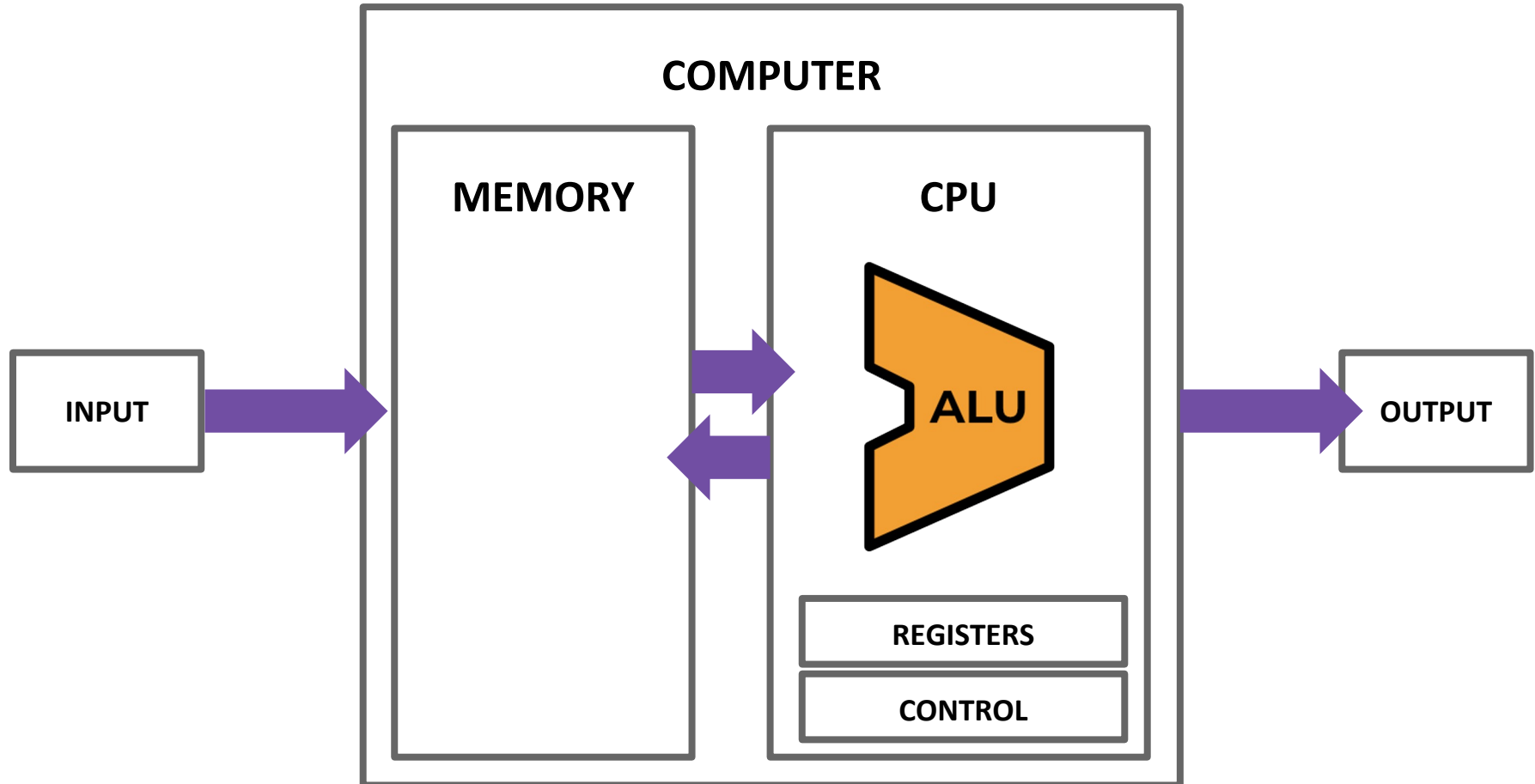

(This picture will get more detailed as we go!)

The Arithmetic Logic Unit

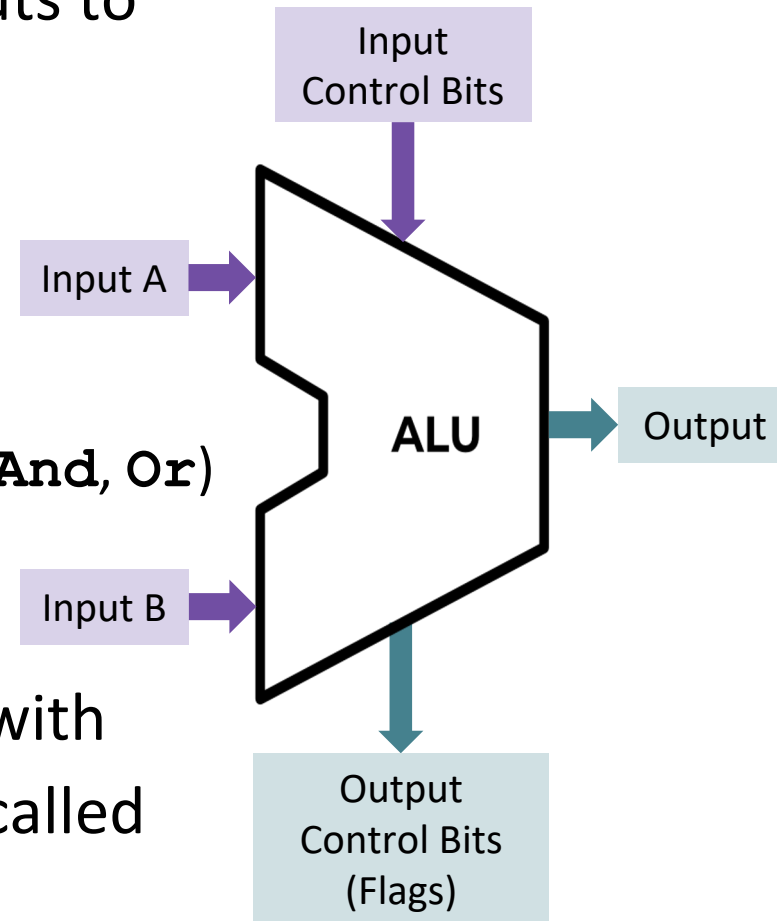- ❖ Computes a function on two inputs to produce an output
- ❖ Input Control Bits specific which function should be computed
 - Supports a combination of logical (**And, Or**) and arithmetic operations (+, -)
- ❖ Indicate properties of the result with **Output Control Bits** (commonly called **Flags**)



Our ALU Implementation

❖ Inputs & Outputs


- 16-bit inputs **x** and **y** and output **out**
- Interpret in Two's Complement

❖ Input Control Bits

- Six control bits (**zx**, **nx**, **zy**, **ny**, **f**, **no**) specify which function to compute
- $2^6 = 64$ different possible functions to choose from (only 18 of interest)

❖ Output Control Bits (Flags)

 - 2 bits (**zr** and **ng**) describing the properties of the output



ALU Functions: Client's View

- ❖ We support 18 different functions of interest
 - 3 that simply give constant values (ignoring operands)
 - 10 that change a single input, possibly with a constant
 - 5 that perform an operation using both inputs

out
0
1
-1
x
y
!x
!y
-x
-y
x+1
y+1
x-1
y-1
x+y
x-y
y-x
x&y
x y

ALU Functions: Client's View


- ❖ We support 18 different functions of interest
 - 3 that simply give constant values (ignoring operands)
 - 10 that change a single input, possibly with a constant
 - 5 that perform an operation using both inputs

- ❖ To select a function, set the control bits to the corresponding combination

zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

ALU Functions: Implementer's View

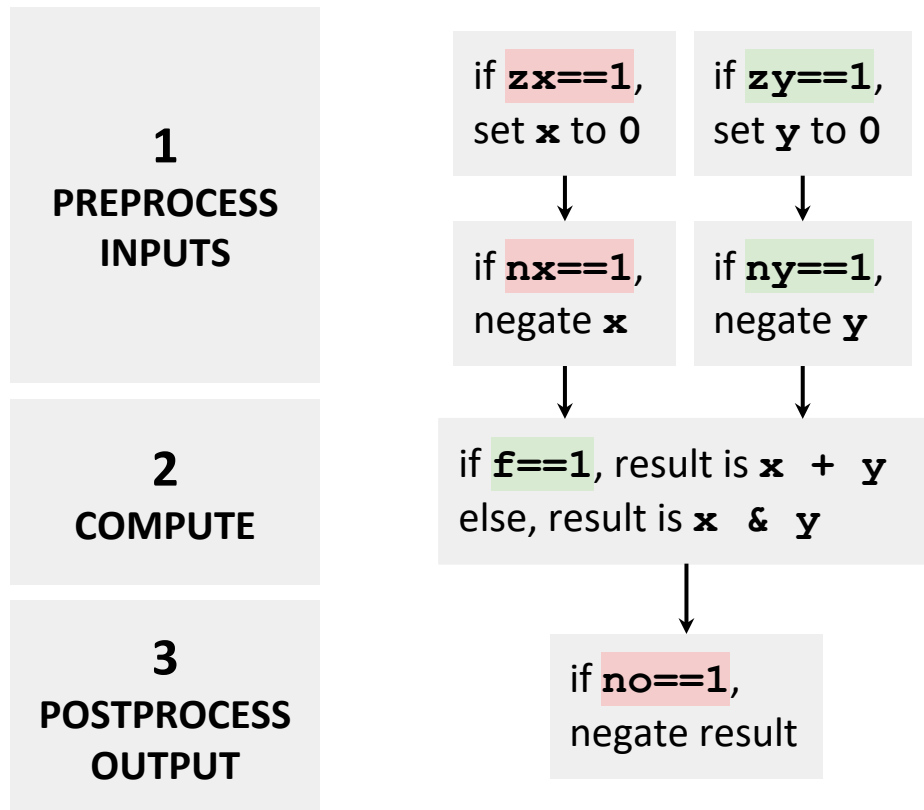- ❖ These 18 functions are really a clever combination of 6 core operations:



zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

ALU Functions: Implementer's View

- ❖ Example: Compute $x - 1$
 - Given inputs $x=0b0101$ (5), $y=0b0010$ (2)


zx	nx	zy	ny	f	no	out
...						...
0	0	1	1	1	0	$x-1$
...						...

ALU Functions: Implementer's View

- ❖ Example: Compute $x - 1$
 - Given inputs $x=0b0101$ (5), $y=0b0010$ (2)

zx	nx	zy	ny	f	no	out
...						...
0	0	1	1	1	0	x-1
...						...

1
PREPROCESS
INPUTS

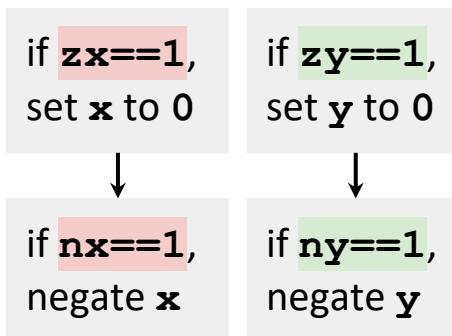

x=0b0101 (5) <i>Unchanged</i>	y=0b0000 (0) <i>Zeroed</i>
x=0b0101 (5) <i>Unchanged</i>	y=0b1111 (-1) <i>Negated</i>

ALU Functions: Implementer's View

- ❖ Example: Compute $x - 1$
 - Given inputs $x=0b0101$ (5), $y=0b0010$ (2)

zx	nx	zy	ny	f	no	out
...						...
0	0	1	1	1	0	x-1
...						...

1
PREPROCESS
INPUTS

2
COMPUTE

if **zx==1**,
set **x** to 0

if **zy==1**,
set **y** to 0

x=0b0101 (5) **y=0b0000** (0)
Unchanged *Zeroed*

if **nx==1**,
negate **x**

if **ny==1**,
negate **y**

x=0b0101 (5) **y=0b1111** (-1)
Unchanged *Negated*

if **f==1**, result is **x + y**
else, result is **x & y**

out=0b0100 (4)
 $x(5) + y(-1)$

ALU Functions: Implementer's View

- ❖ Example: Compute $x - 1$
 - Given inputs $x=0b0101$ (5), $y=0b0010$ (2)

zx	nx	zy	ny	f	no	out
...						...
0	0	1	1	1	0	x-1
...						...

1
PREPROCESS
INPUTS

2
COMPUTE

3
POSTPROCESS
OUTPUT

if **zx**==1,
set **x** to 0

if **zy**==1,
set **y** to 0

x=0b0101 (5) **y**=0b0000 (0)
Unchanged *Zeroed*

if **nx**==1,
negate **x**

if **ny**==1,
negate **y**

x=0b0101 (5) **y**=0b1111 (-1)
Unchanged *Negated*

if **f**==1, result is **x** + **y**
else, result is **x** & **y**

out=0b0100 (4)
x (5) + y (-1)

if **no**==1,
negate result


out=0b0100 (4)
Unchanged

ALU Output Control Bits

- ❖ **zr** is 1 if $\text{out} == 0$
- ❖ **ng** is 1 if $\text{out} < 0$

- ❖ We'll use these in a later project
 - The basis of **comparison**
 - Example: To evaluate if $\mathbf{x} == 4$, compute $\mathbf{x} - 4$ and check **zr** flag

 - ❖ These can be deceptively difficult to implement
 - Start early on Project 3



Five-minute Break!

- ❖ Feel free to stand up, stretch, use the restroom, drink some water, review your notes, or ask questions
- ❖ We'll be back at:
- ❖ Any song recommendations? Respond on Poll Everywhere at <https://pollev.com/cse390b>
- ❖ Research shows mid-lecture breaks reduce the decline of attention in the middle of lecture (Olmsted, 1999)



Vote at <https://pollev.com/cse390b>

Given inputs $x=0b1010$ and $y=0b0110$ and the following input control bits, what is the resulting output and output control bits?

- A. **out=0b1110, zr=0, ng=0**
- B. **out=0b1011, zr=0, ng=1**
- C. **out=0b1101, zr=1, ng=0**
- D. **out=0b1001, zr=1, ng=1**
- E. **We're lost...**

zx	nx	zy	ny	f	no	out
...						...
0	1	1	1	1	1	x+1
...						...

IN

```
x[16], y[16], // 16-bit inputs
zx, // zero the x input?
nx, // negate the x input?
zy, // zero the y input?
ny, // negate the y input?
f, // compute out = x + y
    if 1 or x & y (if 0)
no; // negate the out output?
```

OUT

```
out[16], // 16-bit output
zr, // 1 if (out == 0),
    0 otherwise
ng; // 1 if (out < 0),
    0 otherwise
```

Lecture Outline

- ❖ Growth vs. Fixed Mindset
 - Setting SMART goals
- ❖ Negative Numbers in Binary
 - Unsigned, Signed, and Two's Complement Representations
- ❖ Arithmetic Logic Unit (ALU)
 - Overview and Examples of ALU Functions
- ❖ **Project 3 Overview**
 - **ALU Implementation Strategy**
 - **HDL Tips and Tricks**

Project 3 Overview

- ❖ Part I: 24-Hour Time Audit

- ❖ Part II: Boolean Arithmetic
 - Goal: Implement the ALU, which performs the core computations we need (+ and &)
 - First, implement `HalfAdder.hdl`, `FullAdder.hdl`, and `Add16.hdl`
 - Then, implement the ALU in the order suggested by the specification
 - Chapter 2 of the textbook has more details on the adders and ALU


- ❖ Part III: Project 3 Reflection

ALU Implementation Strategy

- ❖ First, handle zeroing out and negating inputs **x** and **y** and negating the output
 - Ignore the **f** bit (only compute **And**) and ignore flag outputs
 - Test your implementation using `ALU-nostat-noadd.tst`
- ❖ Next, implement the **And** and **Add** operations using **f**
 - How do we make decisions in hardware?
 - Test your implementation using `ALU-nostat.tst`
- ❖ Lastly, implement the logic for the status flags (**zr** and **ng**)
 - Test your full ALU using `ALU.tst`

HDL Tips: Slicing

 - ❖ Sometimes want to connect only part of a multi-bit bus
- ❖ HDL lets us with **slicing notation**
- ❖ Example: **ChipA** has eight output pins, and we want to connect the first four to **ChipB**'s four inputs:




```
ChipA (out[0..3]=w1);  
ChipB (in=w1);
```

- ❖ Note: We can only slice chip connections, not internal wires (e.g., `w1[0..3]` is not allowed)
 - If we need to use half an 8-bit wire, make two 4-bit wires and slice the output they're connected to

HDL Tips: Connections

 
- ❖ Can connect a chip output multiple times, or not at all!
 - Hint: In `Add16.hdl`, do we need to use the last carry bit?



```
ChipA (out[0..3]=w1,  
      out[2..5]=w2,  
      out[5]=w3);  
ChipB (in=w1);  
ChipB (in=w2);  
ChipC (in=w3);
```

HDL Tips: Constants


- ❖ A bus of **true** or **false** contain all 1s or all 0s, respectively, and implicitly act as whatever width is needed
- ❖ Example: **ChipB** has four inputs and **ChipC** has one input
 - **ChipB** (**in=true**) assigns four input bits a value of 1 (**true**)
 - **ChipC** (**in=true**) assigns one input bit a value of 1 (**true**)
 - **ChipC** (**in=false**) assigns one input bit a value of 0 (**false**)

 

```
ChipB (in=true);  
ChipC (in=true);  
ChipC (in=false);
```

Lecture 4 Wrap-up

❖ Exciting topics for Week 3!

- Metacognitive Subject: Note-taking Practices 
- Technical Subject: Sequential Logic & Building Memory

❖ Project Reminders

- **Project 2 due tonight (Thursday, 4/7) at 11:59pm PDT**
- Project 3 (24-Hour Time Audit & Boolean Arithmetic) released, due next Thursday (4/14) at 11:59pm PDT

❖ Join the students-only CSE 390B Discord channel!

- <https://discord.gg/Q6KBuBj8>

