

CSE 390B, Spring 2022

Building Academic Success Through Bottom-Up Computing


# Bloom's Taxonomy & Sequential Logic

Bloom's Taxonomy, Cornell Note Taking Method,  
Representing Time in Hardware, Sequential Logic


# Lecture Outline

- ❖ **Bloom's Taxonomy**
  - **Applying Higher Levels of Cognition to Learning**
- ❖ **Cornell Note Taking Method**
  - System for Taking, Organizing, and Reviewing Notes
- ❖ **Representing Time in Hardware**
  - Sequential Logic vs. Combinational Logic
  - Adding a Clock
- ❖ **Sequential Logic**
  - Data Flip-Flop (DFF) Implementation and Examples

# Bloom's Taxonomy

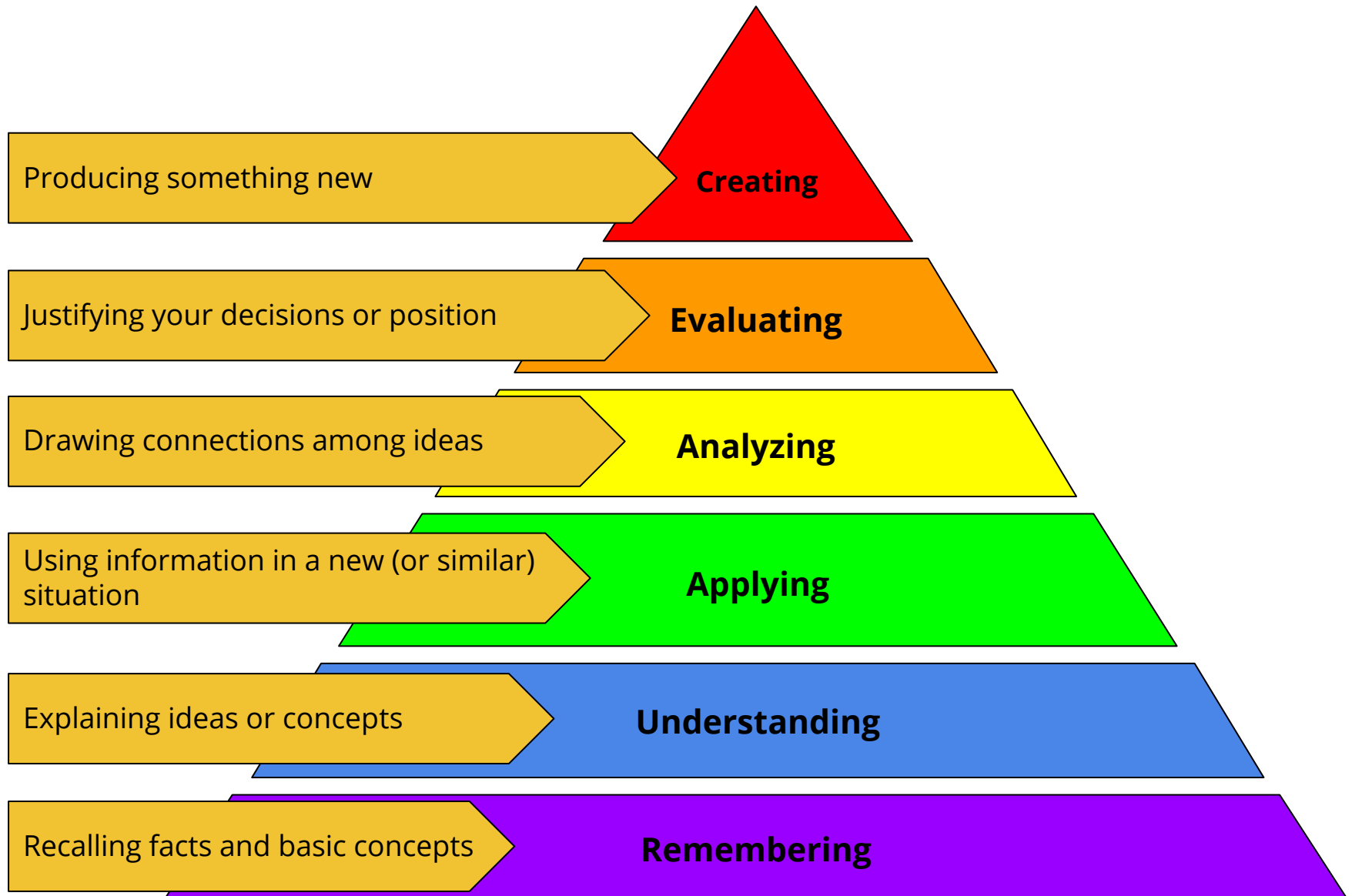

# Bloom's Taxonomy in Action

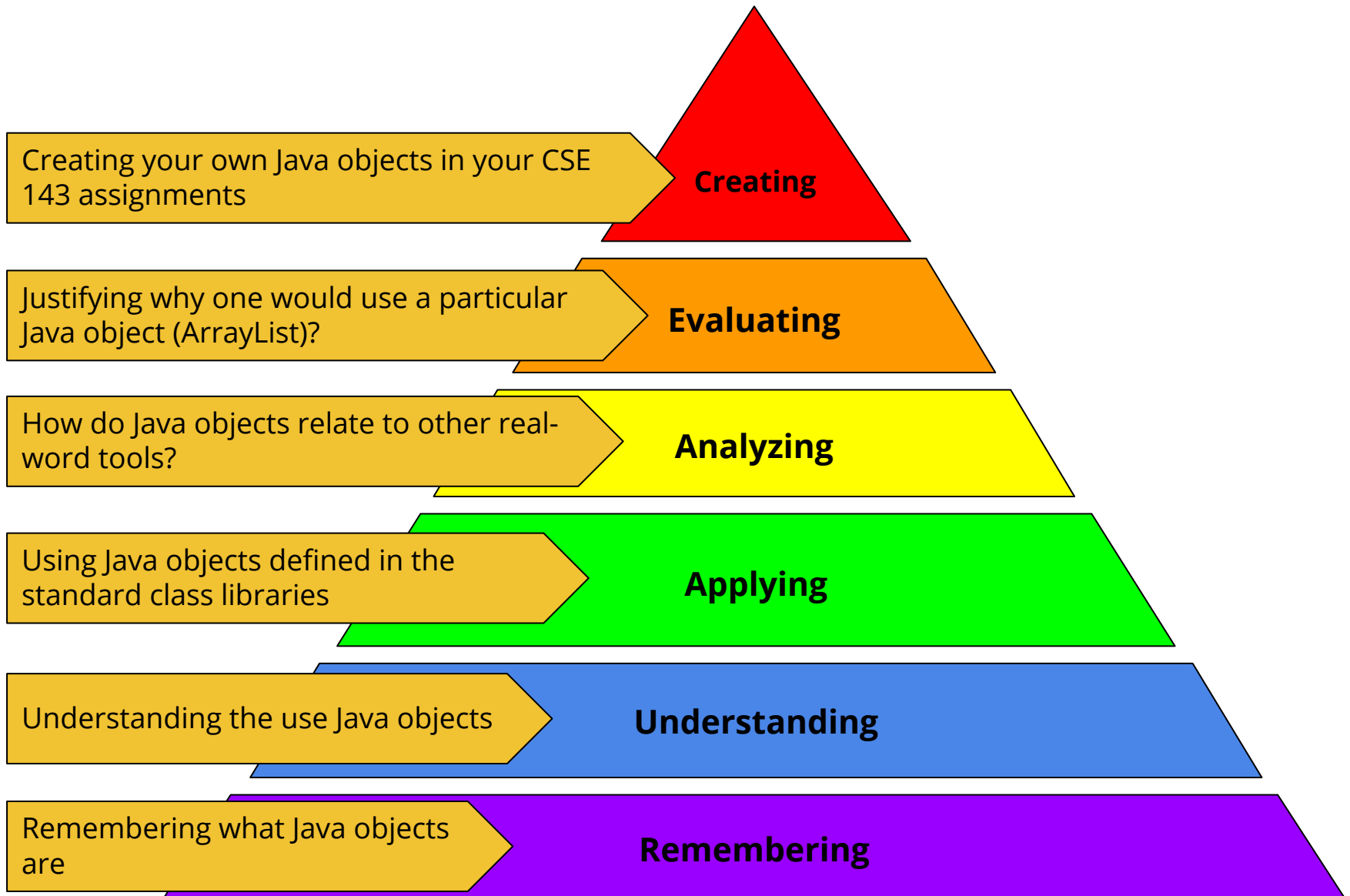

# Lecture Outline

- ❖ Bloom's Taxonomy
  - Applying Higher Levels of Cognition to Learning
- ❖ **Cornell Note Taking Method**
  - **System for Taking, Organizing, and Reviewing Notes**
- ❖ Representing Time in Hardware
  - Sequential Logic vs. Combinational Logic
  - Adding a Clock
- ❖ Sequential Logic
  - Data Flip-Flop (DFF) Implementation and Examples

# Applying the Cornell Note-Taking Method

- ❖ You are going to try it... TODAY!
- ❖ Thursday you will come & contrast Cornell notes with your classmates
- ❖ You are also going to try it with one of your other classes as part of Project 4 (more on Thursday)

# Lecture Outline

- ❖ Bloom's Taxonomy
  - Applying Higher Levels of Cognition to Learning
- ❖ Cornell Note Taking Method
  - System for Taking, Organizing, and Reviewing Notes
- ❖ **Representing Time in Hardware**
  - **Sequential Logic vs. Combinational Logic**
  - **Adding a Clock**
- ❖ Sequential Logic
  - Data Flip-Flop (DFF) Implementation and Examples



Vote at <https://pollev.com/cse390b>

**Which of the following statements about sequential logic is FALSE?**


- A. We represent time with a clock signal that alternates between high and low signals**
- B. The DFF allows us to reuse outputs as inputs in a circuit**
- C. The outputs for a DFF at time  $t=2$  is determined by the inputs at time  $t=3$**
- D. Sequential logic is important because it addresses slight delays caused in circuit gates**
- E. We're lost...**

# Combinational vs. Sequential Logic

- ❖ So far, we have ignored “time” in our circuits
- ❖ Our chips use **combinational logic**
  - When given inputs, the chip computes its output instantaneously
  - The output is a function of the current inputs, with no memory of previous events
- ❖ Today, we'll start exploring what happens when we consider time, ultimately building to **sequential logic**

 
# Why Consider Time Now?

- ❖ Needed for our **abstraction**
  - We need to talk about hardware maintaining state for memory
  - We need vocabulary to talk about time
  
- ❖ Needed for our **implementation**
  - Physical implementations of chips cannot be instantaneous
  - We need to account for physical delays in signal propagation



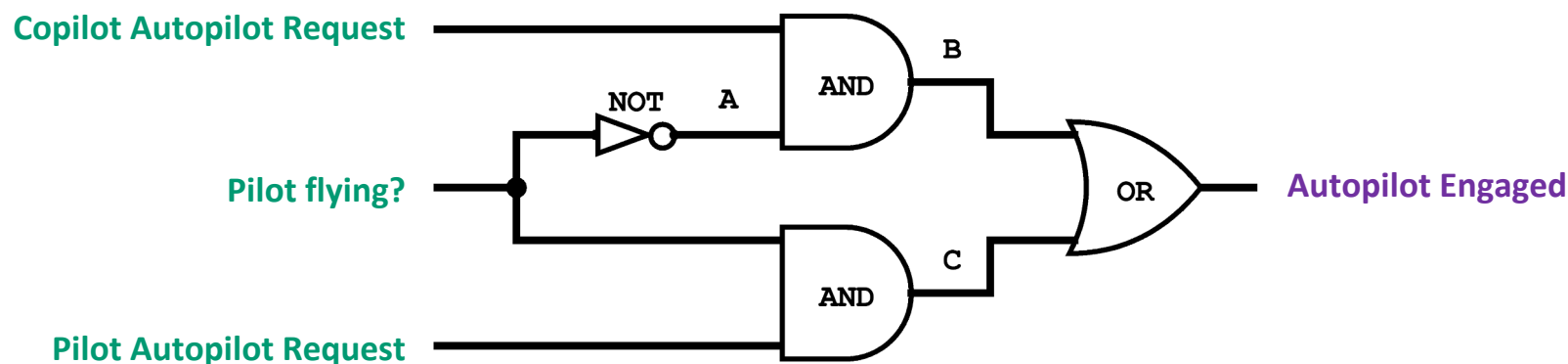
# Autopilot Control Circuit Example

- ❖ Consider this autopilot control circuit:
  - Either the pilot or copilot is flying at any time
  - The pilot and copilot can separately request autopilot
  - Only the person flying can request autopilot




 
# Autopilot Control Circuit Example

- ❖ Consider this autopilot control circuit:
  - Either the pilot or copilot is flying at any time
  - The pilot and copilot can separately request autopilot
  - Only the person flying can request autopilot





- ❖ Let's assume every logic gate takes  $1\text{ms}$  to compute
  - For example, if an input changes at  $t=4\text{ms}$ , the gate will only output the new result at  $t=5\text{ms}$



# Autopilot Control Circuit Example

 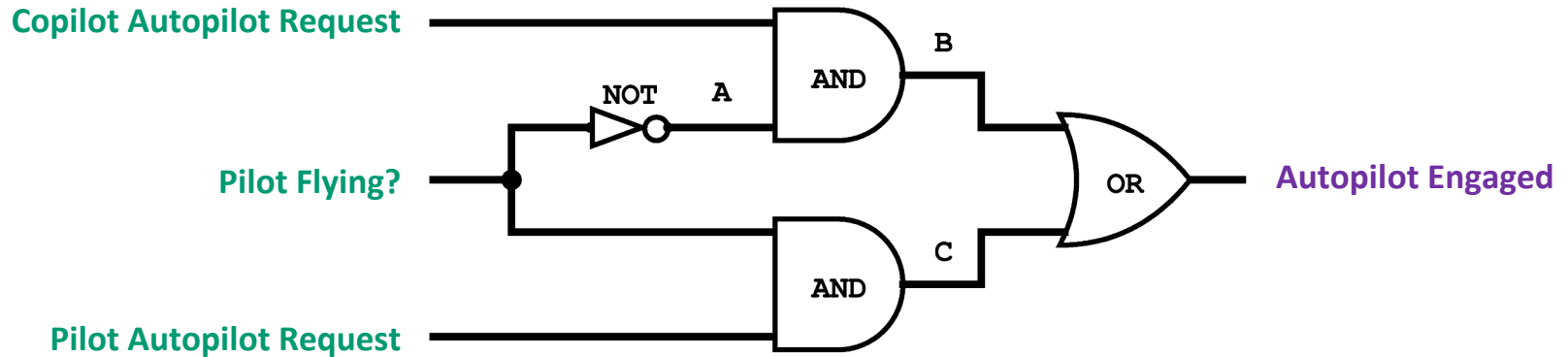



# Autopilot Control Circuit Example

  



# Autopilot Control Circuit Example

 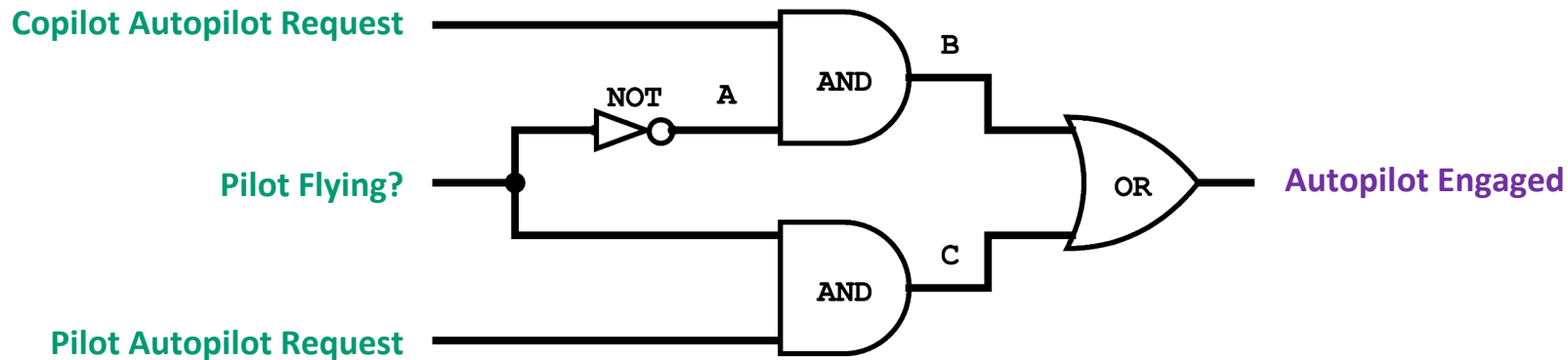

# Autopilot Control Circuit Example

 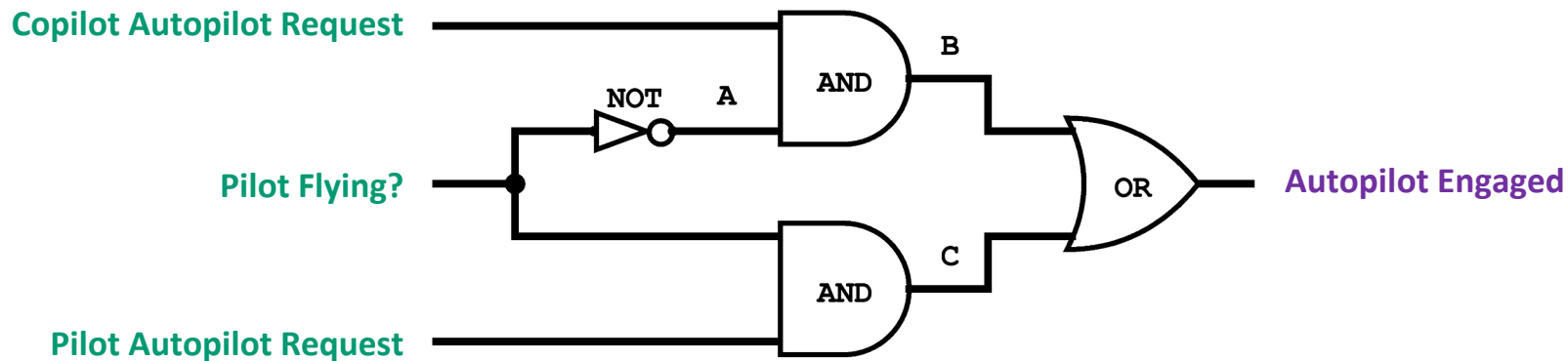



# Autopilot Control Circuit Example

  



Vote at <https://pollev.com/cse390b>

 
 
Describe the behavior of the Autopilot Engaged (AE) output between 1ms to 6ms.







Vote at <https://pollev.com/cse390b>

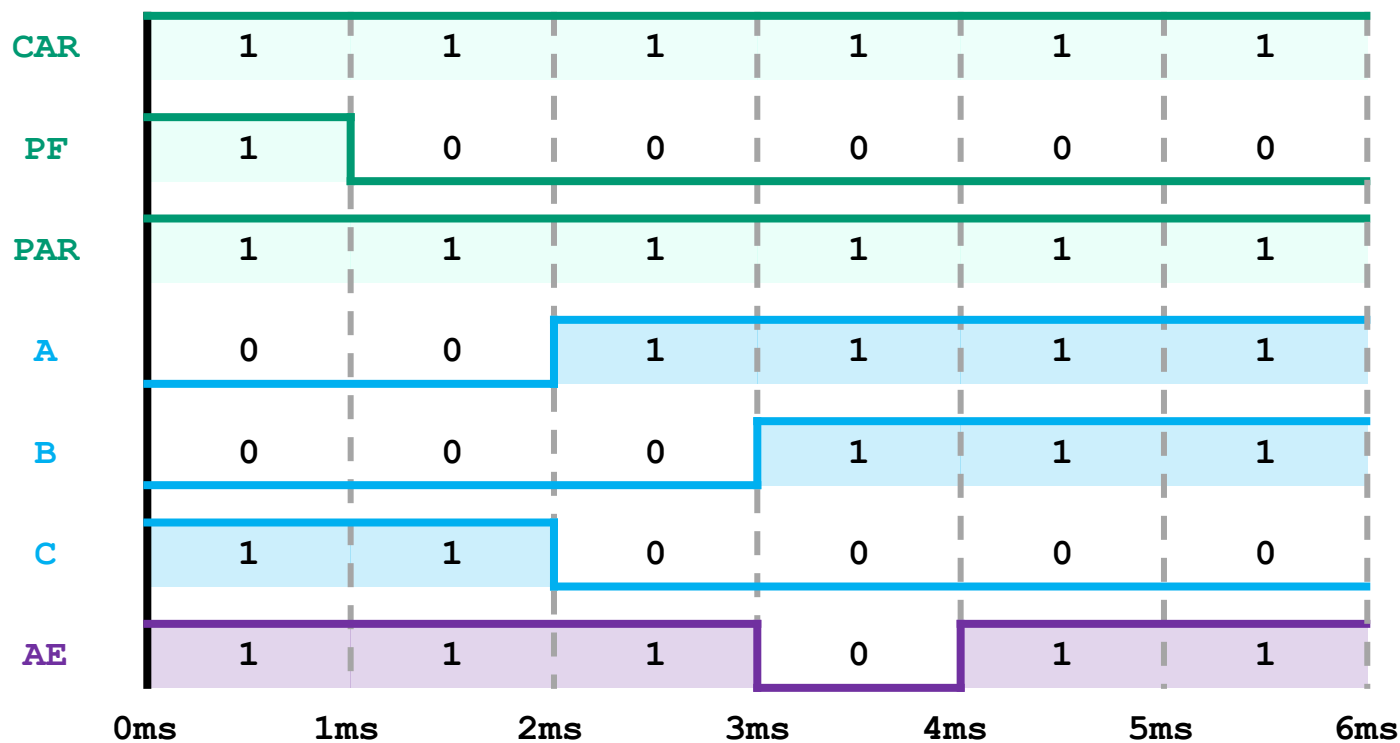 Describe the behavior of the Autopilot Engaged (AE) output between 1ms to 6ms.



# Autopilot Control Circuit Example

 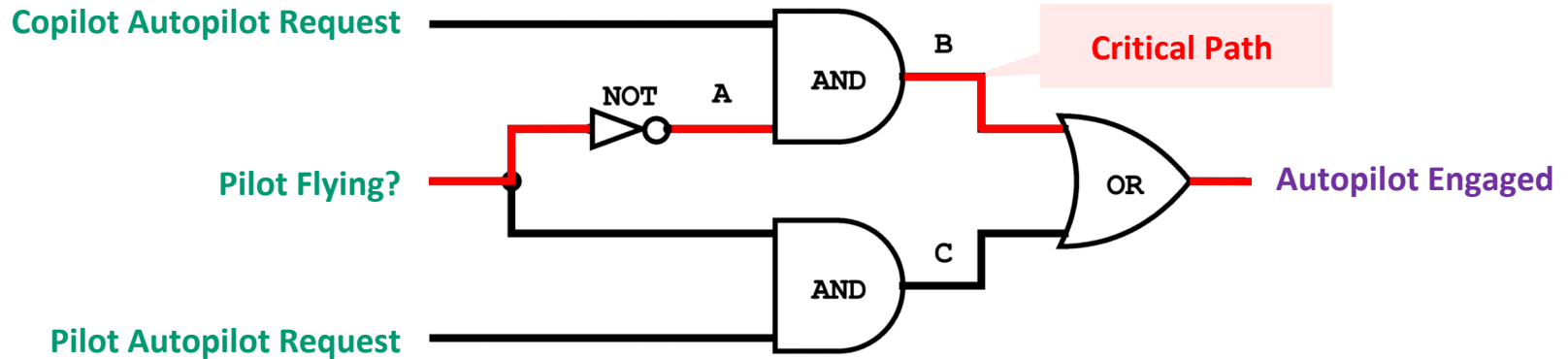

# Physical Timekeeping

- ❖ Hardware keeps track of time using an alternating signal
  - Creates the idea of **discrete time**: state changes only occur in discrete intervals, right when signal alternates

Physical  
Time




Clock  
Signal

1  
0



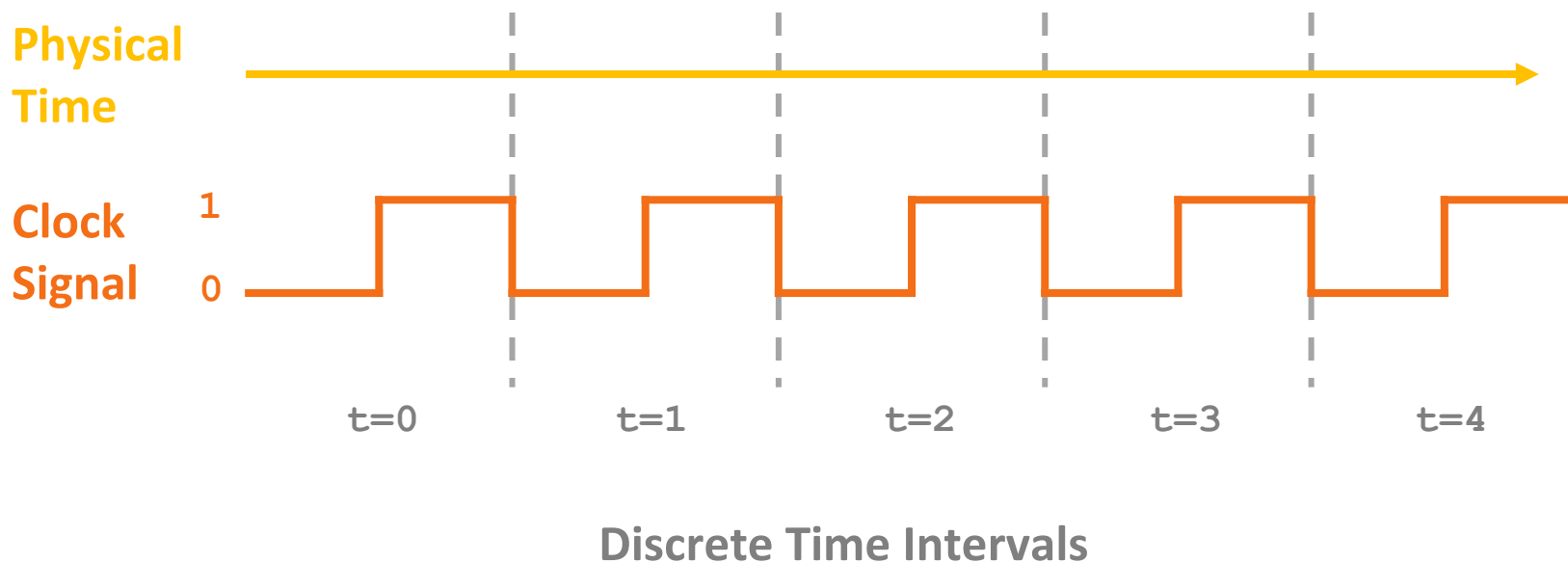
# Physical Timekeeping


- ❖ Hardware keeps track of time using an alternating signal
  - Creates the idea of **discrete time**: state changes only occur in discrete intervals, right when signal alternates



# Adding a Clock: Ideal

 


 - ❖ We want this behavior from a simple, combinational Not gate:



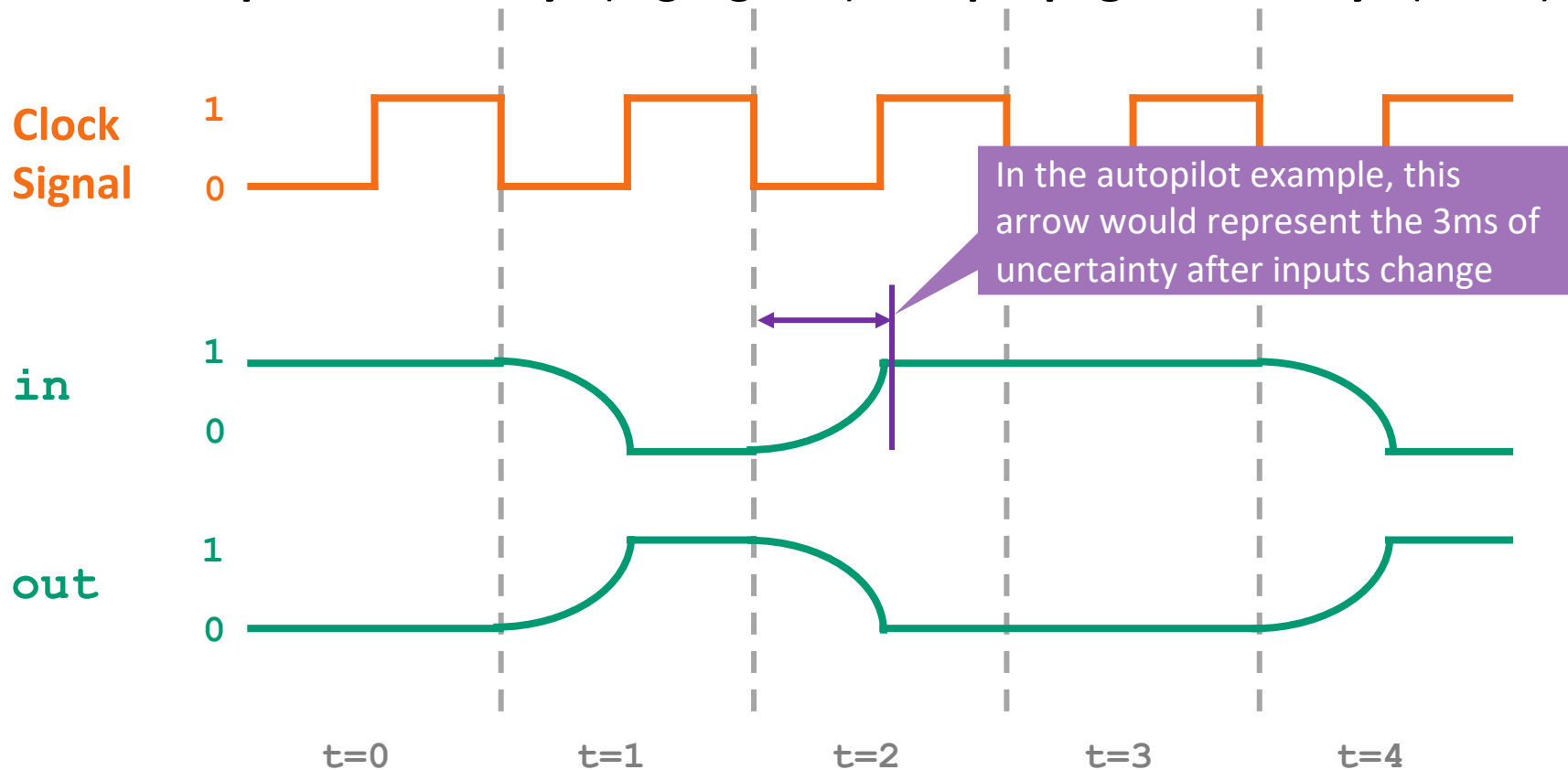
# Adding a Clock: Reality

- ❖ Combinational logic may be incorrect for a period immediately after inputs change
  - **Computation delays** (logic gates) and **propagation delays** (wires)



 
# Adding a Clock: Clock Cycles

- ❖ Choose a clock cycle length slightly longer than the delays


 
# Adding a Clock: Abstraction

- ❖ If we use a long enough clock cycle, we can *pretend* that combinational chips (like Not) work instantly



# Five-minute Break!

- ❖ Feel free to stand up, stretch, use the restroom, drink some water, review your notes, or ask questions
- ❖ We'll be back at:
- ❖ Any song recommendations? Respond on Poll Everywhere at <https://pollev.com/cse390b>
- ❖ Research shows mid-lecture breaks reduce the decline of attention in the middle of lecture (Olmsted, 1999)



Vote at <https://pollev.com/cse390b>

**When is a (or are) better time(s) for Eric's Wednesday office hours (previously Wednesdays from 1:30-2:30pm)?**

- A. Wednesdays, 11:30-12:30pm**
- B. Wednesdays, 5:30-6:30pm**
- C. Thursdays, 11:30-12:30pm**
- D. Thursdays, 12:30-1:30pm**
- E. The time is good as is (Wednesdays, 1:30-2:30pm)**


# Lecture Outline

- ❖ Bloom's Taxonomy
  - Applying Higher Levels of Cognition to Learning
- ❖ Cornell Note Taking Method
  - System for Taking, Organizing, and Reviewing Notes
- ❖ Representing Time in Hardware
  - Sequential Logic vs. Combinational Logic
  - Adding a Clock
- ❖ **Sequential Logic**
  - **Data Flip-Flop (DFF) Implementation and Examples**

 
# Combinational vs. Sequential Abstraction



**Combinational:** a function of the current inputs




 **Sequential:** a function of previous inputs (has “memory”)


 
# The Flip-Flop Gate



- ❖ Simplest state-keeping component
  - 1-bit input, 1-bit output
  - Wired to the clock signal
  - Always outputs its previous input:  $\text{out}(t) = \text{in}(t-1)$
- ❖ Implementation: a gate that can flip between two stable states (remembering 0 vs. remembering 1)
  - Gates with this behavior are “Data Flip Flops” (DFFs)



# Aside: Treating Flip-Flop as Primitive

- ❖ Disclaimer: CAN be made from Nand gates exclusively!
  - But requires wiring them together in a “messy” loop that the hardware simulator can't simulate and isn't very educational
- ❖ For simplicity, we will treat Flip-Flop as primitive in the projects
  - Just like Nand, you can use the built-in implementation

# Flip-Flop Behavior

  


# Sequential Chips

- ❖ A category of chips that utilize the clock signal, in addition to any combinational logic
- ❖ Capable of:
  - Maintaining state
  - Optionally, acting on that state and the current inputs
    - Can incorporate combinational logic as well
- ❖ Constructed from:
  - DFFs
  - Combinational logic (which is entirely constructed from Nand)

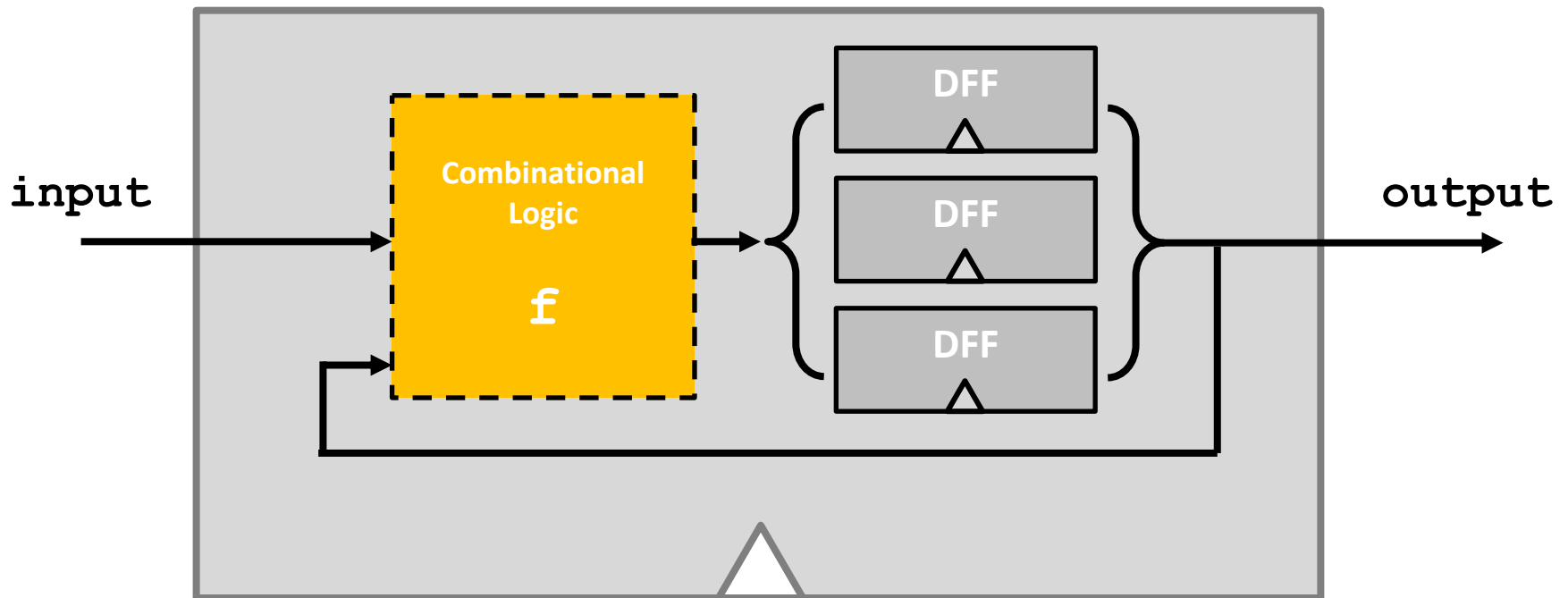
# Sequential Chips

$$\text{output}(t) = f(\text{state}(t-1), \text{input}(t))$$



# Flip-Flop: Time Series

## ❖ DFF Specification:

 

$$\text{out}(t) = \text{in}(t-1)$$

<b>in</b>	0	0	1	1	0	1	0	...
<b>out</b>	0	0	0	1	1	0	1	...
<b>time</b>	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

Example:  $\text{out}(t=3) = \text{in}(t=2)$

# DFF Example 1: Specification

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$


- ❖ Takes two inputs,  $a$  and  $b$ , and outputs the  $\text{XOR}$  of them
  - Note that out at time  $t$  is determined by  $a$  and  $b$  at time  $t-1$
  - We will need to use a DFF
- ❖ Exercise: Draw out the corresponding circuit diagram

# DFF Example 1: Circuit Diagram


- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

- ❖ Circuit diagram:

 

# DFF Example 1: HDL Implementation

 

```
CHIP Example1 {  
    IN a, b;  
    OUT out;
```


**PARTS:**

```
Xor(a=a, b=b, out=xorout);  
DFF(in=xorout, out=out);
```

```
}
```

# DFF Example 1: Time Series

❖ Example specification:

 

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

<b>a</b>	0	0	1	1	1	0	0	...
<b>b</b>	0	1	0	1	1	1	0	...
<b>out</b>	0	0	1	1	0	0	1	...
<b>time</b>	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

Example:  $\text{out}(t=3) = \text{Xor}(a(t=2), b(t=2))$

# DFF Example 2: Specification

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$


- ❖ Notice how the specification uses  $\text{out}(t-1)$  as an input for  $\text{out}(t)$ 
  - Implies the necessity of circular wiring, separated by a DFF
- ❖ Exercise: Draw out the corresponding circuit diagram

# DFF Example 2: Circuit Diagram

- ❖ Example specification:


$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Circuit diagram:

 

# DFF Example 2: HDL Implementation

- ❖ Example specification:

 


$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Exercise: Write out the HDL Implementation

# DFF Example 2: HDL Implementation

- ❖ Example specification:

 

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Exercise: Write out the HDL Implementation

```
CHIP Example2 {
```

```
  IN in;
```

```
  OUT out;
```

```
  PARTS:
```


```
  Xor(a=in, b=prevout, out=xorout);
```

```
  DFF(in=xorout, out=prevout, out=out);
```

```
}
```

# DFF Example 2: Time Series

❖ Example specification:

 

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

<b>in</b>	0	0	1	1	1	0	0	...
<b>out</b>	0	0	0	1	0	1	1	...
<b>time</b>	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

Example:  $\text{out}(t=1) = \text{Xor}(\text{in}(t=0), \text{out}(t=0))$

# DFF Example 3: Specification

- ❖ Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$


- ❖ Exercise: Draw out the corresponding circuit diagram

# DFF Example 3: Circuit Diagram

- ❖ Example specification:


$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

 - ❖ Exercise: Draw out the corresponding circuit diagram



# DFF Example 3: HDL Implementation

- ❖ Example specification:

 


$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

- ❖ Exercise: Write out the HDL Implementation

# DFF Example 3: HDL Implementation

- ❖ Example specification:

 

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

- ❖ Exercise: Write out the HDL Implementation

```
CHIP Example3 {
  IN in;
  OUT out;
```


## **PARTS:**

```
Not(in=prevout, out=notprevout);
And(a=in, b=notprevout, out=andout);
DFF(in=andout, out=prevout, out=out);
```

```
}
```

# DFF Example 3: Time Series

❖ Example specification:

 

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

<b>in</b>	1	1	0	1	1	0	0	...
<b>out</b>	0	1	0	0	1	0	0	...
<b>time</b>	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

Example:  $\text{out}(t=1) = \text{And}(\text{Not}(\text{out}(t=0)), \text{in}(t=0))$

# Lecture 5 Wrap-up

## ❖ Project Reminders

- Project 2 grades released by Thursday (feedback can be viewed on Gradescope)
- **Project 3 due Thursday (4/14) at 11:59pm PDT**

## ❖ Lecture 6 Reading: [Storing Data Using Memory](#)

- ❖ Course staff will create a guide for untagging and Eric will cover the Project 4 overview in greater depth on Thursday