

CSE 390B, Spring 2022

Building Academic Success Through Bottom-Up Computing

Exam Preparation & Building a Computer

Exam Preparation, Overview of Building a Computer, Hack
CPU Logic

Lecture Outline

- ❖ **Exam Preparation**
 - **Study Strategies, Mock Exam Problem**

- ❖ **Overview of Building a Computer**
 - **Architecture, Fetch and Execute Cycle**

- ❖ **Hack CPU Logic**
 - **Implementation and Operations**

Gearing Up For Exams

❖ Make a Study Plan

- What key topics / concepts does your exam cover?
- How might your study guides look different for specific classes?
- What resources, materials, or people might you engage with?

❖ Create a Schedule

- Do not cram
- Office hours, review sessions, study groups
- Reference your weekly time commitments & quarterly calendar

❖ Test Yourself

- What are ways that can help address this?
- Replicate exam-like environments

Exams Preparation Discussion

- ❖ How do you usually prepare for your exams?
- ❖ What is one thing that is effective and ineffective about the way you study? Why?
- ❖ What are some effective exam preparation strategies that you would find most helpful?
- ❖ How might you implement some of these effective strategies for change your exam preparation strategy for this quarter?

Project 6, Part I: Mock Exam Problem

- ❖ Schedule a 30-minute session based on your group members availability to do one mock exam problem
- ❖ Determine how you will connect with each other
- ❖ Determine where your session will be located
- ❖ Comment your group's meeting day and time on the [Project 6 Mock Exam Groups spreadsheet](#)
 - We will make an Ed post with this spreadsheet


Lecture Outline

- ❖ Exam Preparation
 - Study Strategies, Mock Exam Problem
- ❖ **Overview of Building a Computer**
 - **Architecture, Fetch and Execute Cycle**
- ❖ Hack CPU Logic
 - Implementation and Operations


Building a Computer

- ❖ All your hardware efforts are about to pay off!
- ❖ Perspective: **BUILDING A COMPUTER**
- ❖ In Project 6, you will build **Computer.hdl**, the final, top-level chip in this course
 - For all intents and purposes, a real computer
 - Simplified, but organization very similar to your laptop
- ❖ Project 7 onward, we will write software to make it useful

Von Neumann Architecture

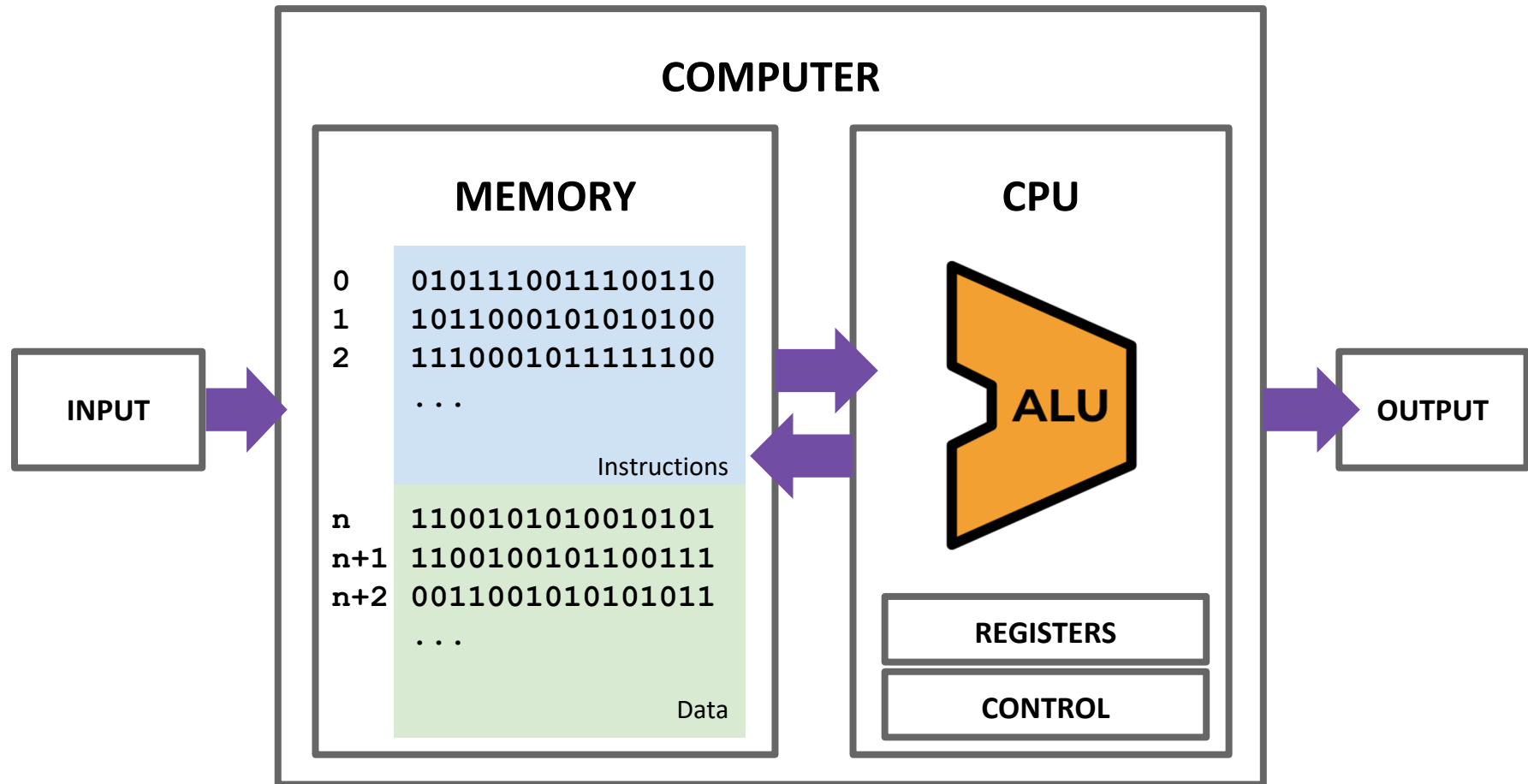

Connecting the Computer: Buses

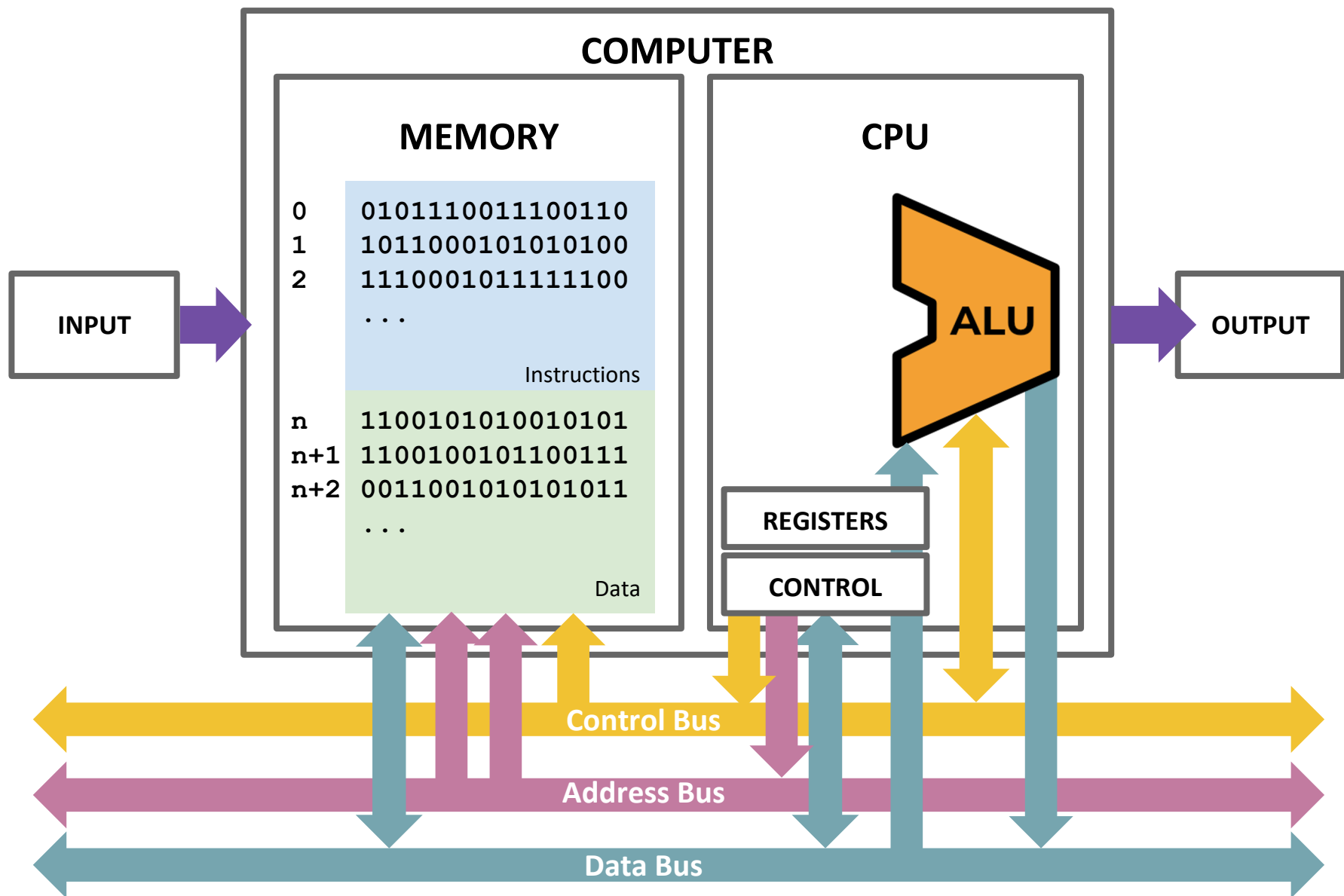


Basic CPU Loop

- ❖ Repeat forever:
 - **Fetch** an instruction from the program memory
 - **Execute** that instruction

Fetching

 - ❖ Specify which instruction to read as the address input to our memory
- ❖ Data output: actual bits of the instruction




Executing


- ❖ The instruction bits describe exactly “what to do”
 - A-instruction or C-instruction?
 - Which operation for the ALU?
 - What memory address to read? To write?
 - Should I jump after this instruction, and if so, where?

- ❖ Executing the instruction involves data of some kind
 - Accessing registers
 - Accessing memory

Combining Fetch & Execute

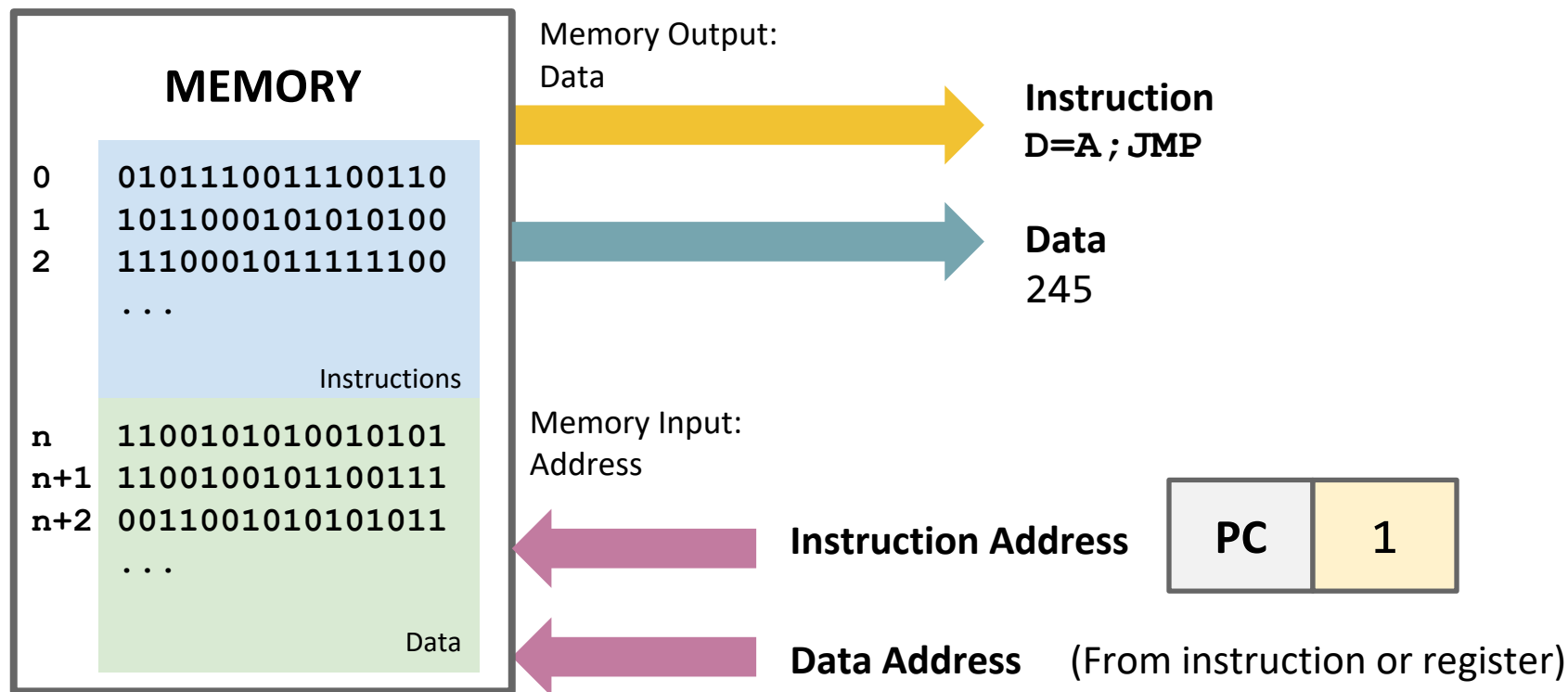


Combining Fetch & Execute

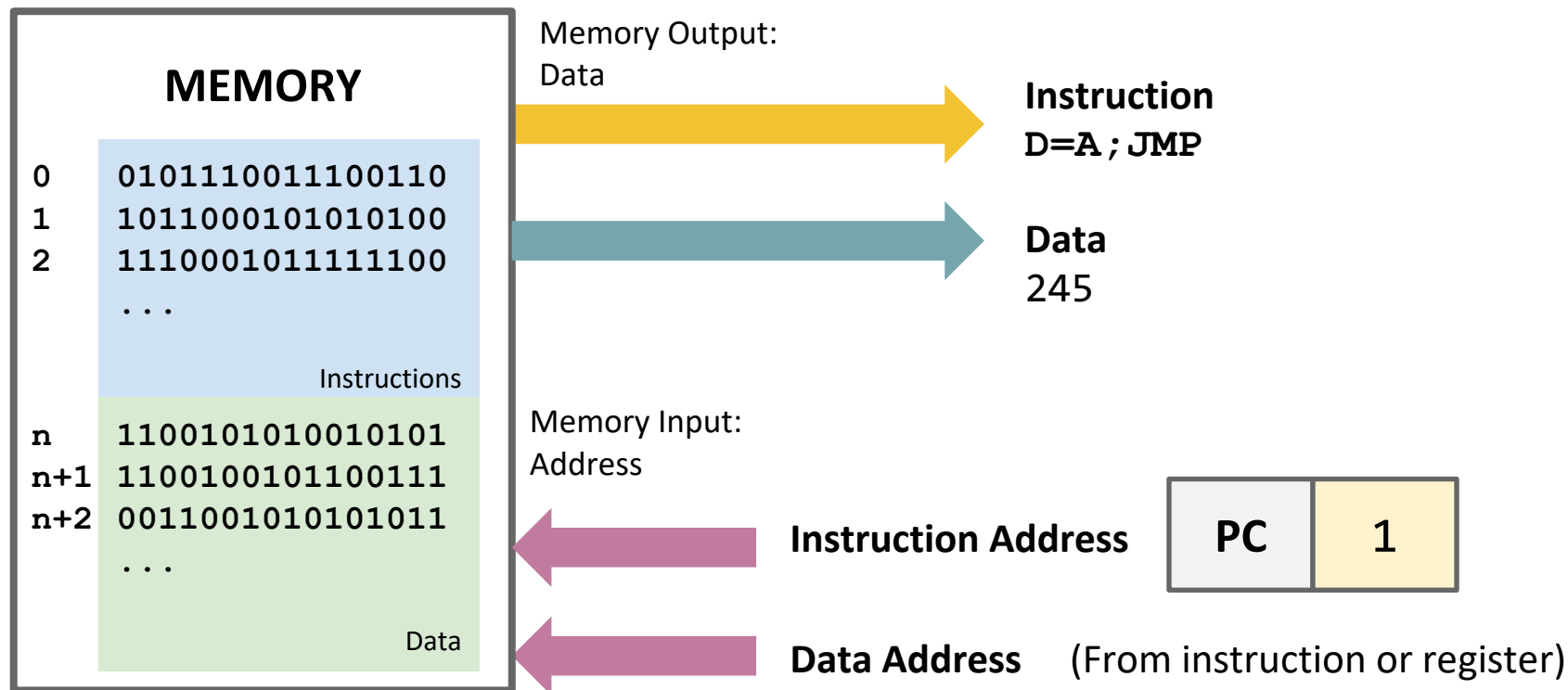

❖ Could we implement with **RAM16K.hd1**?


Combining Fetch & Execute

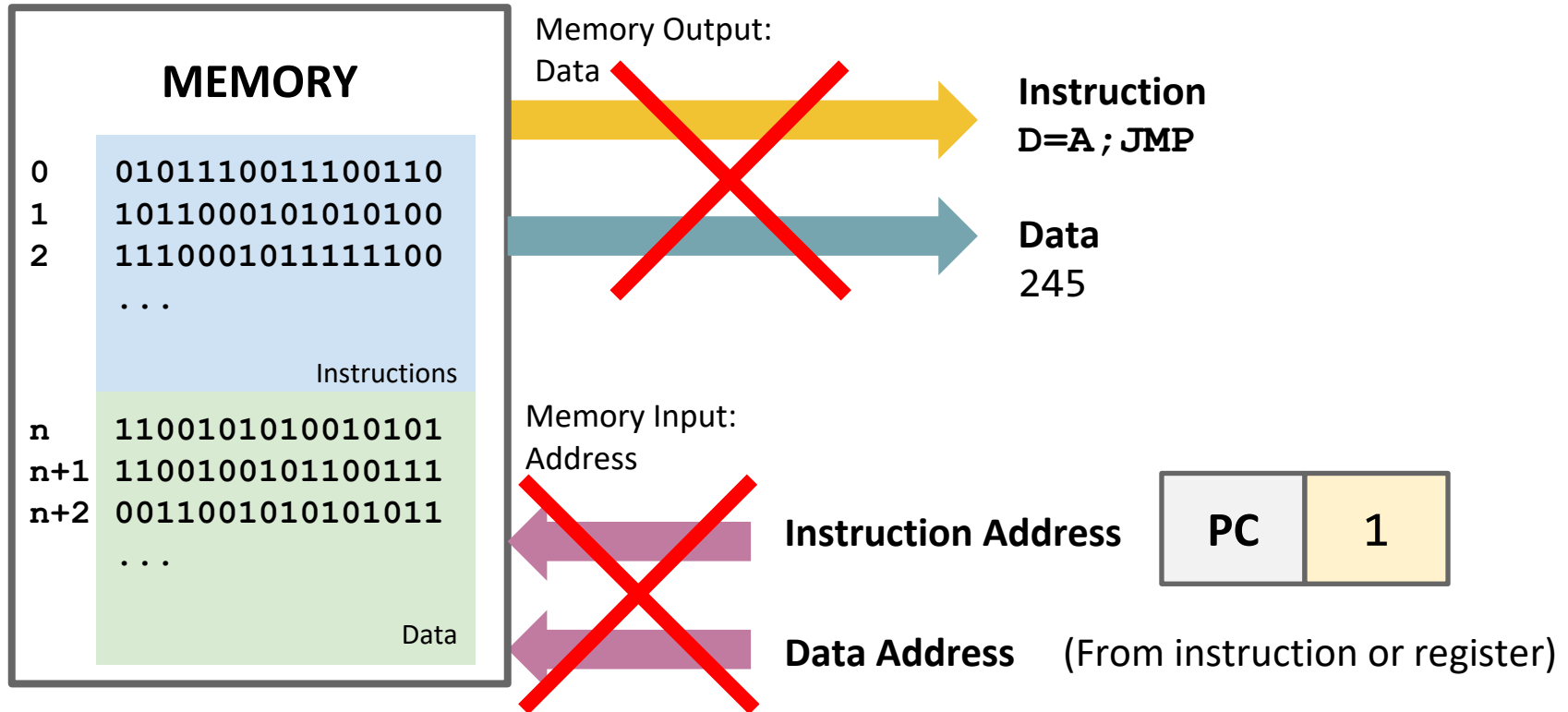

❖ Could we implement with **RAM16K.hd1**?


- **No!** Our memory chips only have one address input and one output

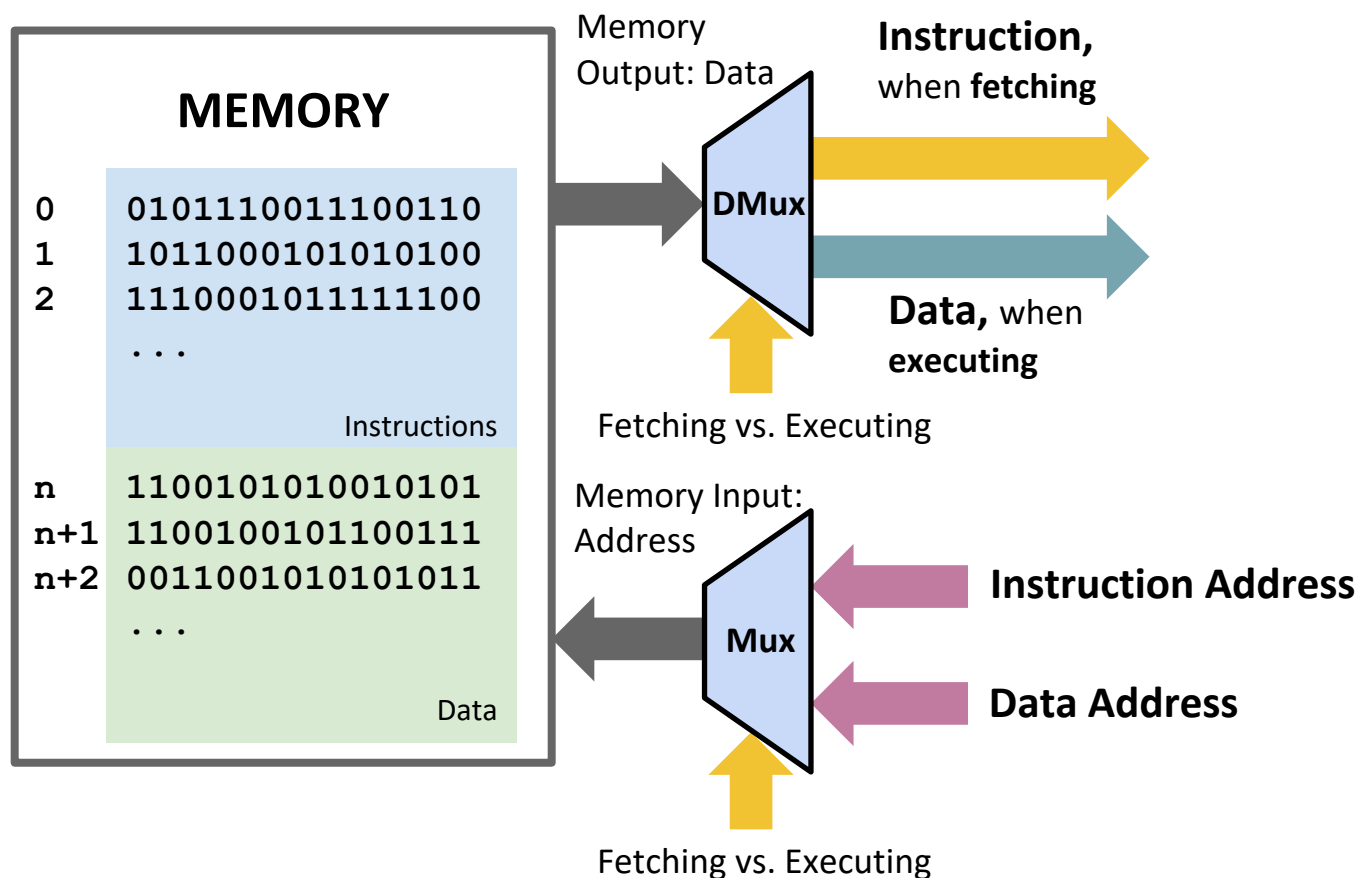Solution 1: Fetching / Executing Separately



❖ Can use multiplexing to share a single input or output

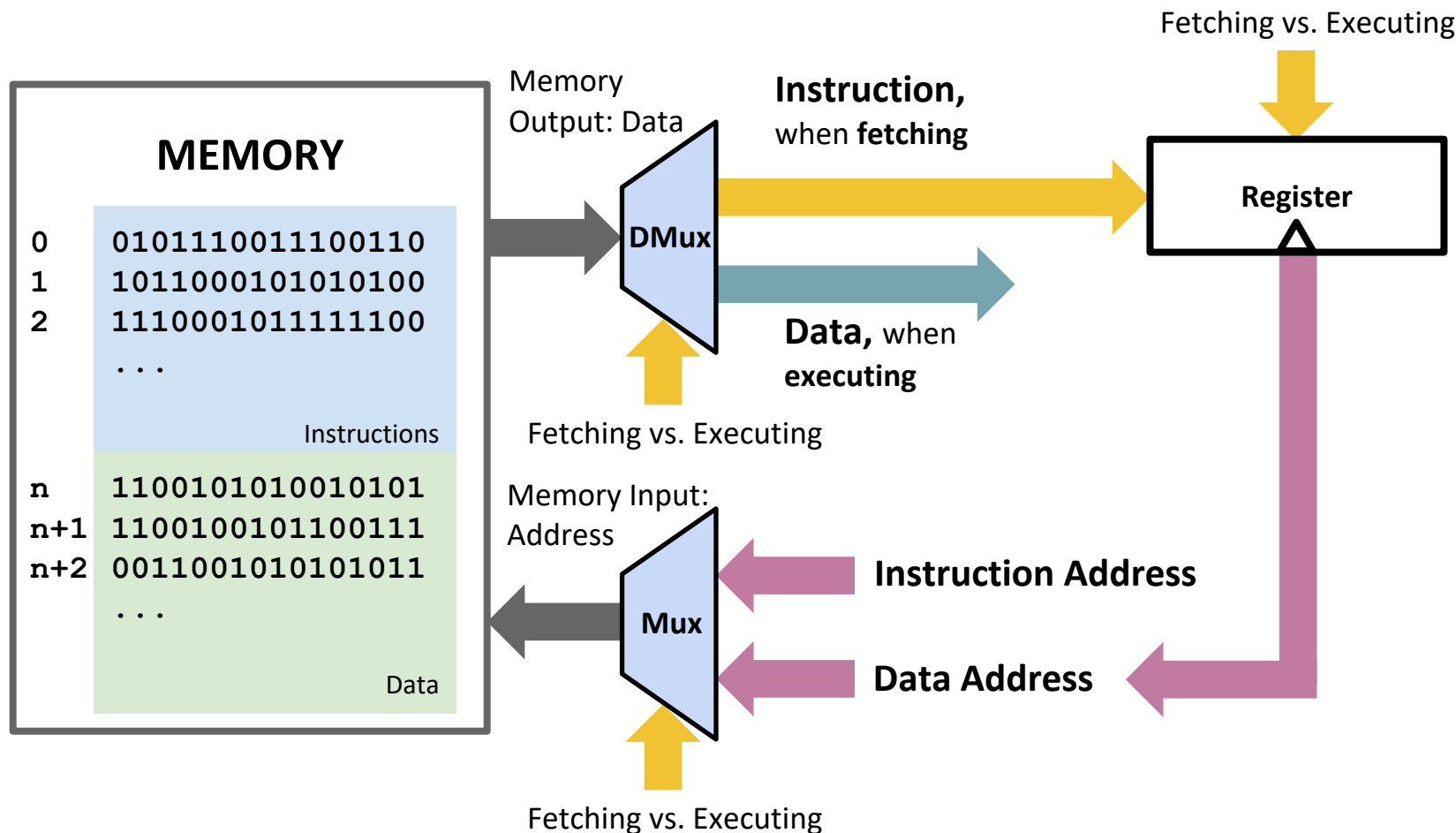Solution 1: Fetching / Executing Separately



- ❖ Need to store fetched instruction so it's available during execution phase

Solution 2: Separate Memory Units

- ❖ Separate instruction memory and data memory into two different chips
 - Each can be independently addressed, read from, written to
- ❖ Pros:
 - Simpler to implement
- ❖ Cons:
 - Fixed size of each partition, rather than flexible storage
 - Two chips → redundant circuitry

Five-minute Break!

- ❖ Feel free to stand up, stretch, use the restroom, drink some water, review your notes, or ask questions
- ❖ We'll be back at:
- ❖ Research shows mid-lecture breaks reduce the decline of attention in the middle of lecture (Olmsted, 1999)

Lecture Outline

- ❖ Exam Preparation
 - Study Strategies, Mock Exam Problem
- ❖ Overview of Building a Computer
 - Architecture, Fetch and Execute Cycle
- ❖ **Hack CPU Logic**
 - **Implementation and Operations**




Vote at <https://pollev.com/cse390b>

Which of the following statements about the Hack CPU is FALSE?


- A. The Mux and ALU output is connected to the A register because it's a possible destination from a C instruction**
- B. The A register and the M pseudo-register are never involved in a computation together**
- C. writeM determines whether the value should be updated in memory at addressM to outM**
- D. We feed the A register's output to the PC because this is the value that we increment**
- E. We're lost...**

Hack CPU

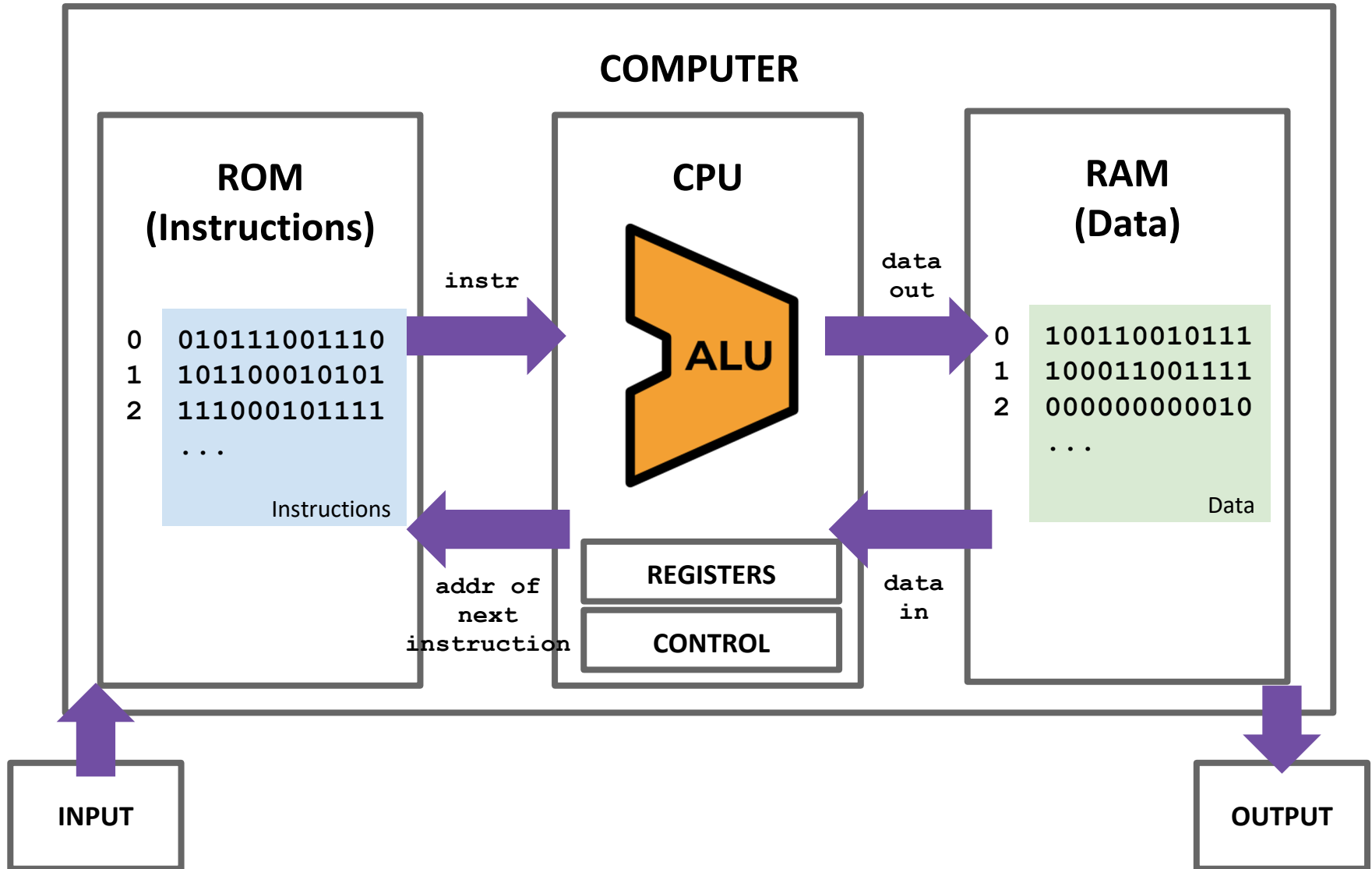


Hack CPU Interface Inputs

 - ❖ **inM**: Value coming from memory
- ❖ **instruction**: 16-bit instruction
- ❖ **reset**: if 1, reset the program




Hack CPU Interface Outputs

 
- ❖ **outM**: value used to update memory if writeM is 1
- ❖ **writeM**: if 1, update value in memory at addressM with outM
- ❖ **addressM**: address to read from or write to in memory
- ❖ **pc**: address of next instruction to be fetched from memory



Hack CPU Implementation

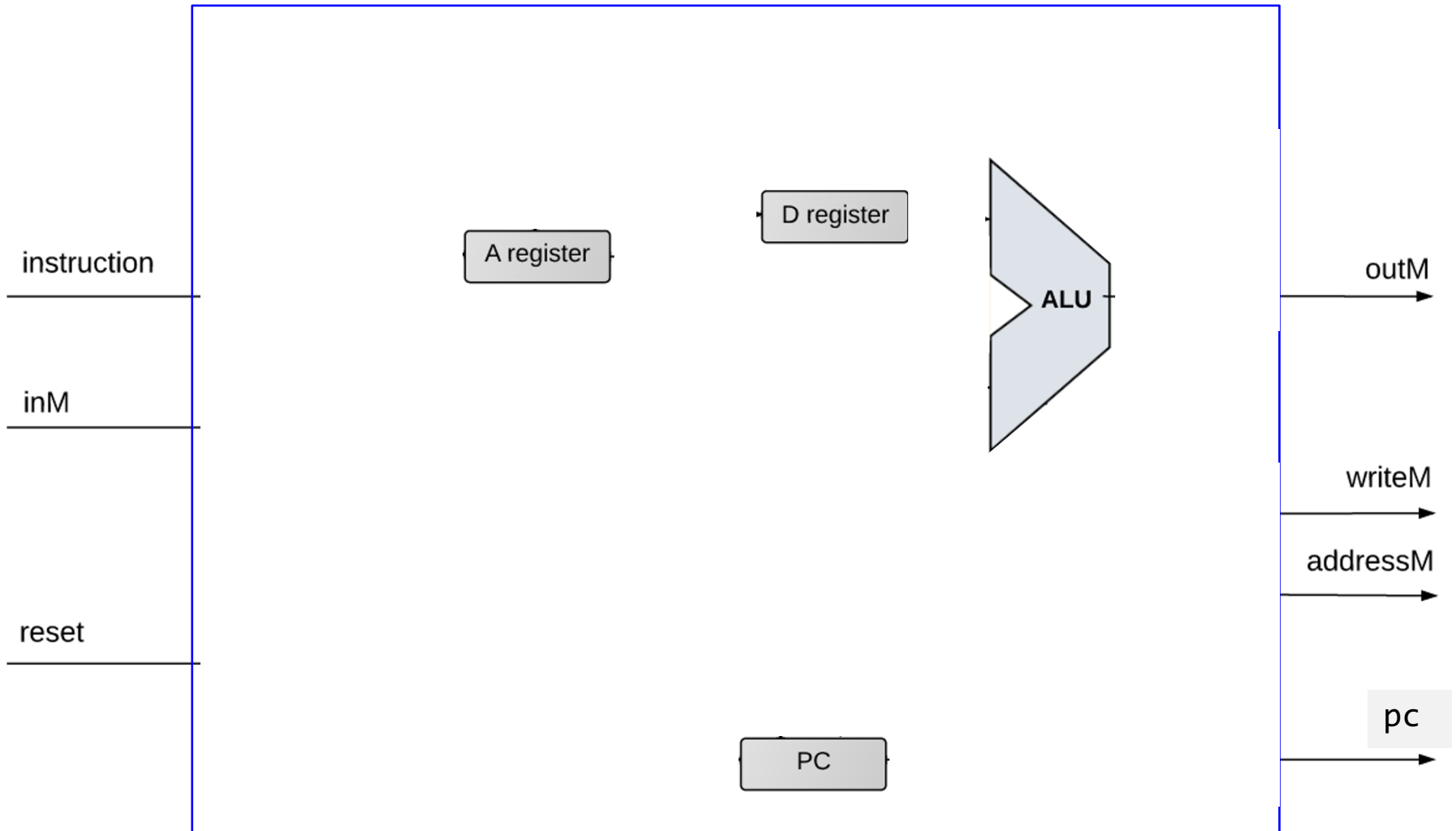


Hack CPU Implementation

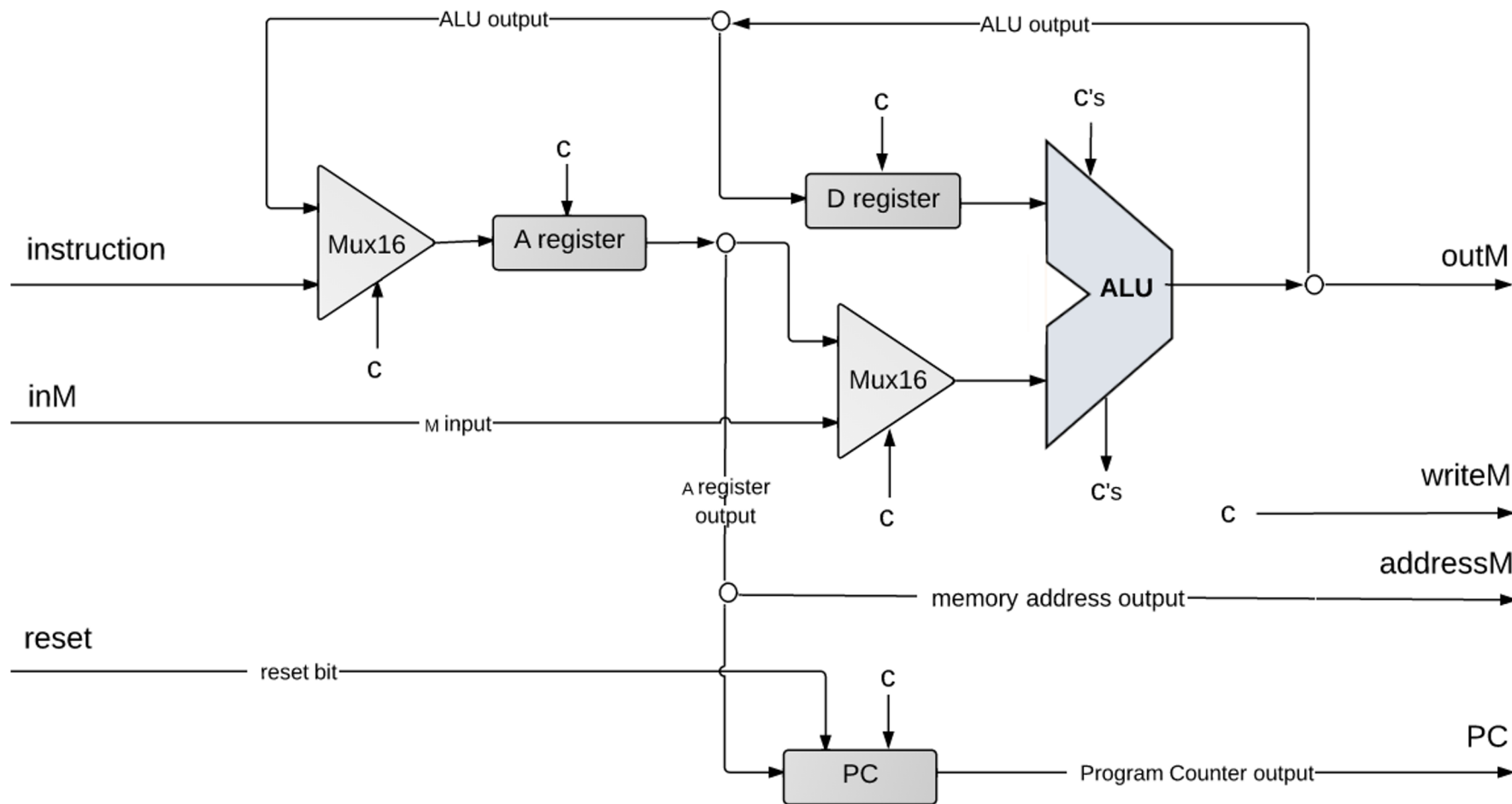


(each "c" symbol represents a control bit)

CPU Operation: Instruction Handling

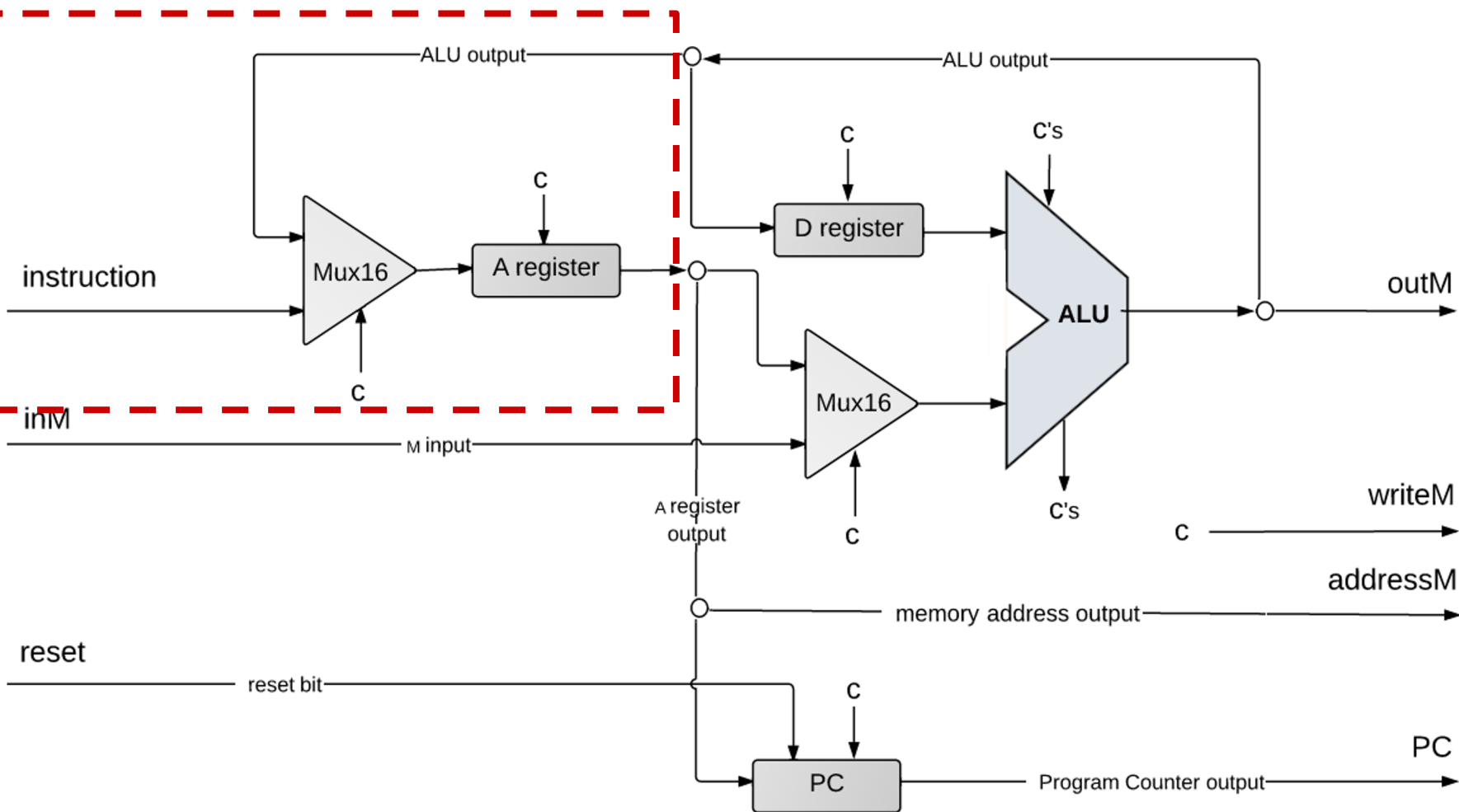


(each "c" symbol represents a control bit)

CPU Operation: Instruction Handling

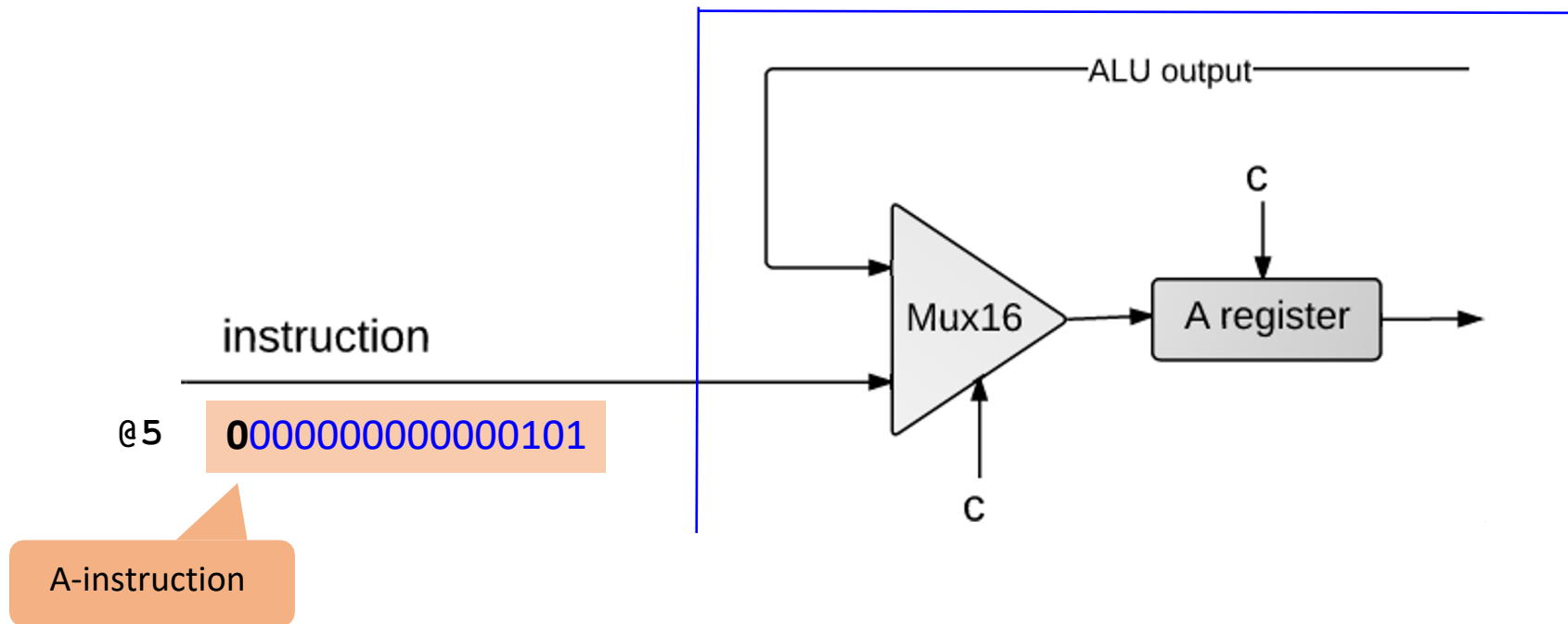


CPU Operation: Instruction Handling

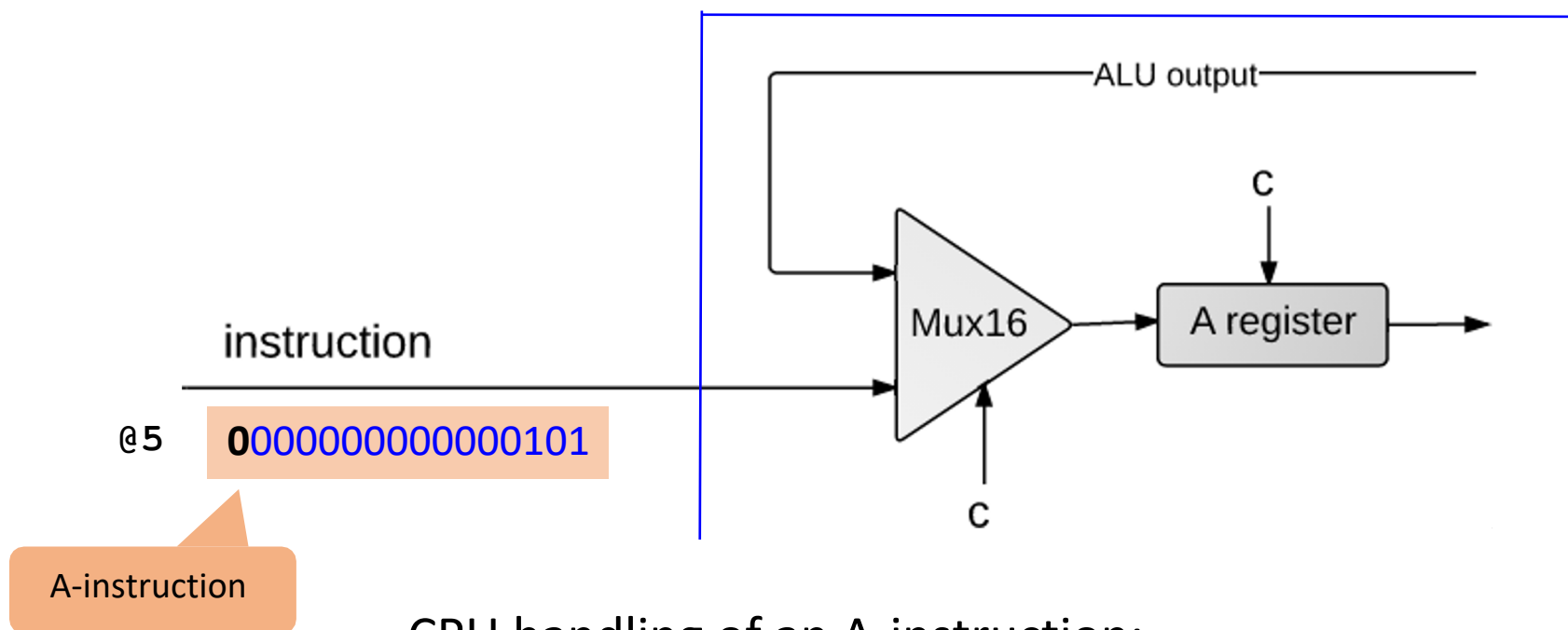


CPU handling of an A-instruction:

- ❖ Decodes the instruction into:
 - op-code
 - 15-bit value
- ❖ Stores the value in the A-register
- ❖ Outputs the value (not shown in this diagram)

CPU Operation: Instruction Handling

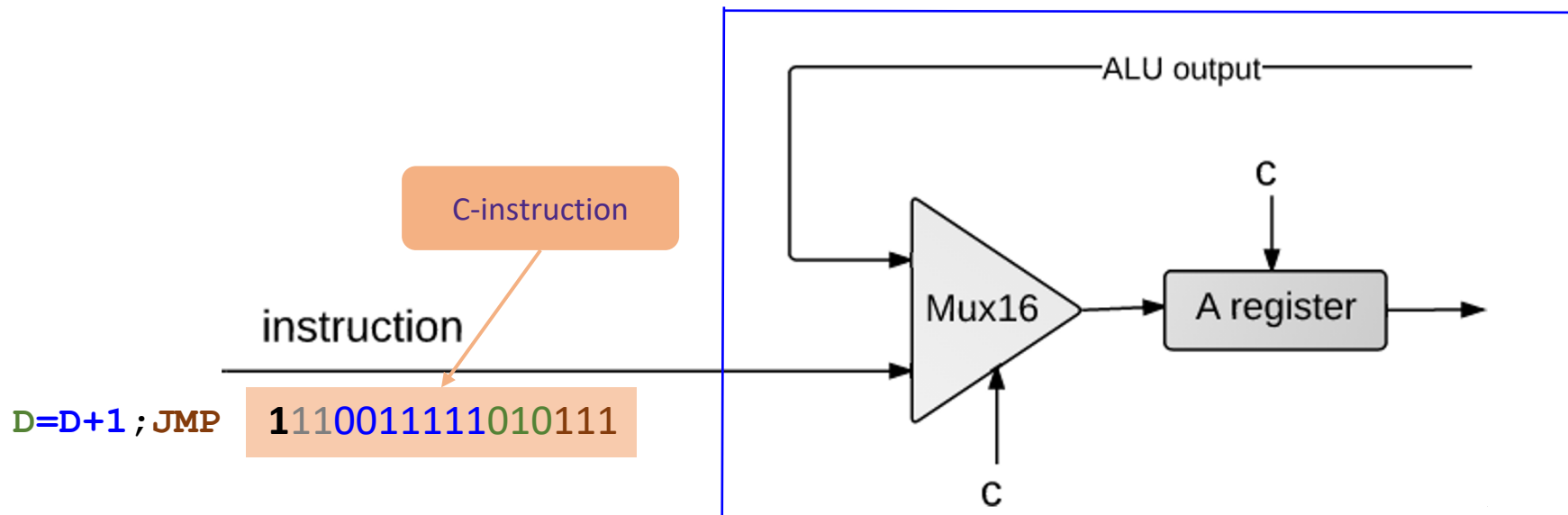


CPU Operation: Instruction Handling

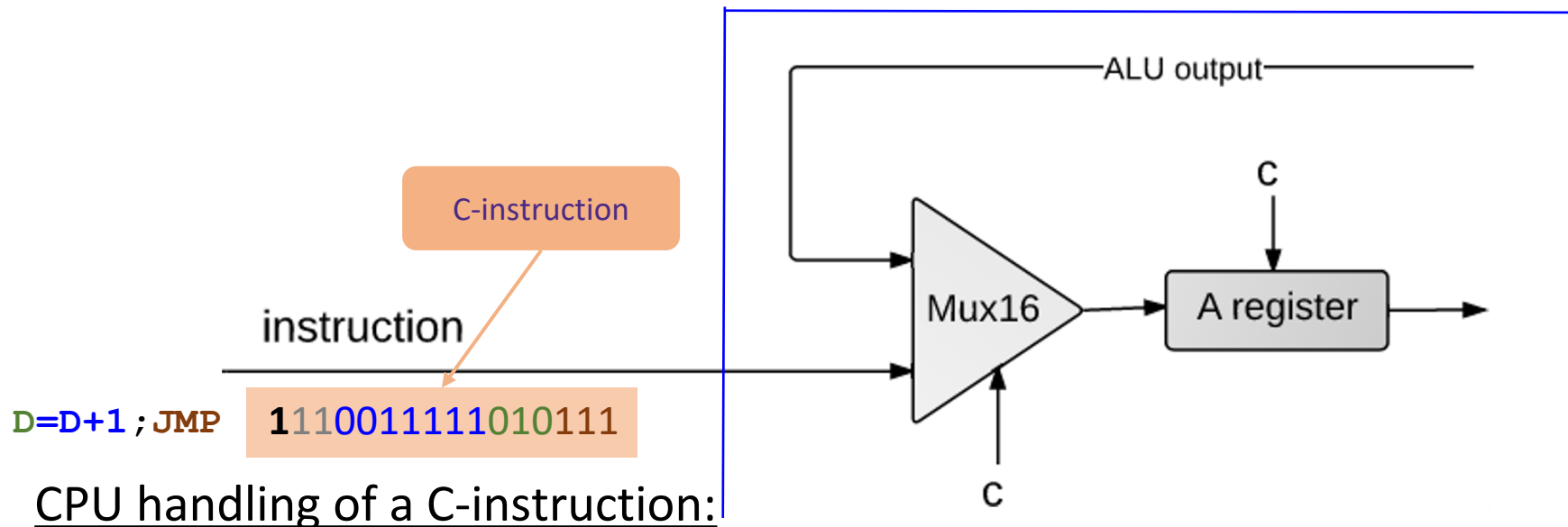

- ❖ Decodes the instruction bits into:
 - Op-code
 - ALU control bits
 - Destination load bits
 - Jump bits
- ❖ Routes these bits to their chip-part destinations
- ❖ The chip-parts (most notably, the ALU) execute the instruction

CPU Operation: Handling C-Instructions

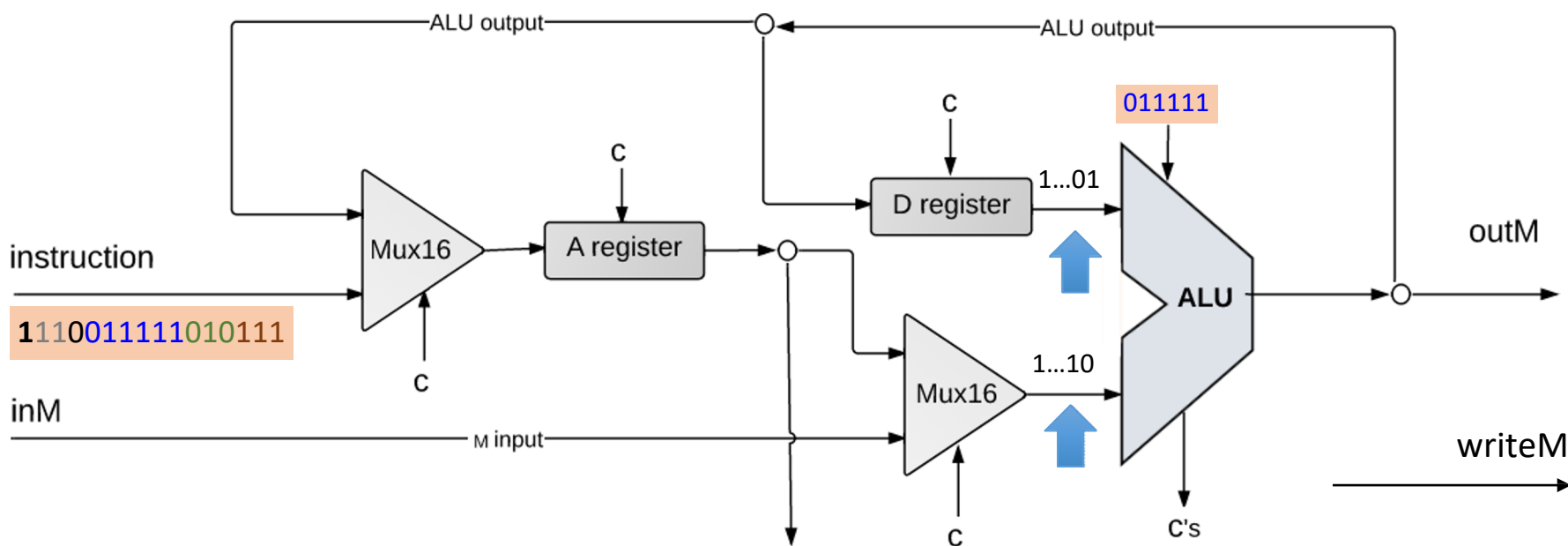


ALU data inputs:

- ❖ Input 1: from the D-register
- ❖ Input 2: from either:
 - A-register, or
 - data memory

ALU control inputs:

- ❖ Control bits (from the instruction)


CPU Operation: Handling C-Instructions

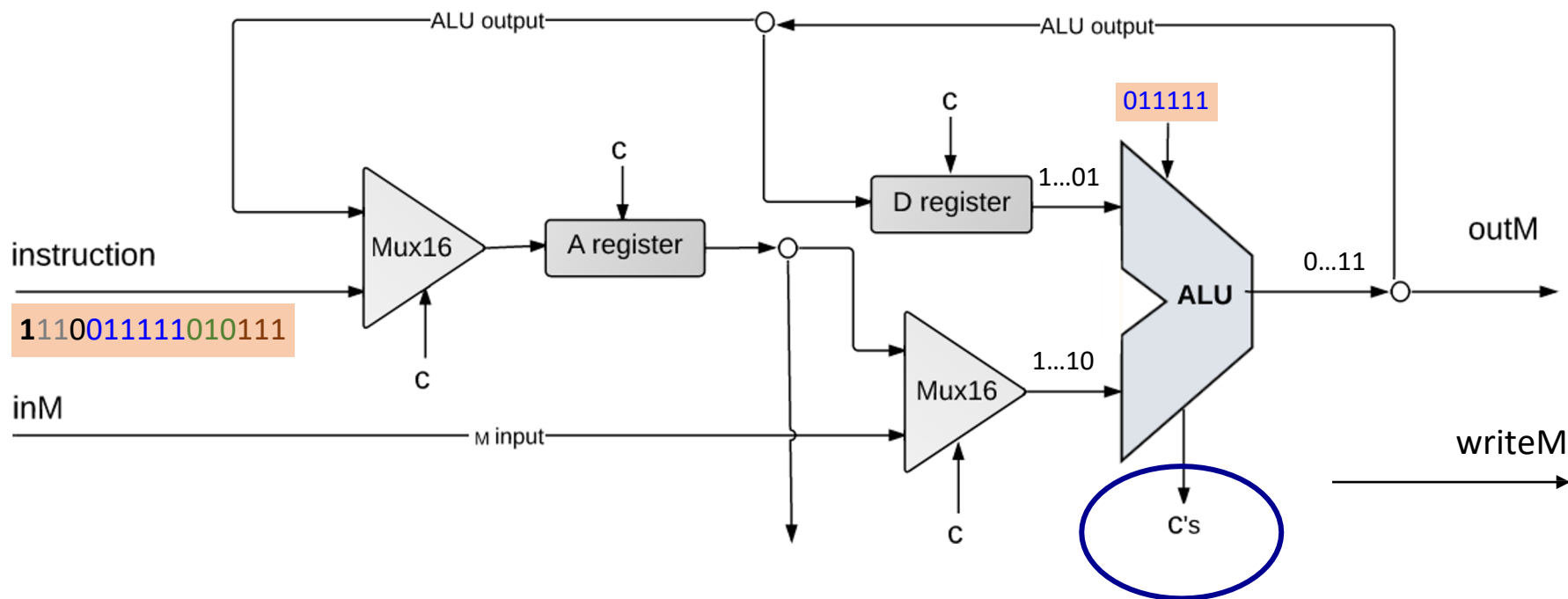


ALU control outputs:

- ❖ Is the output negative?
- ❖ Is the output zero?


CPU Operation: Control

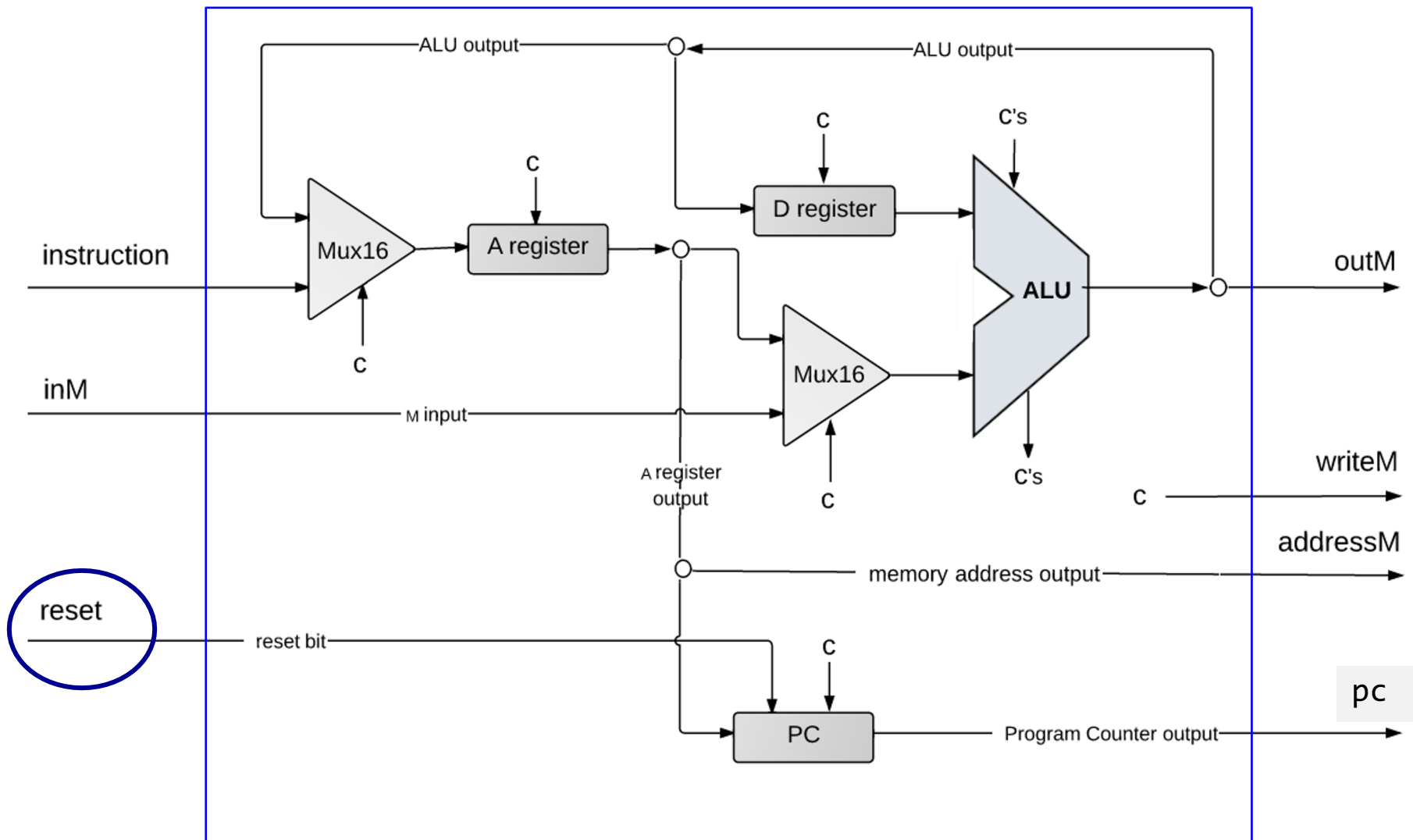

CPU Operation: Control

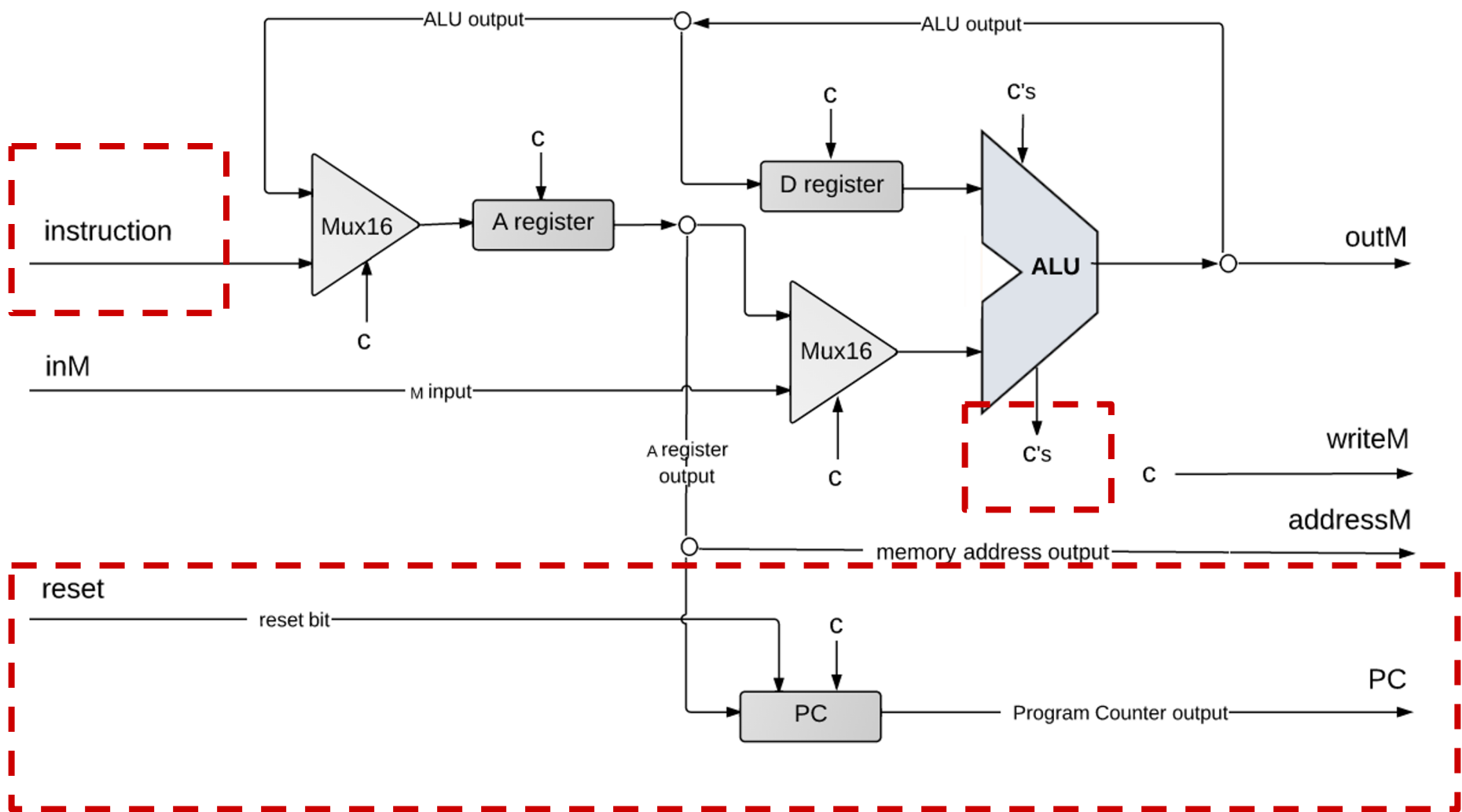

CPU Operation: Control

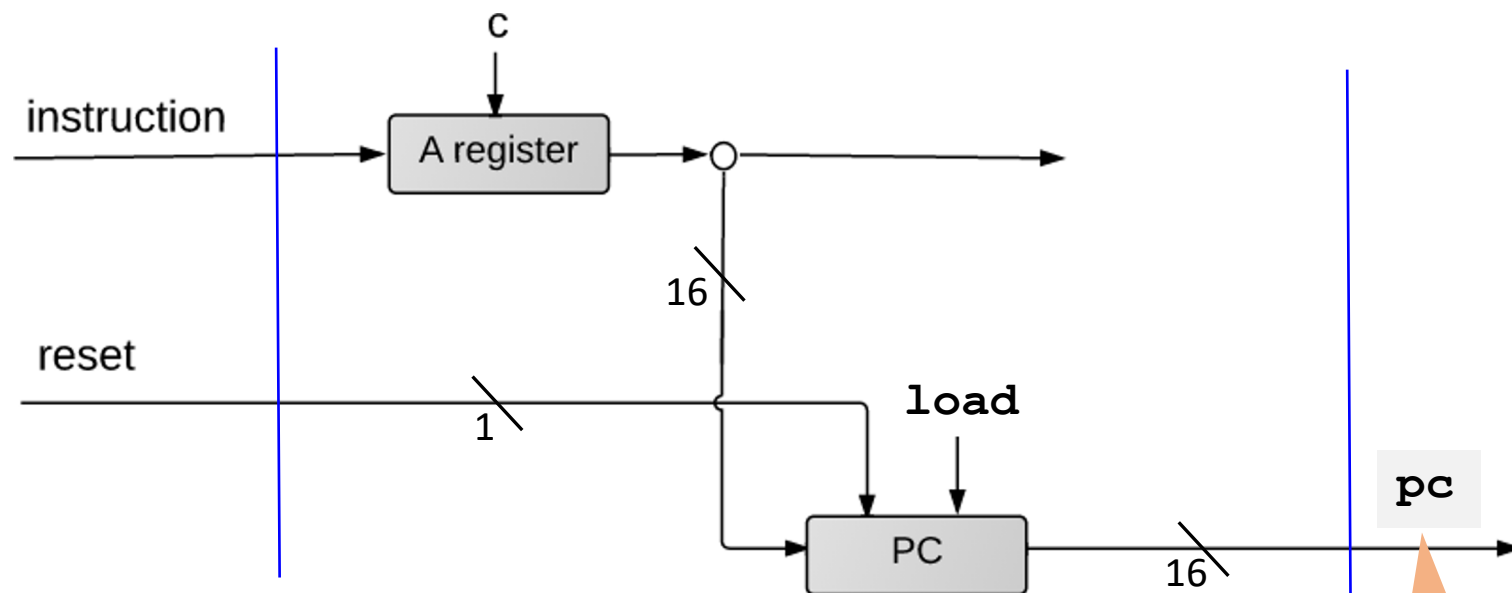

PC operation (abstraction)


Outputs the address of the next instruction:

- ❖ Restart: $PC = 0$
- ❖ No jump: $PC++$
- ❖ Go to: $PC = A$
- ❖ Conditional go to:

if (condition)	$PC = A$
else	$PC ++$

address of next instruction

CPU Operation: Control

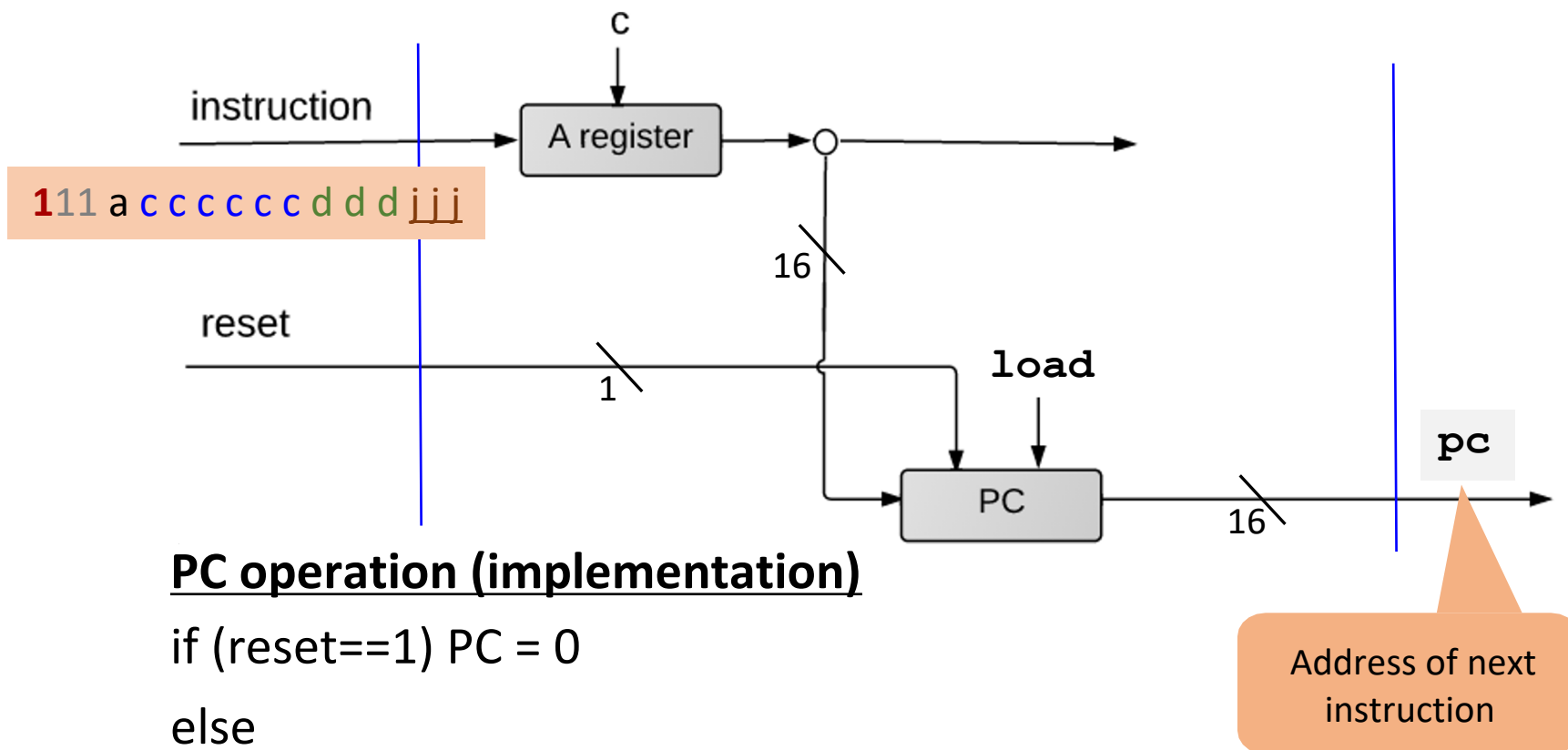

PC operation (implementation)

if (reset==1) PC = 0

else


// In the course of handling the current instruction:

$load = f(\text{jump bits, ALU control outputs})$

if (load == 1) PC = A // jump

else PC++ // next instruction

Hack CPU Implementation: That's It!

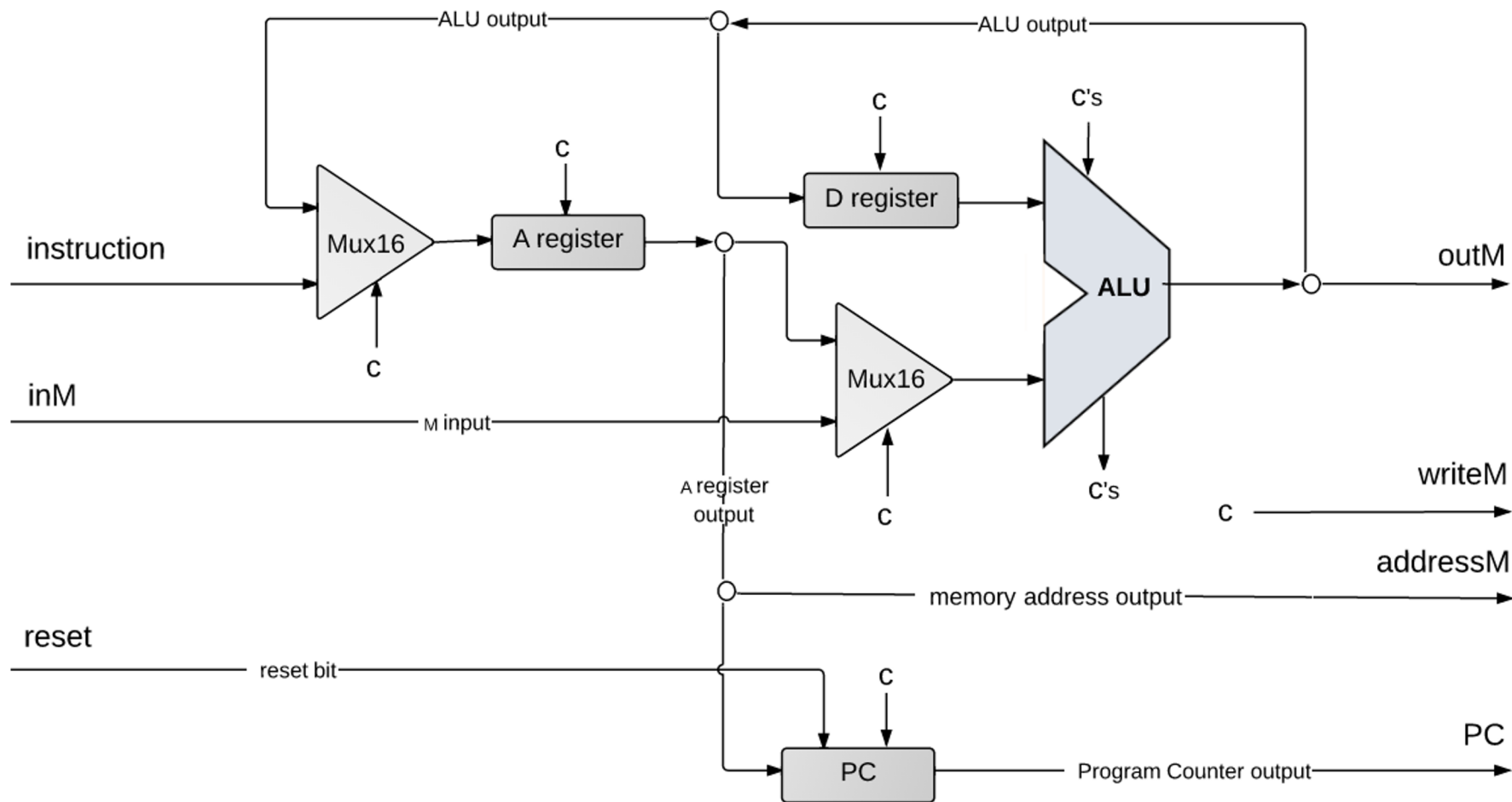

Lecture 9 Wrap-up

- ❖ Project Reminders
 - **Project 5 due Thursday (4/28) at 11:59pm PDT**
- ❖ CSE 390B Midterm Exam next Thursday (5/5) during lecture
- ❖ No reading for this Thursday's lecture