

CSE 390B, Winter 2022

Building Academic Success Through Bottom-Up Computing

Boolean Logic, Project 1 Overview

Study Environment, Circuit Fundamentals, Hardware
Simulation, Project 1 Overview

Lecture Outline

- ❖ **Study Environment Discussion**
- ❖ Reading Overview and Q&A
- ❖ Hardware Design Language
- ❖ Project 1
 - Overview & Example: XOR
 - Demo
 - Group work

Study Environment Discussion

In your small groups, discuss what your ideal study environment looks like.

- ❖ What does your environment look like?
- ❖ What are factors that may impact your ideal study environment?
- ❖ What do your study spaces look like when you're having to do online learning vs. in-person learning?

Lecture Outline

- ❖ Study Environment Discussion
- ❖ **Reading Overview and Q&A**
- ❖ Hardware Design Language
- ❖ Project 1
 - Overview & Example: XOR
 - Demo
 - Group work

Boolean Values

- ❖ A binary choice: True or False
- ❖ Maps to “high” signal (true) or “low” signal (false)



“Off”

False

0



“On”

True

1

Boolean Operations

- ❖ Use simple logical operations to combine Boolean values
 - **Truth Table:** Writing out every possible set of inputs and the corresponding output of the operation
 - Operations correspond to physical hardware gates

- ❖ Examples:

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

$$F = A \text{ OR } B$$


A	F
0	1
1	0

$$F = \text{NOT } A$$

Boolean Operations (cont'd)

- ❖ Combinations of Boolean values/inputs
- ❖ Three ways to specify a Boolean function:
 - Boolean expression: $F = \text{NOT} ((A \text{ OR } B) \text{ AND } C)$

- Circuit diagram with logic gates:

 

- Truth table:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression \rightarrow Truth Table

- ❖ We know how to build a truth table from an expression
 - Evaluate the Boolean expression on all possible inputs

$$F(A, B, C) = \text{NOT} ((A \text{ OR } B) \text{ AND } C)$$




A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression ← Truth Table

❖ But can we do it in reverse?
 
$$F(A, B, C) = \text{NOT} ((A \text{ OR } B) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression ← Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

Boolean Expression ← Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

A AND B AND C

Boolean Expression ← Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C


A AND B AND C

$F = \text{NOT}(A) \text{ AND NOT}(B) \text{ AND } C \text{ OR NOT}(A) \text{ AND } B \text{ AND } C \text{ OR } A \text{ AND } B \text{ AND NOT } C \text{ OR } A \text{ AND } B \text{ AND } C$

Boolean Expression ← Truth Table

- ❖ But can we do it in reverse?
 - Yes, we can! The method we used is **Boolean function synthesis**
 
$$F(A, B, C) = \text{NOT} ((A \text{ OR } B) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Lecture Pre-reading Q&A

- ❖ What questions did you jot down from today's reading?
- ❖ What's something interesting that you learned?
Something that surprised you?

Lecture Outline

- ❖ Study Environment Discussion
- ❖ Reading Overview and Q&A
- ❖ **Hardware Design Language**
- ❖ Project 1
 - Overview & Example: XOR
 - Demo
 - Group work

Hardware Design Language

- ❖ A programming language to specify hardware components and how they're connected
 - Yet another way of writing a Boolean function
- ❖ Many Hardware Design Languages in use today
 - E.g., VHDL, Verilog, SystemVerilog
 - In this course, we'll use a simple HDL language called "HDL"
- ❖ Unlike Java, HDL is a **declarative** language
 - The order of statements doesn't matter
 - Describes a physical system

Hardware Design Language (cont'd)

❖ Makeup of a HDL file

- File comment describes expected behavior
- **IN** names chip inputs, **OUT** names chip outputs
- **PARTS** specify the components that implement the chip
 - For Project 1, this will mostly be specifying Boolean functions

```
/**
 * And gate:
 * out = 1 only if both a and b are 1
 */
CHIP And {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Reusing Components

- ❖ You can use chips you have already implemented to implement subsequent chips
- ❖ We give you one gate, **Nand**, to start out with
 - Implication: Your entire computer essentially built on **Nand** gates
- ❖ We also give you some chips you can use without implementing
 - See project specification for more details


HDL Component Example: AND

- ❖ The chip specification tells us the name of the input and output wires

```
CHIP And {  
    IN a, b;  
    OUT out;  
  
    ...  
}
```

- ❖ Goal: Implement $w1$ AND $w2$

 - HDL Syntax: `And (a=w1, b=w2, out=w3);`
- Equivalent circuit diagram:



Multi-bit Buses in HDL

- ❖ It can be useful to manipulate groups of wires
 - Called a “bus” of wires
- ❖ HDL provides array like syntax for manipulating buses
 - **And4** chip example:

```
/**
 * Bit-wise And of two 4-bit inputs
 */
CHIP And4 {
    IN a[4], b[4];
    OUT out[4];

    PARTS:
    And (a=a[0], b=b[0], out=out[0]);
    And (a=a[1], b=b[1], out=out[1]);
    And (a=a[2], b=b[2], out=out[2]);
    And (a=a[3], b=b[3], out=out[3]);
}
```

HDL Resources

- ❖ HDL will feel unfamiliar at first, and that's okay
- ❖ Some resources for helping you navigate HDL (these are all linked under the [Resources page](#) on the course website)
 - HDL Survival guide
 - Appendix A (HDL Spec)
 - Chip Set Overview (to help you remember the inputs/outputs for various chips)
 - Chapter readings

Lecture Outline

- ❖ Study Environment Discussion
- ❖ Reading Overview and Q&A
- ❖ Hardware Design Language
- ❖ **Project 1**
 - **Overview & Example: XOR**
 - **Demo**
 - **Group work**

Project 1 Overview

- ❖ Part I: Study Skills Inventory
 - Self-assessing your skill level in various study practices and habits
- ❖ Part II: Boolean Logic
 - Clone your GitLab repository, write and test your code
- ❖ Part III: Social Computing Reflection
 - Opportunity to consider how hardware connects to society
- ❖ Part IV: Project 1 Reflection
 - Reflect on your experience working through Project 1
- ❖ **Due next Thursday (1/13) at 11:59 PM PST**

Project 1 Overview (cont'd)

- ❖ It all starts with the NAND gate
- ❖ NAND is short for “Negated And”
 - The same output as the AND gate, but every output bit is negated (flipped)

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

$$F = A \text{ NAND } B$$

Project 1 Overview (cont'd)

- ❖ Turns out every logic gate in our computer can be implemented in terms of **Nand**
- ❖ We provide you only **Nand** to start Project 1
- ❖ You will build other basic gates (**Not**, **And**, etc.) in terms of **Nand** and then increasingly complex gates in terms of other gates you implement
- ❖ Will culminate in the building of a computer entirely based on **Nand** gates

Building gates out of Nand

- ❖ Recall the Boolean synthesis strategy from the reading
 - Represent any truth table or Boolean function in terms of three gates: **Not**, **And**, **Or**

- ❖ First, we can represent **Not** directly from **Nand**
 - $\text{Not } a = a \text{ Nand } a$

Building gates out of Nand

- ❖ Recall the Boolean synthesis strategy from the reading
 - Represent any truth table or Boolean function in terms of three gates: **Not**, **And**, **Or**
- ❖ First, we can represent **Not** directly from **Nand**
 - $\text{Not } a = a \text{ Nand } a$
- ❖ Represent **And** in terms of **Not** and **Nand**
 - $a \text{ And } b = \text{Not}(a \text{ Nand } b)$

Building gates out of Nand

- ❖ Recall the Boolean synthesis strategy from the reading
 - Represent any truth table or Boolean function in terms of three gates: **Not**, **And**, **Or**
- ❖ First, we can represent **Not** directly from **Nand**
 - $\text{Not } a = a \text{ Nand } a$
- ❖ Represent **And** in terms of **Not** and **Nand**
 - $a \text{ And } b = \text{Not}(a \text{ Nand } b)$
- ❖ Represent **Or** in terms of **Not** and **And**
 - Apply De Morgan's Law
 - $a \text{ Or } b = \text{Not}(\text{Not}(a) \text{ And } \text{Not}(b))$ [De Morgan's Law]

Project 1 Example: Xor

- ❖ Let's walkthrough an example of what you'll do in Project 1
- ❖ Together, we'll implement the **Xor** gate

```
/**
 * Xor gate:
 * out = not(a == b)
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```


Project 1 Example: Xor (cont'd)

❖ Plan:

- Generate truth table
- Use truth table to generate Boolean function
- Convert Boolean function to HDL syntax

```
/**
 * Xor gate:
 * out = not(a == b)
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Project 1 Example: Xor (cont'd)

- ❖ Step 1: Build a truth table
 - Interpret the specification: $F = \text{NOT}(A == B)$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

$$F = A \text{ XOR } B$$

Project 1 Example: Xor (cont'd)

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the Boolean function synthesis strategy from the reading

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Project 1 Example: Xor (cont'd)

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the Boolean function synthesis strategy from the reading
 - Row 2 = NOT(A) AND B

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Project 1 Example: Xor (cont'd)

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the Boolean function synthesis strategy from the reading
 - Row 2 = NOT(A) AND B
 - Row 3 = A AND NOT(B)
 - $F = ?$

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$



Vote at <https://pollev.com/ericfan524>

❖ What is the unsimplified Boolean expression result from performing Boolean function synthesis on $F = A \text{ XOR } B$?

A. $(A \text{ AND NOT}(B)) \text{ AND } (\text{NOT}(A) \text{ AND } B)$

B. $\text{NOT}(A) \text{ AND } B) \text{ AND } (A \text{ AND NOT}(B))$

C. $(A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND NOT}(B))$

D. $(\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND NOT}(B))$

E. **We're lost...**

- Row 2 = $\text{NOT}(A) \text{ AND } B$
- Row 3 = $A \text{ AND NOT}(B)$

A	B	F = A XOR B	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

Project 1 Example: Xor (cont'd)

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the Boolean function synthesis strategy from the reading
 - Row 2 = NOT(A) AND B
 - Row 3 = A AND NOT(B)
 - A XOR B = Row 2 OR Row 3

$$= (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND NOT}(B))$$


A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Project 1 Example: Xor (cont'd)

- ❖ Sometimes helpful to convert a Boolean expression to a circuit diagram
 
$$A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$$



Project 1 Example: Xor (cont'd)


- ❖ Step 3: Convert Boolean function to HDL syntax
 - $A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$
 - Assumes **Not**, **And**, and **Or** are already implemented
 - Note the use of intermediary wires: **nota**, **notb**, **x**, and **y**

```
CHIP Xor {  
  IN a, b;  
  OUT out;
```

PARTS:

```
Not (in=a, out=nota);  
Not (in=b, out=notb);  
And (a=a, b=notb, out=x);  
And (a=nota, b=b, out=y);  
Or (a=x, b=y, out=out);
```

```
}
```

 

Project 1 Demo

- ❖ Brief demo of the tools you will use in Project 1
- ❖ Today's goal: Open and tinker with all the tools
- ❖ Stretch goal: Implement the first gate in project 1, **Not**
 - Interacting with the tools and implementing the gates, will help you become familiar with the interface and address any confusion

Project 1 Group Work

- ❖ Group time to work on the first gate, **Not**, in Project 1

- ❖ Complete the following tasks in groups:
 1. Read the **Overview** section of the spec
 2. Estimate how much time you think it will take to finish Project 1
 3. Clone your GitLab repository (instructions in Project 0)
 4. Open the HardwareSimulator (see instructions in the **Tools** section of the specification)
 5. Dive into it! Implement and test the **Not** gate

Wrapping Up

- ❖ What's in store for Week 2?
 - Technical Subject: Boolean Arithmetic & ALU
 - Metacognitive Subject: Time Management
 - Project 2 released next Thursday (1/13)

- ❖ Reminders
 - Project 0 due **tonight (Thursday, 1/6) at 11:59pm PST**
 - Project 1 released
 - Fill out the first Student-TA meeting scheduling spreadsheet [here](#)
 - First Student-TA 1:1 ongoing through next week

- ❖ CSE 390B meets in-person next week!
 - Gates Center (CSE2) G04