

CSE 390B, Winter 2022

Building Academic Success Through Bottom-Up Computing

The ALU, Growth vs. Fixed Mindset

Growth vs. Fixed Mindset, Goal-setting, Multiplexer, ALU,
Project 2 Overview


If you can, please have your camera turned on!



Lecture Outline

- ❖ **Growth vs. Fixed Mindset**
 - **Setting SMART goals**
- ❖ Reading Review and Q&A
 - Negative Numbers in Binary
- ❖ If/Else Logic In Hardware
 - Multiplexer (Mux) logical gate
- ❖ Arithmetic Logic Unit (ALU) Introduction
 - ALU Functions and Implementation Strategy
- ❖ Project 2 Overview
 - HDL Tips

Growth vs. Fixed Mindset

 

Setting SMART Goals

- ❖ **S** – Be specific, simple and significant.
- ❖ **M** – Make sure your goals are measurable. How many times within a week, month, the quarter do you want to do x goal?
- ❖ **A** – Make sure your goals are achievable. Is your goal within your scope of control?
- ❖ **R** – Be realistic and reasonable.
- ❖ **T** – Be time-bound. When will you accomplish x goal?

Breakout Rooms

WINTER QUARTER GOALS

What are skills, practices or habits that are not strengths YET?

SPHERE OF CONTROL

Getting a 4.0 in a course

VS.

Attending course office hours

SMART GOAL FRAMEWORK

S -- Specific

M -- Measurable

A -- Achievable

R -- Realistic

T -- Timebound

Attending CSE 390B office hours at least 5x this quarter (or once every other week)

Lecture Outline

- ❖ Growth vs. Fixed Mindset
 - Setting SMART goals
- ❖ **Reading Review and Q&A**
 - **Negative Numbers in Binary**
- ❖ If/Else Logic In Hardware
 - Multiplexer (Mux) logical gate
- ❖ Arithmetic Logic Unit (ALU) Introduction
 - ALU Functions and Implementation Strategy
- ❖ Project 2 Overview
 - HDL Tips

Two's Complement

- ❖ One binary interpretation to represent negative values
- ❖ Most significant bit (MSB) has a negative weight
 - Add the remaining bits as usual (with positive weights)
- ❖ Example: 0b1101 in Two's Complement
 - $-(1 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) = -8 + 4 + 0 + 1$
 $= -3$
- ❖ Negation procedure: take bitwise complement and add one
 - $-x = \sim x + 1$
 - Example: Negate $x = 4$

Two's Complement

- ❖ One binary interpretation to represent negative values
- ❖ Most significant bit (MSB) has a negative weight
 - Add the remaining bits as usual (with positive weights)
- ❖ Example: 0b1101 in Two's Complement
 - $-(1 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) = -8 + 4 + 0 + 1$
 $= -3$
- ❖ Negation procedure: take bitwise complement and add one
 - $-x = \sim x + 1$
 - Example: Negate $x = 4$
 - $-4 = \sim 0b0100 + 1 = 0b1011 + 0b1 = 0b1100 = -8 + 4 = -4$

4-bit Values in Various Representations

Binary Value	Unsigned Binary	Signed Binary	Two's Complement
0b0000	0	0	0
0b0001	1	1	1
0b0010	2	2	2
0b0011	3	3	3
0b0100	4	4	4
0b0101	5	5	5
0b0110	6	6	6
0b0111	7	7	7
0b1000	8	-0	-8
0b1001	9	-1	-7
0b1010	10	-2	-6
0b1011	11	-3	-5
0b1100	12	-4	-4
0b1101	13	-5	-3
0b1110	14	-6	-2
0b1111	15	-7	-1

Two's Complement Addition

- ❖ The process for adding binary in Two's Complement is the same as that of unsigned binary

- ❖ Hardware performs the exact same calculations
 - It doesn't need to know the sign of the values, it performs the same calculation
 - The only difference is representation of sum

- ❖ Example: $0b1001 + 0b0010$

- Unsigned interpretation:
- Two's Complement interpretation:

carry				
a	1	0	0	1
b	0	0	1	0
sum				

Two's Complement Addition

- ❖ The same process applies for unsigned and Two's Complement binary addition
- ❖ Hardware performs the exact same calculation
 - It doesn't need to know the sign of the values, it performs the same calculation
 - The only difference is representation of sum

❖ Example: $0b1001 + 0b0010 = 0b1011$

- Unsigned interpretation: $9 + 2 = 11$
- Two's Complement interpretation: $-7 + 2 = -5$

carry				
a	1	0	0	1
b	0	0	1	0
sum	1	0	1	1



Vote at <https://pollev.com/cse390b>

- ❖ **What is something you learned, were surprised by, or had a question about from today's reading?**
- ❖ You can choose to respond anonymously by not adding your name (click "Skip")

Welcome to cse390b's presentation!

Introduce yourself

Enter the screen name you would like to appear alongside your responses.

Name 0 / 50


Continue

Skip



Vote at <https://pollev.com/cse390b>

- ❖ **How are you feeling about Project 1? Questions, concerns, or other thoughts?**
- ❖ You can choose to respond anonymously by not adding your name (click “Skip”)

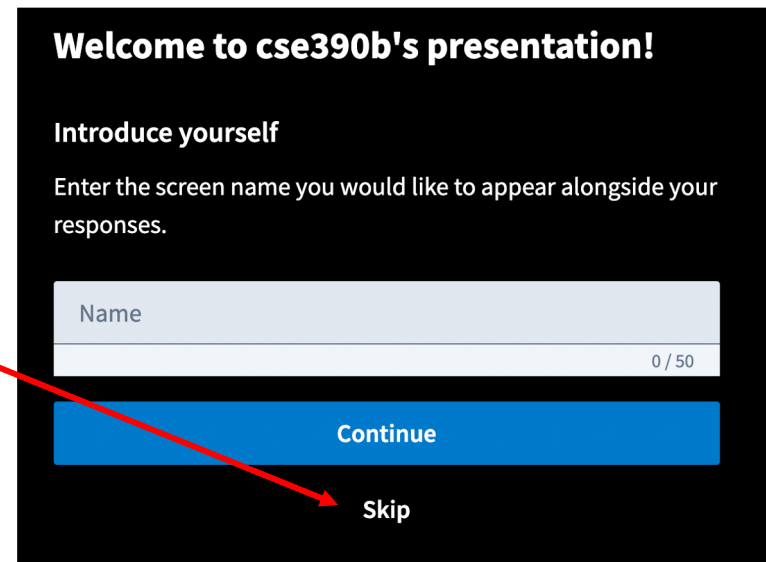A screenshot of the Poll Everywhere interface. The background is black. At the top, it says "Welcome to cse390b's presentation!". Below that, it says "Introduce yourself" and "Enter the screen name you would like to appear alongside your responses." There is a text input field with the placeholder "Name" and a character count "0 / 50" on the right. Below the input field are two buttons: a blue "Continue" button and a white "Skip" button. A red arrow points from the "Skip" button in the screenshot to the text "click 'Skip'" in the list item above.

Lecture Outline

- ❖ Growth vs. Fixed Mindset
 - Setting SMART goals
- ❖ Reading Review and Q&A
 - Negative Numbers in Binary
- ❖ **If/Else Logic In Hardware**
 - **Multiplexer (Mux) logical gate**
- ❖ Arithmetic Logic Unit (ALU) Introduction
 - ALU Functions and Implementation Strategy
- ❖ Project 2 Overview
 - HDL Tips


If/Else Decisions In Hardware

- ❖ We write if/else statements in Java with the understanding that only one of the branches will run
 - For example, in the following code, we expect to compute one of $a \ \& \ b$ or $a \ | \ b$ (not both)

```
if (c == 0) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

If/Else Decisions In Hardware

 - ❖ In hardware, all circuits are always executing
 - We can't "turn off" a circuit based on a condition
- ❖ We create circuits for different conditions and choose which output based on a condition instead
- ❖ We use Multiplexer (Mux) gates to choose which singular input to output



Mux Gate Implementation Example


- ❖ Example of converting pseudocode into a hardware circuit diagram:

```
if (c == 0) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

Mux Gate Implementation Example

- ❖ Example of converting pseudocode into a hardware circuit diagram:

```
if (c == 0) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

 

Mux Gate Practice Problem #1


- ❖ Draw out the hardware circuit diagram that corresponds to the following pseudocode:

```
if (c == 0) {  
    out = ~a | ~b;  
} else {  
    out = a | b;  
}
```

Mux Gate Practice Problem #1

- ❖ Draw out the hardware circuit diagram that corresponds to the following pseudocode:

```
if (c == 0) {  
    out = ~a | ~b;  
} else {  
    out = a | b;  
}
```

 

Mux Gate Practice Problem #2


- ❖ Draw out the hardware circuit diagram that corresponds to the following pseudocode:

```
if (a == b) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

Mux Gate Practice Problem #2

- ❖ Draw out the hardware circuit diagram that corresponds to the following pseudocode:


```
if (a == b) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```

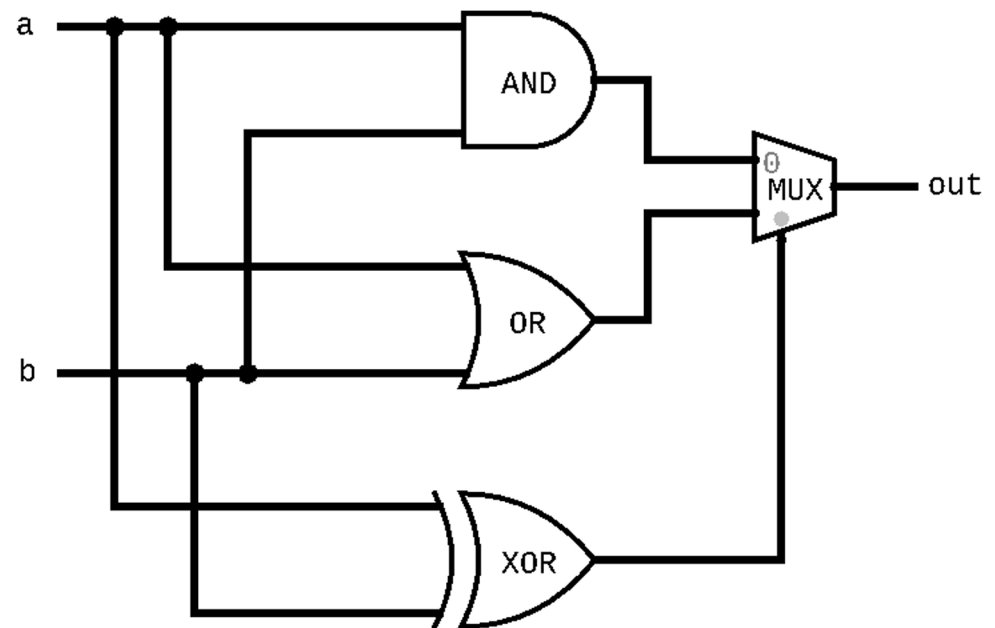

Lecture Outline

- ❖ Growth vs. Fixed Mindset
 - Setting SMART goals
- ❖ Reading Review and Q&A
 - Negative Numbers in Binary
- ❖ If/Else Logic In Hardware
 - Multiplexer (Mux) logical gate
- ❖ **Arithmetic Logic Unit (ALU) Introduction**
 - **ALU Functions and Implementation Strategy**
- ❖ Project 2 Overview
 - HDL Tips


The Von Neumann Architecture

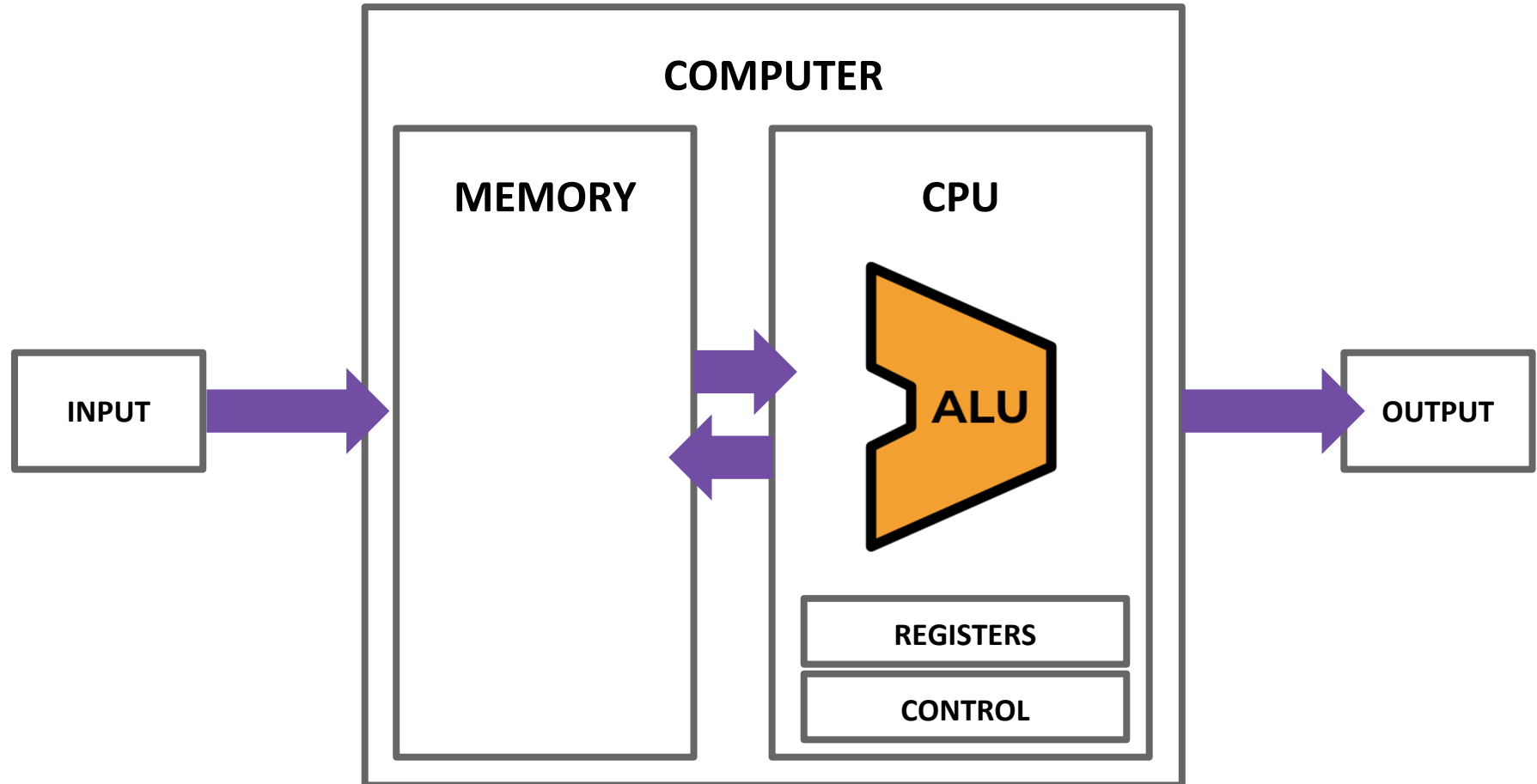

(This picture will get more detailed as we go!)

The Arithmetic Logic Unit

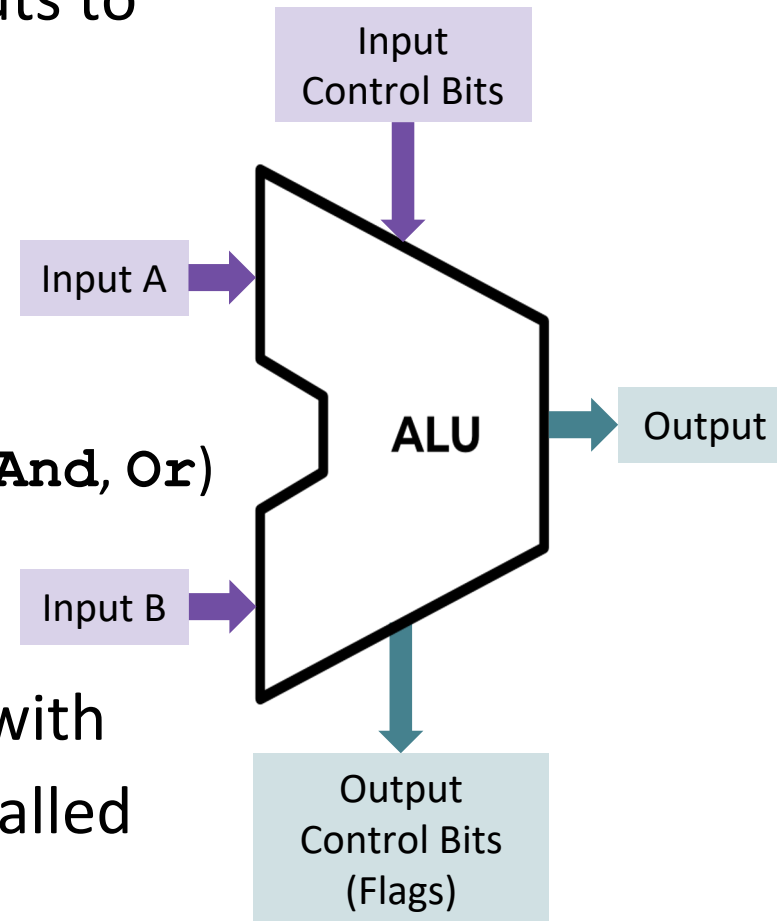- ❖ Computes a function on two inputs to produce an output
- ❖ Input Control Bits specific which function should be computed
 - Supports a combination of logical (**And, Or**) and arithmetic operations (+, -)
- ❖ Indicate properties of the result with Output Control Bits (commonly called Flags)



Our ALU Implementation

❖ Inputs & Output


- 16-bit inputs **x** and **y** and output **out**
- Interpret in Two's Complement

❖ Input Control Bits

- 6 control bits (**zx**, **nx**, **zy**, **ny**, **f**, **no**) specify which function to compute
- $2^6 = 64$ different possible functions to choose from (only 18 of interest)

❖ Output Control Bits (Flags)

 - 2 bits (**zr** and **ng**) describing the properties of the output



ALU Functions: “Black Box” View

- ❖ We support 18 different functions of interest
 - 3 that simply give constant values (ignoring operands)
 - 10 that change a single input, possibly with a constant
 - 5 that perform an operation using both inputs

- ❖ To select a function, set the control bits to the corresponding combination


zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

ALU Functions: Implementer's View


- ❖ Example: Compute $x - 1$
 - Given inputs $x=0101$ (5), $y=0010$ (2)

zx	nx	zy	ny	f	no	out
...						...
0	0	1	1	1	0	$x-1$
...						...


1
PREPROCESS
INPUTS

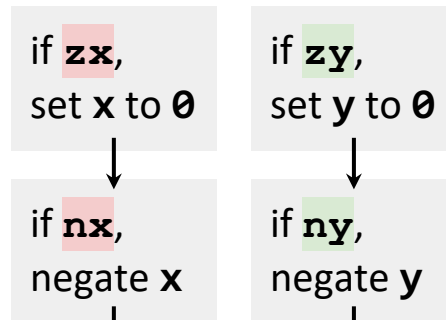

2
COMPUTE

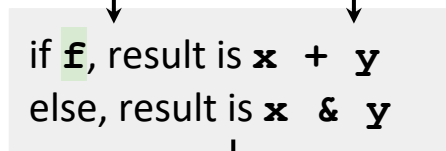

3
POSTPROCESS
OUTPUT

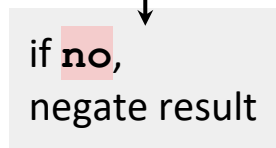

$x=0101$ (5)
Unchanged

$y=0000$ (0)
Zeroed

$x=0101$ (5)
Unchanged

$y=1111$ (-1)
Negated

$out=0100$ (4)
 $x(5) + y(-1)$

$out=0100$ (4)
Unchanged



Vote at <https://pollev.com/cse390b>

❖ Given inputs $x=0b1010$ and $y=0b0110$ and the following input control bits, what is the resulting output and output control bits?

- A. $out=0b1010$, $zr=0$, $ng=1$
- B. $out=0b0111$, $zr=0$, $ng=0$
- C. $out=0b1001$, $zr=1$, $ng=0$
- D. $out=0b1100$, $zr=1$, $ng=1$
- E. We're lost...

zx	nx	zy	ny	f	no
...					
0	1	1	1	0	1
...					

IN

```
x[16], y[16], // 16-bit inputs
zx, // zero the x input?
nx, // negate the x input?
zy, // zero the y input?
ny, // negate the y input?
f, // compute out = x + y
    if 1 or x & y (if 0)
no; // negate the out output?
```

OUT


```
out[16], // 16-bit output
zr, // 1 if (out == 0),
    0 otherwise
ng; // 1 if (out < 0),
    0 otherwise
```

ALU Output Control Bits

- ❖ **zr** is 1 if $\text{out} == 0$
- ❖ **ng** is 1 if $\text{out} < 0$

- ❖ We'll use these in a later project
 - The basis of **comparison**
 - To evaluate if $\mathbf{x} == 4$, compute $\mathbf{x} - 4$ and check **zr** flag

 - ❖ These are deceptively difficult to implement
 - Start early on Project 2



ALU Implementation Strategy

- ❖ We suggest implement the ALU in three steps
- ❖ First, handle zeroing out and negating inputs **x** and **y** and negating the output
 - Ignore the **z** bit (only compute **And**) and ignore flag outputs
 - Test your implementation using `ALU-nostat-noadd.tst`
- ❖ Next, implement the **And** and **Add** operations using **f**
 - Test your implementation using `ALU-nostat.tst`
- ❖ Lastly, implement the logic for the status flags (**zr** and **ng**)
 - Test your full ALU using `ALU.tst`

Lecture Outline

- ❖ Growth vs. Fixed Mindset
 - Setting SMART goals
- ❖ Reading Review and Q&A
 - Negative Numbers in Binary
- ❖ If/Else Logic In Hardware
 - Multiplexer (Mux) logical gate
- ❖ Arithmetic Logic Unit (ALU) Introduction
 - ALU Functions and Implementation Strategy
- ❖ **Project 2 Overview**
 - **HDL Tips**

Project 2 Overview


- ❖ Part I: 24-Hour Time Audit

- ❖ Part II: Boolean Arithmetic
 - Goal: Implement the ALU, which performs the core computations we need (+ and &)
 - First, implement `HalfAdder.hdl`, `FullAdder.hdl`, and `Add16.hdl`
 - Then, implement the ALU in the order suggested by the specification
 - Chapter 2 of the textbook has more details on the adders and ALU

- ❖ Part III: Social Computing Reflection
 - Application of Boolean Arithmetic: Buffer Overflow

HDL Tips: Slicing

 - ❖ Sometimes want to connect only part of a multi-bit bus
- ❖ HDL lets us with **slicing notation**
- ❖ Example: **ChipA** has eight output pins, and we want to connect the first four to **ChipB**'s four inputs:




```
ChipA (out[0..3]=w1);  
ChipB (in=w1);
```

- ❖ Note: We can only slice chip connections, not internal wires (e.g., `w1[0..3]` is not allowed)
 - If we need to use half an 8-bit wire, make two 4-bit wires and slice the output they're connected to

HDL Tips: Connections

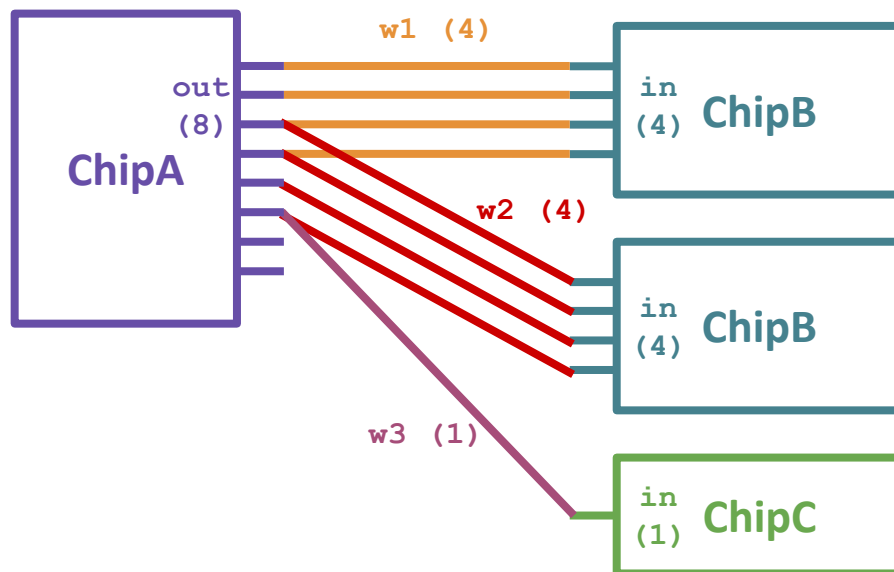
- ❖ Can connect a chip output multiple times, or not at all!
 - Hint: In `Add16.hdl`, do we need to use the last carry bit?



```
ChipA (out[0..3]=w1,  
      out[2..5]=w2,  
      out[5]=w3);  
ChipB (in=w1);  
ChipB (in=w2);  
ChipC (in=w3);
```

HDL Tips: Constants

 - ❖ A bus of true or false contain all 1s or all 0s, respectively, and implicitly act as whatever width is needed
- ❖ Example: **ChipB** has four inputs and **ChipC** has one input
 - **ChipB** (**in=true**) assigns all 4 inputs the value of 1 (true)
 - **ChipC** (**in=true**) assigns the one input the value of 1 (true)
 - **ChipC** (**in=false**) assigns the one input the value of 0 (false)



```
ChipB (in=true);  
ChipC (in=true);  
ChipC (in=false);
```

Post-Lecture 4 Reminders

- ❖ What's in store for Week 3?
 - Technical Subject: Sequential Logic & Building Memory
 - Metacognitive Subject: Note-taking Practices
 - Project 3 released next Thursday (1/20)

- ❖ Reminders
 - Project 1 due **tonight (Thursday, 1/13) 11:59PM PST**
 - Project 2 (Boolean Arithmetic and 24-Hour Time Audit) is released
 - Join the Discord channel!