

CSE 390B, Winter 2022

Building Academic Success Through Bottom-Up Computing

Memory, Cornell Note-Taking Method

Revisiting the Cornell Note-Taking Method, Building Memory

Lecture Outline

- ❖ **Cornell Note-Taking Review**
 - **Group discussion: Compare and contrast notes**
- ❖ **Storing Data: Bit**
 - Bit overview and implementation
- ❖ **Reading Review: Memory Representation**
 - Array abstraction, reading and writing memory
- ❖ **Building Memory: Registers**
 - Building up from Bit to Register, then from Register to RAM
- ❖ **Program Counter (PC) Overview**
 - How do we keep track of which instruction to execute?

Cornell Note-Taking Discussion


- ❖ In small groups, compare and contrast your Cornell Notes from Tuesday's lecture
 - What are some of the key points you wrote in your summary?
 - What were some of the questions you came up with?
 - What are you still left feeling confused/uncertain about after Tuesday's lecture?

Lecture Outline

- ❖ Cornell Note-Taking Review
 - Group discussion: Compare and contrast notes
- ❖ **Storing Data: Bit**
 - **Bit overview and implementation**
- ❖ Reading Review: Memory Representation
 - Array abstraction, reading and writing memory
- ❖ Building Memory: Registers
 - Building up from Bit to Register, then from Register to RAM
- ❖ Program Counter (PC) Overview
 - How do we keep track of which instruction to execute?


Computer Overview

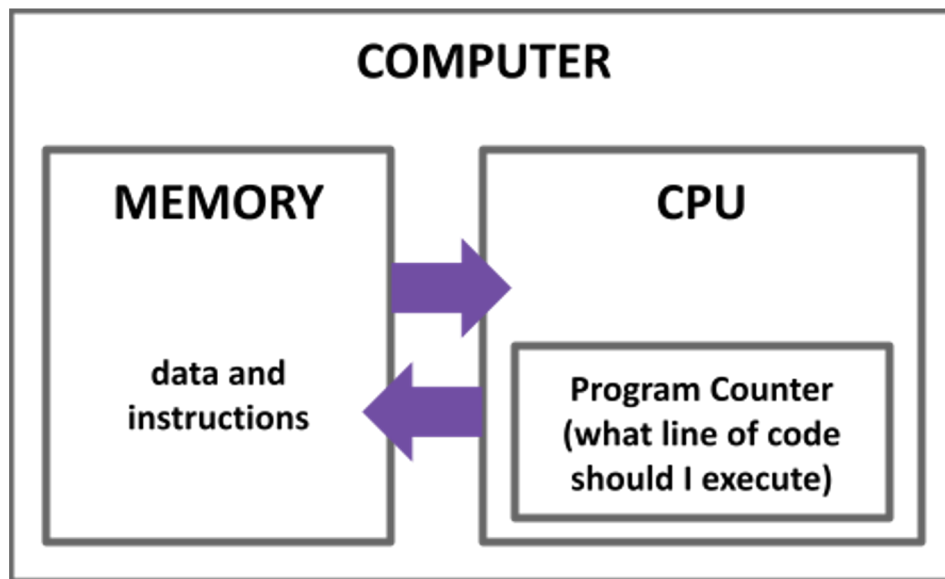- ❖ CPU is the “brain” of our computer
 - Does necessary computations (add, subtract, multiply, etc.)
- ❖ Memory is used to store values for later use
 - Requires persistence across multiple computations
 - Needs to change values at our discretion




Storing Data: Bit

 - ❖ A Flip-Flop changes state *every* clock cycle
- ❖ We will build the abstraction of a “Bit” that only changes when we instruct it to




```
if load(t-1)    out(t) = in(t-1)
else            out(t) = out(t-1)
```

Bit Behavior

 


```
if load(t-1)
else
```
 
```
out(t) = in(t-1)
out(t) = out(t-1)
```




Bit Behavior

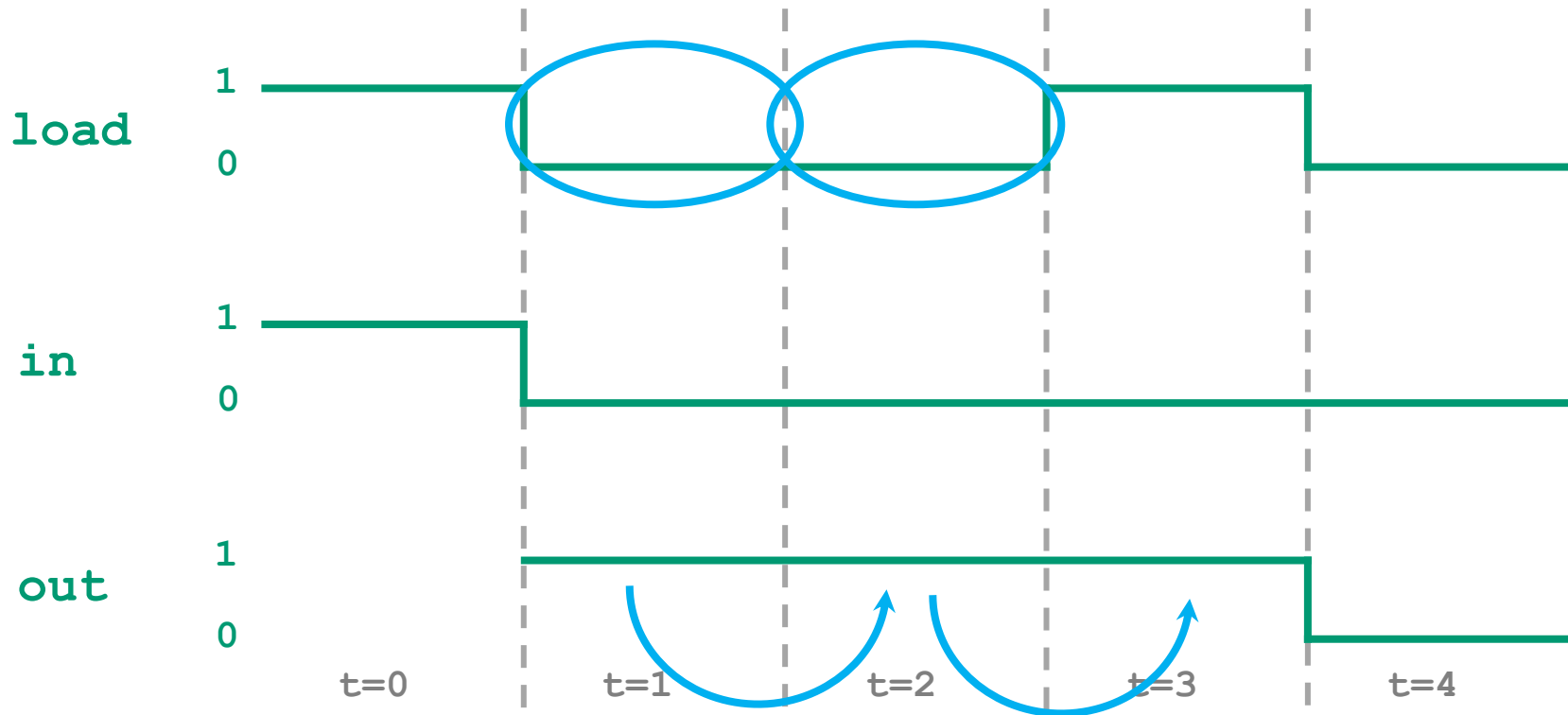

```
if load(t-1)
else
```
 
```
out(t) = in(t-1)
out(t) = out(t-1)
```



Bit Time Series

❖ Bit Specification:

if $\text{load}(t-1)$: $\text{out}(t) = \text{in}(t-1)$
 else: $\text{out}(t) = \text{out}(t-1)$

load	1	0	0	1	1	1	0	...
in	1	0	0	0	1	0	1	...
out	0	1	1	1	0	1	0	...
time	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

Example 1: $\text{load}(t=0) == 1$ so $\text{out}(t=1) = \text{in}(t=0)$

Example 2: $\text{load}(t=2) == 0$ so $\text{out}(t=3) = \text{out}(t=2)$



Vote at <https://pollev.com/cse390b>

❖ What gates will we need to implement a Bit? Select all that apply.


A. Mux

B. Xor

C. And

D. DFF

E. We're lost...

 

```
if load(t-1)
else
```

```
out(t) = in(t-1)
out(t) = out(t-1)
```

Implementing a Bit


- ❖ Bit Specification:

<code>if load(t-1)</code>	<code>out(t) = in(t-1)</code>
<code>else</code>	<code>out(t) = out(t-1)</code>
- ❖ Exercise: Fill in the connections to the gates to create a circuit diagram of Bit
 - May be helpful to review slides on [Mux](#) and [sequential circuits](#)

Implementing a Bit

- ❖ Bit Specification:

<code>if load(t-1)</code>	<code>out(t) = in(t-1)</code>
<code>else</code>	<code>out(t) = out(t-1)</code>
- ❖ Exercise: Fill in the connections to the gates to create a circuit diagram of Bit
 - May be helpful to review slides on [Mux](#) and [sequential circuits](#)

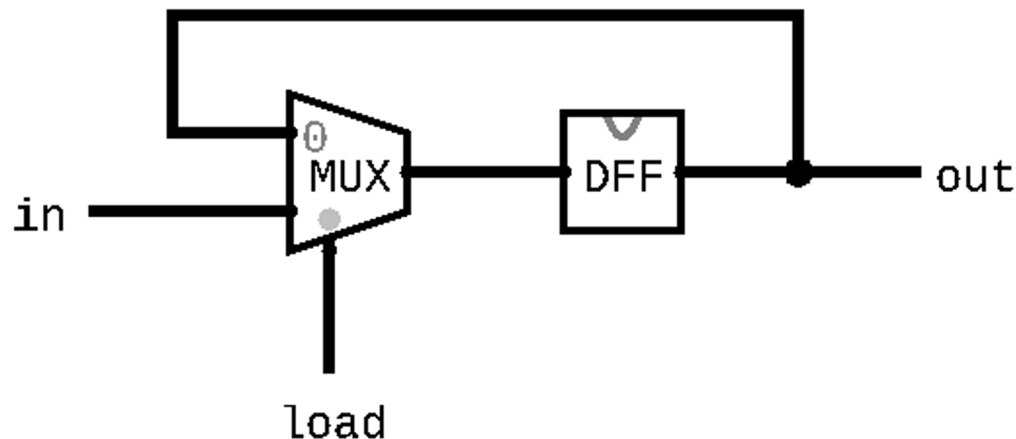

Lecture Outline

- ❖ Cornell Note-Taking Review
 - Group discussion: Compare and contrast notes
- ❖ Storing Data: Bit
 - Bit overview and implementation
- ❖ **Reading Review: Memory Representation**
 - **Array abstraction, reading and writing memory**
- ❖ Building Memory: Registers
 - Building up from Bit to Register, then from Register to RAM
- ❖ Program Counter (PC) Overview
 - How do we keep track of which instruction to execute?

Reading Review: Memory Representation

- ❖ Memory can be abstracted as one huge array
- ❖ Addresses are indices into different memory slots
 - The width of an address is fixed for the system
 - The Nand2Tetris project will use 16-bit addresses
- ❖ Each slot in memory takes up a fixed width
 - Not the same as address width
 - The Nand2Tetris project uses 16-bit slots in memory

Reading Review: Memory Representation

- ❖ Can read and write to memory by specifying an address
 - More details next week
- ❖ Example: $\mathbf{x} = \mathbf{memory}[01\dots00]$
 - Reads the value in memory at address $01\dots00$ and stores it in \mathbf{x}
- ❖ Example: $\mathbf{memory}[01\dots00] = 7$
 - Writes the value 7 in the memory slot at address $01\dots00$

Lecture Outline

- ❖ Cornell Note-Taking Review
 - Group discussion: Compare and contrast notes
- ❖ Storing Data: Bit
 - Bit overview and implementation
- ❖ Reading Review: Memory Representation
 - Array abstraction, reading and writing memory
- ❖ **Building Memory: Registers**
 - **Building up from Bit to Register, then from Register to RAM**
- ❖ Program Counter (PC) Overview
 - How do we keep track of which instruction to execute?

Building Memory: Register

- ❖ Bits store a single value (0 or 1)
 - In memory, we need to store 16-bit values
- ❖ Registers are conceptually the same as a Bit
 - Allows us to store and change 16-bit values
 - Groups together 16 individual bits that share a load signal

```
// if (load(t-1)): out(t) = in(t-1)
//                else: out(t) = out(t-1)
```

```
CHIP Register {
    IN in[16], load;
    OUT out[16];
    ...
}
```

RAM: Random Access Memory

- ❖ Abstraction of Computer Memory: just a giant array
- ❖ Goal: Create hardware that can provide that abstraction

	24	25	26	27	28	29	30	31	
	11000	11001	11010	11011	11100	11101	11110	11111	
...	0	0	-1	25	124	0	9	-15	...
	0000000	0000000	1111111	0011001	1111100	0000000	0001001	1110001	


- ❖ Key attribute of arrays: “random access” lets us index into them at any point

```
memory[26] = -1;
```

Building Memory: RAM8 From Registers

❖ RAM interface:

 - **address:** address used to specify memory slot
- **in:** 16-bit input used to update specified memory slot if load is 1
- **load:** if 1, then in should be written to specified memory slot
- **out:** 16-bit output from the slot specified by address



❖ RAM8 can be built from 8 registers

- address width is $\log_2(8) = 3$ bits


Building Memory: RAM8 From Registers

❖ Step 1: Route **in** to every register

- We don't want to update every register, however
- Solution: choose which register to enable with **address**

❖ Step 2: Choose which register to use for the output

 - ❖ When we think about making *choices* in hardware, we want to think about Mux and Dmux



Building Memory: The rest of RAM


- ❖ After RAM8, can build larger RAM chips from a combination of smaller RAM chips
 - For example, RAM64 can be built using eight RAM8 chips
- ❖ Technique is similar to RAM8 but will have to use different portions of the address
- ❖ The blocks section of the reading will be helpful
 - For example, can think of each RAM8 as a block of RAM64

Lecture Outline

- ❖ Cornell Note-Taking Review
 - Group discussion: Compare and contrast notes
- ❖ Storing Data: Bit
 - Bit overview and implementation
- ❖ Reading Review: Memory Representation
 - Array abstraction, reading and writing memory
- ❖ Building Memory: Registers
 - Building up from Bit to Register, then from Register to RAM
- ❖ **Program Counter (PC) Overview**
 - **How do we keep track of which instruction to execute?**

Program Counter (PC)

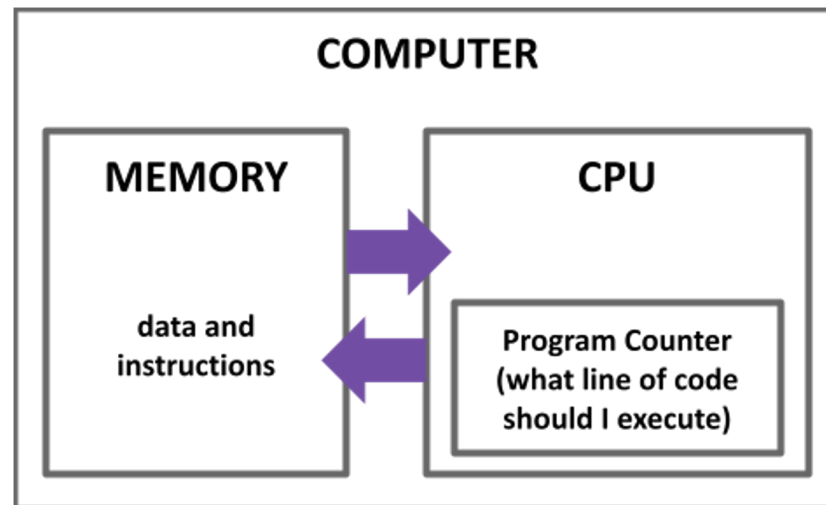
- ❖ Memory is used to store data as well as code
- ❖ Instructions and operations are stored at different addresses in memory
- ❖ Program Counter in the CPU keeps track of which address contains the instruction that should be executed next



Program Counter (PC)

- ❖ Keeps track of what instruction we are executing
 - If the PC outputs 24, on the next clock cycle the computer runs the instruction at address 24 in the code segment
- ❖ Program counter specification:
 
```
if      (reset[t] == 1) out[t+1] = 0
else if (load[t]  == 1) out[t+1] = in[t]
else if (inc[t]  == 1) out[t+1] = out[t] + 1
else                                     out[t+1] = out[t]
```



Project 3 Overview

- ❖ Part I: Cornell Note-Taking Method
 - Practice taking detailed notes in another class
 - Think critically about the technique

- ❖ Part II: Memory
 - Memory & Sequential Logic: Build our first sequential chips, from a 1-bit register to a 16K RAM module
 - Program Counter: Build counter that tracks where we are in a program, with support for several operations we'll need later
 - *Note: Folder split for performance reasons only*

- ❖ Part III: Social Computing Reflection
 - Applications of Memory and Sequential Logic

Post-Lecture 6 Reminders

❖ Reminders

- Project 1 grades and feedback released on Gradescope
- Project 2 due tonight (2/20) at 11:59PM PST
- Eric has office hours after lecture today from 3-4pm

❖ Starting next week, Eric's office hours on Thursday from 3-4pm will be on Wednesdays from 4:30-5:30pm

❖ What's in store for Week 4?

- Technical Subject: Machine and Assembly Languages
- Metacognitive Subject: Annotation Strategies
- Project 4 (Machine Language, Annotation) released next Thursday