

CSE 390B, Winter 2022

Building Academic Success Through Bottom-Up Computing

# Building a Computer, Exam Preparation

Cornell Note-Taking Debrief, Exam Preparation, Building a  
Computer Overview, Hack CPU Logic



Vote at <https://pollev.com/cse390b>

- ❖ **Would you like to keep CSE 390B's original finals time (Friday, March 18th from 2:30-4:30pm) or would you prefer to move it earlier in finals week?**
- ❖ You can choose to respond anonymously by not adding your name (click "Skip")

**Welcome to cse390b's presentation!**

**Introduce yourself**

Enter the screen name you would like to appear alongside your responses.

Name  0 / 50

**Continue**

**Skip**

A red arrow points from the text "click 'Skip'" in the list above to the "Skip" button in the screenshot.

# Lecture Outline

## ❖ Cornell Note-Taking Debrief

- Reflection on notes from CSE 390B and other courses

## ❖ Exam Preparation

- Study strategies, mock exam problem

## ❖ Building a Computer Overview

- Architecture, fetch and execute cycle

## ❖ Hack CPU Logic

- Implementation and operations

# Project 3 Cornell Note-Taking Debrief

- ❖ *Look at your Cornell notes from CSE 390B and from another course that you practiced Cornell note-taking with*
- ❖ What elements of the Cornell note-taking method allowed you to better understand and work on Project 3?
  - How are these elements similar/different when comparing this to your other course?
- ❖ What were barriers that prevented you from fully engaging in the Cornell note-taking method (either in this class or another class)?
  - What are ways that can help address this?

# Lecture Outline

- ❖ Cornell Note-Taking Debrief
  - Reflection on notes from CSE 390B and other courses
- ❖ **Exam Preparation**
  - **Study strategies, mock exam problem**
- ❖ Building a Computer Overview
  - Architecture, fetch and execute cycle
- ❖ Hack CPU Logic
  - Implementation and operations

# Gearing up for your exams...

## ❖ Make a Study Plan

- What key topics/concepts does your exam cover?
- How might your study guides look different for specific classes?
- What resources, materials, or people might you need to engage with?

## ❖ Create a Schedule

- DON'T CRAM
- Office hours, review sessions, study groups
- Reference your weekly time commitments & quarterly calendar

## ❖ Test Yourself

- Utilize your Cornell question notes
- Replicate exam-like environments



# Gearing up for your exams...

## ❖ Make a Study Plan

- What key topics/concepts does your exam cover?
- How might your study guides look different for specific classes?
- What resources, materials, or people might you need to engage with?

## ❖ Create a Schedule

- DON'T CRAM
- Office hours, review sessions, study groups
- Reference your weekly time commitments & quarterly calendar

## ❖ Test Yourself

- Utilize your Cornell question notes
- **Replicate exam-like environments**



# Project 5: Timed Mock Exam Problem

- ❖ Schedule a 30-minute session is based on your group members availability do one mock exam problem
- ❖ Determine how you will get in touch with each other if needed
- ❖ Determine where your session will be located
- ❖ Post your group's meeting day & time to the Ed Board no later than Thursday



# Project 5: Timed Mock Exam Problem

- ❖ Schedule a 30-minute session is based on your group members availability do one mock exam problem
- ❖ Determine how you will get in touch with each other if needed
- ❖ Determine where your session will be located
- ❖ Post your group's meeting day & time to the Ed Board no later than Thursday

## PROJECT 5 GROUP ASSIGNMENTS

-

### GROUP A:

Eman, Hermona, & Kedist

### GROUP B:

Sulaiman & Vasu

### GROUP C:

Aynur & Preston


# Lecture Outline

- ❖ Cornell Note-Taking Debrief
  - Reflection on notes from CSE 390B and other courses
- ❖ Exam Preparation
  - Study strategies, mock exam problem
- ❖ **Building a Computer Overview**
  - **Architecture, fetch and execute cycle**
- ❖ Hack CPU Logic
  - Implementation and operations


# Building a Computer

- ❖ Perspective: **BUILDING A COMPUTER**
- ❖ All your hardware efforts are about to pay off!
- ❖ In Project 5, you will build `Computer.hdl`—the final, top-level chip in this course
  - For all intents and purposes, a real computer
  - Simplified, but organization very similar to your laptop
- ❖ Project 6 onward, we will write software to make it useful

# Von Neumann Architecture

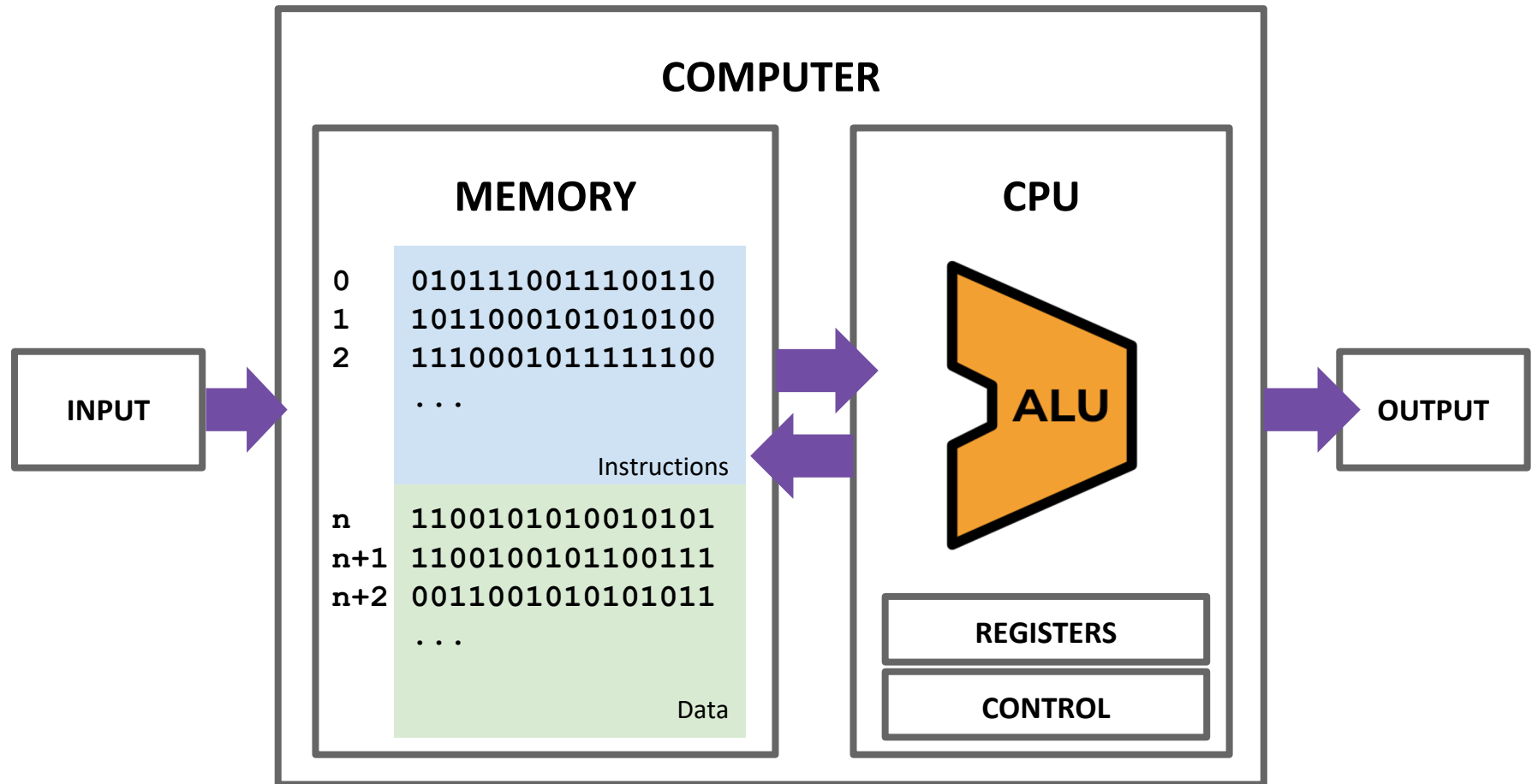

# Connecting the Computer: Buses

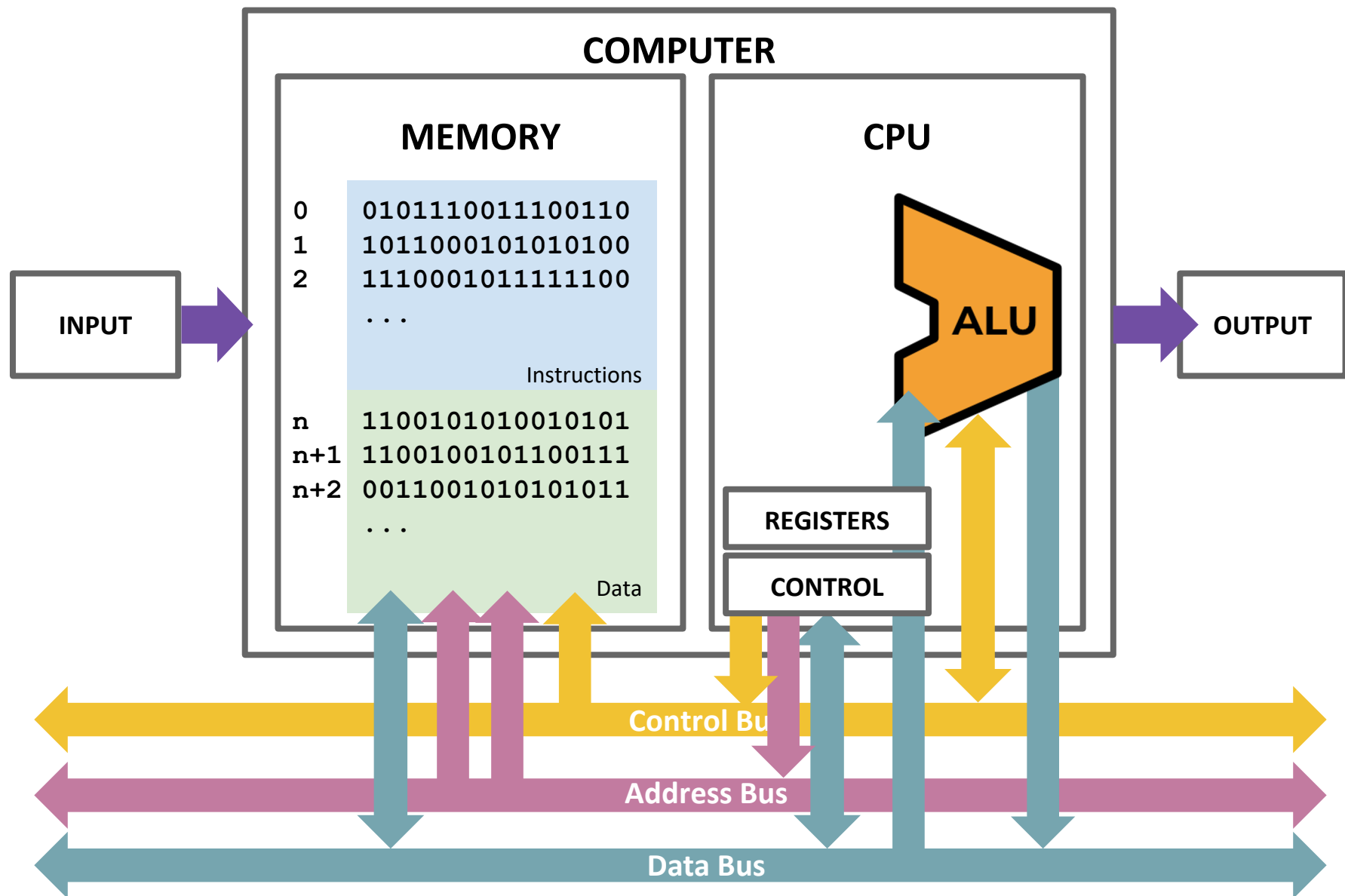


# Basic CPU Loop

- ❖ Repeat forever:
  - **Fetch** an instruction from the program memory
  - **Execute** that instruction
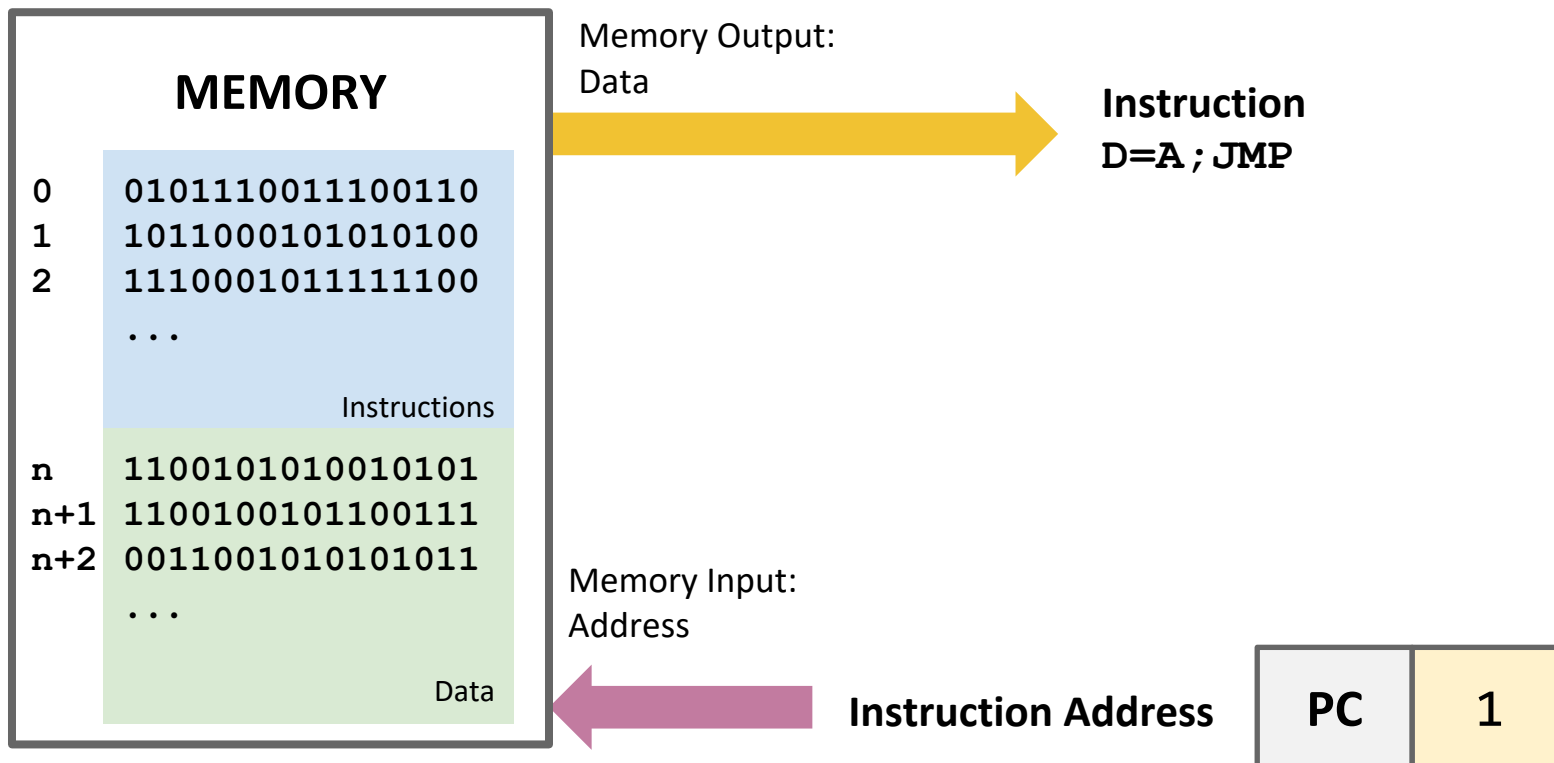
# Fetching

- ❖ Specify which instruction to read as the address input to our memory
- ❖ Data output: actual bits of the instruction




# Executing


- ❖ The instruction bits describe exactly “what to do”
  - A-instruction or C-instruction?
  - Which operation for the ALU?
  - What memory address to read? To write?
  - If I should jump after this instruction, and where?
  
- ❖ Executing the instruction involves data of some kind
  - Accessing registers
  - Accessing memory



# Combining Fetch & Execute

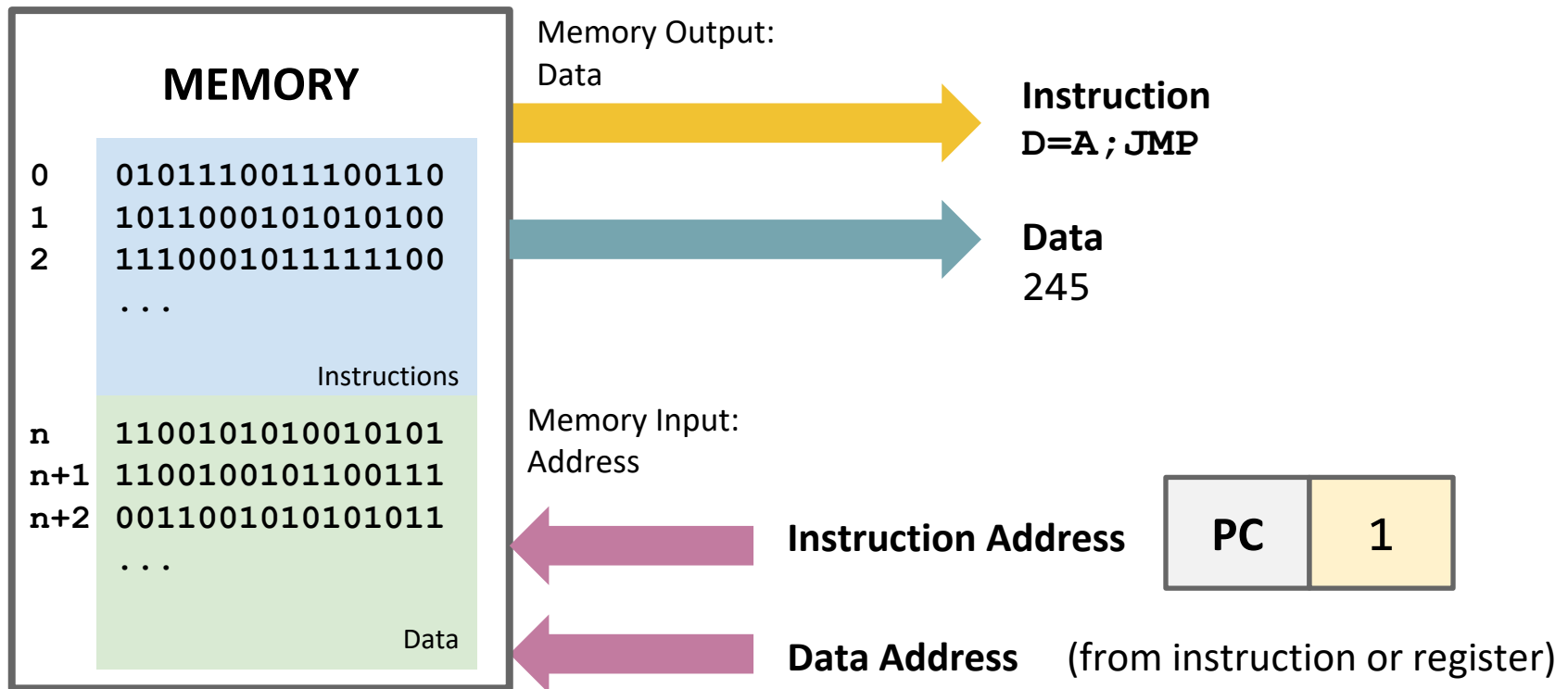


# Combining Fetch & Execute

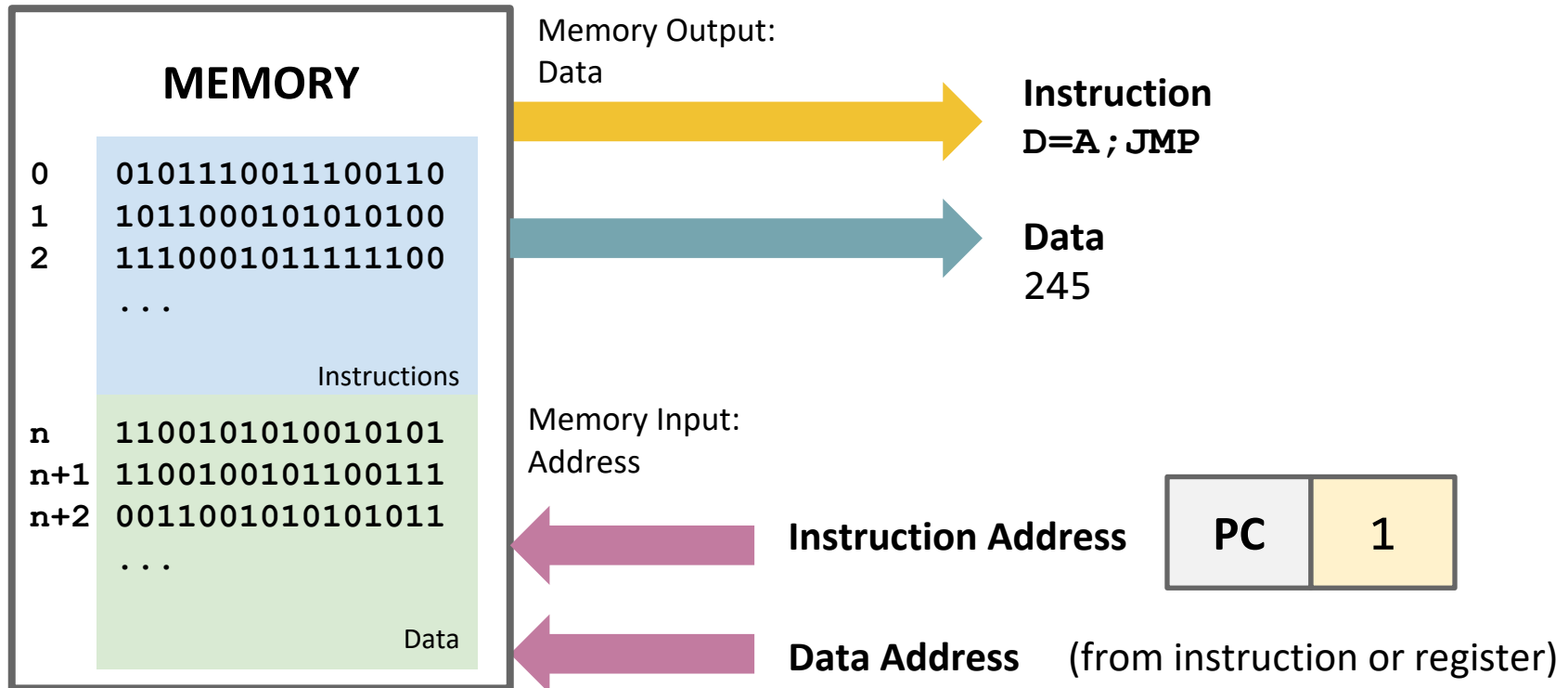

❖ Could we implement with **RAM16K.hd1**?


# Combining Fetch & Execute

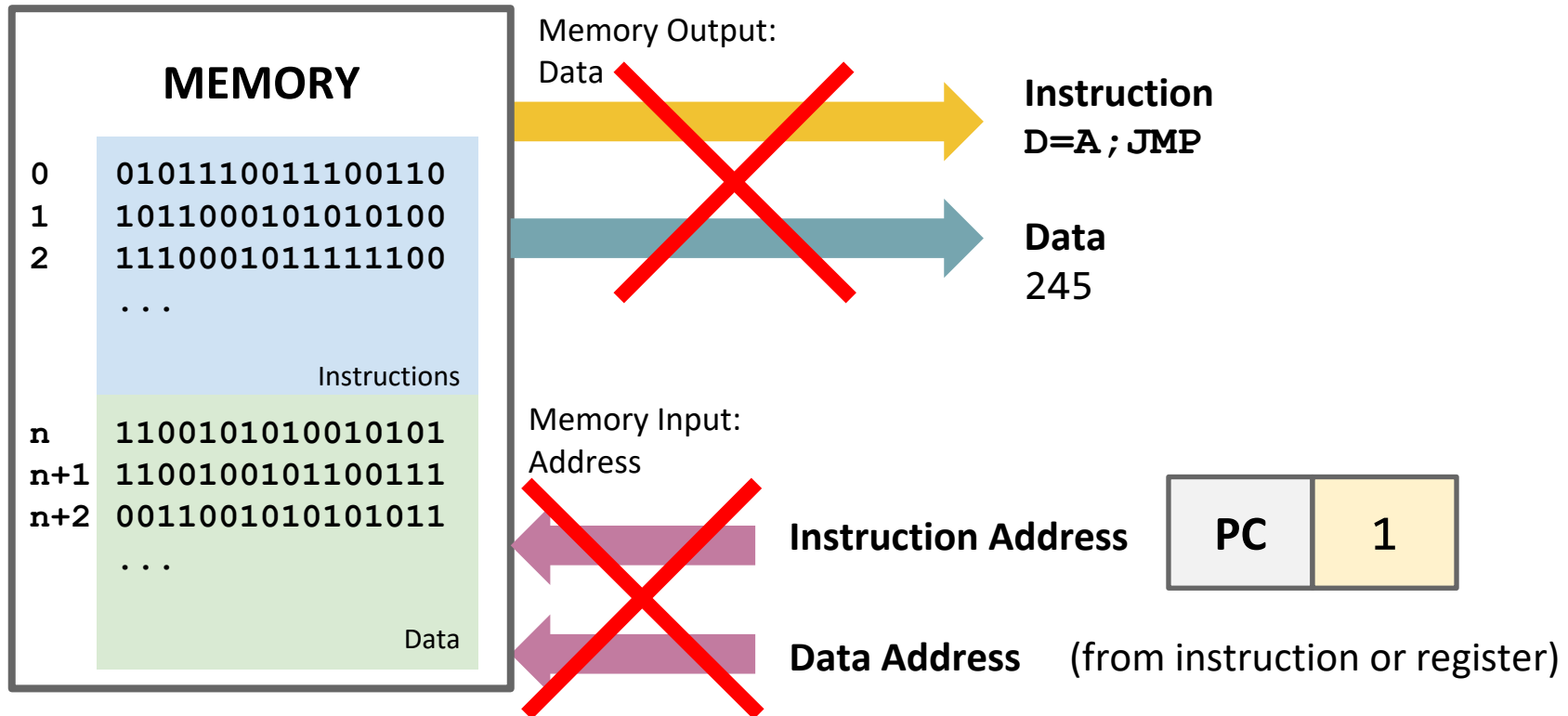

❖ Could we implement with **RAM16K.hd1**?


- **No!** Our memory chips only have one input and one output!
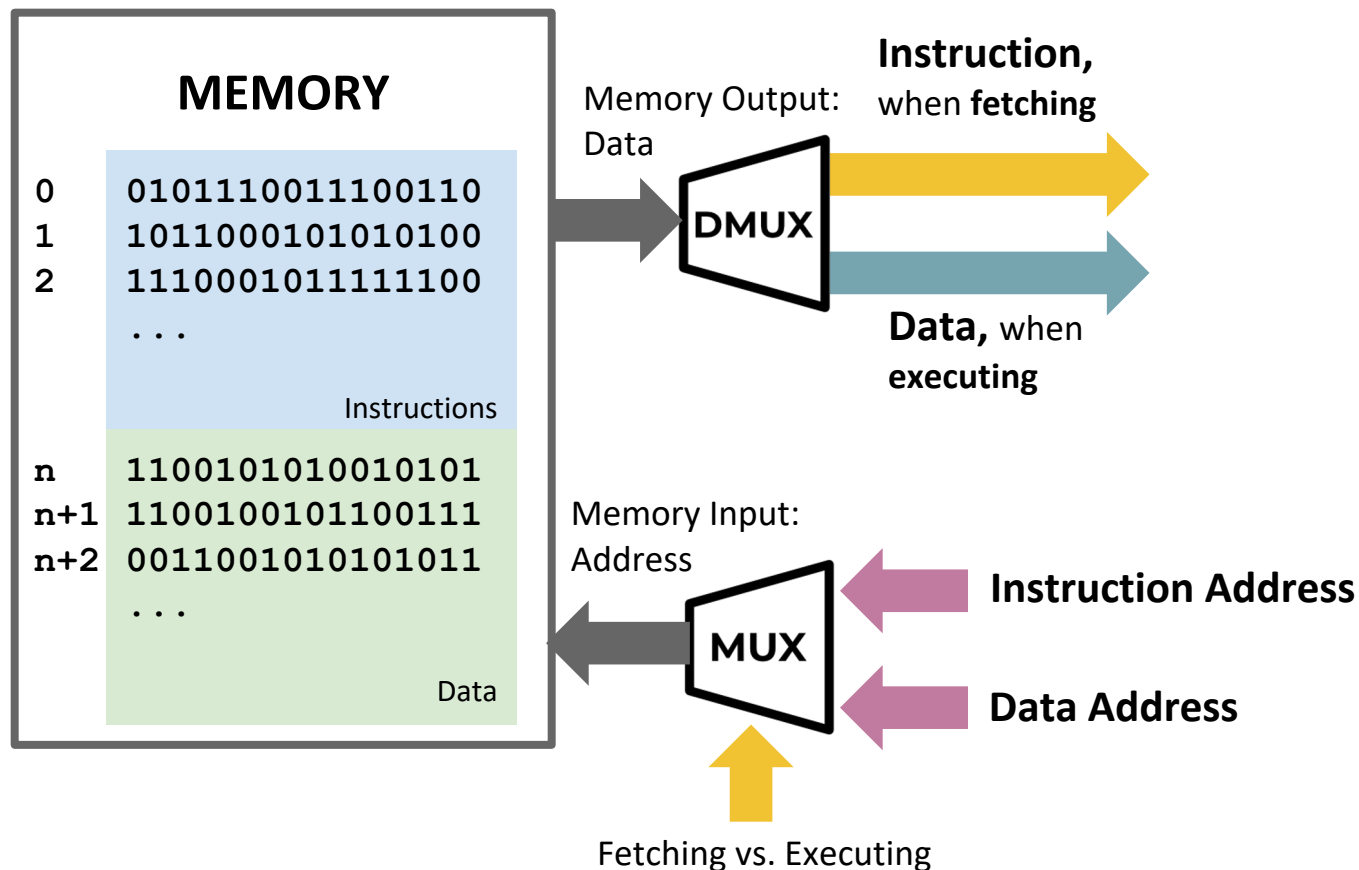
# Solution 1: Handling Single Input / Output



- ❖ Can use multiplexing to share a single input or output
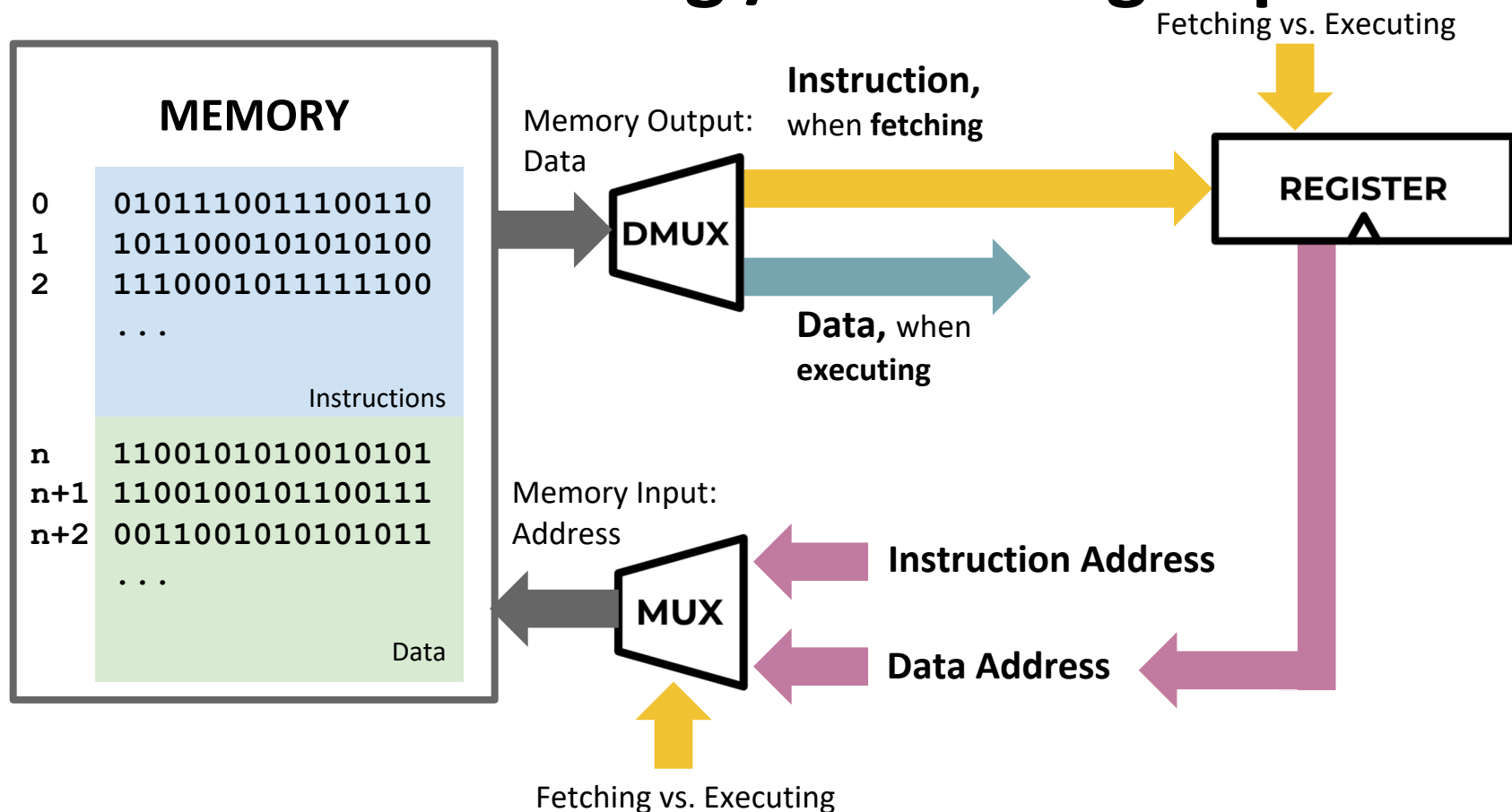
# Solution 1: Fetching / Executing Separately



- ❖ Need to store fetched instruction so it's available during execution phase


# Solution 2: Separate Memory Units

- ❖ Separate instruction memory and data memory into two different chips
  - Each can be independently addressed, read from, written to
- ❖ Pros:
  - Simpler to implement
- ❖ Cons:
  - Fixed size of each partition, rather than flexible storage
  - Two chips → redundant circuitry

# Lecture Outline

- ❖ Cornell Note-Taking Debrief
  - Reflection on notes from CSE 390B and other courses
- ❖ Exam Preparation
  - Study strategies, mock exam problem
- ❖ Building a Computer Overview
  - Architecture, fetch and execute cycle
- ❖ **Hack CPU Logic**
  - **Implementation and operations**


# Hack CPU

 



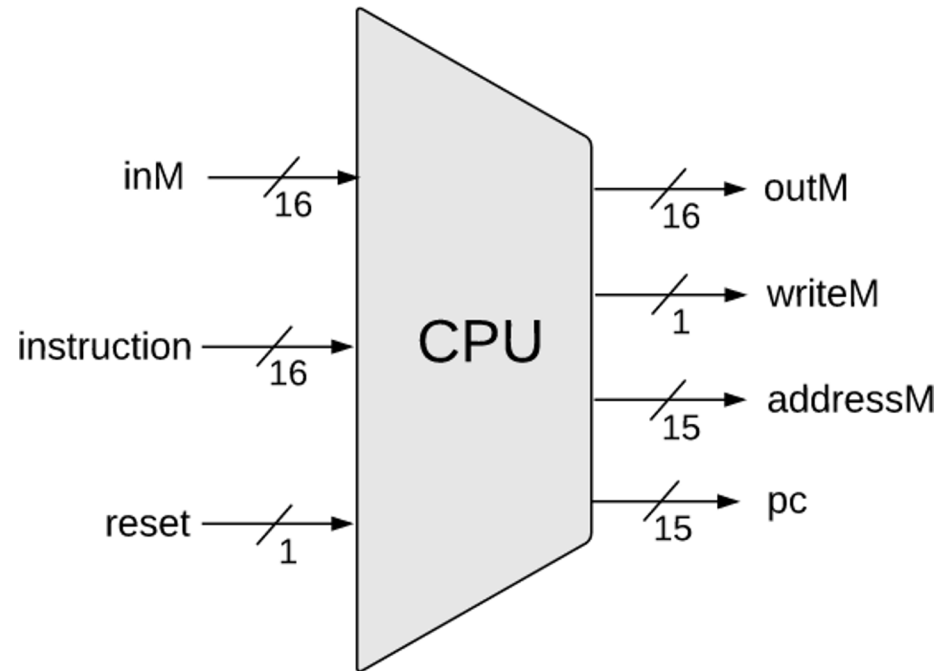
# Hack CPU Interface Inputs

- ❖ **inM**: Value coming from memory
- ❖ **instruction**: 16-bit instruction
- ❖ **reset**: if 1, reset the program



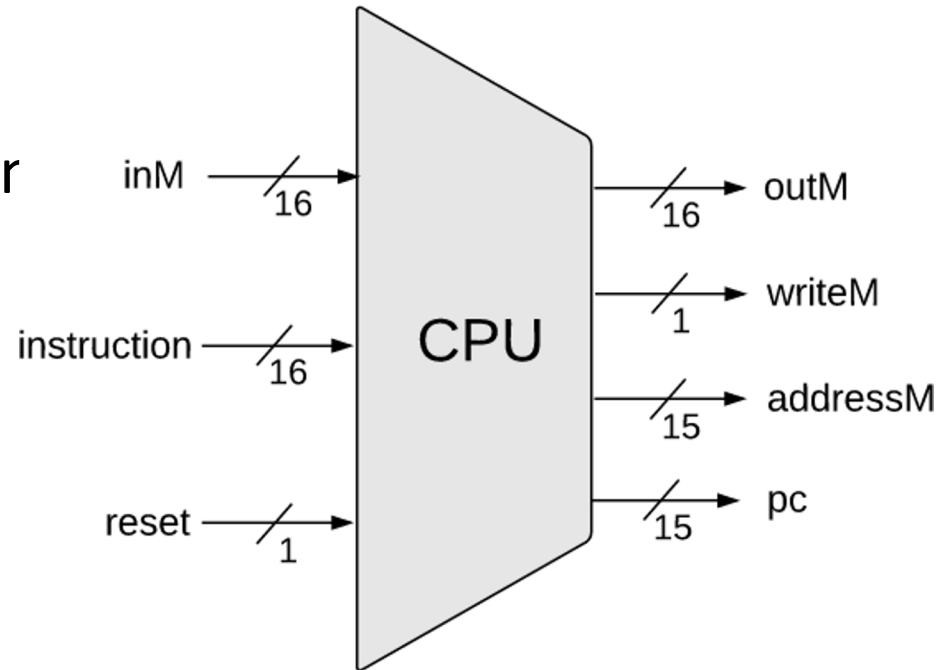
# Hack CPU Interface Outputs


- ❖ **outM**: value used to update memory if writeM is 1
- ❖ **writeM**: if 1, update value in memory at addressM with outM
- ❖ **addressM**: address to read from or write to in memory
- ❖ **pc**: address of next instruction to be fetched from memory



# Hack CPU Implementation

 


# Hack CPU Implementation

 


(each "c" symbol represents a control bit)

# CPU Operation: Instruction Handling

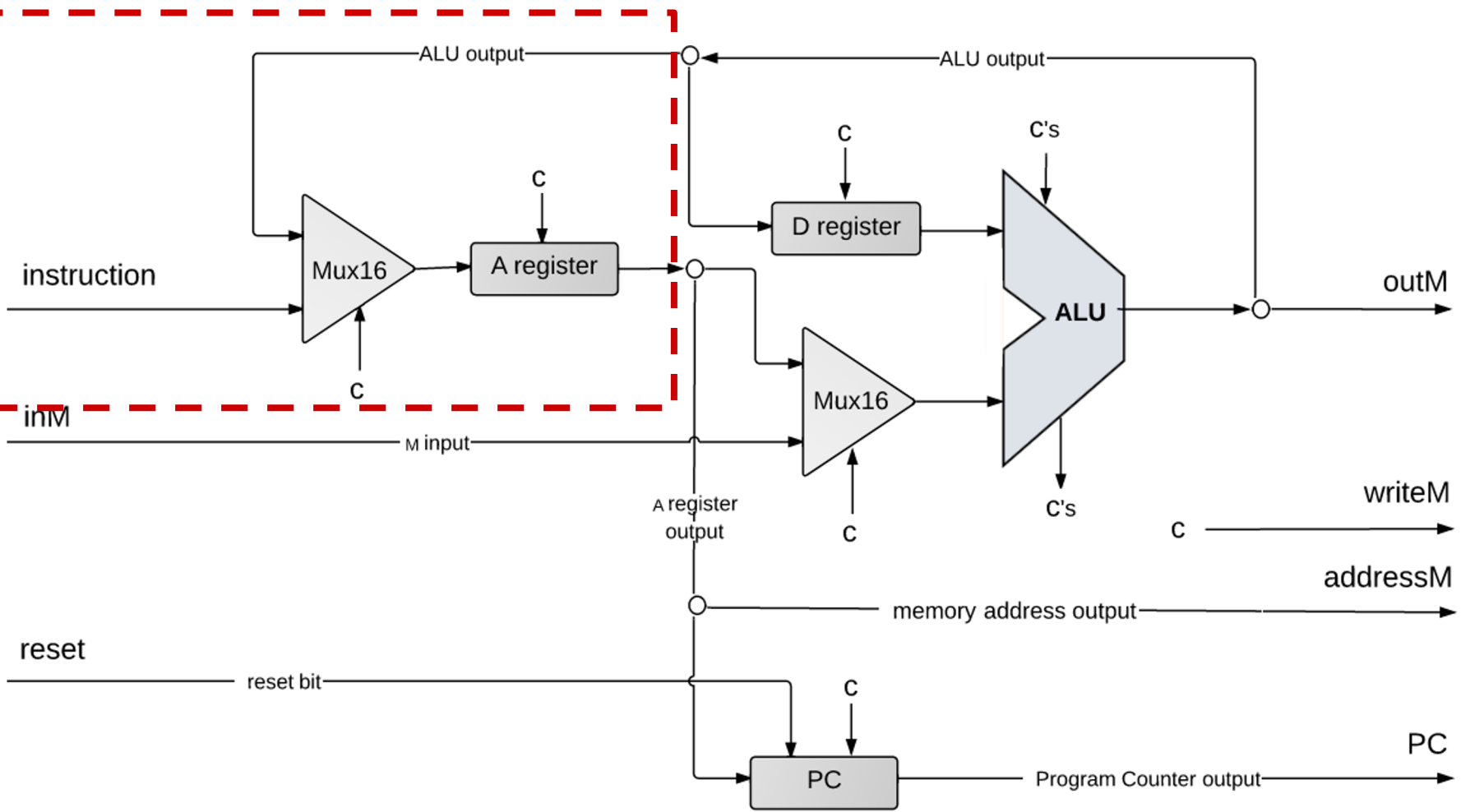


(each "c" symbol represents a control bit)

# CPU Operation: Instruction Handling

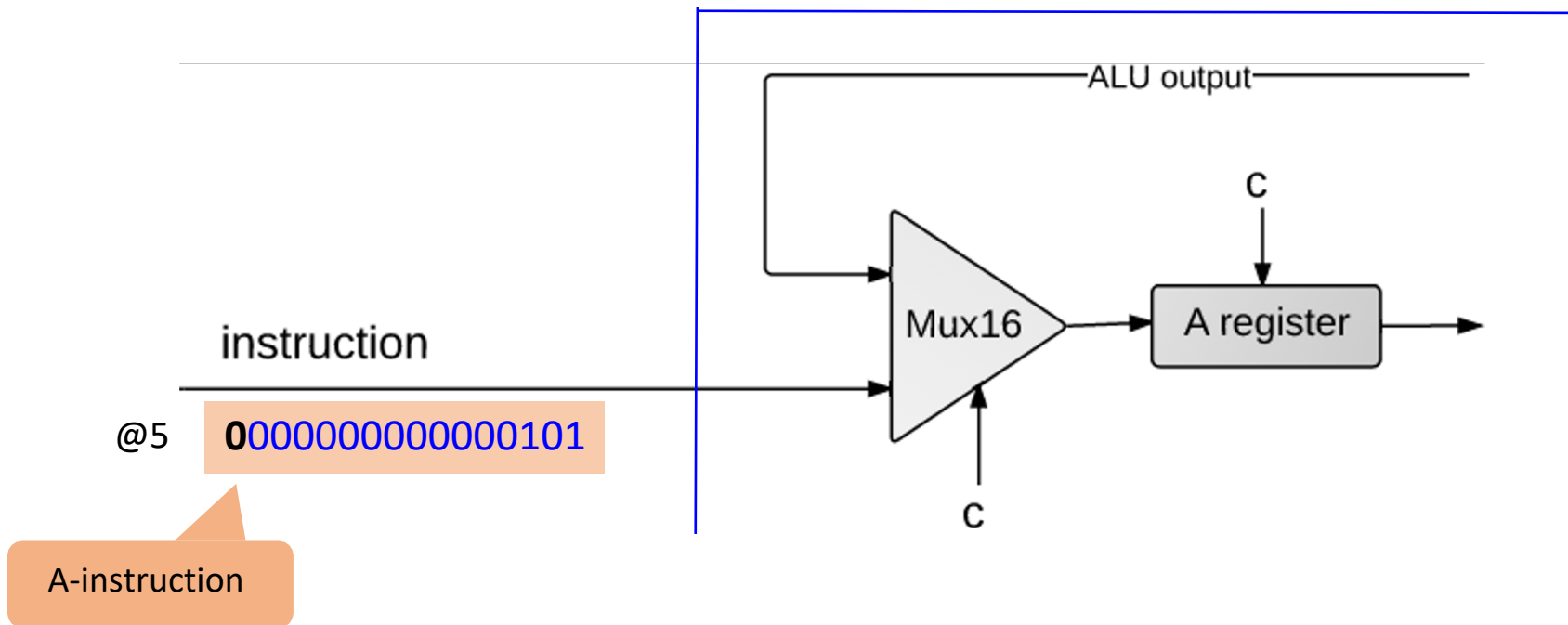


# CPU Operation: Instruction Handling

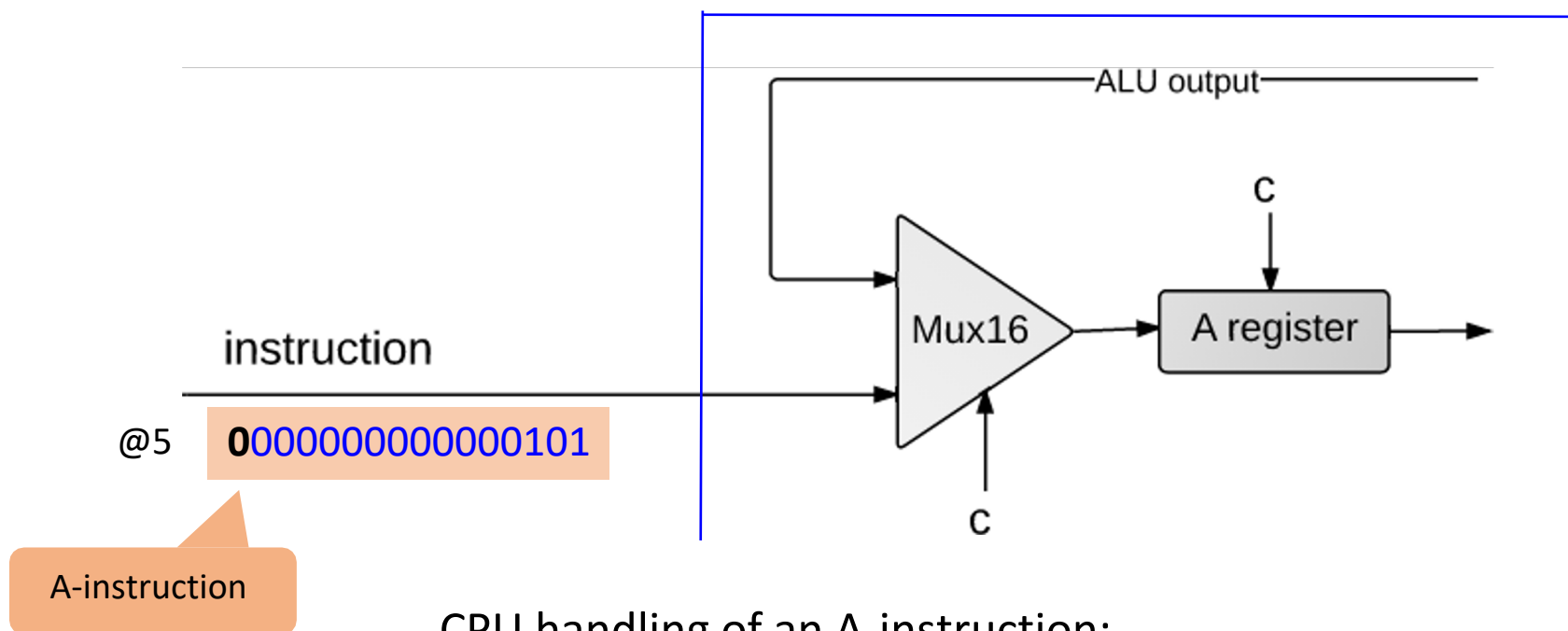

## CPU handling of an A-instruction:


- Decodes the instruction into:
  - op-code
  - 15-bit value
- Stores the value in the A-register
- Outputs the value (not shown in this diagram).

# CPU Operation: Instruction Handling

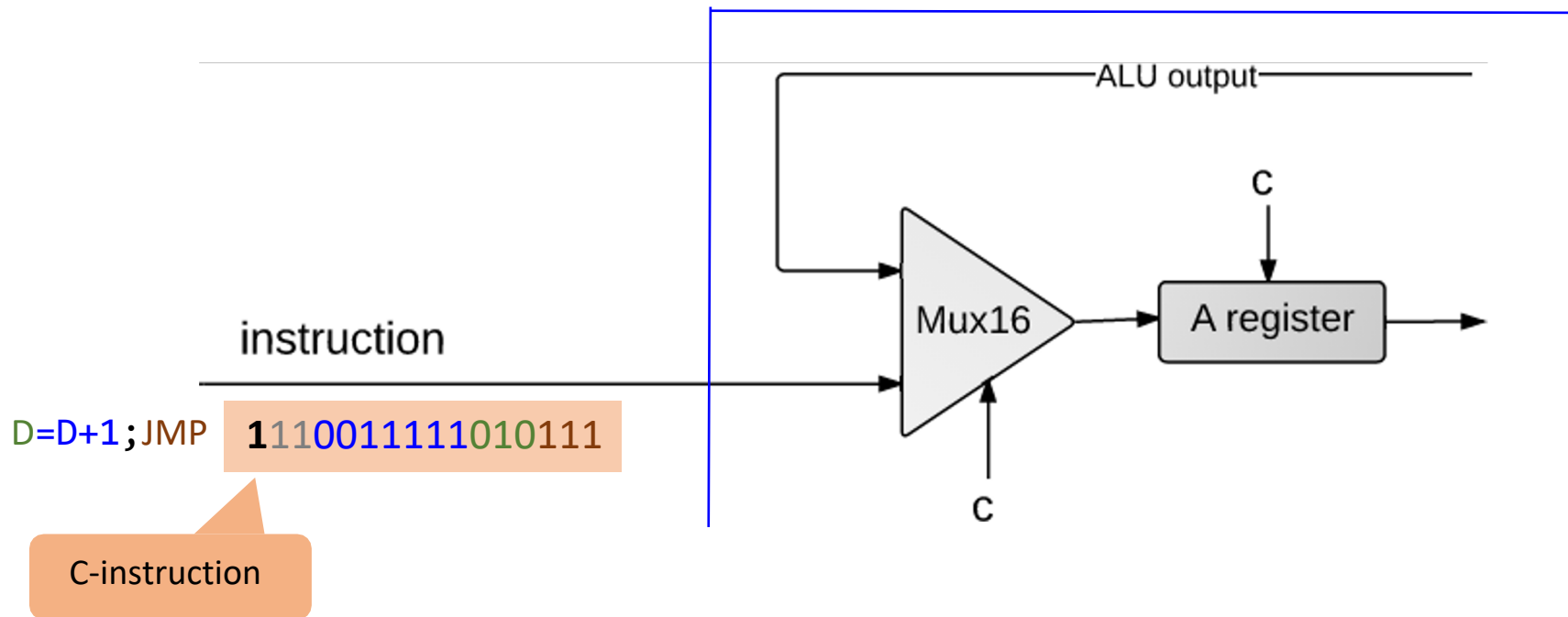



# CPU Operation: Instruction Handling

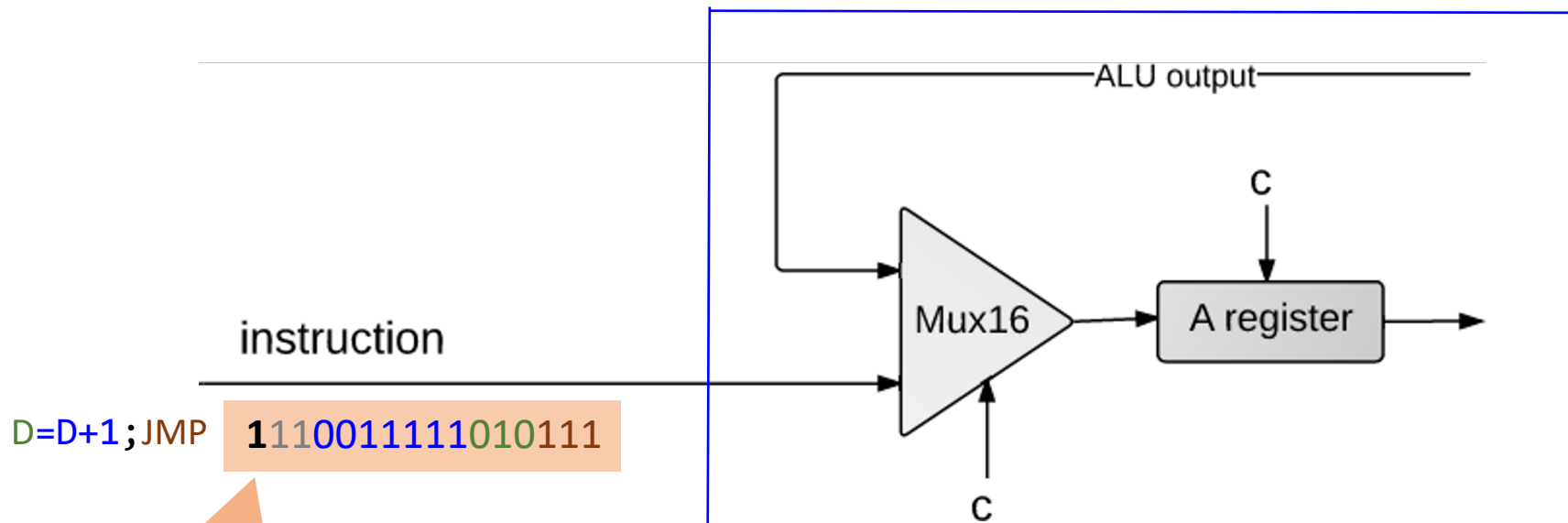

`D=D+1; JMP`


`1110011111010111`

C-instruction

## CPU handling of a C-instruction:

- Decodes the instruction bits into:
  - Op-code
  - ALU control bits
  - Destination load bits
  - Jump bits
- Routes these bits to their chip-part destinations
- The chip-parts (most notably, the ALU) execute the instruction.

# CPU Operation: Handling C-Instructions

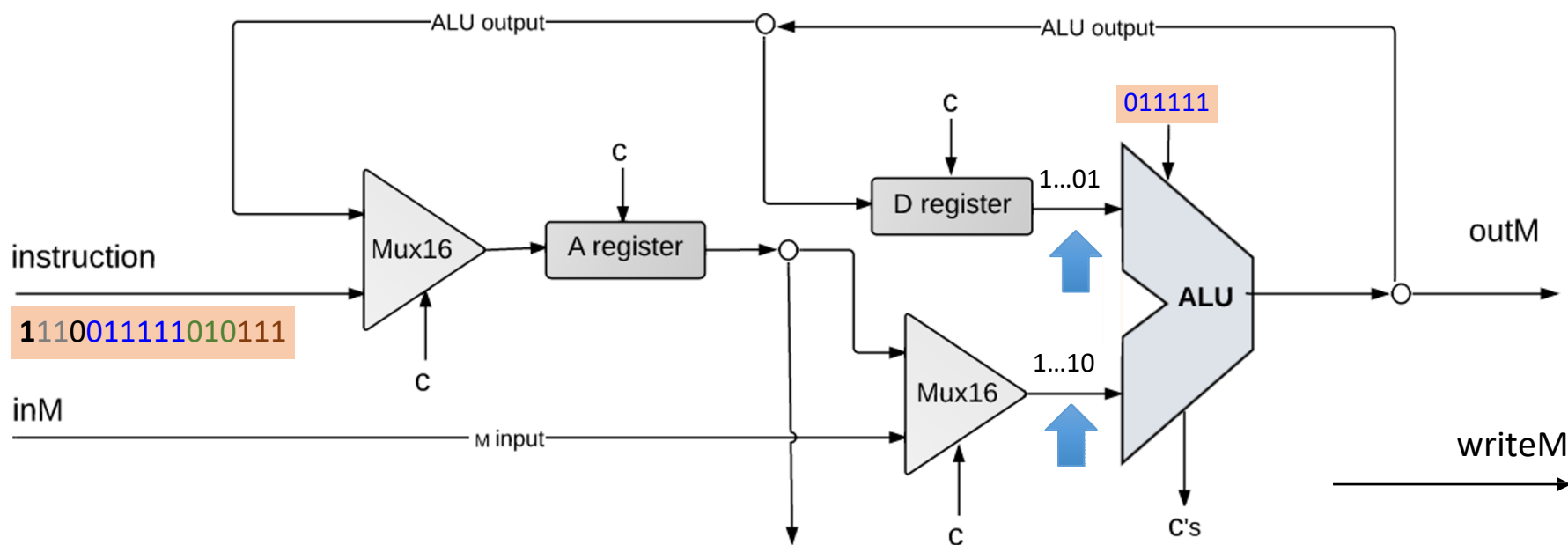


## ALU data inputs:

- Input 1: from the D-register
- Input 2: from either:
  - A-register, or
  - data memory

## ALU control inputs:

- control bits (from the instruction)


# CPU Operation: Handling C-Instructions

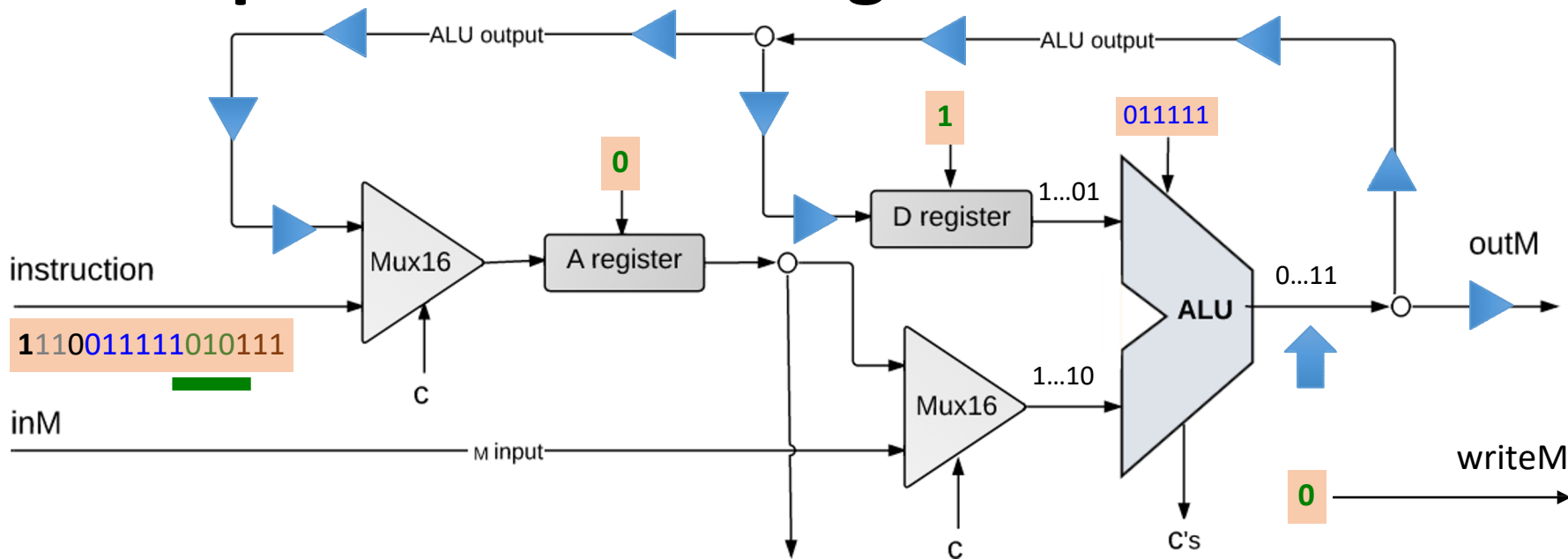

## ALU data output:

- Result of ALU calculation
- Fed simultaneously to: D-register, A-register, data memory
- Which destination *actually* commits to the ALU output is determined by the instruction's **destination bits**.


# CPU Operation: Handling C-Instructions

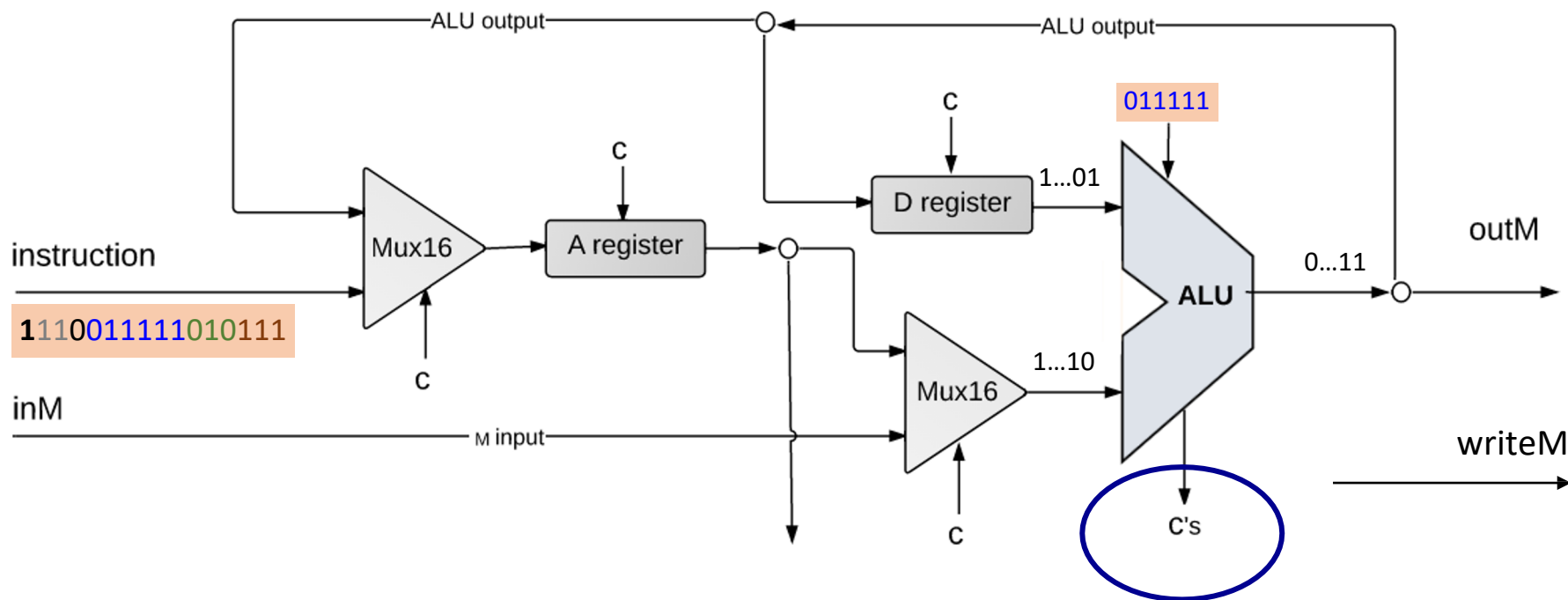


## ALU control outputs:

- is the output negative?
- is the output zero?


# CPU Operation: Control

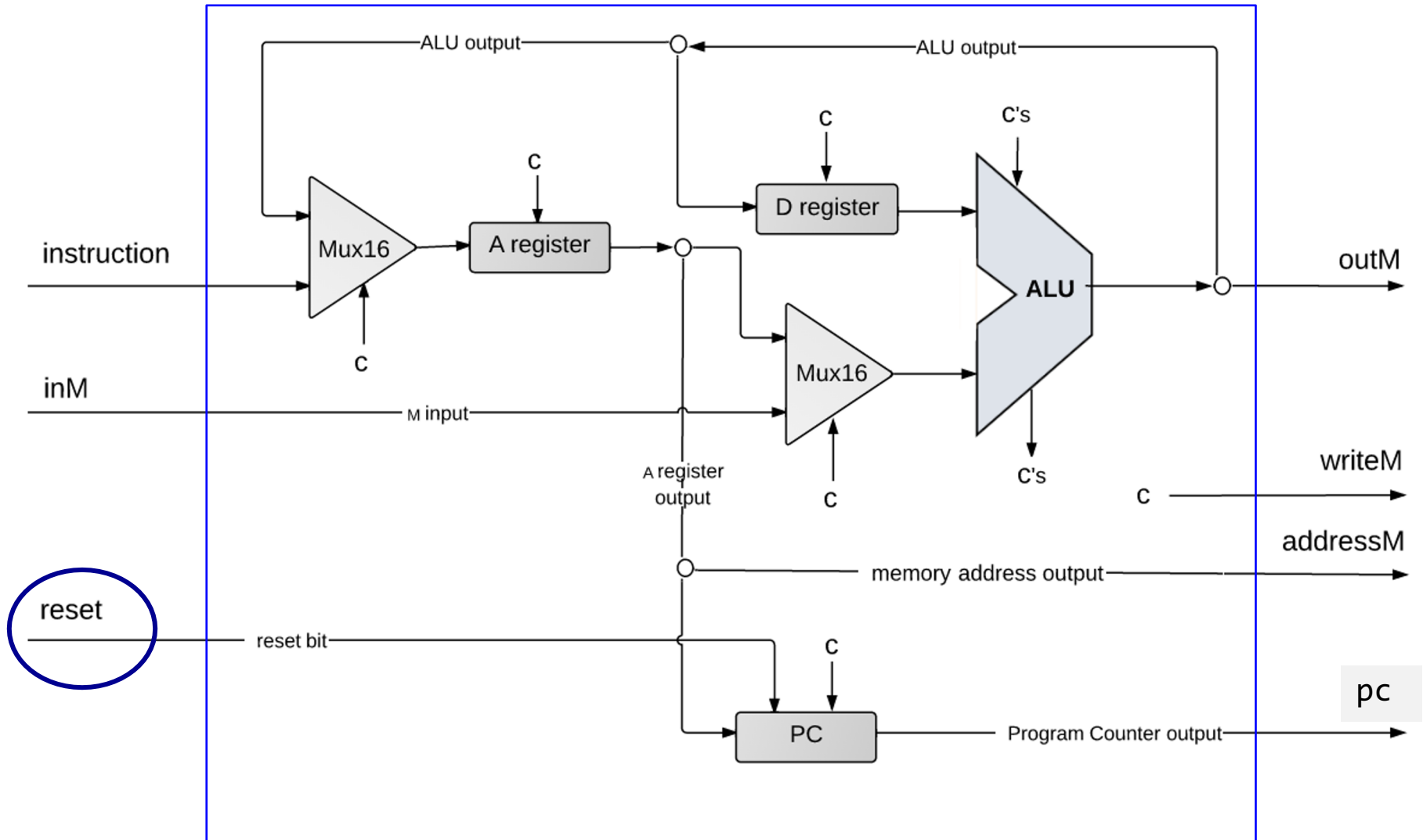

# CPU Operation: Control

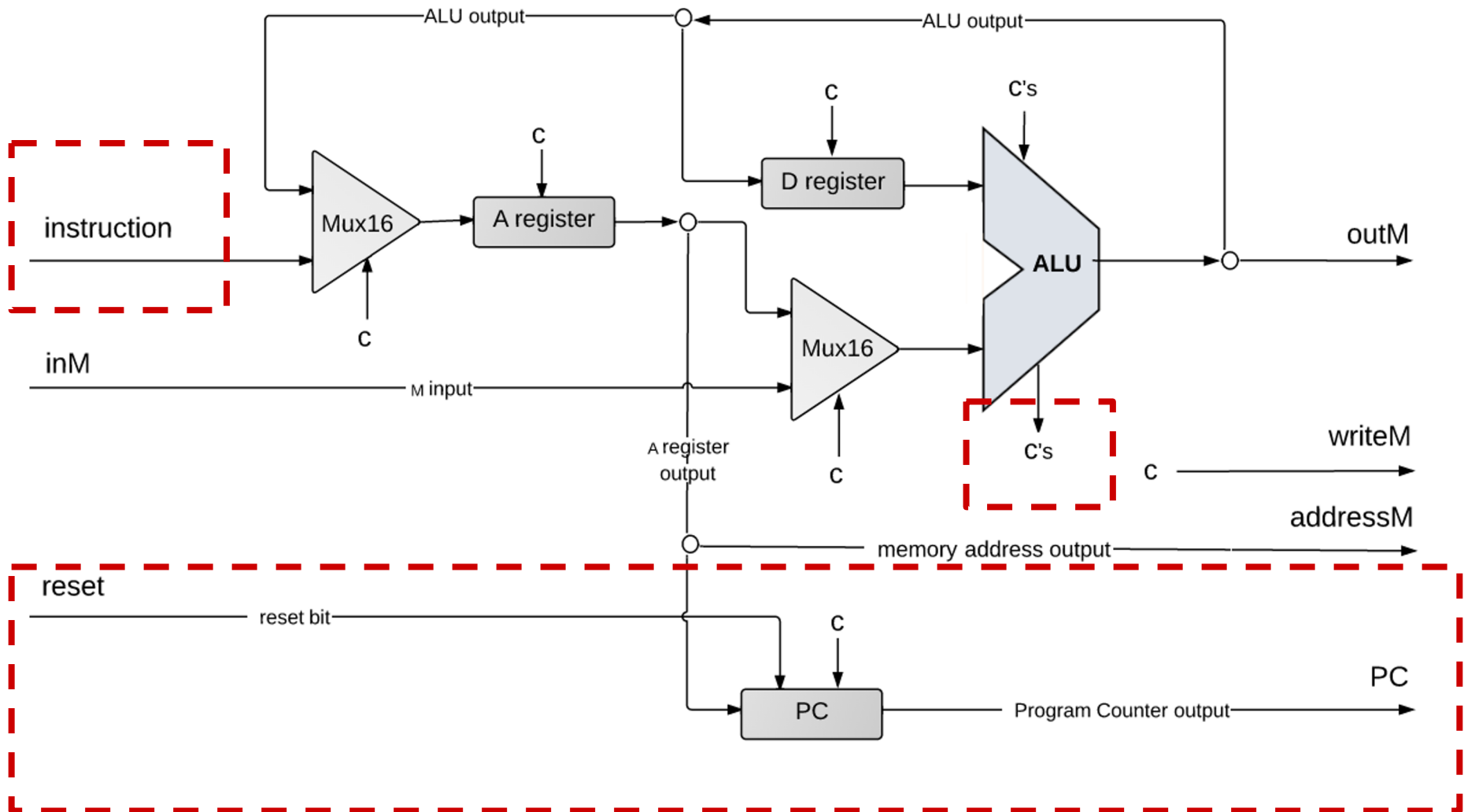

# CPU Operation: Control

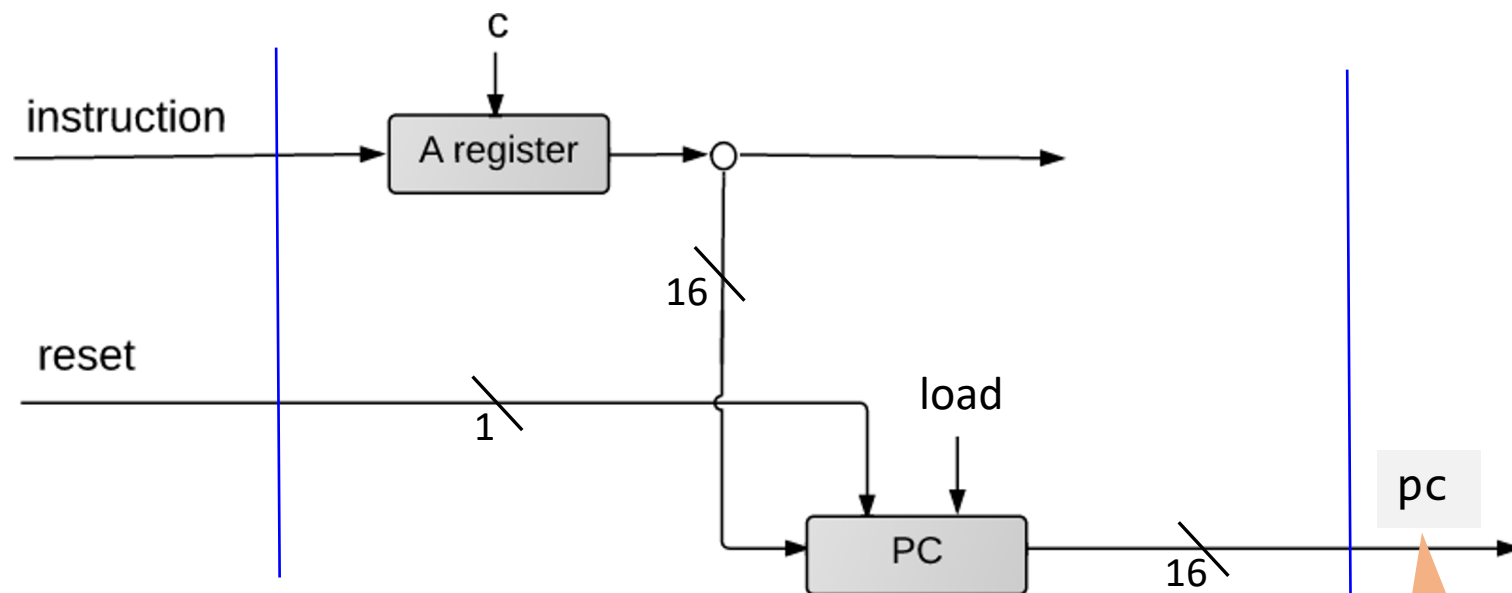


## PC operation (abstraction)

Emits the address of the next instruction:

- restart:     PC = 0
- no jump:    PC++
- goto:        PC=A
- conditional goto:     if (*condition*) PC = A  
                              else PC++

address of next instruction

# CPU Operation: Control

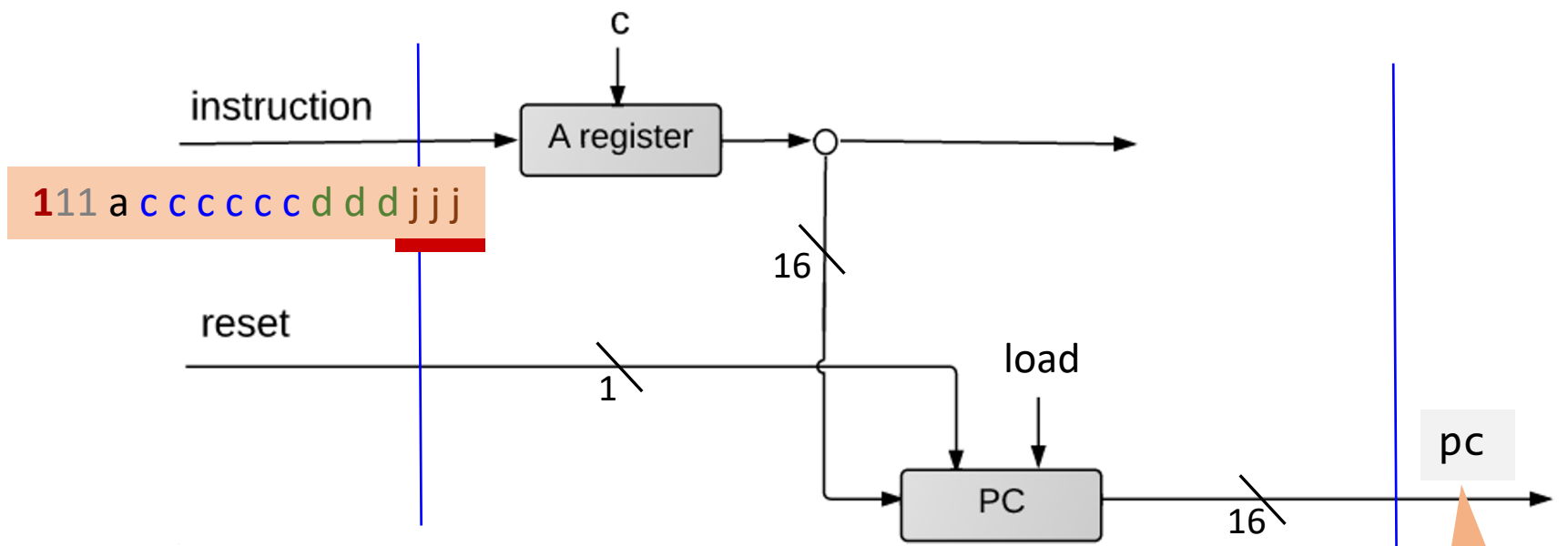

## PC operation (implementation)

```
if (reset==1) PC = 0
```

```
else
```

```
    // in the course of handling the current instruction:
```

```
    load = f (jump bits, ALU control outputs)
```

```
    if (load == 1) PC = A // jump
```


```
    els PC++ // next instruction
```

```
e
```

address of next instruction



# Hack CPU Implementation: That's It!

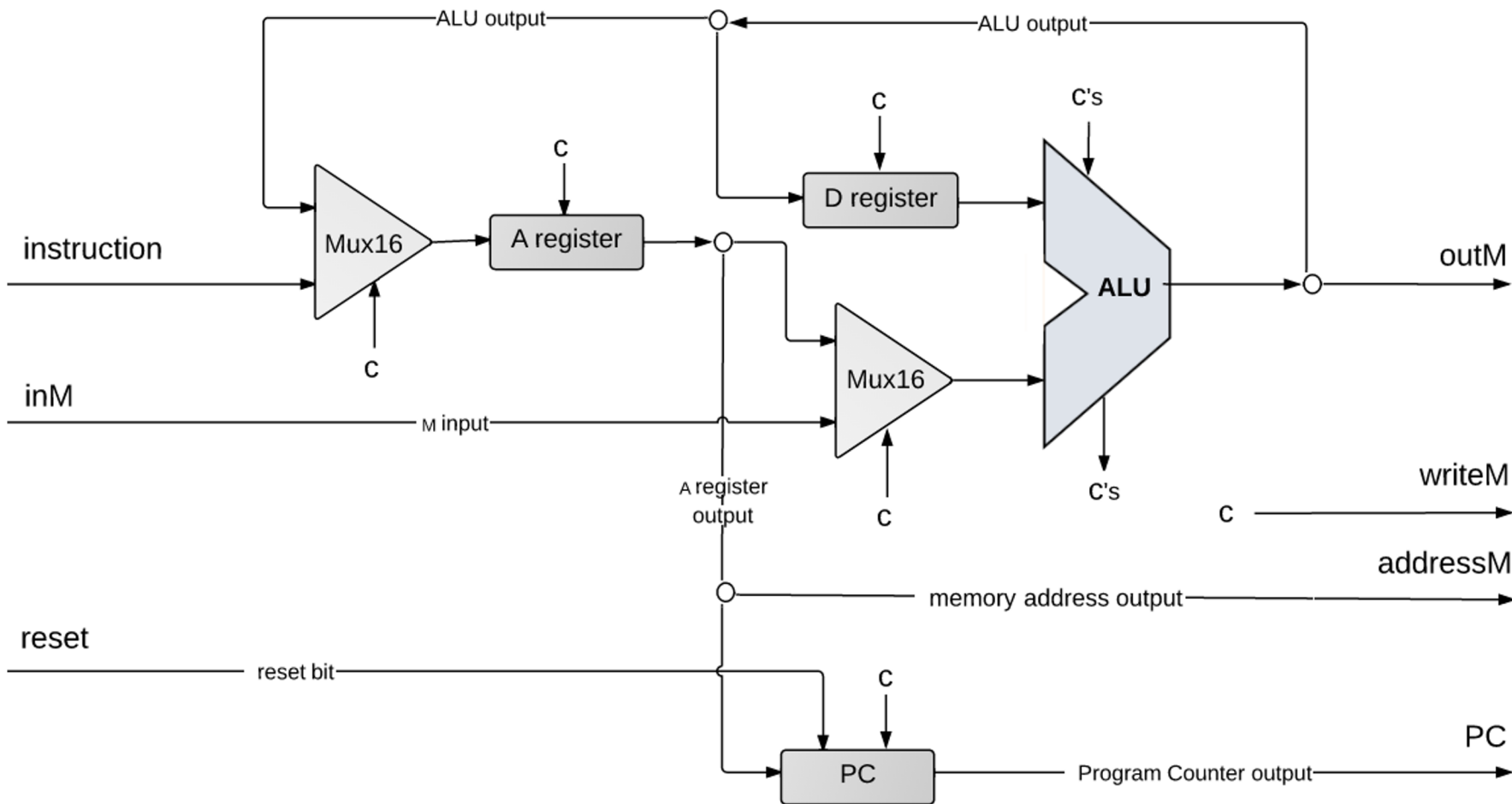

# Post-Lecture 9 Reminders

- ❖ Project 4: Machine Language, Building a Computer Part I, & Annotation
  - Due on Thursday (2/3) at 11:59PM PST
  
- ❖ CSE 390B Midterm
  - Thursday, February 10<sup>th</sup> during lecture