

CSE 390B, Spring 2023

Building Academic Success Through Bottom-Up Computing

Study Environment & Boolean Logic

Study Environment Discussion, Boolean Logic and Functions,
Foundational Logic Gates, Hardware Descriptive Languages

Checking in on Project 1

- ❖ Remember to double-check your submission on GitLab
 - Navigate to GitLab, open tags, and verify that the associated commit includes your expected changes

- ❖ How has Project 1 been coming along?

- ❖ What questions do you have about Project 1?

Lecture Outline

- ❖ **Study Environment Discussion**
- ❖ **Boolean Logic and Functions**
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
- ❖ **Hardware Descriptive Languages (HDL)**
 - HDL Syntax, **And** Gate Example
- ❖ **Foundational Logic Gates**
 - **Nand, Not, And, Or, Xor, Mux, DMux** Gates
 - Example of Implementing an **Xor** Gate in HDL

Study Environment Discussion

In groups of 3-4, discuss the following questions about study environments:

- ❖ On a typical day, what does your study environment look like? Be specific!

- ❖ What contributes to an effective study environment? Why?
 - What changes can you make to introduce some of these factors?

- ❖ What factors hinder a study environment from being effective? Why?
 - What changes can you make to remove some of these factors?

Ideal Study Environment

- ❖ Free from distractions (phones, computer tabs, etc.)
- ❖ Ensure your study environment is well organized and free from clutter
- ❖ Peaceful and quiet, possibly with some background noise
 - Listening to music may help depending on genre and the person
- ❖ Add decoration that can be an inspiration to your study environment (e.g., plants, quotes, stickers)
- ❖ Have your study material out ahead of time

Lecture Outline

- ❖ Study Environment Discussion
- ❖ **Boolean Logic and Functions**
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
- ❖ Hardware Descriptive Languages (HDL)
 - HDL Syntax, **And** Gate Example
- ❖ Foundational Logic Gates
 - **Nand, Not, And, Or, Xor, Mux, DMux** Gates
 - Example of Implementing an **Xor** Gate in HDL

Boolean Values

- ❖ A binary choice: **True** or **False**
- ❖ Also known as a “low” signal (false, “off,” or 0) and a “high” signal (true, “on”, or 1)



“Off”

False

0



“On”

True

1

Boolean Operations

- ❖ Use logical operations to combine Boolean values
 - **Truth table:** A table that lists every possible set of inputs and the corresponding output of the operation
 - Operations correspond to physical hardware gates

- ❖ Examples:

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

$$F = A \text{ OR } B$$

A	F
0	1
1	0

$$F = \text{NOT } A$$


Boolean Functions

- ❖ Combinations of Boolean inputs resulting in single output
- ❖ Multiple ways to specify a Boolean function:
 - Boolean expression: $F = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$

- Circuit diagram with logic gates:

- Truth table:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Boolean Expression \rightarrow Truth Table

- ❖ We can build a truth table from an expression
 - Evaluate the Boolean expression on all possible inputs

$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$




A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Boolean Expression \rightarrow Truth Table

- ❖ We can build a truth table from an expression
 - Evaluate the Boolean expression on all possible inputs
 
$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$




A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression ← Truth Table

❖ But can we do it in reverse?
 
$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression ← Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

A AND B AND C

Boolean Expression \leftarrow Truth Table

- Then, we can combine the rows using OR operations

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C


A AND B AND C

$$F = \text{NOT}(A) \text{ AND NOT}(B) \text{ AND } C \text{ OR NOT}(A) \text{ AND } B \text{ AND } C \text{ OR } \\ A \text{ AND } B \text{ AND NOT } C \text{ OR } A \text{ AND } B \text{ AND } C$$

Boolean Expression ← Truth Table

- ❖ But can we do it in reverse?
 - Yes, we can! The strategy we used is **Boolean Function Synthesis**
 
$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

< **Lecture 2: Study Environment & Boolean Logic**



Loading...



Lecture Outline

- ❖ Study Environment Discussion
- ❖ Boolean Logic and Functions
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
- ❖ **Hardware Descriptive Languages (HDL)**
 - **HDL Syntax, And Gate Example**
- ❖ Foundational Logic Gates
 - **Nand, Not, And, Or, Xor, Mux, DMux** Gates
 - Example of Implementing an **Xor** Gate in HDL

Hardware Design Language (HDL)

- ❖ HDL is a programming language to specify hardware components and how they're connected
 - Another way of describing a Boolean function!
- ❖ Many Hardware Design Languages are used today
 - E.g., VHDL, Verilog, SystemVerilog
 - In this course, we'll use a simple HDL language called "HDL"
- ❖ Unlike Java, HDL is a **declarative** language. This means the following:
 - The order of statements (lines of code) doesn't matter
 - We are describing a physical system

Hardware Design Language (HDL)

❖ Format of an HDL file

- File comment describes expected behavior
- **IN** names chip inputs, **OUT** names chip outputs
- **PARTS** specify the components (i.e., other gates) that implement the chip

```
/**
 * And gate:
 * out = 1 only if both a and b are 1
 */
CHIP And {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Reusing Components

- ❖ You can (and should!) use chips you have already implemented to implement subsequent chips
- ❖ We give you one gate, **Nand**, to start out with
 - Implication: The entire computer you will be building will be use **Nand** gates as its foundation
- ❖ We also provide you with some chips you can use without implementing

HDL Component Example: AND

- ❖ The chip specification tells us the name of the input and output wires


```
CHIP And {  
    IN a, b;  
    OUT out;  
  
    ...  
}
```

- ❖ Goal: Implement $w1$ AND $w2$

- HDL Syntax for using (being a client of the **And** gate):

And(a=w1, b=w2, out=w3);

- Equivalent circuit diagram:

 

Multi-bit Buses in HDL

- ❖ It can be useful to manipulate groups of wires
 - Called a “bus” of wires
- ❖ HDL provides array like syntax for manipulating buses
 - **And4** chip example:

```
/**
 * Bit-wise And of two 4-bit inputs
 */
CHIP And4 {
    IN a[4], b[4];
    OUT out[4];

    PARTS:
    And (a=a[0], b=b[0], out=out[0]);
    And (a=a[1], b=b[1], out=out[1]);
    And (a=a[2], b=b[2], out=out[2]);
    And (a=a[3], b=b[3], out=out[3]);
}
```

HDL Resources

- ❖ HDL will feel unfamiliar at first, and that's okay
- ❖ Resources for helping you navigate HDL linked under the [Resources page](#) on the course website
 - HDL Survival guide
 - Appendix A (HDL Spec)
 - Chip Set Overview (to help you remember the inputs/outputs for various chips)
 - Chapter readings

Lecture Outline

- ❖ Study Environment Discussion
- ❖ Boolean Logic and Functions
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
- ❖ Hardware Descriptive Languages (HDL)
 - HDL Syntax, **And** Gate Example
- ❖ **Foundational Logic Gates**
 - **Nand, Not, And, Or, Xor, Mux, DMux Gates**
 - **Example of Implementing an Xor Gate in HDL**

The Foundational Building Block

- ❖ It all starts with the NAND gate
- ❖ NAND is short for “Not And”
 - The same output as the AND gate, but every output bit is negated (flipped)

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

$$F = A \text{ NAND } B$$

Building Gates From Nand

- ❖ Recall the **Boolean Function Synthesis** strategy from today's reading
 - We saw how we can represent any truth table in terms of three gates: **Not**, **And**, **Or**
- ❖ First, we can represent **Not** directly from **Nand**
 - $\text{Not } a = a \text{ Nand } a$
- ❖ Then, we can represent **And** in terms of **Not** and **Nand**
 - $a \text{ And } b = \text{Not}(a \text{ Nand } b)$
- ❖ Represent **Or** in terms of **Not** and **And**
 - Apply De Morgan's Law
 - $a \text{ Or } b = \text{Not}(\text{Not}(a) \text{ And } \text{Not}(b))$ [De Morgan's Law]

Making Decisions in Hardware


- ❖ We write if/else statements in Java with the understanding that *only one* of the branches will run
 - For example, in the following code, we expect to compute one of $a \& b$ or $a \mid b$ (not both)

```
if (c == 0) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```
- ❖ In hardware, the entire circuit is always executing
 - We can't "turn off" a part of a circuit based on a condition
 - Instead, we create circuits for different conditions and choose which output based on a condition instead

Decisions in Hardware: Mux Gate

❖ We can use a **Multiplexer (Mux)** gate to choose which singular input to output

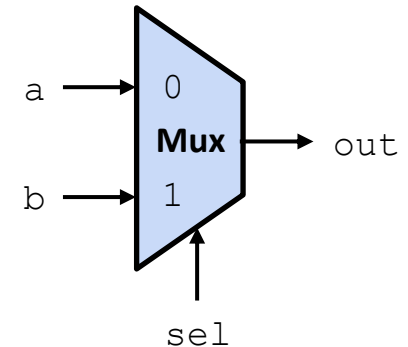- Takes three inputs: a , b , and sel
- If $sel == 0$, then $out = a$
- Otherwise, $out = b$




❖ Mux Gate Truth Table:

a	b	sel	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Decisions in Hardware: DMux Gate

❖ A **Demultiplexer (DMux)** gate passes one input to one of two outputs and 0 to the rest

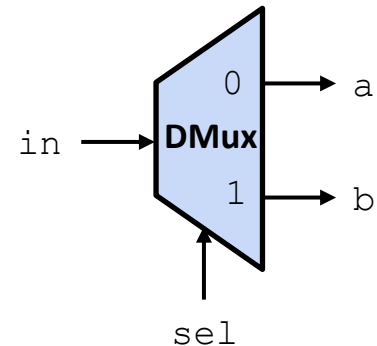- Takes two inputs: `in` and `sel`
- If `sel == 0`, then `a = in` and `b = 0`
- Otherwise, `a = 0` and `b = in`



❖ DMux Gate Truth Table:

in	sel	a	b
0	0	0	0
0	1	0	0
1	0	1	0
1	1	0	1

Implementing an Xor Gate: Overview

- ❖ Let's walk through an example of building a gate that you will work on in Project 2, the **Xor** gate
- ❖ Together, we'll implement the **Xor** gate

```
/**
 * Xor gate:
 * out = not(a == b)
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Implementing an Xor Gate: Overview

❖ Plan of action:

- Step 1: Create the logic operation's **truth table**
- Step 2: Use truth table to generate a **Boolean function** using strategies we've learned, such as the Boolean Function Synthesis
- Step 3: Convert Boolean function to **HDL**

```
/**
 * Xor gate:
 * out = not(a == b)
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Implementing an Xor Gate: Step 1

- ❖ Step 1: Create the truth table for Xor
 - Interpret the specification: $F = \text{NOT}(A == B)$

A	B	F
0	0	
0	1	
1	0	
1	1	

$$F = A \text{ XOR } B$$

Implementing an Xor Gate: Step 1

- ❖ Step 1: Create the truth table for Xor
 - Interpret the specification: $F = \text{NOT}(A == B)$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

$$F = A \text{ XOR } B$$

Implementing an Xor Gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading
 - **Row 2 = NOT(A) AND B**

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Implementing an Xor Gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading
 - Row 2 = NOT(A) AND B
 - **Row 3 = A AND NOT(B)**

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Implementing an Xor Gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading
 - Row 2 = NOT(A) AND B
 - Row 3 = A AND NOT(B)
 - $F = ?$

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

< **Lecture 2: Study Environment & Boolean Logic**



Loading...



Implementing an Xor gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the Boolean function synthesis strategy from the reading
 - Row 2 = NOT(A) AND B
 - Row 3 = A AND NOT(B)
 - $F = \text{Row 2 OR Row 3}$
 $= (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND NOT}(B))$


A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Implementing an Xor gate: Step 3

- ❖ Now that we have a Boolean expression, we can implement the **Xor** gate in HDL
- ❖ Optionally, it can help to express the Boolean expression as a circuit diagram

 
$$A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$$



Implementing an Xor gate: Step 3

- ❖ Step 3: Convert Boolean function to HDL syntax
 - $A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$
 - Assumes **Not**, **And**, and **Or** are already implemented
 - Note the use of intermediary wires: **nota**, **notb**, **x**, and **y**
 
```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
  Not (in=a, out=nota);  
  Not (in=b, out=notb);  
  And (a=a, b=notb, out=x);  
  And (a=nota, b=b, out=y);  
  Or (a=x, b=y, out=out);  
}
```



Project 2 Overview

- ❖ **Metacognitive Component: Study Skills Inventory**
 - Reflect on your academic behaviors, strategies, and practices
 - You will be graded on completing the form, not your responses
 - This activity is for your own benefit, and the more honest you are, the more beneficial it will be
- ❖ **Technical Component: GitLab Setup**
 - Will help prepare you for future CSE 390B projects
- ❖ Estimated time to complete: 6-8 hours
- ❖ **Project 2 is released and will be due next Thursday (4/6) at 11:59pm**

Post-Lecture 2 Reminders

- ❖ **Project 1 due tonight (3/30) at 11:59pm**
- ❖ Project 2 (Study Skills Inventory & Boolean Logic) released today, due next Thursday (4/6) at 11:59pm
- ❖ Anam has office hours after class in CSE2 121
- ❖ First Student-TA meetings starting next week
 - Your TA will be in contact with you about the first meeting