

CSE 390B, Winter 2023

Building Academic Success Through Bottom-Up Computing

Study Environment & Boolean Logic

Study Environment Discussion, Boolean Logic and Functions,
Foundational Logic Gates, Hardware Descriptive Languages

Checking in on Project 1

- ❖ Remember to double-check your submission on GitLab
 - Navigate to GitLab, open tags, and verify that the associated commit includes your expected changes
- ❖ How has Project 1 been coming along?
- ❖ What questions do you have about Project 1?

Lecture Outline

- ❖ **Study Environment Discussion**
- ❖ **Boolean Logic and Functions**
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
- ❖ **Hardware Descriptive Languages (HDL)**
 - HDL Syntax, **And** Gate Example
- ❖ **Foundational Logic Gates**
 - **Nand, Not, And, Or, Xor, Mux, DMux** Gates
 - Example of Implementing an **Xor** Gate in HDL

Study Environment Discussion

In groups of 3-4, discuss the following questions about study environments:

- ❖ On a typical day, what does your study environment look like? Be specific!

- ❖ What contributes to an effective study environment? Why?
 - What changes can you make to introduce some of these factors?

- ❖ What factors hinder a study environment from being effective? Why?
 - What changes can you make to remove some of these factors?

Lecture Outline

- ❖ Study Environment Discussion
- ❖ **Boolean Logic and Functions**
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
- ❖ Hardware Descriptive Languages (HDL)
 - HDL Syntax, **And** Gate Example
- ❖ Foundational Logic Gates
 - **Nand, Not, And, Or, Xor, Mux, DMux** Gates
 - Example of Implementing an **Xor** Gate in HDL

Boolean Values

- ❖ A binary choice: **True** or **False**
- ❖ Also known as a “low” signal (false, “off,” or 0) and a “high” signal (true, “on”, or 1)



“Off”

False

0



“On”

True

1

Boolean Operations

- ❖ Use logical operations to combine Boolean values
 - **Truth table:** A table that lists every possible set of inputs and the corresponding output of the operation
 - Operations correspond to physical hardware gates

- ❖ Examples:

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

$$F = A \text{ OR } B$$

A	F
0	1
1	0

$$F = \text{NOT } A$$


Boolean Functions

- ❖ Combinations of Boolean inputs resulting in single output
- ❖ Multiple ways to specify a Boolean function:
 - Boolean expression: $F = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$

- Circuit diagram with logic gates:

- Truth table:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

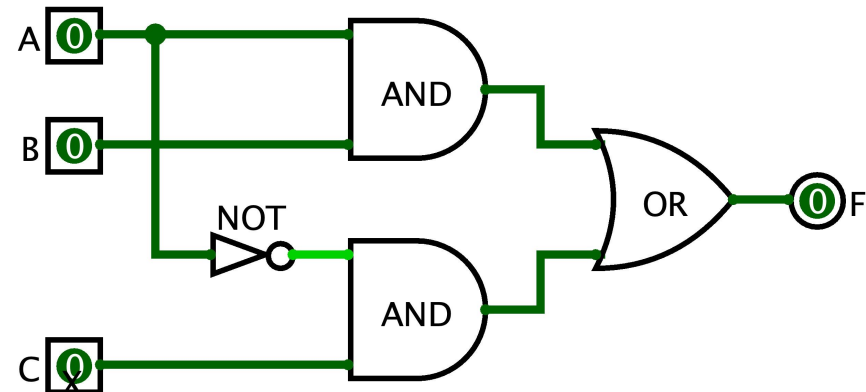

Boolean Expression \rightarrow Truth Table

- ❖ We can build a truth table from an expression
 - Evaluate the Boolean expression on all possible inputs

$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$



A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Boolean Expression \rightarrow Truth Table

- ❖ We can build a truth table from an expression
 - Evaluate the Boolean expression on all possible inputs

$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$




A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression ← Truth Table

❖ But can we do it in reverse?
 
$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

Boolean Expression \leftarrow Truth Table

- ❖ We can describe a single row with AND and NOT

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C

A AND B AND C

Boolean Expression \leftarrow Truth Table

❖ Then, we can combine the rows using OR operations

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

NOT(A) AND NOT(B) AND C

NOT(A) AND B AND C

A AND B AND NOT C


A AND B AND C

$F = \text{NOT}(A) \text{ AND NOT}(B) \text{ AND } C \text{ OR NOT}(A) \text{ AND } B \text{ AND } C \text{ OR}$
 $A \text{ AND } B \text{ AND NOT } C \text{ OR } A \text{ AND } B \text{ AND } C$

Boolean Expression ← Truth Table

- ❖ But can we do it in reverse?
 - Yes, we can! The strategy we used is **Boolean Function Synthesis**
 
$$F(A, B, C) = (A \text{ AND } B) \text{ OR } (\text{NOT}(A) \text{ AND } C)$$



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

< **Lecture 2: Study Environment & Boolean Logic**



Loading...



Lecture Outline

- ❖ Study Environment Discussion
- ❖ Boolean Logic and Functions
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
- ❖ **Hardware Descriptive Languages (HDL)**
 - **HDL Syntax, And Gate Example**
- ❖ Foundational Logic Gates
 - **Nand, Not, And, Or, Xor, Mux, DMux** Gates
 - Example of Implementing an **Xor** Gate in HDL

Hardware Design Language (HDL)

- ❖ HDL is a programming language to specify hardware components and how they're connected
 - Another way of describing a Boolean function!
- ❖ Many Hardware Design Languages are used today
 - E.g., VHDL, Verilog, SystemVerilog
 - In this course, we'll use a simple HDL language called "HDL"
- ❖ Unlike Java, HDL is a **declarative** language. This means the following:
 - The order of statements (lines of code) doesn't matter
 - We are describing a physical system

Hardware Design Language (HDL)

❖ Format of an HDL file

- File comment describes expected behavior
- **IN** names chip inputs, **OUT** names chip outputs
- **PARTS** specify the components (i.e., other gates) that implement the chip

```
/**  
 * And gate:  
 * out = 1 only if both a and b are 1  
 */  
CHIP And {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
    // Put your code here:  
}
```

Reusing Components

- ❖ You can (and should!) use chips you have already implemented to implement subsequent chips
- ❖ We give you one gate, **Nand**, to start out with
 - Implication: The entire computer you will be building will be use **Nand** gates as its foundation
- ❖ We also provide you with some chips you can use without implementing

HDL Component Example: AND

- ❖ The chip specification tells us the name of the input and output wires


```
CHIP And {  
    IN a, b;  
    OUT out;  
  
    ...  
}
```

- ❖ Goal: Implement $w1$ AND $w2$

- HDL Syntax for using (being a client of the **And** gate):

And(a=w1, b=w2, out=w3);

- Equivalent circuit diagram:

 

Multi-bit Buses in HDL

- ❖ It can be useful to manipulate groups of wires
 - Called a “bus” of wires
- ❖ HDL provides array like syntax for manipulating buses
 - **And4** chip example:

```
/**
 * Bit-wise And of two 4-bit inputs
 */
CHIP And4 {
    IN a[4], b[4];
    OUT out[4];

    PARTS:
    And (a=a[0], b=b[0], out=out[0]);
    And (a=a[1], b=b[1], out=out[1]);
    And (a=a[2], b=b[2], out=out[2]);
    And (a=a[3], b=b[3], out=out[3]);
}
```

HDL Resources

- ❖ HDL will feel unfamiliar at first, and that's okay
- ❖ Resources for helping you navigate HDL linked under the [Resources page](#) on the course website
 - HDL Survival guide
 - Appendix A (HDL Spec)
 - Chip Set Overview (to help you remember the inputs/outputs for various chips)
 - Chapter readings

Lecture Outline

- ❖ Study Environment Discussion
- ❖ Boolean Logic and Functions
 - Boolean Expressions, Circuit Diagrams, Truth Tables
 - Boolean Function Synthesis Strategy
- ❖ Hardware Descriptive Languages (HDL)
 - HDL Syntax, **And** Gate Example
- ❖ **Foundational Logic Gates**
 - **Nand, Not, And, Or, Xor, Mux, DMux Gates**
 - **Example of Implementing an Xor Gate in HDL**

The Foundational Building Block

- ❖ It all starts with the NAND gate
- ❖ NAND is short for “Not And”
 - The same output as the AND gate, but every output bit is negated (flipped)

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F = A \text{ AND } B$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

$$F = A \text{ NAND } B$$

Building Gates From Nand

- ❖ Recall the **Boolean Function Synthesis** strategy from today's reading
 - We saw how we can represent any truth table in terms of three gates: **Not**, **And**, **Or**
- ❖ First, we can represent **Not** directly from **Nand**
 - $\text{Not } a = a \text{ Nand } a$
- ❖ Then, we can represent **And** in terms of **Not** and **Nand**
 - $a \text{ And } b = \text{Not}(a \text{ Nand } b)$
- ❖ Represent **Or** in terms of **Not** and **And**
 - Apply De Morgan's Law
 - $a \text{ Or } b = \text{Not}(\text{Not}(a) \text{ And } \text{Not}(b))$ [De Morgan's Law]

Making Decisions in Hardware


- ❖ We write if/else statements in Java with the understanding that *only one* of the branches will run
 - For example, in the following code, we expect to compute one of $a \& b$ or $a \mid b$ (not both)

```
if (c == 0) {  
    out = a & b;  
} else {  
    out = a | b;  
}
```
- ❖ In hardware, the entire circuit is always executing
 - We can't "turn off" a part of a circuit based on a condition
 - Instead, we create circuits for different conditions and choose which output based on a condition instead

Decisions in Hardware: Mux Gate

❖ We can use a **Multiplexer (Mux)** gate to choose which singular input to output

 - Takes three inputs: a , b , and sel
- If $sel == 0$, then $out = a$
- Otherwise, $out = b$




❖ Mux Gate Truth Table:

a	b	sel	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Decisions in Hardware: DMux Gate

❖ A **Demultiplexer (DMux)** gate passes one input to one of two outputs and 0 to the rest

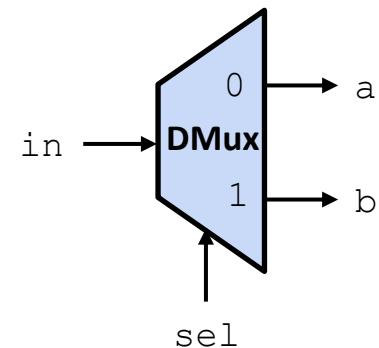- Takes two inputs: `in` and `sel`
- If `sel == 0`, then `a = in` and `b = 0`
- Otherwise, `a = 0` and `b = in`



❖ DMux Gate Truth Table:

in	sel	a	b
0	0	0	0
0	1	0	0
1	0	1	0
1	1	0	1

Implementing an Xor Gate: Overview

- ❖ Let's walk through an example of building a gate that you will work on in Project 2, the **Xor** gate
- ❖ Together, we'll implement the **Xor** gate

```
/**
 * Xor gate:
 * out = not(a == b)
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Implementing an Xor Gate: Overview

❖ Plan of action:

- Step 1: Create the logic operation's **truth table**
- Step 2: Use truth table to generate a **Boolean function** using strategies we've learned, such as the Boolean Function Synthesis
- Step 3: Convert Boolean function to **HDL**

```
/**
 * Xor gate:
 * out = not(a == b)
 */
CHIP Xor {
    IN a, b;
    OUT out;

    PARTS:
    // Put your code here:
}
```

Implementing an Xor Gate: Step 1

- ❖ Step 1: Create the truth table for Xor
 - Interpret the specification: $F = \text{NOT}(A == B)$

A	B	F
0	0	
0	1	
1	0	
1	1	

$$F = A \text{ XOR } B$$

Implementing an Xor Gate: Step 1

- ❖ Step 1: Create the truth table for Xor
 - Interpret the specification: $F = \text{NOT}(A == B)$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

$$F = A \text{ XOR } B$$

Implementing an Xor Gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading
 - **Row 2 = NOT(A) AND B**

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Implementing an Xor Gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading
 - Row 2 = NOT(A) AND B
 - **Row 3 = A AND NOT(B)**

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Implementing an Xor Gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the **Boolean Function Synthesis** strategy from the reading
 - Row 2 = NOT(A) AND B
 - Row 3 = A AND NOT(B)
 - $F = ?$

A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

[← Lecture 2: Study Environment & Boolean Logic](#)

Respond at PollEv.com/cse390b

What is the expression from using Boolean function synthesis on $F = A \text{ XOR } B$?

(A AND NOT(B)) AND (NOT(A) AND B)

(NOT(A) AND B) AND (A AND B)

(A AND B) OR (NOT(A) AND NOT(B))

(NOT(A) AND B) OR (A AND NOT(B))

We're lost...

Total Results: 0

Powered by  Poll Everywhere



Implementing an Xor gate: Step 2

- ❖ Step 2: Use truth table to generate a Boolean function
 - Let's use the Boolean function synthesis strategy from the reading
 - Row 2 = NOT(A) AND B
 - Row 3 = A AND NOT(B)
 - $F = \text{Row 2 OR Row 3}$
 $= (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND NOT}(B))$


A	B	F	
0	0	0	(Row 1)
0	1	1	(Row 2)
1	0	1	(Row 3)
1	1	0	(Row 4)

$$F = A \text{ XOR } B$$

Implementing an Xor gate: Step 3

- ❖ Now that we have a Boolean expression, we can implement the **Xor** gate in HDL
- ❖ Optionally, it can help to express the Boolean expression as a circuit diagram

 
$$A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$$



Implementing an Xor gate: Step 3

- ❖ Step 3: Convert Boolean function to HDL syntax
 - $A \text{ XOR } B = (\text{NOT}(A) \text{ AND } B) \text{ OR } (A \text{ AND } \text{NOT}(B))$
 - Assumes **Not**, **And**, and **Or** are already implemented
 - Note the use of intermediary wires: **nota**, **notb**, **x**, and **y**
 
```
CHIP Xor {  
  IN a, b;  
  OUT out;  
  
  PARTS:  
  Not (in=a, out=nota);  
  Not (in=b, out=notb);  
  And (a=a, b=notb, out=x);  
  And (a=nota, b=b, out=y);  
  Or (a=x, b=y, out=out);  
}
```



Project 2 Overview

- ❖ Metacognitive Component: **Study Skills Inventory**
 - Reflect on your academic behaviors, strategies, and practices
 - You will be graded on completing the form, not your responses
 - This activity is for your own benefit, and the more honest you are, the more beneficial it will be
- ❖ Technical Component: **GitLab Setup**
 - Will help prepare you for future CSE 390B projects
- ❖ Estimated time to complete: 6-8 hours
- ❖ **Project 2 is released and will be due next Thursday (1/12) at 11:59pm**

Post-Lecture 2 Reminders

- ❖ **Project 1 due tonight (1/5) at 11:59pm**
- ❖ Project 2 (Study Skills Inventory & Boolean Logic) released today, due next Thursday (1/12) at 11:59pm
- ❖ Eric has office hours after class in CSE2 153
- ❖ First Student-TA meetings starting next week
 - Your TA will be in contact with you about the first meeting